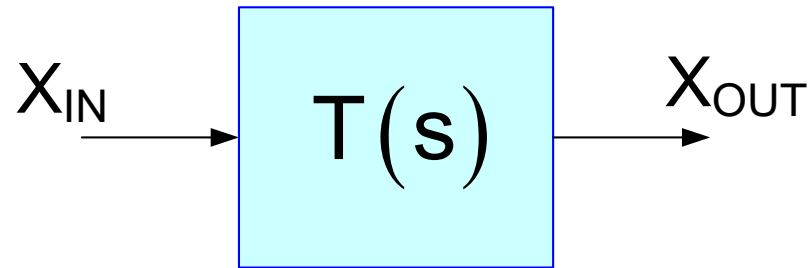


EE 508

Lecture 18

Comparison of Filter Structures
Sensitivity Functions

Consider 2nd Order Lowpass Biquads



$$|T(s)| = H \frac{\omega_0^2}{s^2 + s \left(\frac{\omega_0}{Q} \right) + \omega_0^2}$$



$$BW = \omega_B - \omega_A \neq \frac{\omega_0}{Q}$$

$$\omega_{PEAK} \neq \omega_0$$



Consider 2nd Order Lowpass Biquads

$$|T(s)| = H \frac{\omega_0^2}{s^2 + s\left(\frac{\omega_0}{Q}\right) + \omega_0^2}$$

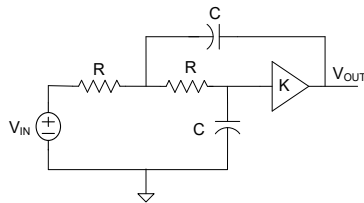
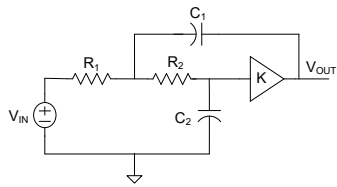
Four basic structures that ideally implement the same transfer function





Sallen and Key +KRC

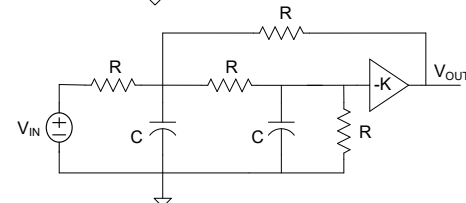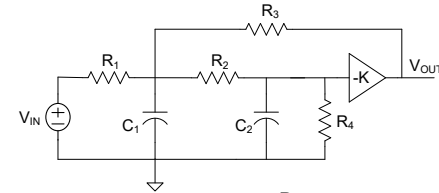

Sallen and Key -KRC

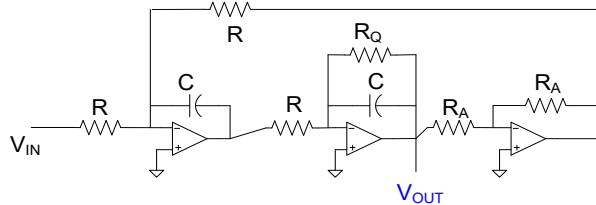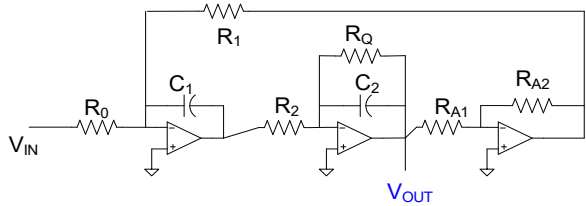


Two Integrator Loop

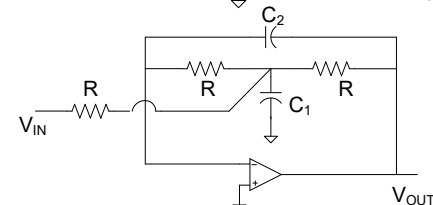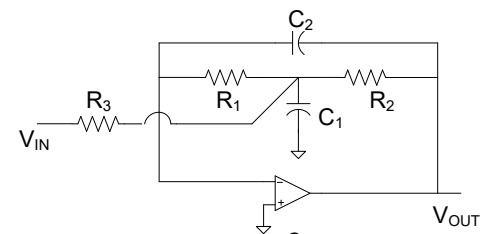


Bridged-T Feedback

Consider 2nd Order Lowpass Biquads

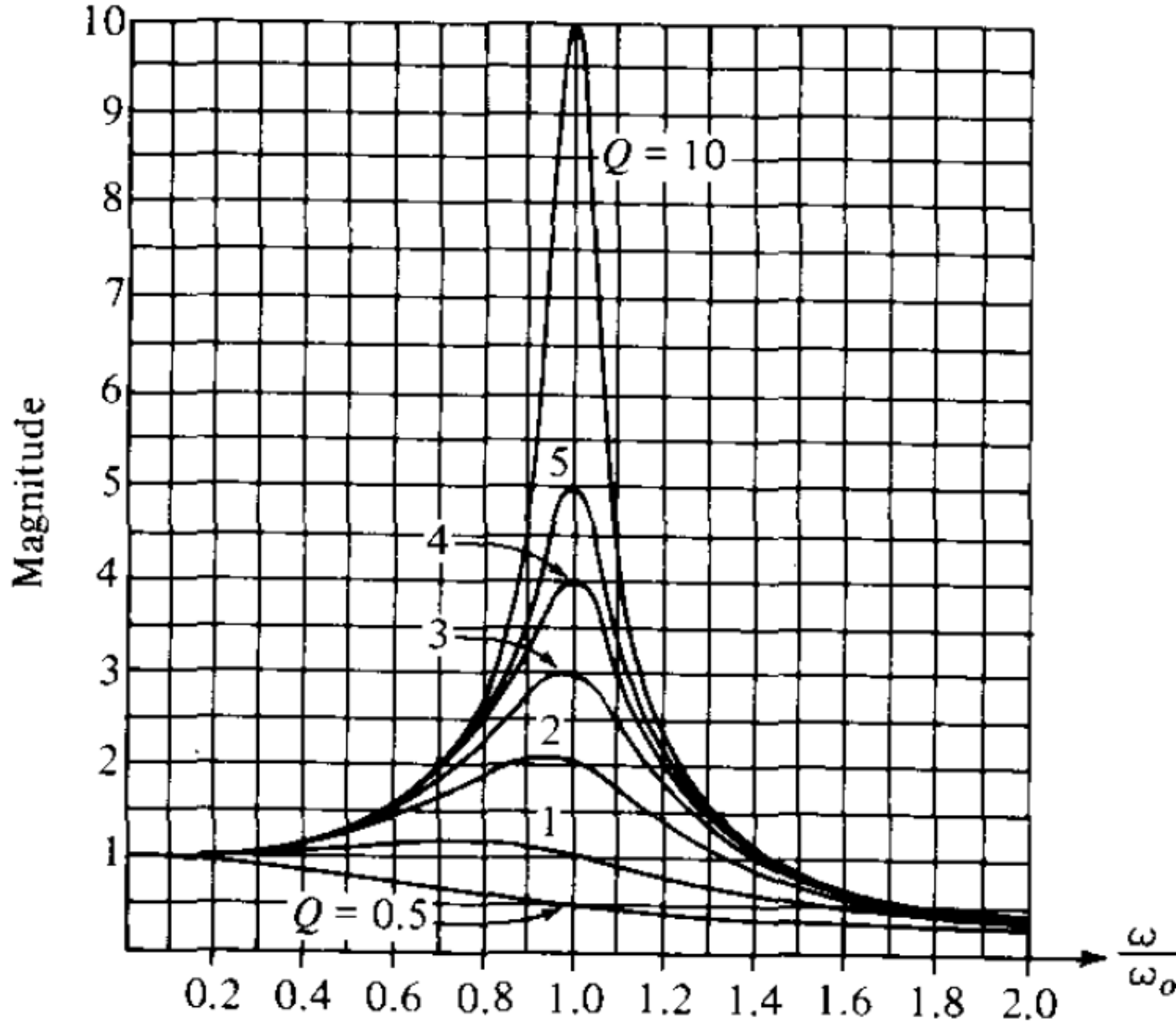


Example: 2nd Order +KRC Lowpass

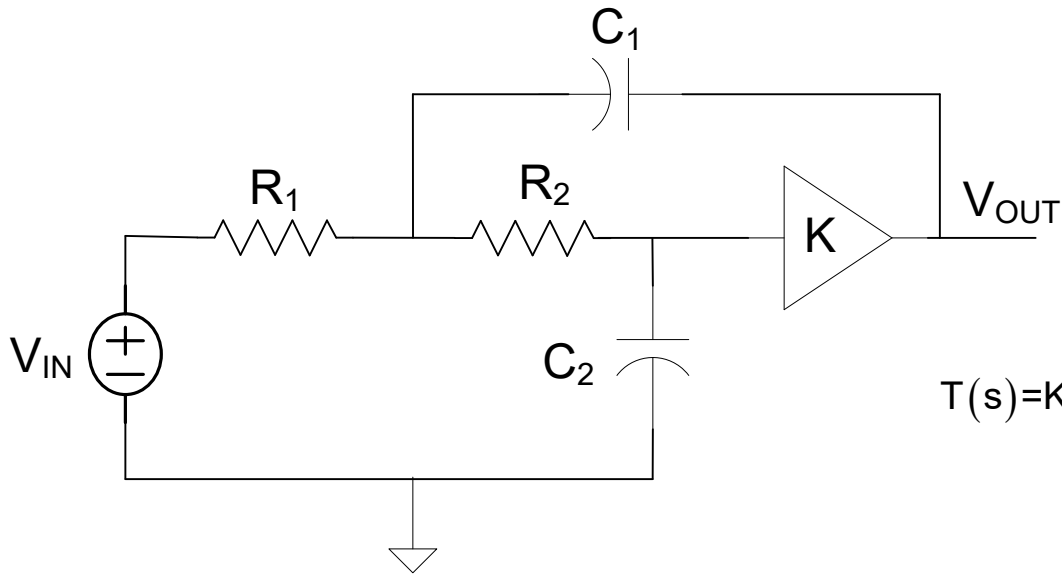

$$T(s) = K \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + s \left[\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$

Equal R, Equal C

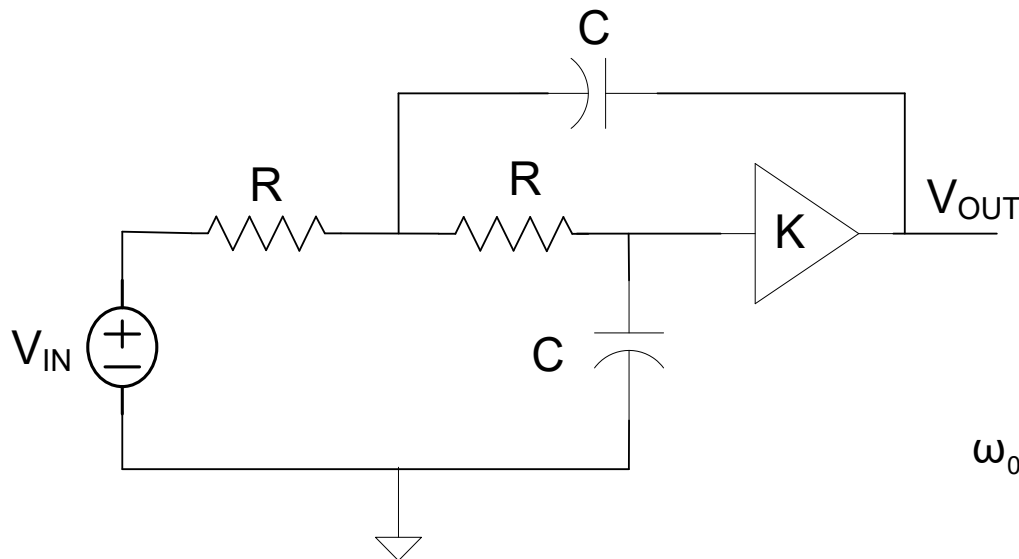


$$T(s) = K \frac{\frac{1}{R^2 C^2}}{s^2 + s \left[\frac{(3-K)}{RC} \right] + \frac{1}{R^2 C^2}}$$

$$\omega_0 = \frac{1}{RC}$$

$$Q = \frac{1}{3-K}$$

Example: 2nd Order +KRC Lowpass



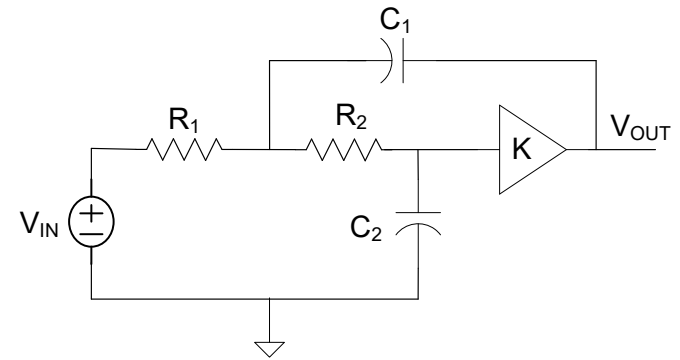


Equal R, K=1

$$T(s) = K \frac{1}{R^2 C_1 C_2} \frac{1}{s^2 + s \left[\frac{2}{RC_1} \right] + \frac{1}{R^2 C_1 C_2}}$$

$$\omega_0 = \frac{1}{R \sqrt{C_1 C_2}}$$

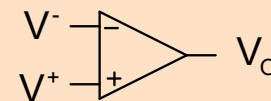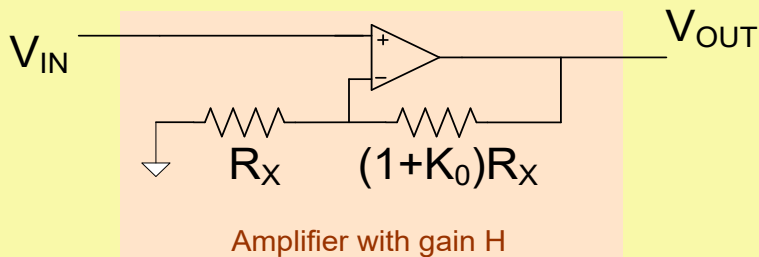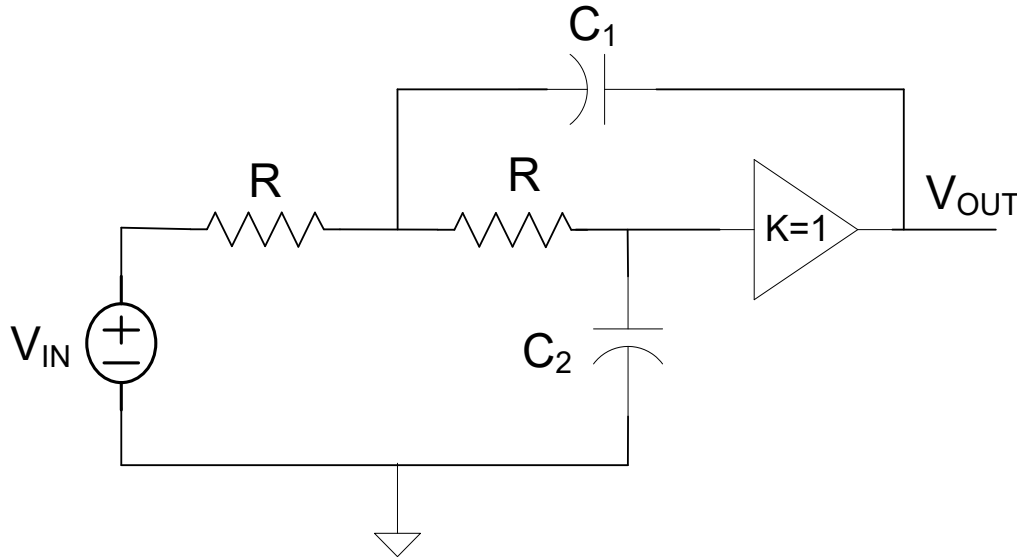
$$Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}}$$



$$A(s) = \frac{V_O}{V^+ - V^-} = \frac{GB}{s}$$

$$K(s) = \frac{K_0}{1 + \frac{K_0}{GB} s}$$


Example: 2nd Order +KRC Lowpass

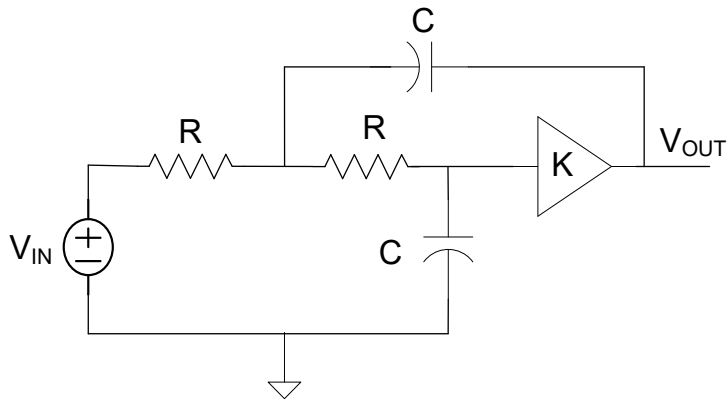



Equal R, Equal C

consider

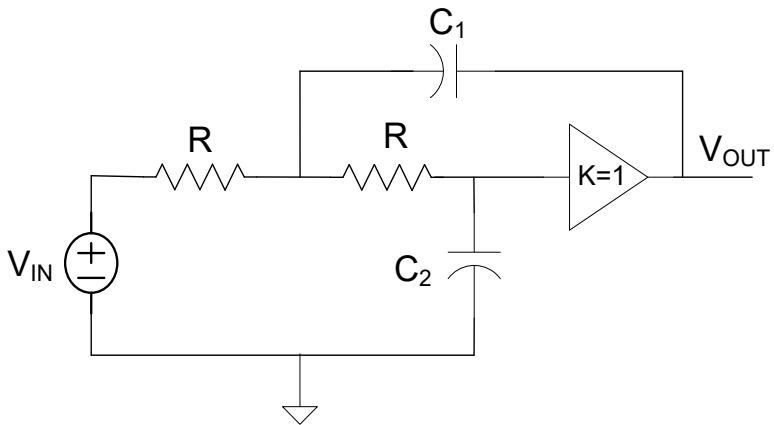
$$\bullet \longleftrightarrow GB_n = \frac{GB}{\omega_0} = 100$$




Equal R, K=1

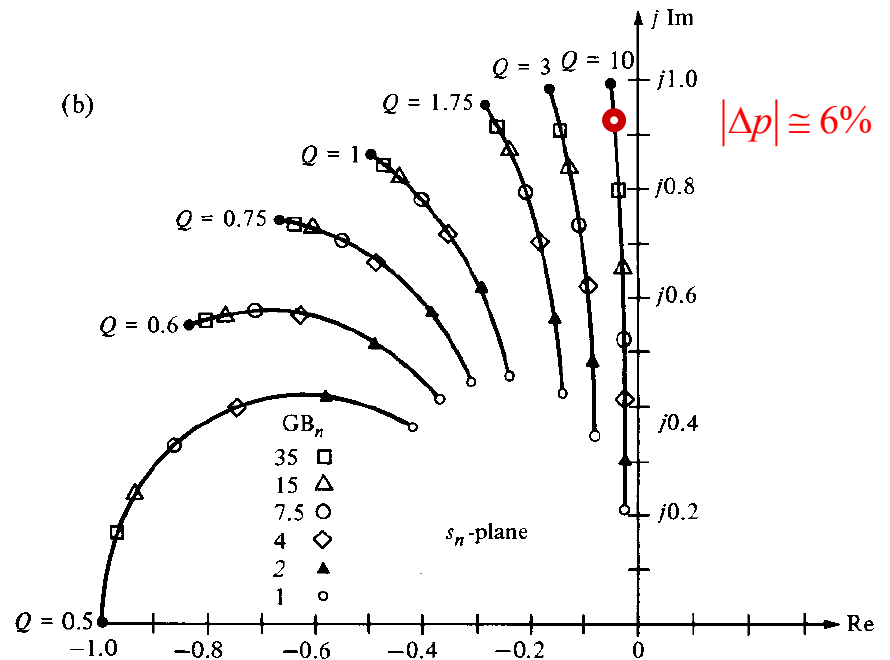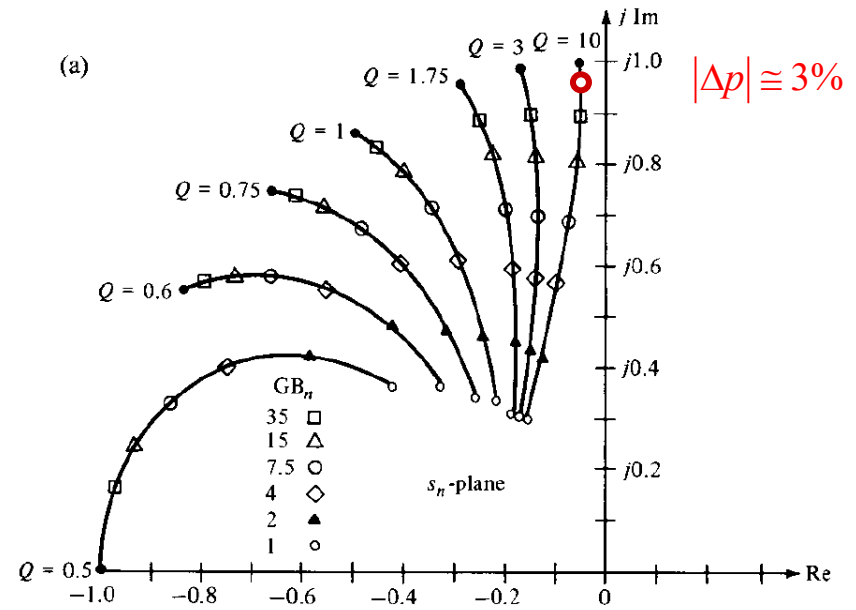

Example: 2nd Order -KRC Lowpass

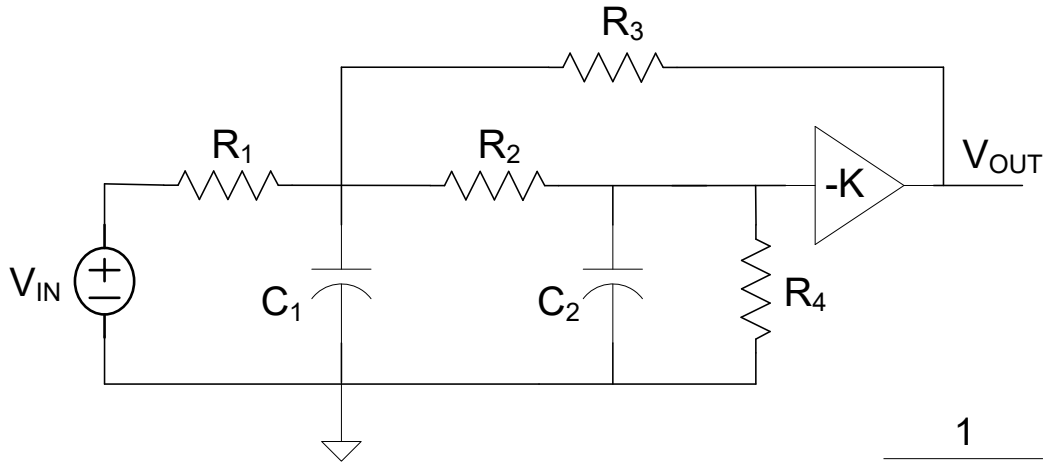
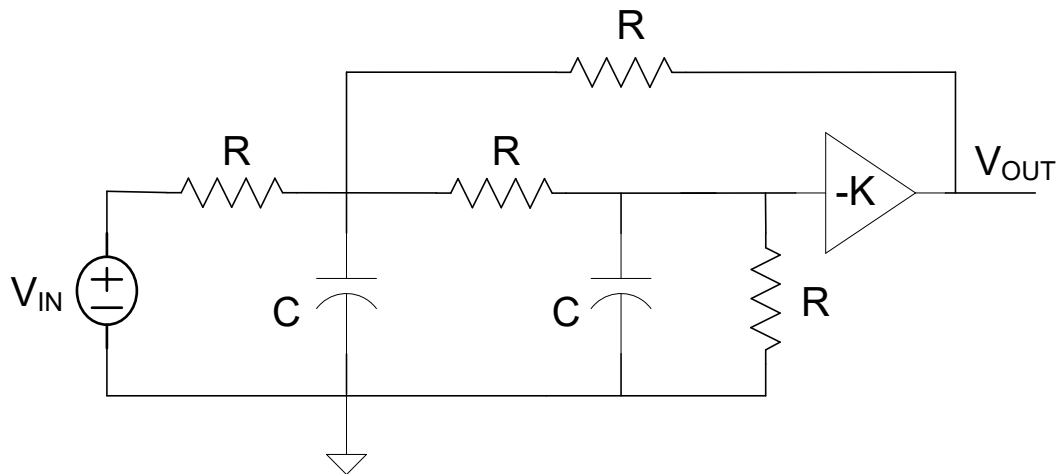
$$T(s) = -K \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{s^2 + s \left[\frac{1}{R_1 C_1} \left(1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left(1 + \frac{C_2}{C_1} \right) \right] + \left[\frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2} \right]}$$




Equal R, Equal C

$$T(s) = -K \frac{1}{R^2 C^2} \frac{1}{s^2 + s \left[\frac{5}{RC} \right] + \left[\frac{5+K}{R^2 C^2} \right]}$$



$$\omega_0 = \frac{\sqrt{5+K}}{RC}$$

$$Q = \frac{\sqrt{5+K}}{5}$$

Example: 2nd Order -KRC Lowpass

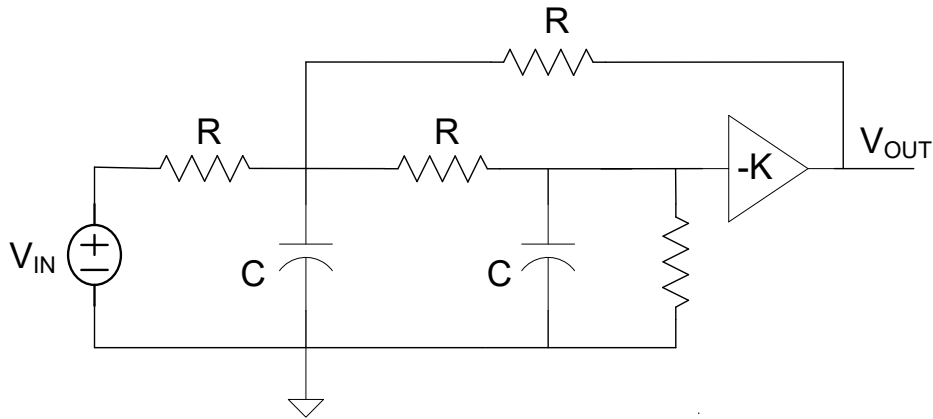

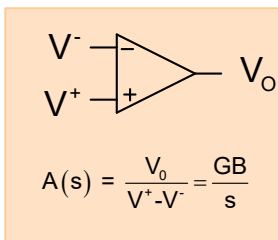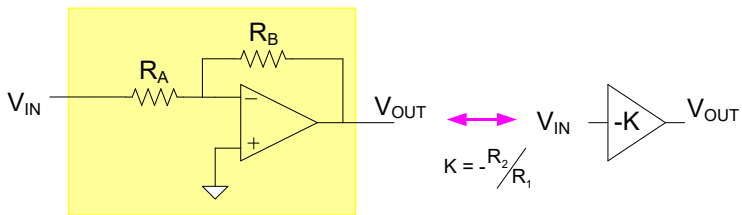
$$\omega_0 = \frac{\sqrt{5+K}}{RC} \quad Q = \frac{\sqrt{5+K}}{5}$$




$$K(s) = -\frac{K_0}{1 + \frac{(1+K_0)s}{GB}}$$

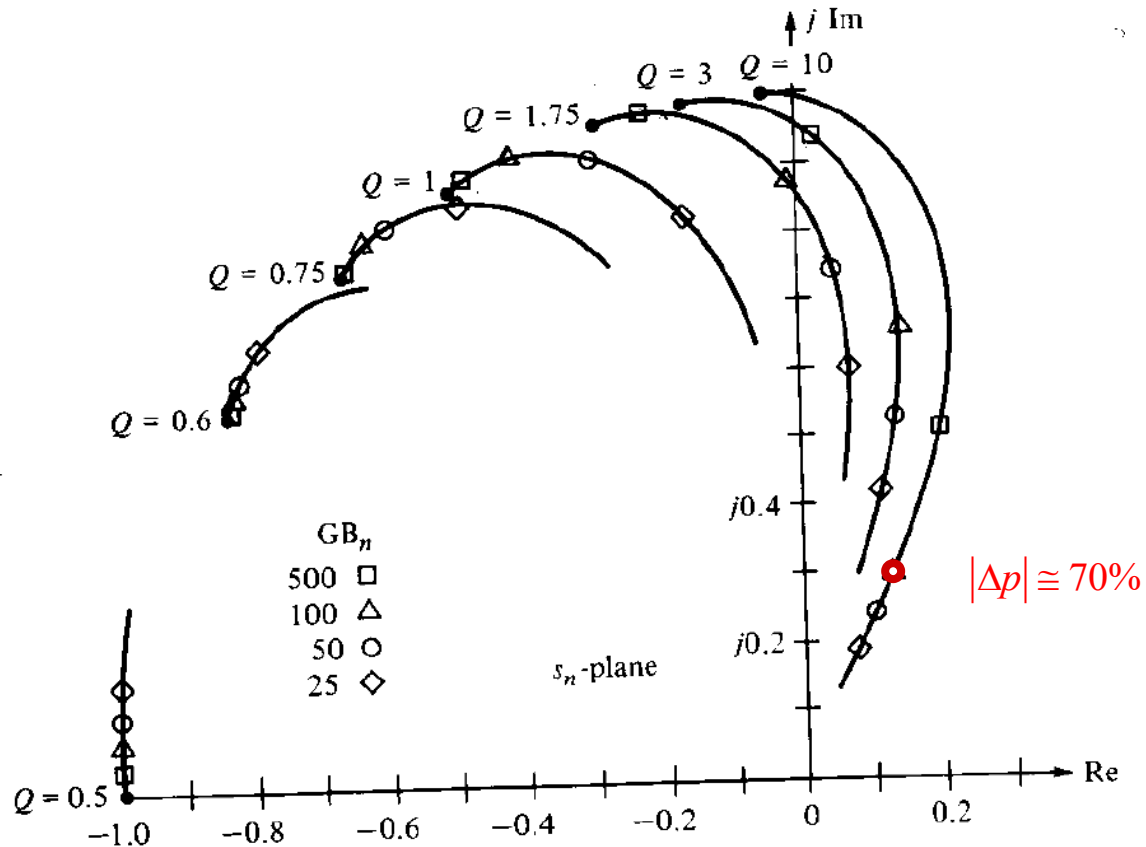consider $\bullet \longleftrightarrow GB_n = \frac{GB}{\omega_0} = 100$




Poles “move” towards RHP as GB degrades
Even very large values of GB will cause instability

Example: 2nd Bridged-T FB Lowpass

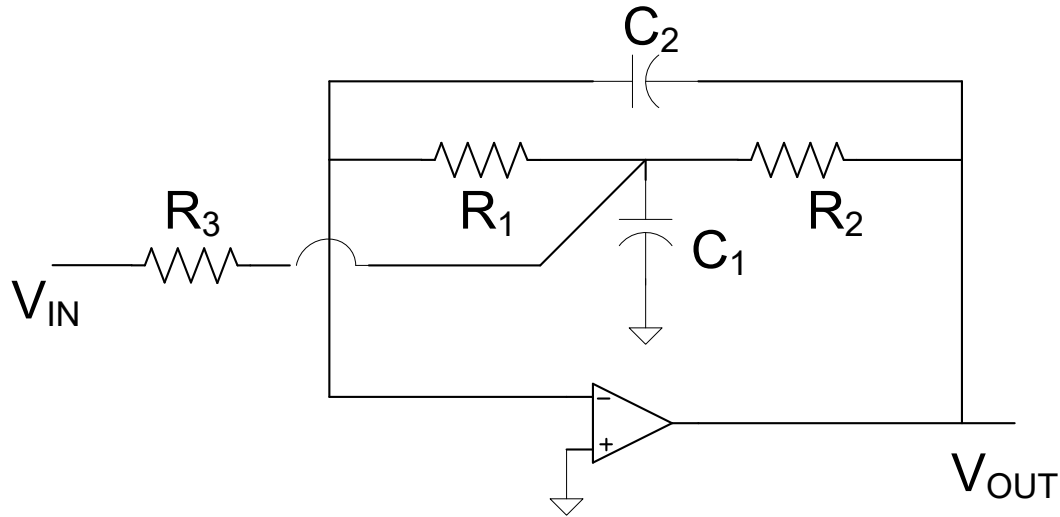
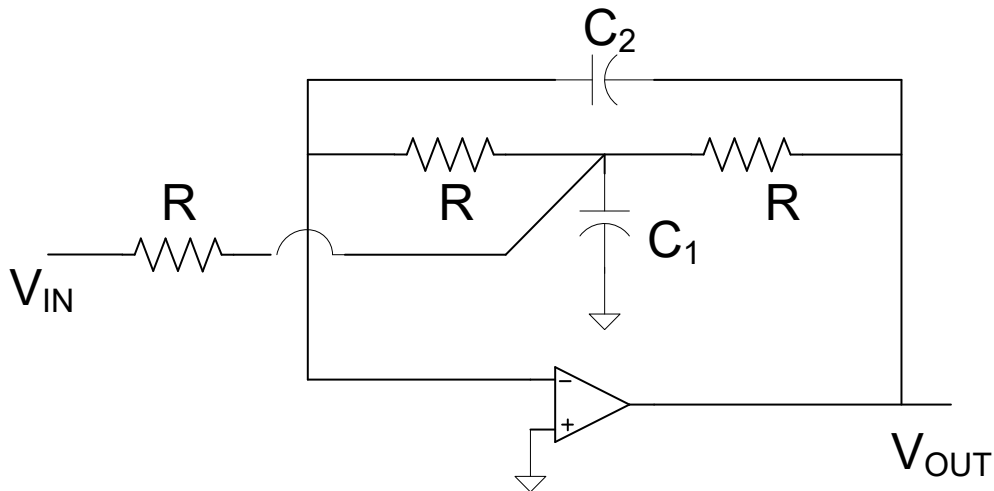
$$T(s) = - \frac{1}{R_2 R_3 C_1 C_2} \frac{1}{s^2 + s \frac{1}{C_1} \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$




Equal R

$$T(s) = - \frac{1}{R^2 C_1 C_2} \frac{1}{s^2 + s \left(\frac{3}{RC_1} \right) + \frac{1}{R^2 C_1 C_2}}$$

$$\omega_0 = \frac{1}{R \sqrt{C_1 C_2}} \quad Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}}$$



Example: 2nd Bridged-T FB Lowpass

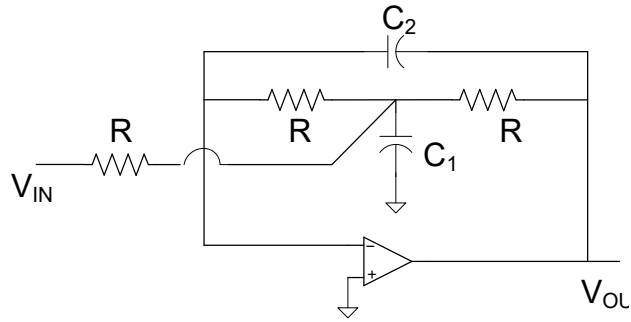


$$\omega_0 = \frac{1}{R\sqrt{C_1 C_2}} \quad Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}}$$

consider

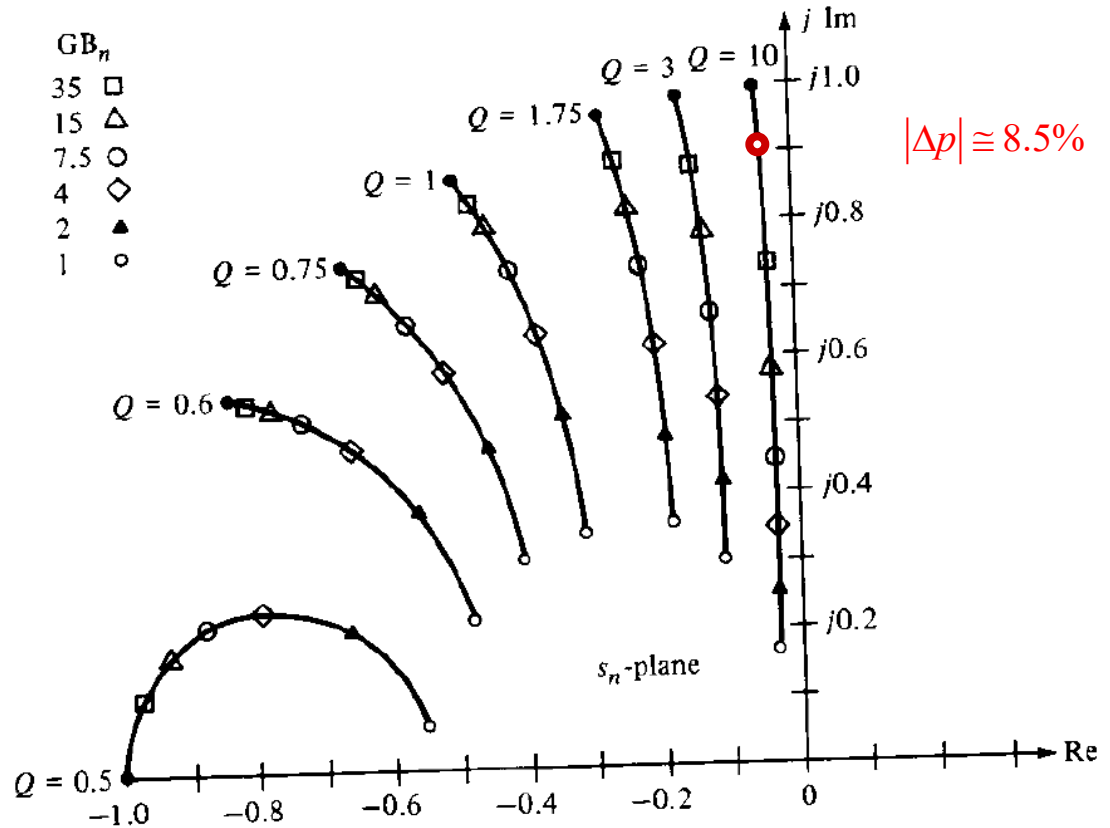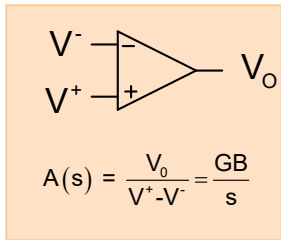
$$\bullet \longleftrightarrow GB_n = \frac{GB}{\omega_0} = 100$$



Example: 2nd Two-Integrator-Loop Lowpass

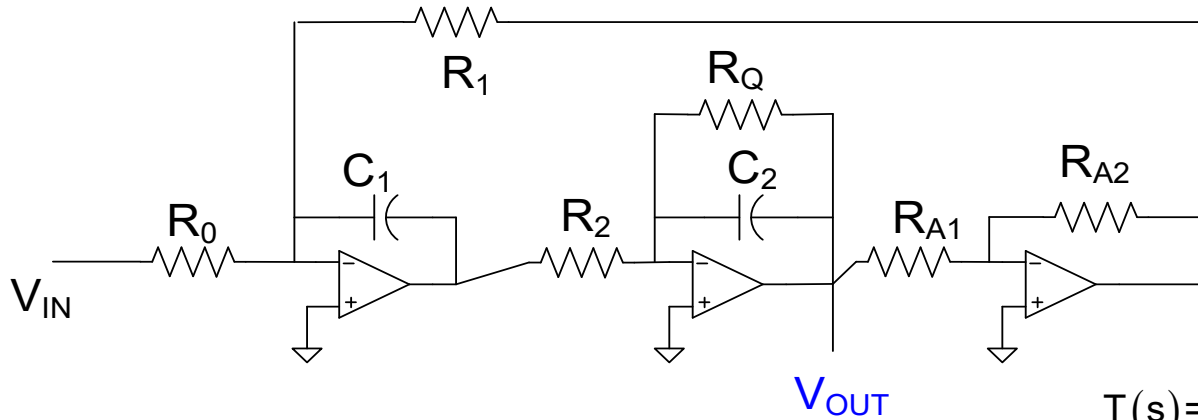
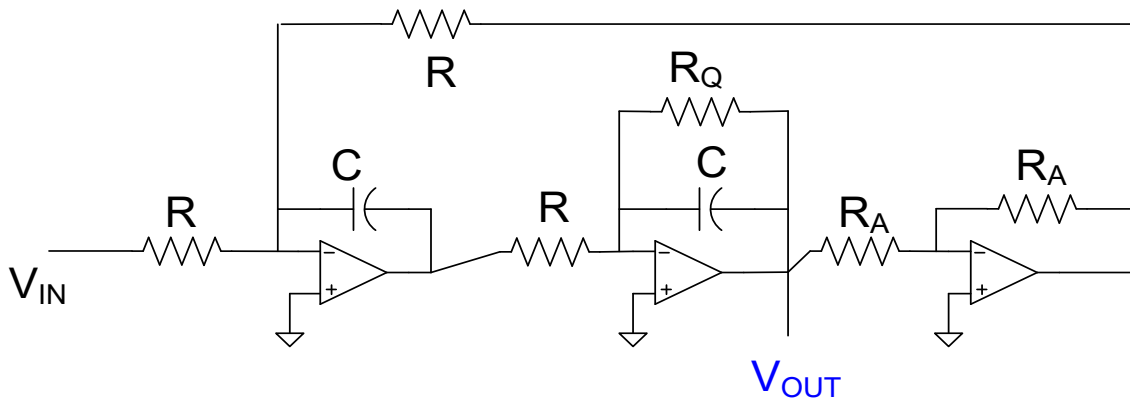
$$T(s) = - \frac{1}{R_0 R_2 C_1 C_2} \frac{1}{s^2 + s \left(\frac{1}{C_2 R_Q} \right) + \frac{R_{A2}/R_{A1}}{R_1 R_2 C_1 C_2}}$$




Equal R, Equal C
(except R_Q)

$$T(s) = - \frac{1}{R^2 C^2} \frac{1}{s^2 + s \left(\frac{1}{C R_Q} \right) + \frac{1}{R^2 C^2}}$$



$$\omega_0 = \frac{1}{RC} \quad Q = \frac{R_Q}{R}$$

Example: 2nd Two-Integrator-Loop Lowpass

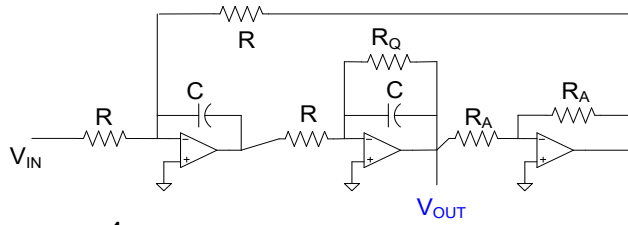








$$\omega_0 = \frac{1}{RC} \quad Q = \frac{R_Q}{R}$$

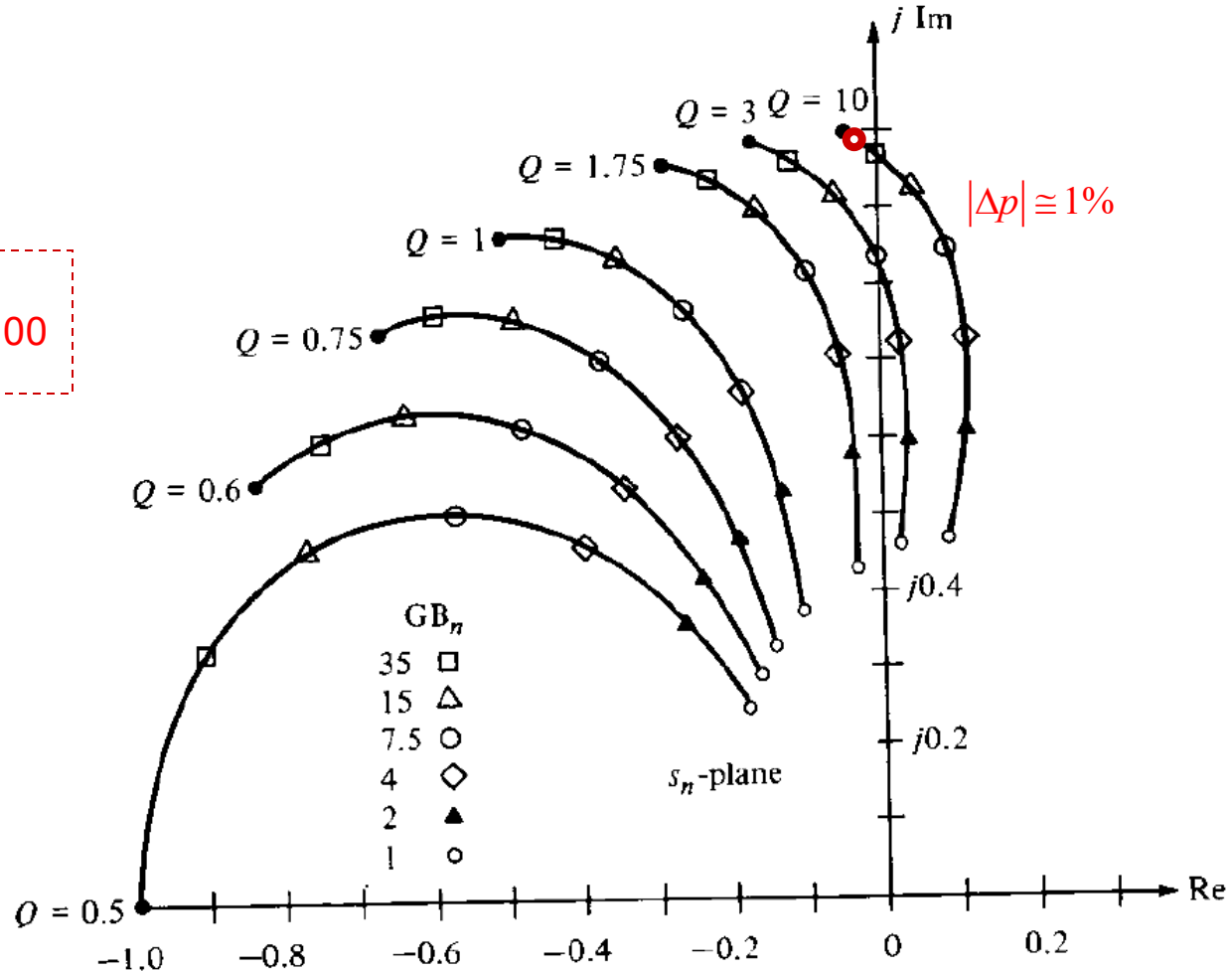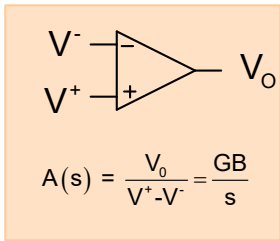consider $\bullet \longleftrightarrow GB_n = \frac{GB}{\omega_0} = 100$




Poles "move" towards RHP as GB degrades

Comparison of 4 second-order LP filters

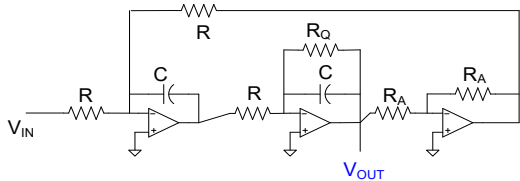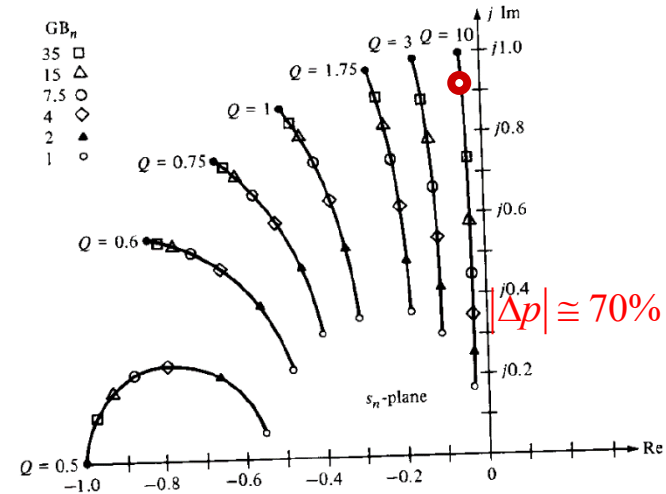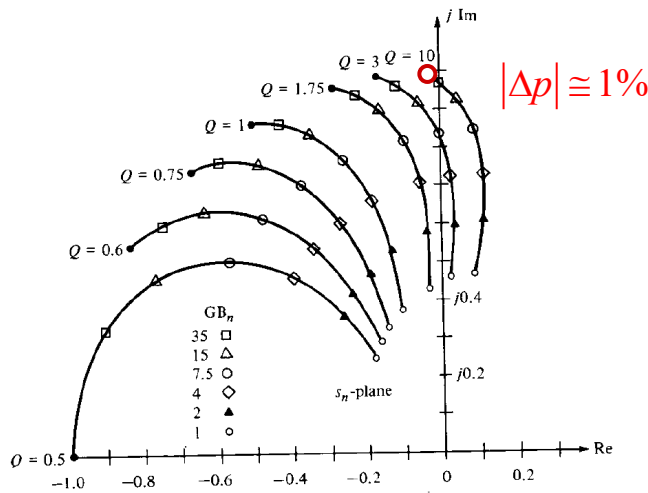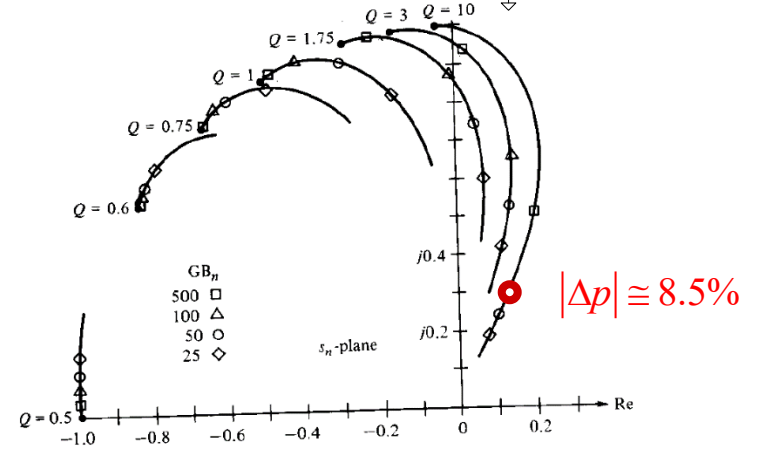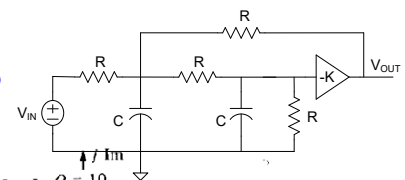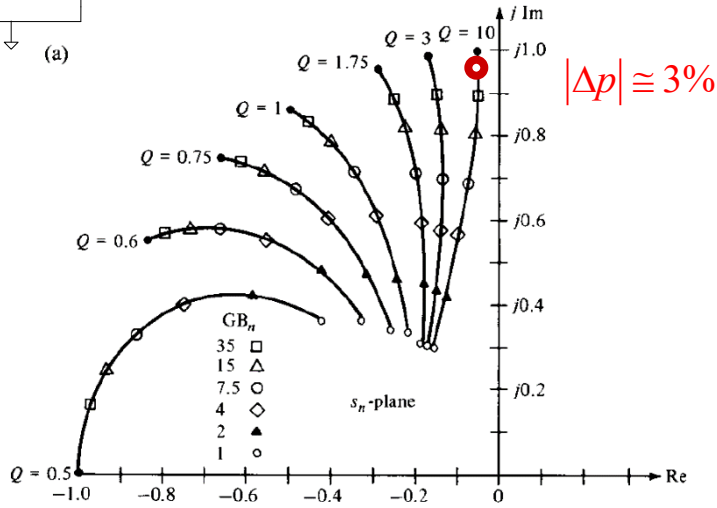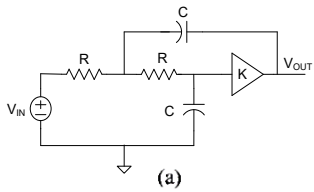

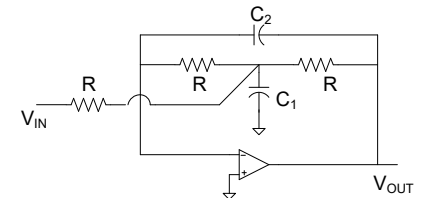consider $\bullet \longleftrightarrow GB_n = \frac{GB}{\omega_0} = .01$




Some Observations


- Seemingly similar structures have dramatically different sensitivity to frequency response of the Op Amp
- Critical to have enough GB if filter is to perform as desired
- Performance strongly affected by both magnitude and direction of pole movement
- Some structures appear to be totally impractical – at least for larger Q
- Different use of the Degrees of Freedom produces significantly different results

Sensitivity analysis is useful for analytical characterization of the performance of a filter

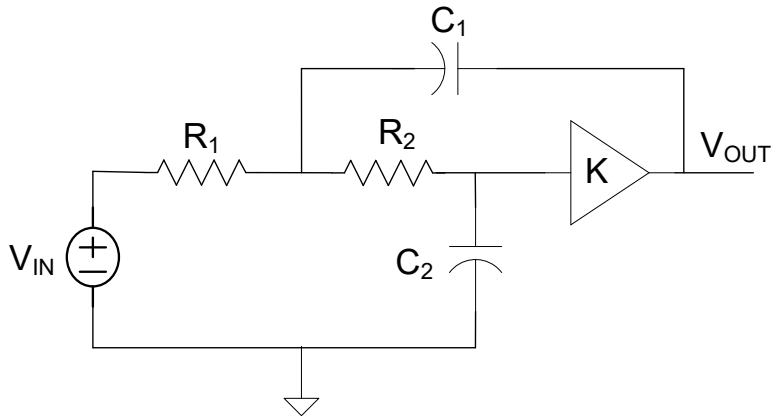
What causes the dramatic differences in performance between these two structures?
 How can the performance of different structures be compared in general?



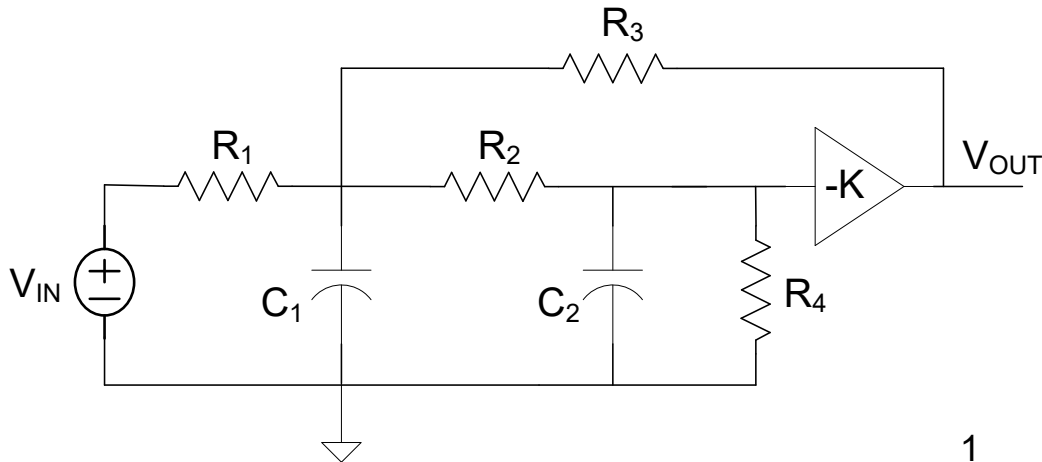
$$T(s) = K \frac{1}{s^2 + s \left[\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$




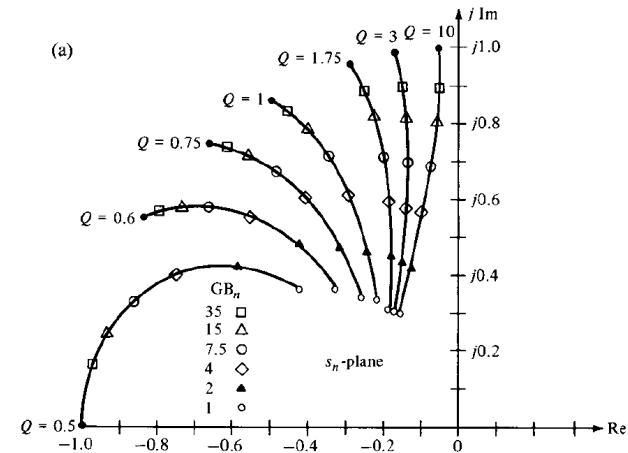
$$T(s) = -K \frac{1}{s^2 + s \left[\frac{1}{R_1 C_1} \left(1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left(1 + \frac{C_2}{C_1} \right) \right] + \left[\frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2} \right]}$$



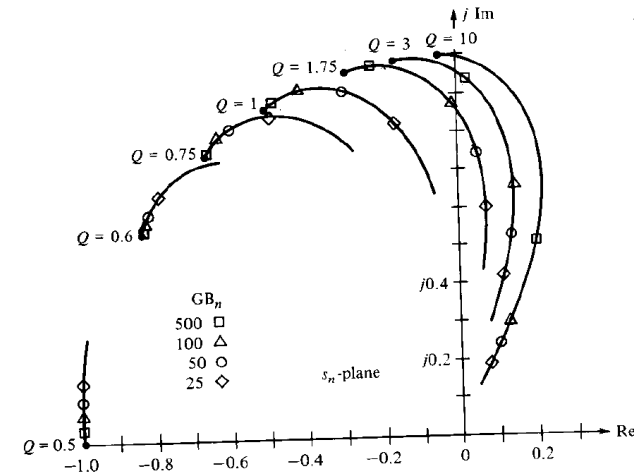Equal R, Equal C, Q=10 Pole Locus vs GB_N



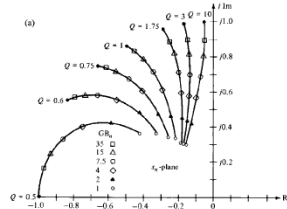
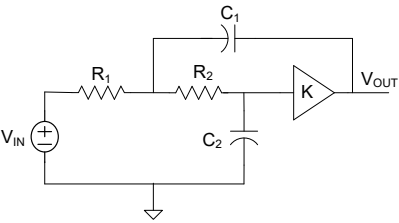
How can the performance of different structures be compared in general?



$$T(s) = K \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{s^2 + s \left[\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$Q = \frac{1}{\sqrt{\frac{R_2 C_2}{R_1 C_1}} + \sqrt{\frac{R_1 C_2}{R_2 C_1}} + (1-K) \sqrt{\frac{R_1 C_1}{R_2 C_2}}}$$
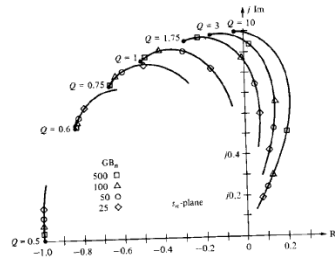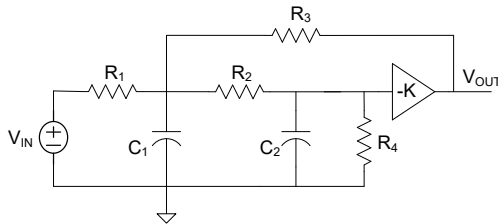
$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$



$$T(s) = -K \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{s^2 + s \left[\frac{1}{R_1 C_1} \left(1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left(1 + \frac{C_2}{C_1} \right) \right] + \left[\frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2} \right]}$$



$$\omega_0 = \sqrt{\frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2}}$$

$$Q = \sqrt{\frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2} \frac{1}{\frac{1}{R_1 C_1} \left(1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left(1 + \frac{C_2}{C_1} \right)}}$$

- Equations for key performance parameters give little insight into the differences
- Expressions for key performance parameters quite complicated



How can the performance of different structures be compared in general?

Equal R, Equal C implementations

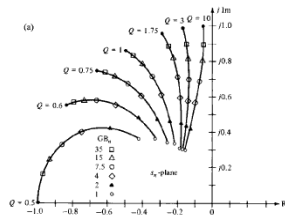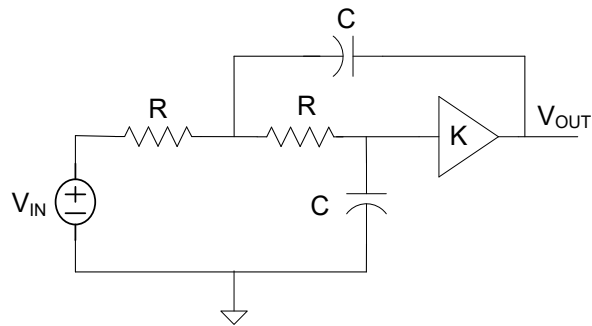

$$T(s) = K \frac{1}{s^2 + s \left[\frac{(3-K)}{RC} \right] + \frac{1}{R^2 C^2}}$$
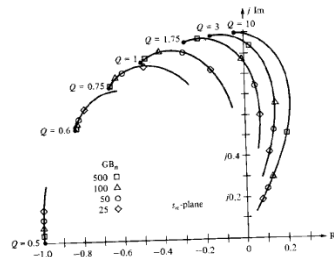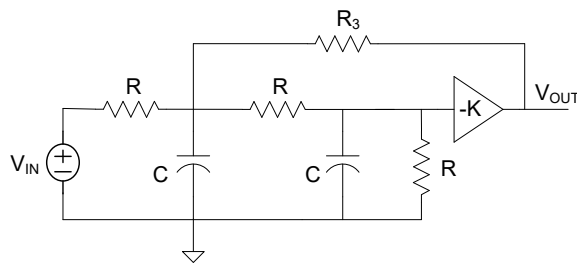
$$Q = \frac{1}{3-K} \quad \omega_0 = \frac{1}{RC}$$





$$T(s) = -K \frac{1}{s^2 + s \left[\frac{5}{RC} \right] + \left[\frac{5+K}{R^2 C^2} \right]}$$

$$Q = \frac{\sqrt{5+K}}{5} \quad \omega_0 = \frac{\sqrt{5+K}}{RC}$$


- Analytical expressions for ω_0 and Q much simpler
- Equations for key performance parameters give little insight into the differences
- Effects of individual components is obscured in these expressions
- GB effects absent in this analytical formulation !!!!

Modeling of the Amplifiers

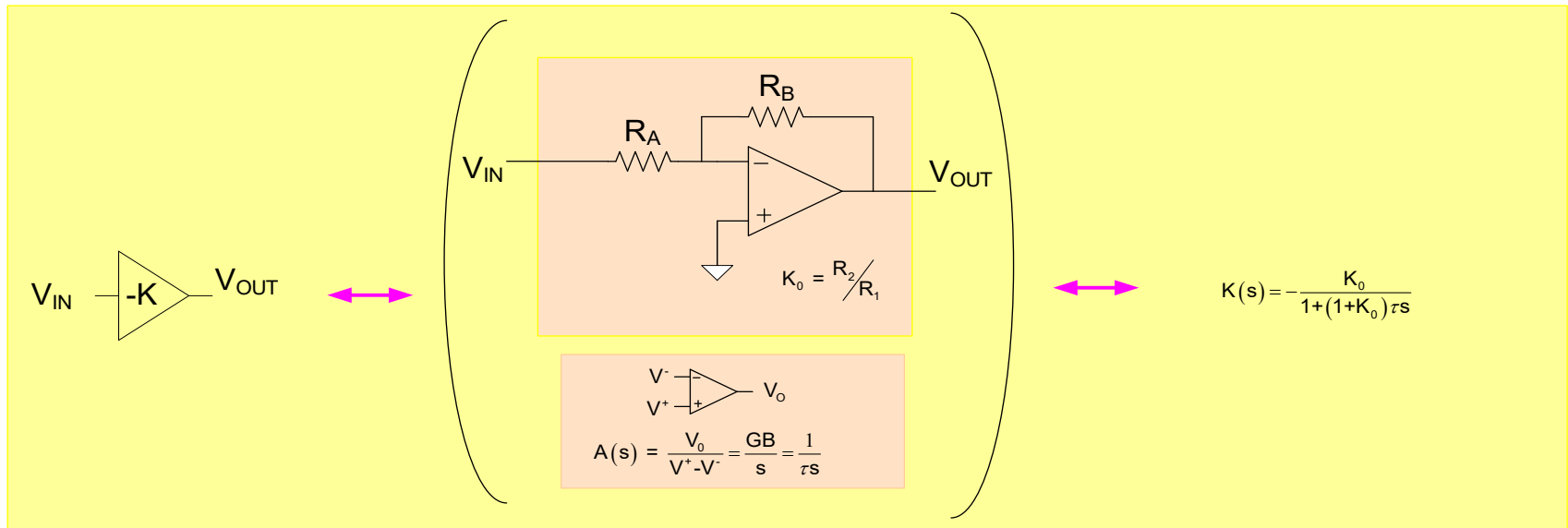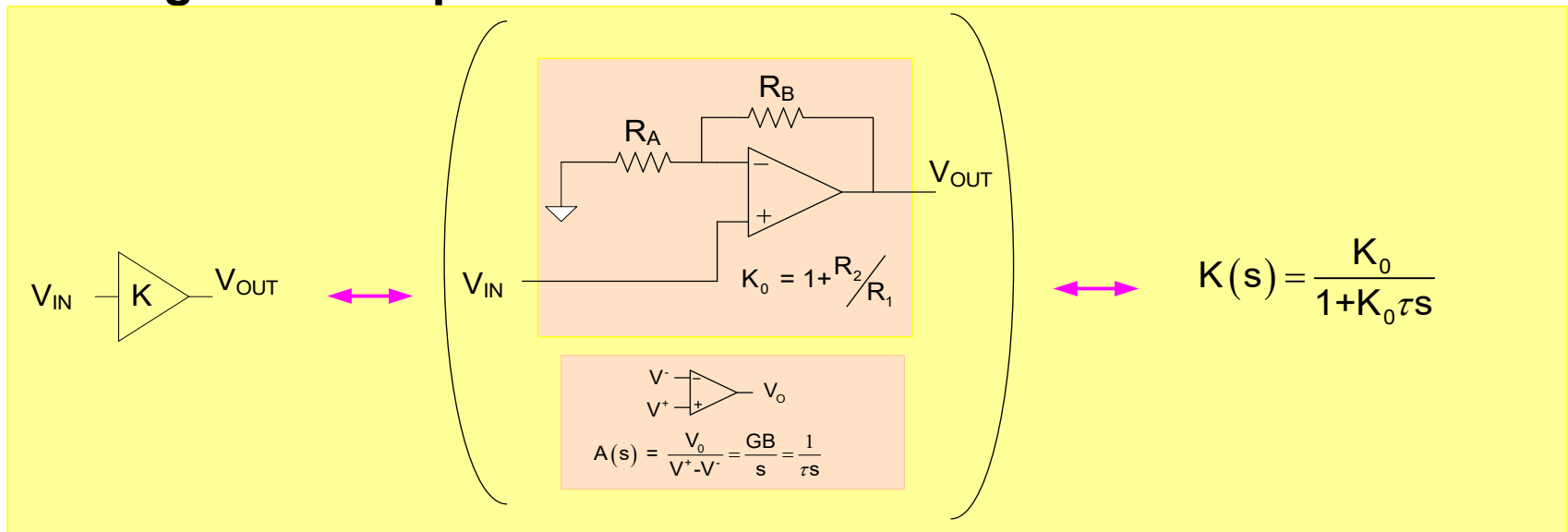

Different implementations of the amplifiers are possible
Have used the op amp time constant in these models $\tau = GB^{-1}$

GB effects in +KRC Lowpass Filter

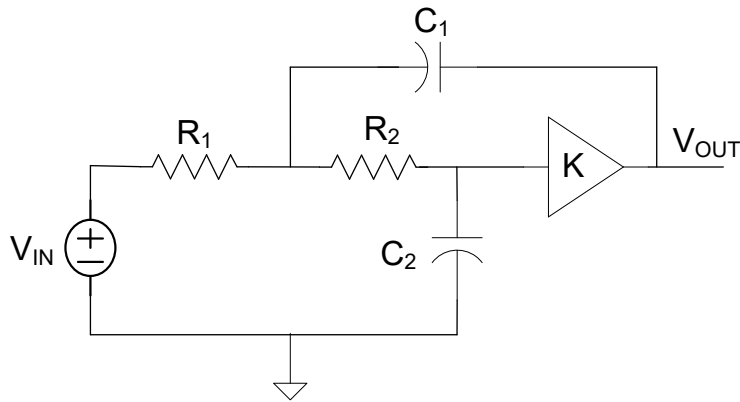

$$T(s) = K \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + s \left[\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$K(s) = \frac{K_0}{1 + K_0 \tau s}$$

$$T(s) = \frac{\frac{K_0}{R_1 R_2 C_1 C_2}}{s^2 + s \left[\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{(1-K_0)}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2} + K_0 \tau s \left(s^2 + s \left[\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2} \right)}$$

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \quad Q = \frac{1}{\sqrt{\frac{R_2 C_2}{R_1 C_1} + \frac{R_1 C_2}{R_2 C_1} + (1-K) \sqrt{\frac{R_1 C_1}{R_2 C_2}}}}$$

ω_0 and Q in these expressions are for ideal op amp

$$T(s) = \frac{K_0 \omega_0^2}{s^2 + s \left[\frac{\omega_0}{Q} \right] + \omega_0^2 + K_0 \tau s \left(s^2 + s \left[\frac{\omega_0}{Q} \left(1 + K_0 Q \sqrt{\frac{R_1 C_1}{R_2 C_2}} \right) \right] + \omega_0^2 \right)}$$

$$T(s) = \frac{\frac{K_0}{R_1 R_2 C_1 C_2}}{D_1(s) + K_0 \tau s (D_{RC0}(s))}$$


$D_1(s)$ is the $D(s)$ if the OA is ideal

$D_{RC0}(s)$ is the $D(s)$ of RC circuit with $K=0$

All linear performance effects can be obtained from this formulation

Op amp introduced an additional pole and moves the desired poles

GB effects in -KRC Lowpass Filter

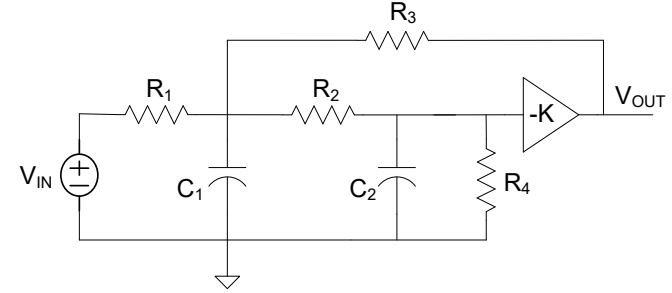

$$T(s) = -K \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{s^2 + s \left[\frac{1}{R_1 C_1} \left(1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left(1 + \frac{C_2}{C_1} \right) \right] + \left[\frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2} \right]}$$

$$K(s) = \frac{-K_0}{1 + (1+K_0)\tau s}$$

$$Q = \sqrt{\frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2} \frac{1}{\frac{1}{R_1 C_1} \left(1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left(1 + \frac{C_2}{C_1} \right)}}$$


$$\omega_0 = \sqrt{\frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2}}$$

ω_0 and Q in these expressions are for ideal op amp


$$T(s) = -K_0 \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{\left(s^2 + s \left[\frac{1}{R_1 C_1} \left(1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left(1 + \frac{C_2}{C_1} \right) \right] + \left[\frac{1 + (R_1/R_3)(1+K_0) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2} \right] \right)} + \tau s (1+K_0) \left(s^2 + s \left[\frac{1}{R_1 C_1} \left(1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left(1 + \frac{C_2}{C_1} \right) \right] + \left[\frac{1 + (R_1/R_3) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2} \right] \right)}$$

$$T(s) = \frac{-K_0}{D_1(s) + (1+K_0)\tau s(D_{RC0}(s))}$$

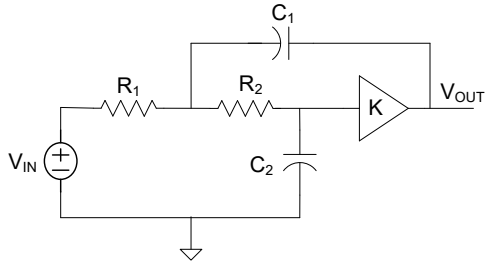GB effects in KRC and -KRC Lowpass Filter


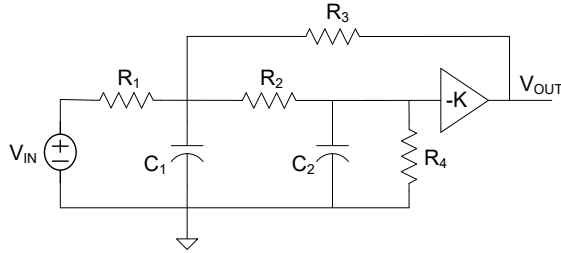
$$T(s) = \frac{K_0 \omega_0^2}{s^2 + s \left[\frac{\omega_0}{Q} \right] + \omega_0^2 + K_0 \tau s \left(s^2 + s \left[\frac{\omega_0}{Q} \left(1 + K_0 Q \sqrt{\frac{R_1 C_1}{R_2 C_2}} \right) \right] + \omega_0^2 \right)}$$



$$T(s) = \frac{K_0}{R_1 R_2 C_1 C_2} \frac{1}{D_I(s) + K_0 \tau s (D_{RC0}(s))}$$


$$T(s) = -K_0 \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{\left(s^2 + s \left[\frac{1}{R_1 C_1} \left(1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left(1 + \frac{C_2}{C_1} \right) \right] + \left[\frac{1 + (R_1/R_3)(1 + K_0) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2} \right] \right)} + \tau s (1 + K_0) \left(s^2 + s \left[\frac{1}{R_1 C_1} \left(1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left(1 + \frac{C_2}{C_1} \right) \right] + \left[\frac{1 + (R_1/R_3) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2} \right] \right)}$$

$$T(s) = \frac{-K_0}{R_1 R_2 C_1 C_2} \frac{1}{D_I(s) + (1 + K_0) \tau s (D_{RC0}(s))}$$

All linear performance effects can be obtained from this formulation

Op amp introduced an additional pole and moves the desired poles

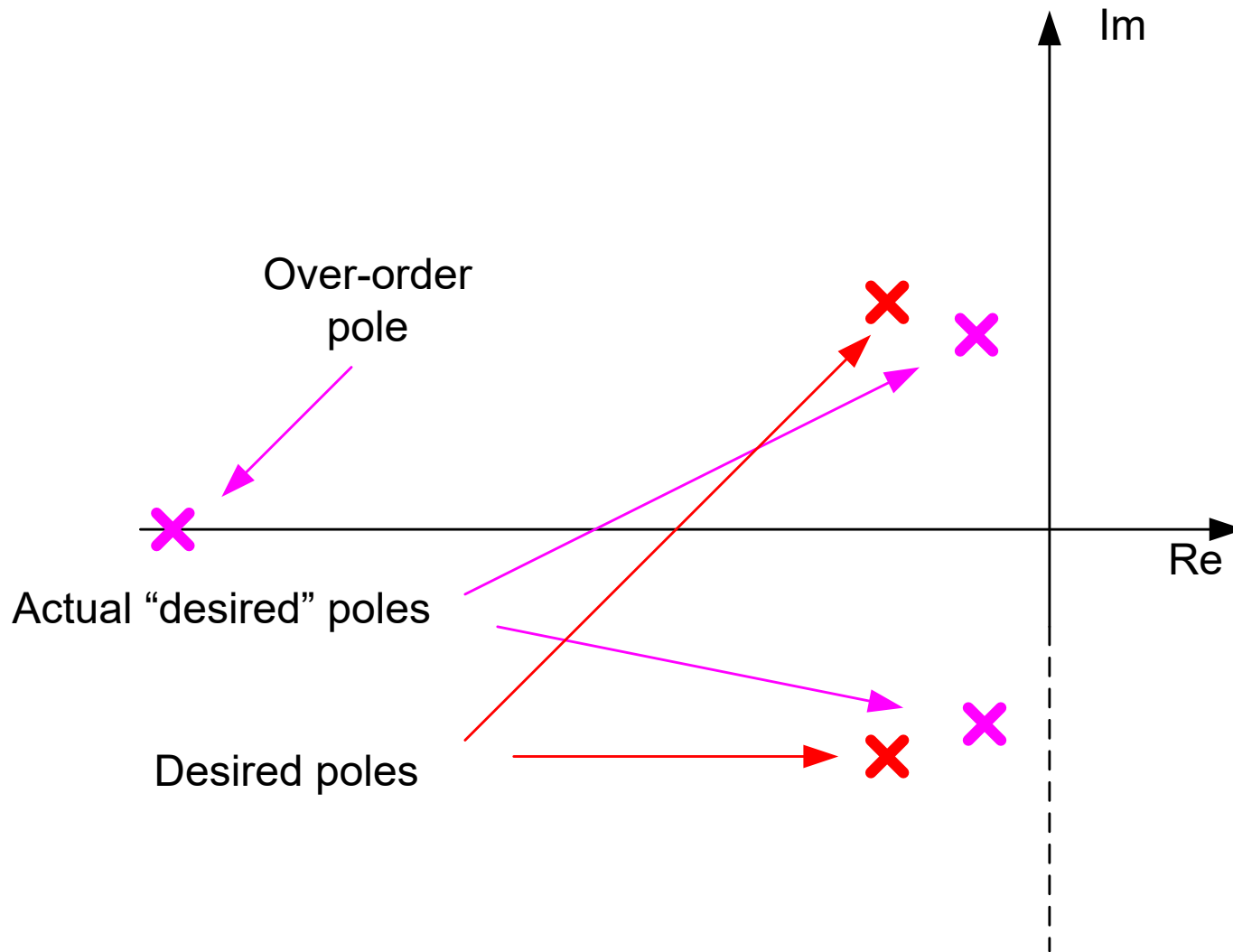Effects of GB on poles of KRC and -KRC Lowpass Filters





Stay Safe and Stay Healthy !

End of Lecture 18