

# EE 508


## Lecture 21

### Sensitivity Functions


- Comparison of Filter Structures
- Performance Prediction

What causes the dramatic differences in performance between these two structures?  
 How can the performance of different structures be compared in general?


Review from last time

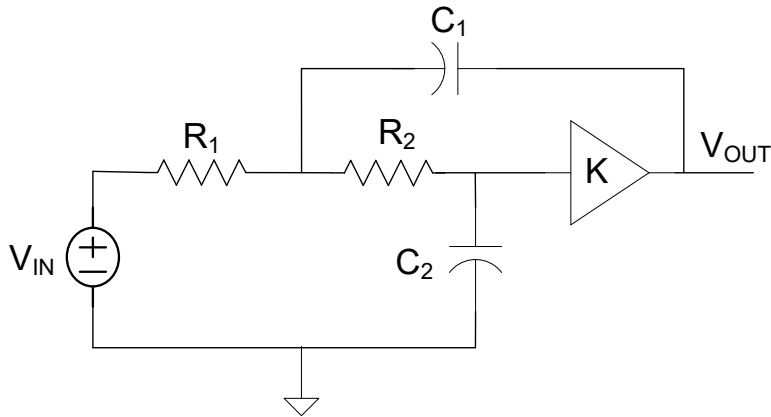

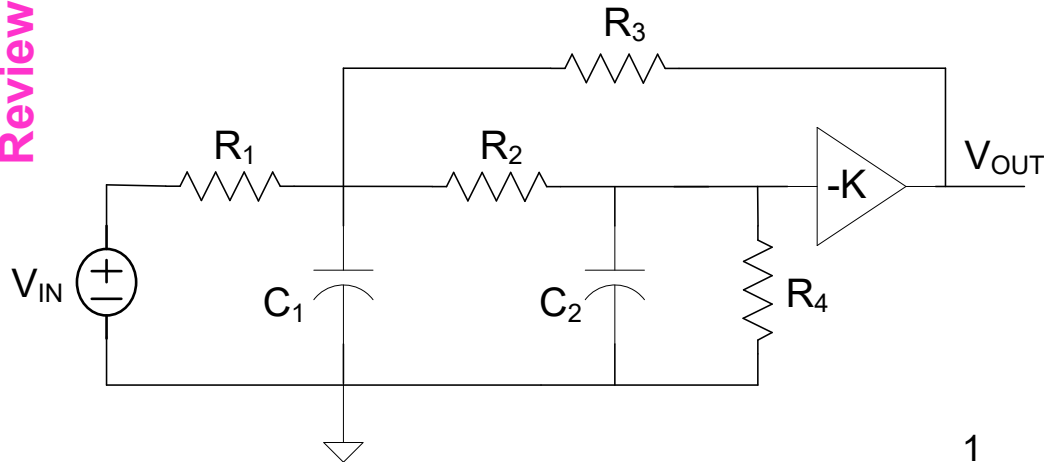
$$T(s) = K \frac{1}{s^2 + s \left[ \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$


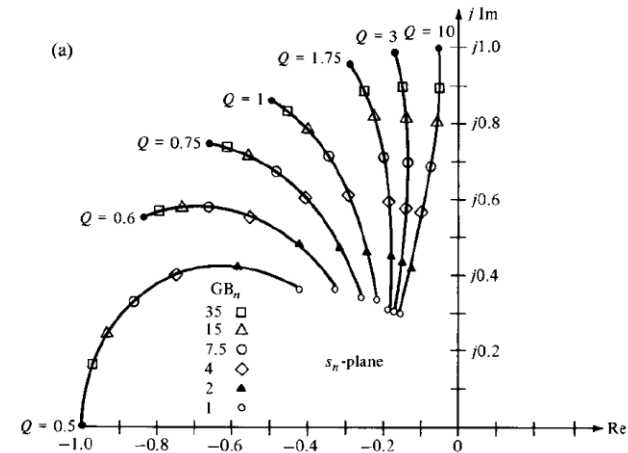
$$T(s) = -K \frac{1}{s^2 + s \left[ \frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right) \right] + \left[ \frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2} \right]}$$




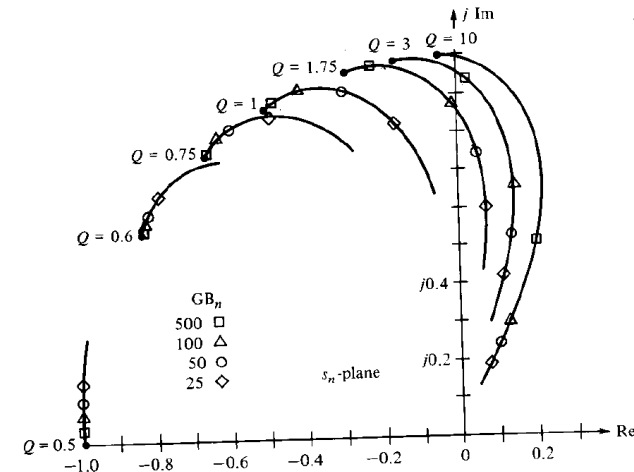Equal R, Equal C, Q=10 Pole Locus vs GB<sub>N</sub>



## Review from last time
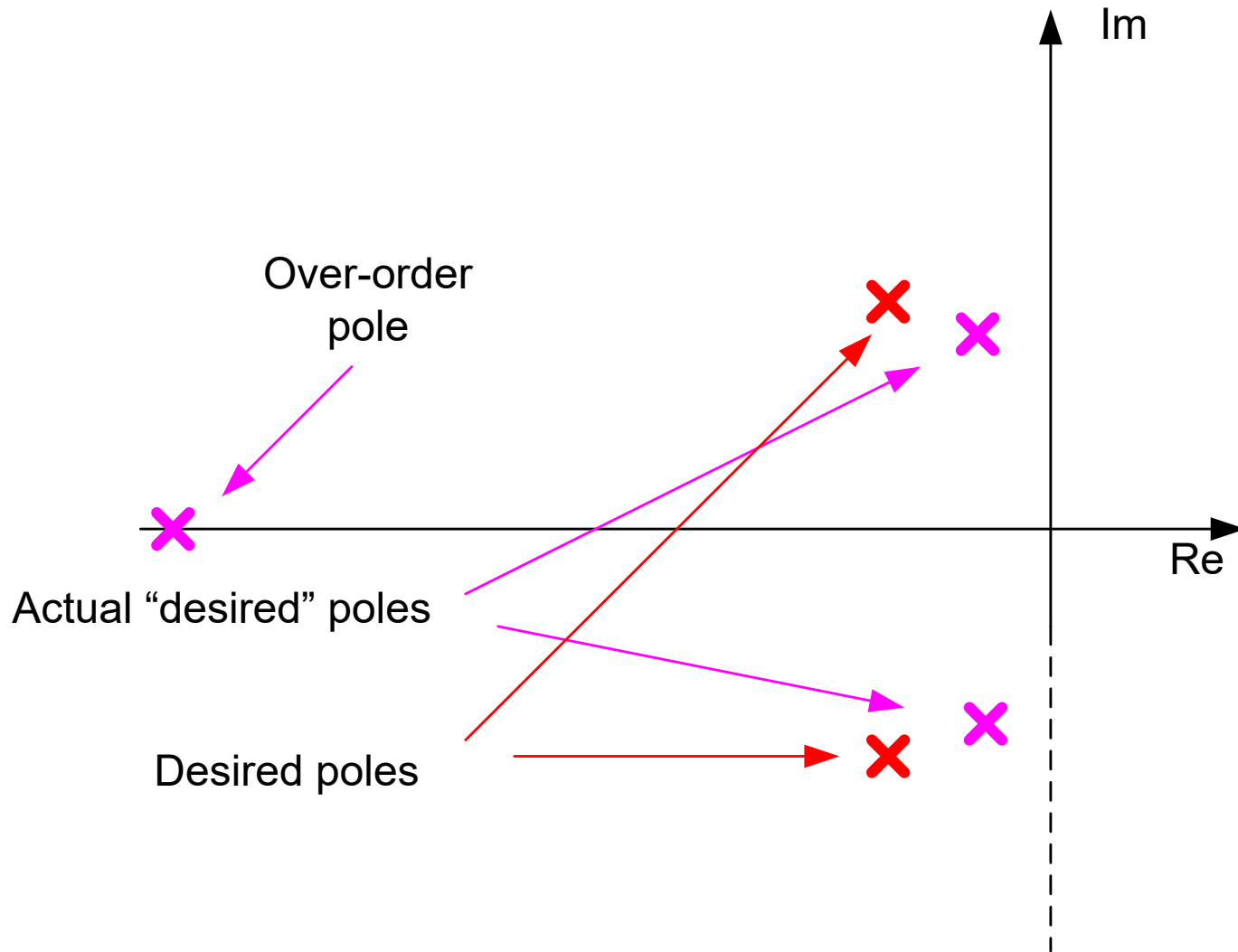
### Effects of GB on poles of KRC and -KRC Lowpass Filters




$$\frac{dF}{F} = \sum_{i=1}^k \left( S_{x_i}^f \bigg|_{\vec{X}_N} \cdot \frac{dx_i}{x_{iN}} \right)$$

**Dependent on circuit structure**  
 (for some circuits, also not dependent  
 on components)

**Dependent only on components**  
 (not circuit structure)

Consider:

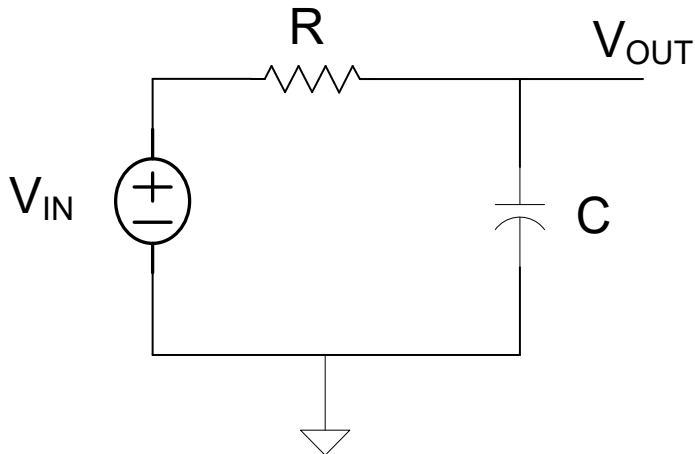

$$T(s) = \frac{1}{1+RCs}$$

$$T(s) = \frac{\omega_0}{s + \omega_0}$$

$$\omega_0 = \frac{1}{RC}$$

## Metrics for Comparing Circuits

### Summed Sensitivity

$$\rho_S = \sum_{i=1}^m \mathbf{S}_{x_i}^f$$

**Not very useful because sum can be small even when individual sensitivities are large**

### Schoeffler Sensitivity

$$\rho = \sum_{i=1}^m \left| \mathbf{S}_{x_i}^f \right|$$

Strictly heuristic but does differentiate circuits with low sensitivities from those with high sensitivities

## Metrics for Comparing Circuits

$$\rho = \sum_{i=1}^m \left| \mathbf{S}_{x_i}^f \right|$$

Often will consider several distinct sensitivity functions to consider effects of different components

$$\rho_R = \sum_{\text{All resistors}} \left| \mathbf{S}_{R_i}^f \right|$$

$$\rho_C = \sum_{\text{All capacitors}} \left| \mathbf{S}_{C_i}^f \right|$$

$$\rho_{OA} = \sum_{\text{All op amps}} \left| \mathbf{S}_{\tau_i}^f \right|$$

## Review from last time

Homogeneity (defn)

A function  $f$  is homogeneous of order  $m$  in the  $n$  variables  $\{x_1, x_2, \dots, x_n\}$  if

$$f(\lambda x_1, \lambda x_2, \dots, \lambda x_n) = \lambda^m f(x_1, x_2, \dots, x_n)$$

Note:  $f$  may be comprised of more than  $n$  variables

## Review from last time

Theorem: If a function  $f$  is homogeneous of order  $m$  in the  $n$  variables  $\{x_1, x_2, \dots, x_n\}$  then

$$\sum_{i=1}^n S_{x_i}^f = m$$

$$f(\lambda x_1, \lambda x_2, \dots, \lambda x_n) = \lambda^m f(x_1, x_2, \dots, x_n)$$

The concept of homogeneity and this theorem were somewhat late to appear

Are there really any useful applications of this rather odd observation?



Let  $T(s)$  be a voltage or current transfer function  
(i.e. dimensionless)

Observation: Impedance scaling does not change  
any of the following, provided Op Amps are ideal:

$$T(s), T(j\omega), |T(j\omega)|, \omega_0, Q, p_k, z_k$$

So, consider impedance scaling by a parameter  $\lambda$

$$R \rightarrow \lambda R$$

$$L \rightarrow \lambda L$$

$$C \rightarrow C / \lambda$$

For these impedance invariant functions

$$f(\lambda x_1, \lambda x_2, \dots, \lambda x_n) = \lambda^0 f(x_1, x_2, \dots, x_n)$$

Thus, all of these functions are homogeneous of order  $m=0$   
in the impedances

# Let $T(s)$ be a Transresistance or Transconductance Transfer Function

Observation: Impedance scaling does not change any of the following, provided Op Amps are ideal:

$\omega_0$ ,  $Q$ ,  $p_k$ ,  $z_k$ , band edge

(these are impedance invariant functions)

So, consider impedance scaling by a parameter  $\lambda$

$$R \rightarrow \lambda R$$

$$L \rightarrow \lambda L$$

$$C \rightarrow C / \lambda$$

For these impedance invariant functions

$$f(\lambda x_1, \lambda x_2, \dots, \lambda x_n) = \lambda^0 f(x_1, x_2, \dots, x_n)$$

Thus, all of these functions are homogeneous of order  $m=0$  in the impedances

Theorem 1: If all op amps in a filter are ideal, then  $\omega_o$ ,  $Q$ , BW, all band edges, and all poles and zeros are homogeneous of order 0 in the impedances.

Theorem 2: If all op amps in a filter are ideal and if  $T(s)$  is a dimensionless transfer function,  $T(s)$ ,  $T(j\omega)$ ,  $|T(j\omega)|$ ,  $\angle T(j\omega)$ , are homogeneous of order 0 in the impedances

**Theorem 1:** If all op amps in a filter are ideal, then  $\omega_o$ ,  $Q$ , BW, all band edges, and all poles and zeros are homogeneous of order 0 in the impedances.

Proof of Theorem 1

These functions are all impedance invariant so it follows trivially that they are homogeneous of order 0 in all of the impedances

Theorem 3: If all op amps in a filter are ideal and if  $T(s)$  is an impedance transfer function,  $T(s)$  and  $T(j\omega)$  are homogeneous of order 1 in the impedances

Theorem 4: If all op amps in a filter are ideal and if  $T(s)$  is a conductance transfer function,  $T(s)$  and  $T(j\omega)$  are homogeneous of order -1 in the impedances

Corollary 1: If all op amps in an RC active filter are ideal and there are  $k_1$  resistors and  $k_2$  capacitors and if a function  $f$  is homogeneous of order 0 in the impedances, then

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^f = \sum_{i=1}^{k_2} \mathbf{S}_{C_i}^f$$

Corollary 2: If all op amps in an RC active filter are ideal and there are  $k_1$  resistors and  $k_2$  capacitors then

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^Q = 0$$

$$\sum_{i=1}^{k_2} \mathbf{S}_{C_i}^Q = 0$$

Corollary 1: If all op amps in an RC active filter are ideal and there are  $k_1$  resistors and  $k_2$  capacitors and if a function  $f$  is homogeneous of order 0 in the impedances, then

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^f = \sum_{i=1}^{k_2} \mathbf{S}_{C_i}^f$$

Corollary 2: If all op amps in an RC active filter are ideal and there are  $k_1$  resistors and  $k_2$  capacitors then

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^Q = 0$$

$$\sum_{i=1}^{k_2} \mathbf{S}_{C_i}^Q = 0$$

## Proof of Corollary 1:

Corollary 1: If all op amps in an RC active filter are ideal and there are  $k_1$  resistors and  $k_2$  capacitors and if a function  $f$  is homogeneous of order 0 in the impedances, then

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^f = \sum_{i=1}^{k_2} \mathbf{S}_{C_i}^f$$

Proof:

Since  $f$  is homogenous of order zero in the impedances,  $z_1, z_2, \dots, z_{k_1+k_2}$ ,

$$\sum_{i=1}^{k_1+k_2} \mathbf{S}_{z_i}^f = 0$$

$$\therefore \sum_{i=1}^{k_1} \mathbf{S}_{R_i}^f + \sum_{i=1}^{k_2} \mathbf{S}_{1/C_i}^f = 0$$



$$\therefore \sum_{i=1}^{k_1} \mathbf{S}_{R_i}^f - \sum_{i=1}^{k_2} \mathbf{S}_{C_i}^f = 0$$





## Proof of Corollary 2:

Recall:

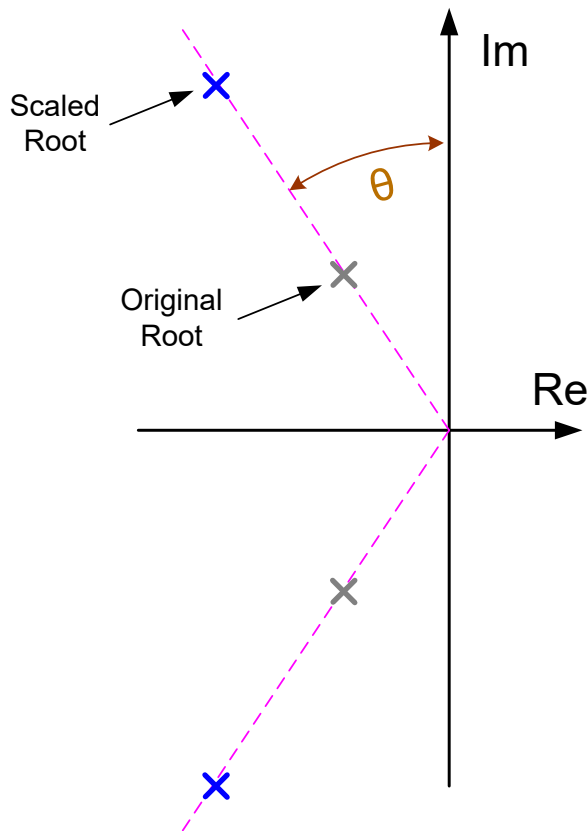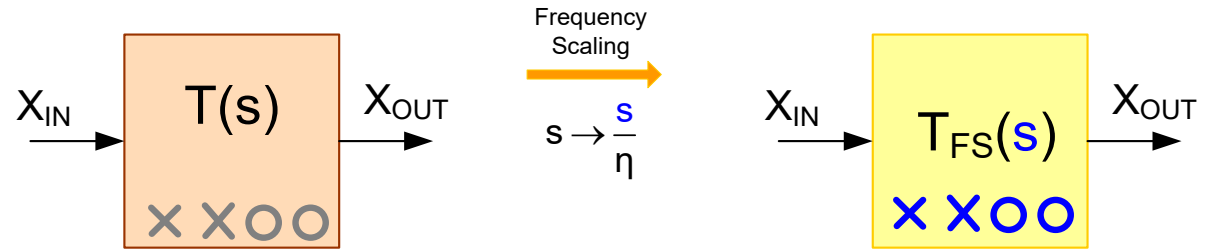

Frequency Scaling: Scaling all frequency-dependent elements by a constant

$$L \rightarrow \eta L$$

$$C \rightarrow \eta C$$


**Theorem:** If all components are frequency scaled, roots (poles and zeros) will move along a constant Q locus

**Proof of Theorem:**

$$T_{FS}(s) = T(s) \Big|_{s=\frac{s}{\eta}}$$

## Proof of Corollary 2:

Recall:

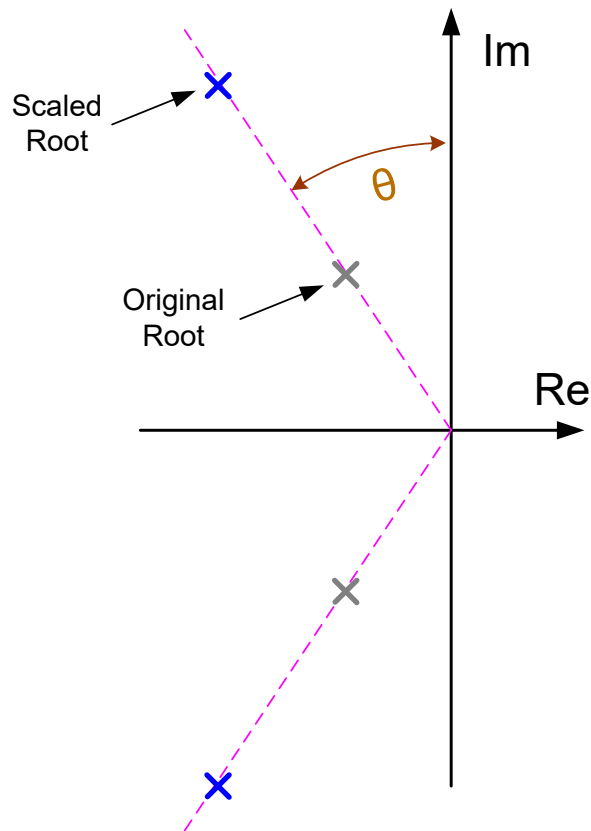

**Theorem:** If all components are frequency scaled, roots (poles and zeros) will move along a constant Q locus

**Proof:**  $T_{FS}(s) = T(s) \Big|_{s=\frac{s}{\eta}}$

Let  $p$  be a pole (or zero) of  $T(s)$

$$T(p) = 0 \quad \text{consider} \quad p = \frac{p}{\eta}$$

$$T_{FS}(s) = T\left(\frac{s}{\eta}\right) = T(s)$$

Since true for any variable, substitute in  $p$

$$T_{FS}(p) = T\left(\frac{p}{\eta}\right) = T(p) = 0$$


Thus  $p$  is a pole (or zero) of  $T_{FS}(s)$

## Proof of Corollary 2:

Recall:

**Theorem:** If all components are frequency scaled, roots (poles and zeros) will move along a constant Q locus

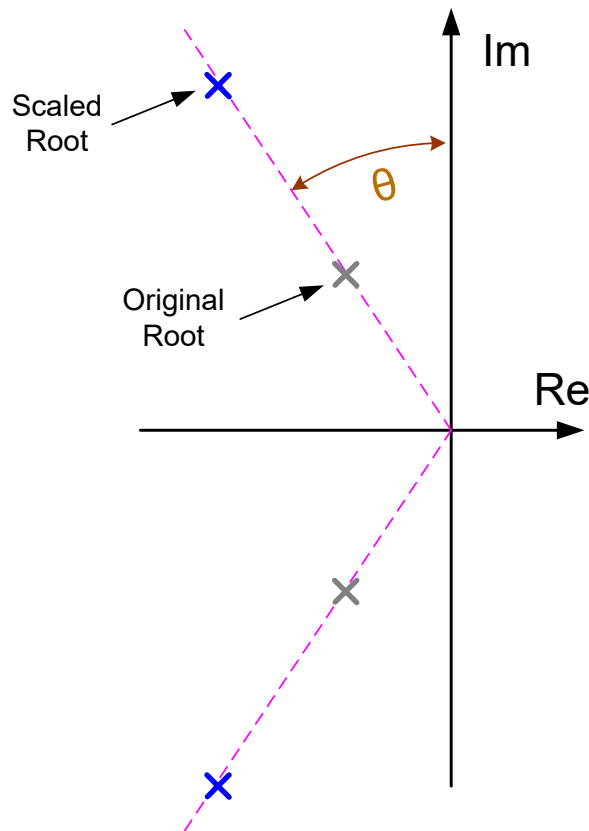**Proof:** Thus  $\mathbf{p}$  is a pole (or zero) of  $T_{FS}(s)$



$$\mathbf{p} = \frac{\mathbf{p}}{\eta}$$

$$\mathbf{p} = \mathbf{p}\eta$$

Express  $\mathbf{p}$  in polar form

$$\mathbf{p} = r e^{j\beta}$$


$$\mathbf{p} = \eta \mathbf{p} = \eta r e^{j\beta}$$

Thus  $\mathbf{p}$  and  $\mathbf{p}$  have the same angle

Thus the scaled root has the same root Q

# Proof of Corollary 2: Impedance and Frequency Scaling

Recall:

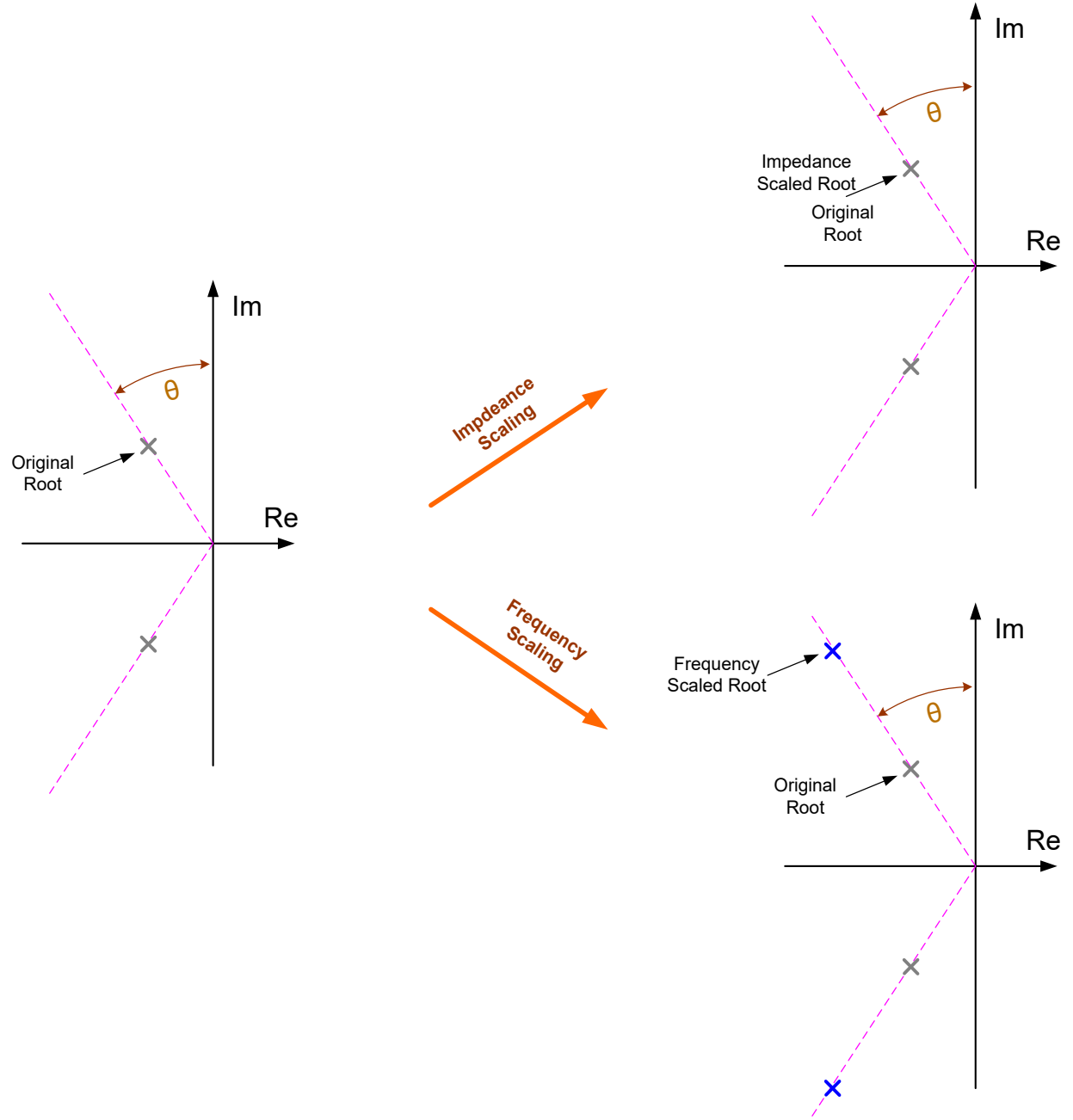

## Proof of Corollary 2:

**Corollary 2:** If all op amps in an RC active filter are ideal and there are  $k_1$  resistors and  $k_2$  capacitors then  $\sum_{i=1}^{k_2} \mathbf{S}_{C_i}^Q = \mathbf{0}$  and  $\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^Q = \mathbf{0}$

Since impedance scaling does not change pole (or zero)  $Q$ , the pole (or zero)  $Q$  must be homogeneous of order 0 in the impedances

(For more generality, assume  $k_3$  inductors)

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^Q + \sum_{i=1}^{k_2} \mathbf{S}_{1/C_i}^Q + \sum_{i=1}^{k_3} \mathbf{S}_{L_i}^Q = \mathbf{0} \quad (1)$$

Since frequency scaling does not change pole (or zero)  $Q$ , the pole (or zero)  $Q$  must be homogeneous of order 0 in the frequency scaling elements

$$\sum_{i=1}^{k_2} \mathbf{S}_{C_i}^Q + \sum_{i=1}^{k_3} \mathbf{S}_{L_i}^Q = \mathbf{0} \quad (2)$$

## Proof of Corollary 2:

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^Q + \sum_{i=1}^{k_2} \mathbf{S}_{1/C_i}^Q + \sum_{i=1}^{k_3} \mathbf{S}_{L_i}^Q = \mathbf{0} \quad (1)$$

$$\sum_{i=1}^{k_2} \mathbf{S}_{C_i}^Q + \sum_{i=1}^{k_3} \mathbf{S}_{L_i}^Q = \mathbf{0} \quad (2)$$

From theorem about sensitivity of reciprocals, can write (1) as

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^Q - \sum_{i=1}^{k_2} \mathbf{S}_{C_i}^Q + \sum_{i=1}^{k_3} \mathbf{S}_{L_i}^Q = \mathbf{0} \quad (3)$$

It follows from (2) and (3) that


$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^Q - 2 \sum_{i=1}^{k_3} \mathbf{S}_{L_i}^Q = \mathbf{0} \quad (4)$$

Since RC network, it follows from (4) and (2) that

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^Q = \mathbf{0} \quad \sum_{i=1}^{k_2} \mathbf{S}_{C_i}^Q = \mathbf{0}$$



# Example

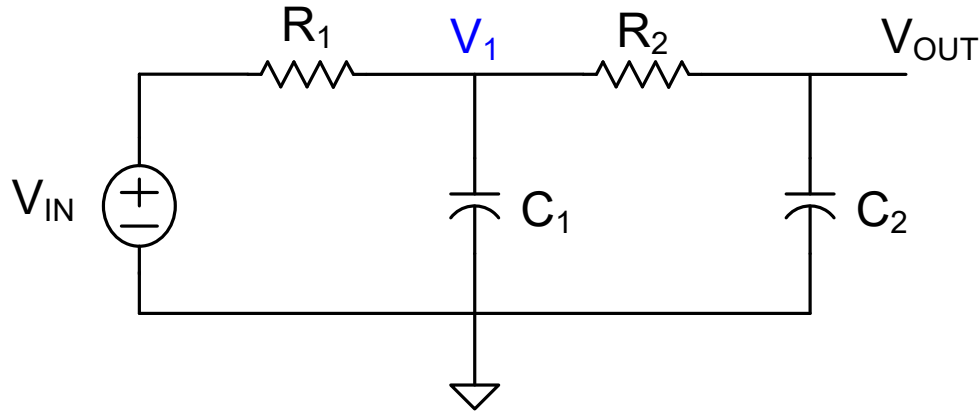

Determine the passive Q sensitivities

$$S_{R_1}^Q \quad S_{R_2}^Q \quad S_{C_1}^Q \quad S_{C_2}^Q$$

$$\left. \begin{aligned} V_{OUT}(sC_1 + G_2) &= V_1 G_2 \\ V_1(sC_1 + G_1 + G_2) &= V_{IN} G_1 + V_{OUT} G_2 \end{aligned} \right\}$$

$$T(s) = \frac{1}{s^2(R_1 R_2 C_1 C_2) + s(R_1 C_1 + R_1 C_2 + R_2 C_2) + 1}$$


$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{R_1 C_1 + R_1 C_2 + R_2 C_2}$$

By the definition of sensitivity, it follows that

$$S_{R_1}^Q = \frac{(R_1 C_1 + R_1 C_2 + R_2 C_2) \frac{1}{2} (R_1 R_2 C_1 C_2)^{-1/2} R_2 C_1 C_2 - (C_1 + C_2) (R_1 R_2 C_1 C_2)^{1/2}}{(R_1 C_1 + R_1 C_2 + R_2 C_2)^2} \cdot \frac{R_1}{Q}$$

# Example

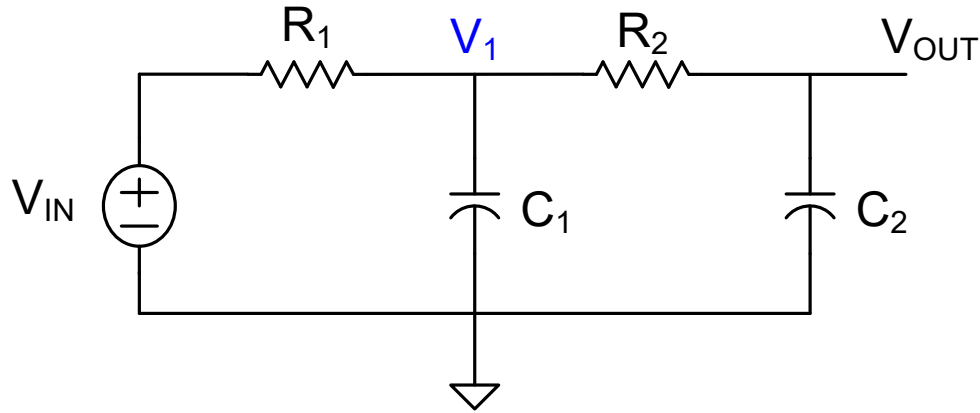

Determine the passive Q sensitivities

$$S_{R_1}^Q \quad S_{R_2}^Q \quad S_{C_1}^Q \quad S_{C_2}^Q$$


$$S_{R_1}^Q = \frac{(R_1 C_1 + R_1 C_2 + R_2 C_1) \frac{1}{2} (R_1 R_2 C_1 C_2)^{-1/2} R_2 C_1 C_2 - (C_1 + C_2) (R_1 R_2 C_1 C_2)^{1/2}}{(R_1 C_1 + R_1 C_2 + R_2 C_2)^2} \cdot \frac{R_1}{Q}$$

Following some tedious manipulations, this simplifies to

$$S_{R_1}^Q = \frac{1}{2} - \frac{R_1 (C_1 + C_2)}{R_1 C_1 + R_1 C_2 + R_2 C_2}$$



## Example

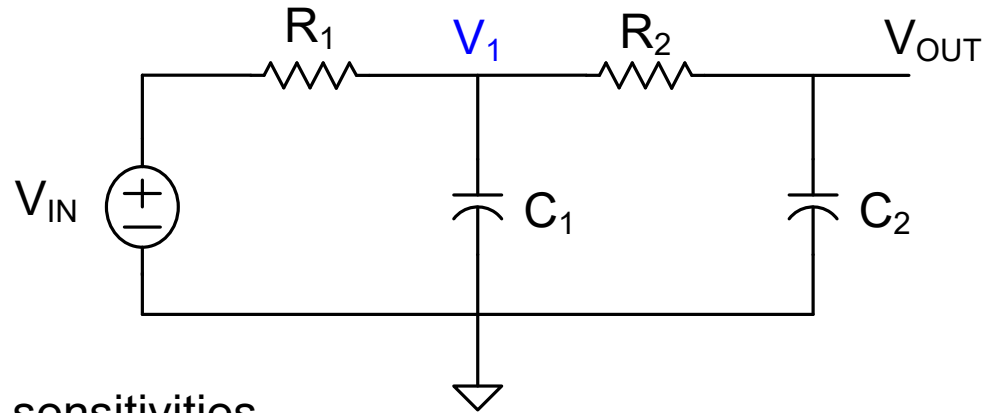

Determine the passive Q sensitivities

Following the same type of calculations, can obtain

$$S_{R_1}^Q = \frac{1}{2} - \frac{R_1(C_1 + C_2)}{R_1C_1 + R_1C_2 + R_2C_2}$$

$$S_{R_2}^Q = \frac{1}{2} - \frac{R_2C_2}{R_1C_1 + R_1C_2 + R_2C_2}$$

$$S_{C_1}^Q = \frac{1}{2} - \frac{R_1C_1}{R_1C_1 + R_1C_2 + R_2C_2}$$

$$S_{C_2}^Q = \frac{1}{2} - \frac{C_2(R_1 + R_2)}{R_1C_1 + R_1C_2 + R_2C_2}$$

Verify

$$\sum_{i=1}^{k_2} S_{C_i}^Q = 0$$

$$\sum_{i=1}^{k_1} S_{R_i}^Q = 0$$

Could have saved considerable effort in calculations by using these theorems after

$S_{R_1}^Q$  and  $S_{C_1}^Q$  were calculated

Corollary 3: If all op amps in an RC active filter are ideal and there are  $k_1$  resistors and  $k_2$  capacitors and if  $p_k$  is any pole and  $z_h$  is any zero, then

$$\sum_{i=1}^{k_1} S_{R_i}^{p_k} = -1 \qquad \sum_{i=1}^{k_2} S_{C_i}^{p_k} = -1$$

and

$$\sum_{i=1}^{k_1} S_{R_i}^{z_h} = -1 \qquad \sum_{i=1}^{k_2} S_{C_i}^{z_h} = -1$$

**Corollary 3:** If all op amps in an RC active filter are ideal and there are  $k_1$  resistors and  $k_2$  capacitors and if  $p_k$  is any pole and  $z_h$  is any zero, then

$$\sum_{i=1}^{k_1} S_{R_i}^{p_k} = -1$$

$$\sum_{i=1}^{k_2} S_{C_i}^{p_k} = -1$$

and

$$\sum_{i=1}^{k_1} S_{R_i}^{z_h} = -1$$

$$\sum_{i=1}^{k_2} S_{C_i}^{z_h} = -1$$

**Proof:**

It was shown that scaling the frequency dependent elements by a factor  $\eta$  divides the pole (or zero) by  $\eta$

Thus roots (poles and zeros) are homogeneous of order -1 in the frequency scaling elements

## Proof:

Thus roots (poles and zeros) are homogeneous of order -1 in the frequency scaling elements

(For more generality, assume  $k_3$  inductors)

$$\sum_{i=1}^{k_2} \mathbf{S}_{C_i}^p + \sum_{i=1}^{k_3} \mathbf{S}_{L_i}^p = -1 \quad (1)$$

Since impedance scaling does not affect the poles, they are homogeneous of order 0 in the impedances

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^p + \sum_{i=1}^{k_2} \mathbf{S}_{1/C_i}^p + \sum_{i=1}^{k_3} \mathbf{S}_{L_i}^p = 0 \quad (2)$$

Since there are no inductors in an active RC network, it follows from (1) that

$$\sum_{i=1}^{k_2} \mathbf{S}_{C_i}^p = -1$$

And then from (2) and the theorem about sensitivity to reciprocals that

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^p = -1$$

Corollary 4: If all op amps in an RC active filter are ideal and there are  $k_1$  resistors and  $k_2$  capacitors and if  $Z_{IN}$  is any input impedance of the network, then

$$\sum_{i=1}^{k_1} S_{R_i}^{Z_{IN}} - \sum_{i=1}^{k_2} S_{C_i}^{Z_{IN}} = 1$$

Claim: If op amps in the filters considered previously are not ideal but are modeled by a gain  $A(s)=1/(\tau s)$ , then all previous summed sensitivities developed for ideal op amps hold provided they are evaluated at the nominal value of  $\tau=0$

# Sensitivity Analysis

If a closed-form expression for a function  $f$  is obtained, a straightforward but tedious analysis can be used to obtain the sensitivity of the function to any components

$$S_x^f = \frac{\partial f}{\partial x} \cdot \frac{x}{f}$$

---

Consider:

$$T(s) = \frac{\sum_{i=0}^m a_i s^i}{\sum_{i=0}^n b_i s^i} = K \frac{\prod_{i=1}^m (s-z_i)}{\prod_{i=1}^n (s-p_i)}$$

Closed-form expressions for  $T(s)$ ,  $T(j\omega)$ ,  $|T(j\omega)|$ ,  $\angle T(j\omega)$ ,  $a_i$ ,  $b_i$ , can be readily obtained

# Sensitivity Analysis

If a closed-form expression for a function  $f$  is obtained, a straightforward but tedious analysis can be used to obtain the sensitivity of the function to any components

$$S_x^f = \frac{\partial f}{\partial x} \cdot \frac{x}{f}$$

---

Consider:

$$T(s) = \frac{\sum_{i=0}^m a_i s^i}{\sum_{i=0}^n b_i s^i} = K \frac{\prod_{i=1}^m (s-z_i)}{\prod_{i=1}^n (s-p_i)}$$

Closed-form expressions for  $p_i$ ,  $z_i$ , pole or zero  $Q$ , pole or zero  $\omega_0$ , peak gain,  $\omega_{3dB}$ , BW, ... (generally the most critical and useful circuit characteristics) are difficult or impossible to obtain !



# Bilinear Property of Electrical Networks

Theorem: Let  $x$  be any component or Op Amp time constant (1<sup>st</sup> order Op Amp model) of any linear active network employing a finite number of amplifiers and lumped passive components. Any transfer function of the network can be expressed in the form

$$T(s) = \frac{N_0(s) + xN_1(s)}{D_0(s) + xD_1(s)}$$


where  $N_0$ ,  $N_1$ ,  $D_0$ , and  $D_1$  are polynomials in  $s$  that are not dependent upon  $x$

A function that can be expressed as given above is said to be a bilinear function in the variable  $x$  and this is termed a bilateral property of electrical networks.

The bilinear relationship is useful for

1. Checking for possible errors in an analysis
2. Pole sensitivity analysis
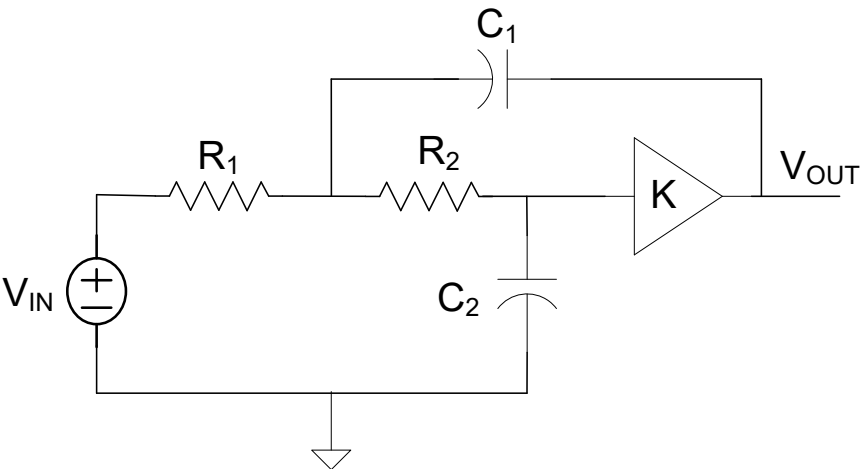
## Example of Bilinear Property : +KRC Lowpass Filter




$$T(s) = \frac{\frac{K_0}{R_1 R_2 C_1 C_2}}{s^2 + s \left[ \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{(1-K_0)}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2} + K_0 \tau s \left( s^2 + s \left[ \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2} \right)}$$

Consider  $R_1$

$$T(s) = \frac{\frac{K_0}{R_2 C_1 C_2}}{R_1 s^2 + s \left[ \frac{1}{C_1} + R_1 \frac{1}{R_2 C_1} + R_1 \frac{(1-K_0)}{R_2 C_2} \right] + \frac{1}{R_2 C_1 C_2} + K_0 \tau s \left( R_1 s^2 + s \left[ \frac{1}{C_1} + R_1 \frac{1}{R_2 C_1} + R_1 \frac{1}{R_2 C_2} \right] + \frac{1}{R_2 C_1 C_2} \right)}$$

$$T(s) = \frac{\left[ \frac{K_0}{R_2 C_1 C_2} \right] + R_1 \cdot [0]}{\left[ s \frac{1}{C_1} + \frac{1}{R_2 C_1 C_2} + K_0 \tau s \left( s \frac{1}{C_1} \right) + \frac{1}{R_2 C_1 C_2} \right] + R_1 \left[ s^2 + s \left[ \frac{1}{R_2 C_1} + \frac{(1-K_0)}{R_2 C_2} \right] + K_0 \tau s \left( s^2 + s \left[ \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} \right] \right) \right]}$$

## Example of Bilinear Property

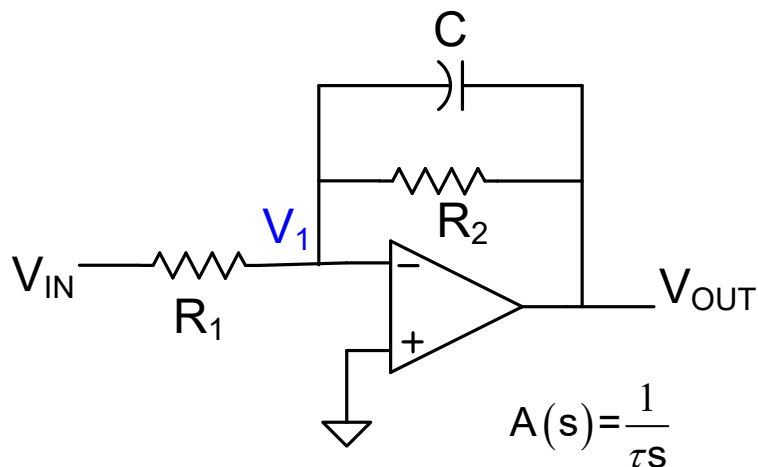

$$\left. \begin{aligned} V_1(G_1 + G_2 + sC) &= V_{IN}G_1 + V_{OUT}(sC + G_2) \\ V_{OUT} &= -V_1\left(\frac{1}{\tau s}\right) \end{aligned} \right\}$$

$$T(s) = \frac{-R_2}{R_1 + R_1 R_2 C s + \tau s (s C R_1 R_2 + R_1 + R_2)}$$


Consider  $R_1$

$$T(s) = \frac{-R_2 + 0 \bullet R_1}{[\tau s R_2] + R_1 [1 + R_2 C s + \tau s (s C R_2 + 1)]}$$

Consider  $\tau$

$$T(s) = \frac{-R_2 + 0 \bullet \tau}{[R_1 (1 + R_2 C s)] + \tau [s R_2 + s R_1 (s C R_2 + 1)]}$$
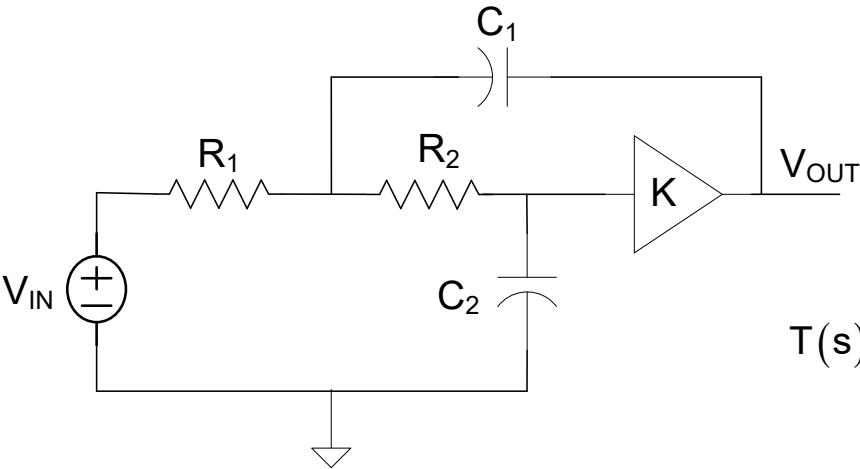
## Example of Bilinear Property : +KRC Lowpass Filter



Equal R Equal C

$$T(s) = \frac{\frac{K_0}{R^2 C^2}}{s^2 + s \left[ \frac{(3-K_0)}{RC} \right] + \frac{1}{R^2 C^2} + K_0 \tau s \left( s^2 + s \left[ \frac{3}{RC} \right] + \frac{1}{R^2 C^2} \right)}$$

$$T(s) = \frac{K_0}{R^2 (C^2 s^2 + K_0 \tau s C^2) + R (s C (3 - K_0) + 3 K_0 C \tau s^2) + (1 + K_0 \tau s)}$$

Can not eliminate the  $R^2$  term

- Bilinear property only applies to individual components
- Bilinear property was established only for  $T(s)$



Stay Safe and Stay Healthy !

End of Lecture 21