


# EE 508

## Lecture 24

# Integrator Design

TA-C Integrators  
Other Integrator Structures

# Integrator Characteristics of Interest

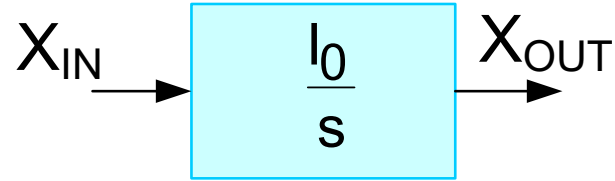

$$I(s) = \frac{I_0}{s}$$

Properties of an ideal integrator:

$$|I(j\omega)| = \frac{I_0}{\omega}$$

Gain decreases with  $1/\omega$

$$\angle I(j\omega) = -90^\circ$$






Phase is a constant  $-90^\circ$

$$|I(jI_0)| = 1$$

Unity Gain Frequency = 1

How important is it that an integrator have all 3 of these properties?


# Some integrator structures

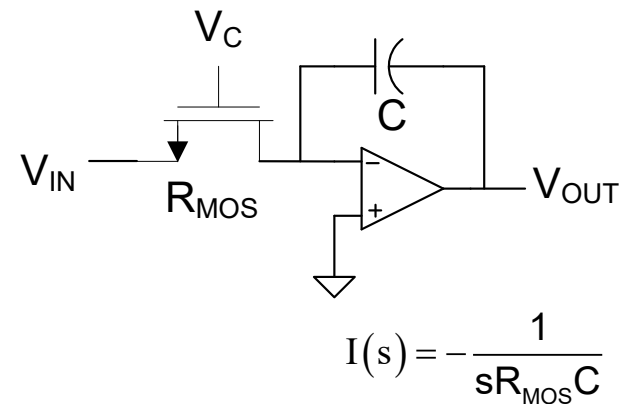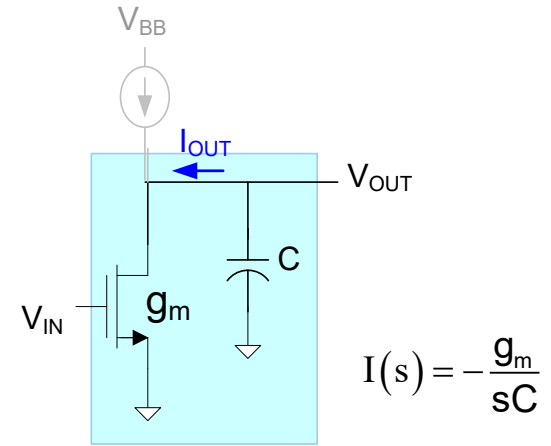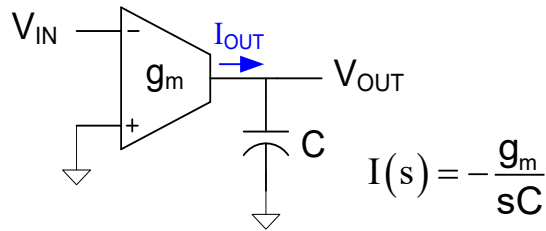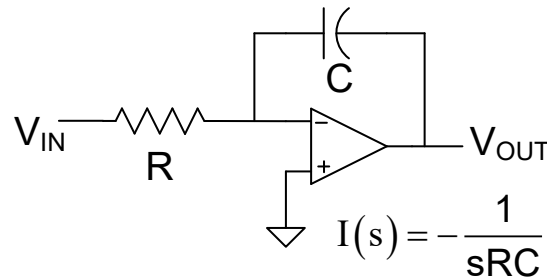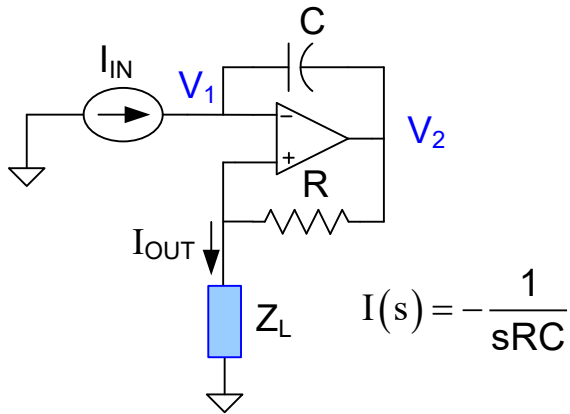

There are other useful integrator structures (some will be introduced later)

There are many different ways to build an inverting integrator

# Integrator-Based Filter Design

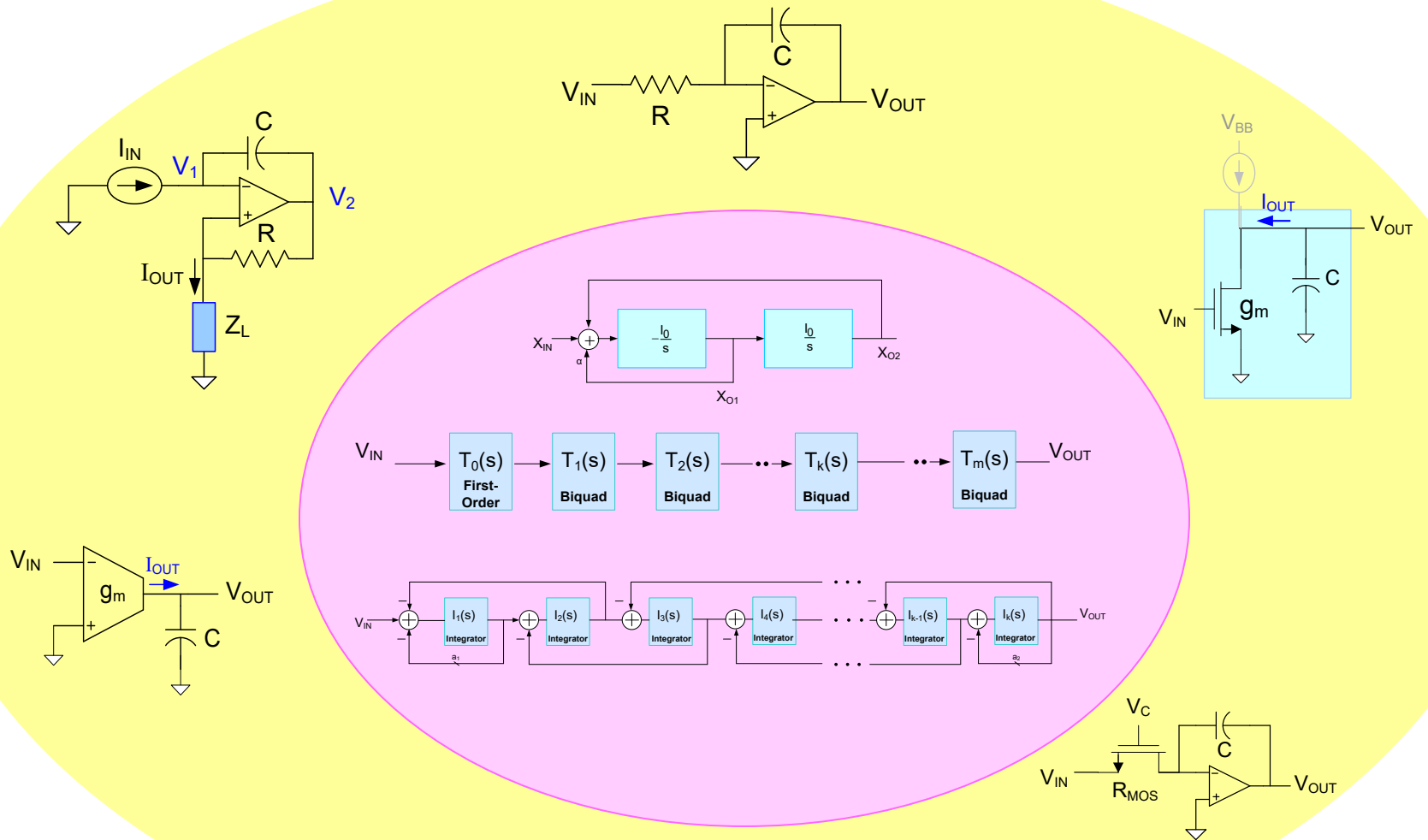

Any of these different types of integrators can be used to build integrator-based filters

# Are new integrators still being invented?

## USPTO PATENT FULL-TEXT AND IMAGE DATABASE

- Home
- Quick
- Advanced
- Pat Num
- Help
- View Cart

Data current through **October 16, 2018..**

Query [\[Help\]](#)

Term 1:  in Field 1:   
AND  
Term 2:  in Field 2:

Select years [\[Help\]](#)

**1976 to present [full-text]**

Search Reset

Patents from 1790 through 1975 are searchable only by Issue Date, Patent Number, and Current US Classification.

When searching for specific numbers in the Patent Number field, utility patent numbers are entered as one to eight numbers in length, excluding commas (which are optional, as are leading zeroes).

Searching US Patent Collection...

Results of Search in US Patent Collection db for:

**TTL/integrator** - 531 patents.

Hits 1 through **50 out of 531**

Next 50 Hits

Jump To

Refine Search

Oct 16 2018




# Review from last time

Nov 2017

Nov 2016

PAT. NO.	Title
1 10,082,922	<a href="#">Increasing the dynamic range of an integrator based mutual-capacitance measurement circuit</a>
2 10,074,004	<a href="#">Capacitive fingerprint sensor with integrator</a>
3 10,070,089	<a href="#">Inverting amplifier, integrator, sample hold circuit, ad converter, image sensor, and imaging apparatus</a>
4 9,985,594	<a href="#">Gated CDS integrator</a>
5 9,972,003	<a href="#">Pregame electronic commerce integrator</a>
6 9,954,514	<a href="#">Output range for interpolation architectures employing a cascaded integrator-comb (CIC) filter with a multiplier</a>
7 9,885,959	<a href="#">Illumination optical apparatus having deflecting member, lens, polarization member to set polarization in circumference direction, and optical integrator</a>
8 9,885,872	<a href="#">Illumination optical apparatus, exposure apparatus, and exposure method with optical integrator and polarization member that changes polarization state of light</a>
9 9,866,237	<a href="#">Low power switched capacitor integrator, analog-to-digital converter and switched capacitor amplifier</a>
10 9,852,283	<a href="#">Confirming the identity of integrator applications</a>
11 9,825,646	<a href="#">Integrator and A/D converter using the same</a>
12 9,817,917	<a href="#">System integrator and method for mapping dynamic COBOL constructs to object instances for the automatic integration to object-oriented computing systems</a>
13 9,806,552	<a href="#">Analog/digital converter with charge rebalanced integrator</a>
14 9,800,256	<a href="#">Semiconductor device including integrator and successive approximation register analog-to-digital converter and driving method of the same</a>
15 9,753,559	<a href="#">Feedback integrator current source, transistor, and resistor coupled to input</a>
16 9,726,521	<a href="#">Signal processing apparatus for processing time variant signal with first and second input signals comprising a weighting integrator, a magnitude detector and a gain-adjustable amplifier</a>
17 9,709,242	<a href="#">Shell integrator</a>
18 9,703,178	<a href="#">Projector having a rod integrator with an entrance plane smaller than an area light source</a>
19 9,680,496	<a href="#">Apparatus for overload recovery of an integrator in a sigma-delta modulator</a>
20 9,671,916	<a href="#">Increasing the dynamic range of an integrator based mutual-capacitance measurement circuit</a>
21 9,647,677	<a href="#">Integrator, AD converter, and radiation detection device</a>
22 9,634,688	<a href="#">Integrator, delta-sigma modulator, and communications device</a>
23 9,628,103	<a href="#">Multi-mode discrete-time delta-sigma modulator power optimization using split-integrator scheme</a>
24 9,608,598	<a href="#">Cascaded integrator-comb filter as a non-integer sample rate converter</a>
25 9,588,147	<a href="#">Electronic integrator for Rogowski coil sensors</a>
26 9,574,735	<a href="#">Shell integrator</a>
27 9,558,845	<a href="#">Sampling network and clocking scheme for a switched-capacitor integrator</a>
28 9,531,718	<a href="#">Confirming the identity of integrator applications</a>
29 9,524,054	<a href="#">Integrator and touch sensing system using the same</a>
30 9,519,462	<a href="#">System integrator and method for mapping dynamic COBOL constructs to object instances for the automatic integration to object-oriented computing systems</a>
31 9,496,969	<a href="#">Double integrator pulse wave shaper apparatus, system and method</a>
32 9,495,563	<a href="#">Analog integrator system and method</a>
33 9,473,075	<a href="#">Dynamic current source for amplifier integrator stages</a>
34 9,467,153	<a href="#">Low power and compact area digital integrator for a digital phase detector</a>
35 9,461,595	<a href="#">Integrator for class D audio amplifier</a>
36 9,454,069	<a href="#">Illumination system having first and second lens arrays including plano-convex lenses wherein some lenses in the second array include a first and a second lens element, projection-type display apparatus, and optical integrator</a>
37 9,405,800	<a href="#">Apparatuses, methods and systems for a universal payment integrator</a>
38 9,389,625	<a href="#">DC-DC converter controller apparatus with dual-counter digital integrator</a>
39 9,383,395	<a href="#">Charge balancing converter using a passive integrator circuit</a>
40 9,379,732	<a href="#">Delta-sigma modulator with reduced integrator requirements</a>
41 9,362,890	<a href="#">Compensation filter for cascaded-integrator-comb decimator</a>
42 9,354,953	<a href="#">System integrator and system integration method with reliability optimized integrated circuit chip selection</a>
43 9,314,389	<a href="#">Therapeutic integrator apparatus</a>
44 9,310,924	<a href="#">Increasing the dynamic range of an integrator based mutual-capacitance measurement circuit</a>
45 9,268,441	<a href="#">Active integrator for a capacitive sense array</a>
46 9,225,351	<a href="#">Current amplifier circuit, integrator, and ad converter</a>
47 9,218,514	<a href="#">Apparatuses and method of switched-capacitor integrator</a>
48 9,171,189	<a href="#">Systems and methods for preventing saturation of analog integrator output</a>
49 9,152,387	<a href="#">System integrator and method for mapping dynamic COBOL constructs to object instances for the automatic integration to object-oriented computing systems</a>
50 9,139,096	<a href="#">One-sided detection and disabling of integrator wind up for speed control in a vehicle</a>
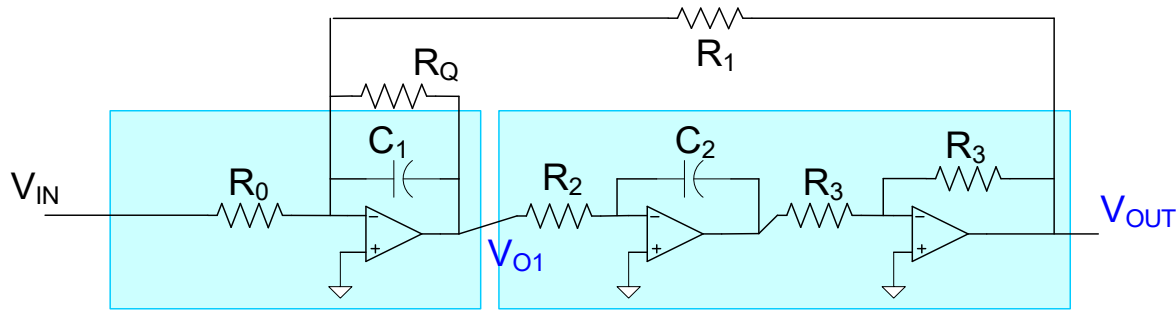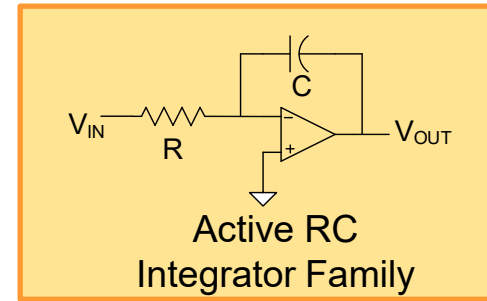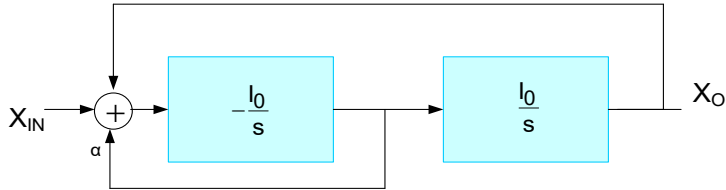
# Example – Active RC Feedback Tow Thomas Biquad



$$\left. \begin{aligned} V_{OUT} &= \frac{1}{sR_2C_2} V_{O1} \\ V_{IN}G_0 + V_{O1}(sC_1 + G_Q) + G_1V_{OUT} &= 0 \end{aligned} \right\}$$




$$\frac{V_{OUT}}{V_{IN}} = - \frac{1}{s^2 + s \frac{1}{R_Q C_1} + \frac{1}{C_1 R_1 R_2 C_2}}$$

If  $R_1 = R_2 = R$  and  $C_1 = C_2 = C$

$$\omega_0 = \frac{1}{RC}$$

$$Q = \frac{R_Q}{R}$$

# Example – OTA-C Tow Thomas Biquad

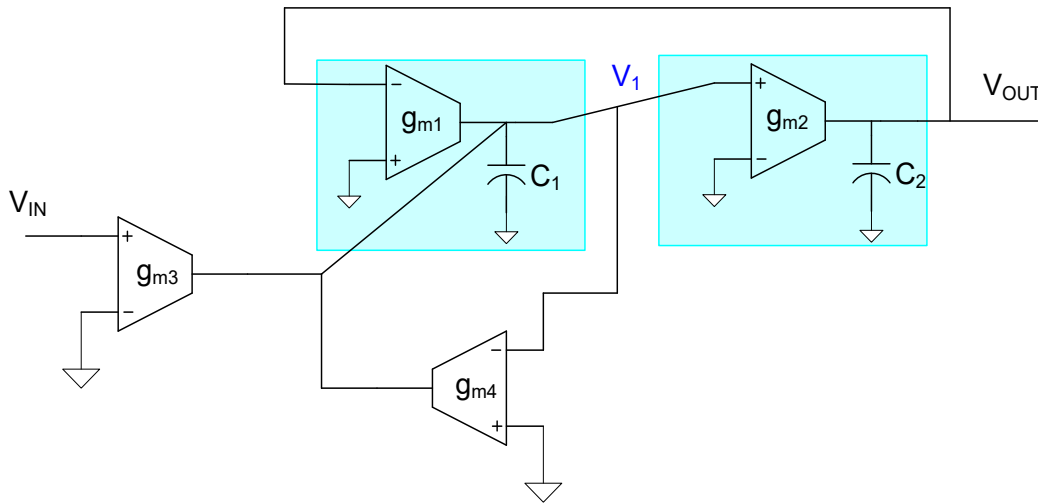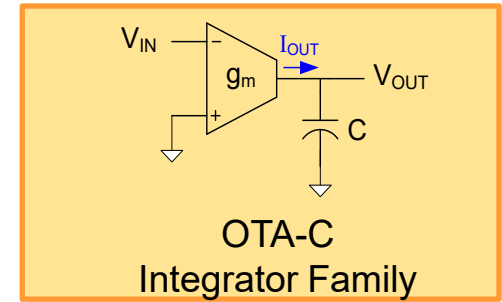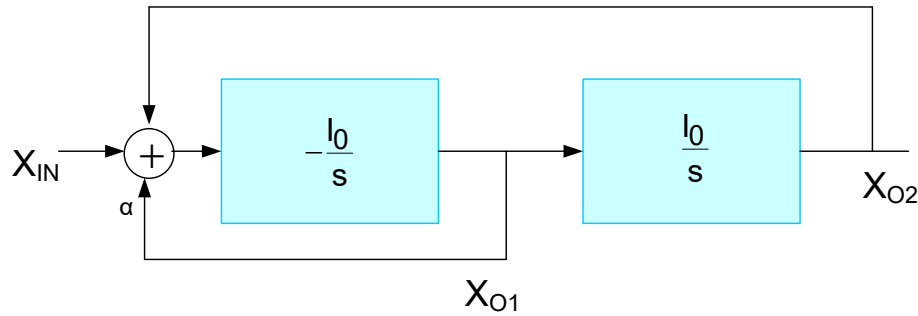

$$\frac{V_{OUT}}{V_{IN}} = \frac{g_{m3}g_{m2}}{(s^2C_1C_2 + sg_{m4}C_2 + g_{m1}g_{m2})}$$

Assume  $g_{m1}=g_{m2}=g_m$ ,  $C_1=C_2=C$

$$\frac{V_{OUT}}{V_{IN}} = \frac{\left(\frac{g_{m3}}{g_m}\right) \frac{g_m^2}{C^2}}{\left(s^2 + s\left(\frac{g_{m4}}{g_m}\right) \frac{g_m}{C} + \frac{g_m^2}{C^2}\right)}$$

express as

$$\frac{V_{OUT}}{V_{IN}} = \frac{\left(\frac{g_{m3}}{g_m}\right) \omega_0^2}{\left(s^2 + s\frac{\omega_0}{Q} + \omega_0^2\right)}$$






where

$$\omega_0 = \frac{g_m}{C} \quad Q = \frac{g_m}{g_{m4}}$$


$$\left. \begin{aligned} V_{OUT} sC_2 &= g_{m2} V_1 \\ V_1 sC_1 &= -g_{m1} V_{OUT} + g_{m3} V_{IN} - g_{m4} V_1 \end{aligned} \right\}$$



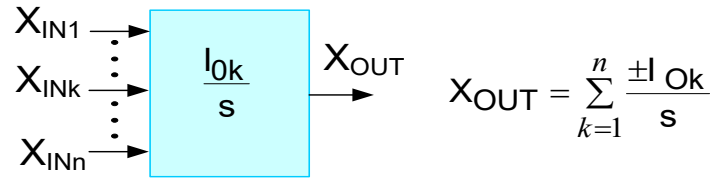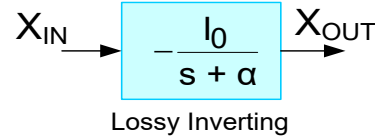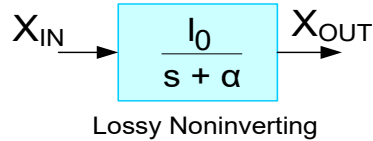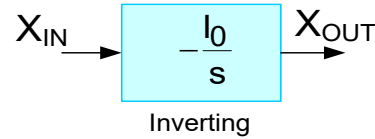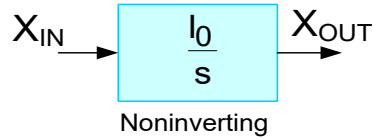
# Basic Integrator Functionality (for all families)



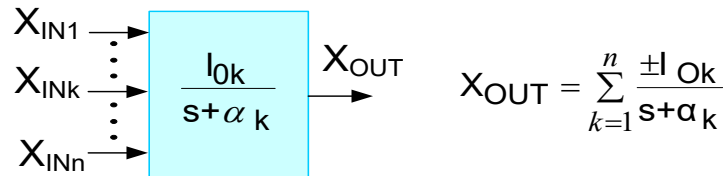Summing (Multiple-Input) Inverting/Noninverting



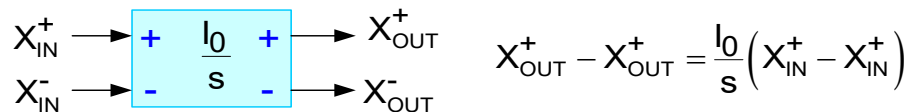Summing (Multiple-Input) Lossy Inverting/Noninverting




Balanced Differential




Fully Differential

# Basic Integrator Functionality

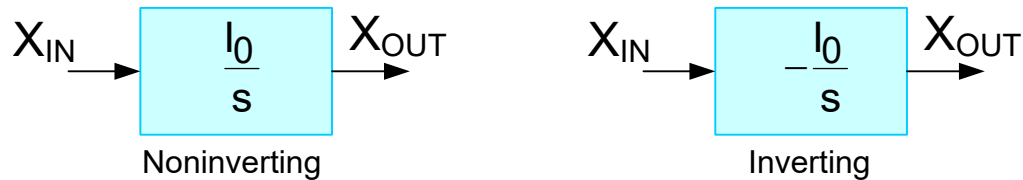


- An inverting/noninverting integrator pair define a family of integrators
- All integrator functional types can usually be obtained from the inverting/noninverting integrator pair
- Suffices to focus primarily on the design of the inverting/noninverting integrator pair since properties of class primarily determined by properties of integrator pair

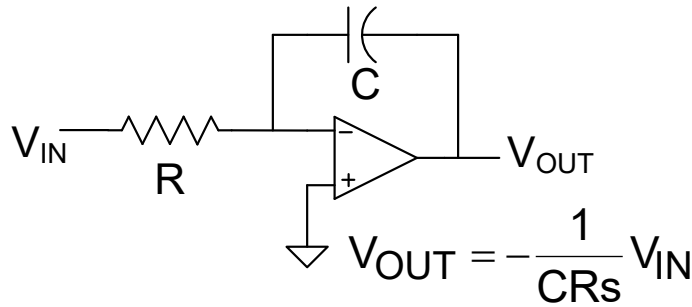
# Example – Basic Op-Amp Feedback Integrator Family



Inverting Integrator of Family

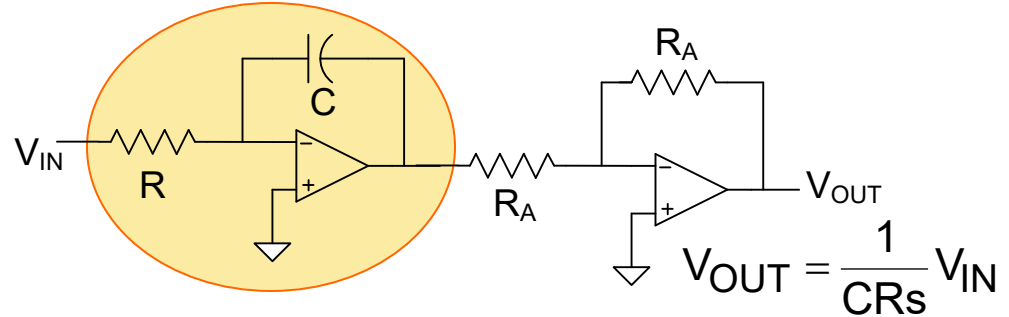


Noninverting Integrator

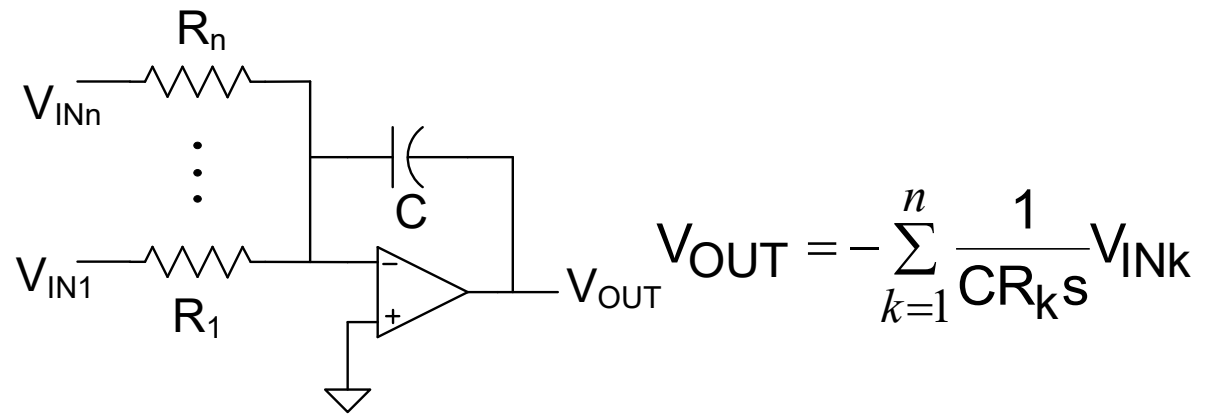


Summing Inverting Integrator
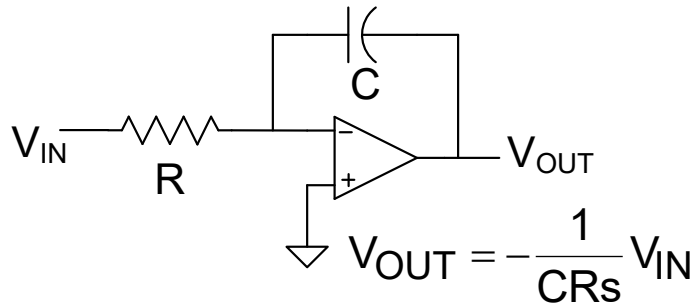
# Example – Basic Op-Amp Feedback Integrator Family




$$V_{OUT} = -\frac{1}{CRs} V_{IN}$$

Inverting Integrator of Family

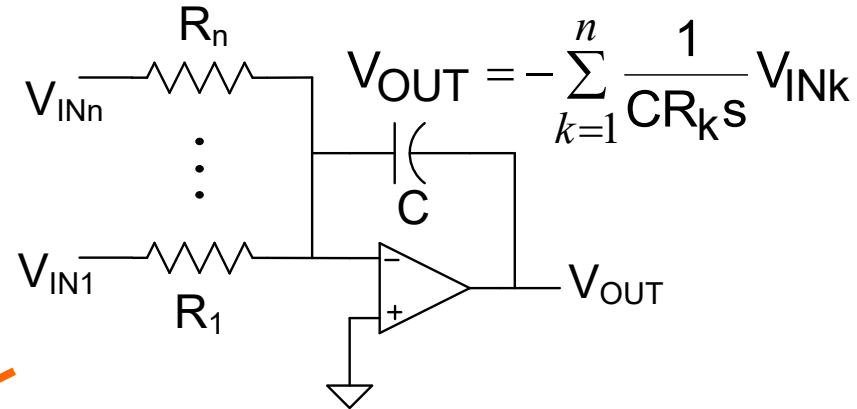


$$V_{OUT} = -\sum_{k=1}^n \frac{1}{CR_k s} V_{INK}$$

Summing Inverting Integrator

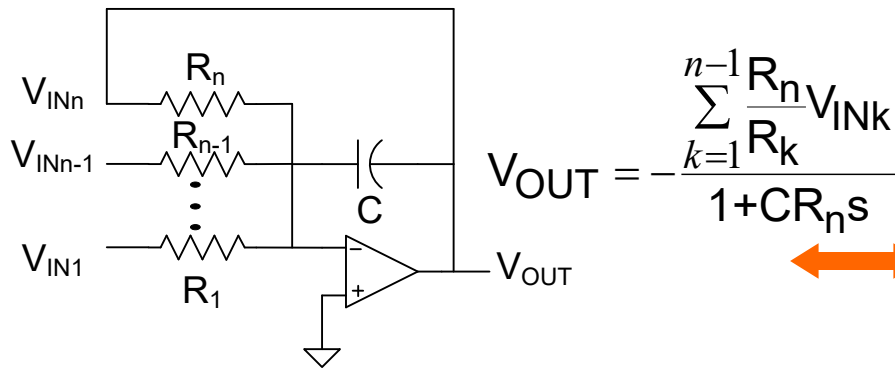


$$V_{OUT} = -\frac{\sum_{k=1}^{n-1} \frac{R_n}{R_k} V_{INK}}{1+CR_n s}$$

Lossy Summing Inverting Integrator

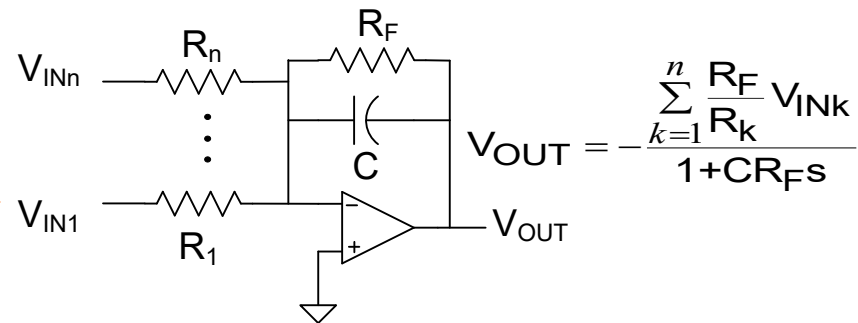


$$V_{OUT} = -\frac{\sum_{k=1}^n \frac{R_F}{R_k} V_{INK}}{1+CR_F s}$$

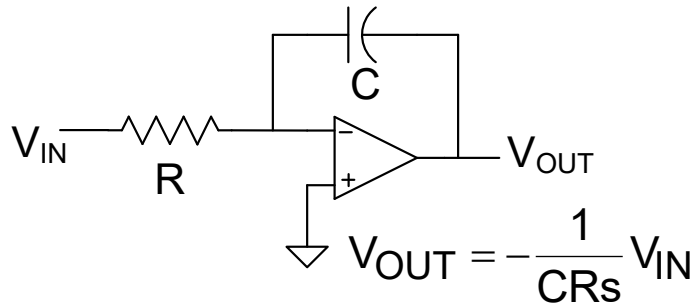
# Example – Basic Op-Amp Feedback Integrator



Inverting Integrator of Family

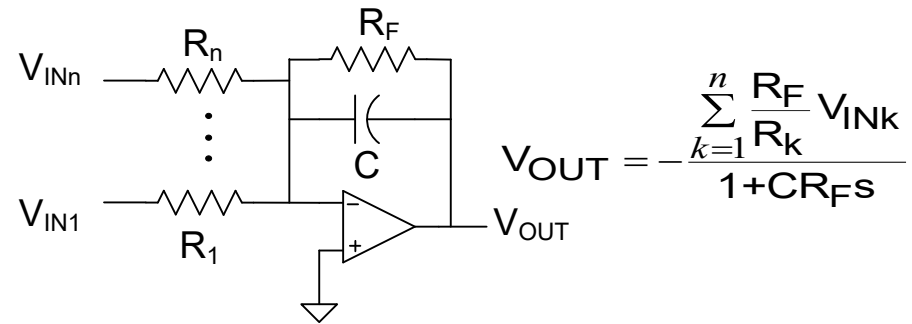


Lossy Summing Inverting Integrator

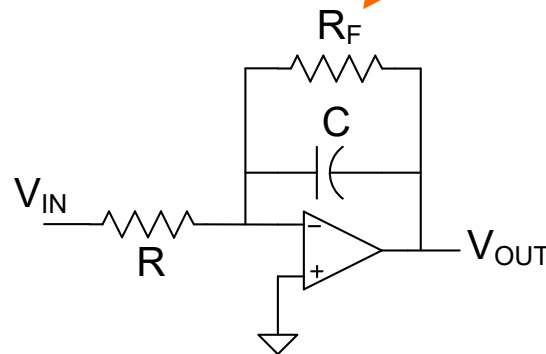


Lossy Inverting Integrator

$$V_{OUT} = -\frac{R_F/R}{1+CR_Fs} V_{IN}$$
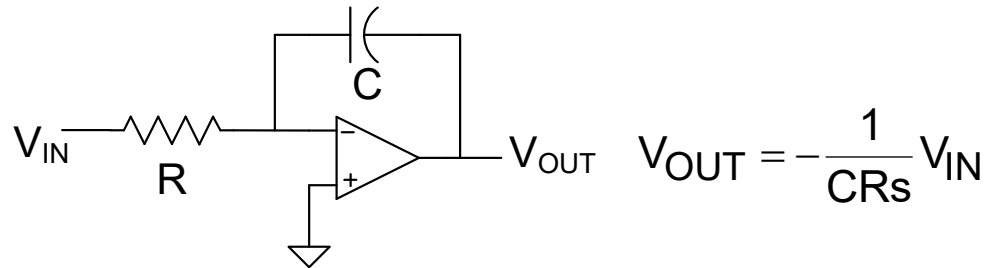
# Example – Basic Op-Amp Feedback Integrator Family




Inverting Integrator of Family

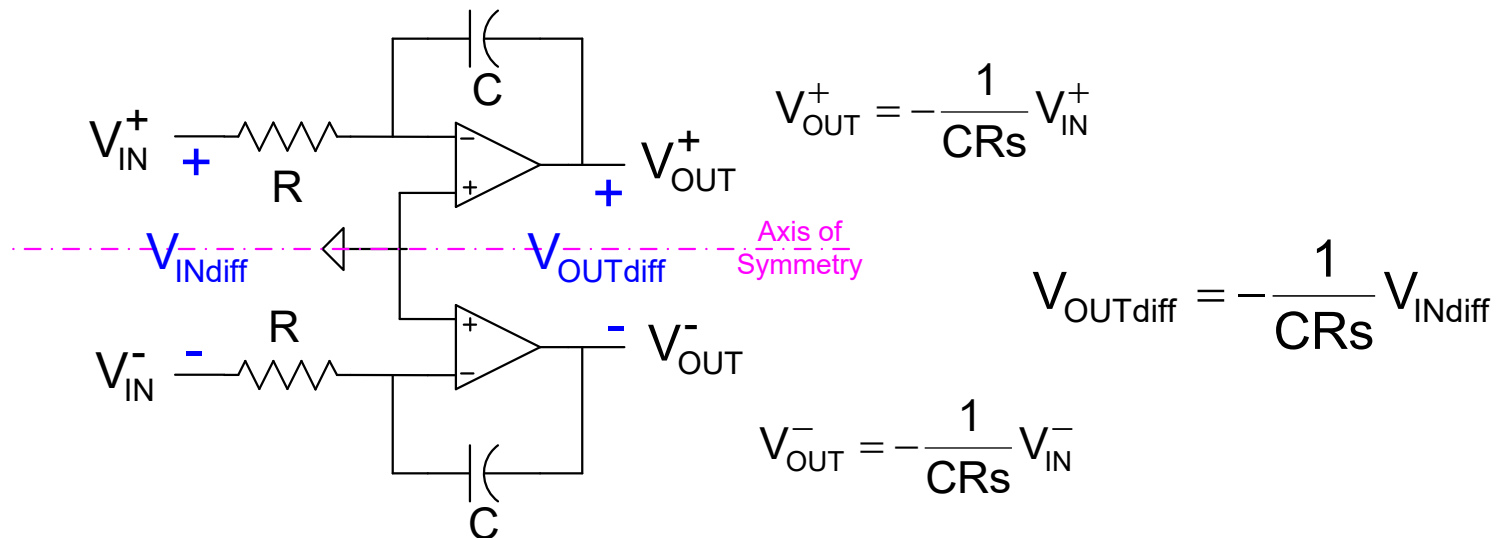


Balanced Differential Inverting Integrator
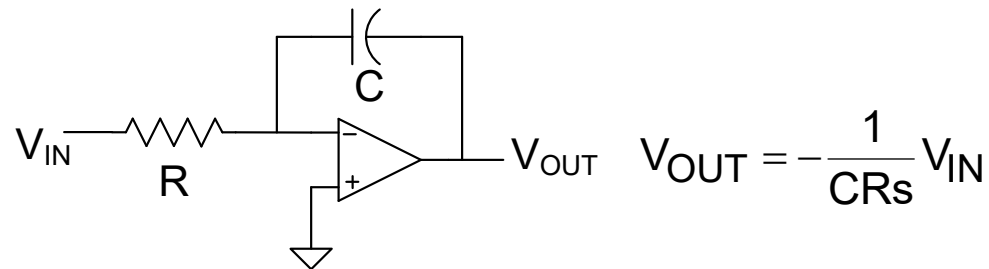
## Example – Basic Op-Amp Feedback Integrator Family




Inverting Integrator of Family

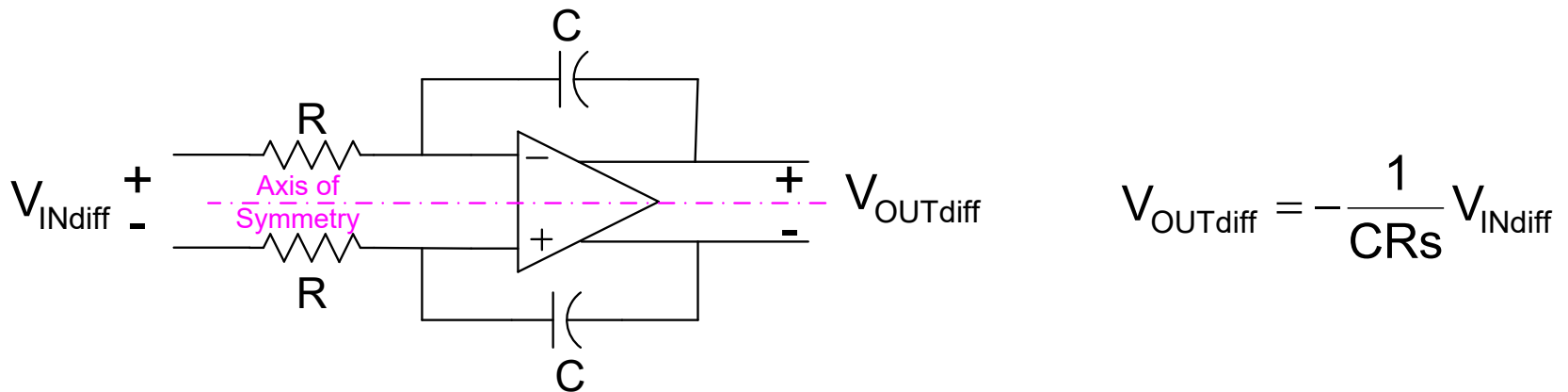


Fully Differential Inverting Integrator

Note distinction between fully balanced and fully differential structures !


# Integrator Types

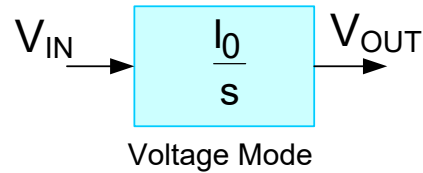


$$V_{OUT} = \frac{I_0}{s} V_{IN}$$

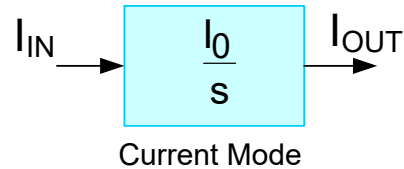

$$I_{OUT} = \frac{I_0}{s} I_{IN}$$

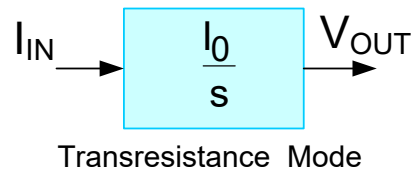

$$V_{OUT} = \frac{I_0}{s} I_{IN}$$

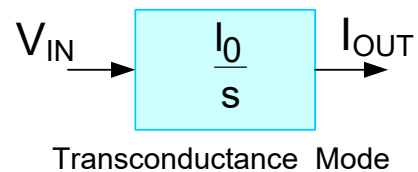

$$I_{OUT} = \frac{I_0}{s} V_{IN}$$

Will consider first the Voltage Mode type of integrators



# Voltage Mode Integrators

→ Active RC (Feedback-based)

- MOSFET-C (Feedback-based)

- OTA-C

- TA-C

} Sometimes termed “current mode”


- Other Continuous-time Structures

- Switched Capacitor

- Switched Resistor

} Discrete Time

# Active RC voltage Mode Integrator

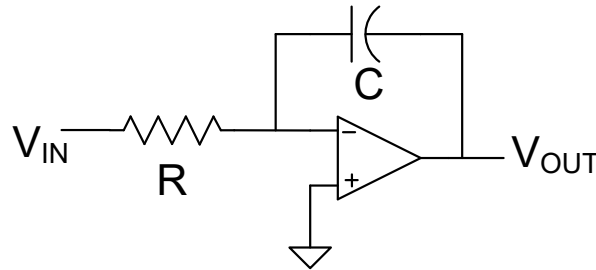


$$V_{OUT} = -\frac{1}{CRs} V_{IN}$$

- Limited to low frequencies because of Op Amp limitations
- No good resistors for monolithic implementations
  - Area for passive resistors is too large at low frequencies
  - Some recent work by Haibo Fei shows promise for some audio frequency applications
- Capacitor area too large at low frequencies for monolithic implementations
- Active devices are highly temperature dependent, proc. dependent, and nonlinear
- No practical tuning or trimming scheme for integrated applications with passive resistors

# Voltage Mode Integrators

- Active RC (Feedback-based)
  - • MOSFET-C (Feedback-based)
  - OTA-C
  - TA-C
- } Sometimes termed “current mode”
- Other Continuous-time Structures
  - Switched Capacitor
  - Switched Resistor
- } Discrete Time

# MOSFET-C Voltage Mode Integrator


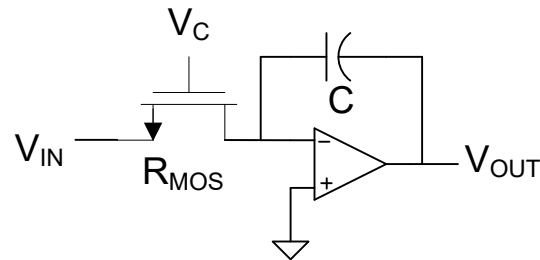


$$V_{OUT} = -\frac{1}{CR_{MOS}S} V_{IN}$$

- Limited to low frequencies because of Op Amp limitations
- Area for  $R_{MOS}$  is manageable !
- Active devices are highly temperature dependent, process dependent
- Potential for tuning with  $V_C$
- Highly Nonlinear (can be partially compensated with cross-coupled input)

A Solution without a Problem

# MOSFET-C Voltage Mode Integrator

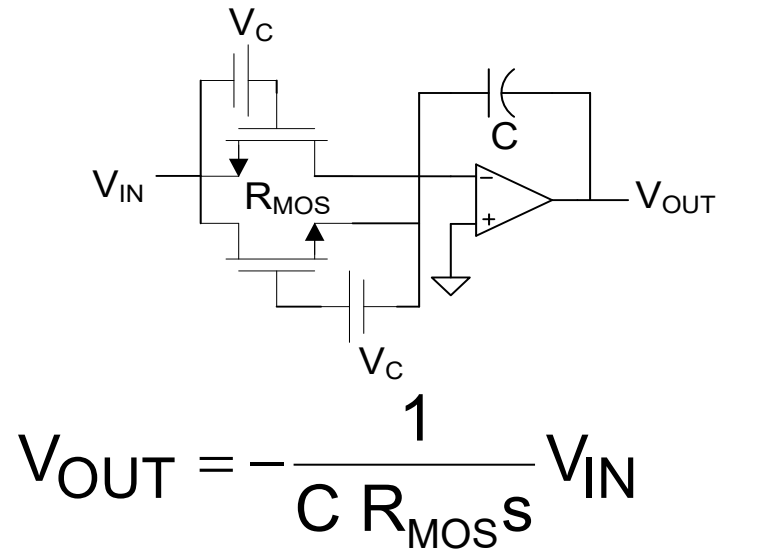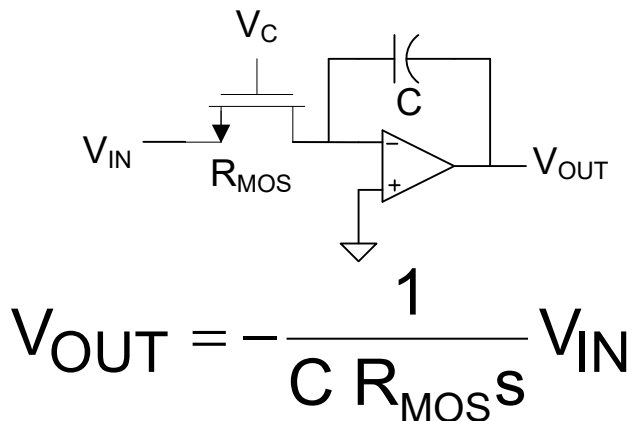


- Improved Linearity
- Some challenges for implementing  $V_C$

Still A Solution without a Problem

# Voltage Mode Integrators


- Active RC (Feedback-based)
  - MOSFET-C (Feedback-based)
  - OTA-C
  - TA-C
- } Sometimes termed “current mode”
- Other Continuous-time Structures
  - Switched Capacitor
  - Switched Resistor
- } Discrete Time

# OTA-C Voltage Mode Integrator

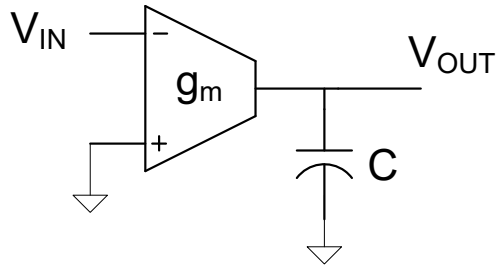

$$V_{OUT} = -\frac{g_m}{sC} V_{IN}$$

Inverting

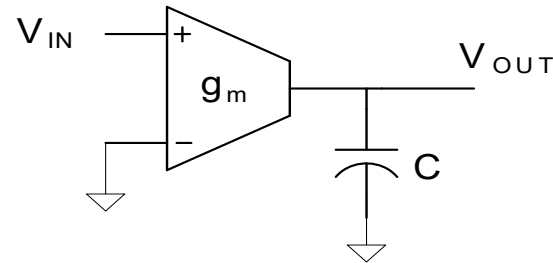


$$V_{OUT} = \frac{g_m}{sC} V_{IN}$$

Noninverting


- Requires only two components
- Inverting and Noninverting structures of same complexity
- Good high-frequency performance
- Small area
- Linearity is limited (no feedback in integrator)
- Susceptible to process and temperature variations
- Tuning control can be readily added

Widely used in high frequency applications

# OTA-C Voltage Mode Integrator

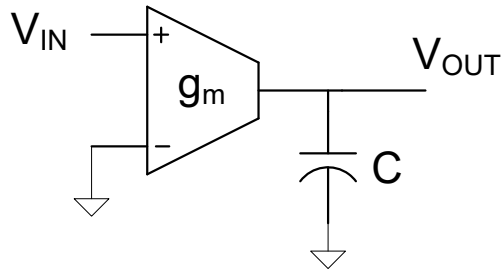

$$V_{OUT} = \frac{g_m}{sC} V_{IN}$$

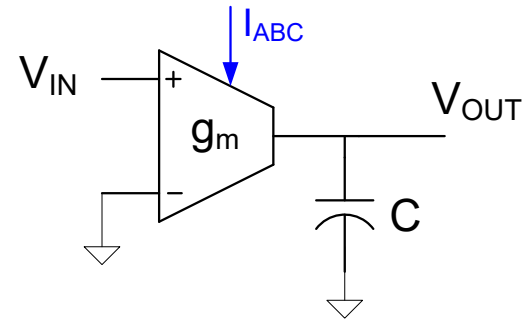


$$V_{OUT} = \frac{g_m}{sC} V_{IN}$$

$$g_m = f(I_{ABC})$$


Programmable Integrator



# OTA-C Voltage Mode Integrator

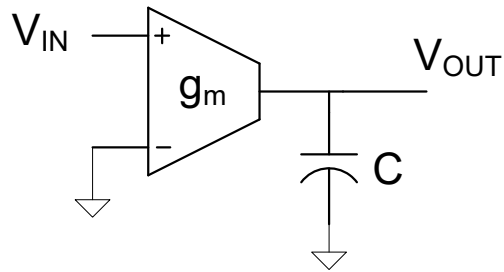

$$V_{OUT} = \frac{g_m}{sC} V_{IN}$$

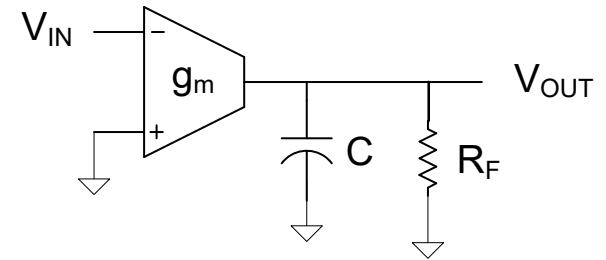


$$\frac{V_{OUT}(s)}{V_{IN}(s)} = \frac{g_m R_F}{1 + s(R_F C)}$$

Lossy Integrator

But  $R_F$  is typically too large for integrated applications

# OTA-C Voltage Mode Integrator

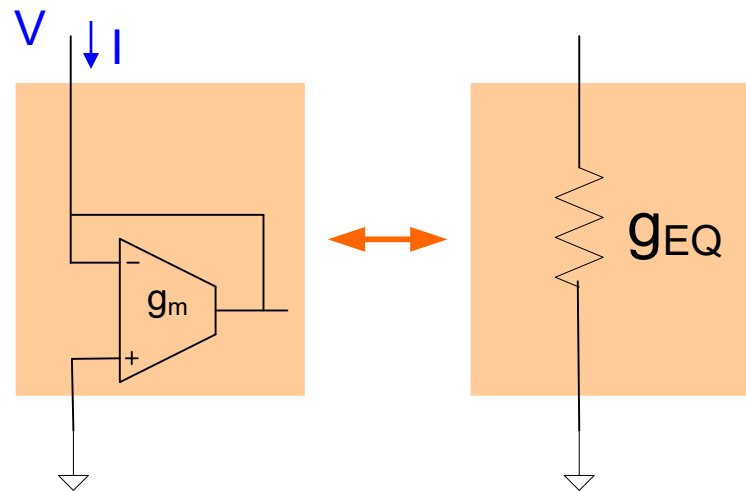


$$I = -g_m V$$

$$g_{EQ} = \frac{I}{V}$$


$$g_{EQ} = g_m$$

OTA is generally much smaller than a resistor

# OTA-C Voltage Mode Integrator

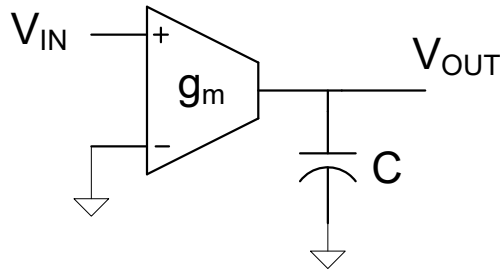

$$V_{OUT} = \frac{g_m}{sC} V_{IN}$$

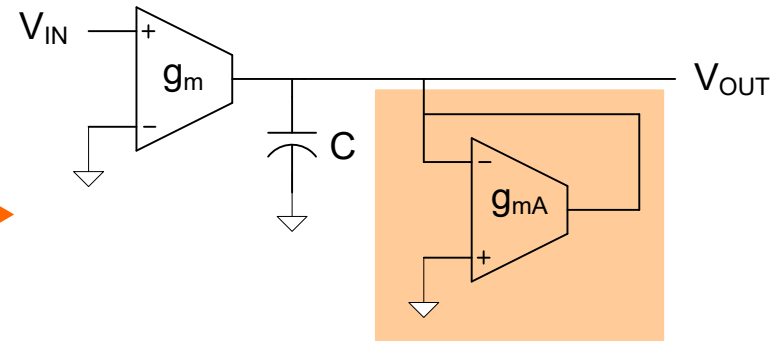


$$\frac{V_{OUT}(s)}{V_{IN}(s)} = \frac{g_m/g_{mA}}{1+s(C/g_{mA})}$$


Lossy Integrator

- Practical implementation
- Both OTAs can be readily programmable

# OTA-C Voltage Mode Integrator

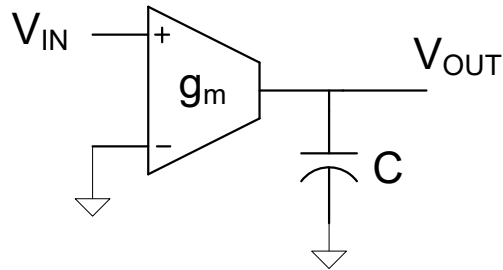

$$V_{OUT} = \frac{g_m}{sC} V_{IN}$$


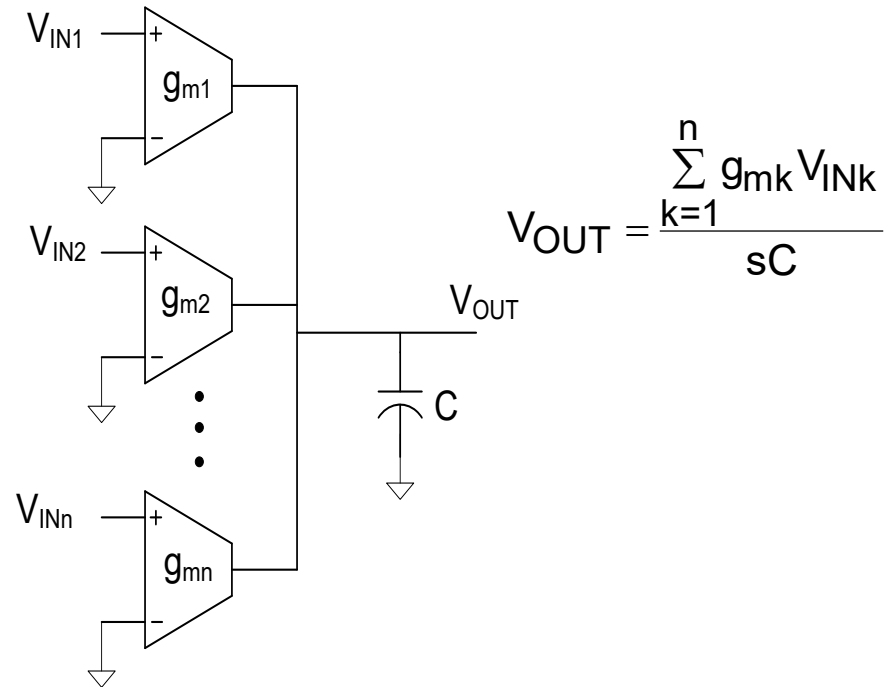


$$V_{OUT} = \frac{\sum_{k=1}^n g_{mk} V_{INk}}{sC}$$

Summing Integrator

- Inverting and noninverting functions can be combined in single summer
- All transconductance gains can be programmable

# OTA Architecture

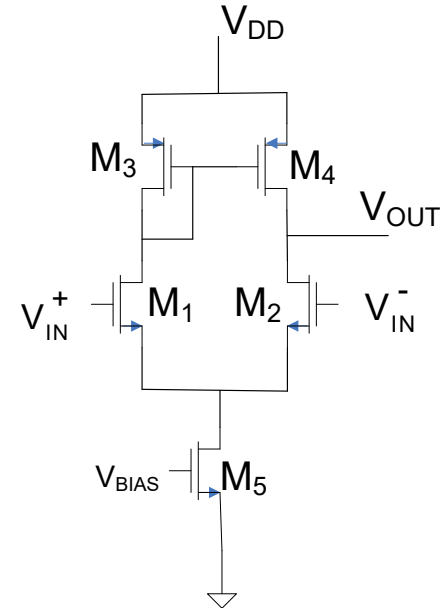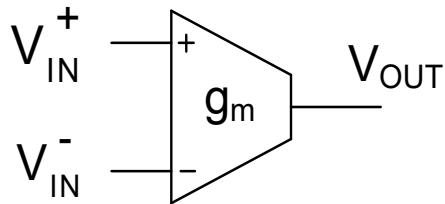

Mid-complexity OTA

- $M_1$  and  $M_2$  matched
- $M_2$  and  $M_4$  matched
- Define  $M$  to be the gain of the current mirror formed with  $M_2$  and  $M_4$
- $g_m$  programmable with  $V_{BIAS}$

$$g_m = \frac{g_{m1}}{2} (1+M)$$

Often  $M=1$


$$g_m = g_{m1}$$

Other OTAs exist, considerable effort expended over past two decades on OTA design


# Voltage Mode Integrators

- Active RC (Feedback-based)
  - MOSFET-C (Feedback-based)
  - OTA-C
  - TA-C
- } Sometimes termed “current mode”
- Other Continuous-time Structures
  - Switched Capacitor
  - Switched Resistor
- } Discrete Time

# TA-C Voltage Mode Integrator

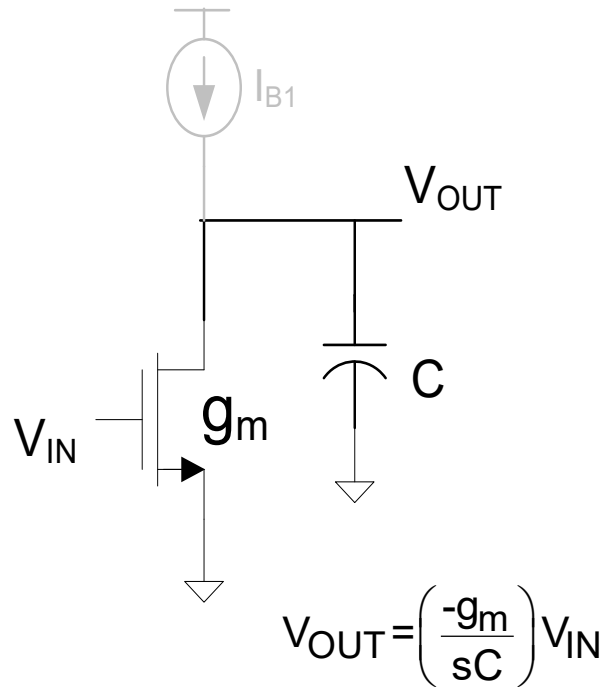

Inverting Integrator

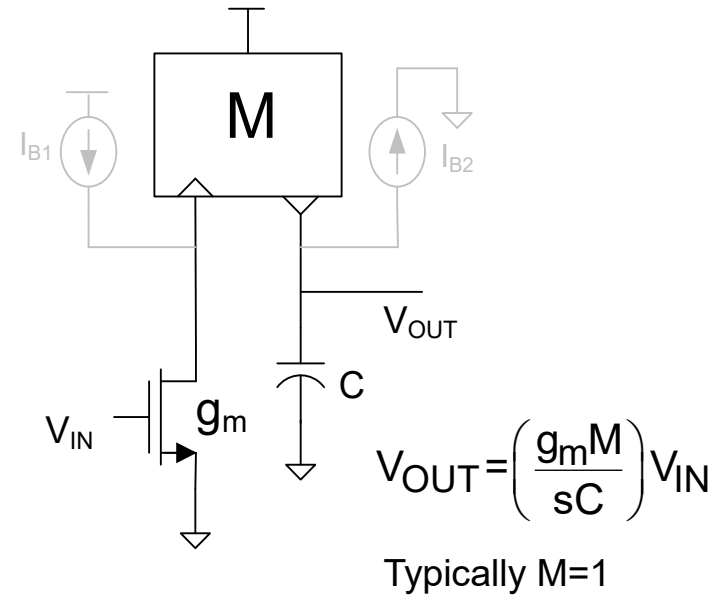


Noninverting Integrator

- Can operate at very high frequencies
- Low device count circuit
- Simplicity is important for operating at very high frequencies
- $I_0$  is process and temperature dependent
- Linearity is limited


# TA-C Voltage Mode Integrator

Some other perspectives

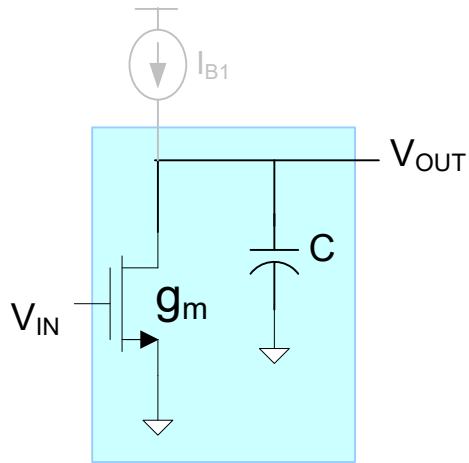

n-channel input
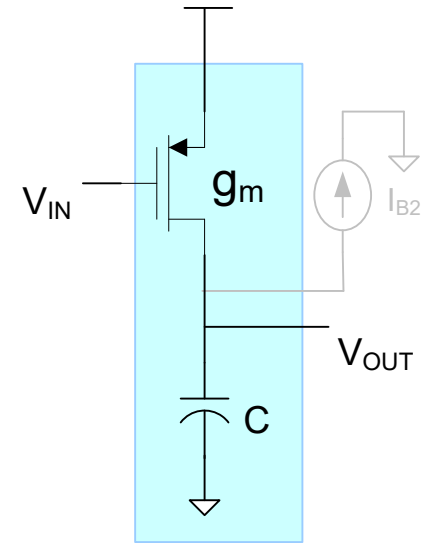
$$V_{OUT} = \left( \frac{-g_m}{sC} \right) V_{IN}$$




p-channel input

Inverting Integrators



# TA-C Voltage Mode Integrator


Some other perspectives

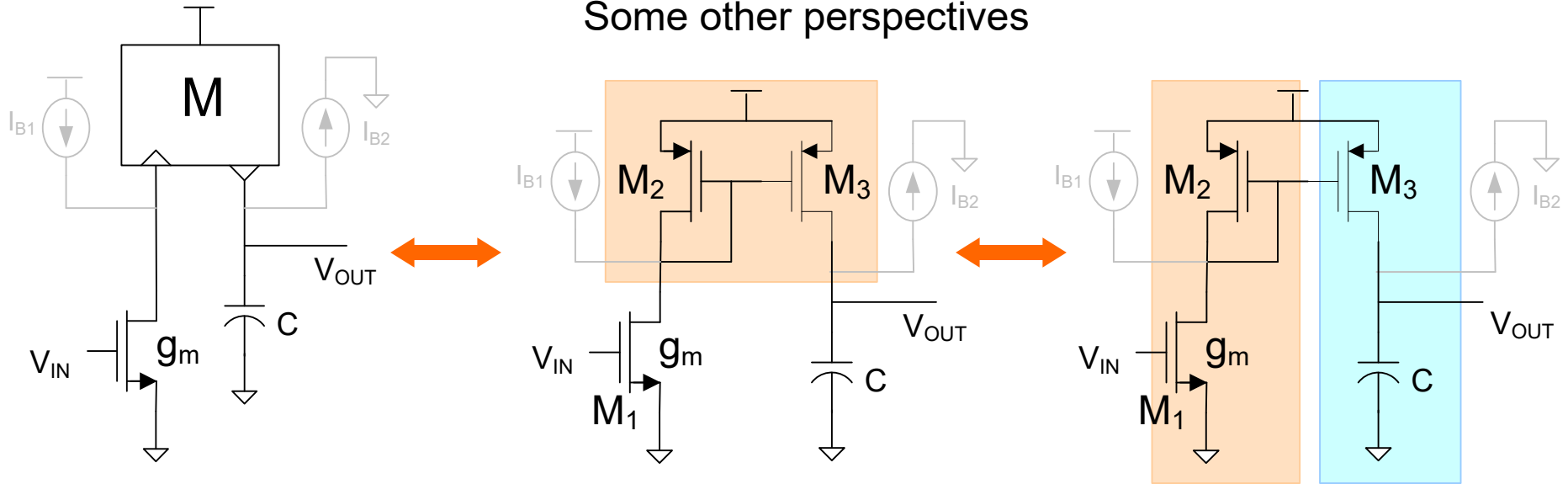


Noninverting Integrator

Can be viewed either as n-channel input with current mirror or as low-gain inverter driving a p-channel input inverting integrator

# TA-C Voltage Mode Integrator

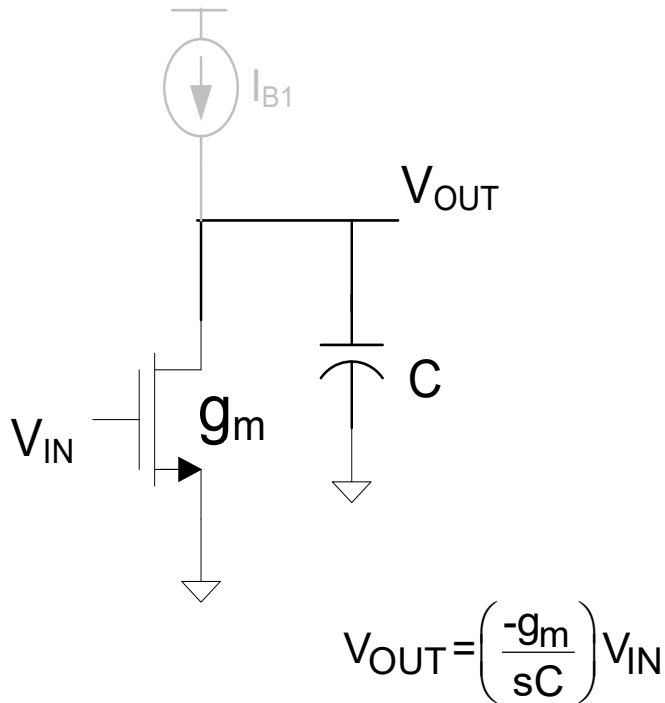


Inverting Integrator

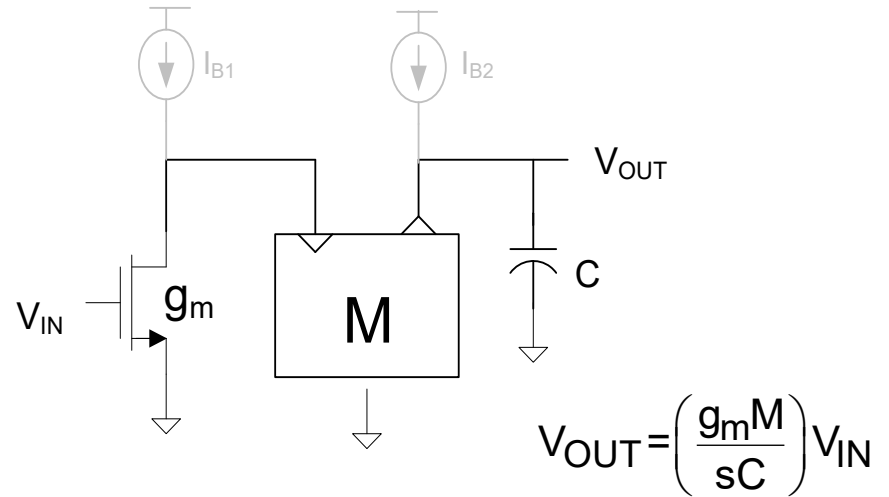

Typically  $M=1$

Alternate noninverting Integrator

# TA-C Voltage Mode Integrator

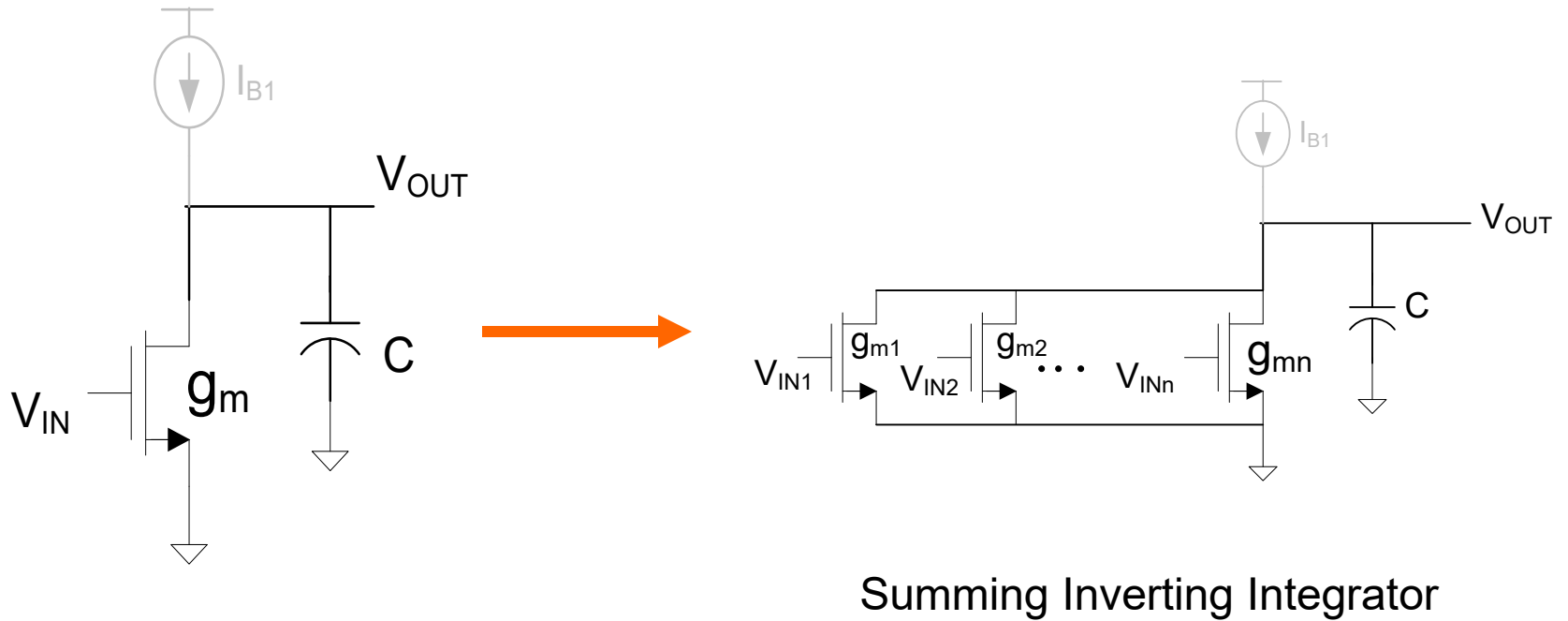


# Voltage Mode Integrators

- Active RC (Feedback-based)
  - MOSFET-C (Feedback-based)
  - OTA-C
  - TA-C
- } Sometimes termed “current mode”

## → Other Continuous-time Structures

- Switched Capacitor
  - Switched Resistor
- } Discrete Time

# Another Voltage Mode Integrator

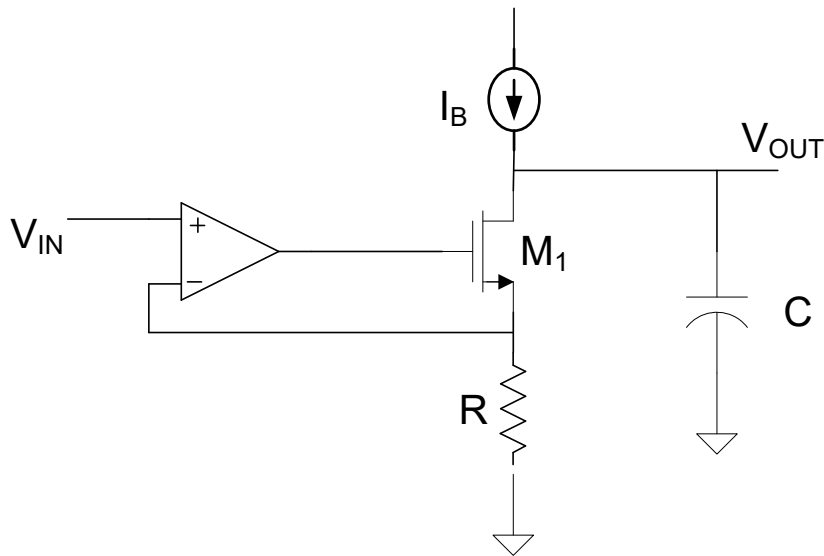


$$V_{OUT} = \left( \frac{-1}{sRC} \right) V_{IN}$$

Inverting Integrator


- **Infinite input impedance (in contrast to basic Active RC Integrator)**
- **Both R and C have one terminal grounded**
- **Requires integrated process**
- **Accuracy limited by process and temperature**
- **Size limitations same as basic Active RC Integrator**
- **Limited to lower frequencies because of Op Amp**
- **Good linearity**

# Another Voltage Mode Integrator

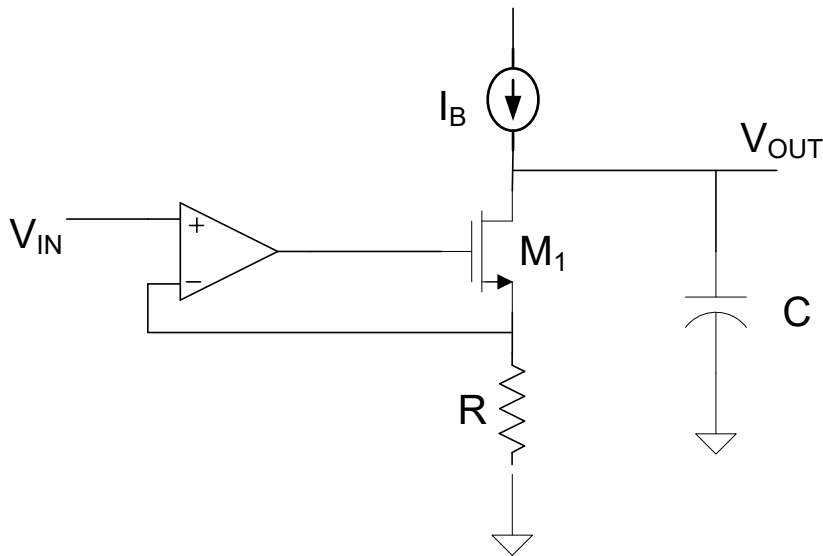

Inverting Integrator

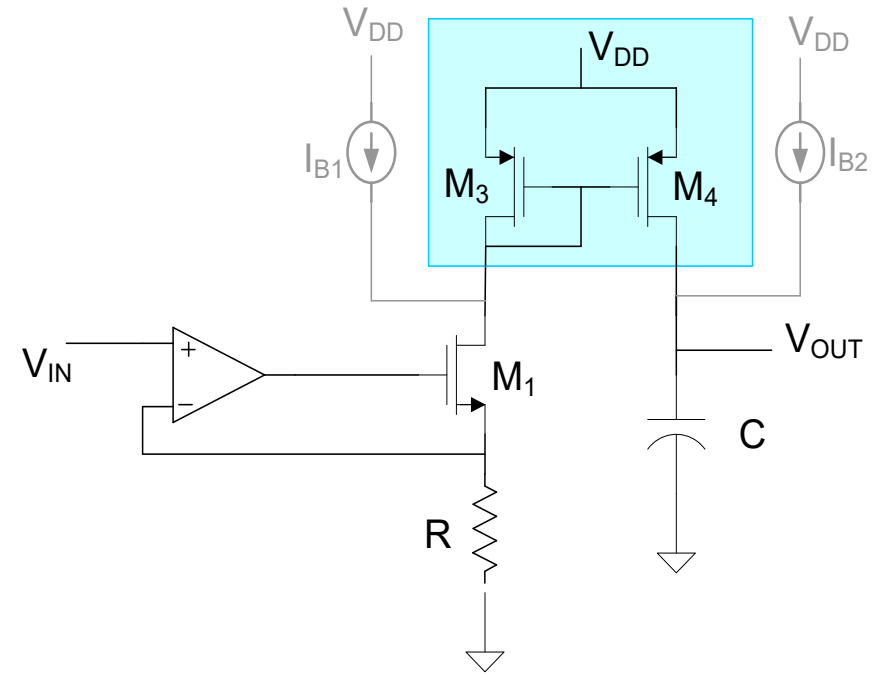
$$V_{OUT} = \left( \frac{-1}{sRC} \right) V_{IN}$$



Noninverting Integrator

$$V_{OUT} = \left( \frac{1}{sRC} \right) V_{IN}$$


# Another Voltage Mode Integrator

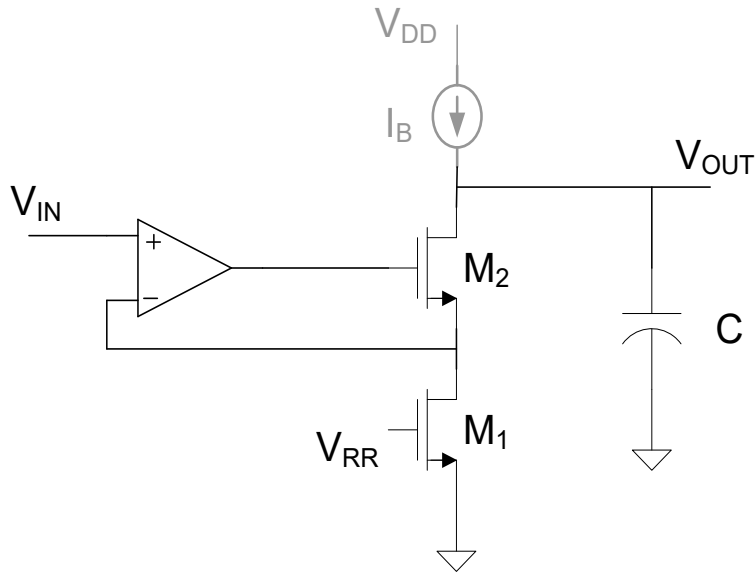

Inverting Integrator

$$V_{OUT} = \left( \frac{-1}{sR_{FET}C} \right) V_{IN}$$

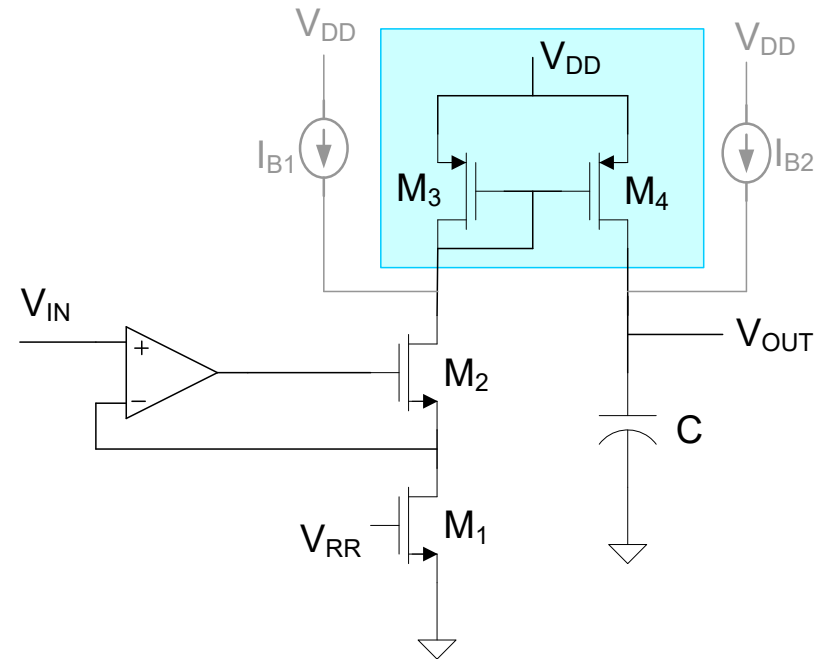
- $M_1$  in triode region
- Reduces Area Concerns but Loss of Linearity
- $I_0$  is programmable with  $V_{RR}$
- Accurate control of  $I_B$  critical



Noninverting Integrator


$$V_{OUT} = \left( \frac{1}{sR_{FET}C} \right) V_{IN}$$
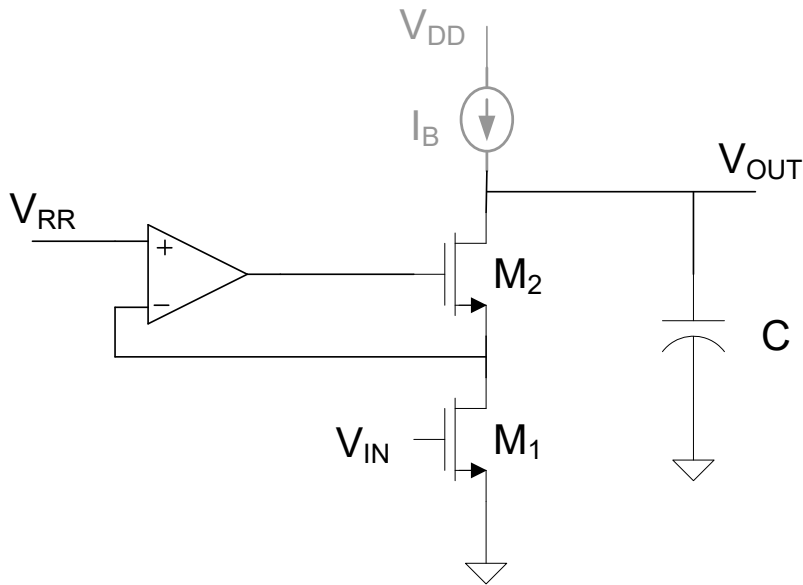
# Regulated Cascode Voltage Mode Integrator



Inverting Integrator
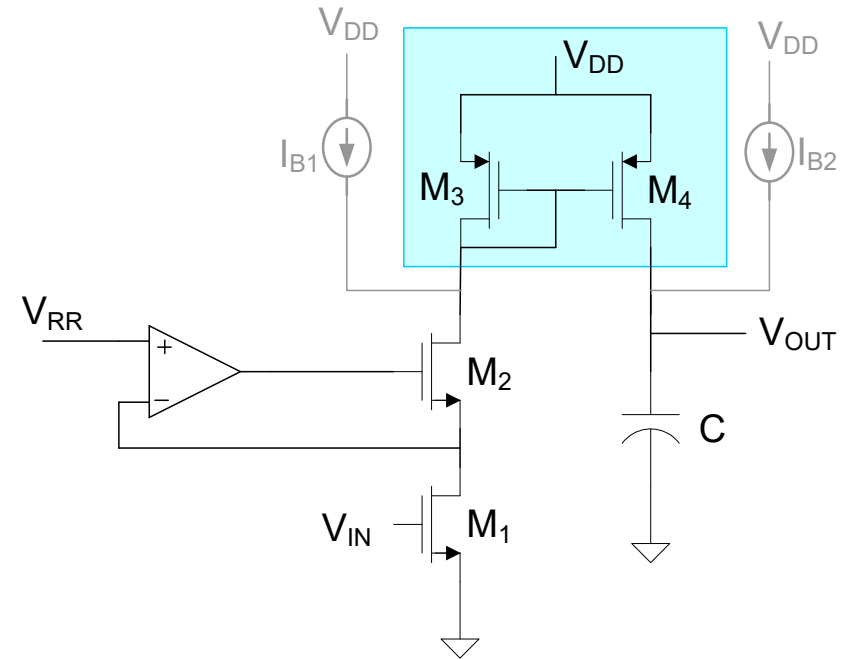
$$V_{OUT} = \left( \frac{-g_{mT}}{sC} \right) V_{IN}$$



Noninverting Integrator


$$V_{OUT} = \left( \frac{g_{mT}}{sC} \right) V_{IN}$$

$g_{mT}$  is triode region transconductance of  $M_1$

- $M_1$  operating in triode region
- $R_{FET}$  programmable with  $V_{RR}$
- Very good linearity properties
- Input impedance still infinite


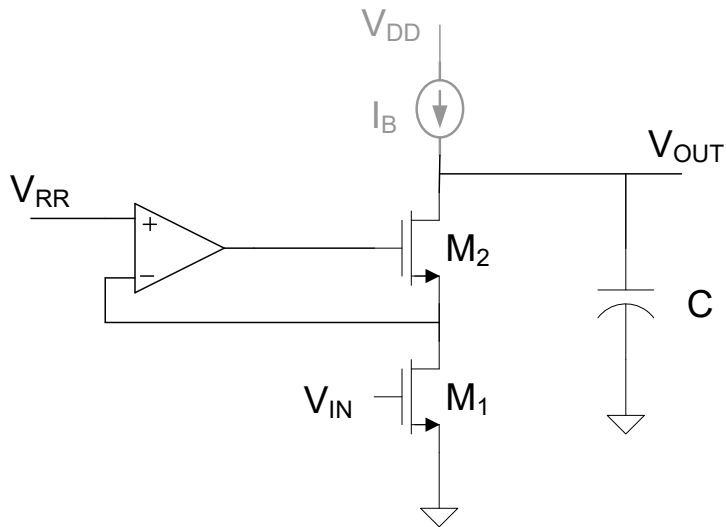
# Regulated Cascode Voltage Mode Integrator



$$V_{OUT} = \left( \frac{-g_{mT}}{sC} \right) V_{IN}$$

Linearity Properties:

Assuming square-law triode model


$$I_{D1} = \frac{\mu C_{OX} W}{L} \left( V_{GS} - V_T - \frac{V_{RR}}{2} \right) V_{RR}$$

$$I_{D1} = \left[ \frac{\mu C_{OX} W}{L} V_{RR} \right] V_{IN} + \left[ \frac{\mu C_{OX} W}{L} \left( V_T + \frac{V_{RR}}{2} \right) V_{RR} \right]$$

Note linear dependence on  $V_{IN}$


$$g_{mT} = \left[ \frac{L}{\mu C_{OX} W V_{RR}} \right]$$
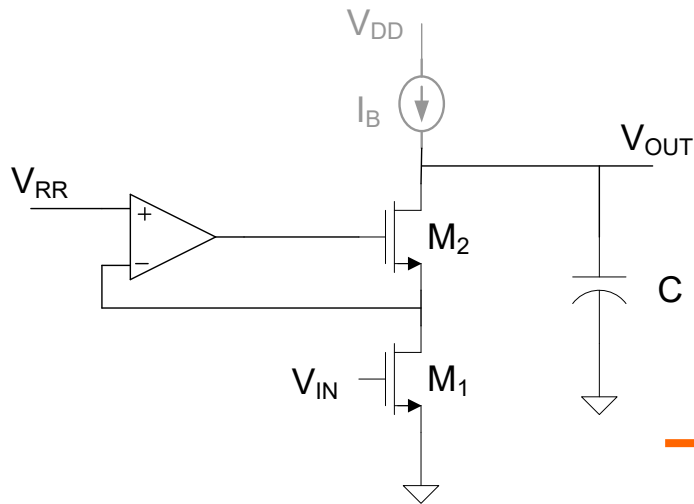
# Regulated Cascode Voltage Mode Integrator




Inverting Integrator
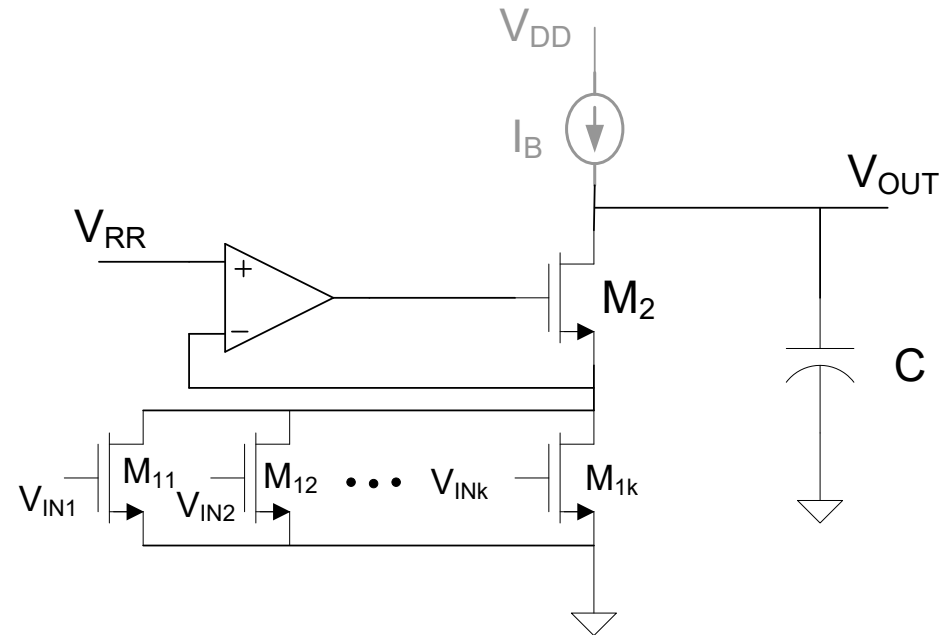
$$V_{OUT} = \left( \frac{-1}{sR_{FET}C} \right) V_{IN}$$




- **Multiple inputs require single additional transistor**
- **Accurate ratioing of gains practical**
- **Can also sum currents on C**
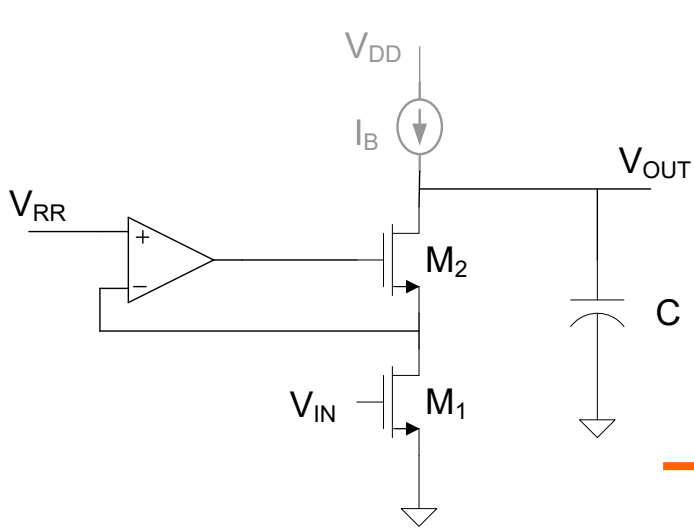
# Regulated Cascode Voltage Mode Integrator



Inverting Integrator
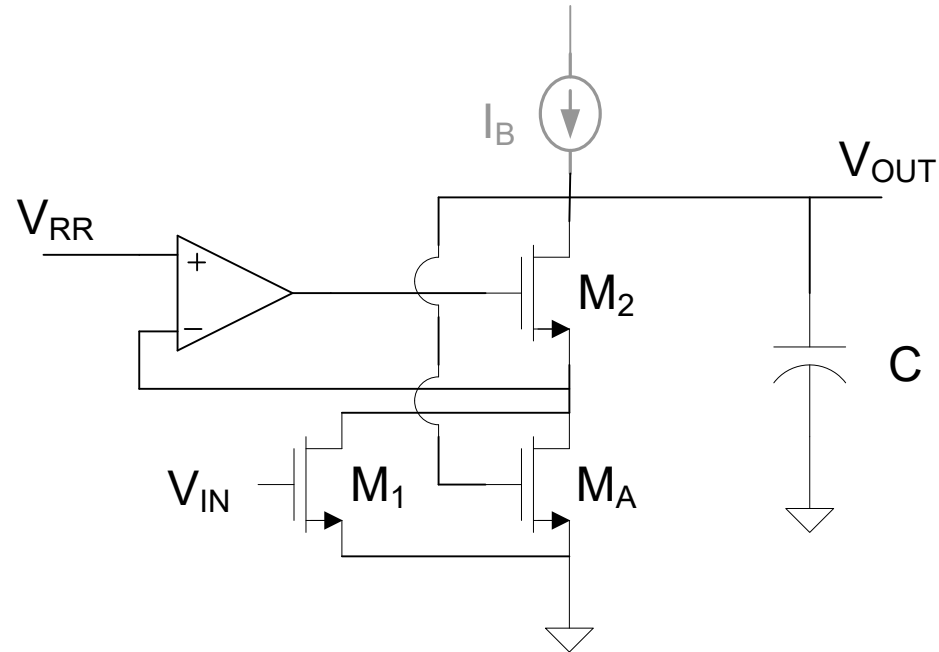
$$V_{OUT} = \left( \frac{-1}{sR_{FET}C} \right) V_{IN}$$



Inverting Lossy Integrator



Stay Safe and Stay Healthy !

**End of Lecture 24**