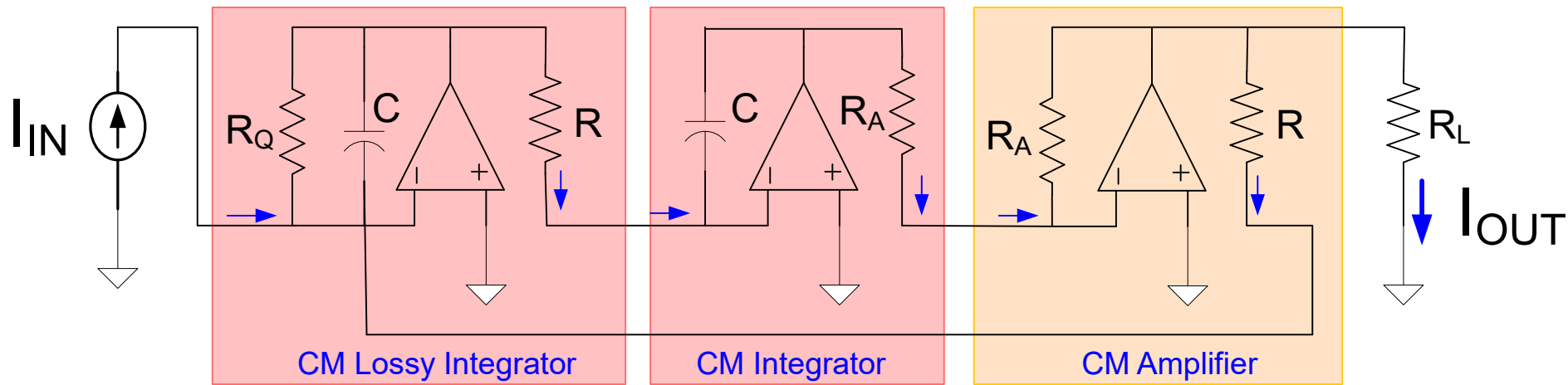


# EE 508

## Lecture 30

Switched-Current Integrators  
Leapfrog filters

# Current-Mode Two Integrator Loop






- Straightforward implementation of the two-integrator loop
- Simple structure

Review from last time

# Current-Mode Two Integrator Loop

An Observation:

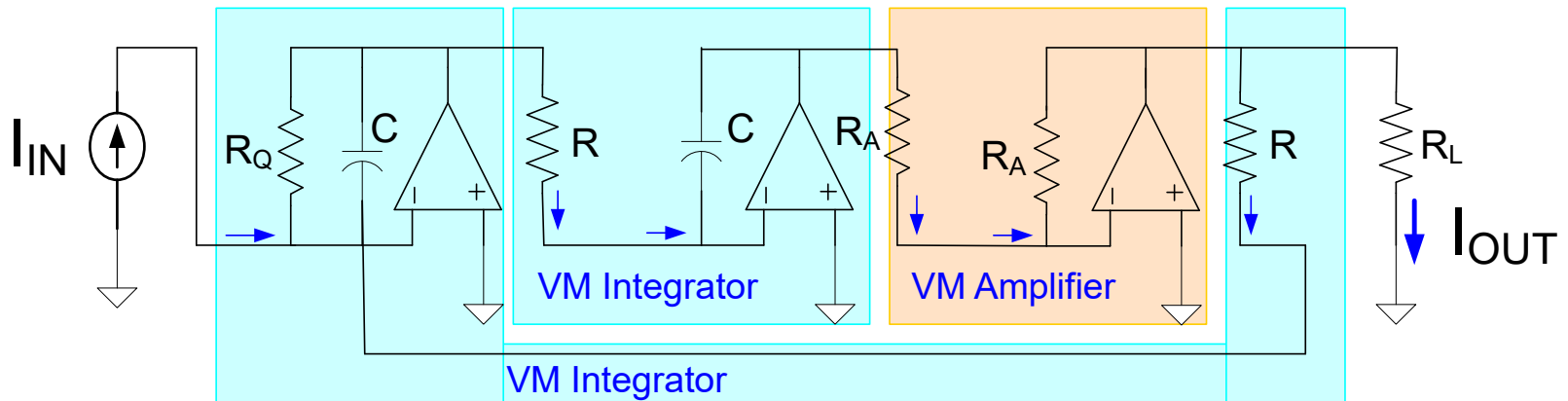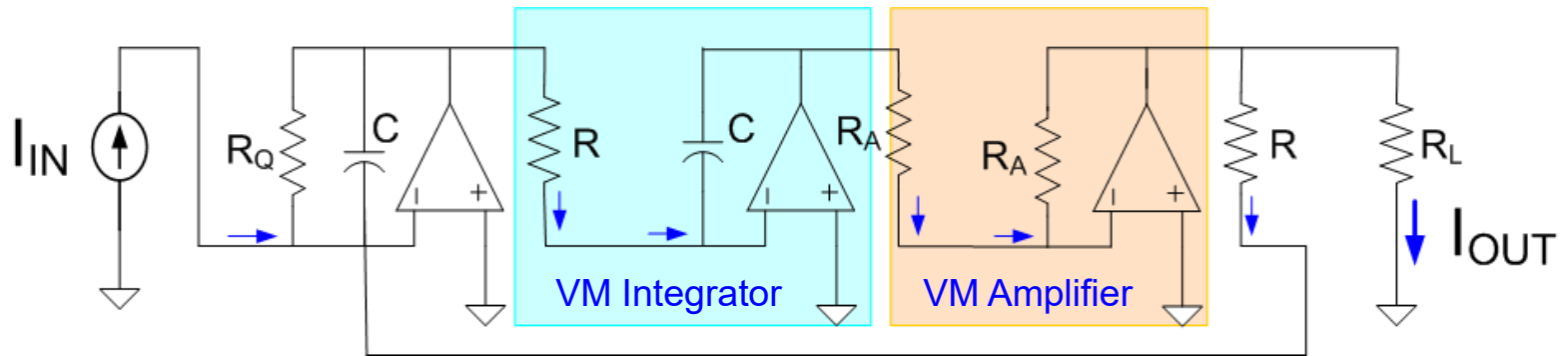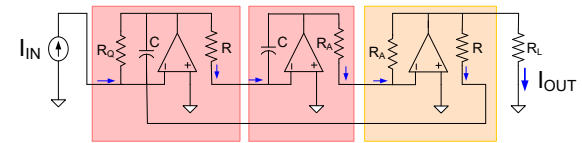


This circuit is identical to another one with two voltage-mode integrators and a voltage-mode amplifier !

Review from last time

# Switched-Current Filters

Basic idea introduced by Hughes and Bird at ISCAS 1989

$$I_{OUT}(nT) = A I_{IN}(nT-T)$$

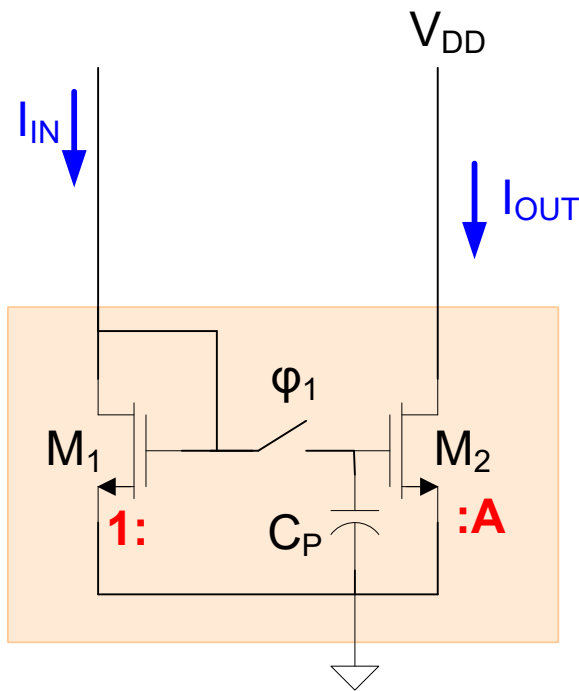

$C_p$  is parasitic gate capacitance on  $M_2$

Very low power dissipation

Potential to operate at very low voltages


Potential for accuracy of a SC circuit at both low and high frequencies but without the Op Amp and large C ratios

Neither capacitor or resistor values needed to do filtering!

A completely new approach to designing filters that offers potential for overcoming most of the problems plaguing filter designers for decades!

Before developing Switch-Current concept, need to review background information in s to z domain transformations

# s-domain to z-domain transformations

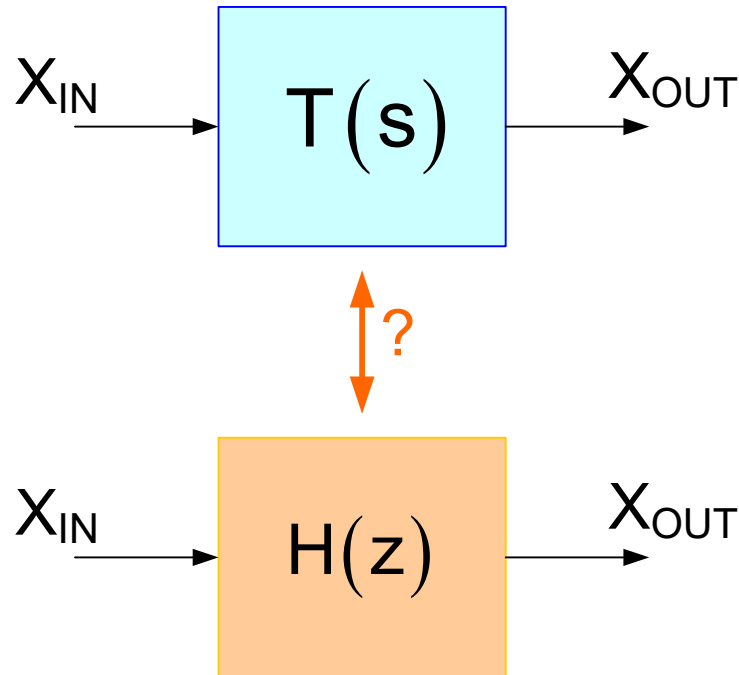


For a given  $T(s)$  would like to obtain a function  $H(z)$  or for a given  $H(z)$  would like to obtain a  $T(s)$  such that preserves the magnitude and phase response

Mathematically, would like to obtain the relationship:

$$T(s) \Big|_{s=j\omega} = H(z) \Big|_{z=e^{j\omega T}}$$

# s-domain to z-domain transformations

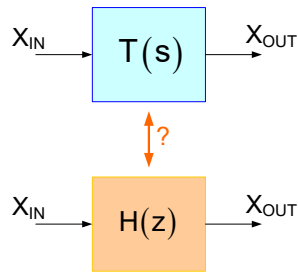

## Three Popular Transformations

$$s = \frac{z-1}{T}$$

Forward Euler

$$s = \frac{1-z^{-1}}{Tz^{-1}}$$

$$s = \frac{z-1}{Tz}$$

Backward Euler

$$s = \frac{1-z^{-1}}{T}$$


$$s = \frac{2}{T} \cdot \frac{z-1}{z+1}$$

Bilinear z  
transform

$$s = \frac{2}{T} \cdot \frac{1-z^{-1}}{1+z^{-1}}$$

- Transformations of standard approximations in s-domain are the corresponding transformations in the z-domain
- Transformations are not unique
- Transformations cause warping of the imaginary axis and may cause change in basic shape
- Transformations do not necessarily guarantee stability
- These transformations preserve order

# z-domain integrators

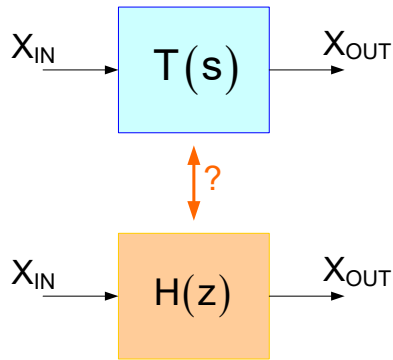

$$T(s) = \frac{I_0}{s}$$

## Some z-domain integrators

$$H(z) = \begin{cases} \frac{TI_0}{z-1} & \text{Forward Euler} \\ \frac{I_0 Tz}{z-1} & \text{Backward Euler} \\ \frac{TI_0}{2} \left( \frac{z+1}{z-1} \right) & \text{Bilinear z} \end{cases}$$

Three Popular Transformations

$$s = \frac{z-1}{T}$$

Forward Euler

$$s = \frac{1-z^{-1}}{Tz^{-1}}$$

$$s = \frac{z-1}{Tz}$$

Backward Euler

$$s = \frac{1-z^{-1}}{T}$$

$$s = \frac{2}{T} \cdot \frac{z-1}{z+1}$$

Bilinear z transform

$$s = \frac{2}{T} \cdot \frac{1-z^{-1}}{1+z^{-1}}$$

## Corresponding difference equations:

$$V_{OUT}(nT+T) = TI_0 V_{IN}(nT) + V_{OUT}(nT)$$

Forward Euler


$$V_{OUT}(nT+T) = I_0 T V_{IN}(nT+T) + V_{OUT}(nT)$$

Backward Euler

$$V_{OUT}(nT+T) = \frac{TI_0}{2} (V_{IN}(nT+T) + V_{IN}(nT)) + V_{OUT}(nT)$$

Bilinear z

# z-domain lossy integrators

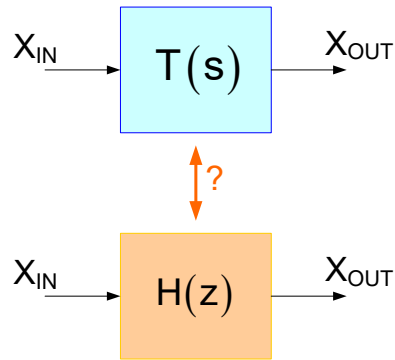

Some z-domain lossy integrators

$$T(s) = \frac{I_0}{s + \alpha}$$

$$H(z) = \begin{cases} \frac{TI_0}{z - 1 + \alpha T} & \text{Forward Euler} \\ \frac{I_0 T z}{z(1 + \alpha T) - 1} & \text{Backward Euler} \\ \frac{TI_0}{2} \left( \frac{z + 1}{z \left( 1 + \frac{\alpha T}{2} \right) + \left( \frac{\alpha T}{2} - 1 \right)} \right) & \text{Bilinear } z \end{cases}$$

Functional Form



Corresponding difference equations:

$$\begin{aligned} V_{\text{OUT}}(nT + T) &= G V_{\text{IN}}(nT) + H V_{\text{OUT}}(nT) && \text{Forward Euler} \\ H V_{\text{OUT}}(nT + T) &= G V_{\text{IN}}(nT + T) + V_{\text{OUT}}(nT) && \text{Backward Euler} \\ V_{\text{OUT}}(nT + T) &= G (V_{\text{IN}}(nT + T) + V_{\text{IN}}(nT)) + H V_{\text{OUT}}(nT) && \text{Bilinear } z \end{aligned}$$



# Switched-Current Integrator


Consider this circuit

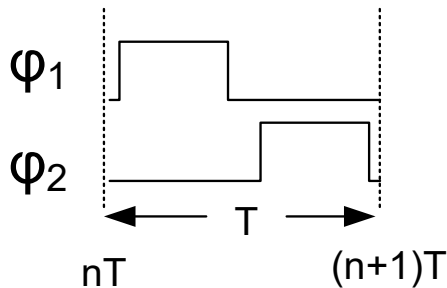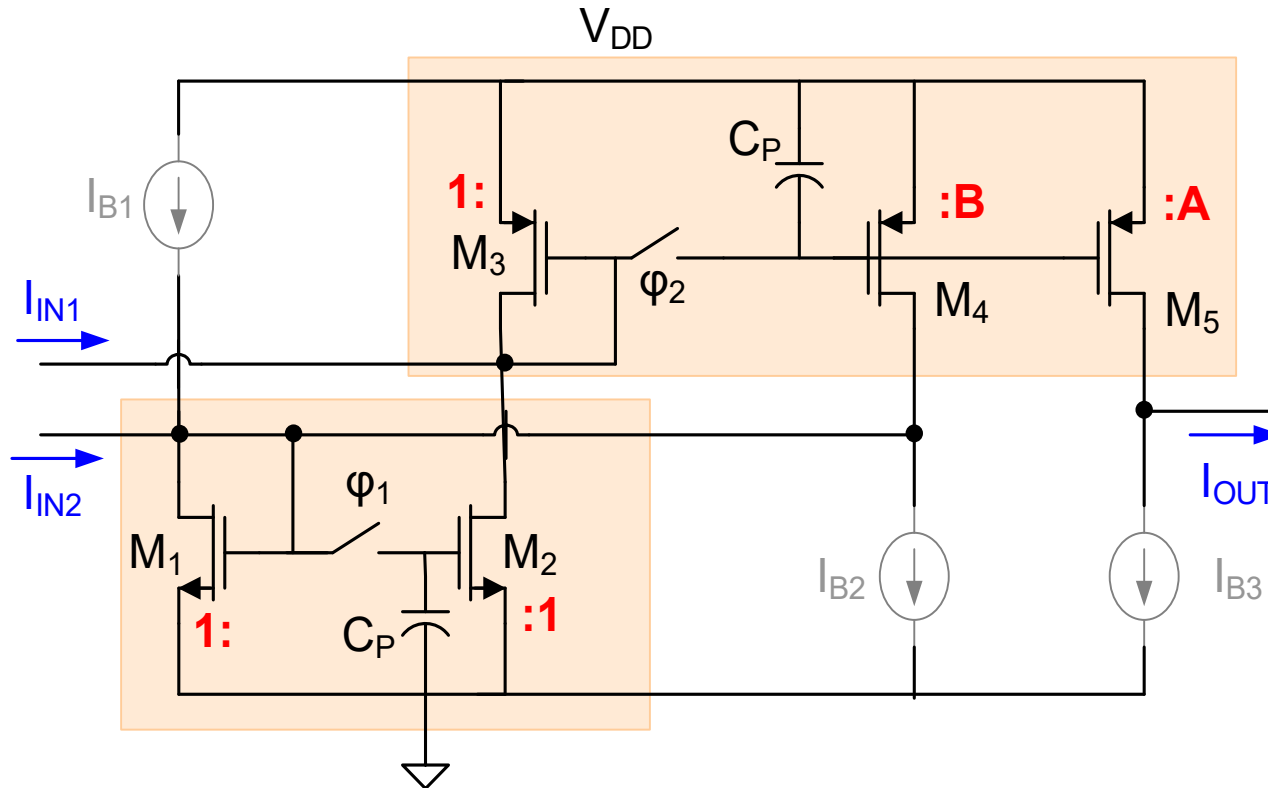

- Clocks complimentary, nonoverlapping
- Phase not critical

**Assume inputs change only during phase  $\Phi_2$**   
(may be outputs from other like stages)

# Switched-Current Integrator

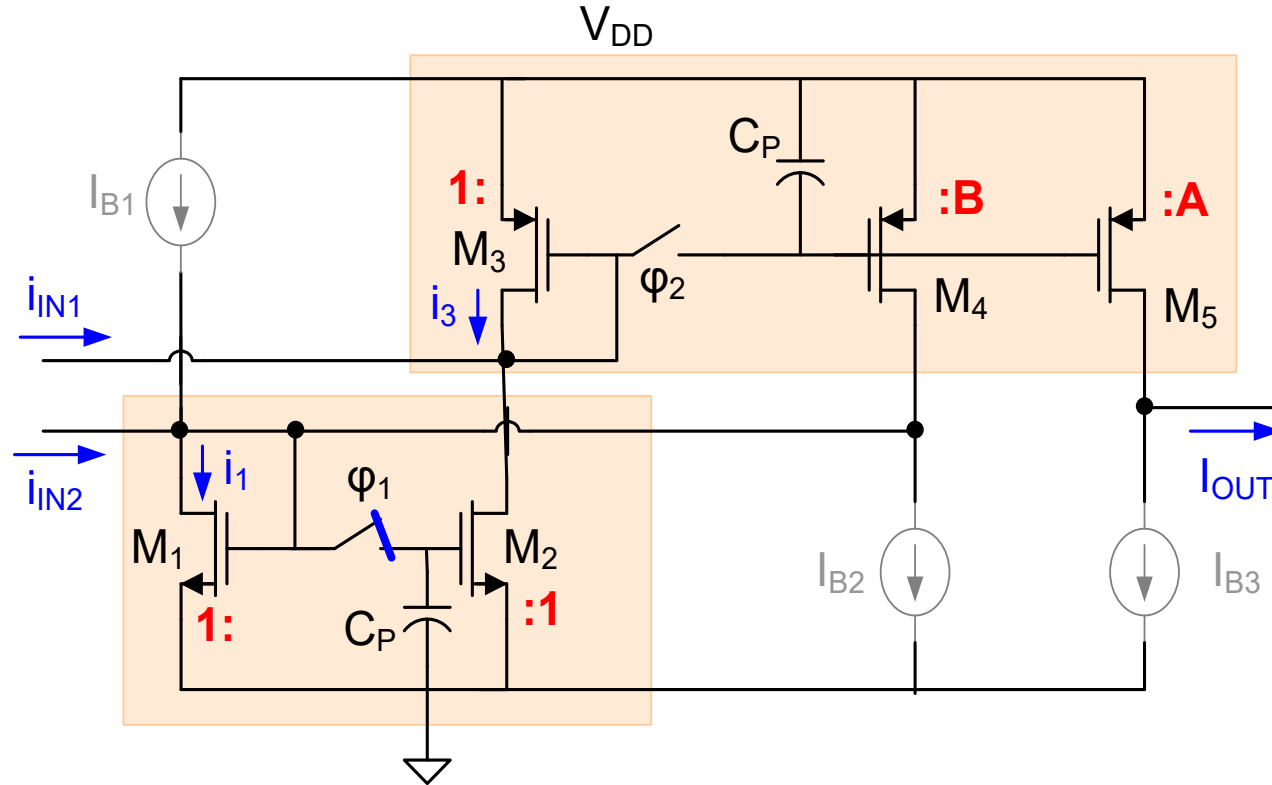


Consider  $\Phi_1$  closed,  $\Phi_2$  open ( $nT-T < t < nT-T/2$ )

$$i_1(t) = Bi_3(nT-T) + i_{iN2}(t)$$

Since current does not change during this interval

$$i_1(nT-T) = Bi_3(nT-T) + i_{iN2}(nT-T)$$

# Switched-Current Integrator

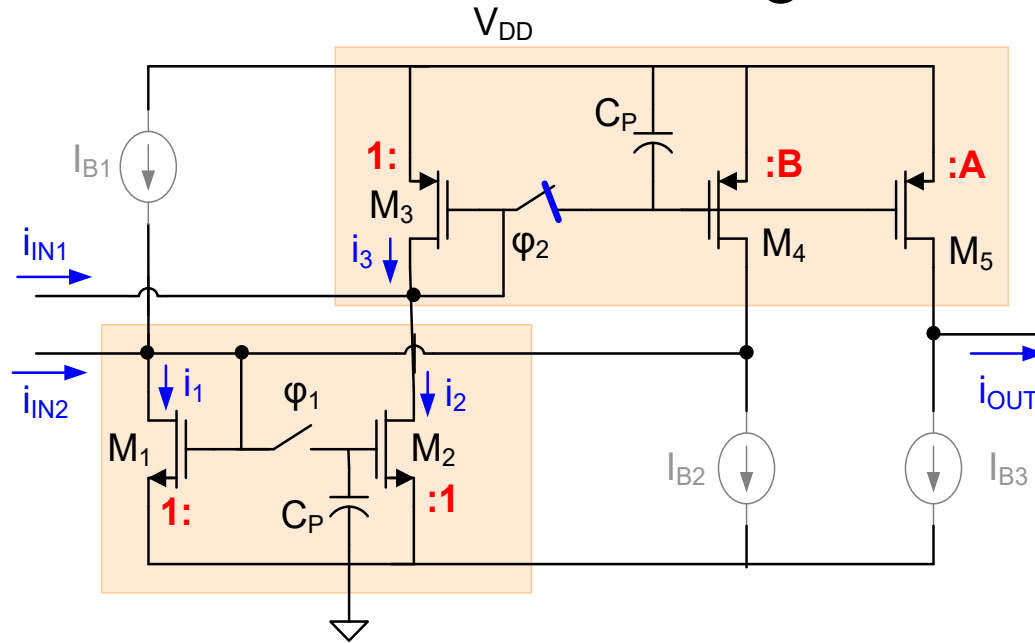

Consider  $\Phi_2$  closed,  $\Phi_1$  open ( $nT - T/2 < t < nT$ )

$$i_2(t) = i_1(nT - T)$$


$$i_2(t) = i_3(t) + i_{IN1}(t)$$

$$i_{OUT}(t) = Ai_3(t)$$

$$i_1(nT - T) = Bi_3(nT - T) + i_{IN2}(nT - T) \quad (\text{from first phase})$$

$$\left(\frac{1}{A}\right)i_{OUT}(t) + i_{IN1}(t) = \frac{B}{A}i_{OUT}(nT - T) + i_{IN2}(nT - T)$$

# Switched-Current Integrator

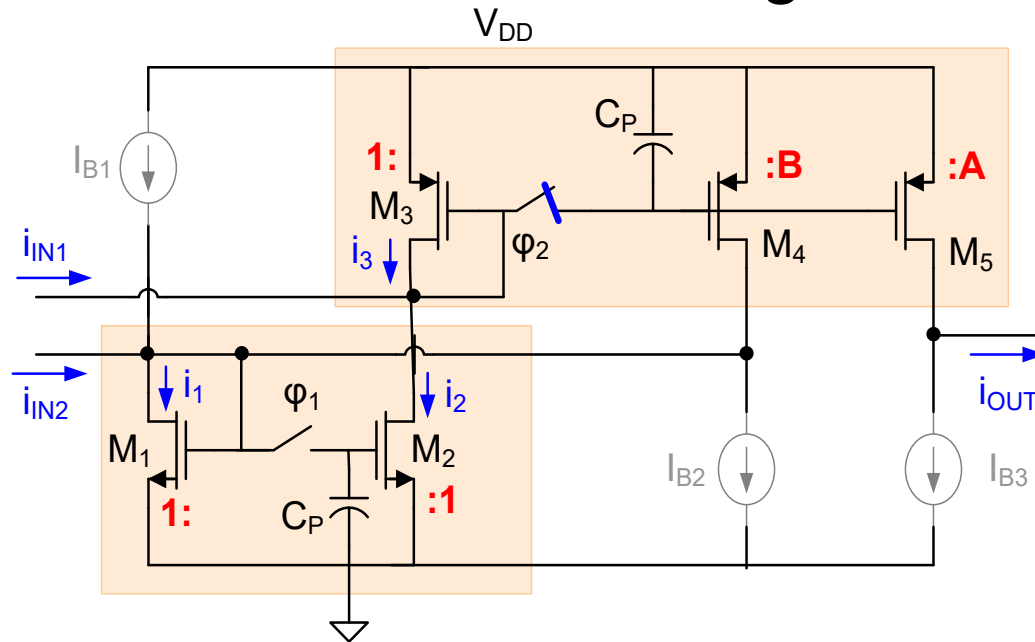

Consider  $\Phi_2$  closed,  $\Phi_1$  open ( $nT - T/2 < t < nT$ )

$$\left(\frac{1}{A}\right) i_{\text{OUT}}(t) + i_{\text{IN1}}(t) = \frac{B}{A} i_{\text{OUT}}(nT - T) + i_{\text{IN2}}(nT - T)$$



Evaluating at  $t = nT$ , we have

$$\left(\frac{1}{A}\right) i_{\text{OUT}}(nT) + i_{\text{IN1}}(nT) = \frac{B}{A} i_{\text{OUT}}(nT - T) + i_{\text{IN2}}(nT - T)$$

Taking z-transform, obtain

$$I_{\text{OUT}}(z) = \left(\frac{Az^{-1}}{1 - Bz^{-1}}\right) I_{\text{IN2}}(z) - \left(\frac{A}{1 - Bz^{-1}}\right) I_{\text{IN1}}(z)$$

# Switched-Current Integrator

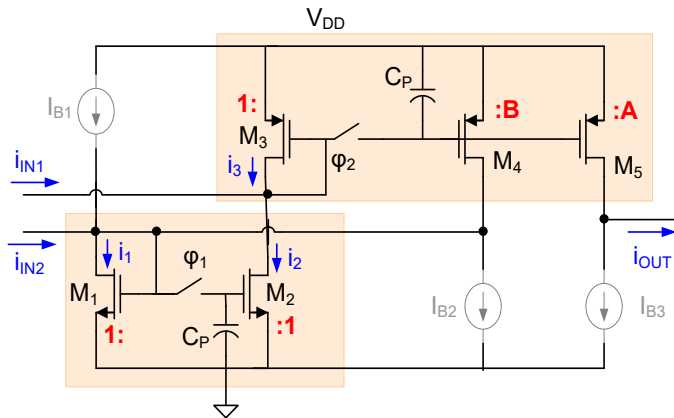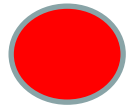

Recall lossy integrators:

$$H(z) = \begin{cases} \frac{Gz^{-1}}{1 - Hz^{-1}} & \text{Forward Euler} \\ \frac{G}{1 - Hz^{-1}} & \text{Backward Euler} \\ G \left( \frac{1 + z^{-1}}{1 - Hz^{-1}} \right) & \text{Bilinear } z \end{cases}$$

For H=1 becomes lossless


$$I_{OUT}(z) = \left( \frac{Az^{-1}}{1 - Bz^{-1}} \right) I_{IN2}(z) - \left( \frac{A}{1 - Bz^{-1}} \right) I_{IN1}(z)$$

If  $I_{IN1}=0$ , becomes Forward Euler integrator

If  $I_{IN2}=0$ , becomes Backward Euler integrator

If  $I_{IN1} = -I_{IN2}$ , becomes Bilinear Integrator


# Switched-Current Integrator

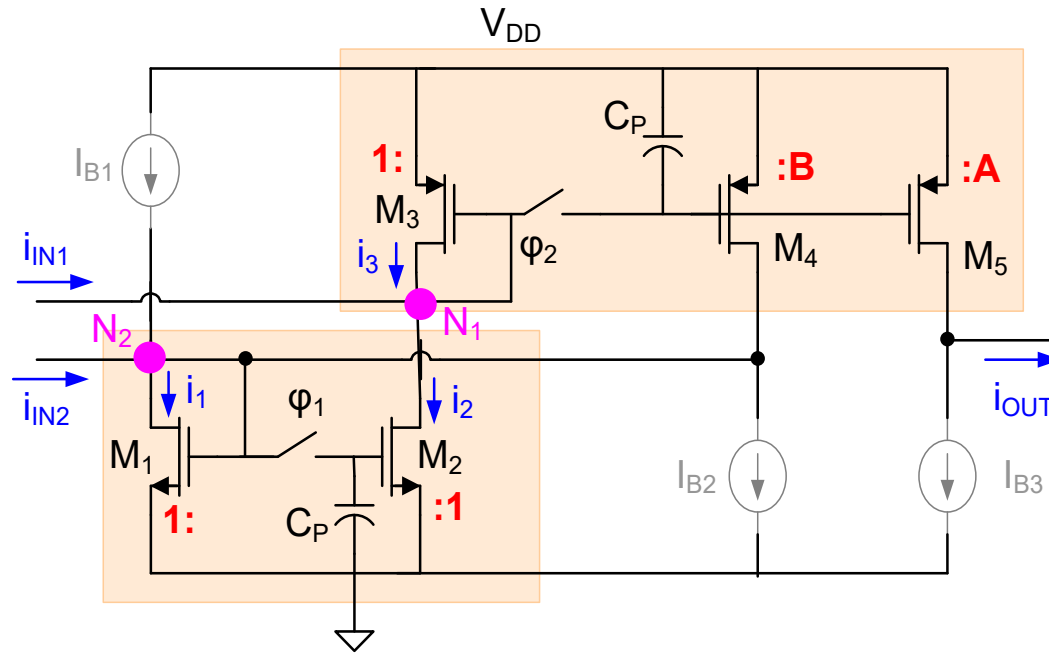


$$I_{OUT}(z) = \left( \frac{Az^{-1}}{1-Bz^{-1}} \right) I_{IN2}(z) - \left( \frac{A}{1-Bz^{-1}} \right) I_{IN1}(z)$$

- Summing inputs can be provided by summing currents on  $N_1$  or  $N_2$  or both
- Multiple outputs can be provided by adding outputs to upper mirror
- Amount of loss determined by mirror gain  $B$

# Switched-Current Integrator

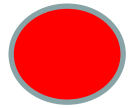

## Sensitivity Analysis

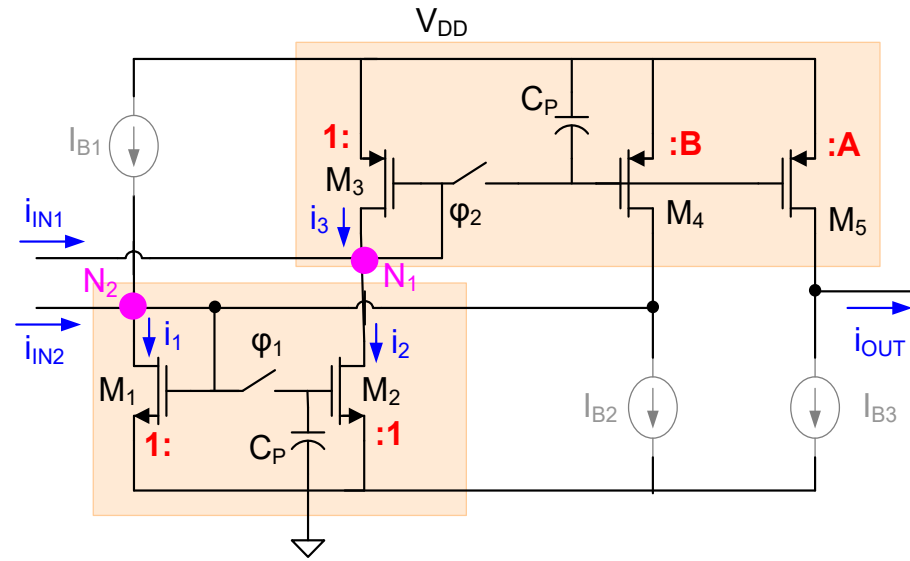

Consider Forward Euler

$$I_{\text{OUT}}(z) = \left( \frac{Az^{-1}}{1-Bz^{-1}} \right) I_{\text{IN2}}(z)$$

$$H(z) = \frac{TI_0}{z-1+\alpha T}$$

$$I_0 = \frac{A}{T} \quad \frac{1-B}{T} = \alpha$$


$$S_A^{I_0} = 1$$

$$S_B^\alpha = \frac{-B}{1-B}$$

For low loss integrator (e.g. ideal integrator), the sensitivity of  $\alpha$  is very large!

# Switched-Current Integrator

## Sensitivity Analysis

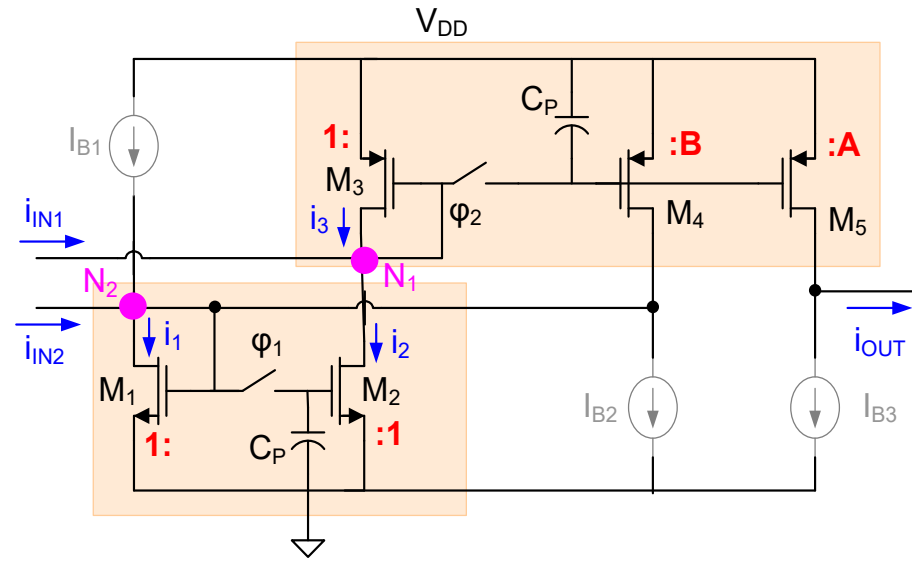

Consider Bilinear  $z$

$$I_{OUT}(z) = A \left( \frac{z^{-1} + 1}{1 - Bz^{-1}} \right) I_{IN}(z)$$

$$H(z) = \frac{TI_0}{2} \left( \frac{z+1}{z \left( 1 + \frac{\alpha T}{2} \right) + \left( \frac{\alpha T}{2} - 1 \right)} \right)$$

$$I_0 = A \frac{2}{T(1+B)} \quad \alpha = \frac{2}{T} \frac{1-B}{1+B}$$

$$S_A^{I_0} = 1$$

$$S_B^\alpha = \frac{-B}{(1-B)(1+B)}$$

For low loss integrator (e.g. ideal integrator), the sensitivity of  $\alpha$  is very large!


What about the sensitivity to the gain of the lower current mirror?



# Switched-Current Integrator

Define  $A_1$  to be the gain of the lower mirror

Sensitivity to  $A_1$ ?

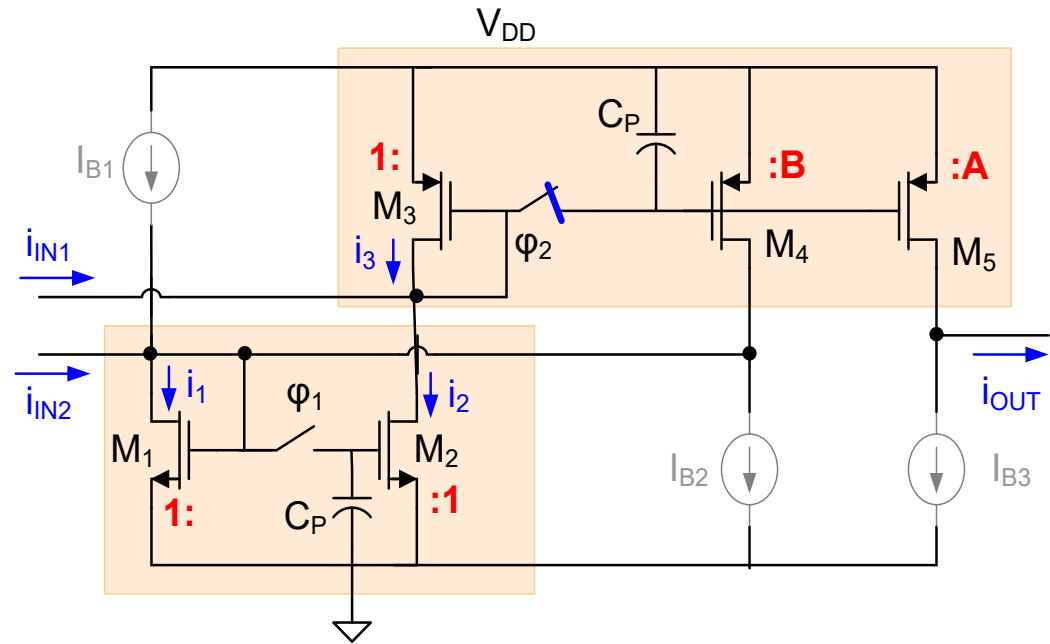

Consider  $\Phi_2$  closed,  $\Phi_1$  open ( $nT - T/2 < t < nT$ )

$$i_2(t) = A_1 i_1(nT - T)$$

$$i_2(t) = i_3(t) + i_{IN1}(t)$$

$$i_{OUT}(t) = A i_3(t)$$


$$i_1(nT - T) = B i_3(nT - T) + i_{IN2}(nT - T) \quad (\text{from first phase})$$

$$\left(\frac{1}{A}\right) i_{OUT}(t) + i_{IN1}(t) = \frac{A_1 B}{A} i_{OUT}(nT - T) + A_1 i_{IN2}(nT - T)$$

# Switched-Current Integrator

Define  $A_1$  to be the gain of the lower mirror

Sensitivity to  $A_1$ ?

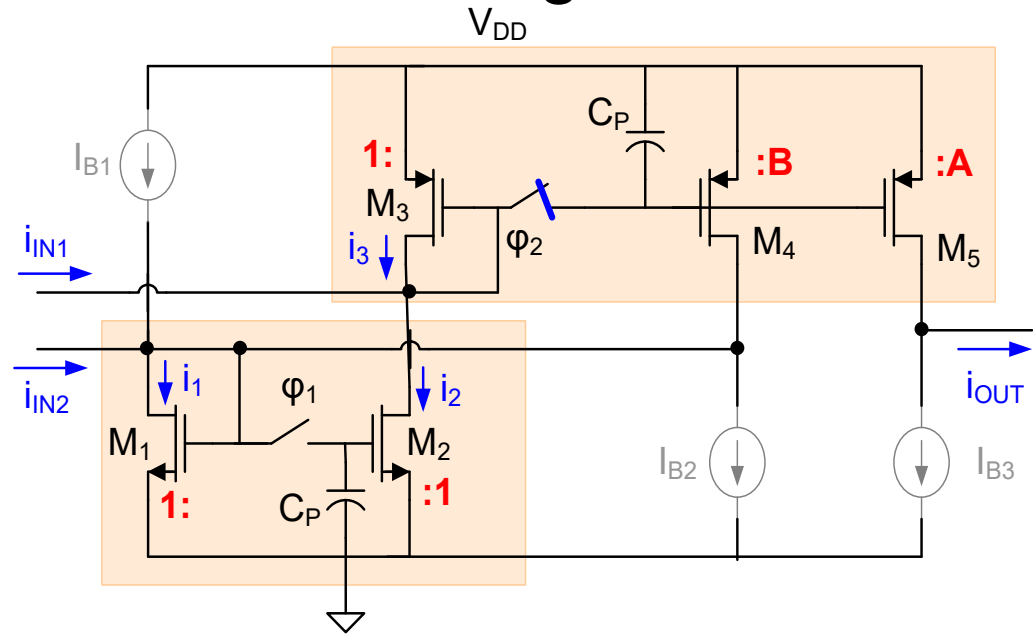

$$\left(\frac{1}{A}\right) i_{\text{OUT}}(nT) + i_{\text{IN1}}(nT) = \frac{A_1 B}{A} i_{\text{OUT}}(nT-T) + A_1 i_{\text{IN2}}(nT-T)$$

Taking z-transform, obtain


$$I_{\text{OUT}}(z) = \left(\frac{A_1 A z^{-1}}{1 - B A_1 z^{-1}}\right) I_{\text{IN2}}(z) - \left(\frac{A}{1 - B A_1 z^{-1}}\right) I_{\text{IN1}}(z)$$

Consider Forward Euler



$$\frac{1 - B A_1}{T} = \alpha \quad S_B^\alpha = \frac{-B A_1}{1 - B A_1} \quad S_{A_1}^\alpha = \frac{-B A_1}{1 - B A_1}$$

Sensitivity to  $A_1$  is also large for low-loss or lossless integrator

# Switched-Current Integrator

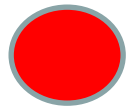

Consider another circuit

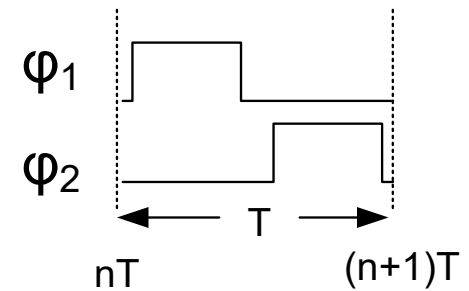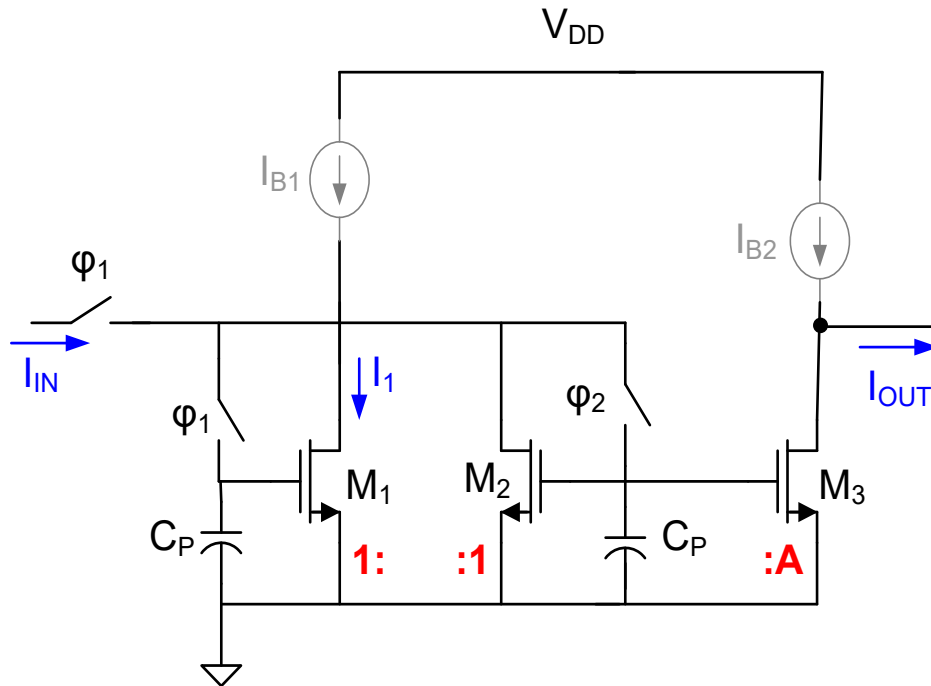


Consider  $\Phi_1$  closed,  $\Phi_2$  open ( $nT-T < t < nT-T/2$ )

$$i_1(t) = \frac{1}{A} i_{\text{OUT}}(nT-T) + i_{\text{IN}}(t)$$

$$i_1(nT-T) = \frac{1}{A} i_{\text{OUT}}(nT-T) + i_{\text{IN}}(nT-T) \quad (1)$$

# Switched-Current Integrator

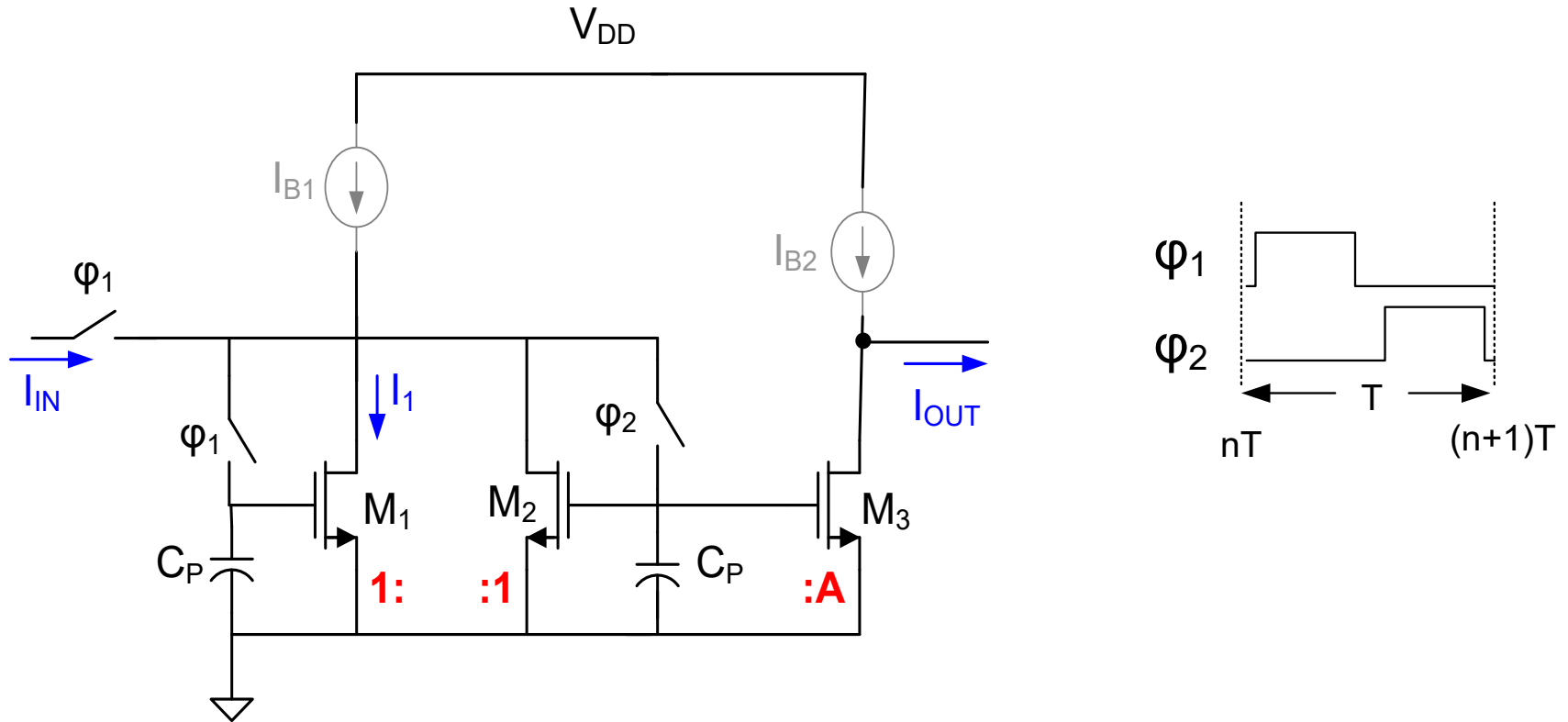

Consider  $\Phi_2$  closed,  $\Phi_1$  open ( $nT - T/2 < t < nT$ )


$$i_{\text{OUT}}(t) = Ai_1(nT - T)$$

$$i_{\text{OUT}}(nT) = Ai_1(nT - T) \quad (2)$$

combining (1) and (2), obtain

$$i_{\text{OUT}}(nT) = A \cdot \frac{1}{A} i_{\text{OUT}}(nT - T) + Ai_{\text{IN}}(nT - T)$$

# Switched-Current Integrator

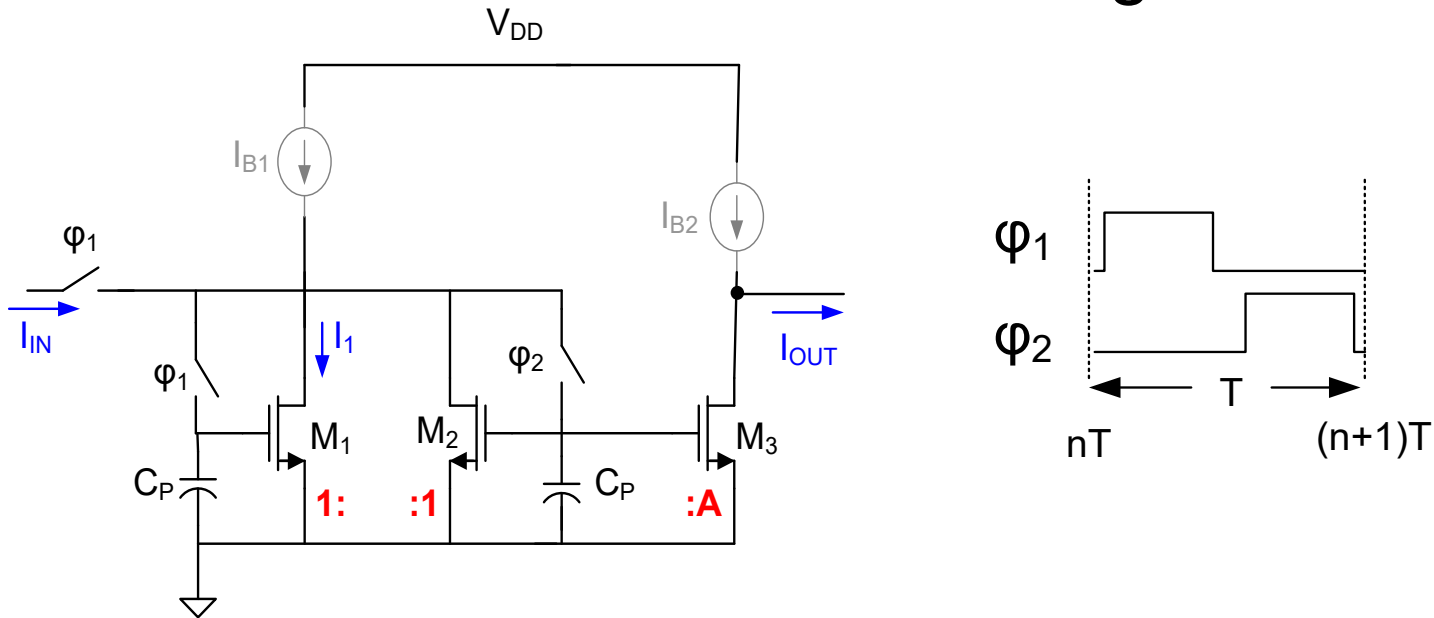

$$i_{\text{OUT}}(nT) = A \cdot \frac{1}{A} i_{\text{OUT}}(nT-T) + A i_{\text{IN}}(nT-T)$$



$$i_{\text{OUT}}(nT) = i_{\text{OUT}}(nT-T) + A i_{\text{IN}}(nT-T)$$

Taking z-transform, obtain

$$I_{\text{OUT}}(z) = \left( \frac{Az^{-1}}{1-z^{-1}} \right) I_{\text{IN}}(z) \quad \text{Forward Euler Integrator}$$

- Lossless Integrator (no matching required!)
- Matching of  $M_1$  and  $M_2$  not required
- Gain  $A$  does not affect coefficient of  $z^{-1}$  in the denominator

# Switched-Current Integrator

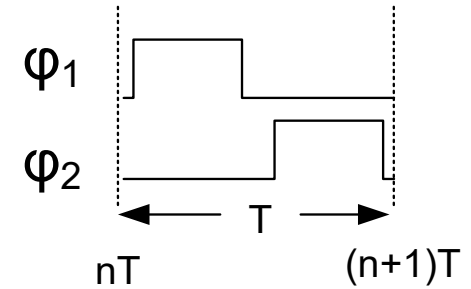
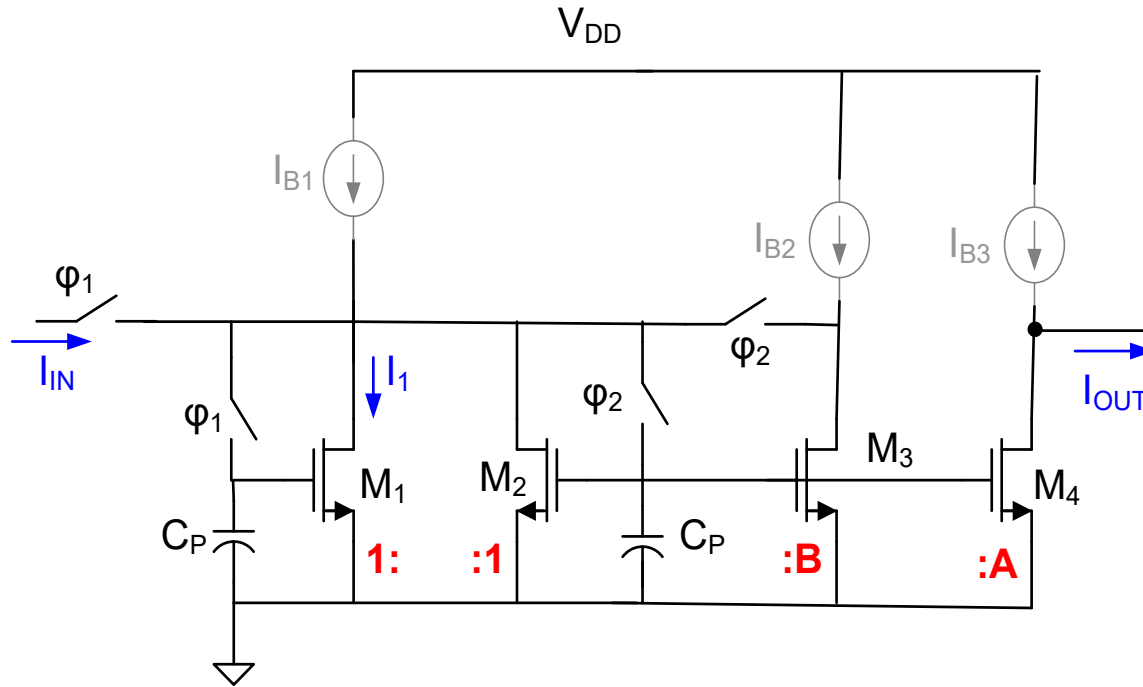


Consider  $\Phi_1$  closed,  $\Phi_2$  open ( $nT-T < t < nT-T/2$ )

$$i_1(t) = \frac{1}{A} i_{\text{OUT}}(nT-T) + i_{\text{IN}}(t)$$

$$i_1(nT-T) = \frac{1}{A} i_{\text{OUT}}(nT-T) + i_{\text{IN}}(nT-T) \quad (1)$$

# Switched-Current Integrator

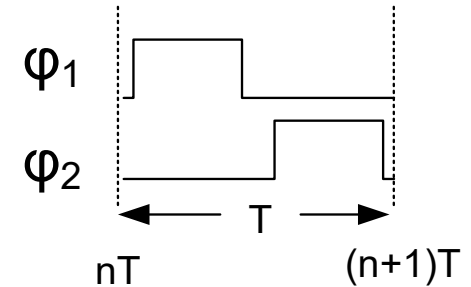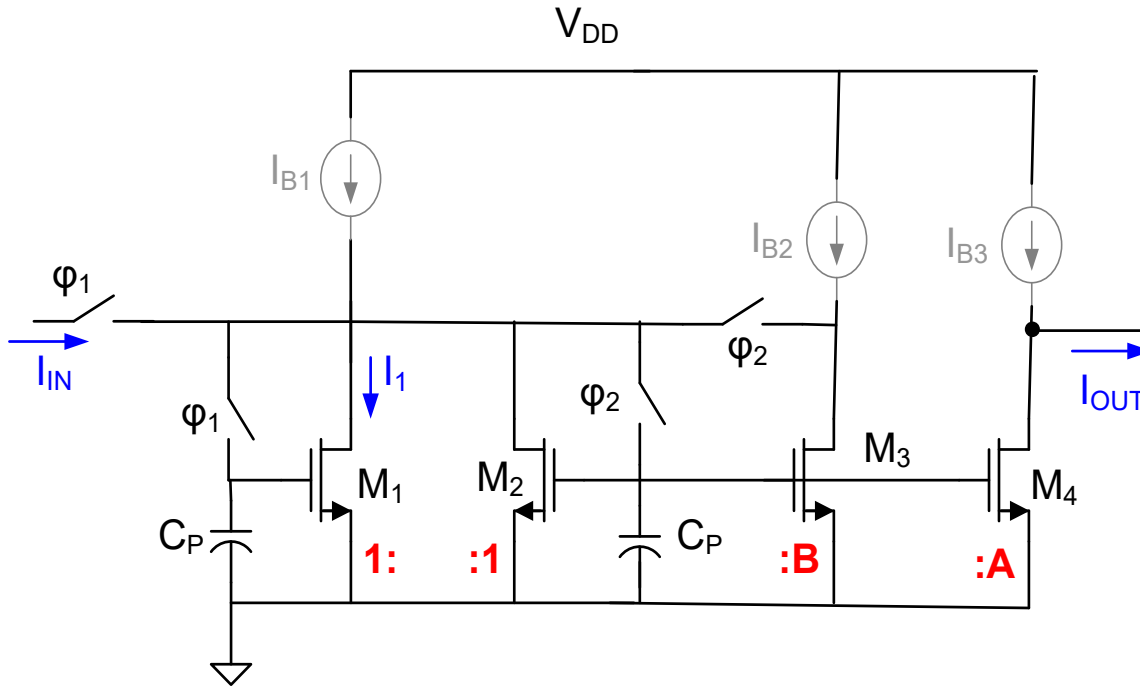

Consider  $\Phi_2$  closed,  $\Phi_1$  open ( $nT - T/2 < t < nT$ )


$$i_{\text{OUT}}(t) = A \left( i_1(nT - T) - \frac{B}{A} i_{\text{OUT}}(t) \right)$$

$$i_{\text{OUT}}(nT) = A \left( i_1(nT - T) - \frac{B}{A} i_{\text{OUT}}(nT) \right) \quad (2)$$

combining (1) and (2), obtain

$$i_{\text{OUT}}(nT) = i_{\text{OUT}}(nT - T) - B i_{\text{OUT}}(nT) + A i_{\text{IN}}(nT - T)$$

# Switched-Current Integrator

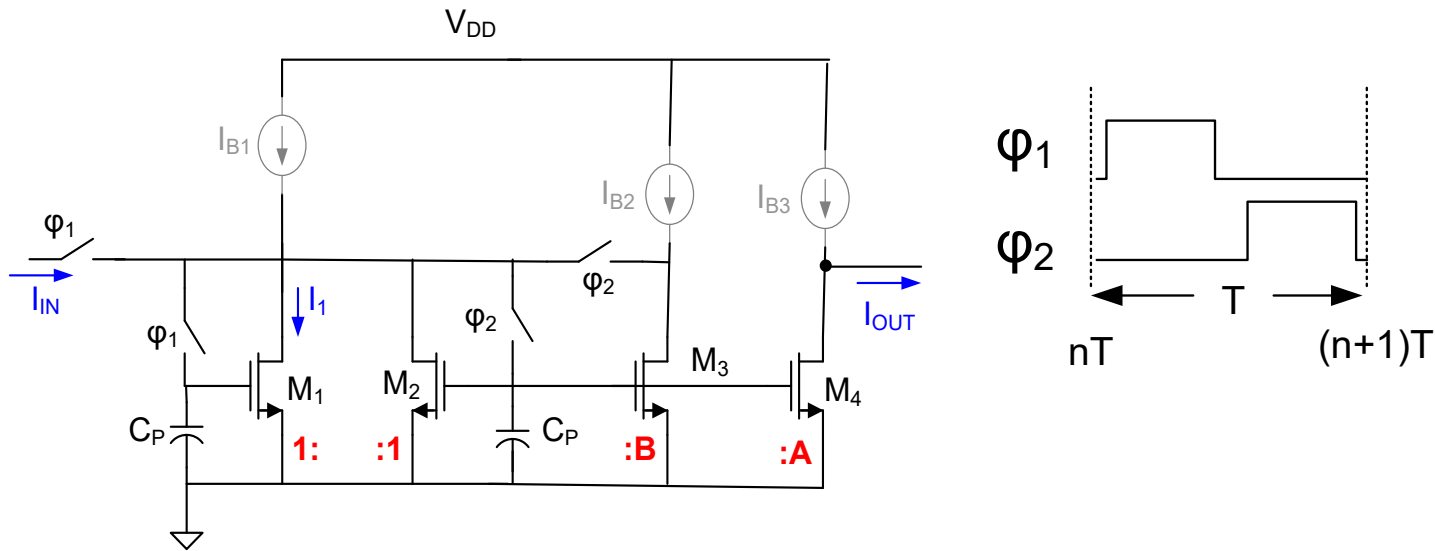

$$i_{\text{OUT}}(nT) = i_{\text{OUT}}(nT-T) - Bi_{\text{OUT}}(nT) + Ai_{\text{IN}}(nT-T)$$

Taking z-transform, obtain

$$I_{\text{OUT}}(z) = \left( \frac{Gz^{-1}}{1-Hz^{-1}} \right) I_{\text{IN}}(z)$$

Forward Euler Integrator (Lossy)

where



$$G = \frac{A}{1+B} \quad H = \frac{1}{1+B}$$

- Lossy Integrator
- Matching of  $M_1$  and  $M_2$  not required
- Gain  $A$  does not affect coefficient of  $z^{-1}$  in the denominator



# Switched-Current Integrator

## Sensitivity Analysis

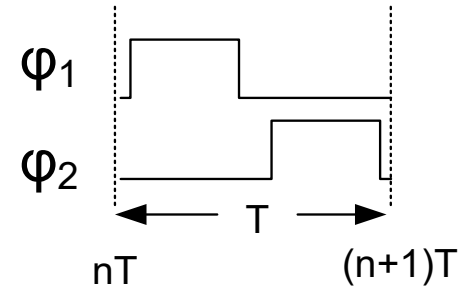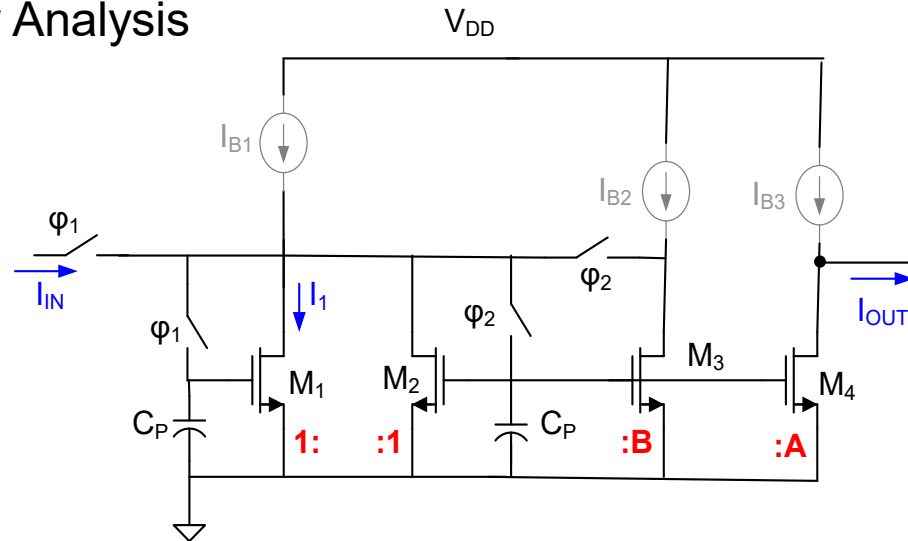

$$I_{\text{OUT}}(z) = \left( \frac{Gz^{-1}}{1-Hz^{-1}} \right) I_{\text{IN}}(z)$$

$$G = \frac{A}{1+B}$$

$$H = \frac{1}{1+B}$$

$$H(z) = \frac{T I_0}{z - 1 + \alpha T}$$

It can be shown that


$$\alpha = \frac{1}{T} \left( \frac{B}{B+1} \right)$$

$$S_B^\alpha = \frac{T}{1+B}$$

For small loss, B is small and so is the sensitivity

# Switched-Current Integrator

Another structure

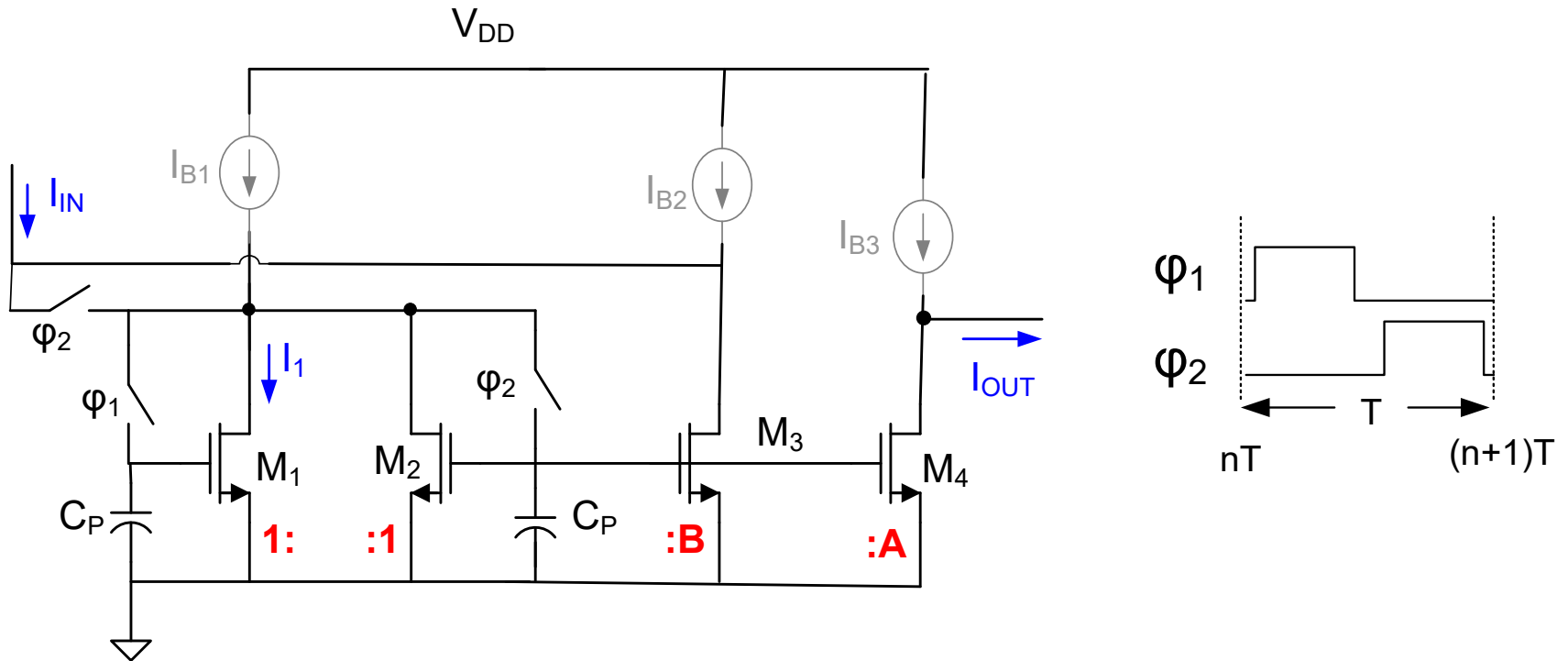



$$I_{OUT}(z) = \left( \frac{-G}{1 - Hz^{-1}} \right) I_{IN}(z)$$

Backward Euler Lossy Inverting

$$G = \frac{A}{1+B} \quad H = \frac{1}{1+B}$$

# Switched-Current Integrator




Another structure

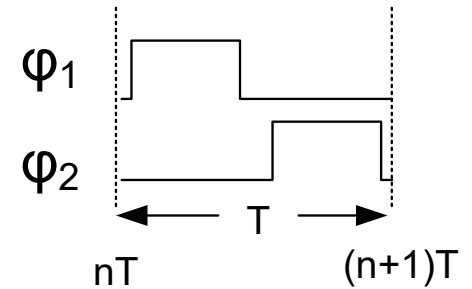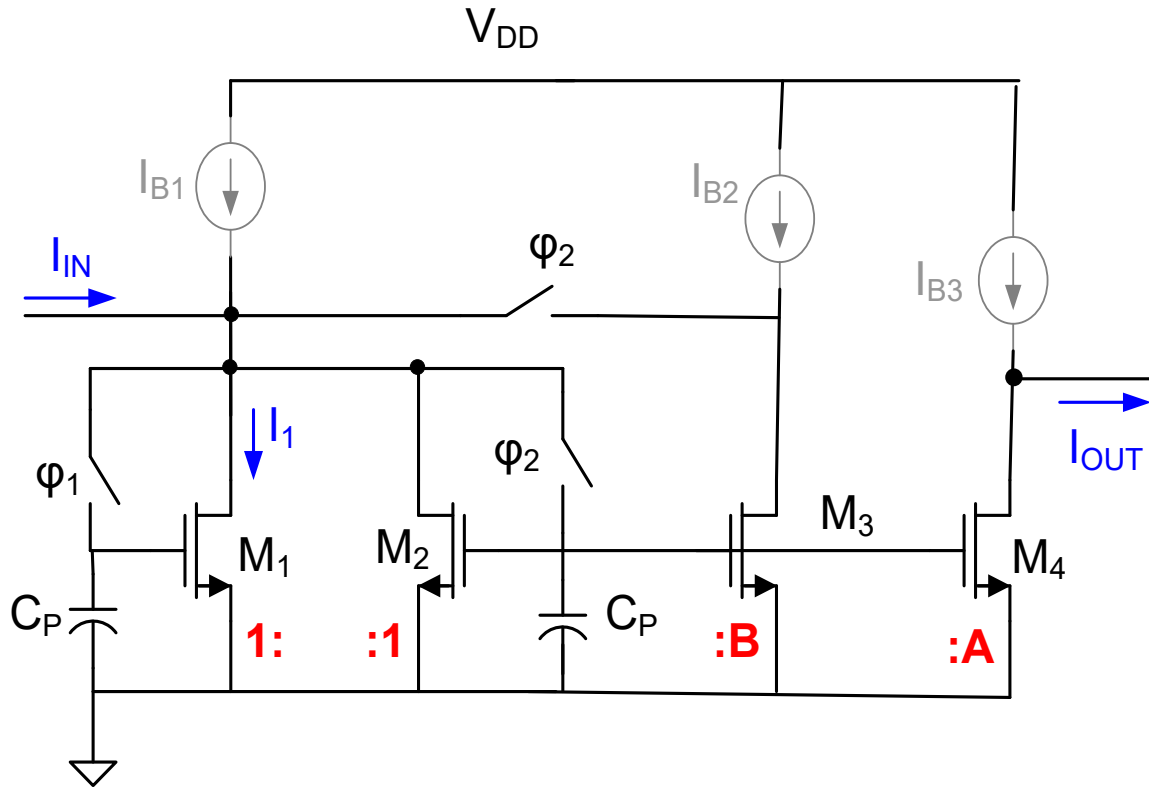

$$I_{OUT}(z) = -G \left( \frac{1-z^{-1}}{1-Hz^{-1}} \right) I_{IN}(z)$$

$$G = \frac{A}{1+B} \quad H = \frac{1}{1+B}$$


# Switched-Current Filters

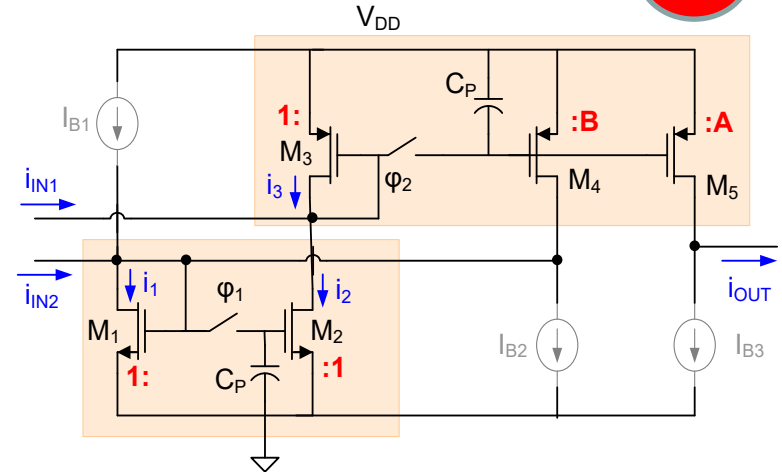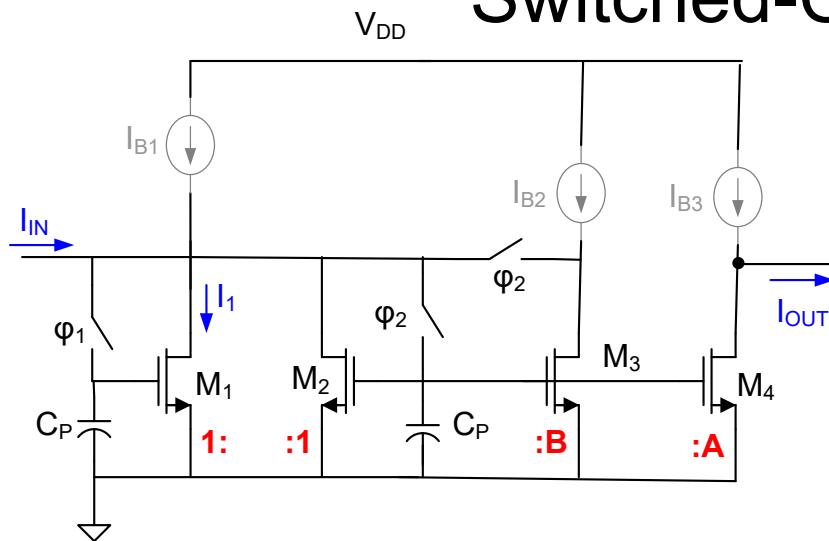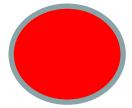


- Switched-current filters is an entirely different approach to designing filters with potential for overcoming many of the major problems facing the filter designer
- Other switched-current filter and integrator blocks have been proposed
- Integrators can be combined to form filter structures
- Single-ended and fully differential structures are readily formed
- Design of Switched-Current Filters is straightforward
- Beyond Hughes, a few others have looked at switched-current filters
- Hughes demonstrated experimentally modest performance with this technique
- Hughes was a world-class researcher and filter expert
- Hughes spent the better part of a decade trying to perfect the switched-current approach but performance remained modest when he retired
- Limited use of switched-current filters today
- Idea is really unique and there are bound to be some major useful applications of the basic concepts embodied in the switched-current filters!

# Filter Design/Synthesis Approaches


## Cascaded Biquads

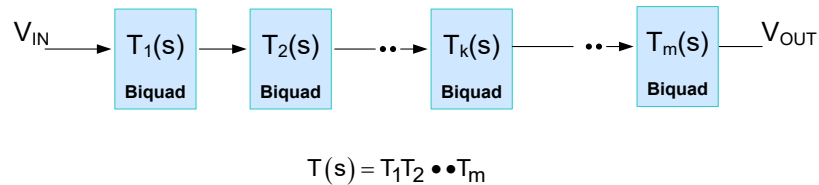


## Leapfrog

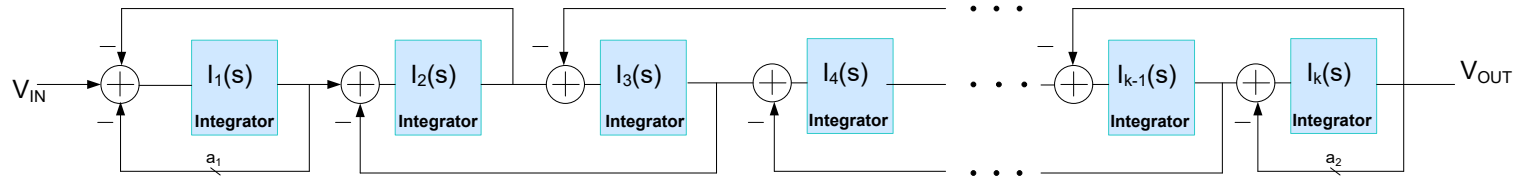
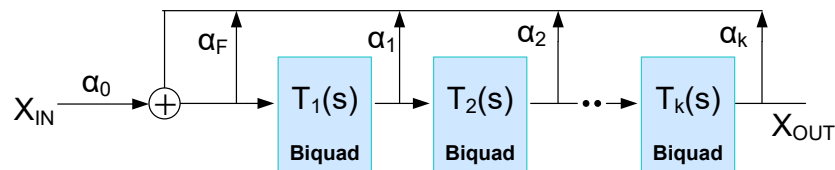
## Multiple-loop Feedback – One type shown




# Leapfrog Filters

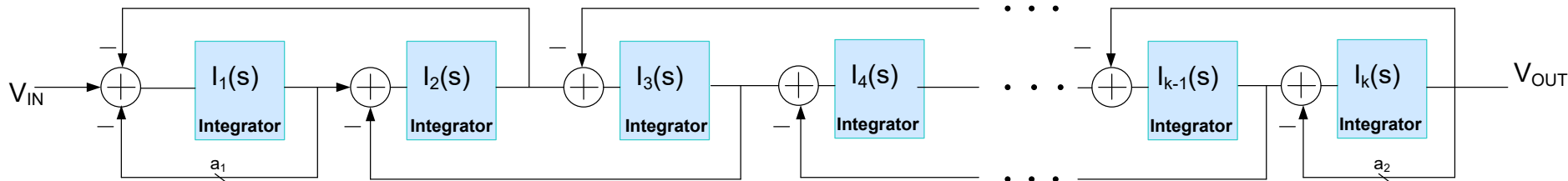

Introduced by Girling and Good, Wireless World, 1970

This structure has some very attractive properties and is widely used though the real benefits and limitations of the structure are often not articulated


# Leapfrog Filters

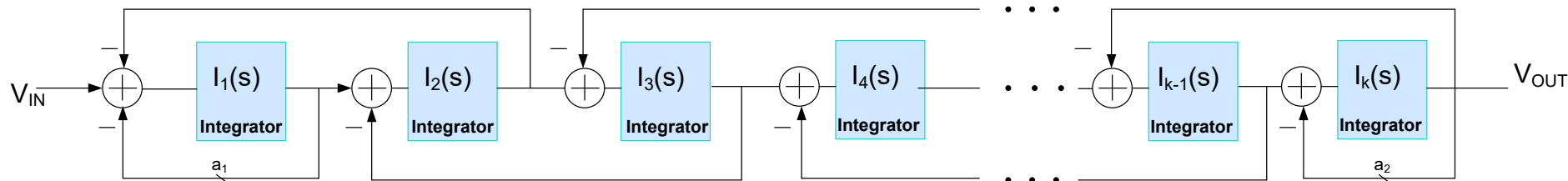

Observation: This structure appears to be dramatically different than anything else ever reported and it is not intuitive why this structure would serve as a filter, much less, have some unique and very attractive properties

To understand how the structure arose, why it has attractive properties, and to identify limitations, some mathematical background is necessary
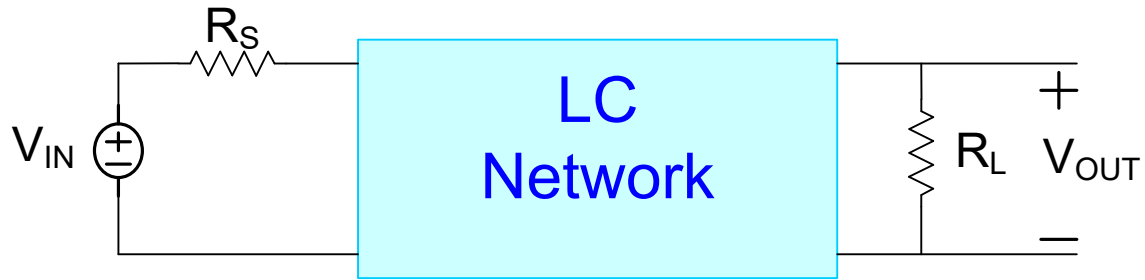
# Background Information for Leapfrog Filters



Assume the impedance  $R_S$  is fixed

Theorem 1: If the LC network delivers maximum power to the load at a frequency  $\omega$ , then


$$S_x^{T(j\omega)} = 0$$

for any circuit element in the system except for  $x = R_L$

This theorem will be easy to prove after we prove the following theorem:



# Background Information for Leapfrog Filters

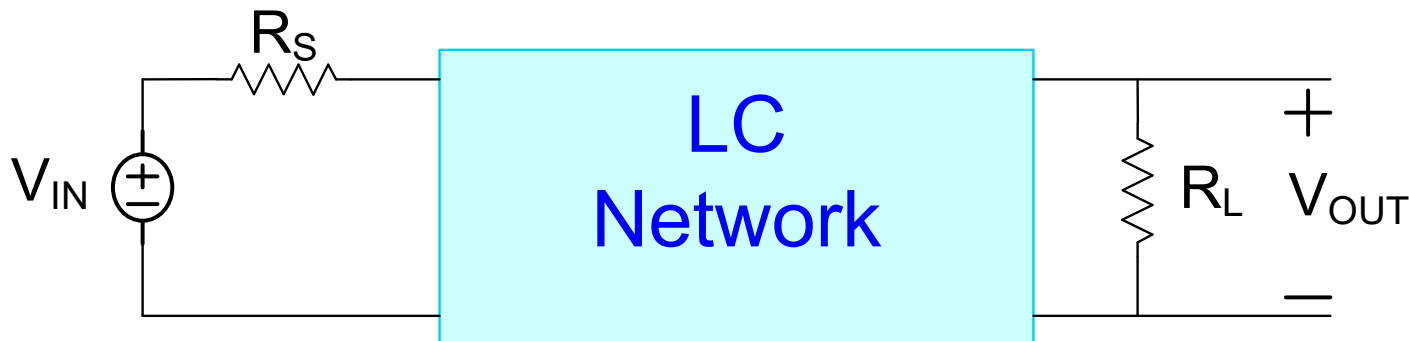

Theorem 2: If the LC network delivers maximum power to the load at a frequency  $\omega$ , then

$$S_x^{P_L(\omega)} = 0$$

where  $P(\omega)$  is the power delivered to the load at input frequency  $\omega$  and where  $x$  is any circuit element in the system except for  $x = R_L$


Note: There is no guarantee that there will be any frequencies where maximum power is transferred to the load and whether this does occur depends strongly on the LC circuit structure and the load  $R_L$ .

Proof of Theorem 2:

First, we will define the input impedance  $Z_{11}$

Proof of Theorem 2:

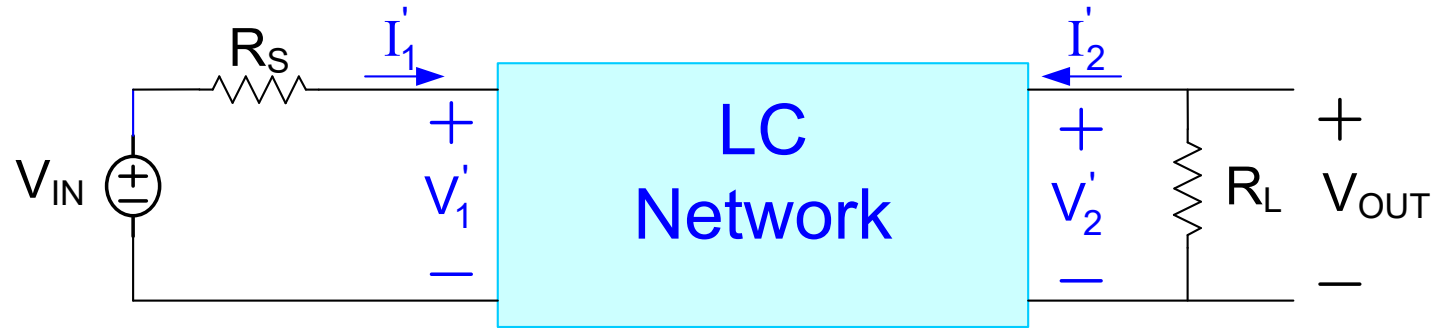Define the port phasors as  $\{V'_1, I'_1, V'_2, I'_2\}$



$$Z_{11} = \frac{V'_1}{I'_1} \quad (\text{input impedance to the loaded LC Network})$$

this can be expressed as

$$Z_{11} = R_1 + jX_1 \quad (R_1 \text{ and } X_1 \text{ are real functions of } \omega \text{ and depend on } R_L)$$

Since the LC network is lossless (dissipates no power) we have

$$P_L = \text{Re}(V'_1 \bullet I'^*_1)$$

$$P_L = \text{Re} \left( \left[ \frac{R_1 + jX_1}{R_S + R_1 + jX_1} V_{in} \right] \bullet \left[ \frac{V_{in}}{R_S + R_1 + jX_1} \right]^* \right)$$

$$P_L = |V_{in}|^2 \text{Re} \left( \frac{R_1 + jX_1}{(R_S + R_1)^2 + X_1^2} \right) = |V_{in}|^2 \frac{R_1}{(R_S + R_1)^2 + X_1^2}$$

Proof of Theorem 2:

$$P_L = |V_{in}|^2 \frac{R_1}{(R_S + R_1)^2 + X_1^2}$$

To maximize power delivered to a fixed load at a frequency  $\omega$ , must have

$$\frac{\partial P_L}{\partial R_1} = 0 \qquad \frac{\partial P_L}{\partial X_1} = 0$$

$$\frac{\partial P_L}{\partial R_1} = |V_{in}|^2 \left[ \frac{((R_S + R_1)^2 + X_1^2) - R_1(2)(R_S + R_1)}{((R_S + R_1)^2 + X_1^2)^2} \right]$$

$$\frac{\partial P_L}{\partial R_1} = |V_{in}|^2 \left[ \frac{(R_S^2 + 2R_1R_S + R_1^2 + X_1^2 - 2R_1R_S - 2R_1^2)}{((R_S + R_1)^2 + X_1^2)^2} \right] = |V_{in}|^2 \left[ \frac{(2(R_S^2 - R_1^2) + X_1^2)}{((R_S + R_1)^2 + X_1^2)^2} \right]$$

$$\left. \begin{array}{l} \frac{\partial P_L}{\partial R_1} = 0 \quad \longrightarrow \quad 2(R_S^2 - R_1^2) + X_1^2 = 0 \\ \frac{\partial P_L}{\partial X_1} = |V_{in}|^2 \left[ \frac{-R_1(2X_1)}{((R_S + R_1)^2 + X_1^2)^2} \right] \\ \frac{\partial P_L}{\partial X_1} = 0 \quad \longrightarrow \quad X_1 = 0 \end{array} \right\} \longrightarrow \begin{array}{l} X_1 = 0 \quad (1) \\ R_1 = R_S \quad (2) \end{array}$$

Proof of Theorem 2:

$$X_1 = 0 \quad (1)$$

$$R_1 = R_s \quad (2)$$

$$P_L = |V_{in}|^2 \frac{R_1}{(R_s + R_1)^2 + X_1^2}$$

Now let x be any element in the LC network

$$\frac{\partial P_L}{\partial x} = \frac{\partial P_L}{\partial R_1} \frac{\partial R_1}{\partial x} + \frac{\partial P_L}{\partial X_1} \frac{\partial X_1}{\partial x}$$

$$\frac{\partial P_L}{\partial x} = \left[ |V_{in}|^2 \left[ \frac{(2(R_s^2 - R_1^2) + X_1^2)}{((R_s + R_1)^2 + X_1^2)^2} \right] \right] \frac{\partial R_1}{\partial x} + \left[ |V_{in}|^2 \left[ \frac{-R_1(2X_1)}{((R_s + R_1)^2 + X_1^2)^2} \right] \right] \frac{\partial X_1}{\partial x}$$

It thus follows from (1) and (2) that at maximum power transfer, the two coefficients in this expression vanish, thus

$$\frac{\partial P_L}{\partial x} = \left[ |V_{in}|^2 \left[ \frac{0}{((R_s + R_1)^2 + X_1^2)^2} \right] \right] \frac{\partial R_1}{\partial x} + \left[ |V_{in}|^2 \left[ \frac{0}{((R_s + R_1)^2 + X_1^2)^2} \right] \right] \frac{\partial X_1}{\partial x} = 0$$


thus

$$S_x^{P_L} = \frac{\partial P_L}{\partial x} \frac{x}{P_L} = 0 \quad \mathbf{I}$$

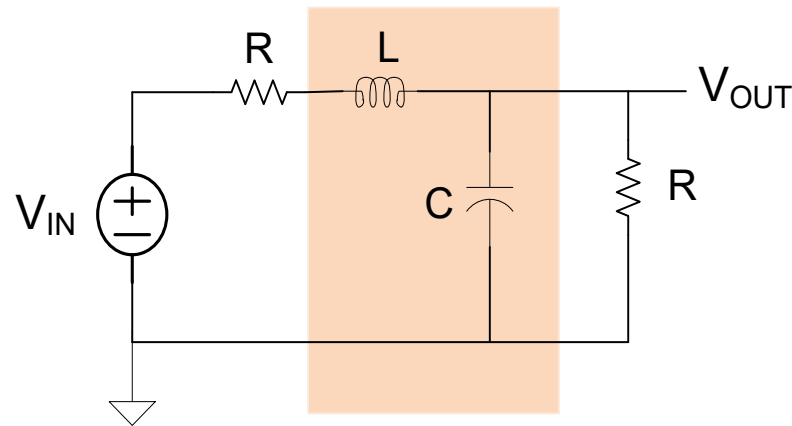Question: Can we also make the claim that  $S_{R_L}^{P_L(\omega)} = 0$  at any frequency where maximum power is transferred to the load?

Yes! Note that the previous analysis is based upon characterizing  $R_1$  and  $X$  which are functions of  $k$  reactive components,  $\{x_1, \dots, x_k\}$  and  $R_L$ .

The following circuit has maximum power transfer at dc and it can be easily analytically shown that the sensitivity of  $P$  to  $L$ ,  $C$ , and  $R_L$  is 0 at dc.



Proof of Theorem 1:  $S_x^{|T(j\omega)|} = ?$

$$P_L = \text{Re} \left( V_{\text{out}} \cdot \left( \frac{V_{\text{out}}}{R_L} \right)^* \right)$$

$$P_L = \text{Re} \left( V_{\text{in}} T(j\omega) \cdot \left( \frac{V_{\text{in}} T(j\omega)}{R_L} \right)^* \right)$$

$$P_L = \left( \frac{|V_{\text{in}}|^2}{R_L} \right) \cdot |T(j\omega)|^2$$

Recall the following two sensitivity relationships

$$S_x^{kf} = S_x^f$$

$$S_x^{f^2} = 2 \cdot S_x^f$$


It thus follows that

$$S_x^{P_L} = 2 \cdot S_x^{|T(j\omega)|} \xrightarrow{S_x^{P_L} = 0} S_x^{|T(j\omega)|} = 0$$



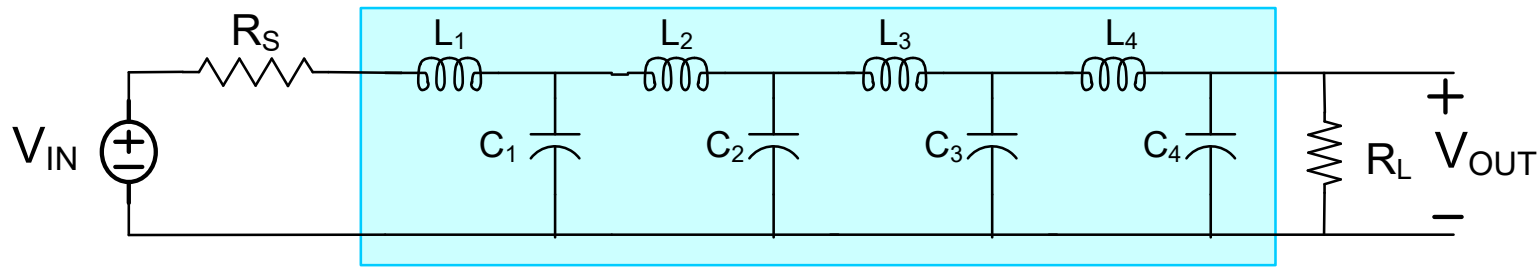
# Implications of Theorem 1

Many passive LC filters such as that shown below exist that have near maximum power transfer in the passband




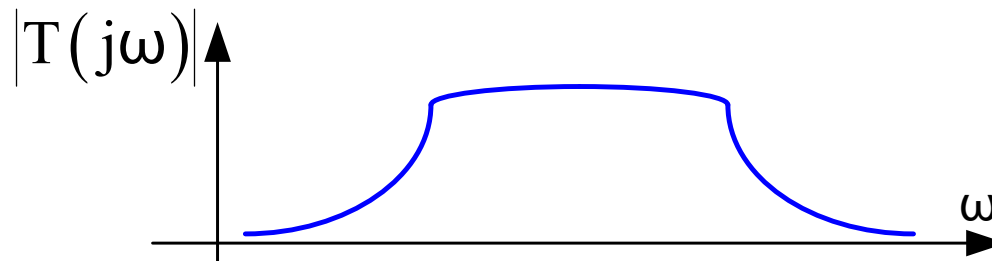If a component in the LC network changes a little, there is little change in the passband gain characteristics (depicted as bandpass)




$$\sum_x |T(j\omega)| \simeq 0 \quad \text{in passband}$$

# Implications of Theorem 1

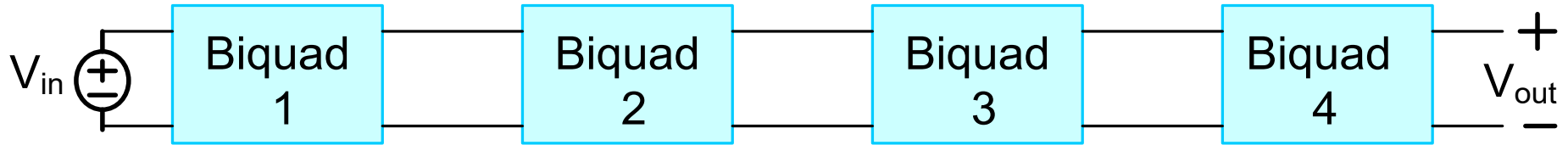

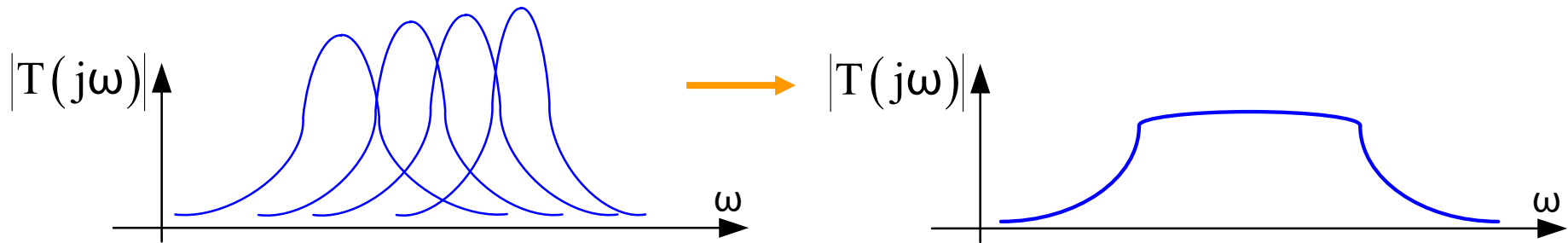
Cascaded Biquad has a response that is the product of the individual second-order transfer functions







If a component in a biquad changes a little, there is often a large change in the passband gain characteristics (depicted as bandpass)



# Implications of Theorem 1

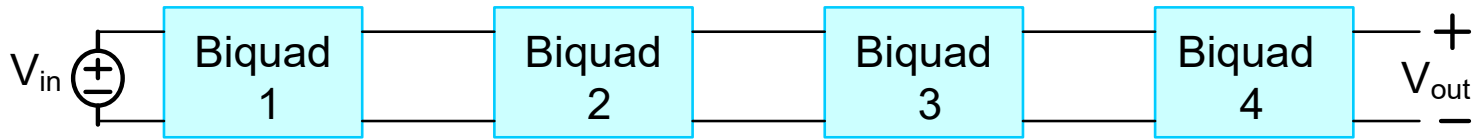


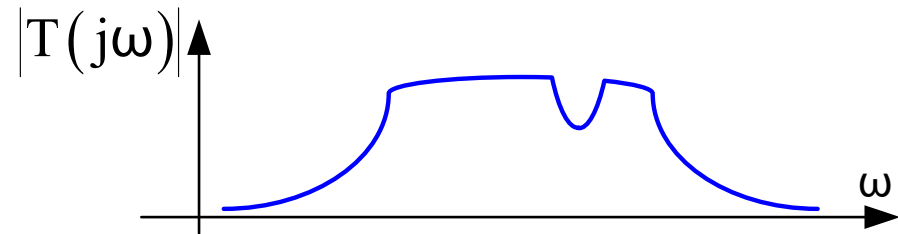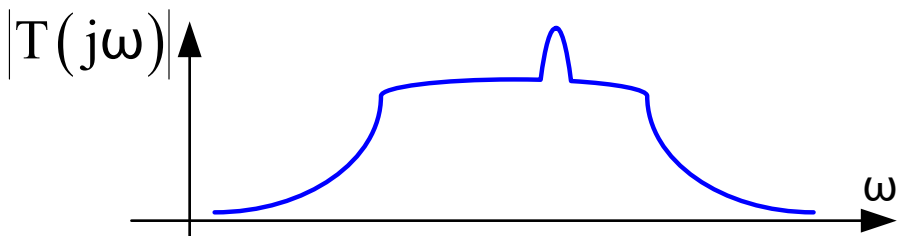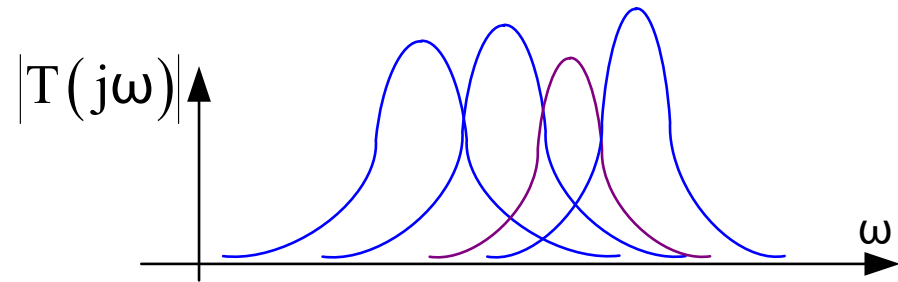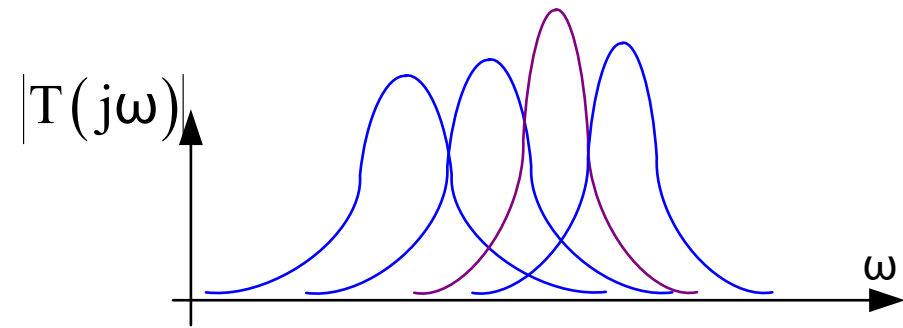If a component in a biquad changes a little, there is often a large change in the passband gain characteristics (depicted as bandpass)



$$\sum_x |T(j\omega)| \neq 0 \quad \text{in passband}$$


# Implications of Theorem 1

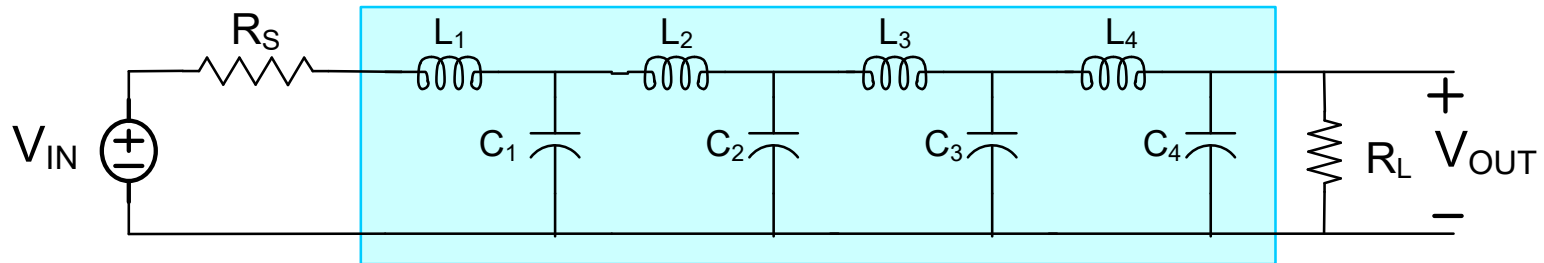

Good doubly-terminated LC networks often much less sensitive to most component values in the passband than are cascaded biquads !

This is a major advantage of the LC networks but can not be applied practically in most integrated applications or even in pc-board based designs

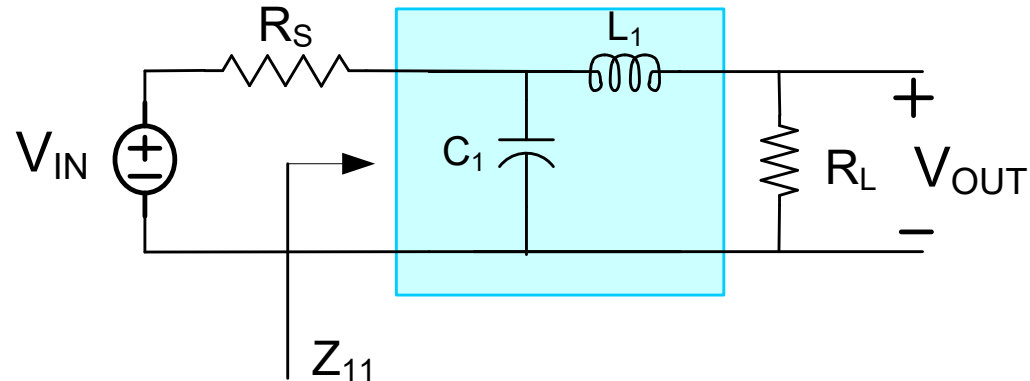Example: Determine at what frequencies maximum-power transfer to the load will occur and what value of  $R_L$  is needed for this to happen



Recall at maximum-power transfer,  $Z_{11}$  is real and equal to  $R_S$

$$Z_{11} = \frac{R_L + sL}{s^2LC + sR_L C + 1}$$


$$Z_{11}(j\omega) = \left( \frac{R_L}{(1 - \omega^2LC)^2 + \omega^2R_L^2C} \right) + j \left( \frac{\omega L - \omega^2R_L^2C - \omega^3L^2C}{(1 - \omega^2LC)^2 + \omega^2R_L^2C} \right)$$

$$\text{Im}(Z_{11}(j\omega)) = 0 \quad \text{only at} \quad \omega=0 \text{ and one other positive value of } \omega$$

To get maximum power transfer at  $\omega=0$ , must have  $R_L=R_S$

Appears not to have maximum power transfer at other frequency where  $\text{Im}(Z_{11}(j\omega)) \neq 0$

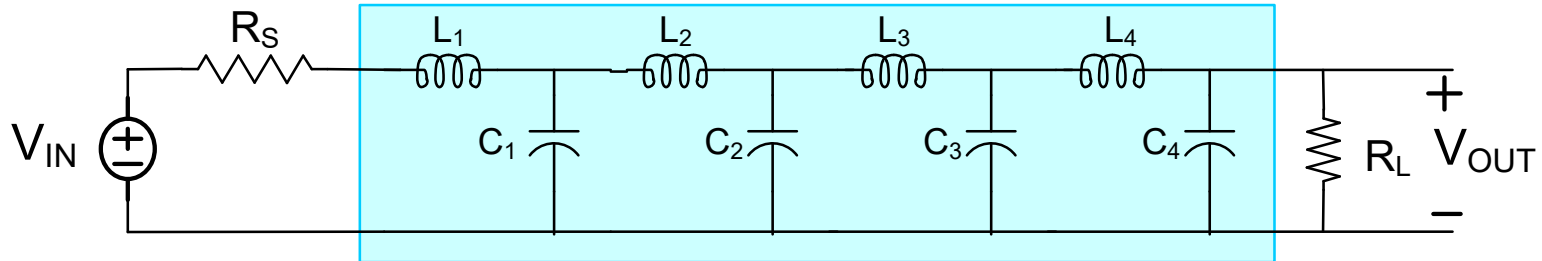Consider again the doubly-terminated circuit that has multiple passband frequencies where maximum power transfer to the load occurs




Observe that this structure is completely characterized by a set of equations that characterize the network

All sensitivity properties are inherently determined by this set of equations

Any circuit that has the same set of equations will have the same sensitivity properties

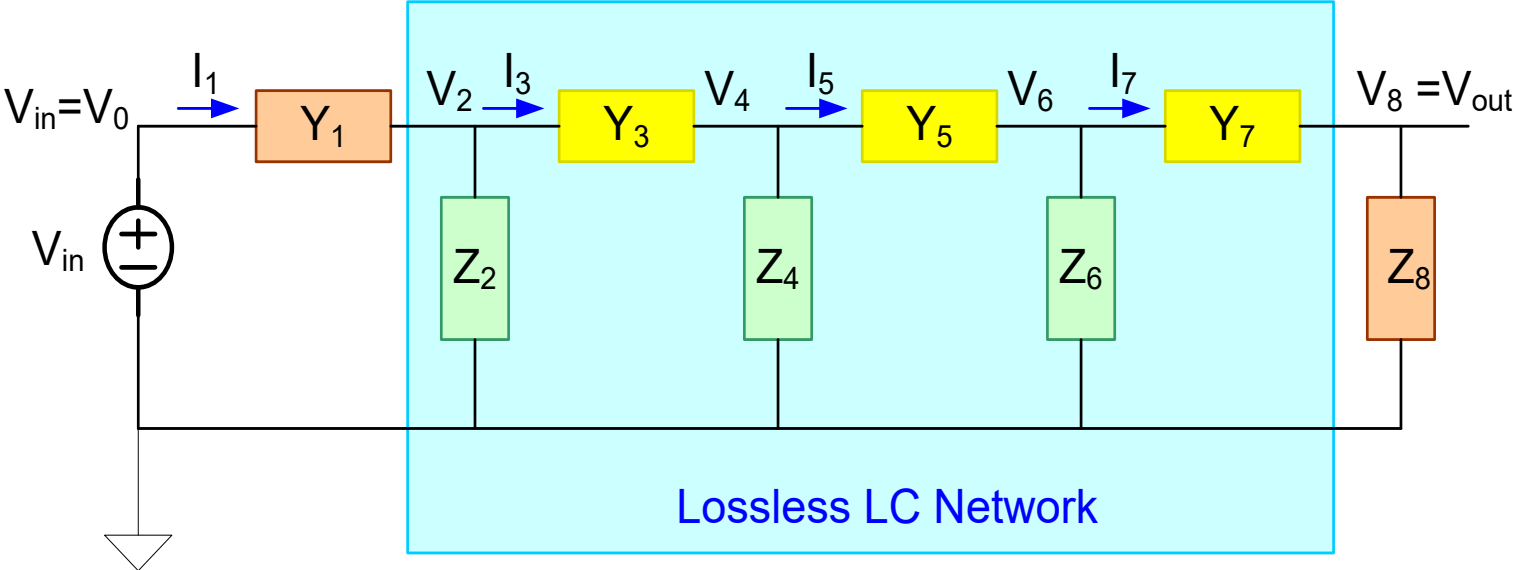
# Doubly-terminated Ladder Network with Low Passband Sensitivities



For components in the LC Network observe

$$Y_k = \frac{1}{sL_k} \qquad Z_k = \frac{1}{sC_k}$$
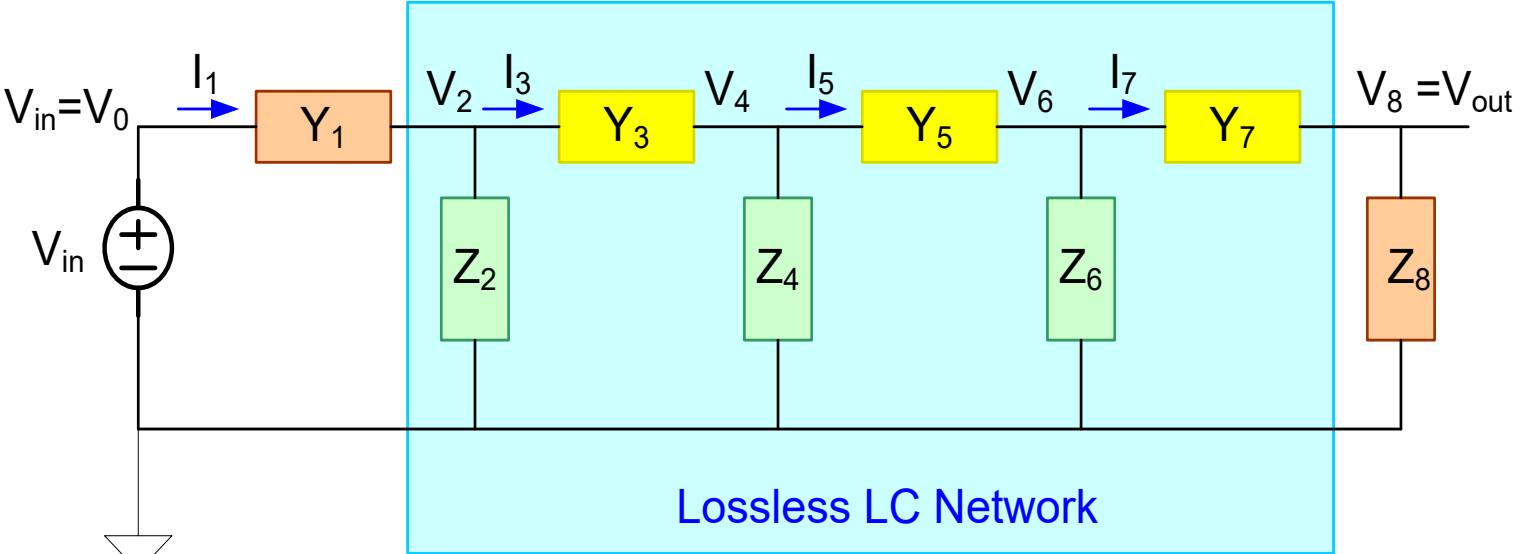
# Doubly-terminated Ladder Network with Low Passband Sensitivities



$$\begin{aligned}
 I_1 &= (V_0 - V_2) Y_1 \\
 V_2 &= (I_1 - I_3) Z_2 \\
 I_3 &= (V_2 - V_4) Y_3 \\
 V_4 &= (I_3 - I_5) Z_4 \\
 I_5 &= (V_4 - V_6) Y_5 \\
 V_6 &= (I_5 - I_7) Z_6 \\
 I_7 &= (V_6 - V_8) Y_7 \\
 V_8 &= I_7 Z_8
 \end{aligned}$$

Complete set of independent equations that characterize this filter

Solution of this set of equations is tedious

**All sensitivity properties of this circuit are inherently embedded in these equations!**



Stay Safe and Stay Healthy !

**End of Lecture 30**