


EE 508 Lecture 36

High Frequency Filters
Noise and Dynamic Range

Review from last lecture

Single-ended High-Frequency TA Integrators

How high can I_0 be?

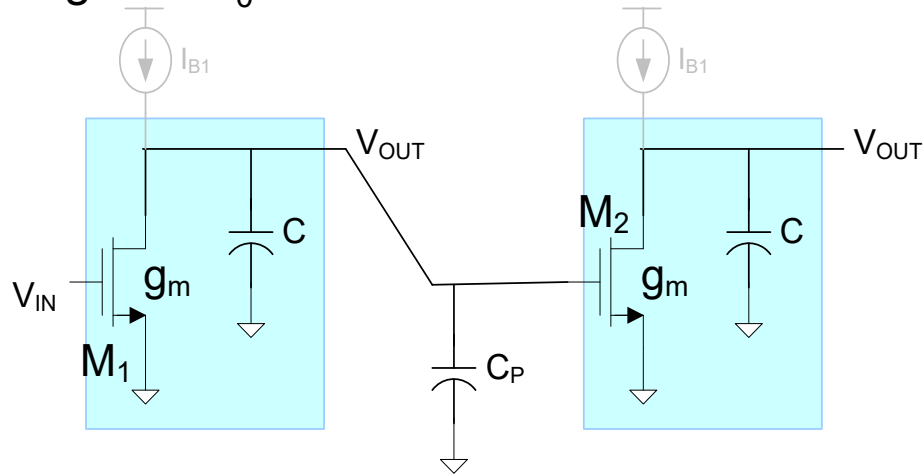

$$I_{0M} = \frac{\mu V_{EB1}}{L_{\min}^2}$$

$$I_{0M} = \omega_T$$

(neglected C and C_P)

Speed of operation increases with V_{EB}

V_{EB} is limited by signal swing requirements and V_{DD}

Signal Swing:


$$V_{DD} - V_T - V_{EB} = V_T + V_{EB} - (V_T + 100\text{mV})$$

$$V_{EB} = \frac{V_{DD} + 100\text{mV} - V_T}{2}$$

$$I_{0MAX} \cong \frac{\mu(V_{DD} + 100\text{mV} - V_T)}{2L_{\min}^2}$$


Review from last lecture

How high can I_0 be?

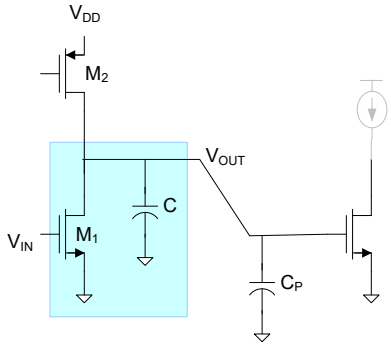

$$I_0 = \frac{\omega_T}{1 + \left(3h_{\text{BOT}} \left[1 + \frac{\mu_n}{\mu_p} \left(\frac{V_{\text{EB1}}}{V_{\text{EB2}}} \right)^2 \right] + h_{\text{SW}} \left[12 \frac{\lambda}{W_1} + 1 + \frac{\mu_n}{\mu_p} \left(\frac{V_{\text{EB1}}}{V_{\text{EB2}}} \right)^2 \right] \right)}$$

Consider a basic layout

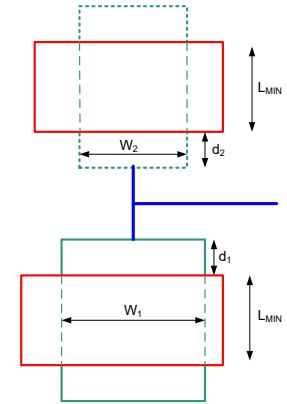

Example: Consider the 0.25u TSMC CMOS Process

$$I_0 = \frac{\omega_T}{1 + \left(3 \cdot 0.31 \left[1 + 4.1 \left(\frac{V_{\text{EB1}}}{V_{\text{EB2}}} \right)^2 \right] + 0.61 \left[12 \frac{0.125}{W_1} + 1 + 4.1 \left(\frac{V_{\text{EB1}}}{V_{\text{EB2}}} \right)^2 \right] \right)}$$

$$h_{\text{BOT}} = 0.31$$

$$h_{\text{SW}} = 0.61$$

$$I_0 = \frac{\omega_T}{1 + \left(0.931 \left[1 + 4.1 \left(\frac{V_{\text{EB1}}}{V_{\text{EB2}}} \right)^2 \right] + 0.61 \left[\frac{1.5}{W_1} + 1 + 4.1 \left(\frac{V_{\text{EB1}}}{V_{\text{EB2}}} \right)^2 \right] \right)}$$

$$\frac{\mu_n}{\mu_p} = 4.1$$

$$\mu_p$$


GATE
term

BOT term


SW term

Review from last lecture

How high can I_0 be?

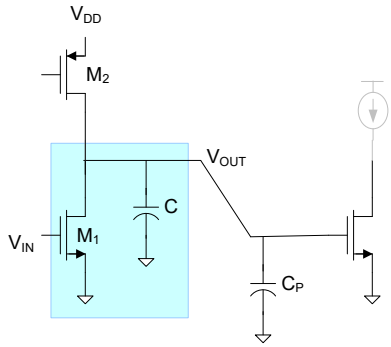

Consider a basic layout

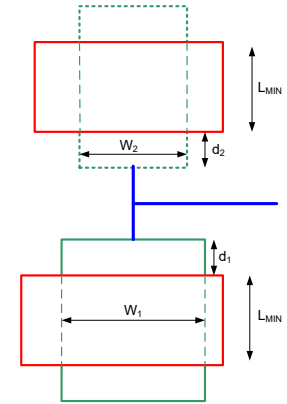

Example: Consider the 0.25u TSMC CMOS Process

$$I_0 = \frac{\omega_T}{1 + \underbrace{\left[0.93 \left[1 + 4.1 \left(\frac{V_{EB1}}{V_{EB2}} \right)^2 \right] \right]}_{\text{BOT term}} + \underbrace{0.61 \left[\frac{1.5}{W_1} + 1 + 4.1 \left(\frac{V_{EB1}}{V_{EB2}} \right)^2 \right]}_{\text{SW term}}}$$


GATE term
BOT term
SW term

If $W_1 = 1.5\mu$ and $V_{EB1} = V_{EB2}$


$$I_0 = \frac{\omega_T}{1 + (4.73 + 4.03)} = .102\omega_T$$

- Designer has control of V_{EB1} and V_{EB2}
- The diffusion capacitance term can dominate the C_{GS} term
- The SW capacitance can be the biggest contributor to the speed limitations
- A factor of 10 or even much more reduction in speed is possible due to the diffusion parasitics and layout
- Maximizing W_1 will minimize I_0 but power will get very large for marginal improvement in speed

How high can I_0 be?

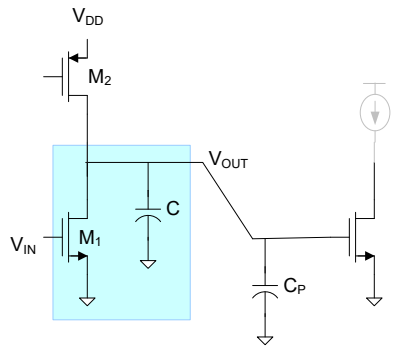

Consider a basic layout

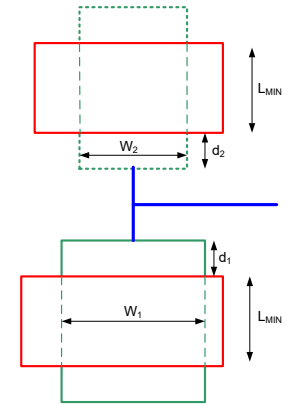

Example: Consider the 0.25u TSMC CMOS Process


$$I_0 = \frac{\omega_T}{1 + \underbrace{\left(0.93 \left[1 + 4.1 \left(\frac{V_{EB1}}{V_{EB2}} \right)^2 \right] \right)}_{\text{BOT term}} + \underbrace{0.61 \left[\frac{1.5}{W_1} + 1 + 4.1 \left(\frac{V_{EB1}}{V_{EB2}} \right)^2 \right]}_{\text{SW term}}}$$

This example shows that layout is really critical when high speed operation is needed


Designer can also manage design with V_{EB1}/V_{EB2} ratio

What can be done with layout to improve performance?

How high can I_0 be?

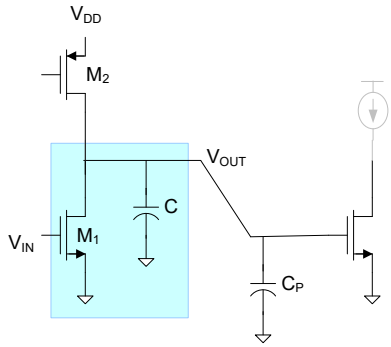



Consider a basic layout

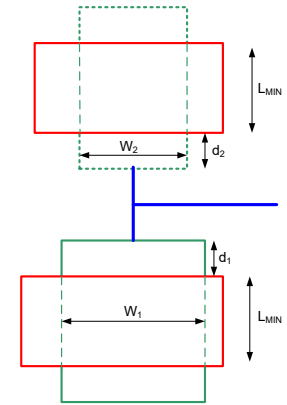


What can be done with layout to improve performance?

Reducing the diffusion capacitances on the drains will have a major impact on speed!

Consider a concentric layout approach:

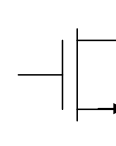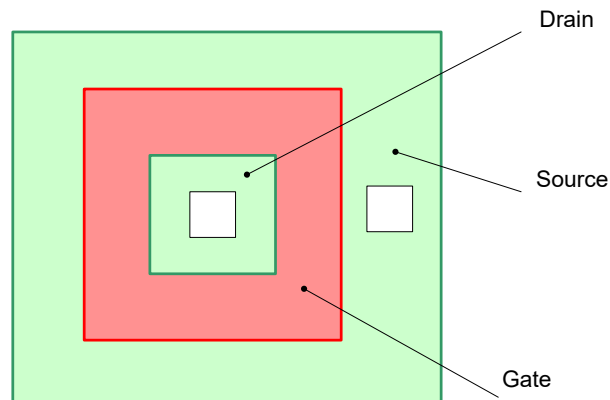

Concentric Layouts

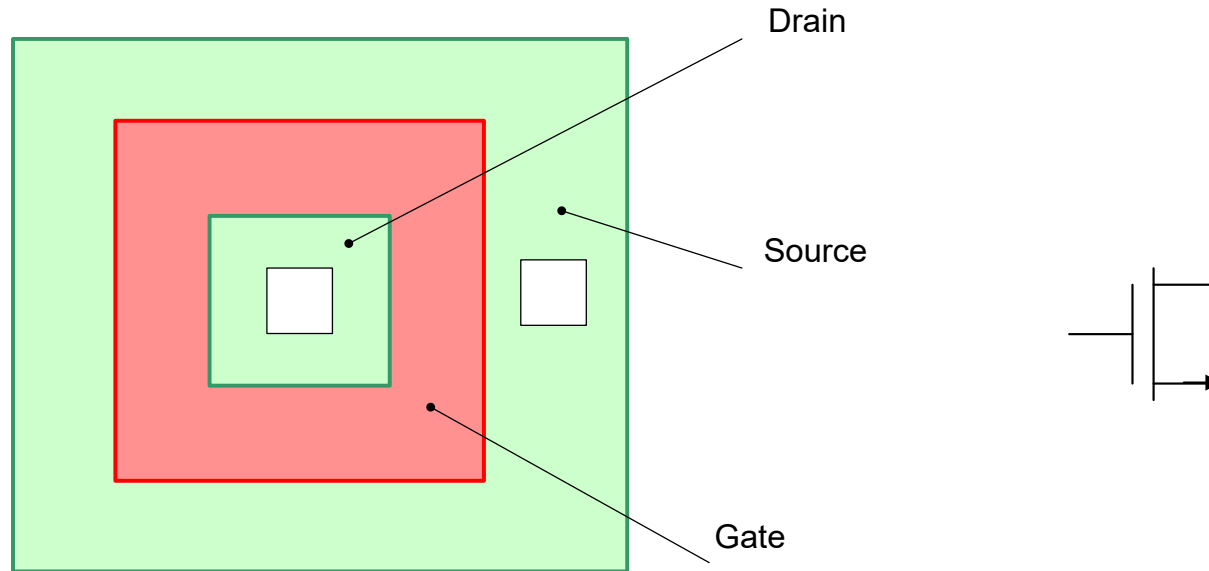


Can be shown this is equivalent to a rectangular transistor (W_{EQ}/L_{EQ})

Drain area and perimeter dramatically reduced

Source area and perimeter dramatically increased (but does not degrade performance)

Only drain sidewall is adjacent to the gate and C_{SW} is usually considerably lower here though some models do not provide separate characterization

Concentric Layouts

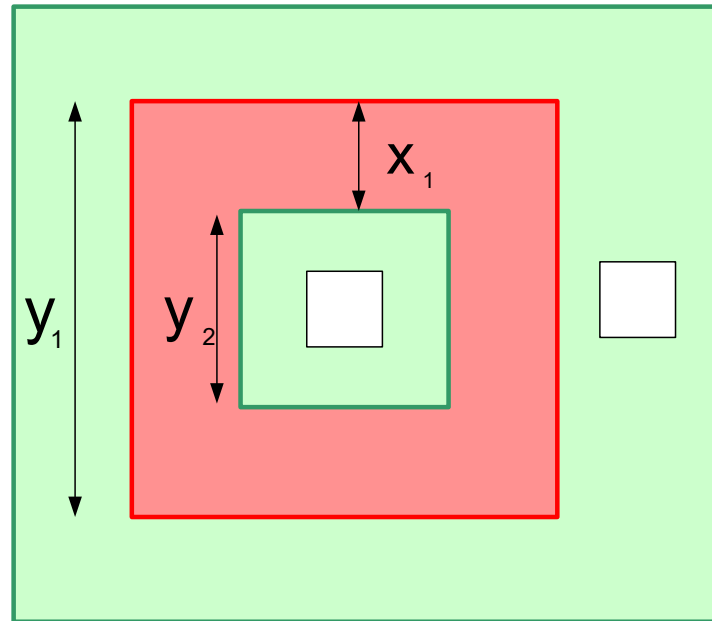


$$W_{\text{EQ}} \cong 4 \left(\frac{y_1 + y_2}{2} \right) \quad \text{or} \quad W_{\text{EQ}} \cong 4 \left(y_2 + \sqrt{2} \left[\frac{y_1 - y_2}{4} \right] \right)$$

$$L_{\text{EQ}} \cong x_1$$

Exact closed-form expressions exist which are somewhat more complicated

How high can I_0 be?

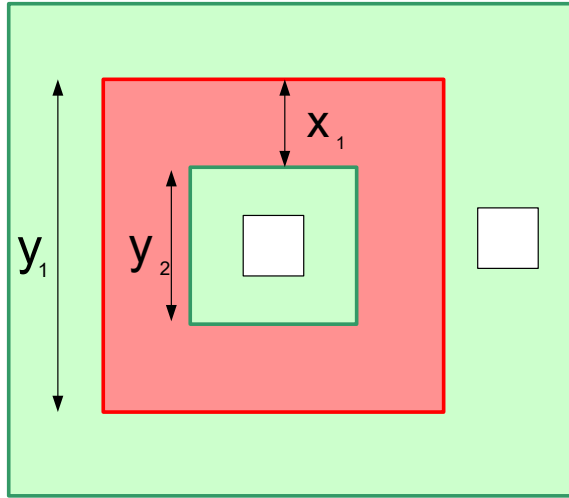Consider concentric layouts for M_1 and M_2



Recall
$$\frac{W_2}{W_1} = \frac{\mu_n}{\mu_p} \left(\frac{V_{EB1}}{V_{EB2}} \right)^2$$

Assume $W_2 > W_1$

Will minimize the diffusion capacitance by starting with a minimum-sized concentric device

Thus $y_2 = 6\lambda$ $x_1 = 2\lambda$ $y_1 = 10\lambda$ $W_{1min} \cong 4\lambda(6 + \sqrt{2})$

Define K_1 to be the scaling factor of W_1 above that of the minimum-sized concentric device


$$K_1 = \frac{W_1}{W_{1min}}$$

Assume, for convenience, that K is an integer

M_1 realized by placing K_1 minimum-sized concentric devices in parallel

How high can I_0 be?

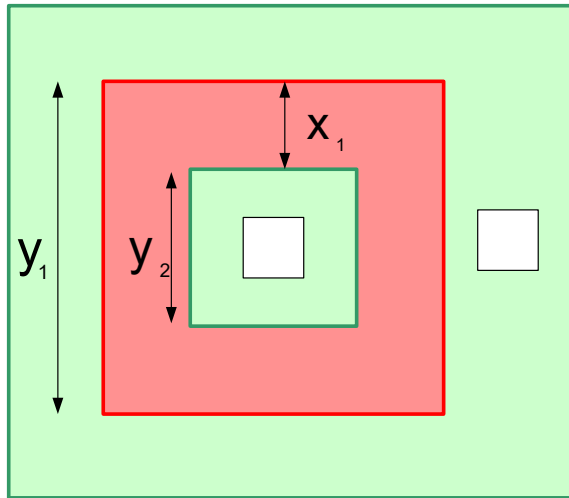Consider concentric layouts for M_1 and M_2



$$y_2 = 6\lambda \quad x_1 = 2\lambda \quad y_1 = 10\lambda$$

$$W_{1\min} \cong 4\lambda(6 + \sqrt{2})$$

$$K_1 = \frac{W_1}{W_{1\min}}$$

Consider now the concentric layout for M_1

$$P_{D1} = K_1 24\lambda$$

$$A_{D1} = K_1 (6\lambda)^2$$

$$A_{\text{GATE}1} = K_1 (48\lambda^2 + 16\lambda^2)$$

Consider now the concentric layout for M_2

The minimum-sized layout (gate, source, and drain) for the p-channel transistors are identical to those for n-channel transistors


Define K_2 to be the scaling factor for W_2 above that of a minimum-sized concentric device

$$P_{D2} = K_2 24\lambda$$

$$A_{D2} = K_2 (6\lambda)^2$$

How high can I_0 be?

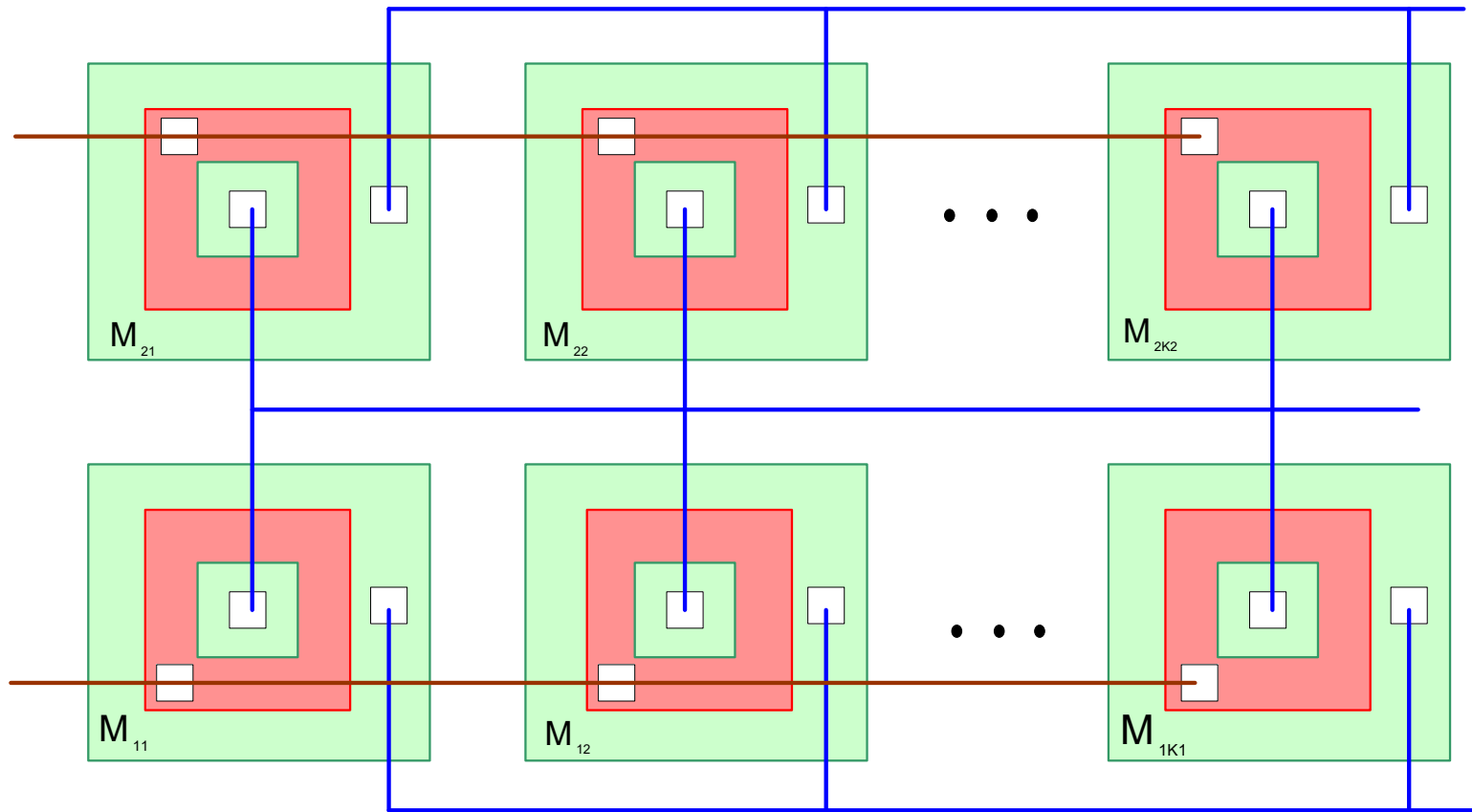Consider concentric layouts for M_1 and M_2




Individual segments can be a little bigger than minimum sized w/o major change in performance

May select $K_1=K_2=1$

How high can I_0 be?

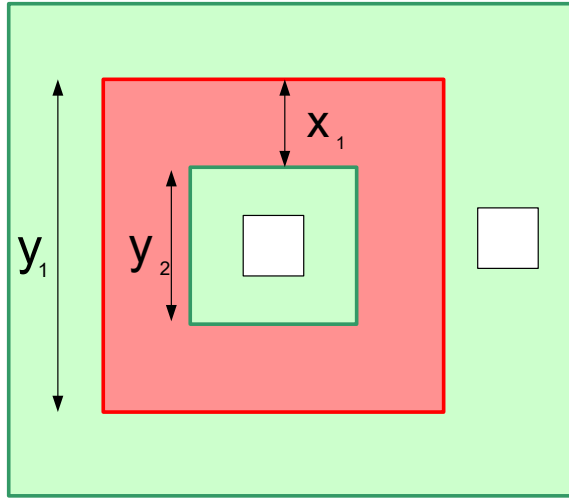Consider concentric layouts for M_1 and M_2



$$K_2 = \frac{W_2}{W_{1\min}} \quad W_2 = W_1 \frac{\mu_n}{\mu_p} \left(\frac{V_{EB1}}{V_{EB2}} \right)^2$$

$$K_2 = \frac{W_1}{W_{1\min}} \frac{\mu_n}{\mu_p} \left(\frac{V_{EB1}}{V_{EB2}} \right)^2 = K_1 \frac{\mu_n}{\mu_p} \left(\frac{V_{EB1}}{V_{EB2}} \right)^2$$

$$I_0 = \frac{\mu C_{OX} W_1 V_{EB1}}{L_{\min} (C_{P1} + C_{P2}) + C_{OX} W_1 L_{\min}^2}$$




$$I_0 = \frac{\frac{\mu C_{OX} W_1 V_{EB1}}{L_{\min}}}{(C_{P1} + C_{P2}) + C_{GS1}}$$

$$I_0 = \frac{\frac{\mu V_{EB1}}{L_{\min}^2}}{(C_{P1} + C_{P2}) + C_{GS1}} \cdot C_{OX} L_{\min} W_1$$

$$I_0 = \frac{\omega_T}{(C_{P1} + C_{P2}) + C_{GS1}} \cdot \frac{1}{2\lambda C_{OX} W_1}$$

How high can I_0 be?

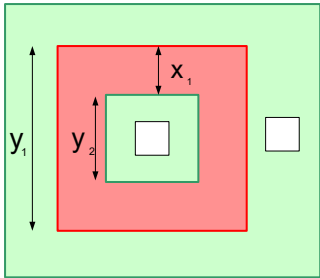Consider concentric layouts for M_1 and M_2



$$I_0 = \frac{\omega_T}{\frac{(C_{P1} + C_{P2}) + C_{GS1}}{2\lambda C_{OX} W_1}}$$

$$P_{D1} = K_1 24\lambda$$

$$A_{D1} = K_1 (6\lambda)^2$$

$$A_{GATE1} = K_1 (48\lambda^2 + 16\lambda^2)$$

$$P_{D2} = K_2 24\lambda$$

$$A_{D2} = K_2 (6\lambda)^2$$


$$W_1 \cong 4K_1\lambda(6 + \sqrt{2})$$

$$I_0 = \frac{\omega_T}{\frac{C_{OX} K_1 (48\lambda^2 + 16\lambda^2) + (C_{SWn} K_1 24\lambda + C_{BOTn} K_1 (6\lambda)^2 + C_{SWp} K_2 24\lambda + C_{BOTp} K_2 (6\lambda)^2)}{2\lambda C_{OX} 4K_1\lambda(6 + \sqrt{2})}}$$

$$I_0 = \frac{\omega_T}{\frac{C_{OX} K_1 (48\lambda^2 + 16\lambda^2) + C_{BOT} (6\lambda)^2 (K_1 + K_2) + C_{SW} 24\lambda (K_1 + K_2)}{2\lambda C_{OX} 4K_1\lambda(6 + \sqrt{2})}}$$

How high can I_0 be?

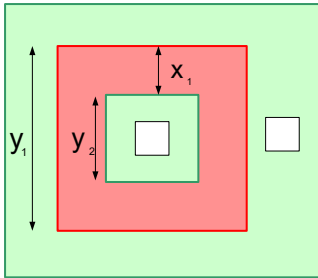Consider concentric layouts for M_1 and M_2




$$I_0 = \frac{\omega_T}{\frac{C_{OX}K_1(48\lambda^2 + 16\lambda^2) + C_{BOT}(6\lambda)^2(K_1 + K_2) + C_{SW}24\lambda(K_1 + K_2)}{2\lambda C_{OX}4K_1\lambda(6 + \sqrt{2})}}$$


$$I_0 = \frac{\omega_T}{\frac{(8) + h_{BOT}4.5(1 + K_2/K_1) + h_{SW}3(1 + K_2/K_1)}{(6 + \sqrt{2})}}$$

$$I_0 = \frac{\omega_T}{1.08 + h_{BOT}.61(1 + K_2/K_1) + h_{SW}0.4(1 + K_2/K_1)}$$

How high can I_0 be?

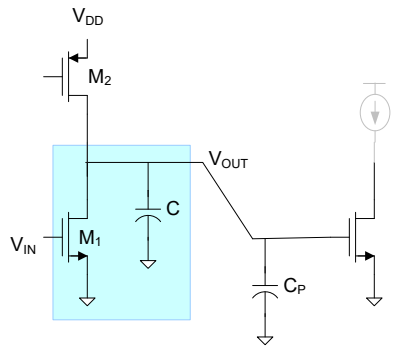

Consider concentric layout

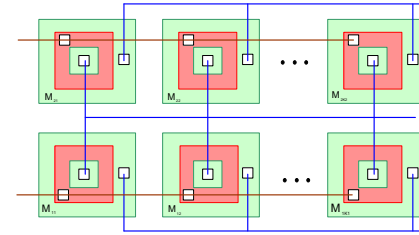

$$I_0 = \frac{\omega_T}{1.08 + h_{BOT} \cdot 61(1 + K_2 / K_1) + h_{SW} \cdot 0.4(1 + K_2 / K_1)}$$

Example: Consider the 0.25u TSMC CMOS Process with $W_1=1.5u$ and $V_{EB1}=V_{EB2}$

$$\frac{K_2}{K_1} = \frac{\mu_n}{\mu_p} \left(\frac{V_{EB1}}{V_{EB2}} \right) \quad \frac{\mu_n}{\mu_p} = 4.1$$

$$\frac{K_2}{K_1} = 4.1 \left(\frac{V_{EB1}}{V_{EB2}} \right)$$

$$I_0 = \frac{\omega_T}{1.08 + \underbrace{.19(5.1)}_{\text{BOT term}} + \underbrace{0.24(5.1)}_{\text{SW term}}}$$

$$I_0 = \frac{\omega_T}{1.08 + .95 + 1.2}$$

$$I_0 = .31\omega_T$$

Diffusion parasitics still dominate frequency degradation



SW term probably over-estimated since it is an internal SW capacitance

But a factor of 3 faster with the concentric layout compared to standard layout

How high can I_0 be?


Other layouts for enhancing speed of operation

Goal: reduce area and perimeter on drain

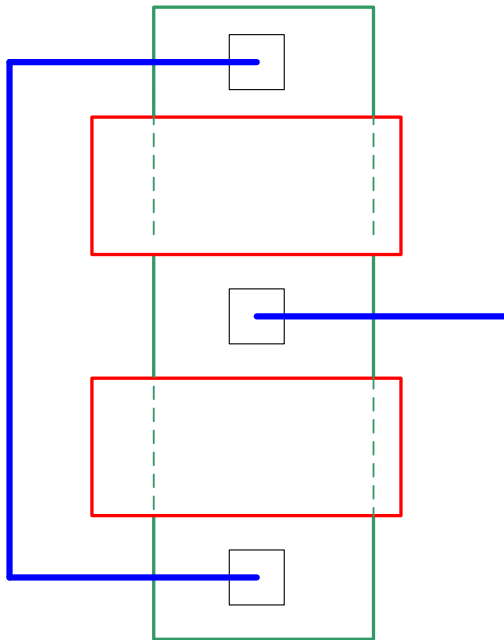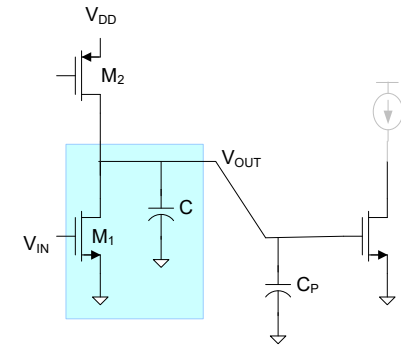

Shared-drain structure

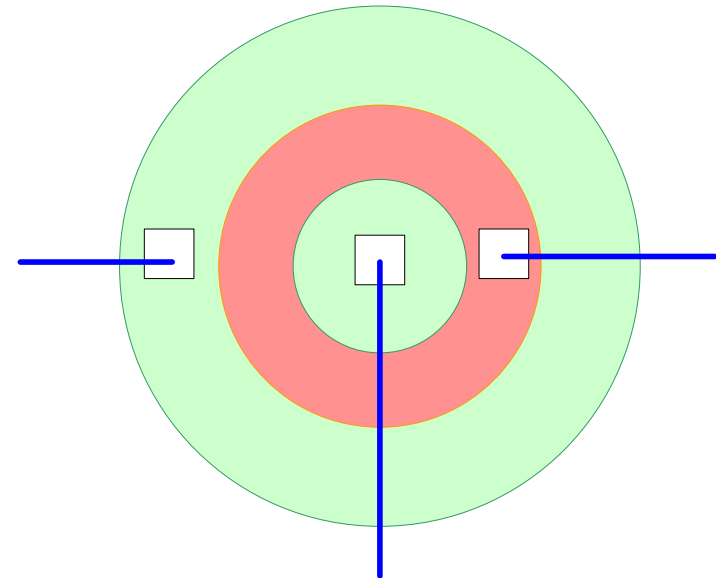(but would not be applicable if one device in well and one outside of well)




Circular-concentric structure

Though the reduced size drain structures work very well, CAD support may be limited for layout, simulation, and extraction


How high can I_0 be?

Other layouts for enhancing speed of operation

Goal: reduce area and perimeter on drain

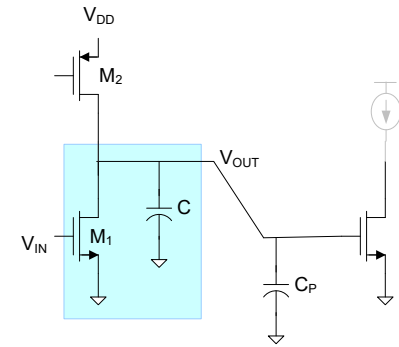

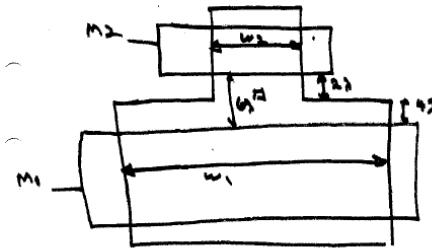n-channel load, simple layout $w_1 = 4w_2$



(but would not be applicable if one device in well and one outside of well)

$$A_D = 4\lambda w_1 + 2\lambda w_2 = 18\lambda w_2$$

$$P_D = 12\lambda + 2w_1 = 12\lambda + 8w_2$$

$$A_{G1} = 2\lambda w_1 = 8\lambda w_2$$

$$A_{G2} = 2\lambda w_2$$

$$\tilde{\omega}_0 = \frac{\sqrt{3}}{2} \frac{g_m}{C_L}$$

$$\tilde{\omega}_0 = \frac{\sqrt{3}}{2} \frac{M_1 V_{DD}}{4\lambda^2} \quad k = \frac{w_2}{6\lambda}$$

$$\frac{5/4 + 9/4 k_{\text{over}} + (1 + \frac{1}{4k}) h_{\text{sw}}}{}$$

Useful for adding loss or in high-speed gain stages

(can add loss with n-channel or p-channel device)

Parameters from 25u TSMC Process
 u 3.74E+10 1/(V*sec)

2*lambda 0.25 u
 hsw 0.61 none
 cot 0.32 none
 u/up 4.1

Integrator Io for Special Layouts

file: integrator-speed-comp

Note: Process parameters may be a little optimistic but relative performance should be as predicted

Conventional Layout

VEB1/ VEB2	K	W1	W2	SWn	SWp	BOTn	BOTp	SW comp Total	Bot comp Total	Load comp	Den	VEB1	Io, no dcf GHz	Io GHz
1	1	0.75	3.075	0.92	3.42	0.96	3.94	4.33	4.90	1	10.2	1	95.3	9.3
1	2	1.5	6.15	0.61	3.11	0.96	3.94	3.72	4.90	1	9.6	1	95.3	9.9
1	4	3	12.3	0.46	2.96	0.96	3.94	3.42	4.90	1	9.3	1	95.3	10.2
1	8	6	24.6	0.38	2.88	0.96	3.94	3.26	4.90	1	9.2	1	95.3	10.4
1	16	12	49.2	0.34	2.84	0.96	3.94	3.19	4.90	1	9.1	1	95.3	10.5
0.5	1	0.75	0.769	0.92	1.54	0.96	0.98	2.46	1.94	1	5.4	1	95.3	17.6
0.5	2	1.5	1.538	0.61	1.24	0.96	0.98	1.85	1.94	1	4.8	1	95.3	19.9
0.5	4	3	3.075	0.46	1.08	0.96	0.98	1.54	1.94	1	4.5	1	95.3	21.2
0.5	8	6	6.15	0.38	1.01	0.96	0.98	1.39	1.94	1	4.3	1	95.3	22.0
0.5	16	12	12.3	0.34	0.97	0.96	0.98	1.31	1.94	1	4.3	1	95.3	22.4
2	1	0.75	12.3	0.92	10.92	0.96	15.74	11.83	16.70	1	29.5	1	95.3	3.2
2	2	1.5	24.6	0.61	10.61	0.96	15.74	11.22	16.70	1	28.9	1	95.3	3.3
2	4	3	49.2	0.46	10.46	0.96	15.74	10.92	16.70	1	28.6	1	95.3	3.3
2	8	6	98.4	0.38	10.39	0.96	15.74	10.77	16.70	1	28.5	1	95.3	3.3
2	16	12	196.8	0.34	10.35	0.96	15.74	10.69	16.70	1	28.4	1	95.3	3.4
1	1	0.75	3.075	0.92	3.42	0.96	3.94	4.33	4.90	1	10.2	1.5	142.9	14.0
1	2	1.5	6.15	0.61	3.11	0.96	3.94	3.72	4.90	1	9.6	1.5	142.9	14.9
1	4	3	12.3	0.46	2.96	0.96	3.94	3.42	4.90	1	9.3	1.5	142.9	15.3
1	8	6	24.6	0.38	2.88	0.96	3.94	3.26	4.90	1	9.2	1.5	142.9	15.6
1	16	12	49.2	0.34	2.84	0.96	3.94	3.19	4.90	1	9.1	1.5	142.9	15.7
0.5	1	0.75	0.769	0.92	1.54	0.96	0.98	2.46	1.94	1	5.4	1.5	142.9	26.5
0.5	2	1.5	1.538	0.61	1.24	0.96	0.98	1.85	1.94	1	4.8	1.5	142.9	29.8
0.5	4	3	3.075	0.46	1.08	0.96	0.98	1.54	1.94	1	4.5	1.5	142.9	31.9
0.5	8	6	6.15	0.38	1.01	0.96	0.98	1.39	1.94	1	4.3	1.5	142.9	33.0
0.5	16	12	12.3	0.34	0.97	0.96	0.98	1.31	1.94	1	4.3	1.5	142.9	33.6
2	1	0.75	12.3	0.92	10.92	0.96	15.74	11.83	16.70	1	29.5	1.5	142.9	4.8
2	2	1.5	24.6	0.61	10.61	0.96	15.74	11.22	16.70	1	28.9	1.5	142.9	4.9
2	4	3	49.2	0.46	10.46	0.96	15.74	10.92	16.70	1	28.6	1.5	142.9	5.0
2	8	6	98.4	0.38	10.39	0.96	15.74	10.77	16.70	1	28.5	1.5	142.9	5.0
2	16	12	196.8	0.34	10.35	0.96	15.74	10.69	16.70	1	28.4	1.5	142.9	5.0
1	1	0.75	3.075	0.92	3.42	0.96	3.94	4.33	4.90	1	10.2	2	190.6	18.6
1	2	1.5	6.15	0.61	3.11	0.96	3.94	3.72	4.90	1	9.6	2	190.6	19.8
1	4	3	12.3	0.46	2.96	0.96	3.94	3.42	4.90	1	9.3	2	190.6	20.5
1	8	6	24.6	0.38	2.88	0.96	3.94	3.26	4.90	1	9.2	2	190.6	20.8
1	16	12	49.2	0.34	2.84	0.96	3.94	3.19	4.90	1	9.1	2	190.6	21.0
0.5	1	0.75	0.769	0.92	1.54	0.96	0.98	2.46	1.94	1	5.4	2	190.6	35.3
0.5	2	1.5	1.538	0.61	1.24	0.96	0.98	1.85	1.94	1	4.8	2	190.6	39.8
0.5	4	3	3.075	0.46	1.08	0.96	0.98	1.54	1.94	1	4.5	2	190.6	42.5
0.5	8	6	6.15	0.38	1.01	0.96	0.98	1.39	1.94	1	4.3	2	190.6	44.0
0.5	16	12	12.3	0.34	0.97	0.96	0.98	1.31	1.94	1	4.3	2	190.6	44.8
2	1	0.75	12.3	0.92	10.92	0.96	15.74	11.83	16.70	1	29.5	2	190.6	6.5
2	2	1.5	24.6	0.61	10.61	0.96	15.74	11.22	16.70	1	28.9	2	190.6	6.5
2	4	3	49.2	0.46	10.46	0.96	15.74	10.92	16.70	1	28.6	2	190.6	6.7
2	8	6	98.4	0.38	10.39	0.96	15.74	10.77	16.70	1	28.5	2	190.6	6.7
2	16	12	196.8	0.34	10.35	0.96	15.74	10.69	16.70	1	28.4	2	190.6	6.7

Note: Significant change in speed with optimal choice of design variables

Parameters from .25u TSMC Process
 u 3.74E+10 1/(V*sec)
 2*lambda 0.25 u
 hsw 0.61 none
 hbot 0.32 none
 un/up 4.1

Integrator Io for Special Layouts

file: integrato-speed-corrp

Note: Process parameters may be a little optimistic but relative performance should be as predicted

Concentric Layout

VEB1/ VEB2	K	K2	K2^A	W1	W2	SWn	SWp	BOTn	BOTp	SW comp Total	Got comp Total	Load Comp	Den	VEBt	Io, no dif GHz	Io GHz
1	1	4.8		3.7	15.2	0.25	1.19	0.19	4.53	1.44	4.73	1.08	7.24	1	88.3	13.2
1	2	8.9		6.7	27.5	0.27	1.22	0.43	8.96	1.49	8.99	1.04	11.53	1	91.3	8.3
1	4	17.1		12.7	52.1	0.29	1.23	0.91	16.63	1.52	17.53	1.02	20.08	1	93.1	4.7
1	1	4.8		3.7	15.2	0.25	1.19	0.19	4.53	1.44	4.73	1.08	7.24	1.5	132.5	19.7
1	2	8.9		6.7	27.5	0.27	1.22	0.43	8.96	1.49	8.99	1.04	11.53	1.5	136.9	12.4
1	4	17.1		12.7	52.1	0.29	1.23	0.91	16.63	1.52	17.53	1.02	20.08	1.5	139.7	7.1
1	1	4.8		3.7	15.2	0.25	1.19	0.19	4.53	1.44	4.73	1.08	7.24	2	176.6	26.3
1	2	8.9		6.7	27.5	0.27	1.22	0.43	8.96	1.49	8.99	1.04	11.53	2	182.6	16.5
1	4	17.1		12.7	52.1	0.29	1.23	0.91	16.63	1.52	17.53	1.02	20.08	2	186.3	9.5
0.5	1	1.0		3.7	3.8	0.25	0.25	0.19	0.21	0.50	0.40	1.08	1.98	1	88.3	48.1
0.5	2	2.1		6.7	6.9	0.27	0.28	0.43	0.45	0.55	0.88	1.04	2.48	1	91.3	36.4
0.5	4	4.1		12.7	13.0	0.29	0.30	0.91	0.96	0.58	1.86	1.02	3.47	1	93.1	27.5
0.5	1	1.0		3.7	3.8	0.25	0.25	0.19	0.21	0.50	0.40	1.08	1.98	1.5	132.5	72.2
0.5	2	2.1		6.7	6.9	0.27	0.28	0.43	0.45	0.55	0.88	1.04	2.48	1.5	136.9	52.6
0.5	4	4.1		12.7	13.0	0.29	0.30	0.91	0.96	0.58	1.86	1.02	3.47	1.5	139.7	41.2
0.5	1	1.0		3.7	3.8	0.25	0.25	0.19	0.21	0.50	0.40	1.08	1.98	2	176.6	96.2
0.5	2	2.1		6.7	6.9	0.27	0.28	0.43	0.45	0.55	0.88	1.04	2.48	2	182.6	78.8
0.5	4	4.1		12.7	13.0	0.29	0.30	0.91	0.96	0.58	1.86	1.02	3.47	2	186.3	54.9
2	1	20.0		3.7	60.8	0.25	4.94	0.19	77.92	5.19	78.11	1.08	84.38	1	88.3	1.1
2	2	36.4		6.7	110.0	0.27	4.97	0.43	142.47	5.24	142.90	1.04	149.18	1	91.3	0.8
2	4	69.2		12.7	208.4	0.29	4.99	0.91	271.56	5.27	272.47	1.02	278.77	1	93.1	0.3
2	1	20.0		3.7	60.8	0.25	4.94	0.19	77.92	5.19	78.11	1.08	84.38	1.5	132.5	1.7
2	2	36.4		6.7	110.0	0.27	4.97	0.43	142.47	5.24	142.90	1.04	149.18	1.5	136.9	1.0
2	4	69.2		12.7	208.4	0.29	4.99	0.91	271.56	5.27	272.47	1.02	278.77	1.5	139.7	0.5
2	1	20.0		3.7	60.8	0.25	4.94	0.19	77.92	5.19	78.11	1.08	84.38	2	176.6	2.3
2	2	36.4		6.7	110.0	0.27	4.97	0.43	142.47	5.24	142.90	1.04	149.18	2	182.6	1.3
2	4	69.2		12.7	208.4	0.29	4.99	0.91	271.56	5.27	272.47	1.02	278.77	2	186.3	0.7

Segmented Concentric Layout

1	1	4.8	2.3	3.71	15.2	0.25	1.13	0.19	2.05	1.38	2.24	1.08	4.70	1	88.3	20.3
1	2	8.9	4.35	6.71	27.5	0.27	1.19	0.43	4.06	1.46	4.49	1.04	6.99	1	91.3	13.6
1	4	17.1	8.45	12.71	52.1	0.29	1.22	0.91	8.09	1.50	8.99	1.02	11.52	1	93.1	8.3
1	1	4.8	2.3	3.71	15.2	0.25	1.13	0.19	2.05	1.38	2.24	1.08	4.70	1.5	132.5	30.4
1	2	8.9	4.35	6.71	27.5	0.27	1.19	0.43	4.06	1.46	4.49	1.04	6.99	1.5	136.9	20.4
1	4	17.1	8.45	12.71	52.1	0.29	1.22	0.91	8.09	1.50	8.99	1.02	11.52	1.5	139.7	12.4
1	1	4.8	2.3	3.71	15.2	0.25	1.13	0.19	2.05	1.38	2.24	1.08	4.70	2	176.6	40.5
1	2	8.9	4.35	6.71	27.5	0.27	1.19	0.43	4.06	1.46	4.49	1.04	6.99	2	182.6	27.3
1	4	17.1	8.45	12.71	52.1	0.29	1.22	0.91	8.09	1.50	8.99	1.02	11.52	2	186.3	16.5
0.5	1	1.0	0.4	3.71	3.8	0.25	0.20	0.19	0.06	0.44	0.26	1.08	1.78	1	88.3	53.6
0.5	2	2.1	0.91	6.71	6.9	0.27	0.25	0.43	0.18	0.52	0.61	1.04	2.17	1	91.3	43.9
0.5	4	4.1	1.94	12.71	13.0	0.29	0.28	0.91	0.42	0.57	1.33	1.02	2.92	1	93.1	32.6
0.5	1	1.0	0.4	3.71	3.8	0.25	0.20	0.19	0.06	0.44	0.26	1.08	1.78	1.5	132.5	80.4
0.5	2	2.1	0.91	6.71	6.9	0.27	0.25	0.43	0.18	0.52	0.61	1.04	2.17	1.5	136.9	65.8
0.5	4	4.1	1.94	12.71	13.0	0.29	0.28	0.91	0.42	0.57	1.33	1.02	2.92	1.5	139.7	48.9
0.5	1	1.0	0.4	3.71	3.8	0.25	0.20	0.19	0.06	0.44	0.26	1.08	1.78	2	176.6	107.2
0.5	2	2.1	0.91	6.71	6.9	0.27	0.25	0.43	0.18	0.52	0.61	1.04	2.17	2	182.6	87.7
0.5	4	4.1	1.94	12.71	13.0	0.29	0.28	0.91	0.42	0.57	1.33	1.02	2.92	2	186.3	65.2
2	1	20.0	9.9	3.71	60.8	0.25	4.89	0.19	38.05	5.13	38.24	1.08	44.45	1	88.3	2.1
2	2	36.4	18.1	6.71	110.0	0.27	4.94	0.43	70.31	5.21	70.74	1.04	77.00	1	91.3	1.2
2	4	69.2	34.5	12.71	208.4	0.29	4.97	0.91	134.86	5.26	135.77	1.02	142.04	1	93.1	0.7
2	1	20.0	9.9	3.71	60.8	0.25	4.89	0.19	38.05	5.13	38.24	1.08	44.45	1.5	132.5	3.2
2	2	36.4	18.1	6.71	110.0	0.27	4.94	0.43	70.31	5.21	70.74	1.04	77.00	1.5	136.9	1.9
2	4	69.2	34.5	12.71	208.4	0.29	4.97	0.91	134.86	5.26	135.77	1.02	142.04	1.5	139.7	1.0
2	1	20.0	9.9	3.71	60.8	0.25	4.89	0.19	38.05	5.13	38.24	1.08	44.45	2	176.6	4.3
2	2	36.4	18.1	6.71	110.0	0.27	4.94	0.43	70.31	5.21	70.74	1.04	77.00	2	182.6	2.5
2	4	69.2	34.5	12.71	208.4	0.29	4.97	0.91	134.86	5.26	135.77	1.02	142.04	2	186.3	1.3

Parameters from 0.25u TSMC process

u 3.74E+10 1/(V*sec)
 2*lambda 0.25 u
 hsw 0.61 none
 hbot 0.32 none
 'up 4.1

Lossy Integrator

Note: Process parameters may be a little optimistic but relative performance should be as predicted.



File:lossy-integrator-speed-comp

K	W2	W1	SWn	SWp	BOTn	BOTp	SW comp Total	Bot comp Total	Load comp	Den	VEB1	Io,no dif GHz	Io GHz
P-channel Load, Conventional Layout													
1	0.75	0.73	1.24	1.25	0.96	0.96	2.49	1.94	2.03	6.45	1	40.8	12.8
2	1.50	1.46	0.92	0.94	0.96	0.96	1.86	1.94	2.03	5.83	1	40.8	14.2
4	3.00	2.93	0.77	0.78	0.96	0.96	1.55	1.94	2.03	5.52	1	40.8	15.0
1	0.75	0.73	1.24	1.25	0.96	0.96	2.49	1.94	2.03	6.45	1.5	61.1	19.2
2	1.50	1.46	0.92	0.94	0.96	0.96	1.86	1.94	2.03	5.83	1.5	61.1	21.2
4	3.00	2.93	0.77	0.78	0.96	0.96	1.55	1.94	2.03	5.52	1.5	61.1	22.4
1	0.75	0.73	1.24	1.25	0.96	0.96	2.49	1.94	2.03	6.45	2	61.5	25.6
2	1.50	1.46	0.92	0.94	0.96	0.96	1.86	1.94	2.03	5.83	2	61.5	28.3
4	3.00	2.93	0.77	0.78	0.96	0.96	1.55	1.94	2.03	5.52	2	61.5	29.9
P-channel Load, Concentric Layout													
1	3.80	3.71	0.25	0.254	0.194	0.206	0.50	0.40	2.18	3.08	1	37.8	26.7
2	6.87	6.71	0.27	0.28	0.429	0.454	0.55	0.88	2.11	3.55	1	39.1	23.3
4	13.02	12.71	0.29	0.296	0.907	0.955	0.58	1.86	2.07	4.52	1	39.8	18.3
1	3.80	3.71	0.25	0.254	0.194	0.206	0.50	0.40	2.18	3.08	1.5	56.7	40.1
2	6.87	6.71	0.27	0.28	0.429	0.454	0.55	0.88	2.11	3.55	1.5	58.6	34.9
4	13.02	12.71	0.29	0.296	0.907	0.955	0.58	1.86	2.07	4.52	1.5	59.8	27.4
1	3.80	3.71	0.25	0.254	0.194	0.206	0.50	0.40	2.18	3.08	2	75.6	53.5
2	6.87	6.71	0.27	0.28	0.429	0.454	0.55	0.88	2.11	3.55	2	78.1	46.6
4	13.02	12.71	0.29	0.296	0.907	0.955	0.58	1.86	2.07	4.52	2	79.7	36.5
N-Channel Load, Simple Layout													
1	0.75	3.00					0.76	0.72	1.25	2.73	1	66.0	30.2
2	1.50	6.00					0.69	0.72	1.25	2.66	1	66.0	31.1
4	3.00	12.00					0.65	0.72	1.25	2.62	1	66.0	31.5
1	0.75	3.00					0.76	0.72	1.25	2.73	1.5	99.0	46.3
2	1.50	6.00					0.69	0.72	1.25	2.66	1.5	99.0	46.6
4	3.00	12.00					0.65	0.72	1.25	2.62	1.5	99.0	47.3
1	0.75	3.00					0.76	0.72	1.25	2.73	2	132.0	60.4
2	1.50	6.00					0.69	0.72	1.25	2.66	2	132.0	62.1
4	3.00	12.00					0.65	0.72	1.25	2.62	2	132.0	63.0
N-Channel Load, Concentric Layout													
1	3.71	14.83					0.31	0.24	1.35	1.90	1	61.2	43.4
2	6.71	26.83					0.34	0.54	1.30	2.18	1	63.3	37.8
4	12.71	50.83					0.36	1.13	1.28	2.77	1	64.5	29.8
1	3.71	14.83					0.31	0.24	1.35	1.90	1.5	91.8	65.1
2	6.71	26.83					0.34	0.54	1.30	2.18	1.5	94.9	56.7
4	12.71	50.83					0.36	1.13	1.28	2.77	1.5	96.8	44.2
1	3.71	14.83					0.31	0.24	1.35	1.90	2	122.4	86.9
2	6.71	26.83					0.34	0.54	1.30	2.18	2	126.5	75.6
4	12.71	50.83					0.36	1.13	1.28	2.77	2	129.1	59.5


Noise and Dynamic Range

Noise is a random time-domain signal that characterizes movement of electrons in devices

Example: Noise in Resistors

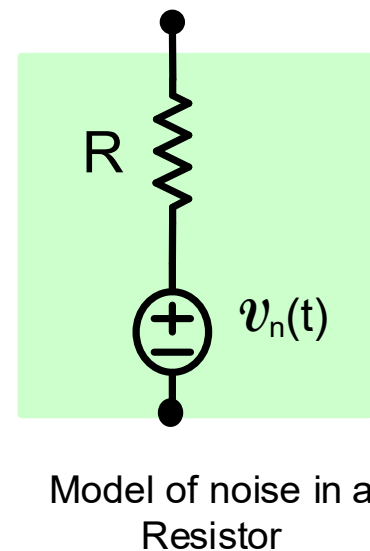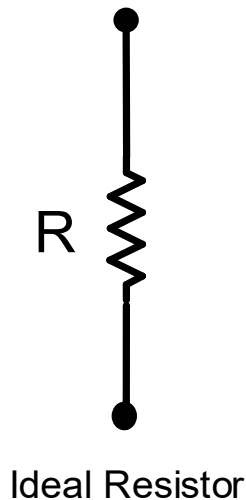

Typical noise waveform for a resistor

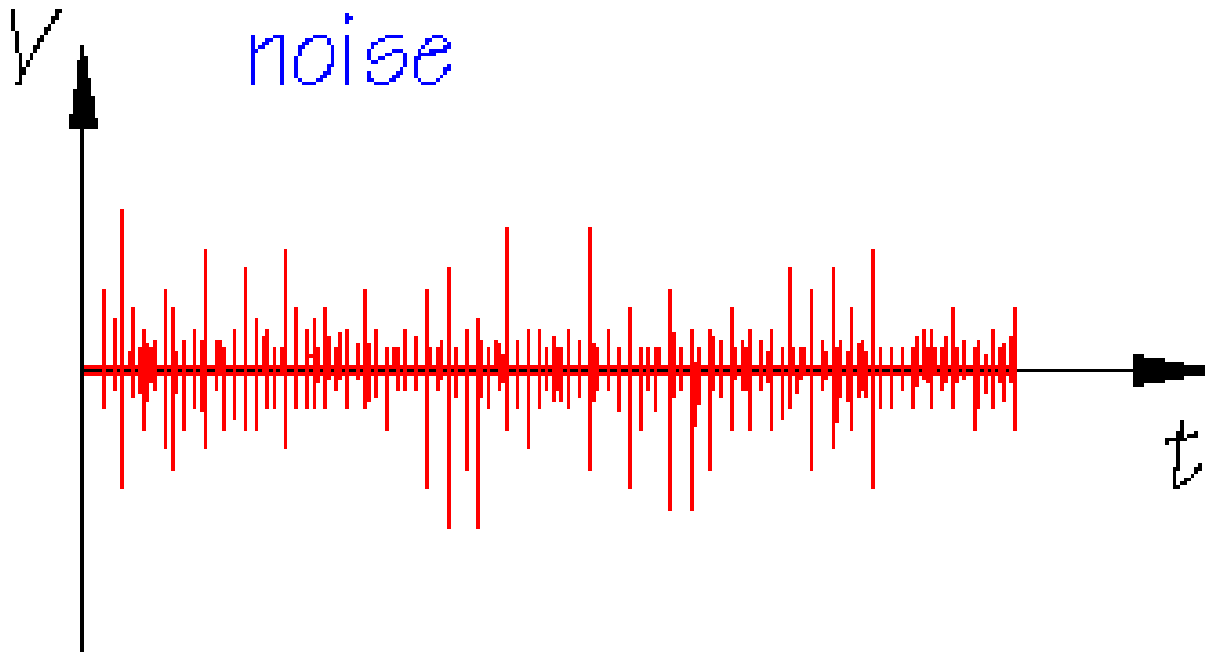


Noise sources in electronic devices are time-domain sources and can be modeled with independent voltage and current sources

Noise sources have a polarity though the statistical characteristics are independent of how the polarity is assigned


Noise is often quantified by the corresponding RMS value of the noise voltage or current at a node or branch in a circuit

Noise in a System

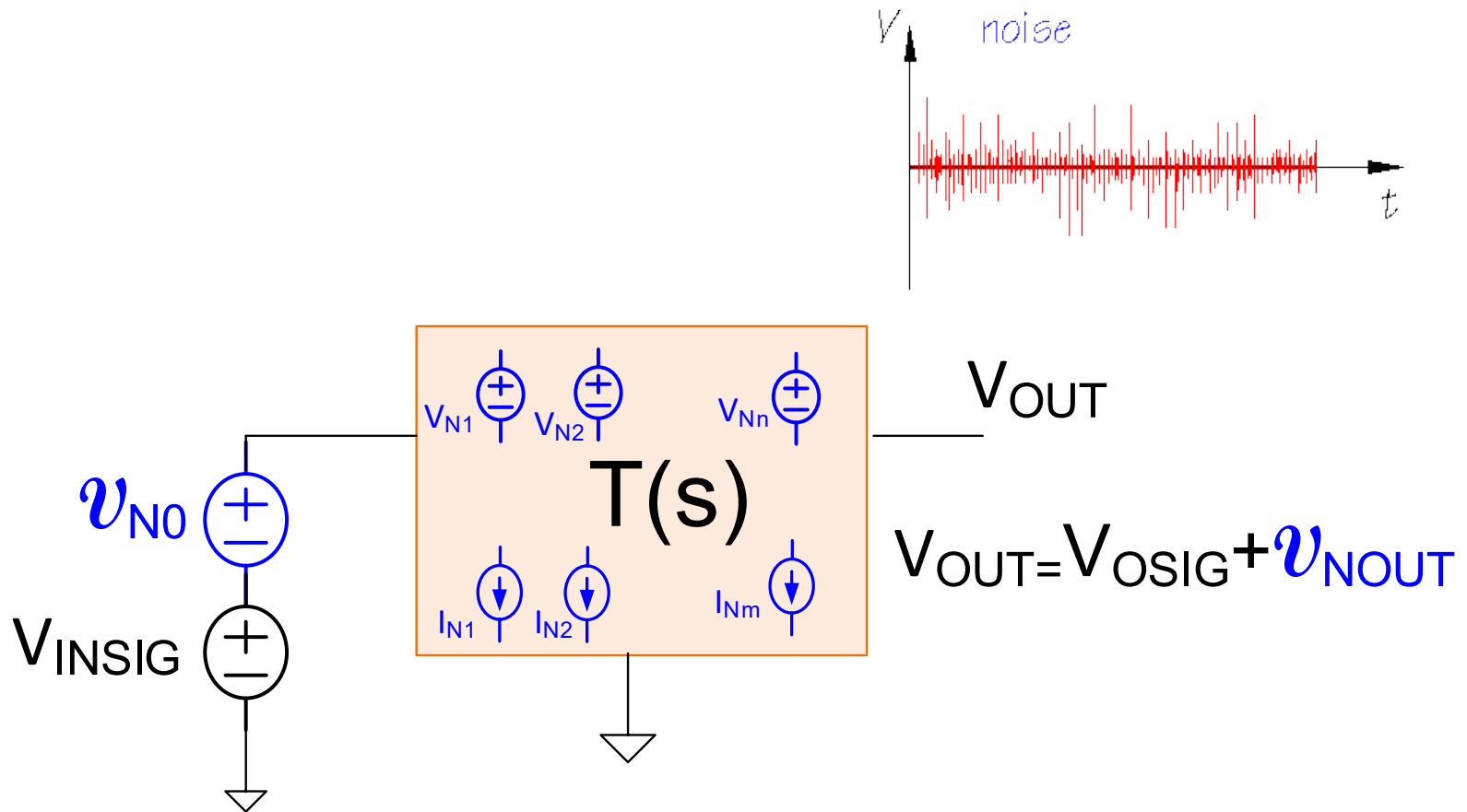

- Often many noises sources present
- One can be corrupting the input and others are internal to the system
- Noises sources often sufficiently small that superposition can be applied to determine the combined effects of all noise sources on v_{NOUT}

Characterization of a Noise Signal

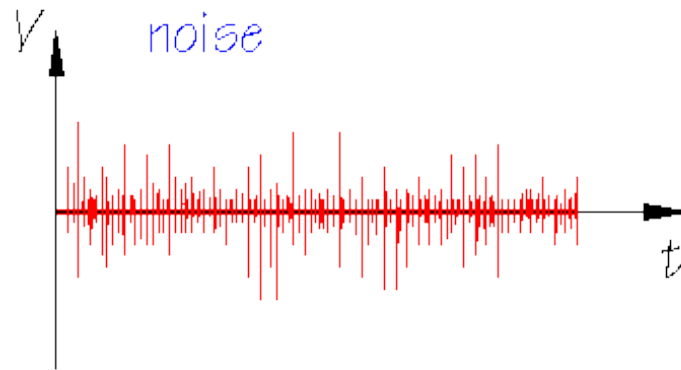


Noise naturally characterized by its RMS value

$$v_{RMS} = \lim_{T \rightarrow \infty} \int_{t_1}^{t_1+T} v^2(t) dt$$

Noise sources in electronic circuits

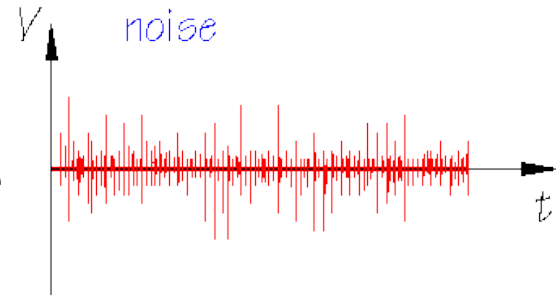Resistors, Transistors, and Diodes all have one or more internal noise sources



Capacitors and Inductors are noiseless


The presence of noise sources in devices is the only reason that input signals in filters are not made arbitrarily small to reduce effects of nonlinearity to arbitrarily small levels

The concept of “Dynamic Range” is used to characterize how small of input signals can be practically used in filters

To achieve acceptable linearity in a filter, the designer should provide just enough “dynamic range” to satisfy the requirements of an application. Any extra dynamic range will invariably come at the expense of increased design efforts, cost, complexity, and power dissipation

Dynamic Range


From Wikipedia:

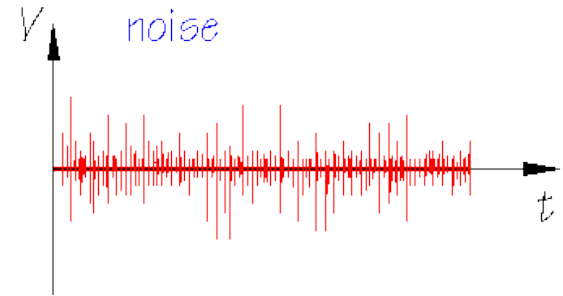

“Dynamic range is the ratio of a specified maximum level of a parameter (e.g. quantity), such as power, current, voltage, or frequency, to the minimum detectable value of that parameter “

- The maximum level of such a quantity is strongly dependent upon the distortion acceptable in a particular application
- This value may be dependent upon frequency
- The minimum detectable value of a quantity may be dependent upon application
 - Some authors interpret the minimum detectable value to be the RMS value of the quantity when the input signal is zero
- The use of a single value for the DR for a filter without knowing the specific applications is of questionable use

Dynamic Range

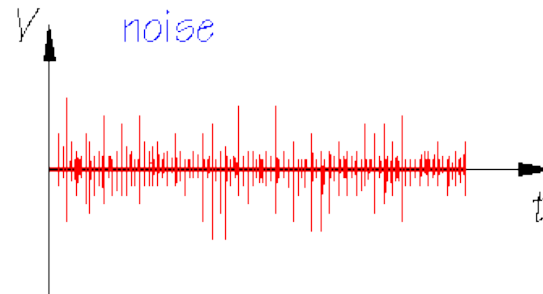

From Allen and Holberg:


“whereas noise imposes a lower limit on the range of signal amplitudes that can be meaningfully processed by a circuit, linearity often imposes the upper limit. The difference between them is the dynamic range”

From Gregorian and Temes: (in the context of op amp circuits)

“Due to the limited linear range of the op-amp, there is a maximum input signal amplitude, $V_{in,max}$ which the device can handle without generating an excessive amount of nonlinear distortion. Due to spurious signals (noise, clock feedthrough, low-level distortion such as crossover distortion, etc.) there is also a minimum input signal $V_{in,min}$ which still does not drown in noise and distortion. The dynamic range of the op amp is then defined as $20\log_{10}\left(\frac{V_{in,max}}{V_{in,min}}\right)$ measured in decibels.”

Numerous definitions for DR include some “qualitative” terms in the definition making it difficult to identify a universally accepted definition of the DR though the concept is useful

Dynamic Range


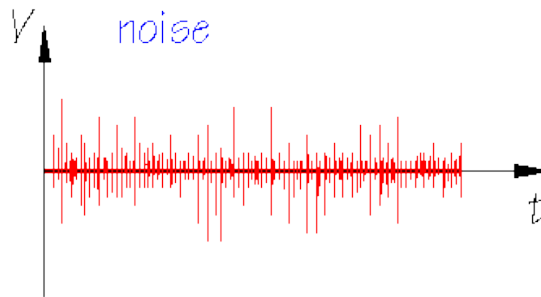


Numerous definitions for DR include some “qualitative” terms in the definition making it difficult to identify a universally accepted definition of the DR though the concept is useful

SNDR is a metric that is rigorously defined that captures some of the DR properties

Though the concept of DR is often not discussed rigorously and though there are various definitions of DR, Dynamic Range should be the primary driver of signal swing, power dissipation, and architecture selection not only in filter circuits but in analog circuit design in general

Statistical Characterization of Noise

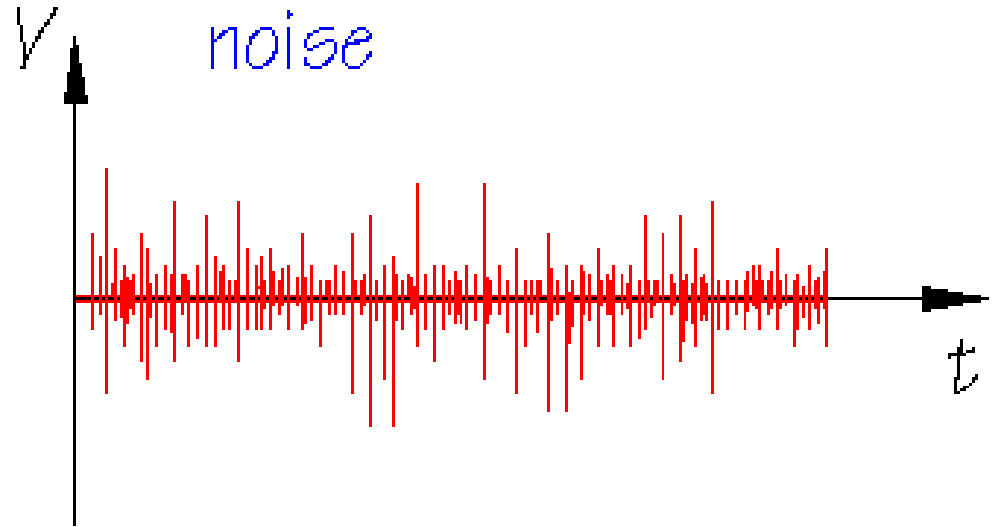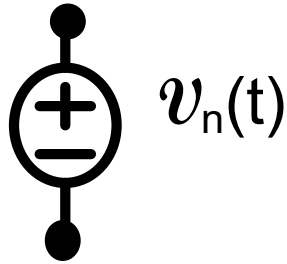

If $v_n(t_1)$ is a sample of $v_n(t)$, then $v_n(t_1)$ is a random variable


For almost all noise sources, the distribution of $v_n(t_1)$ is zero mean and often Gaussian

For many noise sources, if $v_n(t_1)$ and $v_n(t_2)$ are two distinct samples with $t_1 \neq t_2$, these random variables are identically distributed and uncorrelated (iid)

Noise (voltage) is also characterized by how it is distributed throughout the frequency spectrum by its power spectral density, S , or voltage spectral density S_v

Thus noise is characterized by both S and the amplitude distribution function and these are distinct characterizations

Statistical Characterization of Noise

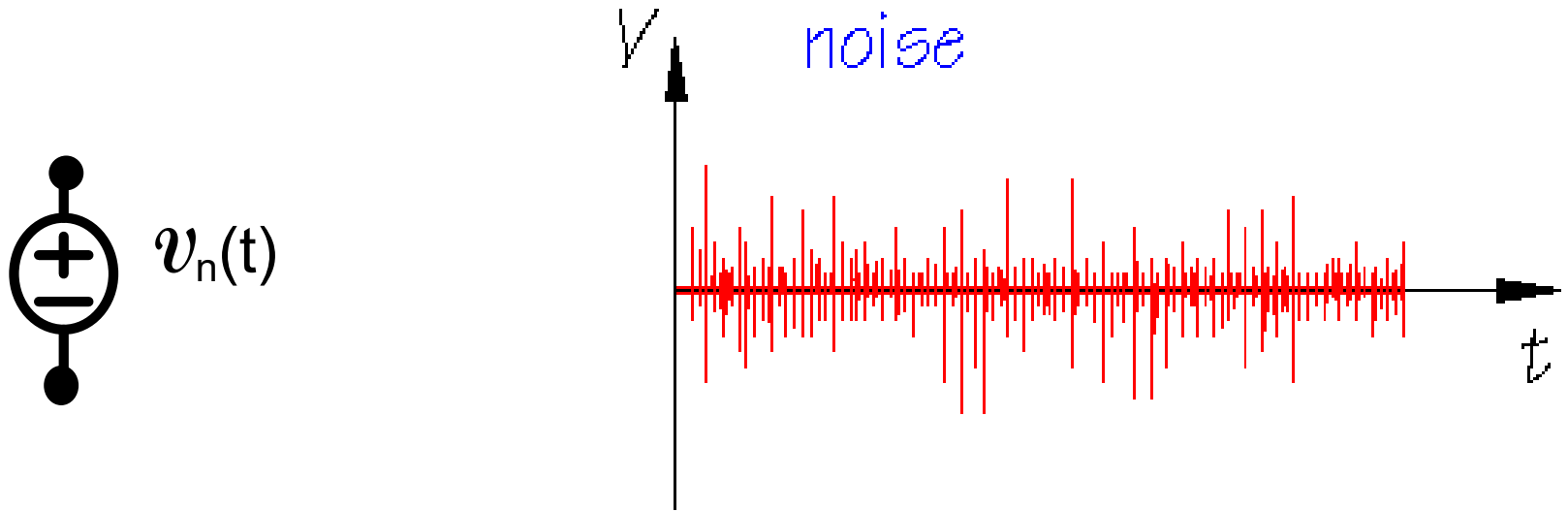

The RMS noise voltage in the frequency band $[f_1, f_2]$ is given by the expression

$$v_{RMS}(f_1, f_2) = \sqrt{\int_{f_1}^{f_2} S df}$$

$$S = S_V^2$$



or

$$S = S_I^2$$


And the total RMS noise voltage is given by the expression

$$v_{RMS} = \sqrt{\int_0^{\infty} S df}$$

Statistical Characterization of Noise

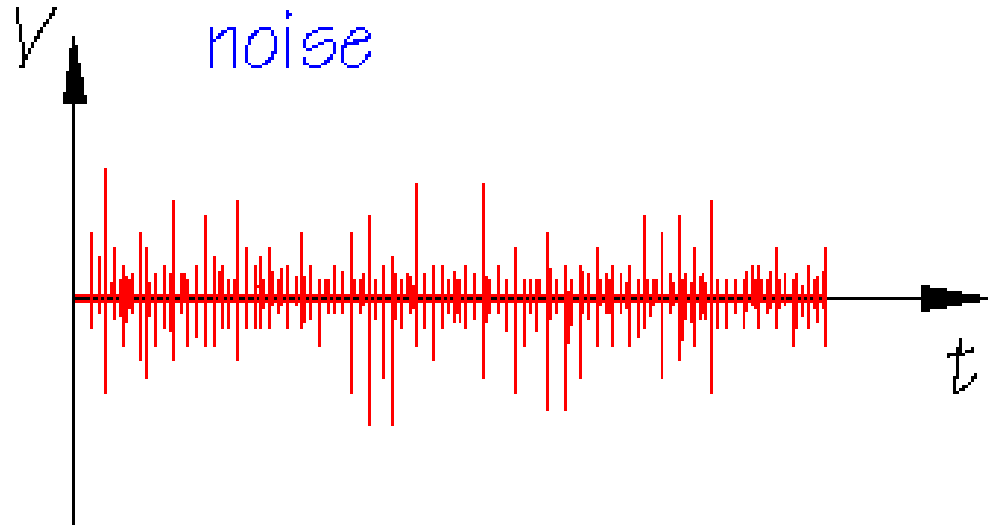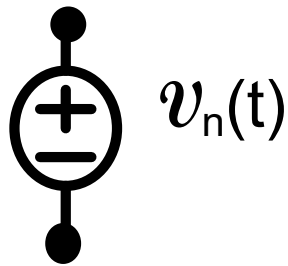
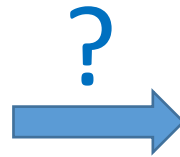
$$v_{RMS} = \sqrt{\left(\int_0^{\infty} S df \right)}$$





$$v_{RMS} = \lim_{T \rightarrow \infty} \int_{t_1}^{t_1+T} v^2(t) dt$$

Parseval's Theorem

$$\sqrt{\int_{f=0}^{\infty} S df} = \lim_{T \rightarrow \infty} \int_{t_1}^{t_1+T} v^2(t) dt$$


Statistical Characterization of Noise

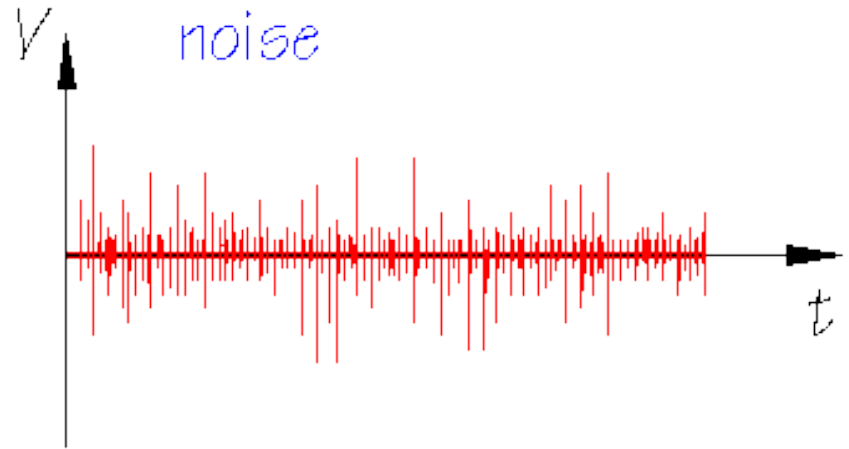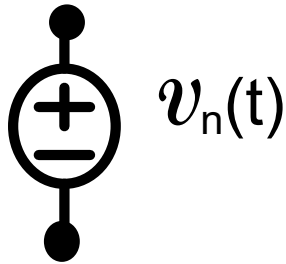

If the spectrum is flat, then the noise is termed “white” noise


White noise can have an amplitude distribution that is Gaussian or non-Gaussian

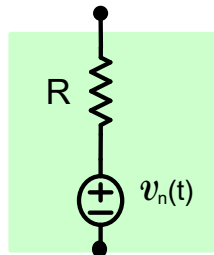For a resistor, the noise spectrum is white (over a very wide frequency range), the amplitude distribution is Gaussian, and any two distinct samples are iid.



$$S = 4kTR \quad (V^2 / \text{Hz} \text{ or } V^2 \text{ sec})$$

Dynamic Range

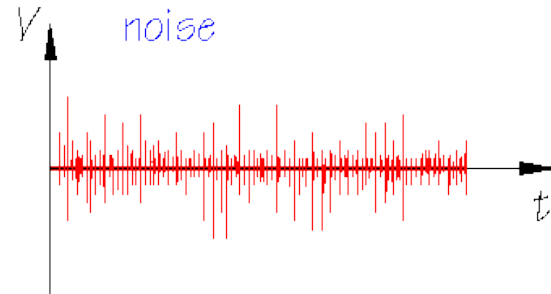

Often for audio filters, the DR is defined to be the ratio at the output between that due to a signal at 1% THD to the RMS noise voltage with the actual output spectrum multiplied by that of a C-Message bandpass filter


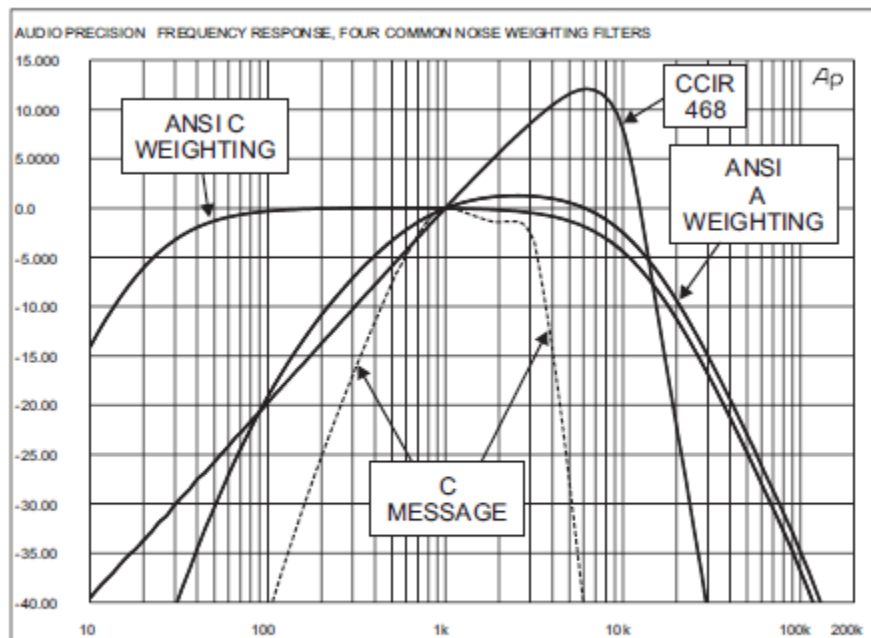


Figure 5. Weighting filter responses, actual measurements. Note that ANSI and C weighting filters are undefined above 20 kHz.


From "Audio Measurement Handbook" by Bob Metzlar

Analysis of Noise in Filter Circuits

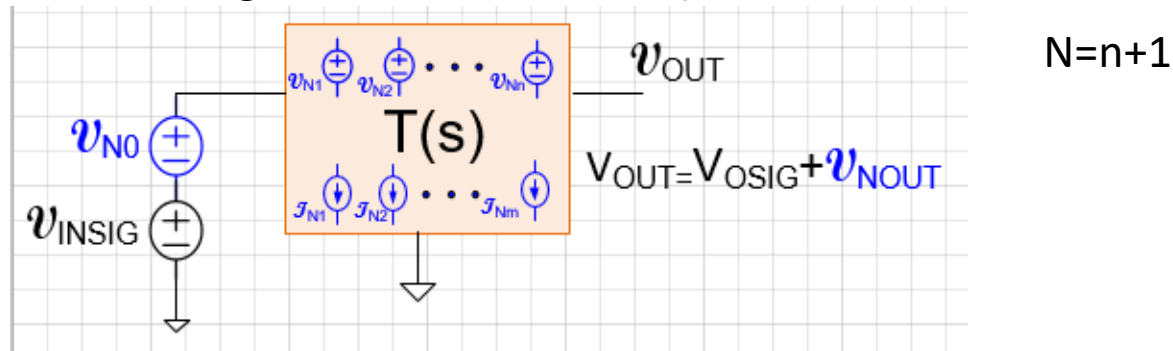Consider a filter circuit with N noise voltage sources (can be easily modified to include both noise voltage and current sources)



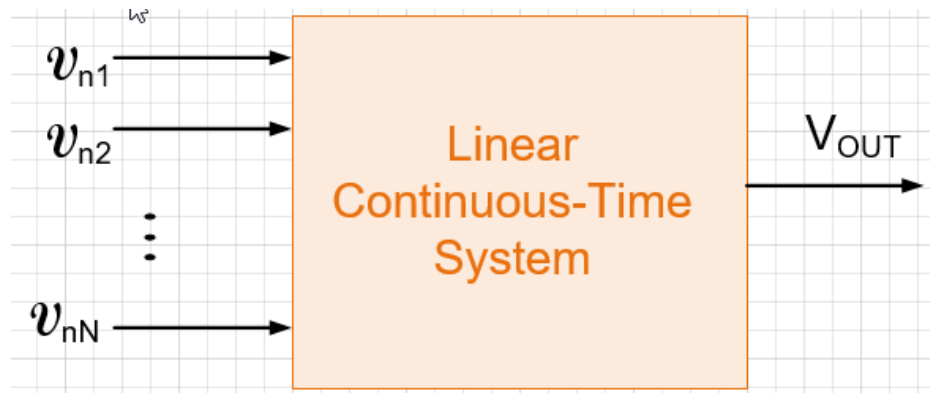The noise sources can be represented by the block diagram shown below




Assume $T_k(s)$ is the transfer function from the k th source to the output

By superposition

$$V_{OUT}(s) = \sum_{i=1}^N T_i(s) V_i(s)$$

Analysis of Noise in Filter Circuits

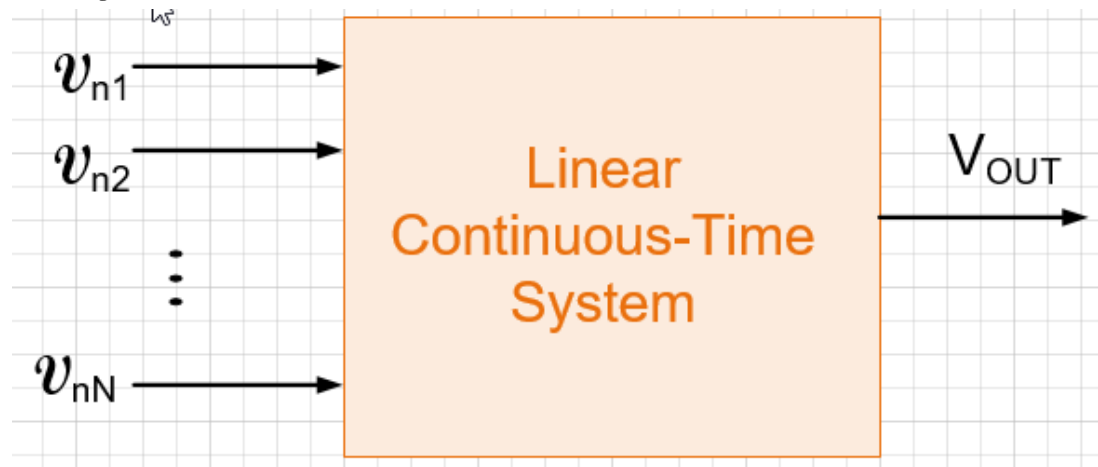


$$V_{OUT}(s) = \sum_{i=1}^N T_i(s) V_i(s)$$

If the noise sources are uncorrelated with spectral density S_1, \dots, S_N , the spectral density and the RMS noise voltage at the output are given by the equations:

$$S_{OUT} = \sum_{i=1}^N S_i \cdot |T_i(j\omega)|^2$$

$$v_{OUT_RMS} = \sqrt{\int_{f=0}^{\infty} S_{OUT} df} = \sqrt{\int_{f=0}^{\infty} \sum_{i=1}^N S_i \cdot |T_i(j\omega)|^2 df}$$

Analysis of Noise in Filter Circuits

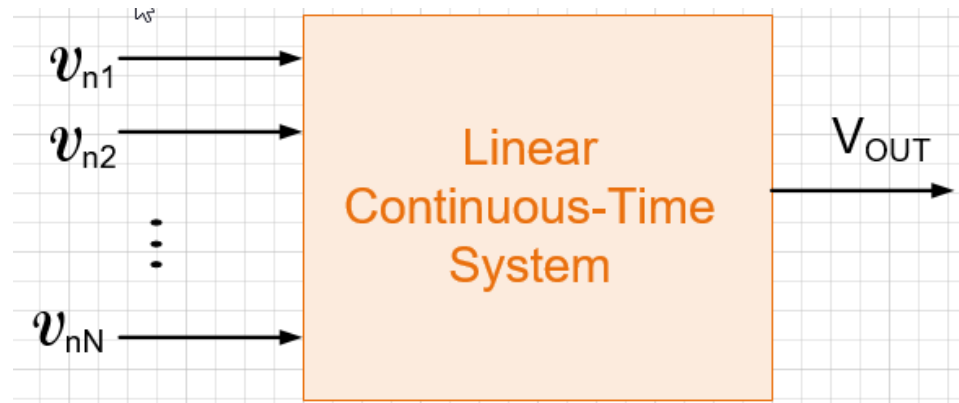

$$V_{OUT_RMS} = \sqrt{\int_{f=0}^{\infty} S_{OUT} df} = \sqrt{\int_{f=0}^{\infty} \sum_{i=1}^N S_i \cdot |T_i(j\omega)|^2 df}$$


A noise analysis in the frequency domain can be easily run in Spectre to obtain the RMS noise voltage at the output

This can be referred back to the input by dividing by the gain from the input to the output to determine the input-referred SNR (see next page)

There is now a time-domain noise analysis capability in Cadence so actual time-domain noise analysis is possible

v_{NO} usually not part of the filter so affects system but not filter

Input-Referred Noise in Filter Circuits

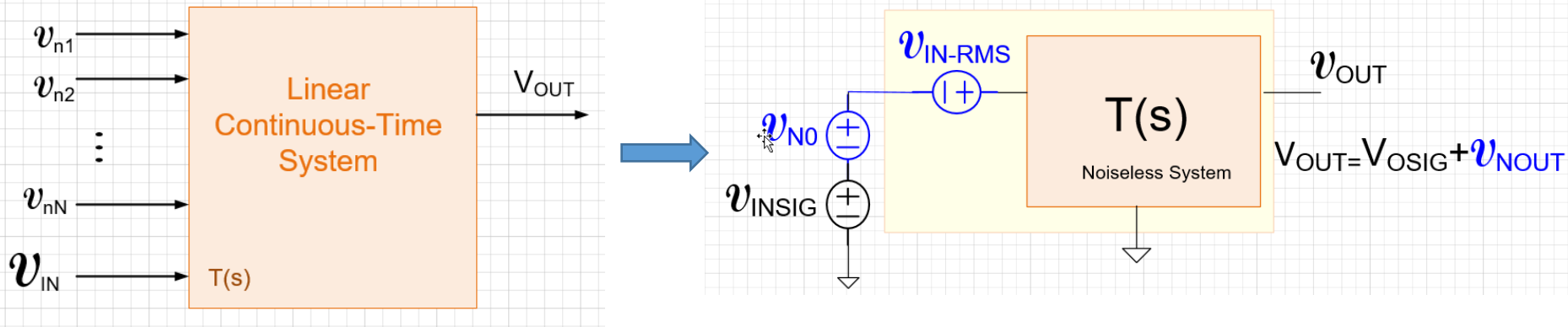

$$v_{OUT_RMS} = \sqrt{\int_{f=0}^{\infty} S_{OUT} df} = \sqrt{\int_{f=0}^{\infty} \sum_{i=1}^N S_i \cdot |T_i(j\omega)|^2 df}$$

Let $T(s)$ be the transfer function from the input to the output. (usually $T(s)$ will be distinct from each of the noise transfer functions).


The input-referred noise spectral density is given by the expression

$$S_{IN} = \frac{S_{OUT}}{|T(j\omega)|^2}$$

The input-referred RMS voltage is thus given by

$$v_{IN_RMS} = \sqrt{\int_{f=0}^{\infty} \frac{S_{OUT}}{|T(j\omega)|^2} df} = \sqrt{\int_{f=0}^{\infty} \sum_{i=1}^N S_i \cdot \frac{|T_i(j\omega)|^2}{|T(j\omega)|^2} df}$$

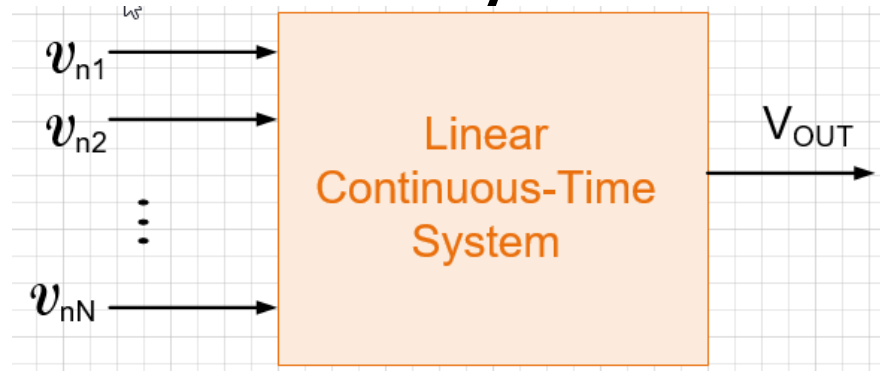Relationship between frequency domain and time domain noise analysis




$$v_{OUT_RMS} = \sqrt{\int_{f=0}^{\infty} S_{OUT} df} = \sqrt{\int_{f=0}^{\infty} \sum_{i=1}^N S_i \cdot |T_i(j\omega)|^2 df}$$

$$V_{RMS_OUT} = E \left(\sqrt{\lim_{T \rightarrow \infty} \left(\frac{1}{T} \int_0^T V_{OUT}^2(t) dt \right)} \right) \approx \sqrt{\lim_{T \rightarrow \infty} \left(\frac{1}{T} \int_0^T V_{OUT}^2(t) dt \right)}$$

Parseval's Theorem

$$V_{RMS_OUT} = v_{OUT_RMS}$$

Example: First-Order RC Network

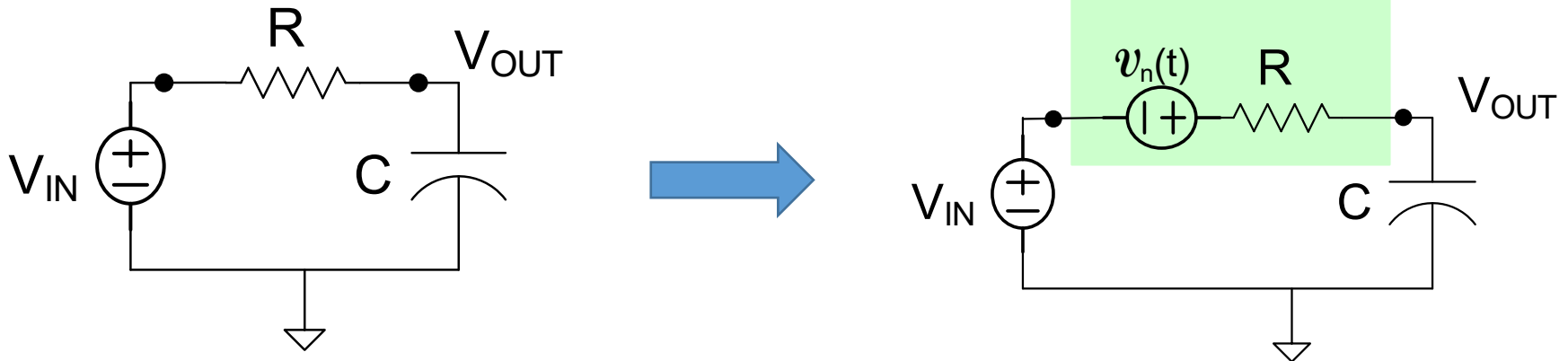


$$T(s) = \frac{1}{1+RCs}$$

$$S_{VOUT} = 4kTR \left(\frac{1}{1+(RC\omega)^2} \right)$$

$$v_{n_{RMS}} = \sqrt{\int_{f=0}^{\infty} S_{VOUT} df} = \sqrt{\int_{f=0}^{\infty} \frac{4kTR}{1+\omega^2 R^2 C^2} df}$$

Example: First-Order RC Network

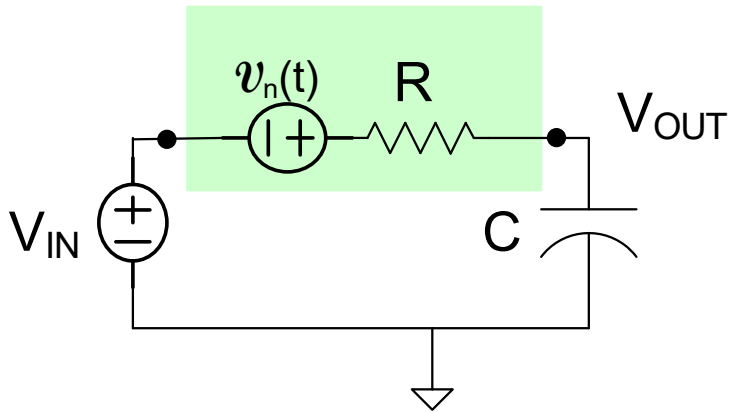



$$v_{n_{RMS}} = \sqrt{\int_{f=0}^{\infty} S_{V_{OUT}} df} = \sqrt{\int_{f=0}^{\infty} \frac{4kTR}{1 + \omega^2 R^2 C^2} df}$$

From a standard change of variable with a trig identity, it follows that

$$v_{n_{RMS}} = \sqrt{\int_{f=0}^{\infty} S_{V_{OUT}} df} = \sqrt{\frac{kT}{C}}$$

- Note the continuous-time noise voltage has an RMS value that is independent of R
- The noise contributed by the resistor is dependent only upon the capacitor value C
- This is often referred to as kT/C noise and it can be decreased at a given T only by increasing C

Example: First-Order RC Network

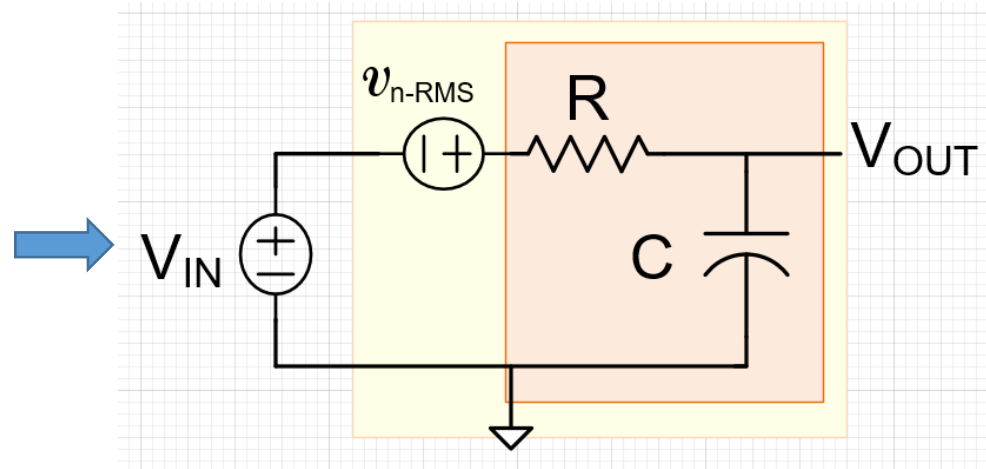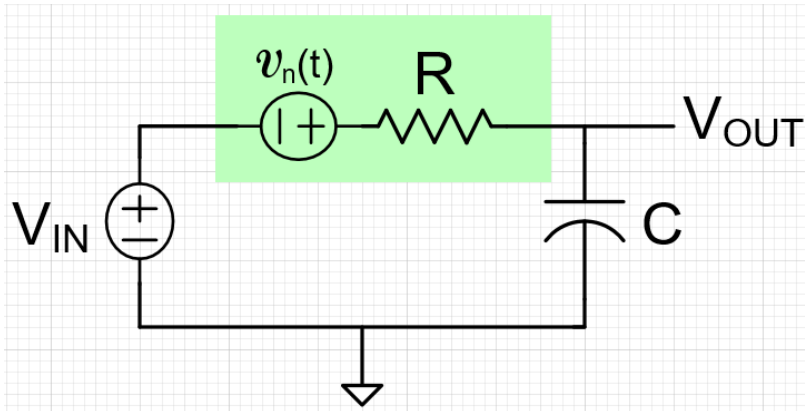


From a standard change of variable with a trig identity, it follows that

$$v_{n_{RMS}} = \sqrt{\int_{f=0}^{\infty} S_{V_{OUT}} df} = \sqrt{\frac{kT}{C}}$$


- Note the continuous-time noise voltage has an RMS value that is independent of R
- The noise contributed by the resistor is dependent only upon the capacitor value C
- This is often referred to as kT/C noise and it can be decreased at a given T only by increasing C

Noise Associated with Capacitors



"kT/C" Noise at T=300K

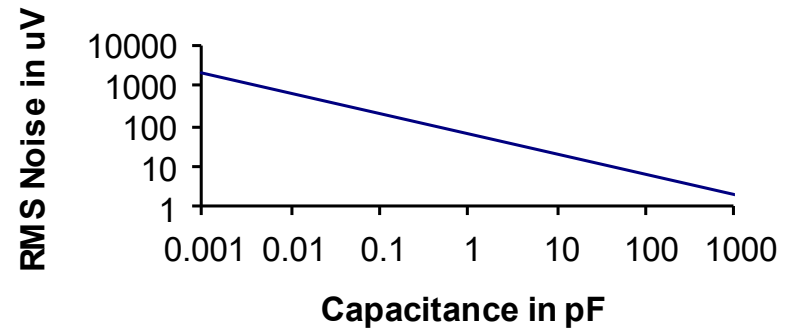


"kT/C" Noise at T=300K

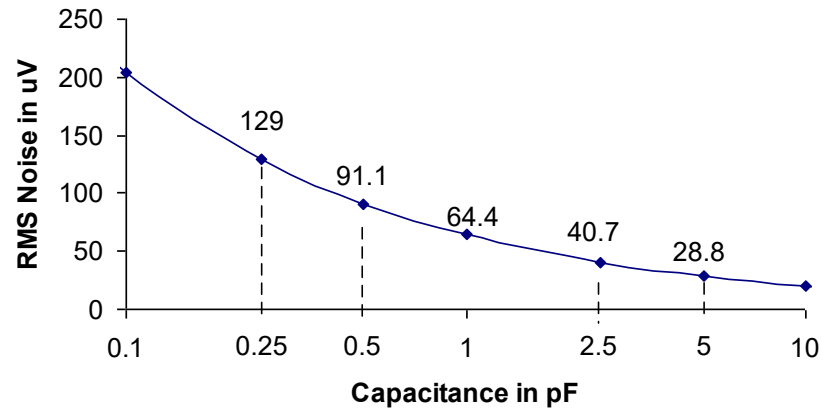

Example: Switched Capacitor Sampler

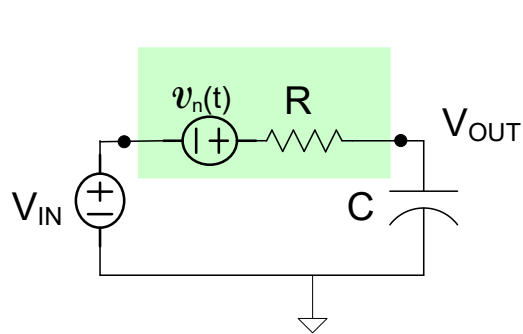
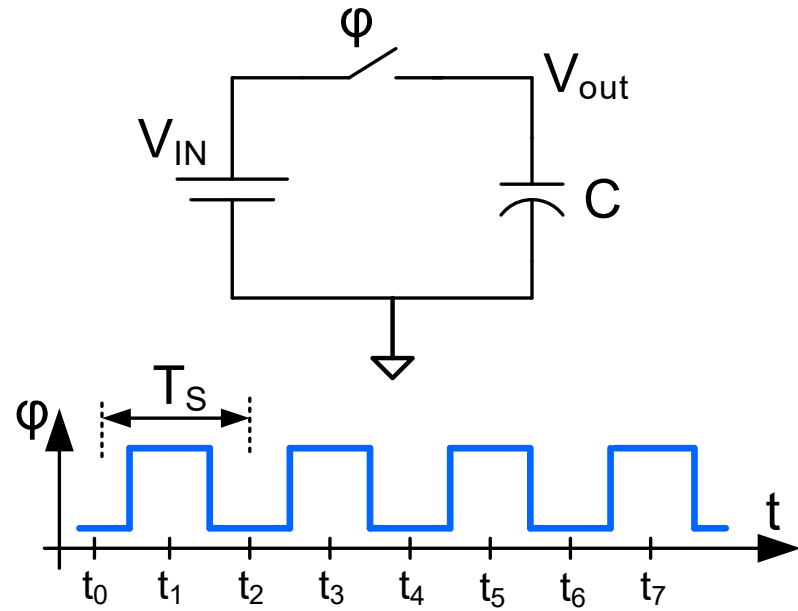


Track mode

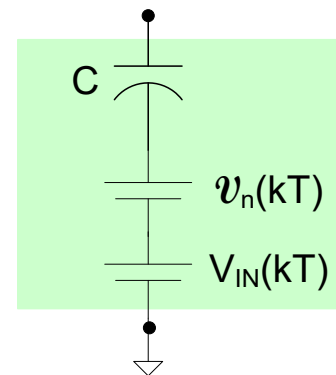


Hold mode

Example: Switched Capacitor Sampler

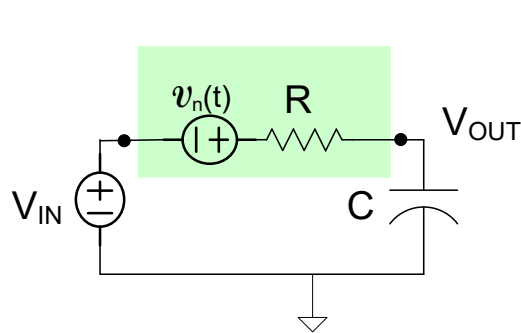
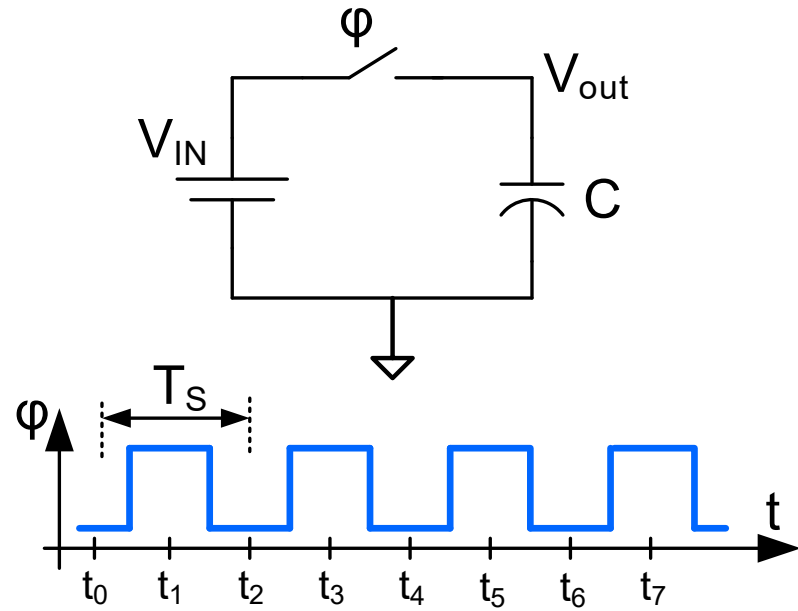


Track mode

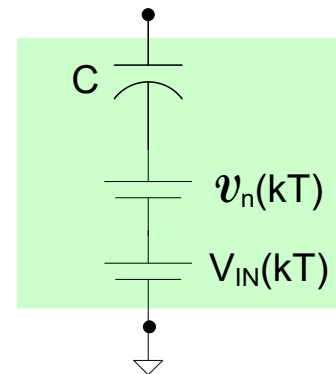


Hold mode

Example: Switched Capacitor Sampler

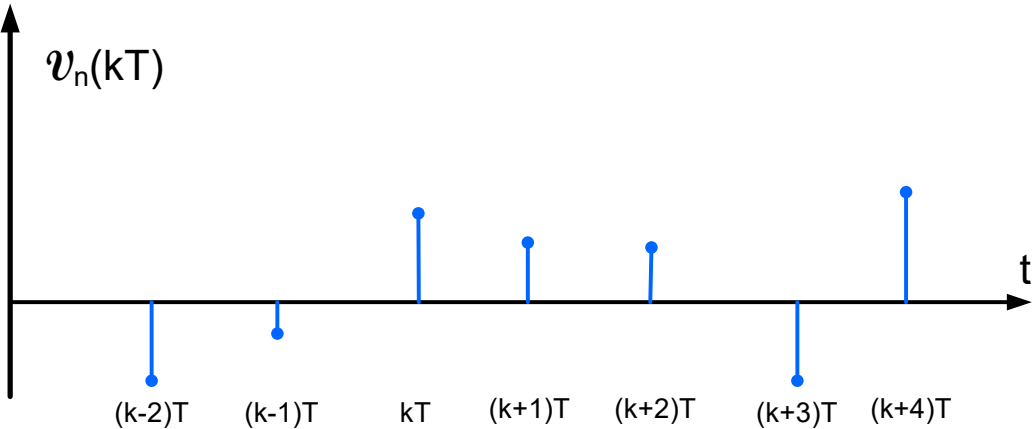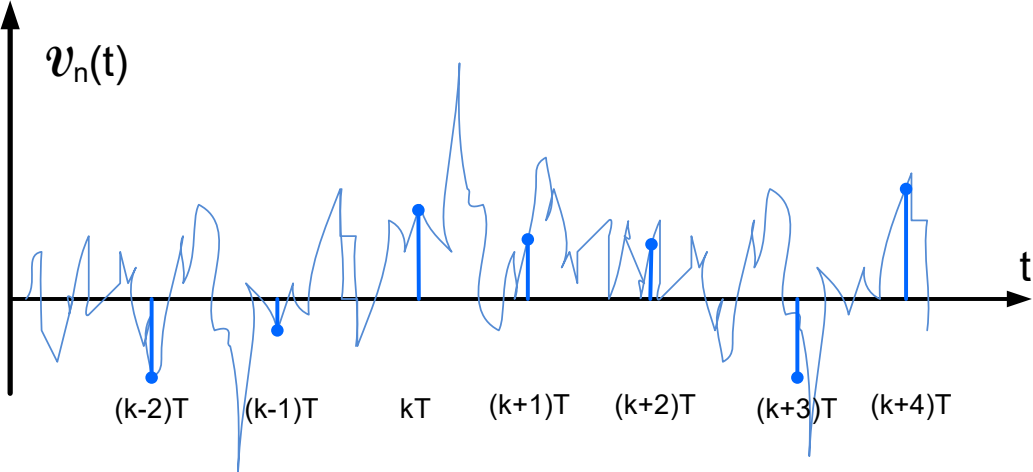

$v_n(kT)$ is a discrete-time sequence obtained by sampling a continuous-time noise waveform

Characterization of a noise sequence



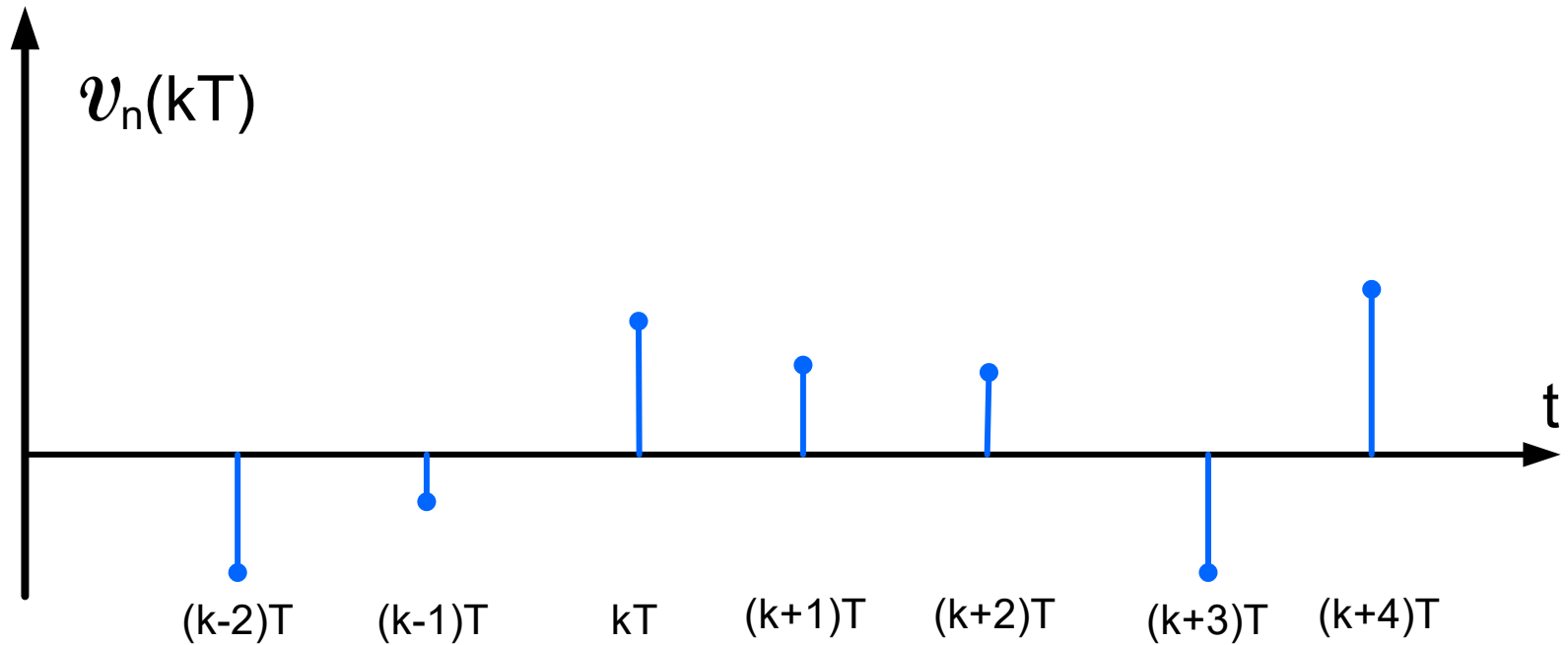


$$\hat{v}_{\text{RMS}} = E \left(\sqrt{\lim_{N \rightarrow \infty} \left(\frac{1}{N} \sum_{k=1}^N v^2(kT) \right)} \right) \underset{N/\text{large}}{\approx} \sqrt{\frac{1}{N} \sum_{k=1}^N v^2(kT)}$$


Theorem If $\mathcal{V}(t)$ is a continuous-time zero-mean noise source and $\langle \mathcal{V}(kT) \rangle$ is a sampled version of $\mathcal{V}(t)$ sampled at times $T, 2T, \dots$ then the RMS value of the continuous-time waveform is the same as that of the sampled version of the waveform. This can be expressed as $\mathcal{V}_{\text{RMS}} = \hat{\mathcal{V}}_{\text{RMS}}$

Theorem If $\mathcal{V}(t)$ is a continuous-time zero-mean noise signal and $\langle \mathcal{V}(kT) \rangle$ is a sampled version of $\mathcal{V}(t)$ sampled at times $T, 2T, \dots$ then the standard deviation of the random variable $\mathcal{V}(kT)$, denoted as $\sigma_{\hat{\mathcal{V}}}$ satisfies the expression $\sigma_{\hat{\mathcal{V}}} = \mathcal{V}_{\text{RMS}} = \hat{\mathcal{V}}_{\text{RMS}}$

Example: Switched Capacitor Sampler

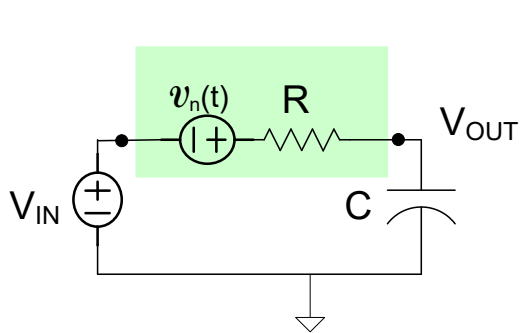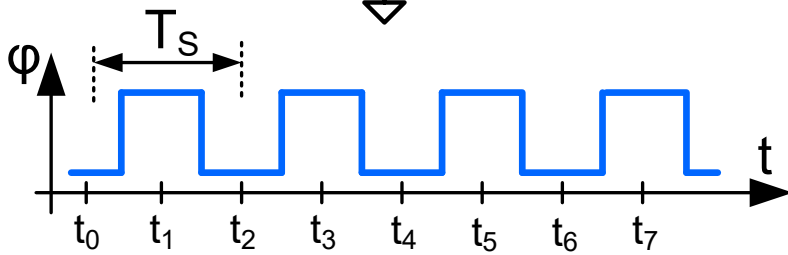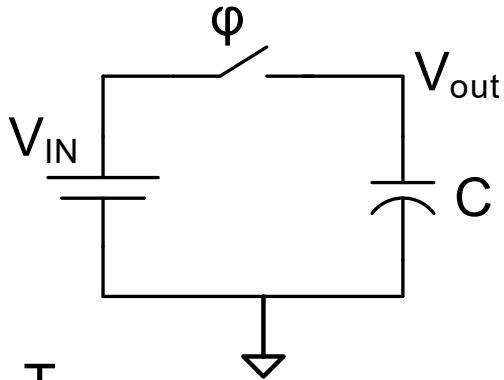


Track mode

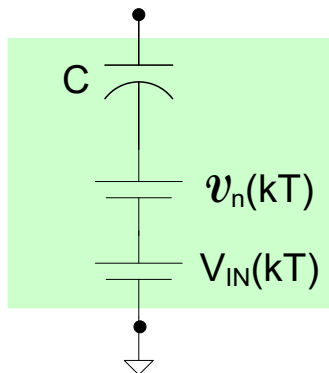


Hold mode

$$v_{n_{RMS}} = \sqrt{\frac{kT}{C}}$$

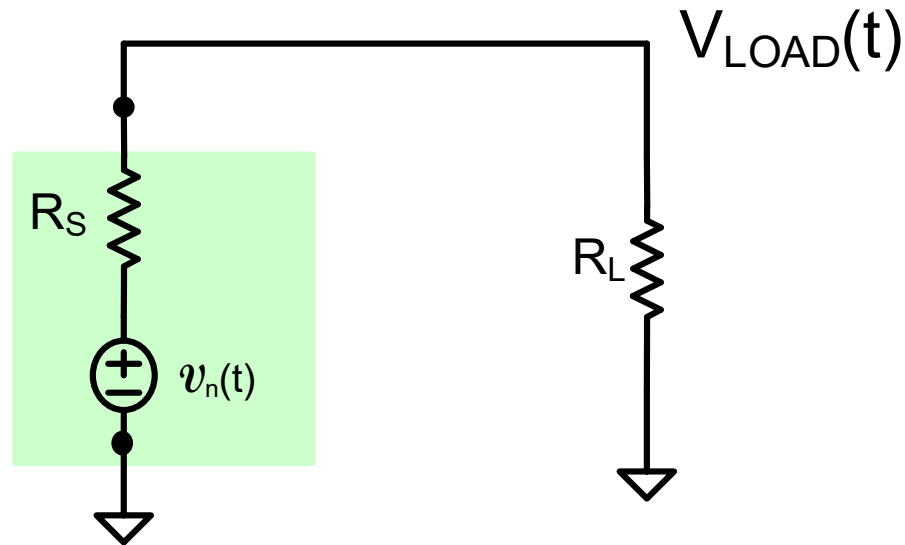What is the RMS value of the output noise voltage due to the noise on R_S ?



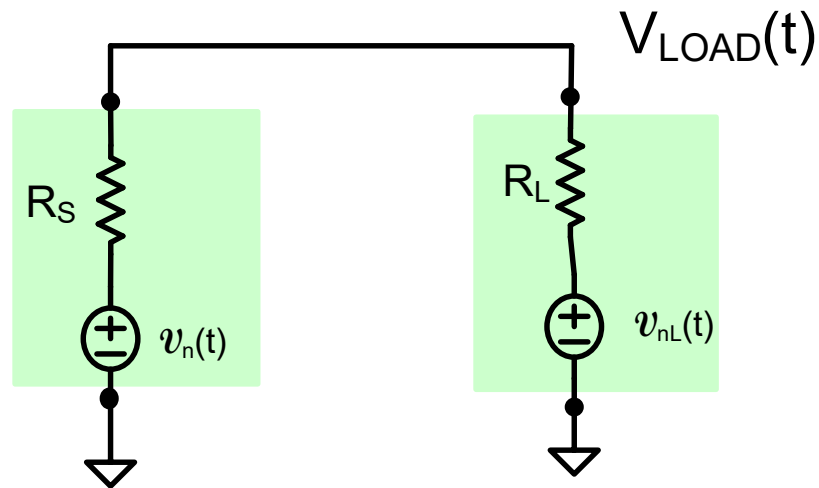What is the RMS value of the output noise voltage due to the noise on R_L and R_S ?





Stay Safe and Stay Healthy !

End of Lecture 36