

EE 508




Lecture 41

Basic Filter Components

- All Pass Networks
- Arbitrary Transfer Function Synthesis
- Impedance Transformation Circuits
- Equalizers

Update from Lecture 31 Final Project Support

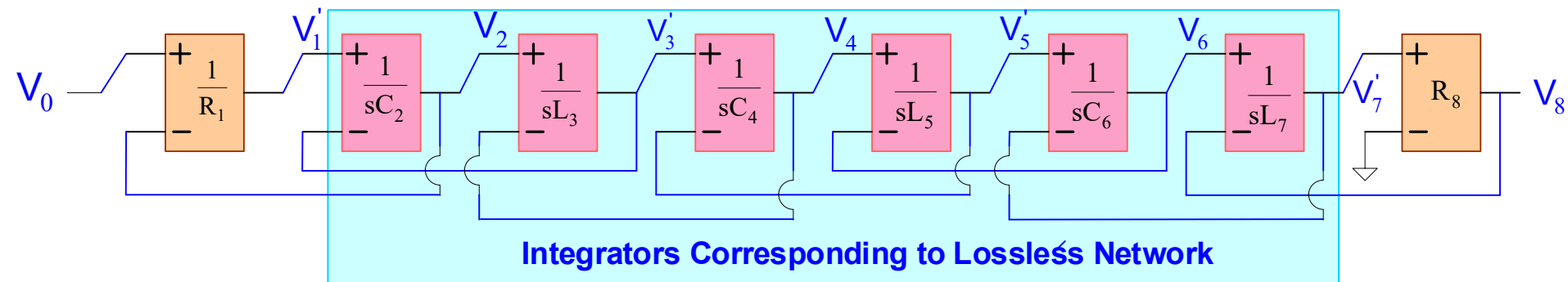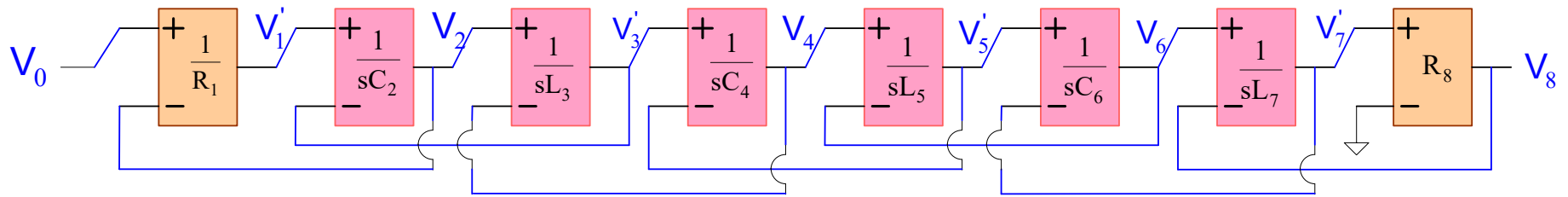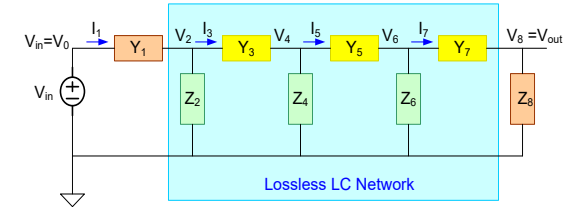
Consider now only the set of equations and disassociate them from the circuit from where they came





$$V_0 = V_{in}$$

$$V_8 = V_{out}$$

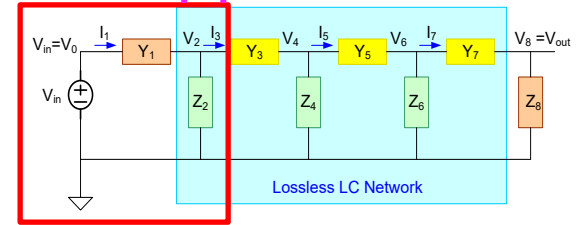Update from Lecture 31 Final Project Support



Consider the first two stages:


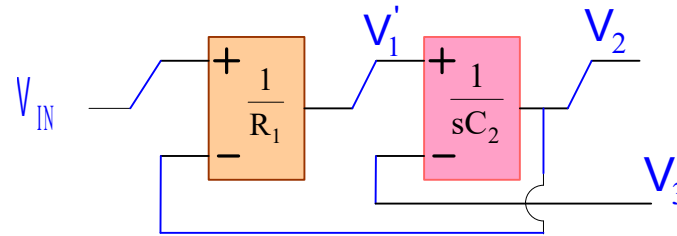
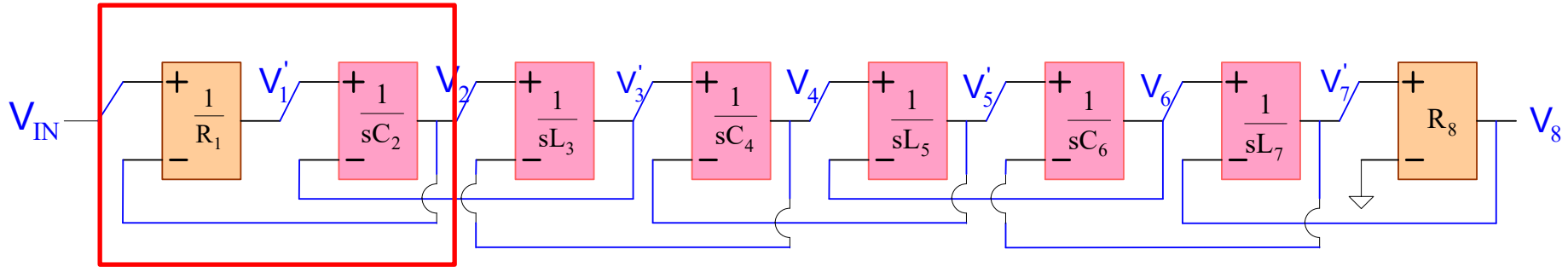


$$\left. \begin{aligned} V_1' &= (V_0 - V_2) \frac{1}{R_1} \\ V_2 &= (V_1' - V_3) \frac{1}{sC_2} \end{aligned} \right\} \begin{aligned} V_2 &= \left((V_0 - V_2) \frac{1}{R_1} - V_3 \right) \frac{1}{sC_2} \\ V_2 &= V_{IN} \left(\frac{1}{1 + R_1 C_2 s} \right) - V_3 \left(\frac{R_1}{1 + R_1 C_2 s} \right) \end{aligned}$$

These two blocks act as a single summing lossy integrator block with loss factor R_1

Update from Lecture 31 Final Project Support

Consider the last two stages:

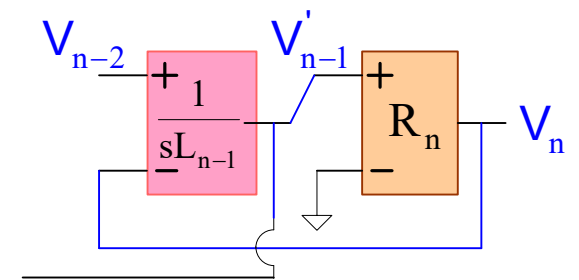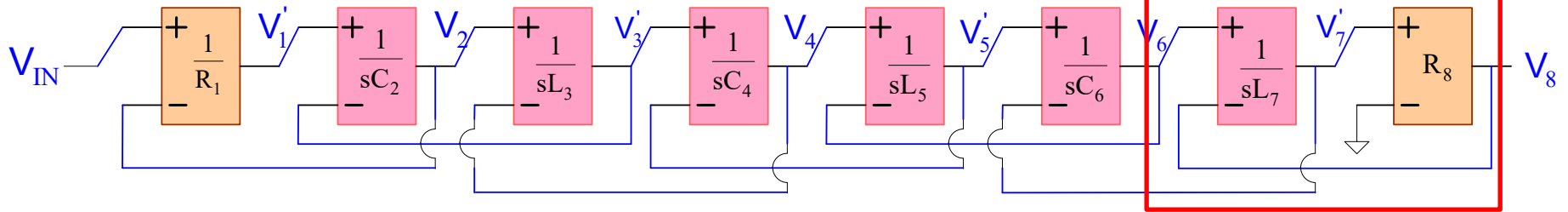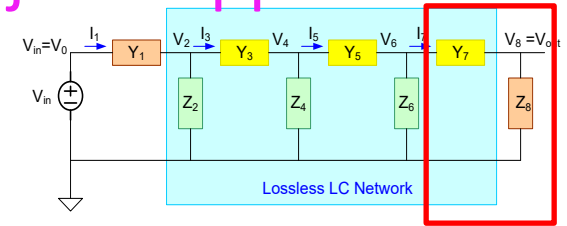


$$\left. \begin{aligned} V'_{n-1} &= (V_{n-2} - V_n) \frac{1}{sL_{n-1}} \\ V_n &= V'_{n-1} R_n \end{aligned} \right\} \begin{aligned} V_n &= (V_{n-2} - V_n) \frac{1}{sL_{n-1}} R_n \\ V_n &= V_{n-2} \left(\frac{R_n}{sL_{n-1} + R_n} \right) \end{aligned}$$


These two blocks act as a lossy integrator block with loss factor R_n

Update from Lecture 31 Final Project Support

Implementation with OTA-C Integrators:

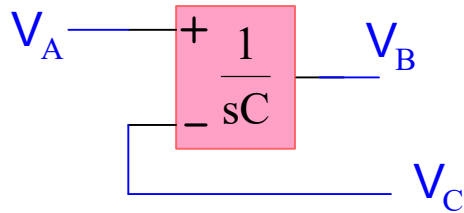

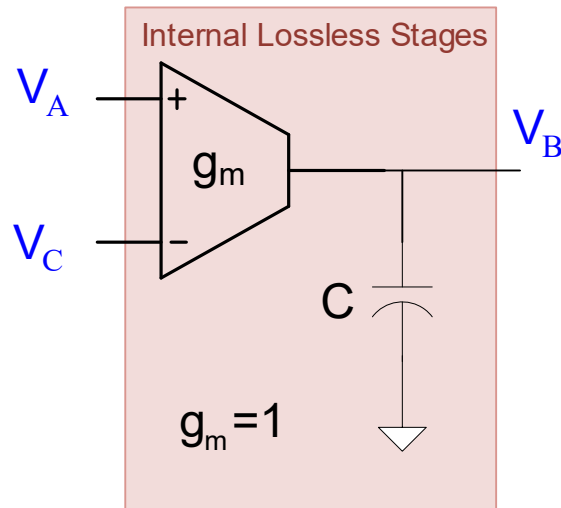
$$V_B = V_A \left(\frac{1}{sC} \right) - V_C \left(\frac{1}{sC} \right)$$




Can fix either g_m or C on each stage (showing here for $g_m=1$)

Update from Lecture 31 Final Project Support


Implementation with OTA-C Integrators:

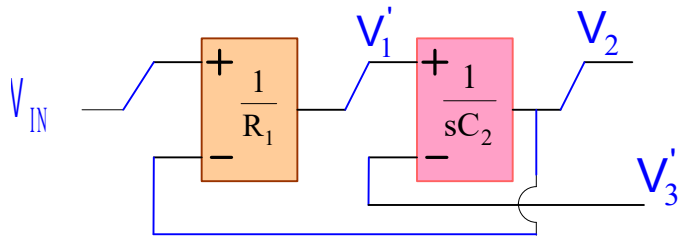
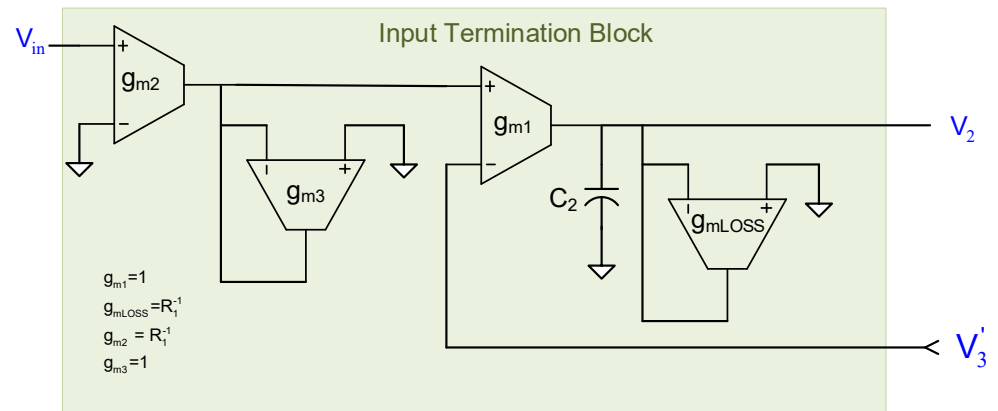
$$V_2 = V_{IN} \left(\frac{1}{1 + R_1 C_2 s} \right) - V_3' \left(\frac{R_1}{1 + R_1 C_2 s} \right)$$



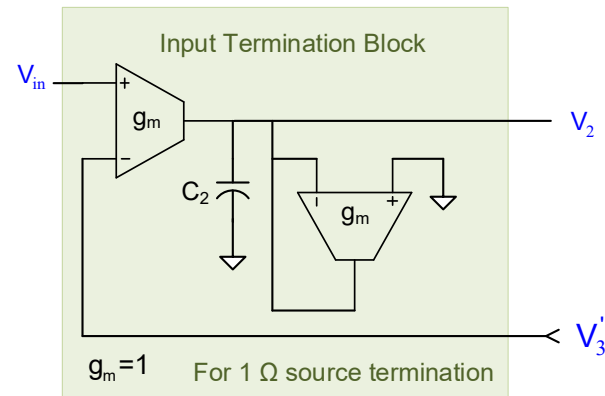
For 1 Ω source termination this simplifies to:




Can fix either g_m or C on each stage (showing here for $g_m=1$)

Update from Lecture 31 Final Project Support


Implementation with OTA-C Integrators:

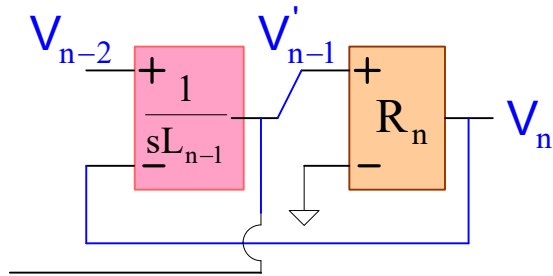
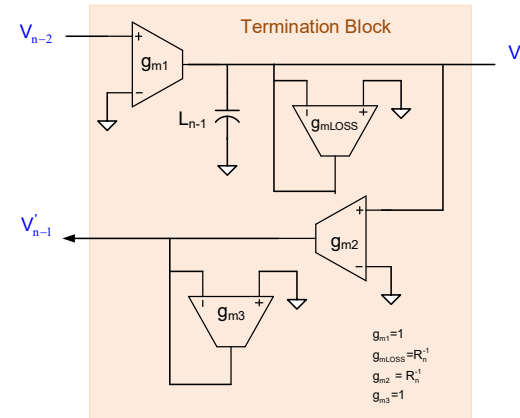
$$V_n = V_{n-2} \left(\frac{R_n}{sL_{n-1} + R_n} \right)$$



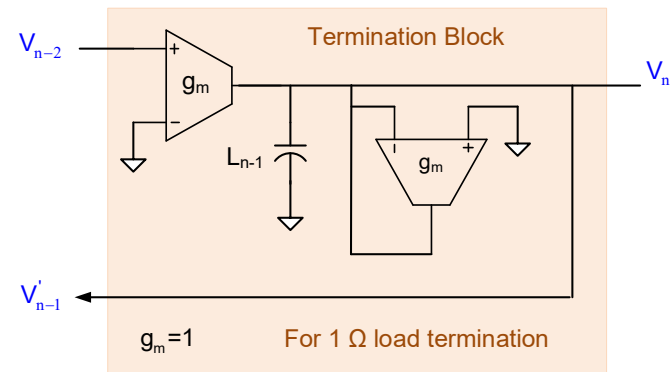For 1 Ω load termination this simplifies to:



Can fix either g_m or C on each stage (showing here for $g_m=1$)

Basic Filter Components




- All Pass Networks
- Arbitrary Transfer Function Synthesis
- Impedance Transformation Circuits
- Equalizers

All-Pass Circuits


- Magnitude of Gain is Constant
- Phase Changes with Frequency
- Used to correct undesired phase characteristics of a filter

First-Order All Pass


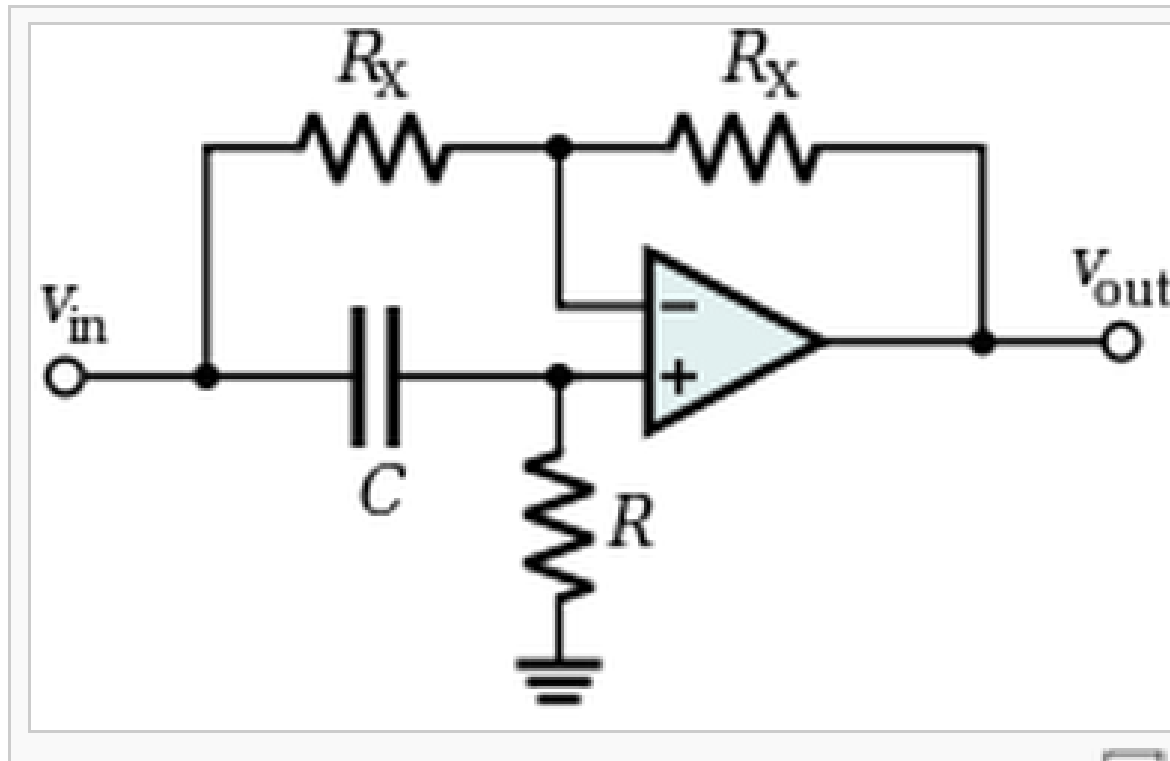


$$T(s) = \frac{s - \frac{1}{RC}}{s + \frac{1}{RC}}$$


First-Order All Pass

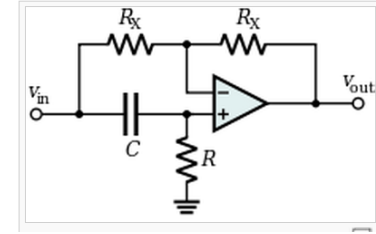
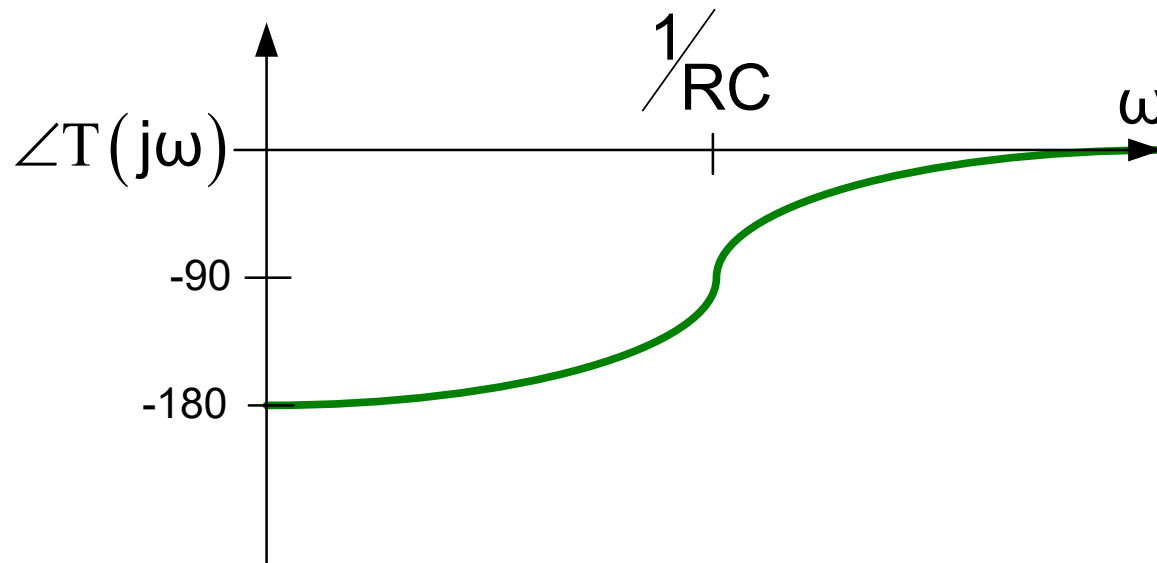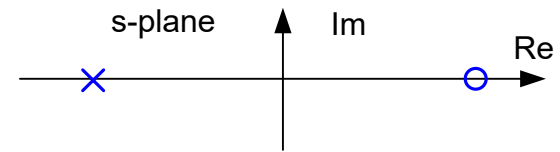
$$T(s) = \frac{s - \frac{1}{RC}}{s + \frac{1}{RC}}$$




First-Order All Pass

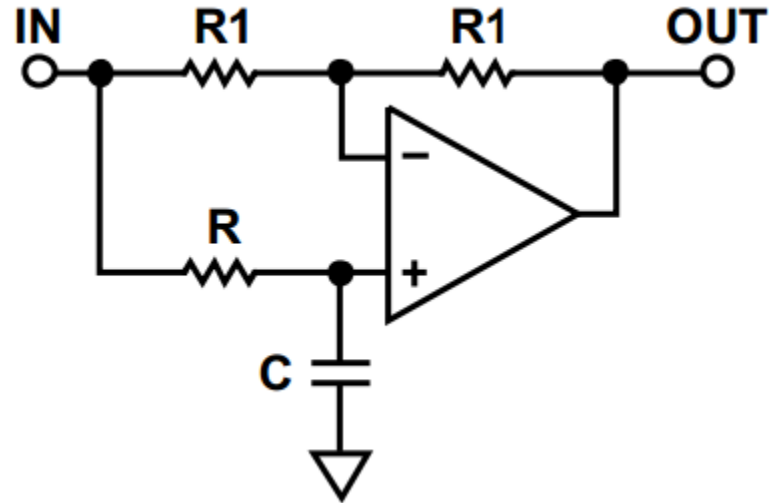



102

$$T(s) = - \frac{s - \frac{1}{RC}}{s + \frac{1}{RC}}$$


First-Order All Pass

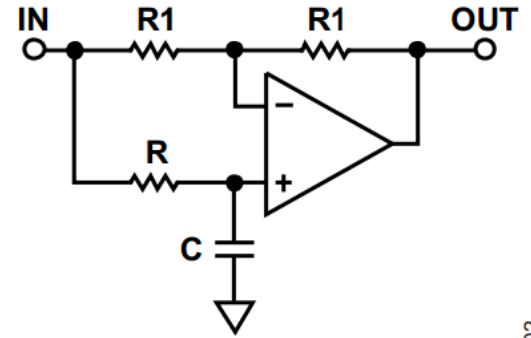
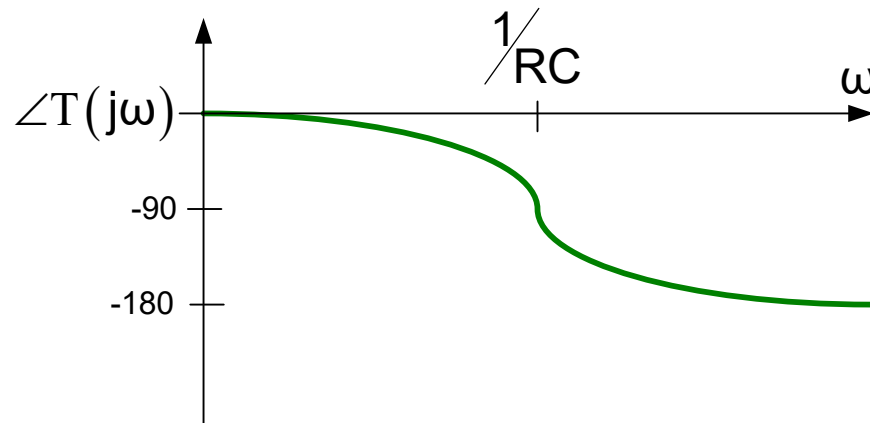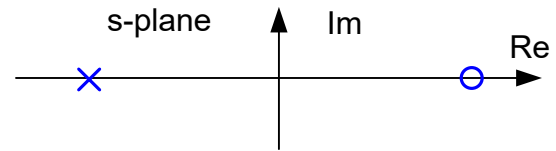
$$T(s) = - \frac{s - \frac{1}{RC}}{s + \frac{1}{RC}}$$



Second-Order All Pass



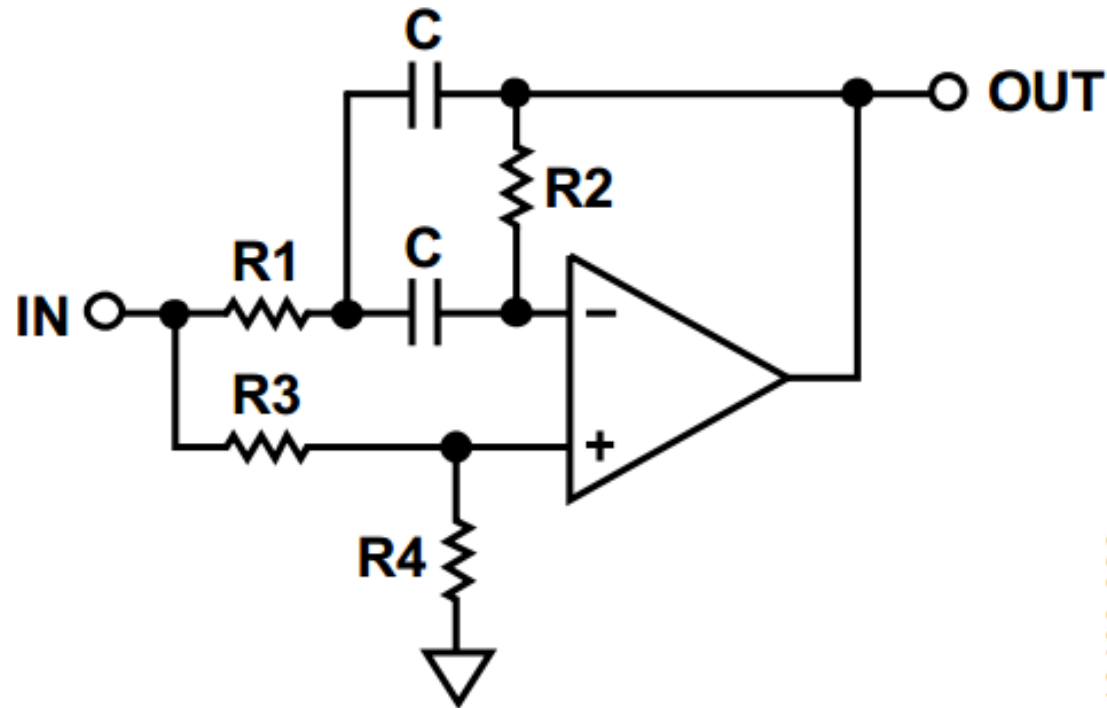


$$\frac{V_O}{V_{IN}} = \frac{s^2 - s\left(\frac{2}{R_2 C}\right) + \frac{1}{R_1 R_2 C^2}}{s^2 + s\left(\frac{2}{R_2 C}\right) + \frac{1}{R_1 R_2 C^2}}$$

Based upon Bridged-T Feedback Structure

Second-Order All Pass
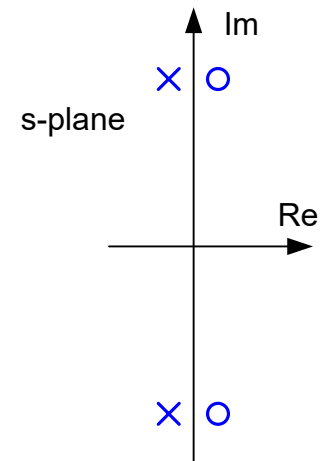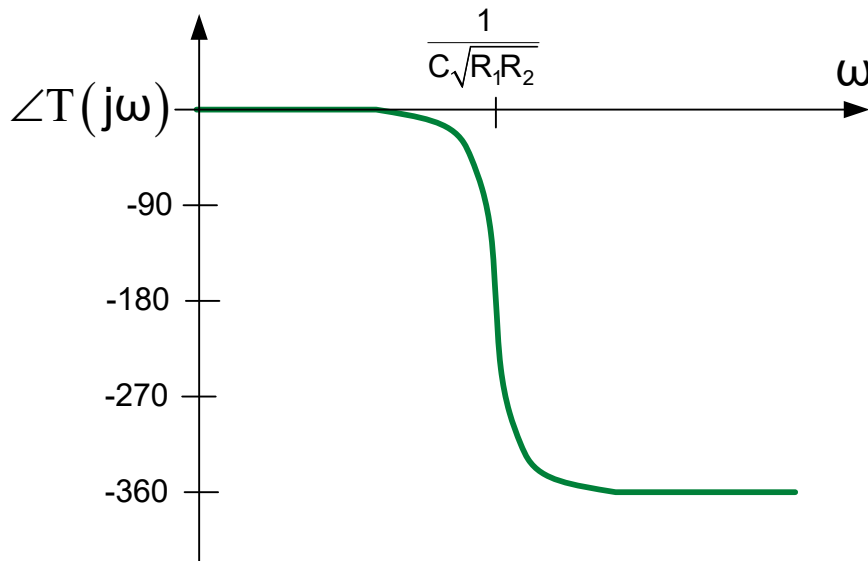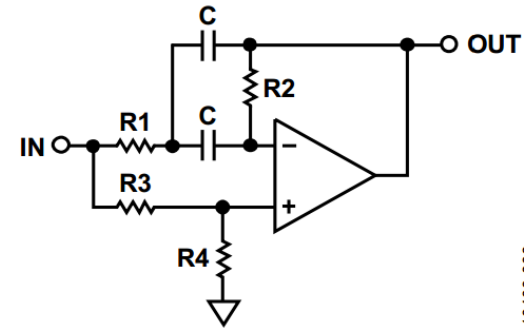
$$\frac{V_O}{V_{IN}} = \frac{s^2 - s\left(\frac{2}{R_2 C}\right) + \frac{1}{R_1 R_2 C^2}}{s^2 + s\left(\frac{2}{R_2 C}\right) + \frac{1}{R_1 R_2 C^2}}$$



Basic Filter Components


- All Pass Networks
- Arbitrary Transfer Function Synthesis
- Impedance Transformation Circuits
- Equalizers



Arbitrary Transfer Function Synthesis

- Based upon coefficient derivation
- Can be used to implement/solve an arbitrary differential equation
- Versatile
- Basic concept of Analog Computer

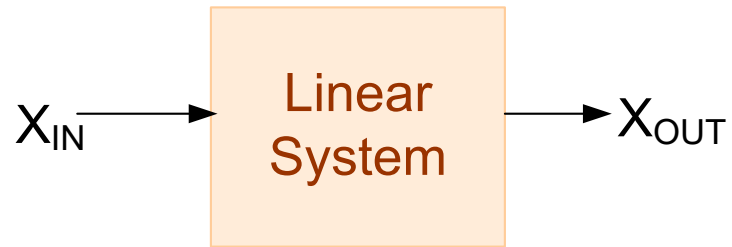Applications of integrators to solving differential equations



Standard Integral form of a differential equation

$$X_{OUT} = b_1 \int X_{OUT} + b_2 \iint X_{OUT} + b_3 \iiint X_{OUT} + \dots + a_0 X_{IN} + \int X_{IN} + \iint X_{IN} + \dots$$


Standard differential form of a differential equation

$$X_{OUT} = \alpha_1 X'_{OUT} + \alpha_2 X''_{OUT} + \alpha_3 X'''_{OUT} + \dots + \beta_1 X_{IN} + \beta_2 X'_{IN} + \beta_3 X''_{IN} + \dots$$

Initial conditions not shown


Can express any system in either differential or integral form

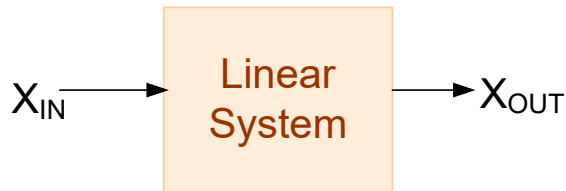Applications of integrators to solving differential equations



Consider the standard integral form
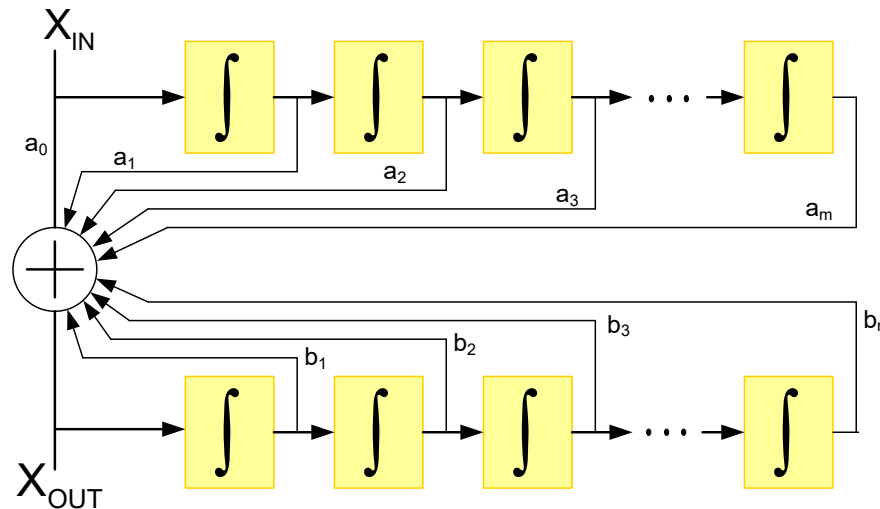
$$X_{OUT} = b_1 \int X_{OUT} + b_2 \iint X_{OUT} + b_3 \iiint X_{OUT} + \dots + a_0 X_{IN} + \int X_{IN} + \iint X_{IN} + \dots$$




One Implementation (direct and intuitive)

This circuit is comprised of summers and integrators

Can solve an arbitrary linear differential equation

This concept was used in Analog Computers in the past

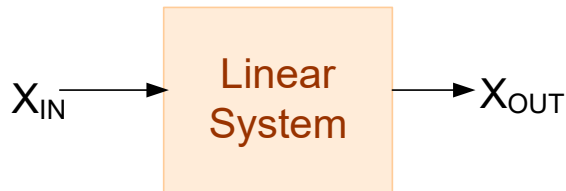Applications of integrators to solving differential equations



Consider the standard integral form

$$X_{OUT} = b_1 \int X_{OUT} + b_2 \iint X_{OUT} + b_3 \iiint X_{OUT} + \dots + a_0 X_{IN} + \int X_{IN} + \iint X_{IN} + \dots$$

Take the Laplace transform of this equation

$$\mathcal{X}_{OUT} = b_1 \frac{1}{s} \mathcal{X}_{OUT} + b_2 \frac{1}{s^2} \mathcal{X}_{OUT} + b_3 \frac{1}{s^3} \mathcal{X}_{OUT} + \dots + b_n \frac{1}{s^n} + a_0 \mathcal{X}_{IN} + a_1 \frac{1}{s} \mathcal{X}_{IN} + a_2 \frac{1}{s^2} \mathcal{X}_{IN} + a_3 \frac{1}{s^3} \mathcal{X}_{IN} + \dots + a_m \frac{1}{s^m}$$


Multiply by s^n and assume $m=n$ (some of the coefficients can be 0)

$$s^n \mathcal{X}_{OUT} = b_1 s^{n-1} \mathcal{X}_{OUT} + b_2 s^{n-2} \mathcal{X}_{OUT} + b_3 s^{n-3} \mathcal{X}_{OUT} + \dots + b_n + a_0 s^n \mathcal{X}_{IN} + a_1 s^{n-1} \mathcal{X}_{IN} + a_2 s^{n-2} \mathcal{X}_{IN} + a_3 s^{n-3} \mathcal{X}_{IN} + \dots + a_n$$

$$\mathcal{X}_{OUT} (s^n - b_1 s^{n-1} - b_2 s^{n-2} - b_3 s^{n-3} - \dots - b_n) = \mathcal{X}_{IN} (a_0 s^n + a_1 s^{n-1} + a_2 s^{n-2} + a_3 s^{n-3} + \dots + a_n)$$

$$T(s) = \frac{\mathcal{X}_{OUT}}{\mathcal{X}_{IN}} = \frac{a_0 s^n + a_1 s^{n-1} + a_2 s^{n-2} + a_3 s^{n-3} + \dots + a_n}{s^n - b_1 s^{n-1} - b_2 s^{n-2} - b_3 s^{n-3} - \dots - b_n}$$

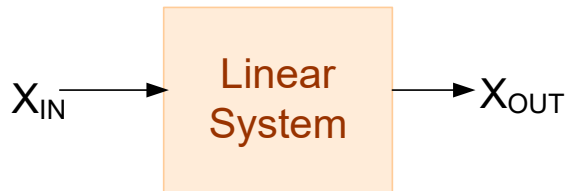Applications of integrators to solving differential equations



Consider the standard integral form


$$X_{OUT} = b_1 \int X_{OUT} + b_2 \iint X_{OUT} + b_3 \iiint X_{OUT} + \dots + a_0 X_{IN} + \int X_{IN} + \iint X_{IN} + \dots$$

$$T(s) = \frac{\mathcal{X}_{OUT}}{\mathcal{X}_{IN}} = \frac{a_0 s^n + a_1 s^{n-1} + a_2 s^{n-2} + a_3 s^{n-3} + \dots + a_n}{s^n - b_1 s^{n-1} - b_2 s^{n-2} - b_3 s^{n-3} - \dots - b_n}$$


This can be written in more standard form

$$T(s) = \frac{\alpha_n s^n + \alpha_{n-1} s^{n-1} + \dots + \alpha_1 s + \alpha_0}{s^n + \beta_{n-1} s^{n-1} + \dots + \beta_1 s + \beta_0}$$

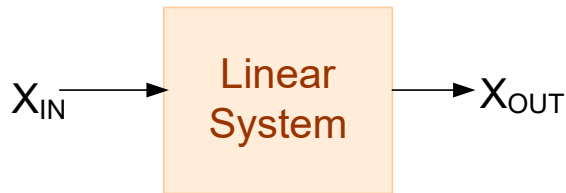Applications of integrators to filter design


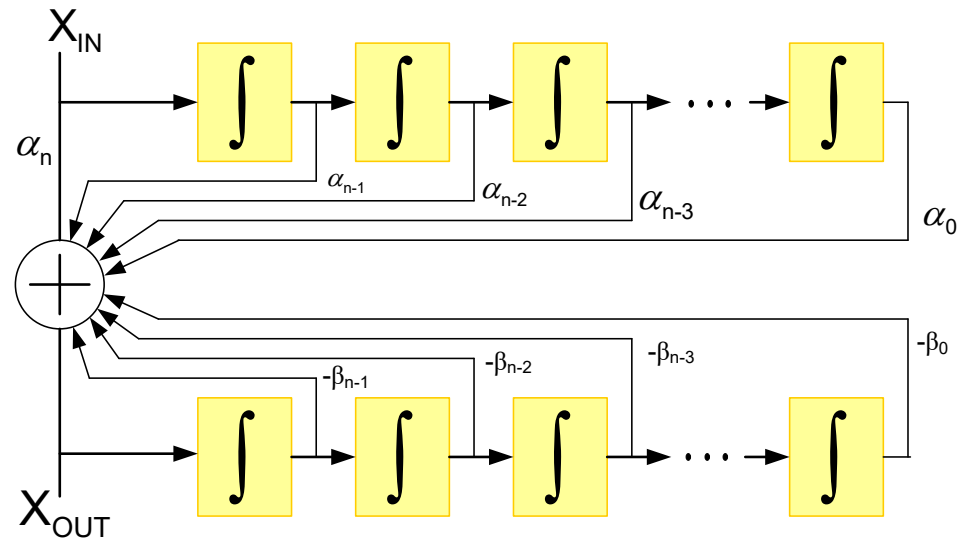
$$T(s) = \frac{\alpha_n s^n + \alpha_{n-1} s^{n-1} + \dots + \alpha_1 s + \alpha_0}{s^n + \beta_{n-1} s^{n-1} + \dots + \beta_1 s + \beta_0}$$




One Implementation (direct and intuitive)

Can design (synthesize) any $T(s)$ with just integrators and summers !


Integrators are not used "open loop" so loss is not added

Although this approach to filter design works, often more practical methods are used

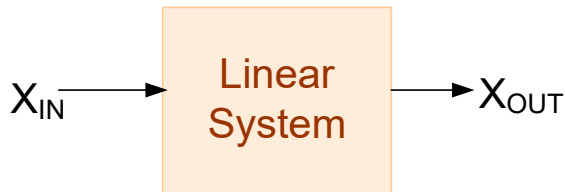Applications of integrators to filter design


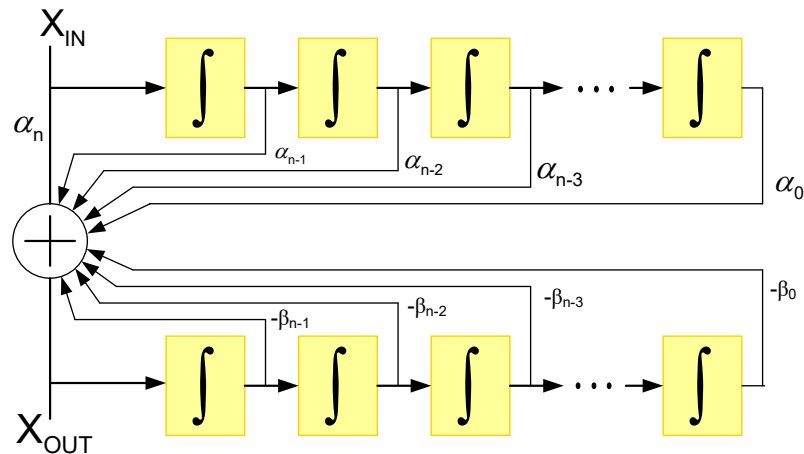
$$T(s) = \frac{\alpha_n s^n + \alpha_{n-1} s^{n-1} + \dots + \alpha_1 s + \alpha_0}{s^n + \beta_{n-1} s^{n-1} + \dots + \beta_1 s + \beta_0}$$



One Implementation (direct and intuitive)

What are some other architectural implementations?

Cascaded Biquads

Leapfrog

Though these other implementations may have better performance, not as easily programmable to realize different functions

Basic Filter Components



- All Pass Networks
- Arbitrary Transfer Function Synthesis
- Impedance Transformation Circuits
- Equalizers



Impedance Synthesis


- Focus on synthesizing impedance rather than transfer function
- Gyration will provide inductance simulation
- Capacitance Multiplication
- Synthesis of super components

Impedance Converters

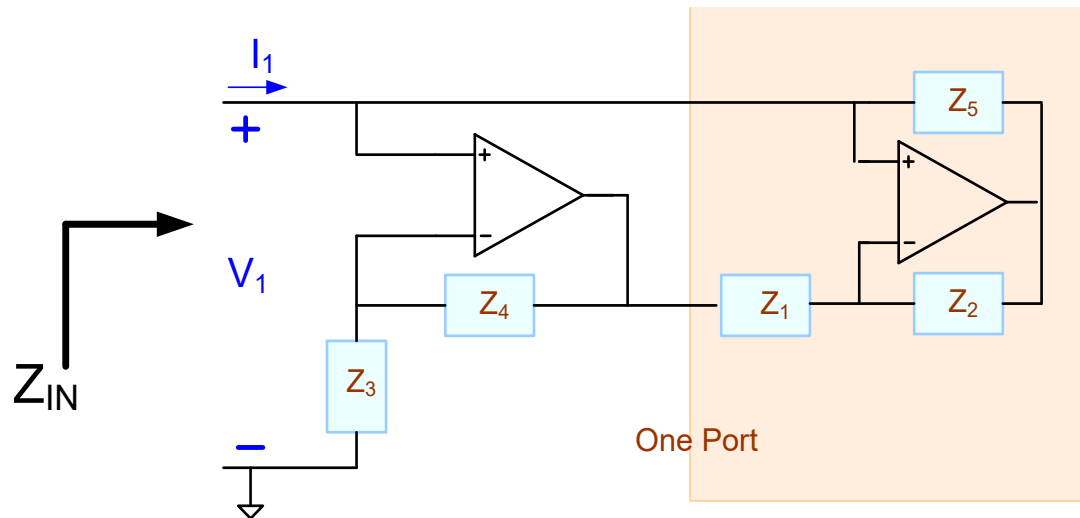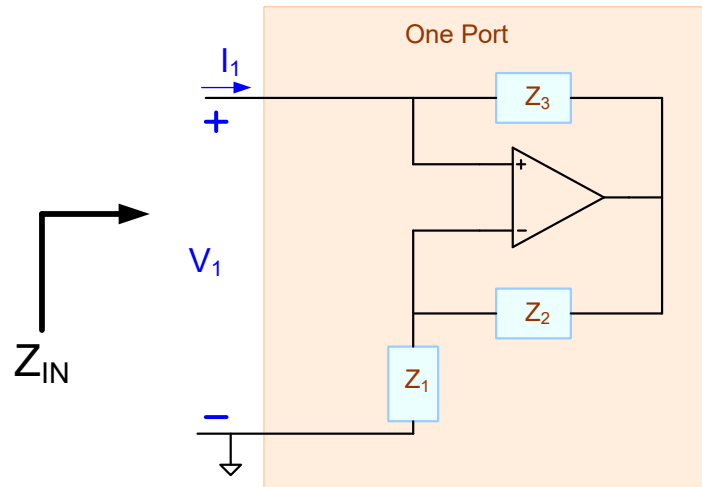

Note these circuits are strictly one-ports and have no output node

Impedance Converters

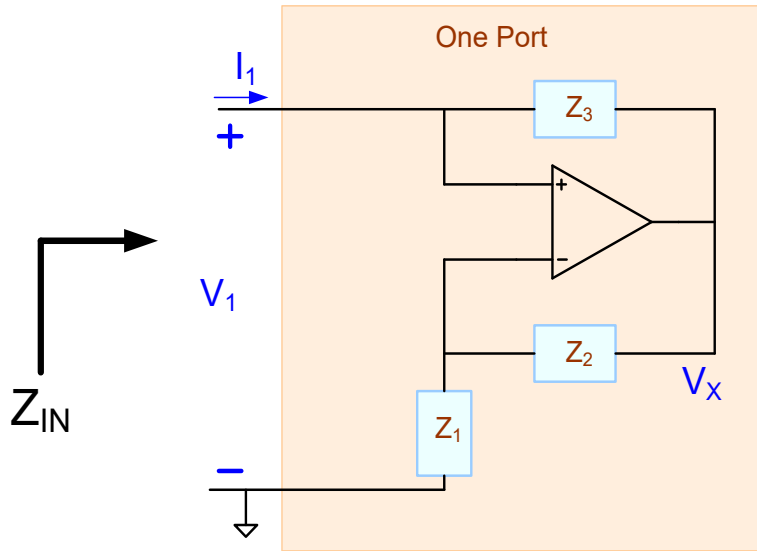


$$\left. \begin{aligned} V_1(G_1+G_2) &= V_X G_2 \\ I_1 &= (V_1 - V_X) G_3 \end{aligned} \right\}$$

$$Z_{IN} = -\frac{Z_1 Z_3}{Z_2}$$

Observe this input impedance is negative!

Impedance Converters

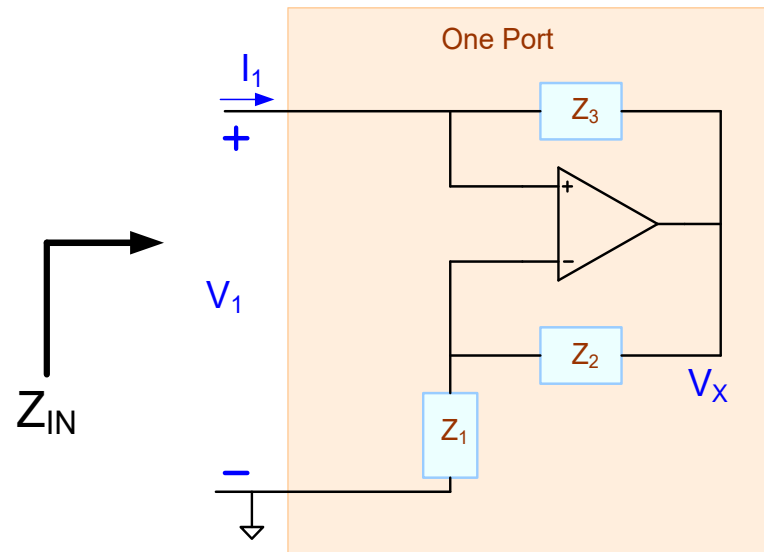

$$Z_{IN} = -\frac{Z_1 Z_3}{Z_2}$$


If $Z_1=R_1$, $Z_2=R_2$ and $Z_3=R_3$, $Z_{IN} = -\frac{R_1 R_3}{R_2}$ This is a negative resistor !

If $Z_2=1/sC$, $Z_1=R_1$ and $Z_3=R_3$, $Z_{IN} = -sCR_1 R_3$ This is a negative inductor !

If $Z_2=R_2$, $Z_1=1/sC$ and $Z_3=R_3$, $Z_{IN} = -\frac{R_3}{sCR_2}$ This is a negative capacitor !

This is termed a Negative Impedance Converter

Impedance Converters

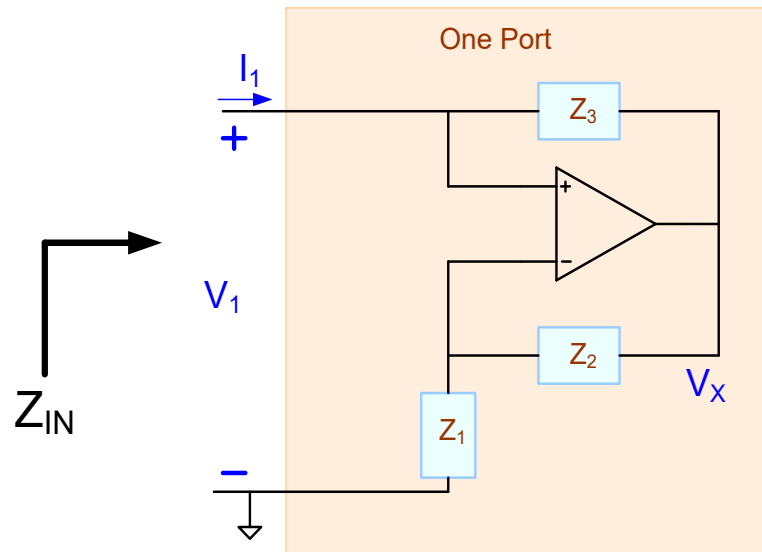



$$Z_{IN} = -\frac{Z_1 Z_3}{Z_2}$$

If $Z_2 = 1/sC$, $Z_1 = R_1$ and $Z_3 = R_3$, $Z_{IN} = -sCR_1R_3$


Modification of NIC to provide a positive inductance:

Replace Z_1 itself with a second NIC that has a negative input impedance


Negative Impedance Converter

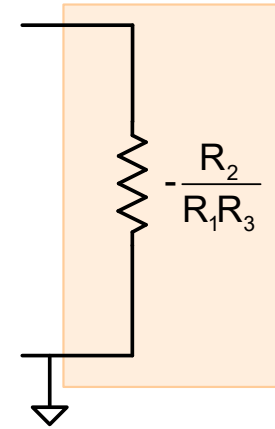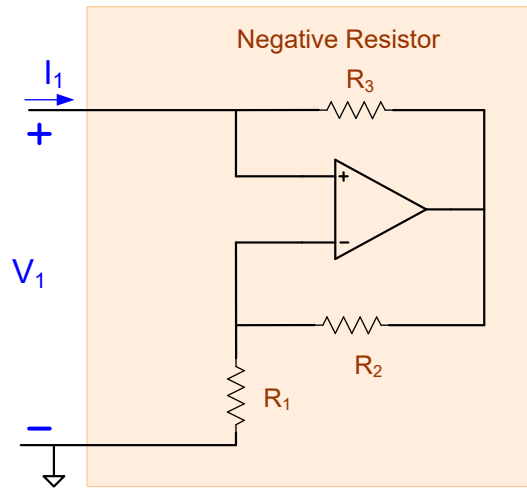

One application of NIC

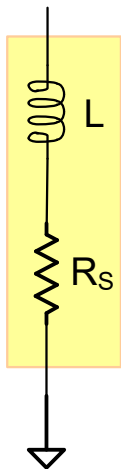


Lossy Inductor

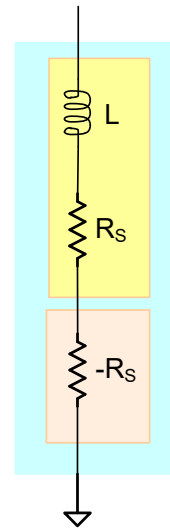

If select components so that $R_s = \frac{R_2}{R_1 R_3}$

Lossless Inductor


Impedance Converters

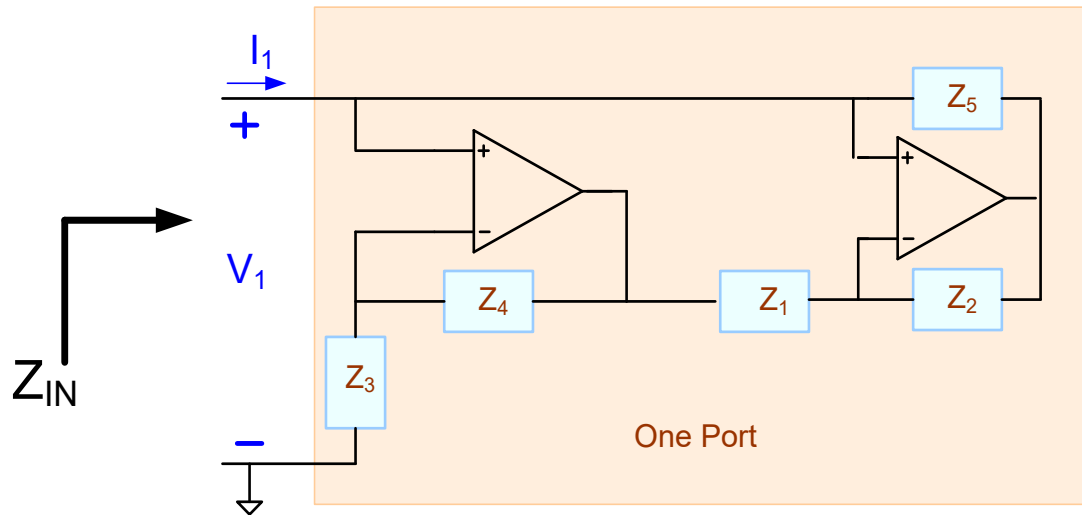

$$Z_{IN} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$

This circuit is often called a Gyrator

Gyrator Analysis

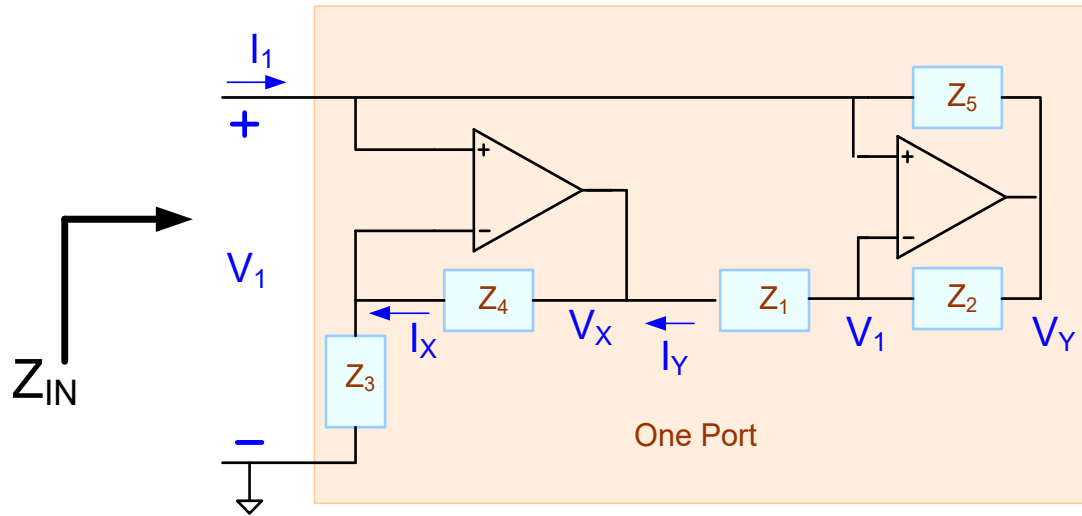

$$I_X = V_1 G_3$$

$$V_X = V_1 + V_1 G_3 / G_4 = V_1 \left(1 + \frac{G_3}{G_4} \right)$$


$$I_Y = (V_1 - V_X) G_1 = V_1 \left(-\frac{G_3}{G_4} \right) G_1$$

$$V_Y = V_1 + I_Y / G_2 = V_1 \left(1 - \frac{G_3}{G_4} \left(\frac{G_1}{G_2} \right) \right)$$

$$I_1 = (V_1 - V_Y) G_5 = V_1 \left(\frac{G_3}{G_4} \left(\frac{G_1}{G_2} \right) \right) G_5$$

$$Z_{IN} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$

Gyrator Applications

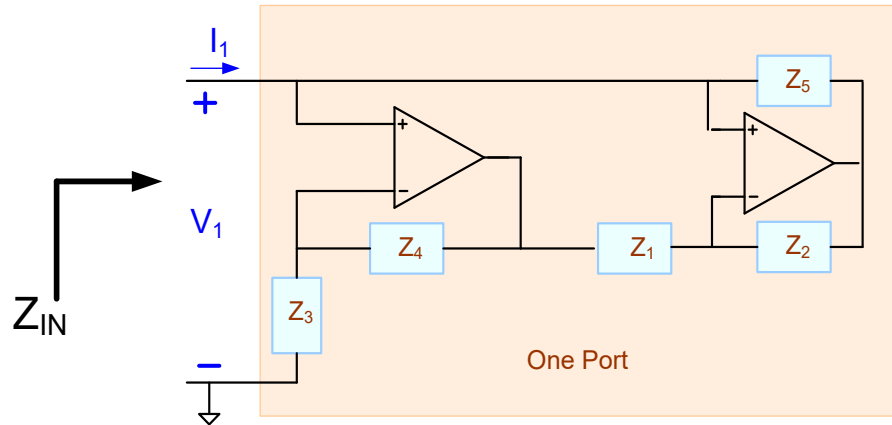

$$Z_{IN} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$


If $Z_1=Z_3=Z_4=Z_5=R$ and $Z_2=1/sC$ $Z_{IN} = (R^2C)s$ This is an inductor of value $L=R^2C$

If $Z_2=R_2$, $Z_3=R_3$, $Z_4=R_4$, $Z_5=R_5$ and $Z_1=1/sC$ $Z_{IN} = \frac{R_3 R_5}{s C R_2 R_4}$

This is a capacitor of value $C_{EQ} = C \frac{R_2 R_4}{R_3 R_5}$ (can scale capacitance up or down)

If $Z_2=Z_4=Z_5=R$ and $Z_1=Z_3=1/sC$ $Z_{IN} = (R^3 C^2)s^2$ This is a "super" capacitor of value $R^3 C^2$

Impedance Converters

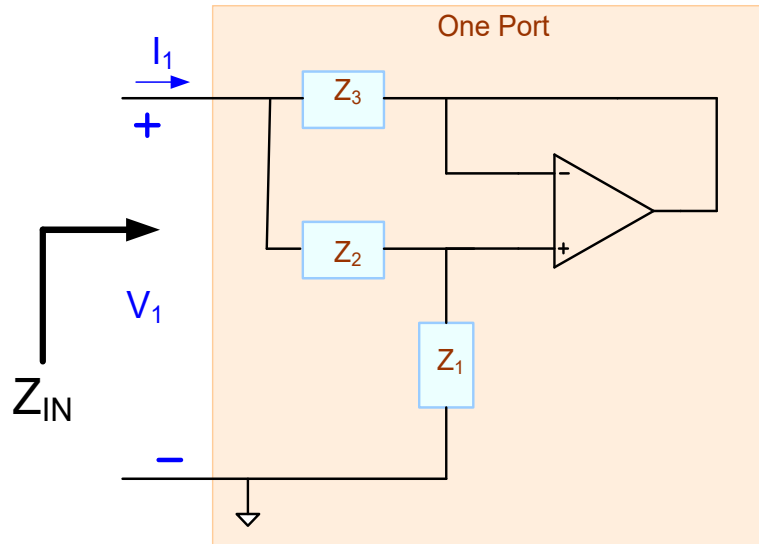


$$I_1 = \left(V_1 - \left(\frac{Z_1}{Z_1 + Z_2} \right) V_1 \right) G_3$$

$$Z_{IN} = Z_3 \left(1 + \frac{Z_2}{Z_1} \right)$$

If $Z_3 = R_3$, $Z_2 = R_2$ and $Z_1 = 1/sC$

$$Z_{IN} = R_3 + s(CR_2R_3)$$

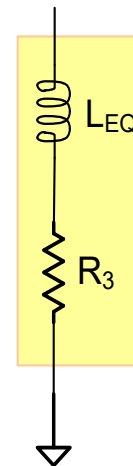

$$L_{EQ} = CR_2R_3$$

Basic Filter Components


- All Pass Networks
- Arbitrary Transfer Function Synthesis
- Impedance Transformation Circuits

• Equalizers

Shelving Equalizers


- Widely used in audio applications
- User-programmable filter response

Shelving Equalizers

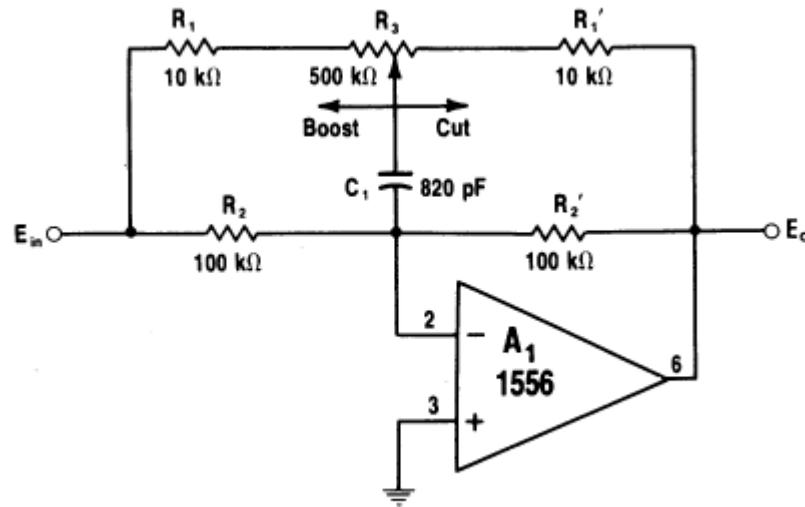

(A) High frequency.


Shelving Equalizers

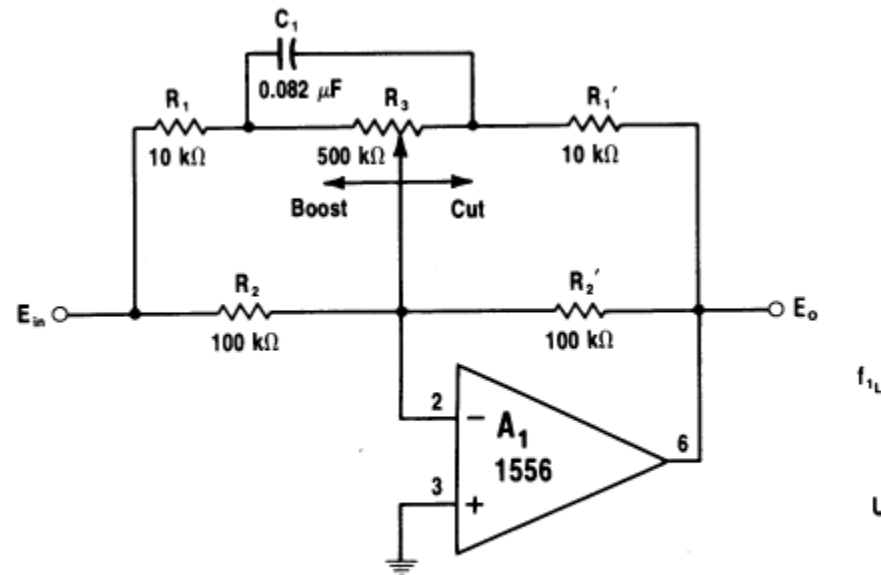



(B) Low frequency.

Fig. 6-37. Shelving equalizers.

Shelving Equalizers

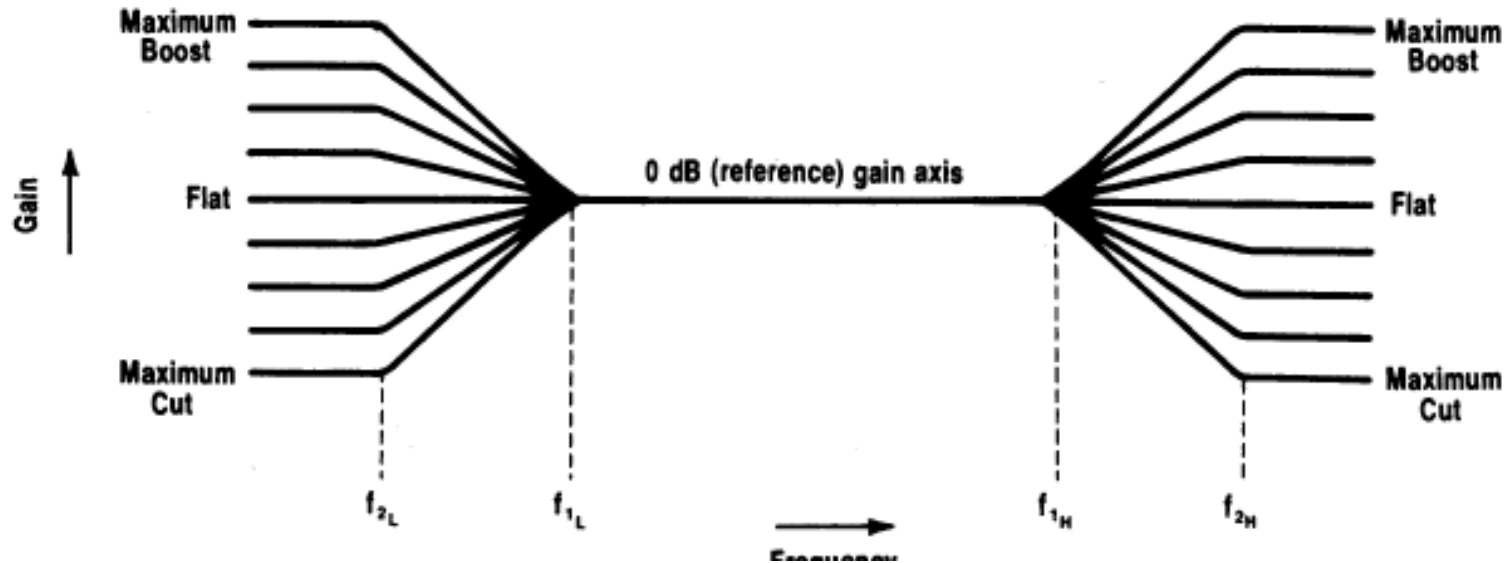

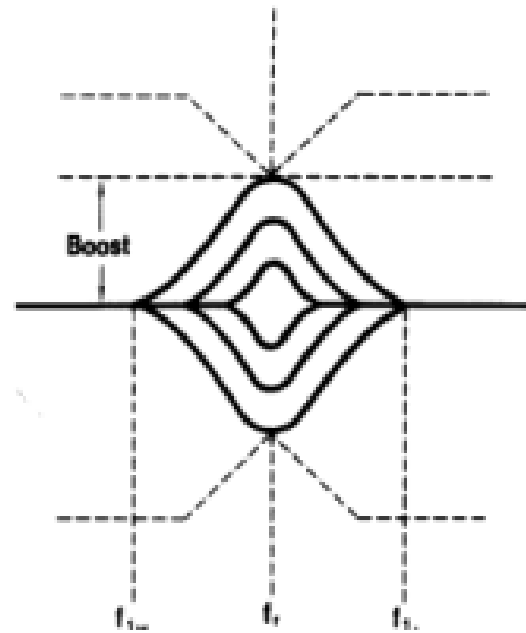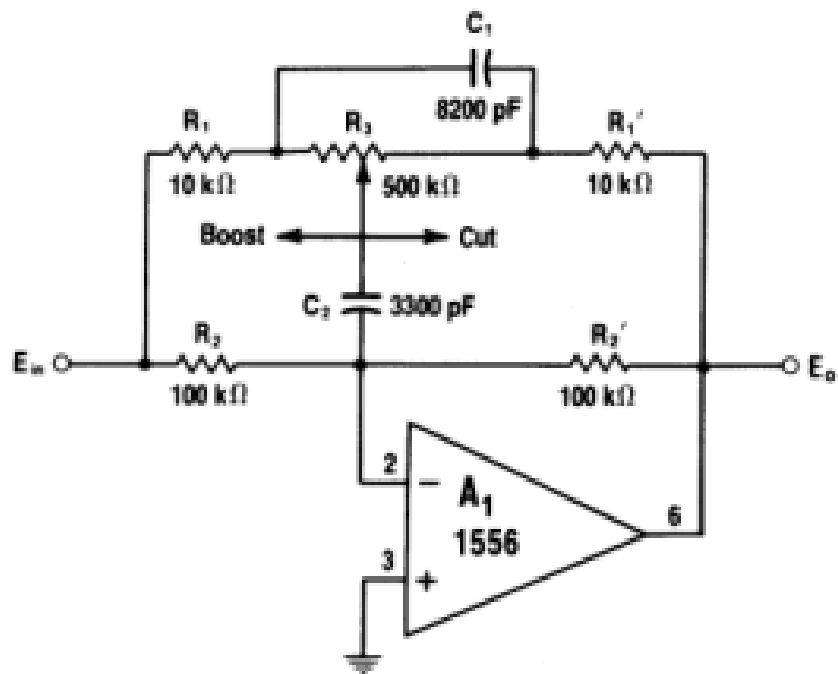- The expressions for f_L and f_H for the previous two circuits show a small movement with the potentiometer position in contrast to the fixed point location depicted in this figure
- The OTA-C filters discussed earlier in the course can be designed to have fixed values for f_L and f_H when cut or boost is used.





Stay Safe and Stay Healthy !

End of Lecture 42