




# EE 508

## Lecture 18



Comparison of Filter Structures  
Sensitivity Functions

# How does the performance of these bandpass filters compare?


Review from last time

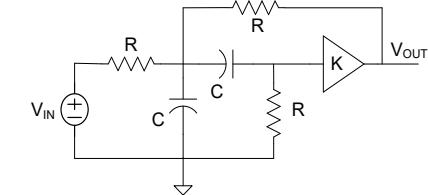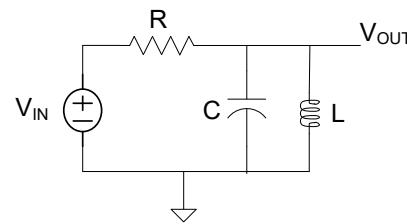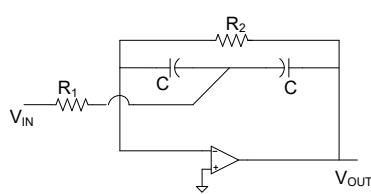

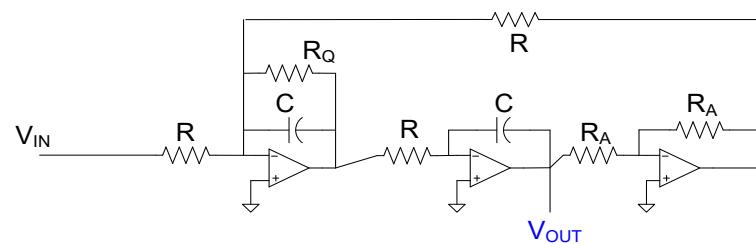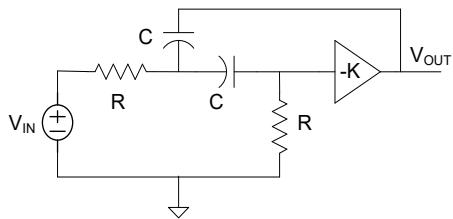- Component Spread
- Number of Op Amps
- Is the performance strongly dependent upon how DOF are used?
- Ease of tunability/calibration (but practical structures often are not calibrated)
- Total capacitance or total resistance
- Power Dissipation
- Sensitivity
- Effects of Op Amps


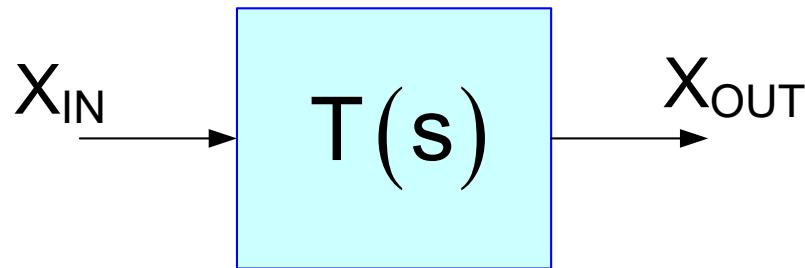
# Consider 2<sup>nd</sup> Order Lowpass Biquads





$$|T(s)| = H \frac{\omega_0^2}{s^2 + s\left(\frac{\omega_0}{Q}\right) + \omega_0^2}$$

$$\text{BW} = \omega_B - \omega_A \neq \frac{\omega_0}{Q}$$
$$\omega_{PEAK} \neq \omega_0$$



# Consider 2<sup>nd</sup> Order Lowpass Biquads

$$|T(s)| = H \frac{\omega_0^2}{s^2 + s\left(\frac{\omega_0}{Q}\right) + \omega_0^2}$$

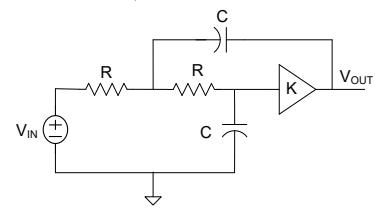
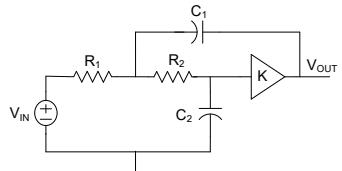
Four basic structures that ideally implement the same transfer function





Sallen and Key +KRC

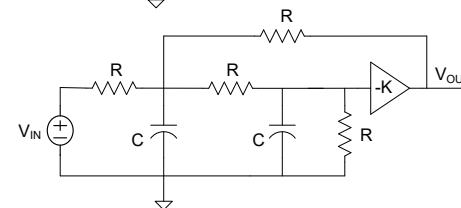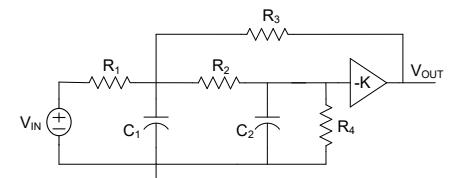

Sallen and Key -KRC

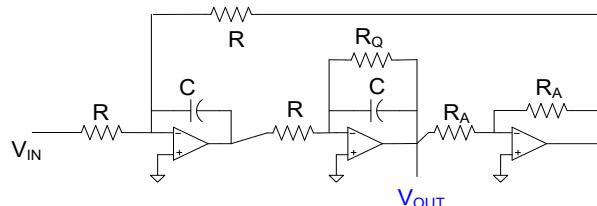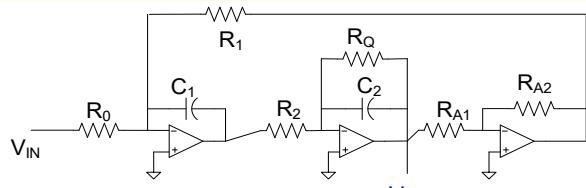


Two Integrator Loop

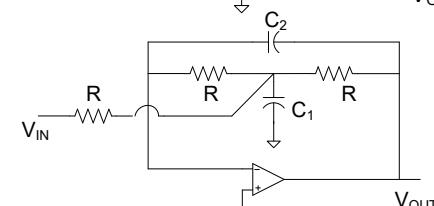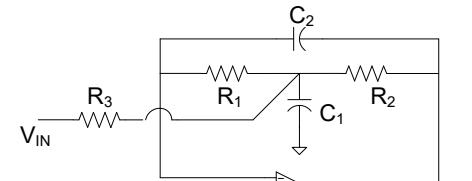


Bridged-T Feedback
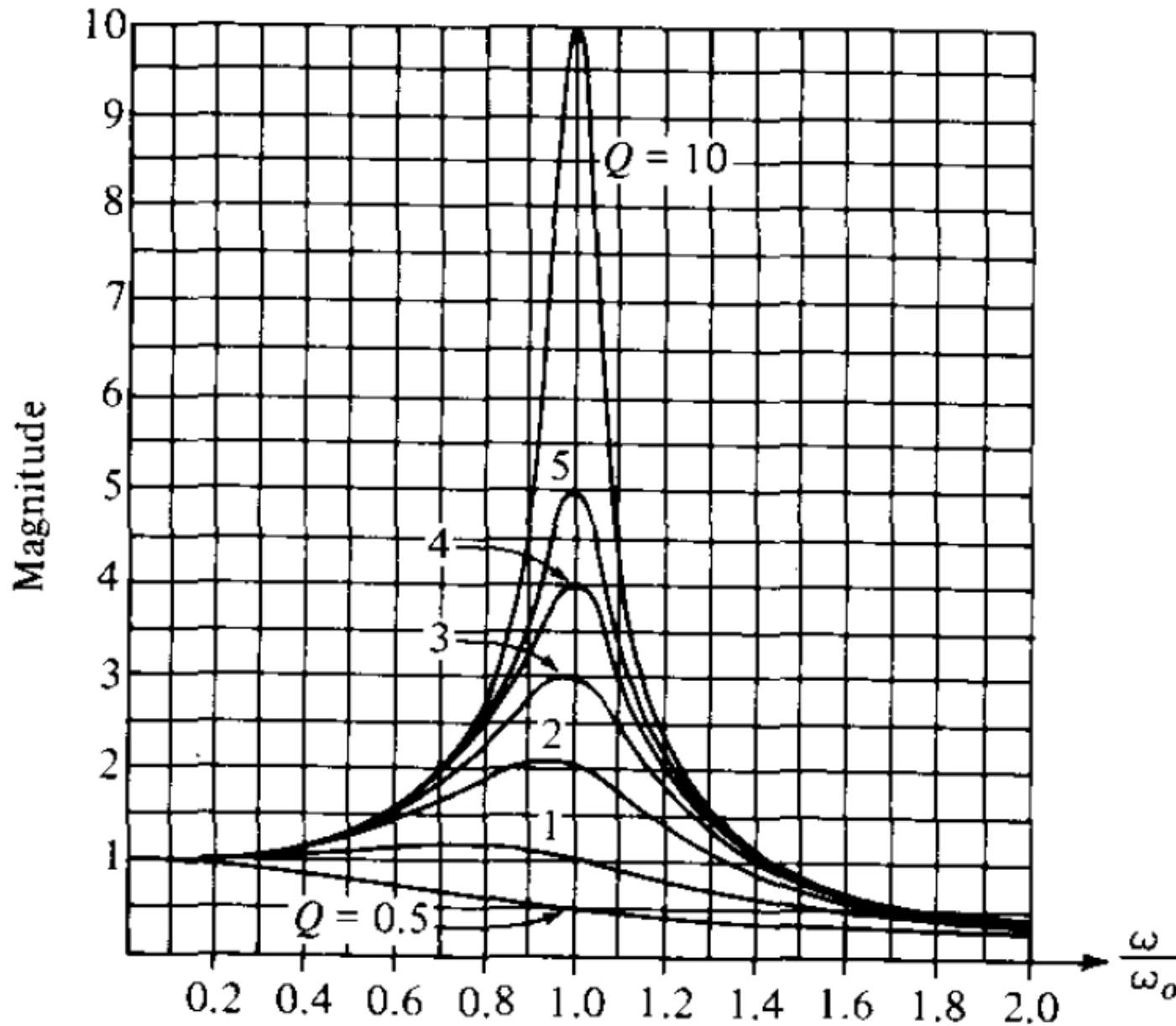
# Consider 2<sup>nd</sup> Order Lowpass Biquads


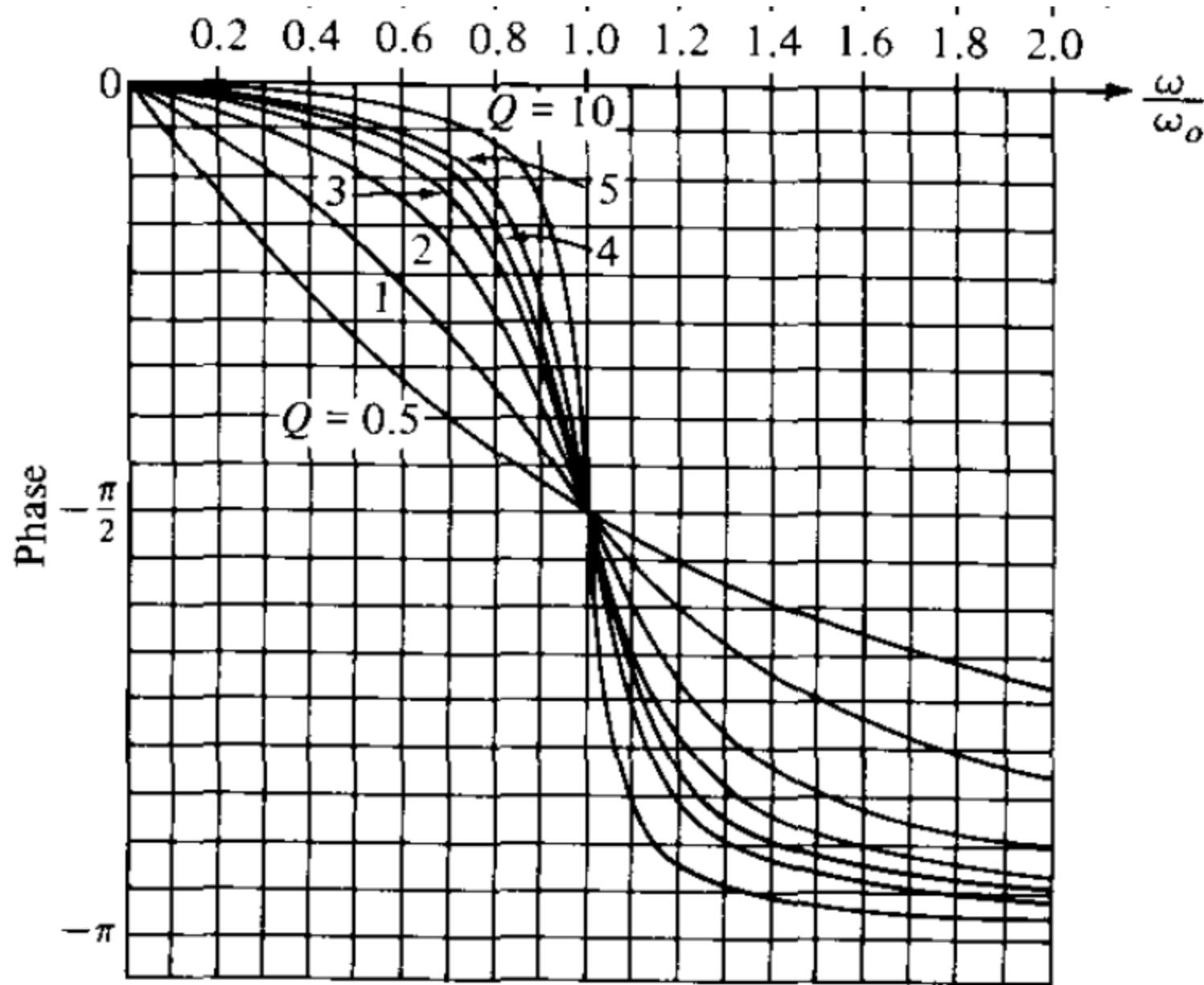
# Consider 2<sup>nd</sup> Order Lowpass Biquads




# Performance Comparison of Selected Second-Order Lowpass Filters

$$|T(s)| = H \frac{\omega_0^2}{s^2 + s\left(\frac{\omega_0}{Q}\right) + \omega_0^2}$$


$$\text{BW} = \omega_B - \omega_A \neq \frac{\omega_0}{Q}$$
$$\omega_{\text{PEAK}} \neq \omega_0$$

- ➡ Component Spread
  - Number of Op Amps
- ➡ Is the performance strongly dependent upon how DOF are used?
  - Ease of tunability/calibration (but practical structures often are not calibrated)
  - Total capacitance or total resistance
  - Power Dissipation
  - Sensitivity
- ➡ Effects of Op Amps
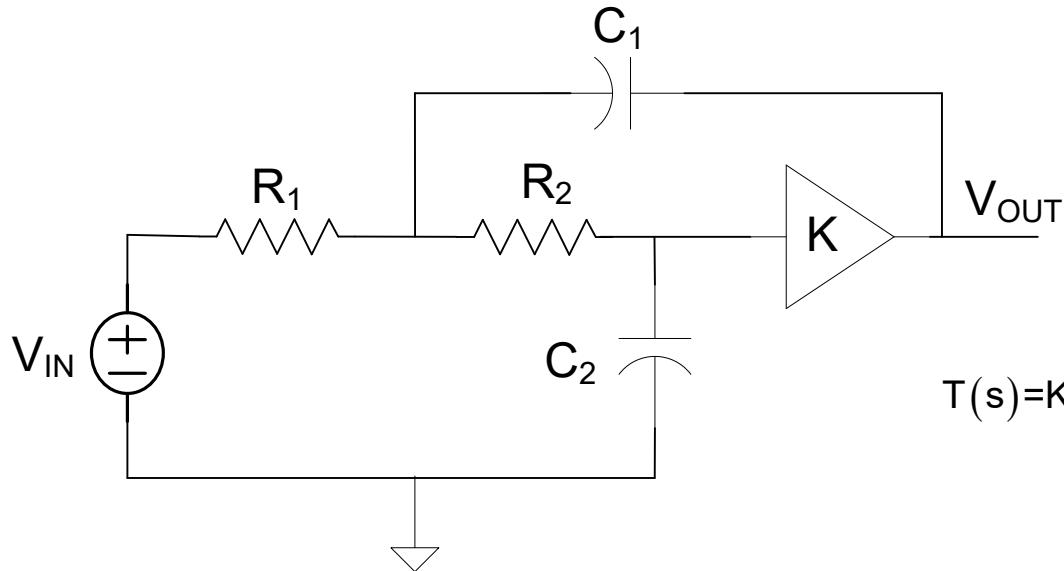
## Example: 2<sup>nd</sup> Order +KRC Lowpass


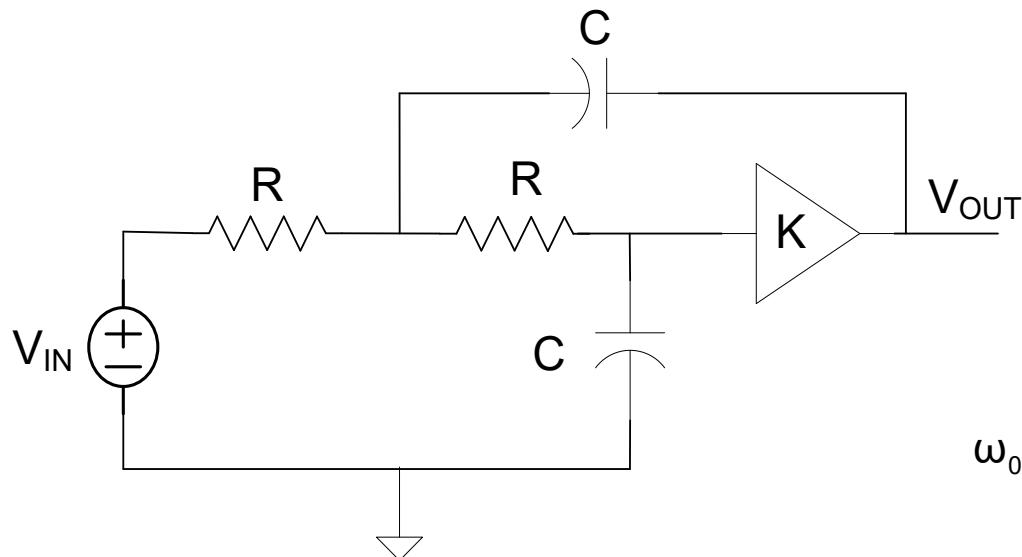
$$T(s) = K \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + s \left[ \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$




Equal R, Equal C

$$T(s) = K \frac{\frac{1}{R^2 C^2}}{s^2 + s \left[ \frac{(3-K)}{RC} \right] + \frac{1}{R^2 C^2}}$$


$$\omega_0 = \frac{1}{RC}$$

$$Q = \frac{1}{3-K}$$

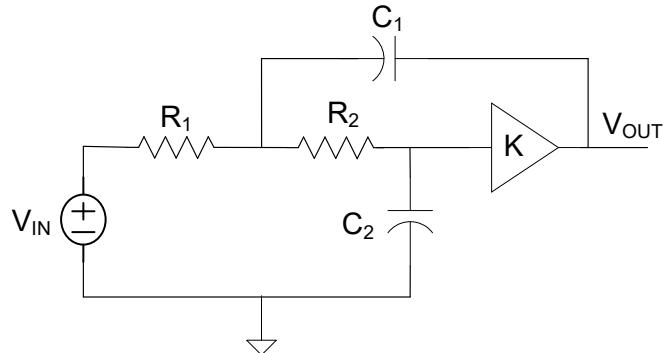Example: 2<sup>nd</sup> Order +KRC Lowpass



Equal R, K=1

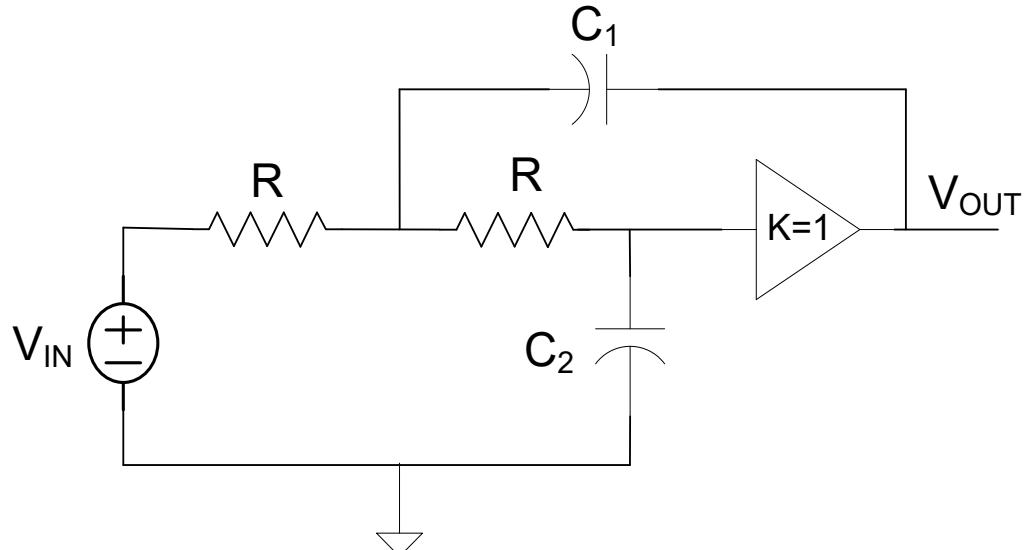



$$T(s) = K \frac{1}{s^2 + s \left[ \frac{2}{RC_1} \right] + \frac{1}{R^2 C_1 C_2}}$$

$$\omega_0 = \frac{1}{R\sqrt{C_1 C_2}}$$

$$Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}}$$

## Example: 2<sup>nd</sup> Order +KRC Lowpass

### Op Amp Model

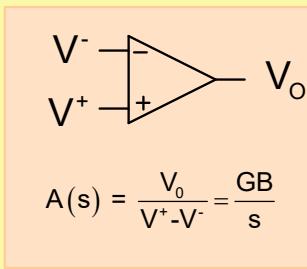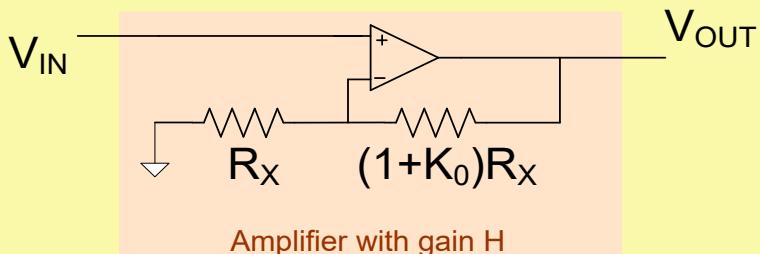

$$K(s) = \frac{K_0}{1 + \frac{K_0}{GB}s}$$


$$T(s) = H \frac{\omega_0^2}{s^2 + s\left(\frac{\omega_0}{Q}\right) + \omega_0^2}$$

Define

$$GB_n = \frac{GB}{\omega_0}$$

Example: 2<sup>nd</sup> Order +KRC Lowpass


## Root Locus Plots

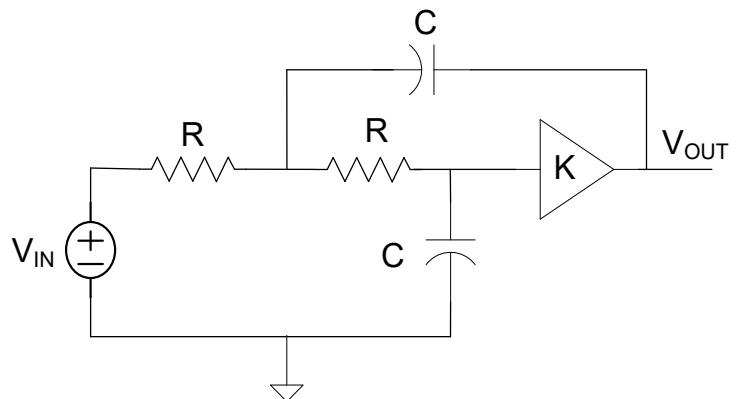



Equal R, Equal C

consider

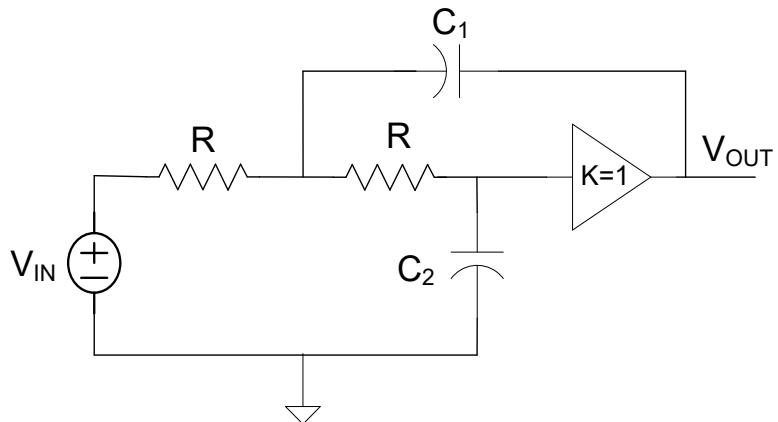
$$\textcircled{1} \leftrightarrow GB_n = \frac{GB}{\omega_0} = 100$$




Equal R, K=1

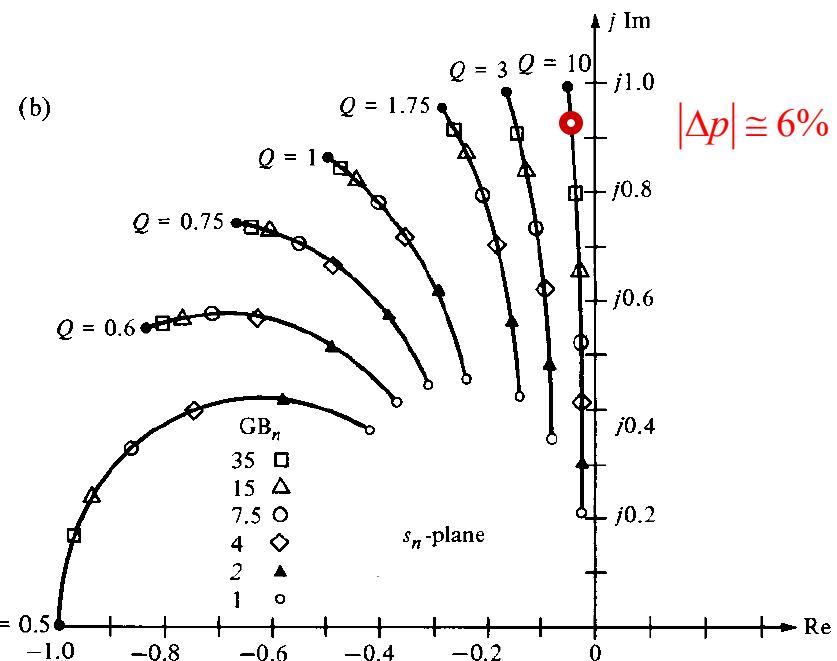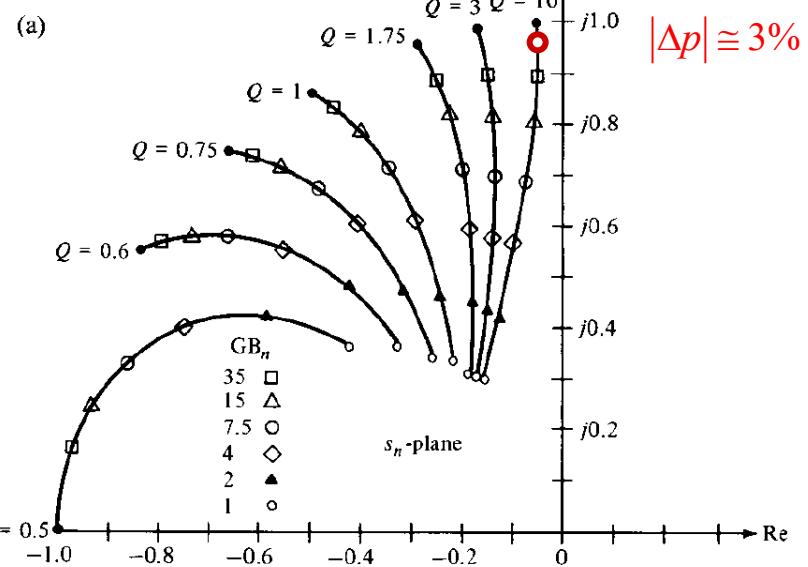
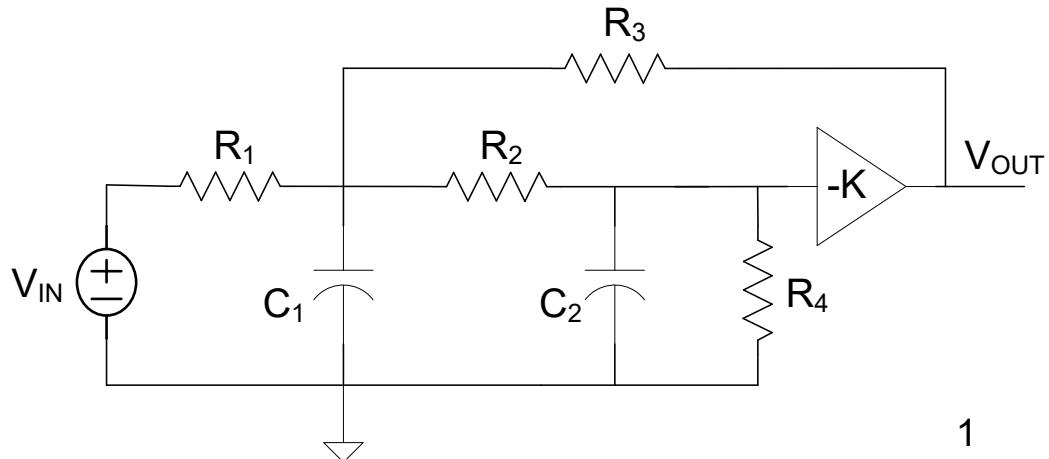
## Example: 2<sup>nd</sup> Order -KRC Lowpass


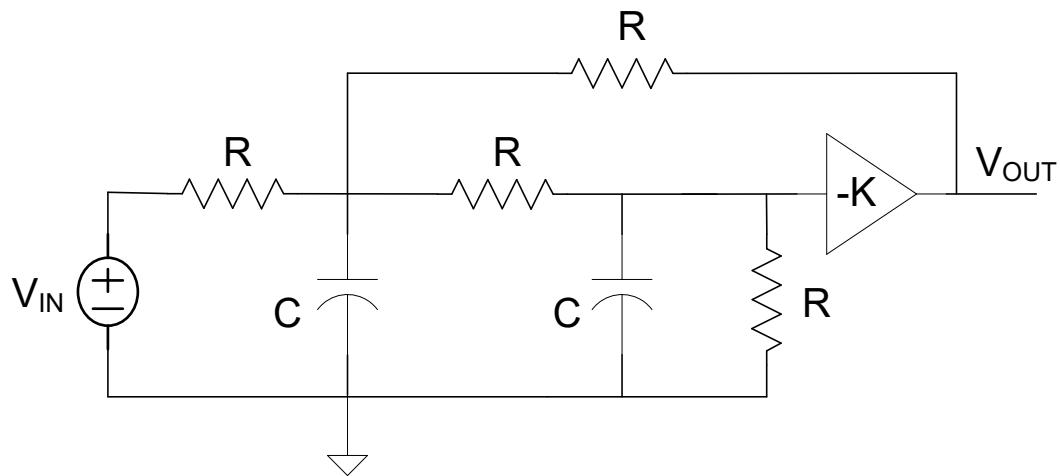
$$T(s) = -K \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + s \left[ \frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right) \right] + \left[ \frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1+(R_2/R_3)+(R_2/R_1))}{R_1 R_2 C_1 C_2} \right]}$$




Equal R, Equal C

$$T(s) = -K \frac{\frac{1}{R^2 C^2}}{s^2 + s \left[ \frac{5}{RC} \right] + \left[ \frac{5+K}{R^2 C^2} \right]}$$


$$\omega_0 = \frac{\sqrt{5+K}}{RC}$$

$$Q = \frac{\sqrt{5+K}}{5}$$

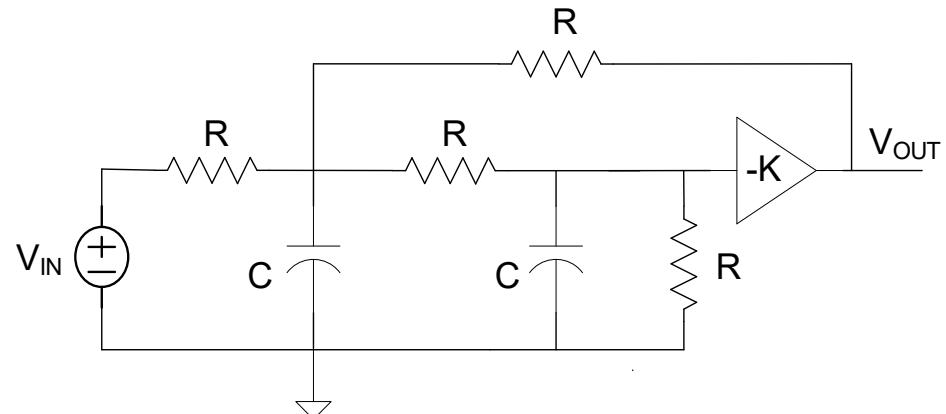
## Example: 2<sup>nd</sup> Order -KRC Lowpass


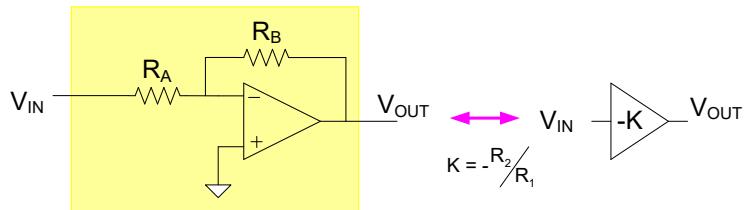
$$\omega_0 = \frac{\sqrt{5+K}}{RC} \quad Q = \frac{\sqrt{5+K}}{5}$$



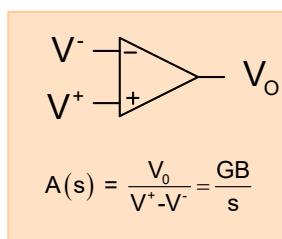
Assume either  $R_A=R$  or  $R_A$  very large



$$K(s) = -\frac{K_0}{1 + \frac{(1+K_0)s}{GB}}$$


consider

$$GB_n = \frac{GB}{\omega_0} = 100$$

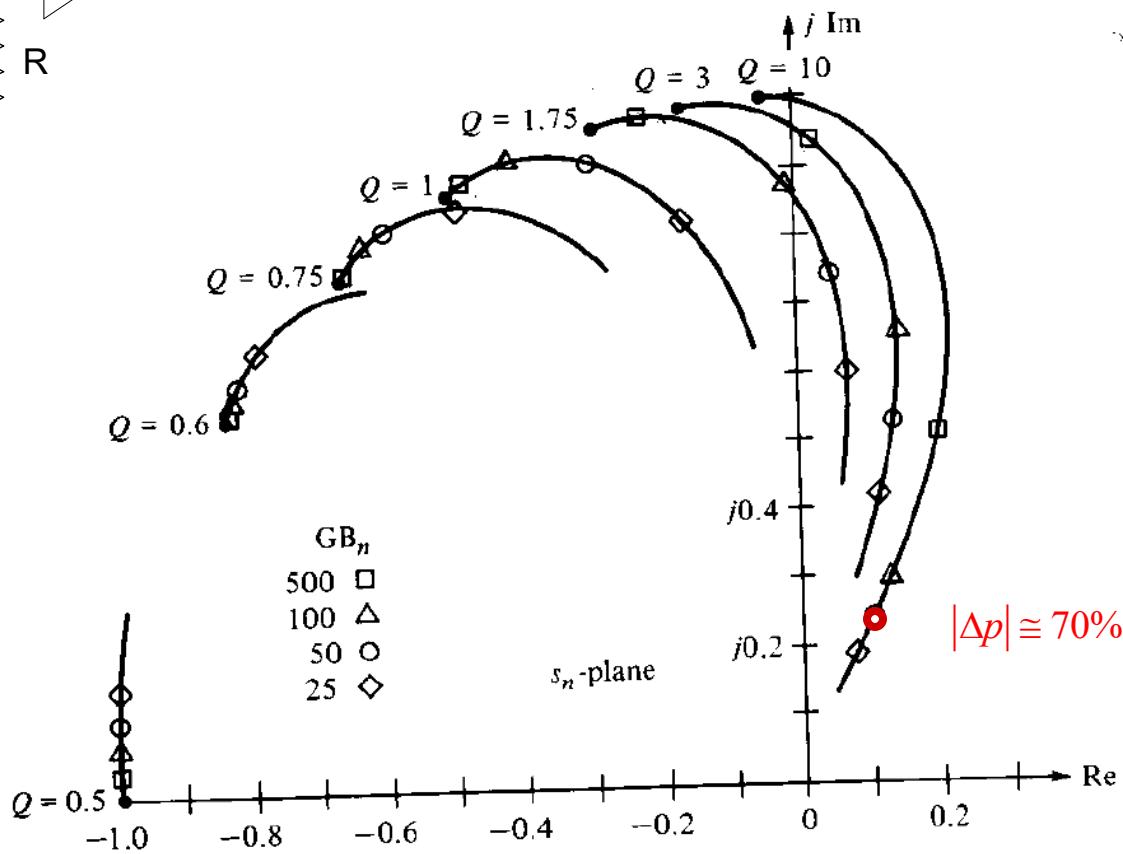


Poles “move” towards RHP as GB degrades  
Even very large values of GB will cause instability
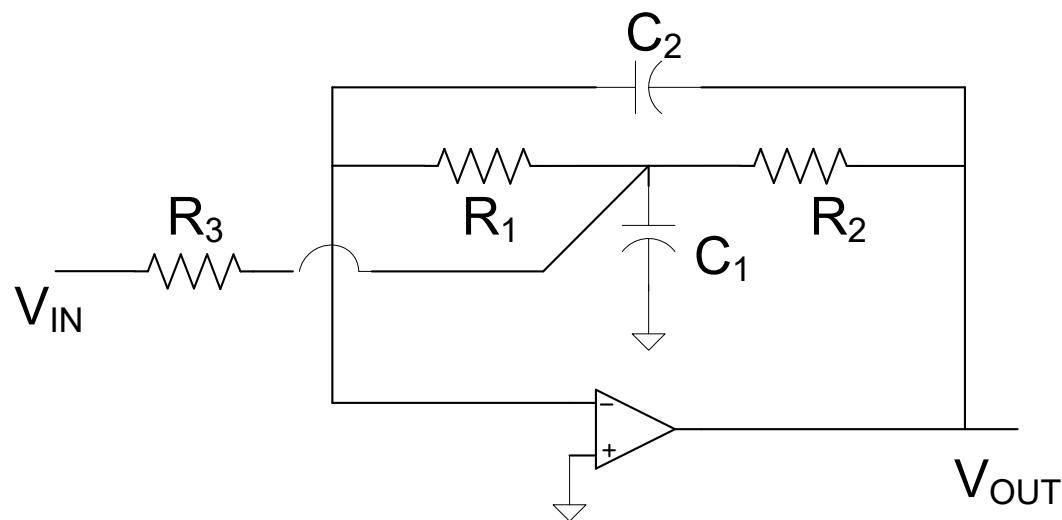
## Example: 2<sup>nd</sup> Bridged-T FB Lowpass


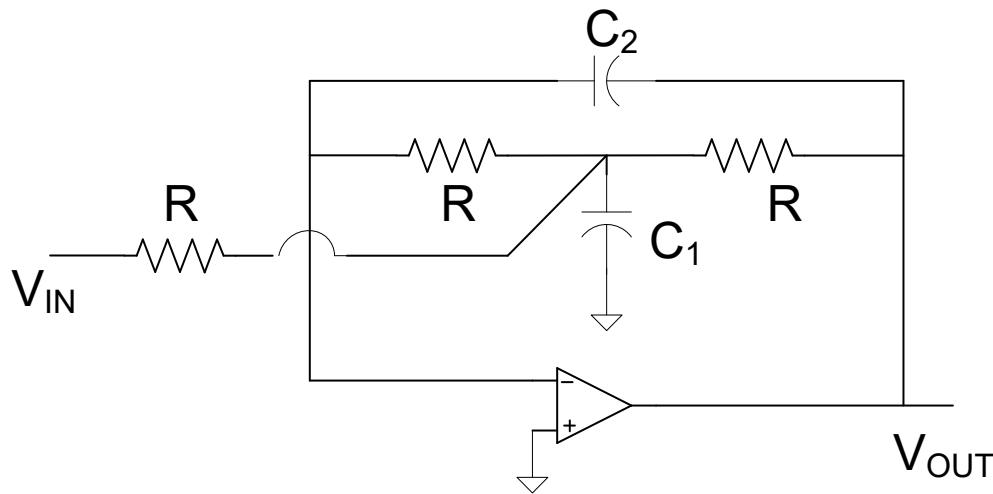
$$T(s) = - \frac{\frac{1}{R_2 R_3 C_1 C_2}}{s^2 + s \frac{1}{C_1} \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$




Equal R

$$T(s) = - \frac{\frac{1}{R^2 C_1 C_2}}{s^2 + s \left( \frac{3}{RC_1} \right) + \frac{1}{R^2 C_1 C_2}}$$

$$\omega_0 = \frac{1}{R \sqrt{C_1 C_2}} \quad Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}}$$
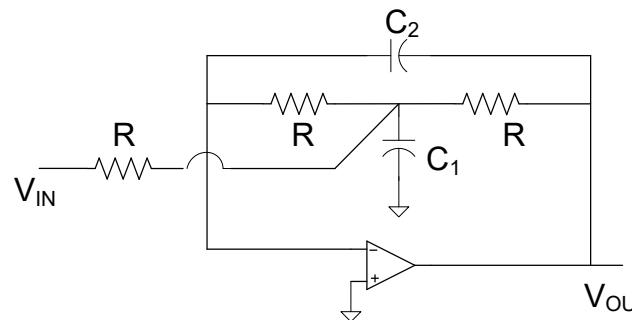
## Example: 2<sup>nd</sup> Bridged-T FB Lowpass




$$\omega_0 = \frac{1}{R\sqrt{C_1 C_2}} \quad Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}}$$

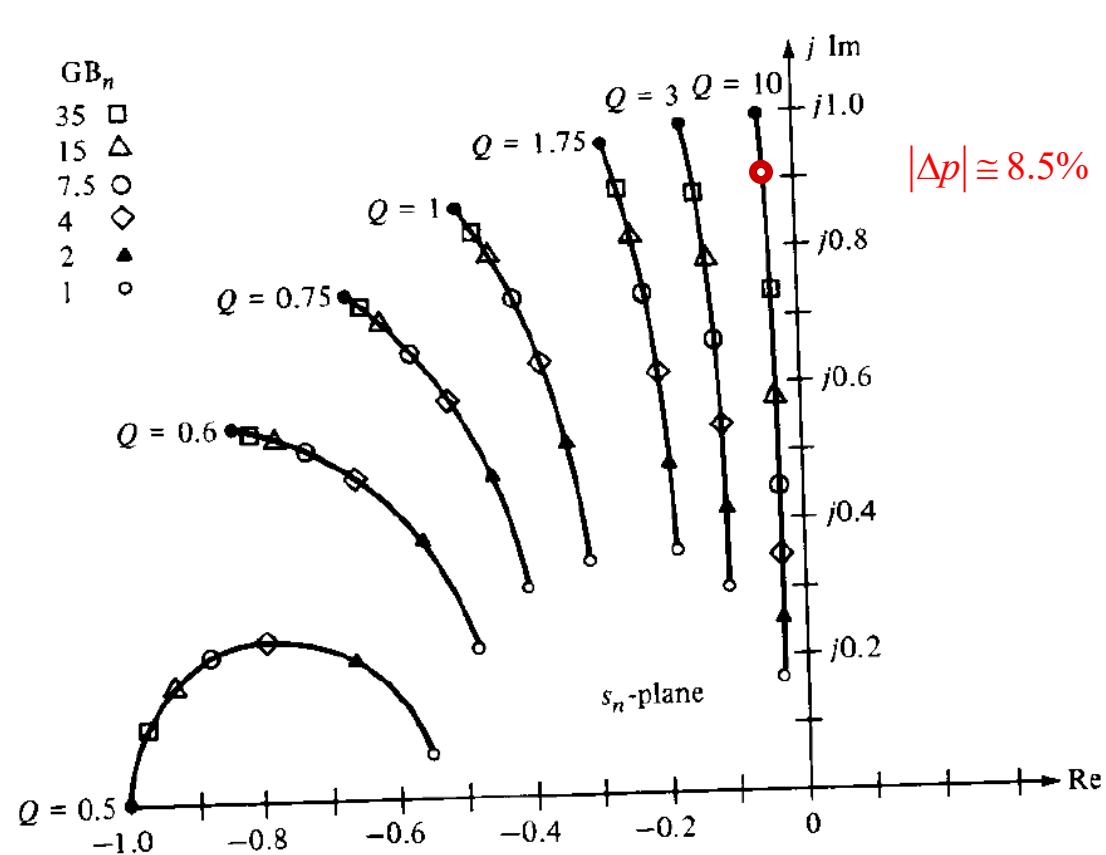
**consider**

$$\bullet \longleftrightarrow GB_n = \frac{GB}{\omega_0} = 100$$


$$A(s) = \frac{V_o}{V^+ - V^-} = \frac{GB}{s}$$


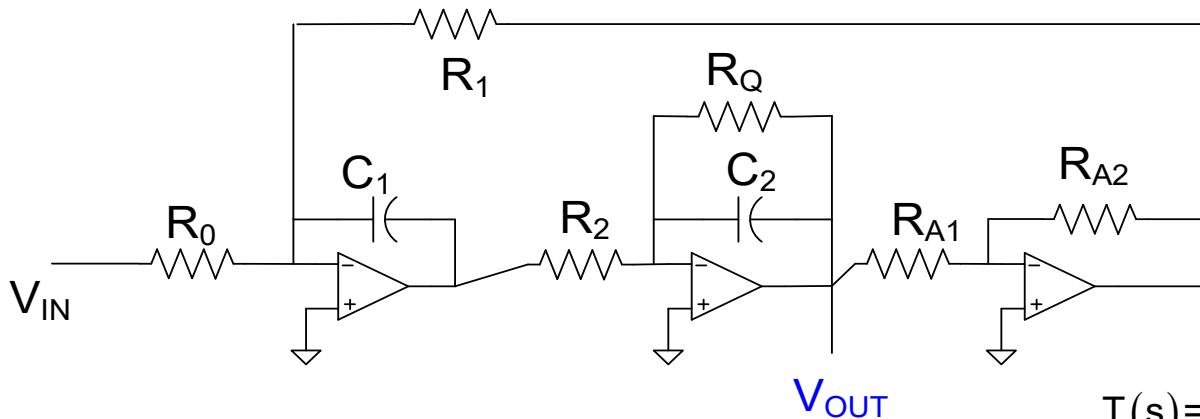
## Example: 2<sup>nd</sup> Two-Integrator-Loop Lowpass


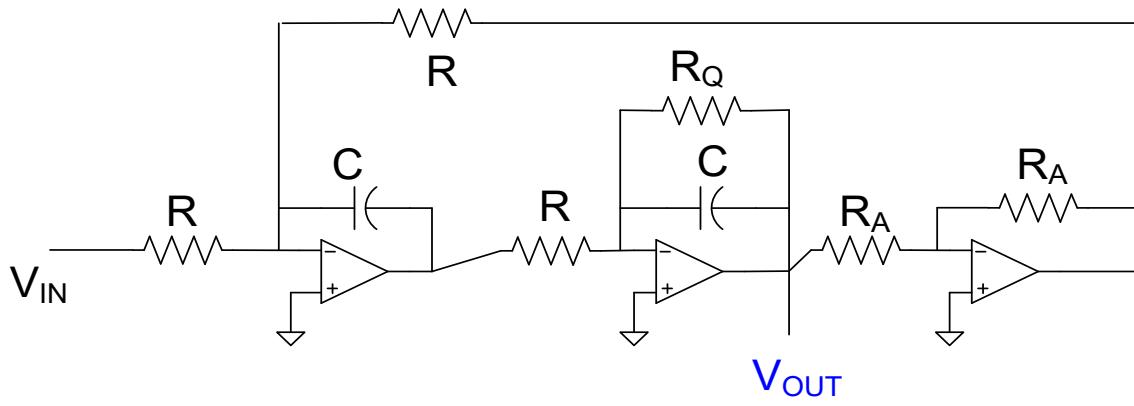
$$T(s) = -\frac{\frac{1}{R_0 R_2 C_1 C_2}}{s^2 + s \left( \frac{1}{C_2 R_Q} \right) + \frac{R_{A2}/R_{A1}}{R_1 R_2 C_1 C_2}}$$




Equal R, Equal C  
(except R<sub>Q</sub>)

$$T(s) = -\frac{\frac{1}{R^2 C^2}}{s^2 + s \left( \frac{1}{CR_Q} \right) + \frac{1}{R^2 C^2}}$$

$$\omega_0 = \frac{1}{RC}$$

$$Q = \frac{R_Q}{R}$$


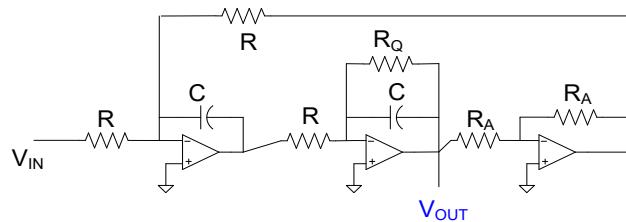
## Example: 2<sup>nd</sup> Two-Integrator-Loop Lowpass



$$\omega_0 = \frac{1}{RC} \quad Q = \frac{R_Q}{R}$$







consider
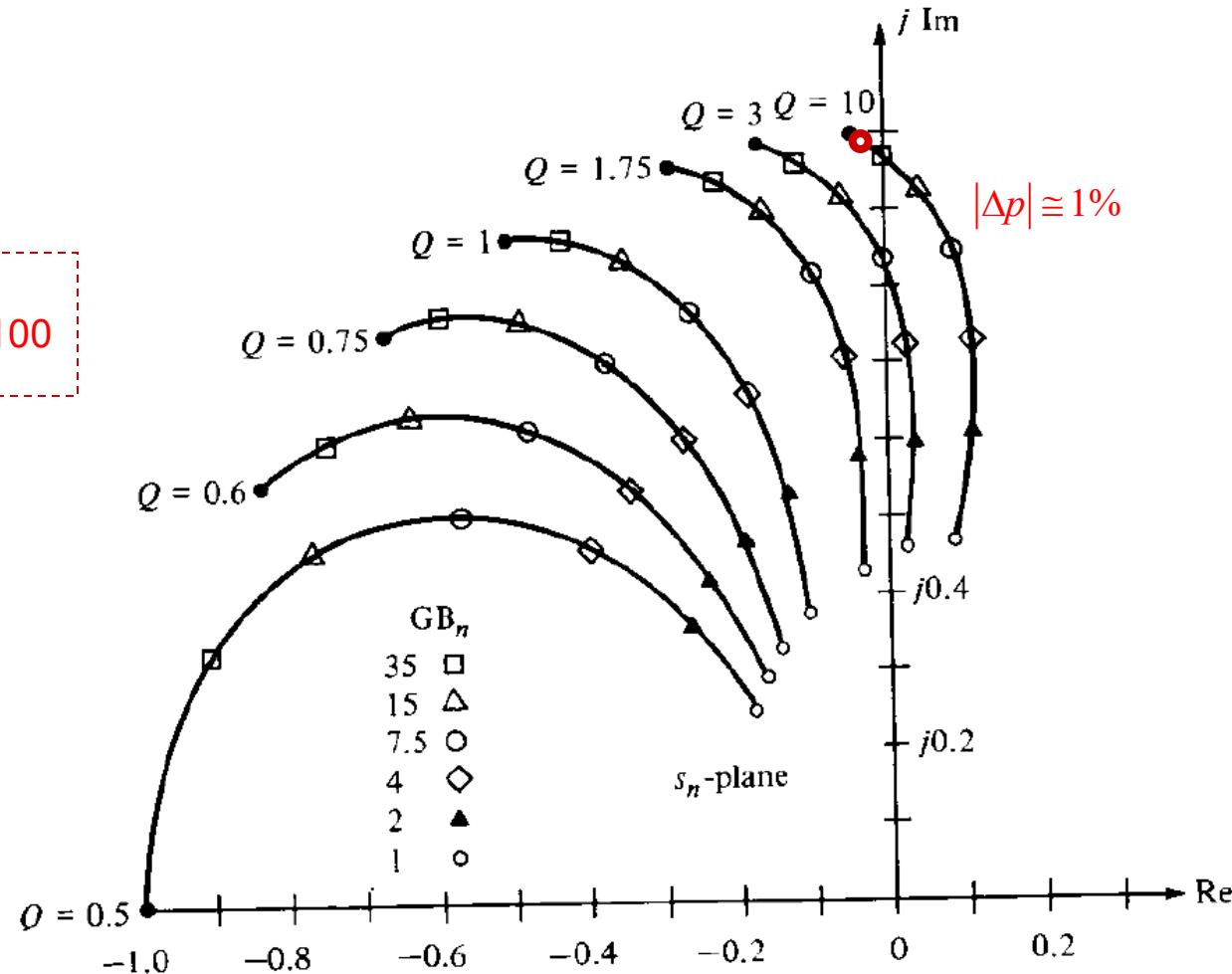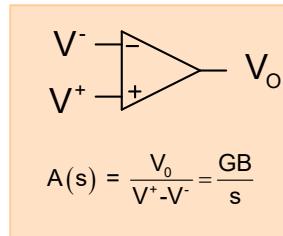
$$\bullet \longleftrightarrow GB_n = \frac{GB}{\omega_0} = 100$$



Poles “move” towards RHP as GB degrades

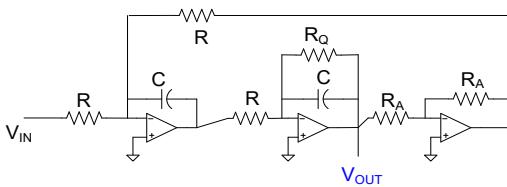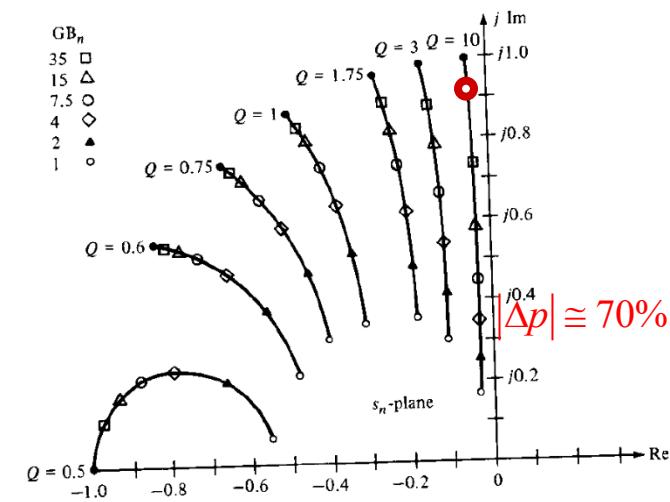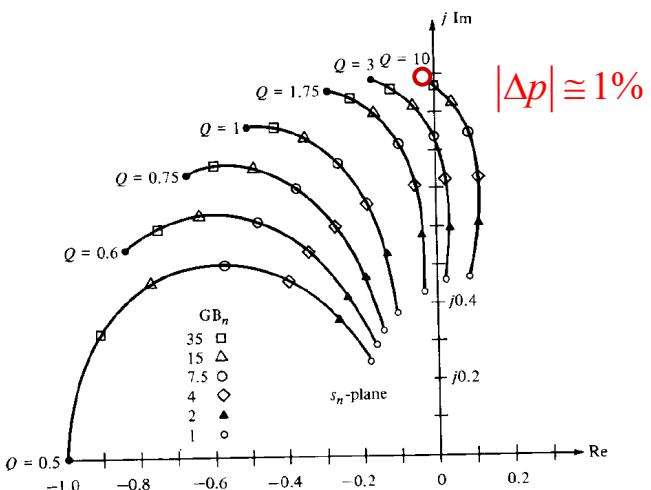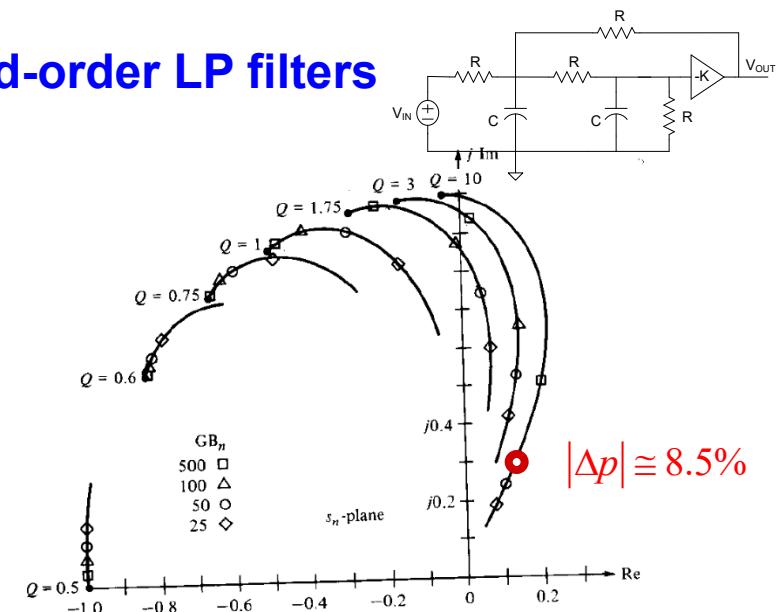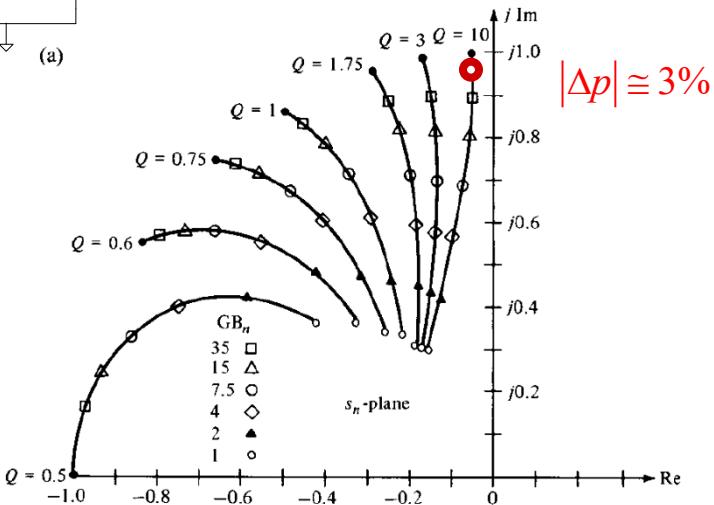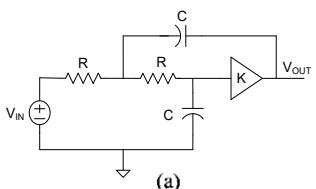
# Comparison of 4 second-order LP filters



consider


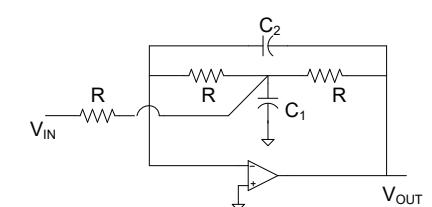
$$\longleftrightarrow \text{GB}_n = \frac{\text{GB}}{\omega_0} = .01$$




# Some Observations


- Seemingly similar structures have dramatically different sensitivity to frequency response of the Op Amp
- Critical to have enough GB if filter is to perform as desired
- Performance strongly affected by both magnitude and direction of pole movement
- Some structures appear to be totally impractical – at least for larger Q
- Different use of the Degrees of Freedom produces significantly different results

Sensitivity analysis is useful for analytical characterization of the performance of a filter

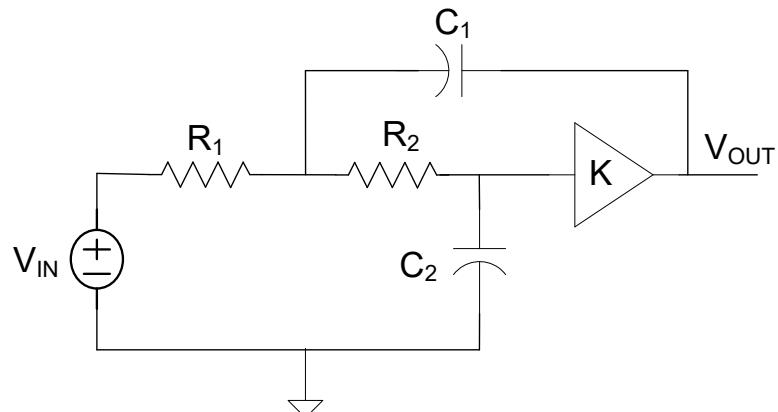
What causes the dramatic differences in performance between these two structures?  
How can the performance of different structures be compared in general?



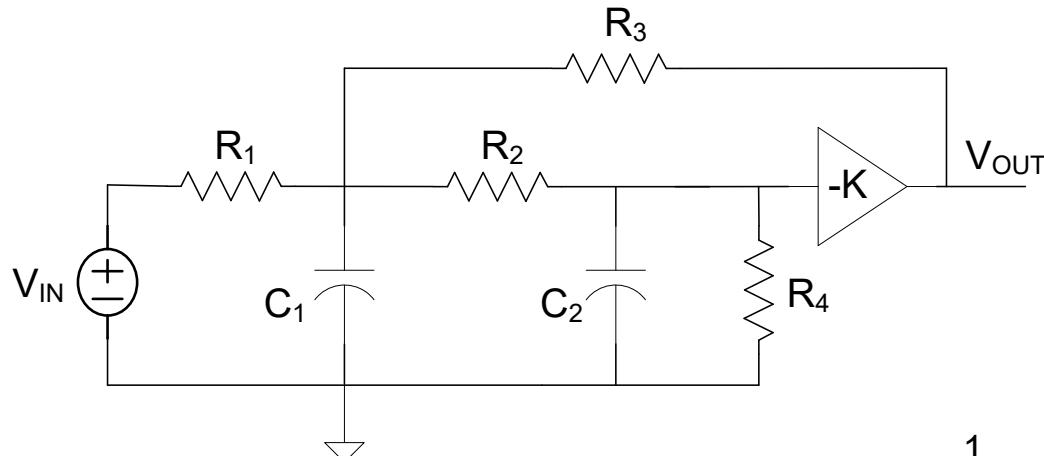
$$T(s) = K \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + s \left[ \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$




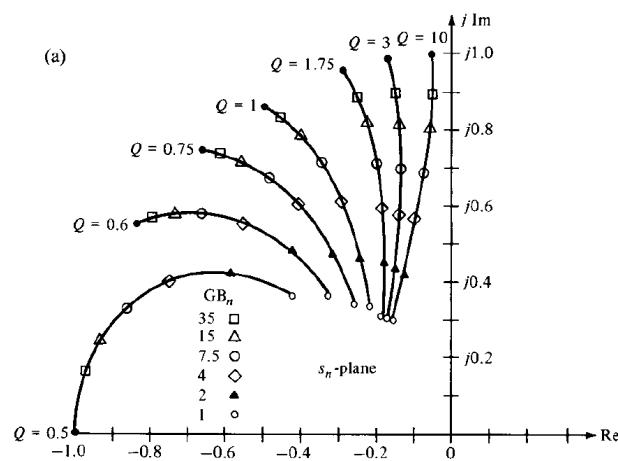
$$T(s) = -K \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + s \left[ \frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right) \right] + \left[ \frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1+(R_2/R_3)+(R_2/R_1))}{R_1 R_2 C_1 C_2} \right]}$$



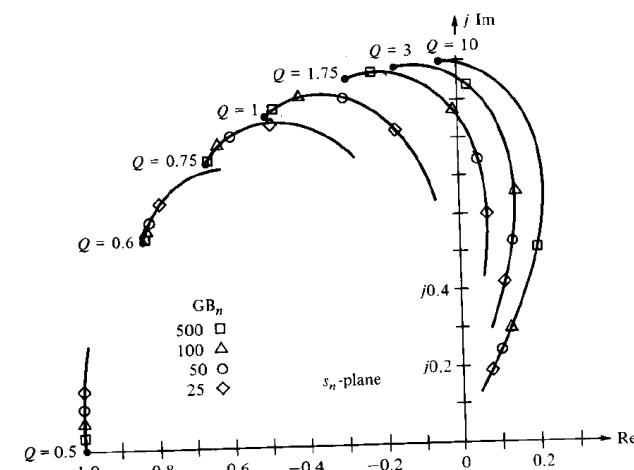**Equal R, Equal C, Q=10 Pole Locus vs  $GB_N$**



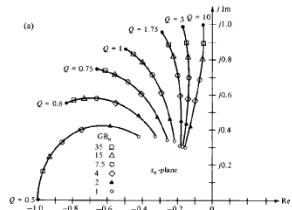
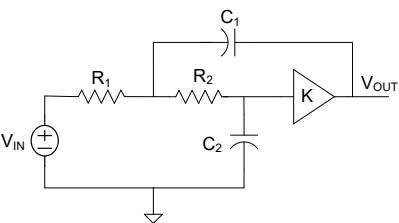
# How can the performance of different structures be compared in general?



$$T(s) = K \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + s \left[ \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$Q = \frac{1}{\sqrt{\frac{R_2 C_2}{R_1 C_1}} + \sqrt{\frac{R_1 C_2}{R_2 C_1}} + (1-K) \sqrt{\frac{R_1 C_1}{R_2 C_2}}}$$
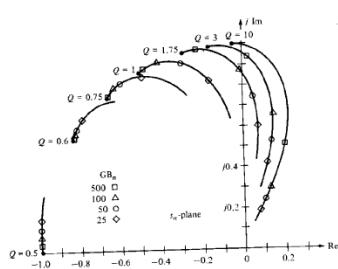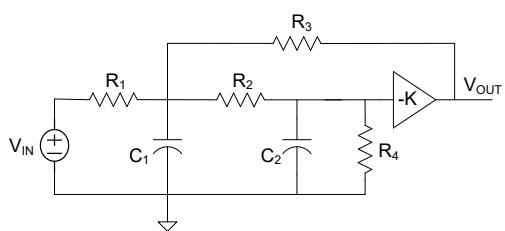
$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$



$$T(s) = -K \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + s \left[ \frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right) \right] + \left[ \frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1+(R_2/R_3)+(R_2/R_1))}{R_1 R_2 C_1 C_2} \right]}$$





$$\omega_0 = \sqrt{\frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1+(R_2/R_3)+(R_2/R_1))}{R_1 R_2 C_1 C_2}}$$

$$Q = \sqrt{\frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1+(R_2/R_3)+(R_2/R_1))}{R_1 R_2 C_1 C_2}} \cdot \frac{1}{\frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right)}$$

- Equations for key performance parameters give little insight into the differences
- Expressions for key performance parameters quite complicated

# How can the performance of different structures be compared in general?

Equal R, Equal C implementations

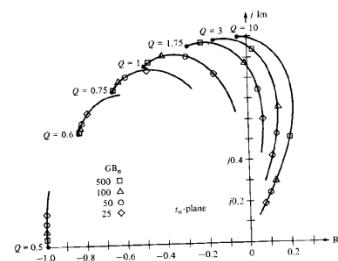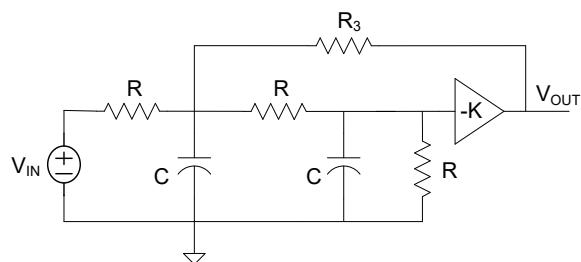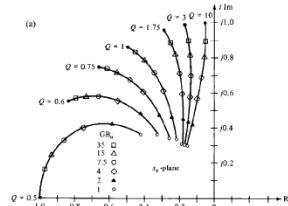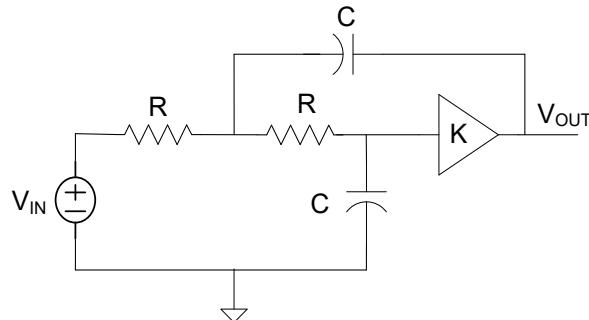

$$T(s) = K \frac{\frac{1}{R^2 C^2}}{s^2 + s \left[ \frac{(3-K)}{RC} \right] + \frac{1}{R^2 C^2}}$$



$$Q = \frac{1}{3-K} \quad \omega_0 = \frac{1}{RC}$$

$$T(s) = -K \frac{\frac{1}{R^2 C^2}}{s^2 + s \left[ \frac{5}{RC} \right] + \left[ \frac{5+K}{R^2 C^2} \right]}$$

$$Q = \frac{\sqrt{5+K}}{5} \quad \omega_0 = \frac{\sqrt{5+K}}{RC}$$


- Analytical expressions for  $\omega_0$  and Q much simpler
- Equations for key performance parameters give little insight into the differences
- Effects of individual components is obscured in these expressions
- GB effects absent in this analytical formulation !!!!

# Modeling of the Amplifiers

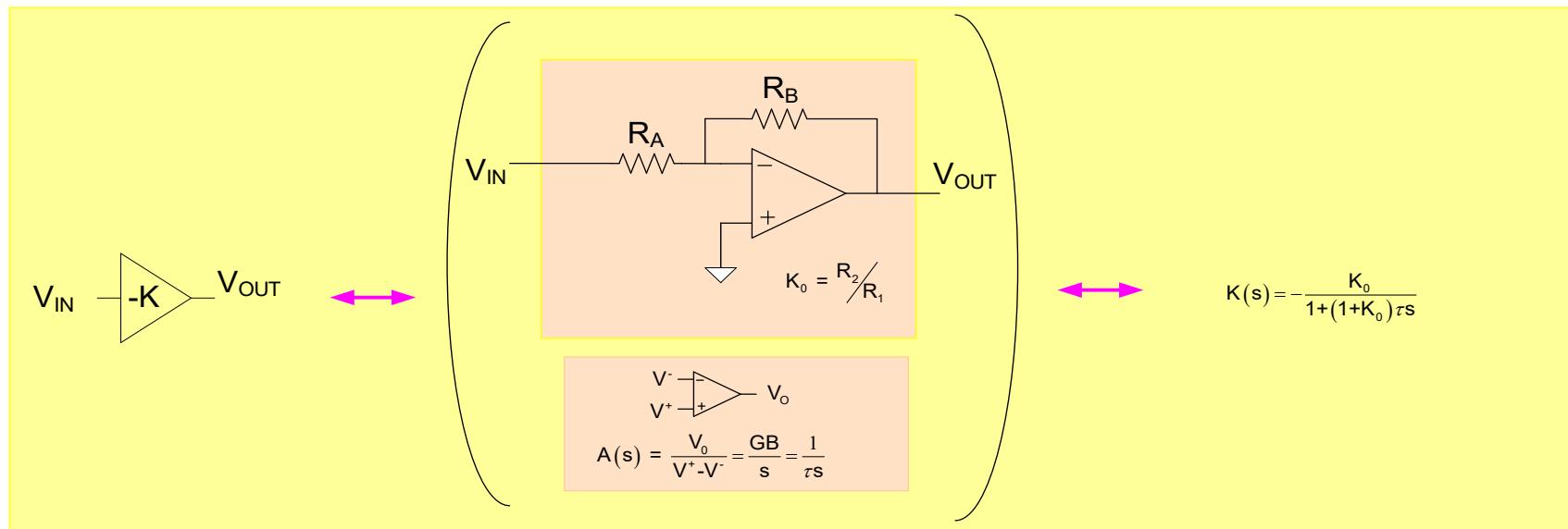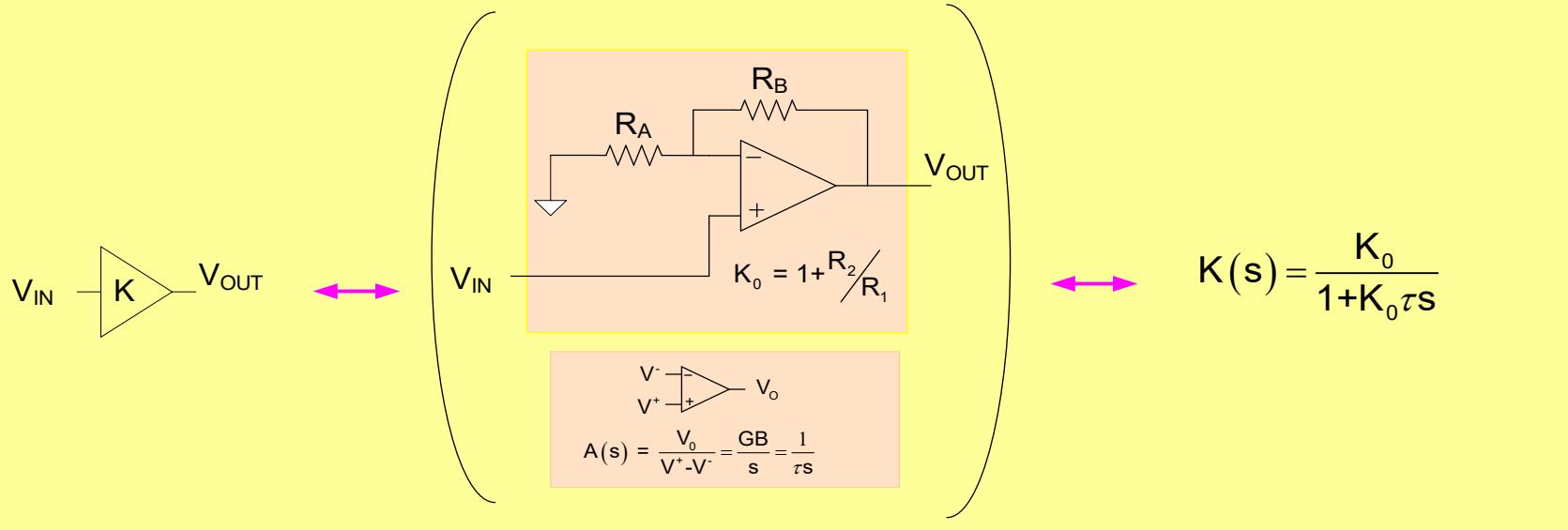

Different implementations of the amplifiers are possible  
Have used the op amp time constant in these models  $\tau = GB^{-1}$

## GB effects in +KRC Lowpass Filter

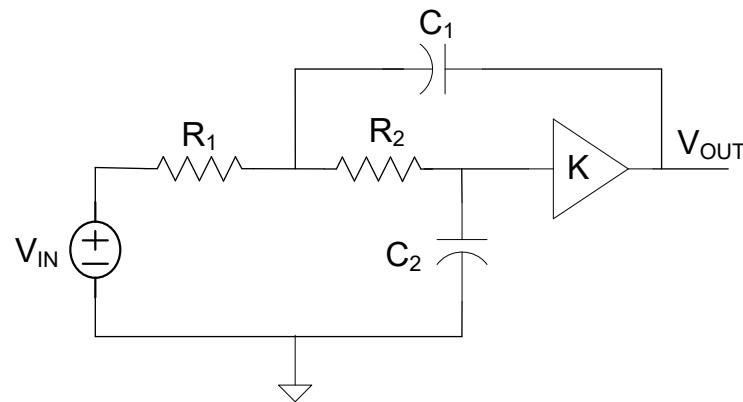

$$T(s) = K \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + s \left[ \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$K(s) = \frac{K_0}{1 + K_0 \tau s}$$

$$T(s) = \frac{\frac{K_0}{R_1 R_2 C_1 C_2}}{s^2 + s \left[ \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{(1-K_0)}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2} + K_0 \tau s \left( s^2 + s \left[ \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2} \right)}$$

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$Q = \frac{1}{\sqrt{\frac{R_2 C_2}{R_1 C_1}} + \sqrt{\frac{R_1 C_2}{R_2 C_1}} + (1-K) \sqrt{\frac{R_1 C_1}{R_2 C_2}}}$$

$\omega_0$  and Q in these expressions are for ideal op amp

$$T(s) = \frac{K_0 \omega_0^2}{s^2 + s \left[ \frac{\omega_0}{Q} \right] + \omega_0^2 + K_0 \tau s \left( s^2 + s \left[ \frac{\omega_0}{Q} \left( 1 + K_0 Q \sqrt{\frac{R_1 C_1}{R_2 C_2}} \right) \right] + \omega_0^2 \right)}$$


$$T(s) = \frac{\frac{K_0}{R_1 R_2 C_1 C_2}}{D_I(s) + K_0 \tau s (D_{RC0}(s))}$$

$D_I(s)$  is the  $D(s)$  if the OA is ideal  
 $D_{RC0}(s)$  is the  $D(s)$  of RC circuit with  $K=0$

All linear performance effects can be obtained from this formulation

Op amp introduced an additional pole and moves the desired poles

## GB effects in -KRC Lowpass Filter

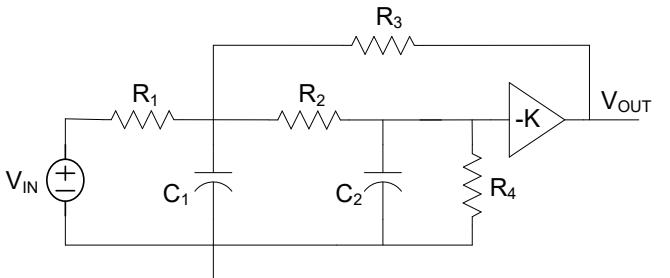

$$T(s) = -K \frac{1}{s^2 + s \left[ \frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right) \right] + \left[ \frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1+(R_2/R_3)+(R_2/R_1))}{R_1 R_2 C_1 C_2} \right]}$$

$$Q = \frac{\sqrt{\frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1+(R_2/R_3)+(R_2/R_1))}{R_1 R_2 C_1 C_2}}}{\frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right)}$$

$$\omega_0 = \sqrt{\frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1+(R_2/R_3)+(R_2/R_1))}{R_1 R_2 C_1 C_2}}$$


$\omega_0$  and Q in these expressions are for ideal op amp

Now consider:  $K(s) = \frac{-K_0}{1 + (1 + K_0)\tau s}$


$$T(s) = -K_0 \frac{1}{s^2 + s \left[ \frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right) \right] + \left[ \frac{1 + (R_1/R_3)(1+K_0) + (R_1/R_4)(1+(R_2/R_3)+(R_2/R_1))}{R_1 R_2 C_1 C_2} \right]} + \tau s (1 + K_0) \left( s^2 + s \left[ \frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right) \right] + \left[ \frac{1 + (R_1/R_3) + (R_1/R_4)(1+(R_2/R_3)+(R_2/R_1))}{R_1 R_2 C_1 C_2} \right] \right)$$

$$T(s) = \frac{\frac{-K_0}{R_1 R_2 C_1 C_2}}{D_1(s) + (1 + K_0)\tau s (D_{RC0}(s))}$$
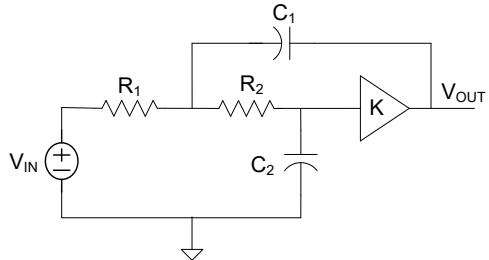
## GB effects in KRC and -KRC Lowpass Filter


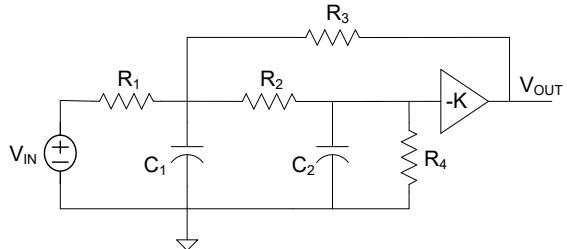
$$T(s) = \frac{K_0 \omega_0^2}{s^2 + s\left[\frac{\omega_0}{Q}\right] + \omega_0^2 + K_0 \tau s \left( s^2 + s\left[\frac{\omega_0}{Q} \left(1 + K_0 Q \sqrt{\frac{R_1 C_1}{R_2 C_2}}\right)\right] + \omega_0^2 \right)}$$



$$T(s) = \frac{\frac{K_0}{R_1 R_2 C_1 C_2}}{D_I(s) + K_0 \tau s (D_{RC0}(s))}$$


$$T(s) = -K_0 \left( \frac{1}{R_1 R_2 C_1 C_2} \left[ s^2 + s \left[ \frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right) \right] + \left[ \frac{1 + (R_1/R_3)(1+K_0) + (R_1/R_4)(1+(R_2/R_3)+(R_2/R_1))}{R_1 R_2 C_1 C_2} \right] \right) \right. \\ \left. + \tau s (1+K_0) \left( s^2 + s \left[ \frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right) \right] + \left[ \frac{1 + (R_1/R_3) + (R_1/R_4)(1+(R_2/R_3)+(R_2/R_1))}{R_1 R_2 C_1 C_2} \right] \right) \right]$$

$$T(s) = \frac{\frac{-K_0}{R_1 R_2 C_1 C_2}}{D_I(s) + (1+K_0) \tau s (D_{RC0}(s))}$$

All linear performance effects can be obtained from this formulation

Op amp introduced an additional pole and moves the desired poles
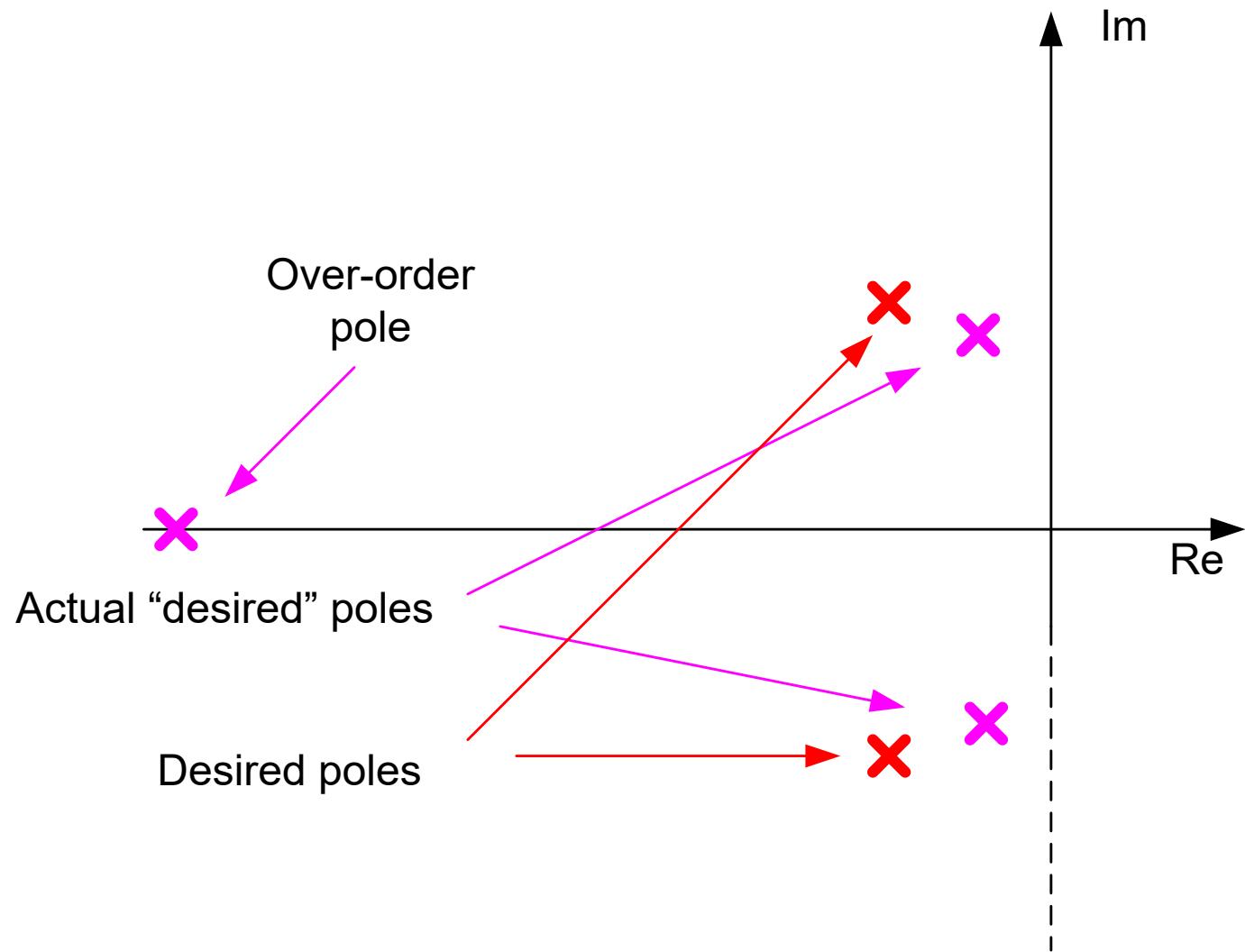
## Effects of GB on poles of KRC and -KRC Lowpass Filters





**Stay Safe and Stay Healthy !**

# **End of Lecture 18**