

EE 508

Lecture 21

Sensitivity Functions


- Comparison of Filter Structures
- Performance Prediction

$$\frac{dF}{F} = \sum_{i=1}^k \left(S_{x_i}^f \bigg|_{\vec{X}_N} \cdot \frac{dx_i}{x_{iN}} \right)$$

Dependent on circuit structure
 (for some circuits, also not dependent
 on components)

Dependent only on components
 (not circuit structure)

Consider:

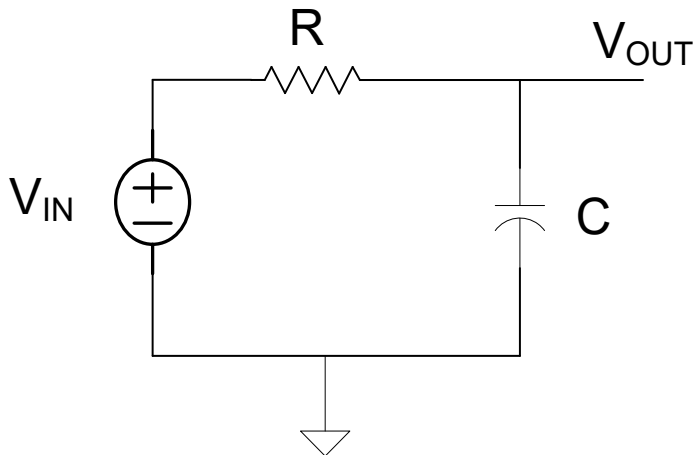

$$T(s) = \frac{1}{1+RCs}$$

$$T(s) = \frac{\omega_0}{s + \omega_0}$$

$$\omega_0 = \frac{1}{RC}$$

Metrics for Comparing Circuits

Summed Sensitivity

$$\rho_S = \sum_{i=1}^m \mathbf{S}_{x_i}^f$$

Not very useful because sum can be small even when individual sensitivities are large

Schoeffler Sensitivity

$$\rho = \sum_{i=1}^m \left| \mathbf{S}_{x_i}^f \right|$$

Strictly heuristic but does differentiate circuits with low sensitivities from those with high sensitivities

Metrics for Comparing Circuits

$$\rho = \sum_{i=1}^m \left| \mathbf{S}_{x_i}^f \right|$$

Often will consider several distinct sensitivity functions to consider effects of different components

$$\rho_R = \sum_{\text{All resistors}} \left| \mathbf{S}_{R_i}^f \right|$$

$$\rho_C = \sum_{\text{All capacitors}} \left| \mathbf{S}_{C_i}^f \right|$$

$$\rho_{OA} = \sum_{\text{All op amps}} \left| \mathbf{S}_{\tau_i}^f \right|$$

Review from last time

Homogeneity (defn)

A function f is homogeneous of order m in the n variables $\{x_1, x_2, \dots, x_n\}$ if

$$f(\lambda x_1, \lambda x_2, \dots, \lambda x_n) = \lambda^m f(x_1, x_2, \dots, x_n)$$

Note: f may be comprised of more than n variables

Review from last time

Theorem: If a function f is homogeneous of order m in the n variables $\{x_1, x_2, \dots, x_n\}$ then

$$\sum_{i=1}^n S_{x_i}^f = m$$

$$f(\lambda x_1, \lambda x_2, \dots, \lambda x_n) = \lambda^m f(x_1, x_2, \dots, x_n)$$

The concept of homogeneity and this theorem were somewhat late to appear

Are there really any useful applications of this rather odd observation?

Let $T(s)$ be a voltage or current transfer function
(i.e. dimensionless)

Observation: Impedance scaling does not change
any of the following, provided Op Amps are ideal:

$$T(s), T(j\omega), |T(j\omega)|, \omega_0, Q, p_k, z_k$$

So, consider impedance scaling by a parameter λ

$$R \rightarrow \lambda R$$

$$L \rightarrow \lambda L$$

$$C \rightarrow C / \lambda$$

For these impedance invariant functions

$$f(\lambda x_1, \lambda x_2, \dots, \lambda x_n) = \lambda^0 f(x_1, x_2, \dots, x_n)$$

Thus, all of these functions are homogeneous of order $m=0$
in the impedances

Let $T(s)$ be a Transresistance or Transconductance Transfer Function

Observation: Impedance scaling does not change any of the following, provided Op Amps are ideal:

ω_0 , Q , p_k , z_k , band edge

(these are impedance invariant functions)

So, consider impedance scaling by a parameter λ

$$R \rightarrow \lambda R$$

$$L \rightarrow \lambda L$$

$$C \rightarrow C / \lambda$$

For these impedance invariant functions

$$f(\lambda x_1, \lambda x_2, \dots, \lambda x_n) = \lambda^0 f(x_1, x_2, \dots, x_n)$$

Thus, all of these functions are homogeneous of order $m=0$ in the impedances

Theorem 1: If all op amps in a filter are ideal, then ω_o , Q , BW, all band edges, and all poles and zeros are homogeneous of order 0 in the impedances.

Theorem 2: If all op amps in a filter are ideal and if $T(s)$ is a dimensionless transfer function, $T(s)$, $T(j\omega)$, $|T(j\omega)|$, $\angle T(j\omega)$, are homogeneous of order 0 in the impedances

Theorem 1: If all op amps in a filter are ideal, then ω_o , Q , BW, all band edges, and all poles and zeros are homogeneous of order 0 in the impedances.

Proof of Theorem 1

These functions are all impedance invariant so it follows trivially that they are homogeneous of order 0 in all of the impedances

Theorem 3: If all op amps in a filter are ideal and if $T(s)$ is an impedance transfer function, $T(s)$ and $T(j\omega)$ are homogeneous of order 1 in the impedances

Theorem 4: If all op amps in a filter are ideal and if $T(s)$ is a conductance transfer function, $T(s)$ and $T(j\omega)$ are homogeneous of order -1 in the impedances

Corollary 1: If all op amps in an RC active filter are ideal and there are k_1 resistors and k_2 capacitors and if a function f is homogeneous of order 0 in the impedances, then

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^f = \sum_{i=1}^{k_2} \mathbf{S}_{C_i}^f$$

Corollary 2: If all op amps in an RC active filter are ideal and there are k_1 resistors and k_2 capacitors then

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^Q = 0$$

$$\sum_{i=1}^{k_2} \mathbf{S}_{C_i}^Q = 0$$

Corollary 1: If all op amps in an RC active filter are ideal and there are k_1 resistors and k_2 capacitors and if a function f is homogeneous of order 0 in the impedances, then

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^f = \sum_{i=1}^{k_2} \mathbf{S}_{C_i}^f$$

Corollary 2: If all op amps in an RC active filter are ideal and there are k_1 resistors and k_2 capacitors then for any pole or zero Q factor

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^Q = 0 \qquad \sum_{i=1}^{k_2} \mathbf{S}_{C_i}^Q = 0$$

Proof of Corollary 1:

Corollary 1: If all op amps in an RC active filter are ideal and there are k_1 resistors and k_2 capacitors and if a function f is homogeneous of order 0 in the impedances, then

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^f = \sum_{i=1}^{k_2} \mathbf{S}_{C_i}^f$$

Proof:

Since f is homogenous of order zero in the impedances, $z_1, z_2, \dots, z_{k_1+k_2}$,

$$\sum_{i=1}^{k_1+k_2} \mathbf{S}_{z_i}^f = 0$$



$$\therefore \sum_{i=1}^{k_1} \mathbf{S}_{R_i}^f + \sum_{i=1}^{k_2} \mathbf{S}_{1/C_i}^f = 0$$

$$\therefore \sum_{i=1}^{k_1} \mathbf{S}_{R_i}^f - \sum_{i=1}^{k_2} \mathbf{S}_{C_i}^f = 0$$



Proof of Corollary 2:

Recall:

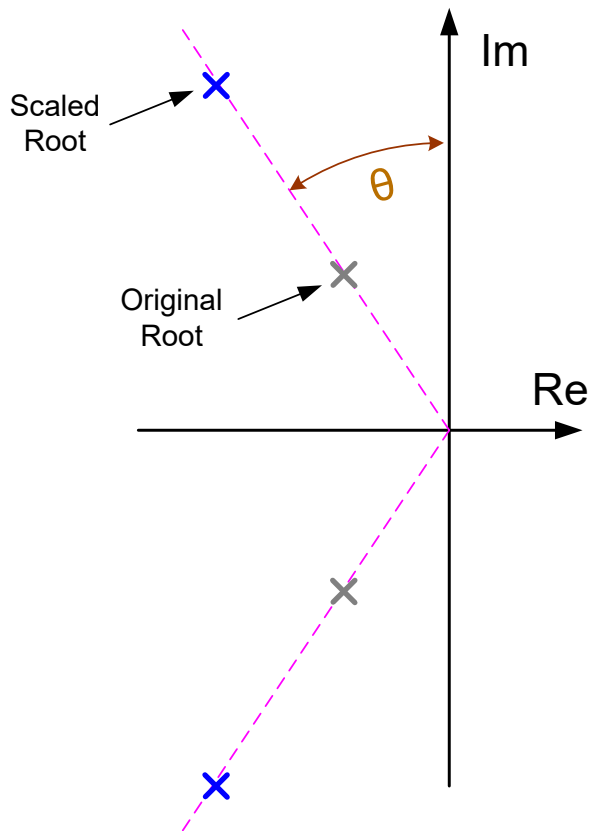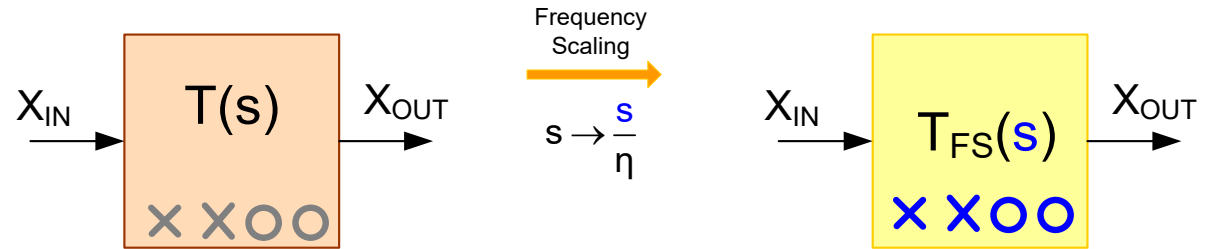

Frequency Scaling: Scaling all frequency-dependent elements by a constant

$$L \rightarrow \eta L$$

$$C \rightarrow \eta C$$


Theorem: If all components are frequency scaled, roots (poles and zeros) will move along a constant Q locus

Proof of Theorem:

$$T_{FS}(s) = T(s) \Big|_{s=\frac{s}{\eta}}$$

Proof of Corollary 2:

Recall:

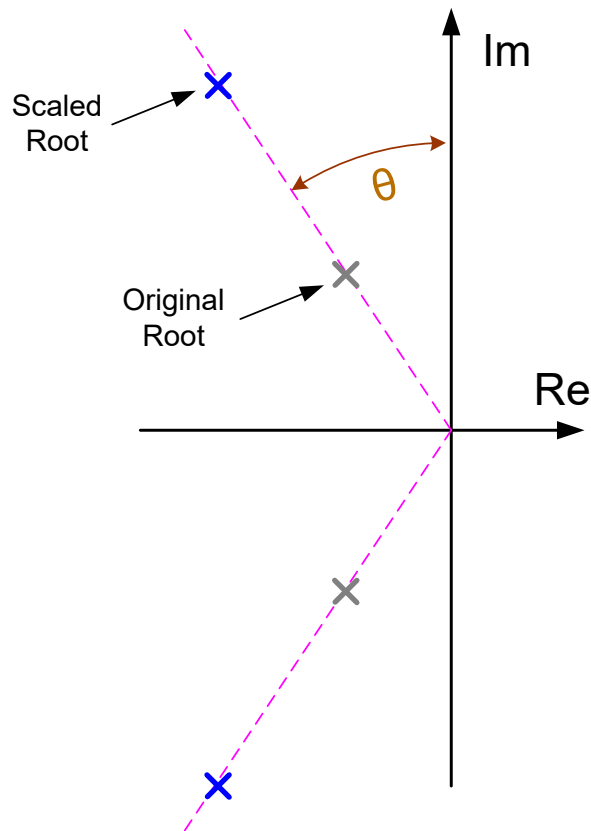

Theorem: If all components are frequency scaled, roots (poles and zeros) will move along a constant Q locus

Proof: $T_{FS}(s) = T(s) \Big|_{s=\frac{s}{\eta}}$

Let p be a pole (or zero) of $T(s)$

$$T(p)=0 \quad \text{consider} \quad p = \frac{p}{\eta}$$

$$T_{FS}(s) = T\left(\frac{s}{\eta}\right) = T(s)$$

Since true for any variable, substitute in p

$$T_{FS}(p) = T\left(\frac{p}{\eta}\right) = T(p) = 0$$


Thus p is a pole (or zero) of $T_{FS}(s)$

Proof of Corollary 2:

Recall:

Theorem: If all components are frequency scaled, roots (poles and zeros) will move along a constant Q locus

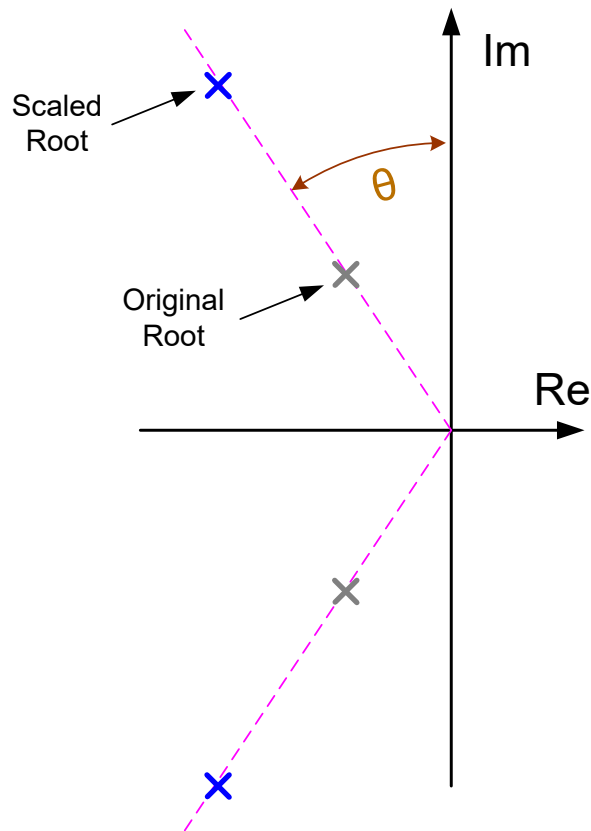Proof: Thus \mathbf{p} is a pole (or zero) of $T_{FS}(s)$



$$\mathbf{p} = \frac{\mathbf{p}}{\eta}$$

$$\mathbf{p} = \mathbf{p}\eta$$

Express \mathbf{p} in polar form

$$\mathbf{p} = r e^{j\beta}$$


$$\mathbf{p} = \eta \mathbf{p} = \eta r e^{j\beta}$$

Thus \mathbf{p} and \mathbf{p} have the same angle

Thus the scaled root has the same root Q



Proof of Corollary 2: Impedance and Frequency Scaling

Recall:

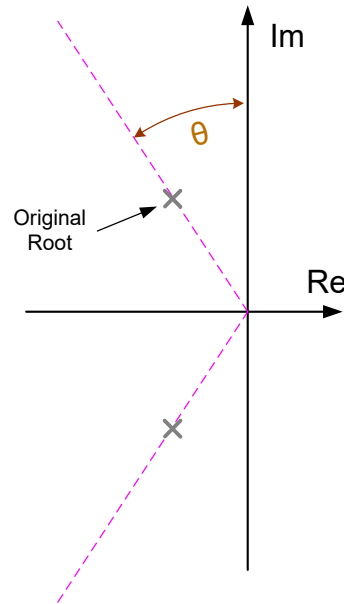

Impedance Scaling

Frequency Scaling

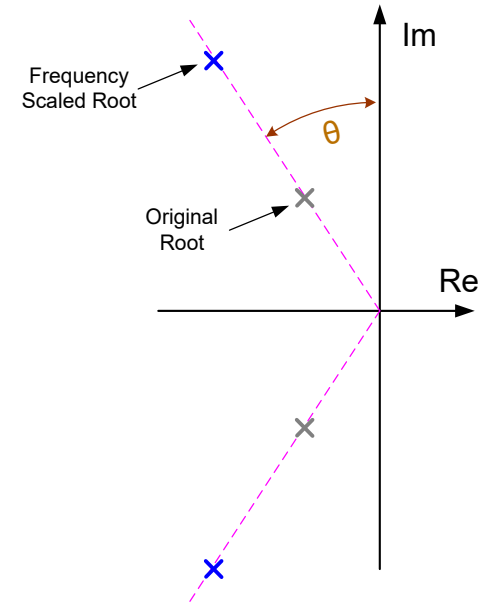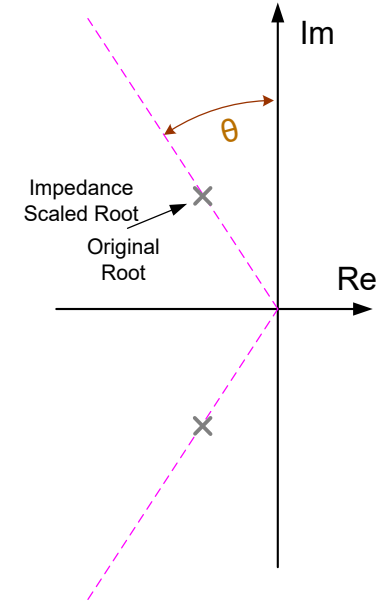

Proof of Corollary 2:

Corollary 2: If all op amps in an RC active filter are ideal and there are k_1 resistors and k_2 capacitors then $\sum_{i=1}^{k_2} \mathbf{S}_{C_i}^Q = \mathbf{0}$ and $\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^Q = \mathbf{0}$

Since impedance scaling does not change pole (or zero) Q , the pole (or zero) Q must be homogeneous of order 0 in the impedances

(For more generality, assume k_3 inductors)

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^Q + \sum_{i=1}^{k_2} \mathbf{S}_{1/C_i}^Q + \sum_{i=1}^{k_3} \mathbf{S}_{L_i}^Q = \mathbf{0} \quad (1)$$

Since frequency scaling does not change pole (or zero) Q , the pole (or zero) Q must be homogeneous of order 0 in the frequency scaling elements

$$\sum_{i=1}^{k_2} \mathbf{S}_{C_i}^Q + \sum_{i=1}^{k_3} \mathbf{S}_{L_i}^Q = \mathbf{0} \quad (2)$$

Proof of Corollary 2:

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^Q + \sum_{i=1}^{k_2} \mathbf{S}_{1/C_i}^Q + \sum_{i=1}^{k_3} \mathbf{S}_{L_i}^Q = \mathbf{0} \quad (1)$$

$$\sum_{i=1}^{k_2} \mathbf{S}_{C_i}^Q + \sum_{i=1}^{k_3} \mathbf{S}_{L_i}^Q = \mathbf{0} \quad (2)$$

From theorem about sensitivity of reciprocals, can write (1) as

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^Q - \sum_{i=1}^{k_2} \mathbf{S}_{C_i}^Q + \sum_{i=1}^{k_3} \mathbf{S}_{L_i}^Q = \mathbf{0} \quad (3)$$

It follows from (2) and (3) that


$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^Q = \mathbf{0} \quad (4)$$

Since RC network, it follows from (4) and (2) that

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^Q = \mathbf{0} \quad \sum_{i=1}^{k_2} \mathbf{S}_{C_i}^Q = \mathbf{0}$$



Example

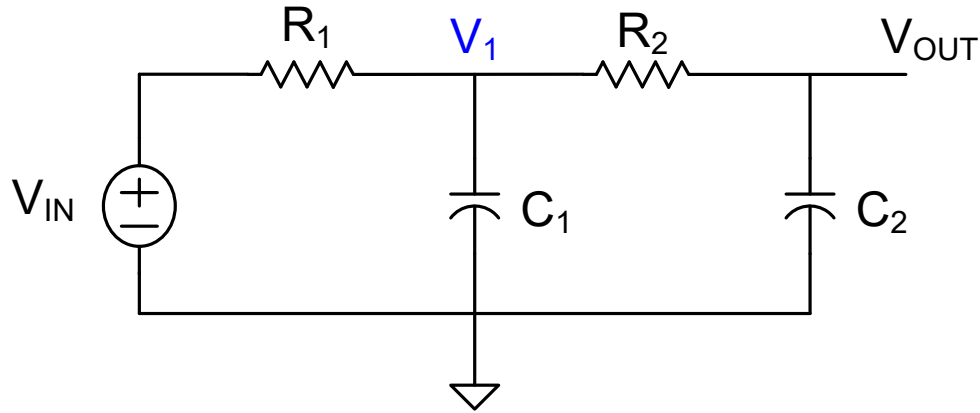

Determine the passive Q sensitivities

$$S_{R_1}^Q \quad S_{R_2}^Q \quad S_{C_1}^Q \quad S_{C_2}^Q$$

$$\left. \begin{aligned} V_{OUT}(sC_1 + G_2) &= V_1 G_2 \\ V_1(sC_1 + G_1 + G_2) &= V_{IN} G_1 + V_{OUT} G_2 \end{aligned} \right\}$$

$$T(s) = \frac{1}{s^2(R_1 R_2 C_1 C_2) + s(R_1 C_1 + R_1 C_2 + R_2 C_2) + 1}$$


$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{R_1 C_1 + R_1 C_2 + R_2 C_2}$$

By the definition of sensitivity, it follows that

$$S_{R_1}^Q = \frac{(R_1 C_1 + R_1 C_2 + R_2 C_2) \frac{1}{2} (R_1 R_2 C_1 C_2)^{-1/2} R_2 C_1 C_2 - (C_1 + C_2) (R_1 R_2 C_1 C_2)^{1/2}}{(R_1 C_1 + R_1 C_2 + R_2 C_2)^2} \cdot \frac{R_1}{Q}$$

Example

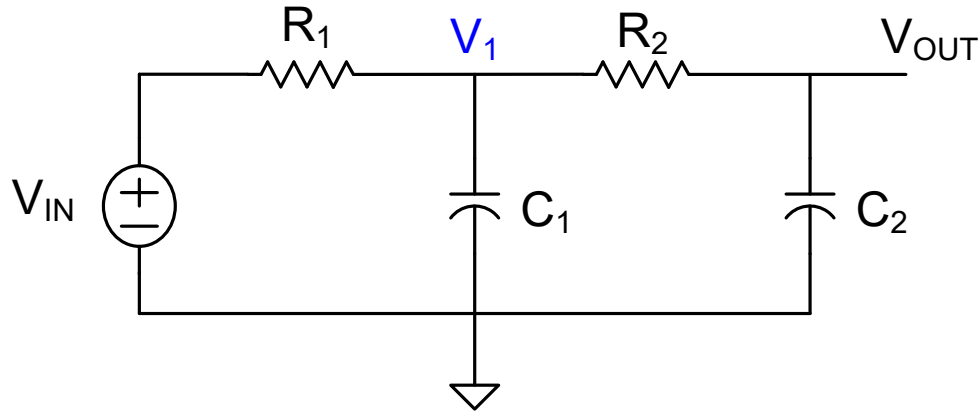

Determine the passive Q sensitivities


$$S_{R_1}^Q \quad S_{R_2}^Q \quad S_{C_1}^Q \quad S_{C_2}^Q$$

$$S_{R_1}^Q = \frac{(R_1 C_1 + R_1 C_2 + R_2 C_1) \frac{1}{2} (R_1 R_2 C_1 C_2)^{-1/2} R_2 C_1 C_2 - (C_1 + C_2) (R_1 R_2 C_1 C_2)^{1/2}}{(R_1 C_1 + R_1 C_2 + R_2 C_2)^2} \cdot \frac{R_1}{Q}$$

Following some tedious manipulations, this simplifies to

$$S_{R_1}^Q = \frac{1}{2} - \frac{R_1 (C_1 + C_2)}{R_1 C_1 + R_1 C_2 + R_2 C_2}$$

Example

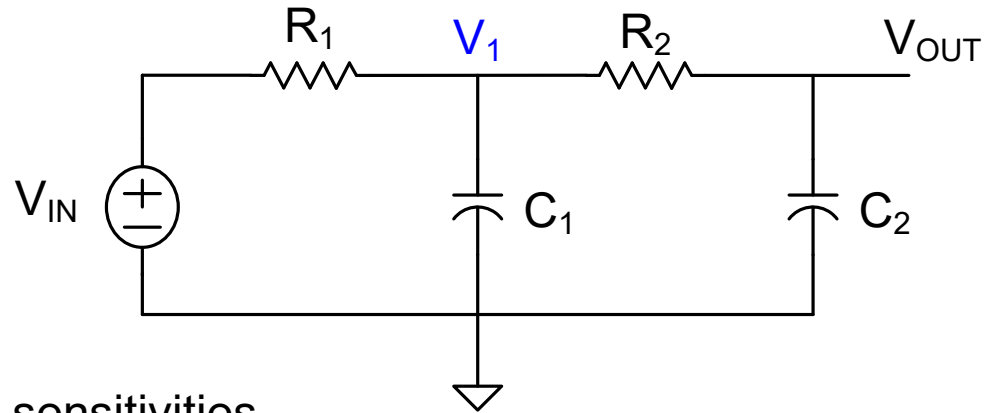

Determine the passive Q sensitivities

Following the same type of calculations, can obtain

$$S_{R_1}^Q = \frac{1}{2} - \frac{R_1(C_1 + C_2)}{R_1C_1 + R_1C_2 + R_2C_2}$$

$$S_{R_2}^Q = \frac{1}{2} - \frac{R_2C_2}{R_1C_1 + R_1C_2 + R_2C_2}$$

$$S_{C_1}^Q = \frac{1}{2} - \frac{R_1C_1}{R_1C_1 + R_1C_2 + R_2C_2}$$

$$S_{C_2}^Q = \frac{1}{2} - \frac{C_2(R_1 + R_2)}{R_1C_1 + R_1C_2 + R_2C_2}$$

Verify

$$\sum_{i=1}^{k_2} S_{C_i}^Q = 0$$

$$\sum_{i=1}^{k_1} S_{R_i}^Q = 0$$

Could have saved considerable effort in calculations by using these theorems after

$S_{R_1}^Q$ and $S_{C_1}^Q$ were calculated

Corollary 3: If all op amps in an RC active filter are ideal and there are k_1 resistors and k_2 capacitors and if p_k is any pole and z_h is any zero, then

$$\sum_{i=1}^{k_1} S_{R_i}^{p_k} = -1$$

$$\sum_{i=1}^{k_2} S_{C_i}^{p_k} = -1$$

and

$$\sum_{i=1}^{k_1} S_{R_i}^{z_h} = -1$$

$$\sum_{i=1}^{k_2} S_{C_i}^{z_h} = -1$$

Corollary 3: If all op amps in an RC active filter are ideal and there are k_1 resistors and k_2 capacitors and if p_k is any pole and z_h is any zero, then

$$\sum_{i=1}^{k_1} S_{R_i}^{p_k} = -1$$

$$\sum_{i=1}^{k_2} S_{C_i}^{p_k} = -1$$

and

$$\sum_{i=1}^{k_1} S_{R_i}^{z_h} = -1$$

$$\sum_{i=1}^{k_2} S_{C_i}^{z_h} = -1$$

Proof:

It was shown that scaling the frequency dependent elements by a factor η divides the pole (or zero) by η

Thus roots (poles and zeros) are homogeneous of order -1 in the frequency scaling elements

Proof:

Thus roots (poles and zeros) are homogeneous of order -1 in the frequency scaling elements

(For more generality, assume k_3 inductors)

$$\sum_{i=1}^{k_2} \mathbf{S}_{C_i}^p + \sum_{i=1}^{k_3} \mathbf{S}_{L_i}^p = -1 \quad (1)$$

Since impedance scaling does not affect the poles, they are homogeneous of order 0 in the impedances

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^p + \sum_{i=1}^{k_2} \mathbf{S}_{1/C_i}^p + \sum_{i=1}^{k_3} \mathbf{S}_{L_i}^p = 0 \quad (2)$$

Since there are no inductors in an active RC network, it follows from (1) that

$$\sum_{i=1}^{k_2} \mathbf{S}_{C_i}^p = -1$$

And then from (2) and the theorem about sensitivity to reciprocals that

$$\sum_{i=1}^{k_1} \mathbf{S}_{R_i}^p = -1$$

Corollary 4: If all op amps in an RC active filter are ideal and there are k_1 resistors and k_2 capacitors and if Z_{IN} is any input impedance of the network, then

$$\sum_{i=1}^{k_1} S_{R_i}^{Z_{IN}} - \sum_{i=1}^{k_2} S_{C_i}^{Z_{IN}} = 1$$

Claim: If op amps in the filters considered previously are not ideal but are modeled by a gain $A(s)=1/(\tau s)$, then all previous summed sensitivities developed for ideal op amps hold provided they are evaluated at the nominal value of $\tau=0$

Sensitivity Analysis

If a closed-form expression for a function f is obtained, a straightforward but tedious analysis can be used to obtain the sensitivity of the function to any components

$$S_x^f = \frac{\partial f}{\partial x} \cdot \frac{x}{f}$$

Consider:

$$T(s) = \frac{\sum_{i=0}^m a_i s^i}{\sum_{i=0}^n b_i s^i} = K \frac{\prod_{i=1}^m (s-z_i)}{\prod_{i=1}^n (s-p_i)}$$

Closed-form expressions for $T(s)$, $T(j\omega)$, $|T(j\omega)|$, $\angle T(j\omega)$, a_i , b_i , can be readily obtained

Sensitivity Analysis

If a closed-form expression for a function f is obtained, a straightforward but tedious analysis can be used to obtain the sensitivity of the function to any components

$$S_x^f = \frac{\partial f}{\partial x} \cdot \frac{x}{f}$$

Consider:

$$T(s) = \frac{\sum_{i=0}^m a_i s^i}{\sum_{i=0}^n b_i s^i} = K \frac{\prod_{i=1}^m (s-z_i)}{\prod_{i=1}^n (s-p_i)}$$

Closed-form expressions for p_i , z_i , pole or zero Q , pole or zero ω_0 , peak gain, ω_{3dB} , BW, ... (generally the most critical and useful circuit characteristics) are difficult or impossible to obtain !

Bilinear Property of Electrical Networks

Theorem: Let x be any component or Op Amp time constant (1st order Op Amp model) of any linear active network employing a finite number of amplifiers and lumped passive components. Any transfer function of the network can be expressed in the form

$$T(s) = \frac{N_0(s) + xN_1(s)}{D_0(s) + xD_1(s)}$$


where N_0 , N_1 , D_0 , and D_1 are polynomials in s that are not dependent upon x

A function that can be expressed as given above is said to be a bilinear function in the variable x and this is termed a bilateral property of electrical networks.

The bilinear relationship is useful for

1. Checking for possible errors in an analysis
2. Pole sensitivity analysis

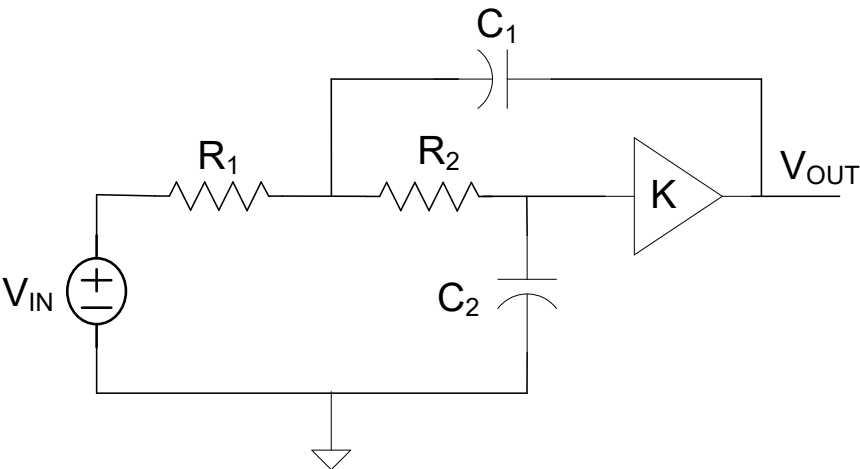Example of Bilinear Property : +KRC Lowpass Filter




$$T(s) = \frac{\frac{K_0}{R_1 R_2 C_1 C_2}}{s^2 + s \left[\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{(1-K_0)}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2} + K_0 \tau s \left(s^2 + s \left[\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2} \right)}$$

Consider R_1

$$T(s) = \frac{\frac{K_0}{R_2 C_1 C_2}}{R_1 s^2 + s \left[\frac{1}{C_1} + R_1 \frac{1}{R_2 C_1} + R_1 \frac{(1-K_0)}{R_2 C_2} \right] + \frac{1}{R_2 C_1 C_2} + K_0 \tau s \left(R_1 s^2 + s \left[\frac{1}{C_1} + R_1 \frac{1}{R_2 C_1} + R_1 \frac{1}{R_2 C_2} \right] + \frac{1}{R_2 C_1 C_2} \right)}$$

$$T(s) = \frac{\left[\frac{K_0}{R_2 C_1 C_2} \right] + R_1 \cdot [0]}{\left[s \frac{1}{C_1} + \frac{1}{R_2 C_1 C_2} + K_0 \tau s \left(s \frac{1}{C_1} \right) + \frac{1}{R_2 C_1 C_2} \right] + R_1 \left[s^2 + s \left[\frac{1}{R_2 C_1} + \frac{(1-K_0)}{R_2 C_2} \right] + K_0 \tau s \left(s^2 + s \left[\frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} \right] \right) \right]}$$

Example of Bilinear Property

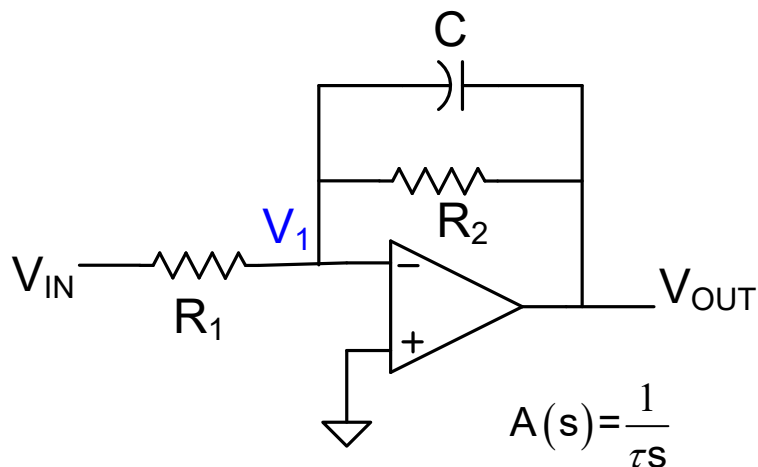

$$\left. \begin{aligned} V_1(G_1 + G_2 + sC) &= V_{IN}G_1 + V_{OUT}(sC + G_2) \\ V_{OUT} &= -V_1\left(\frac{1}{\tau s}\right) \end{aligned} \right\}$$

$$T(s) = \frac{-R_2}{R_1 + R_1 R_2 C s + \tau s (s C R_1 R_2 + R_1 + R_2)}$$


Consider R_1

$$T(s) = \frac{-R_2 + 0 \bullet R_1}{[\tau s R_2] + R_1 [1 + R_2 C s + \tau s (s C R_2 + 1)]}$$

Consider τ

$$T(s) = \frac{-R_2 + 0 \bullet \tau}{[R_1 (1 + R_2 C s)] + \tau [s R_2 + s R_1 (s C R_2 + 1)]}$$

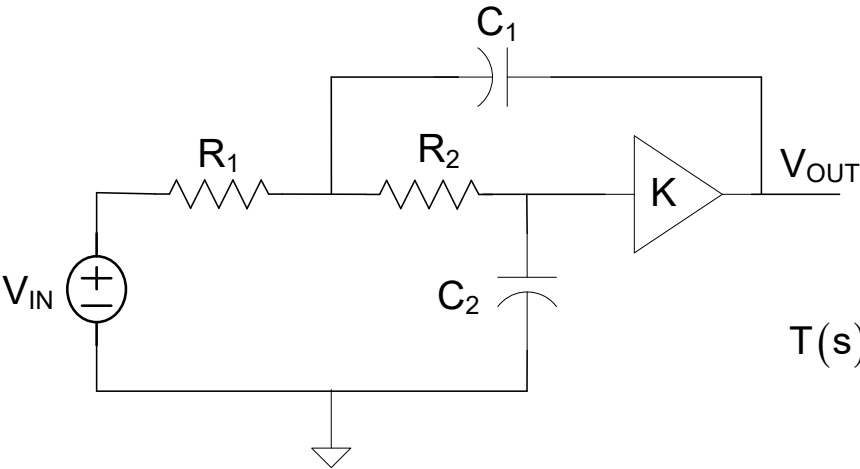Example of Bilinear Property : +KRC Lowpass Filter



Equal R Equal C

$$T(s) = \frac{\frac{K_0}{R^2 C^2}}{s^2 + s \left[\frac{(3-K_0)}{RC} \right] + \frac{1}{R^2 C^2} + K_0 \tau s \left(s^2 + s \left[\frac{3}{RC} \right] + \frac{1}{R^2 C^2} \right)}$$

$$T(s) = \frac{K_0}{R^2 (C^2 s^2 + K_0 \tau s C^2) + R (s C (3-K_0) + 3 K_0 C \tau s^2) + (1 + K_0 \tau s)}$$

Can not eliminate the R^2 term

- Bilinear property only applies to individual components
- Bilinear property was established only for $T(s)$



Stay Safe and Stay Healthy !

End of Lecture 21