

EE 508

Lecture 36



Oscillators, VCOs, and Oscillator/VCO-Derived Filters

Review from last lecture:

Only two of these circuits are useful directly as bias generators!

Inverse Widlar

Not stable
equilibrium point !

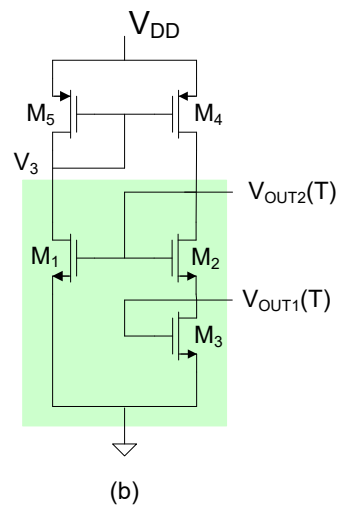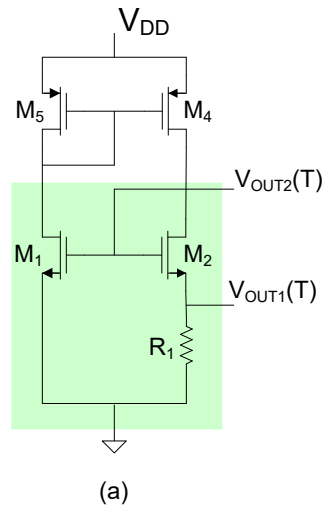

Inverse Widlar

$$V_{O1} = V_{Tn} \left(\frac{1 - \sqrt{\frac{W_2 L_1}{M_{IW} W_1 L_2}}}{1 + \sqrt{\frac{W_2 L_3}{W_3 L_2} - \sqrt{\frac{W_2 L_1}{M_{IW} W_1 L_2}}}} \right)$$

$$V_{O2} = V_{Tn} \left(\frac{1 + \sqrt{\frac{W_2 L_3}{W_3 L_2} - 2 \sqrt{\frac{W_2 L_1}{M_{IW} W_1 L_2}}}}{1 + \sqrt{\frac{W_2 L_3}{W_3 L_2} - \sqrt{\frac{W_2 L_1}{M_{IW} W_1 L_2}}}} \right)$$



Widlar

$$V_{O1} = \left(\frac{\theta_1}{2} \pm \sqrt{\frac{\theta_1 V_{Tn}}{2} + \left(\frac{\theta_1}{2} \right)^2} \right) \left(1 - \sqrt{\frac{W_1 L_2}{M_W W_2 L_1}} \right)$$

$$V_{O2} = V_{Tn} + \frac{\theta_1}{2} \pm \sqrt{\frac{\theta_1 V_{Tn}}{2} + \left(\frac{\theta_1}{2} \right)^2}$$

$$I_{D1} = M_W I_{D2}$$
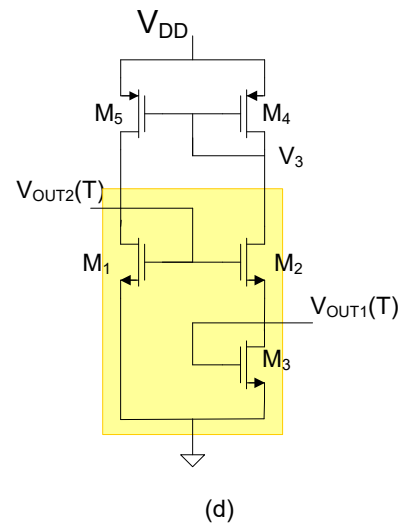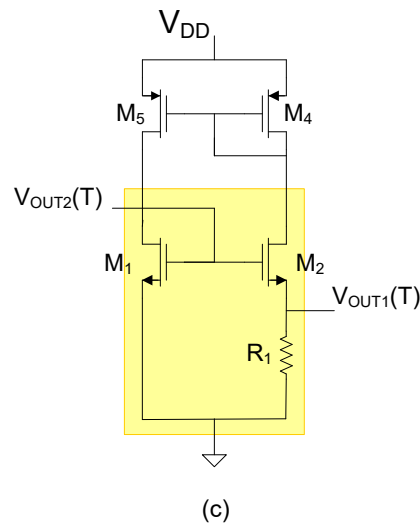
$$\theta_1 = \frac{M_W 2 L_1}{R \mu_n C_{OX} W_1}$$




Widlar


Not stable
equilibrium point !

Review from last lecture:

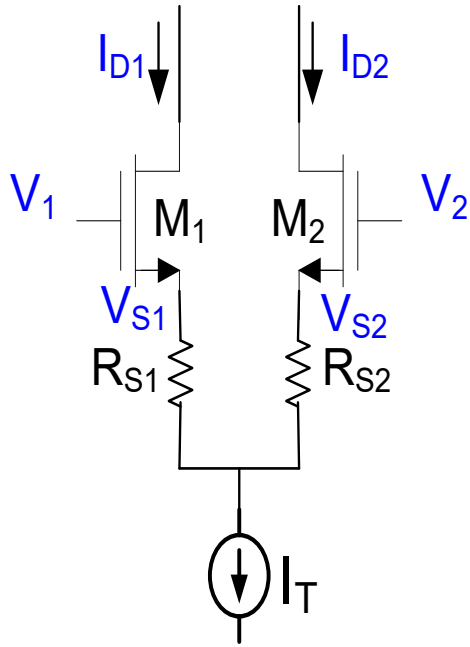Transconductance Linearization Strategies



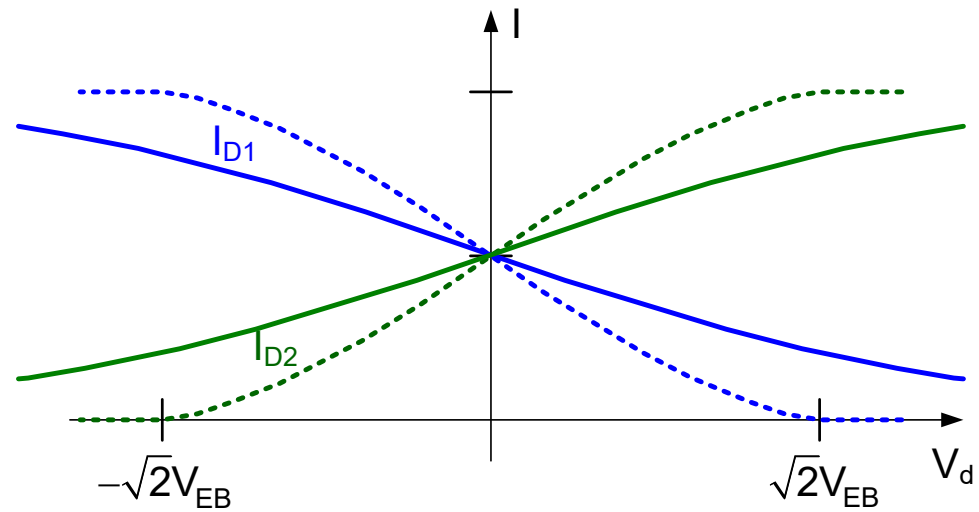
$$\sqrt{\frac{1}{\beta}} \left(\sqrt{I_T - I_{D1}} - \sqrt{I_{D1}} \right) + R_S (I_T - 2I_{D1}) = V_d$$



Review from last lecture:


Programmable Filter Structures

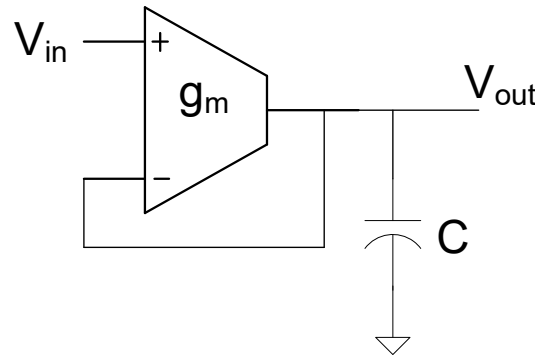It will be assumed that the transconductance gain can be programmed with either a dc current or a dc voltage





$$T(s) = \frac{g_m}{g_m + sC}$$

Programmable First-Order Low-Pass Filter

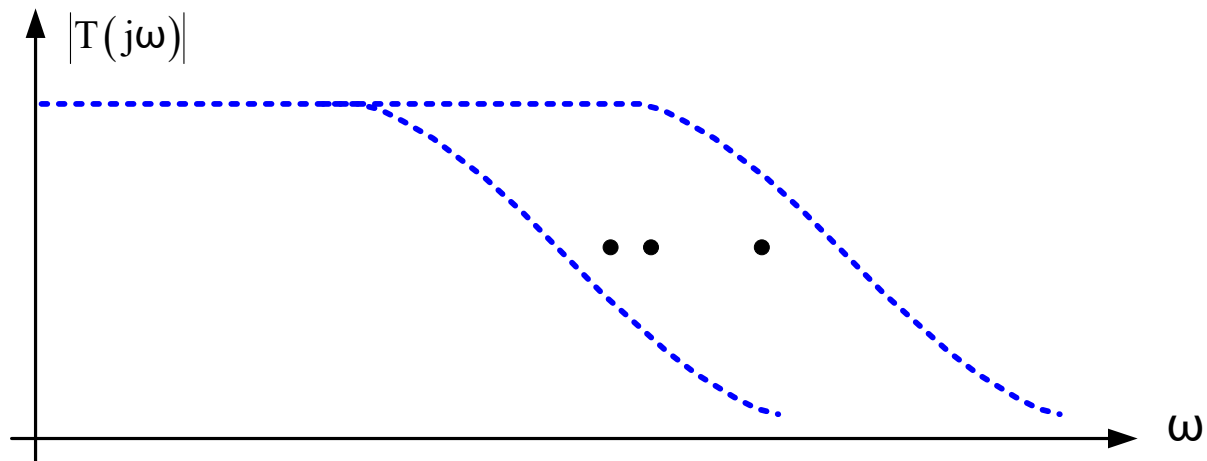

Voltage-controlled Filters

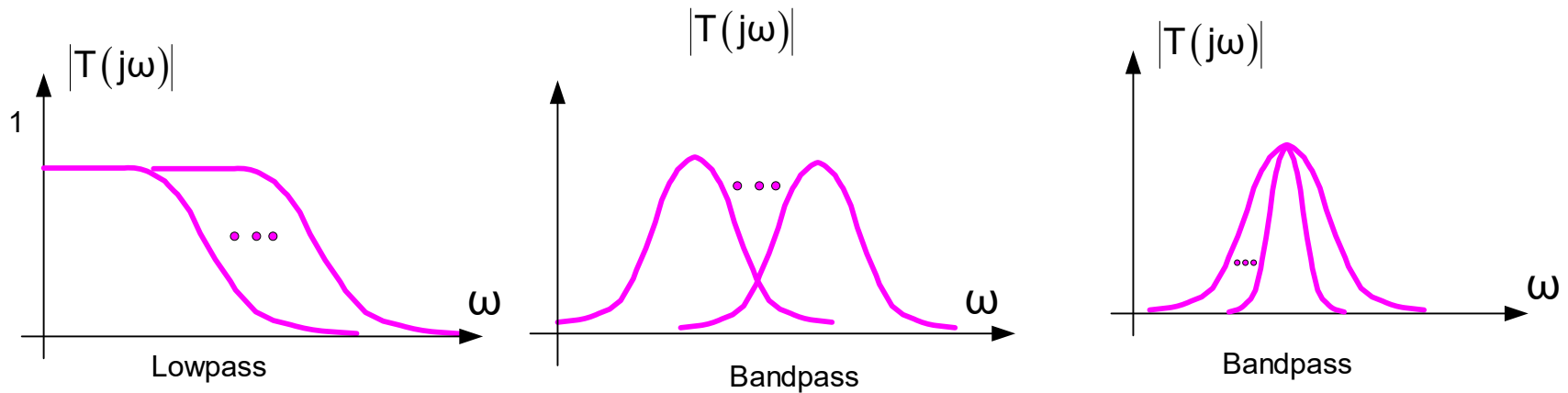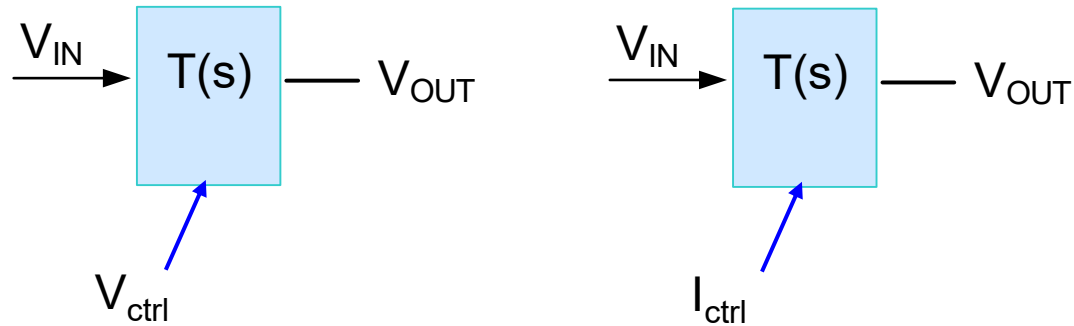


Filter characteristics can be controlled by an analog voltage (V_{CTRL}), an analog current (I_{CTRL}), or a Boolean signal

Much more controllability than with a potentiometer

Useful when microcontroller manages a signal path requiring filters

Programmable Filter Structures

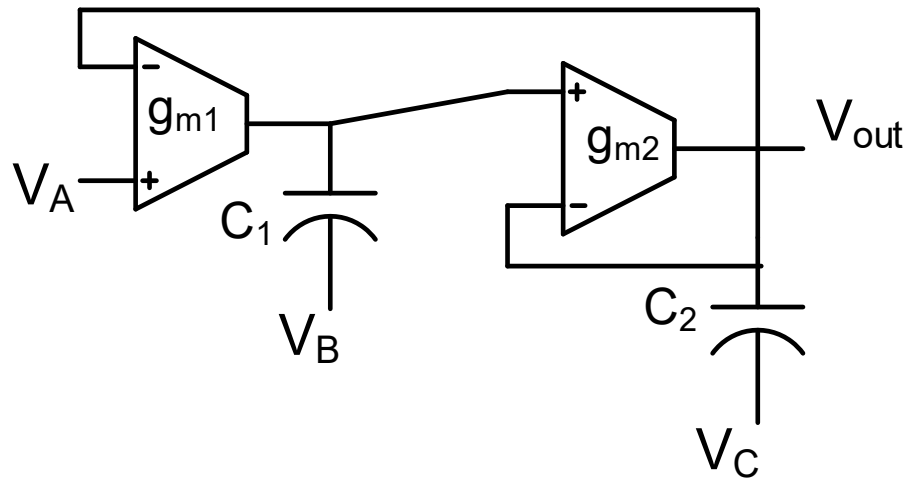It will be assumed that the transconductance gain can be programmed with either a dc current or a dc voltage




$$V_{OUT} = \frac{s^2 C_1 C_2 V_C + s C_1 g_{m2} V_B + g_{m1} g_{m2} V_A}{s^2 C_1 C_2 + s C_1 g_{m2} + g_{m1} g_{m2}}$$

Programmable Second-Order Filter

Programmable Filter Structures

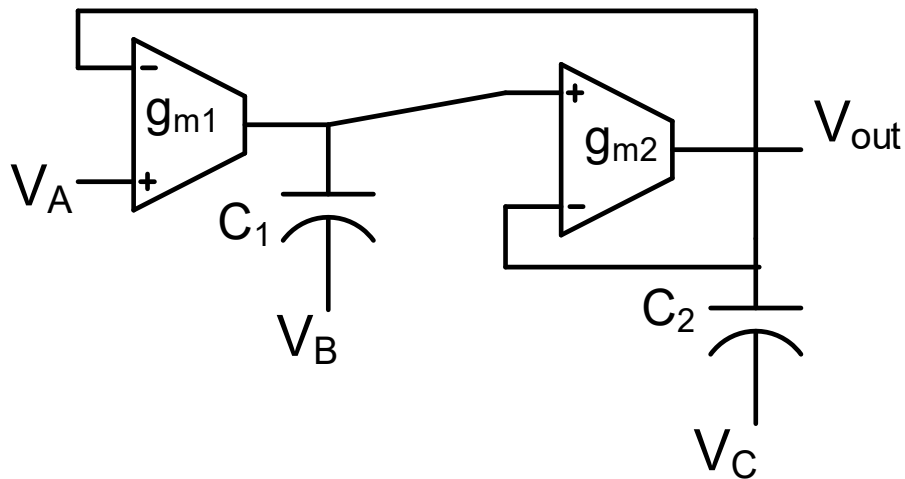It will be assumed that the transconductance gain can be programmed with either a dc current or a dc voltage



$$V_{\text{OUT}} = \frac{s^2 C_1 C_2 V_C + s C_1 g_{m2} V_B + g_{m1} g_{m2} V_A}{s^2 C_1 C_2 + s C_1 g_{m2} + g_{m1} g_{m2}}$$


Programmable Second-Order Filter

$$\omega_0 = \sqrt{\frac{g_{m1} g_{m2}}{C_1 C_2}}$$

$$Q = \sqrt{\frac{C_2}{C_1}} \sqrt{\frac{g_{m1}}{g_{m2}}}$$

Programmable Filter Structures

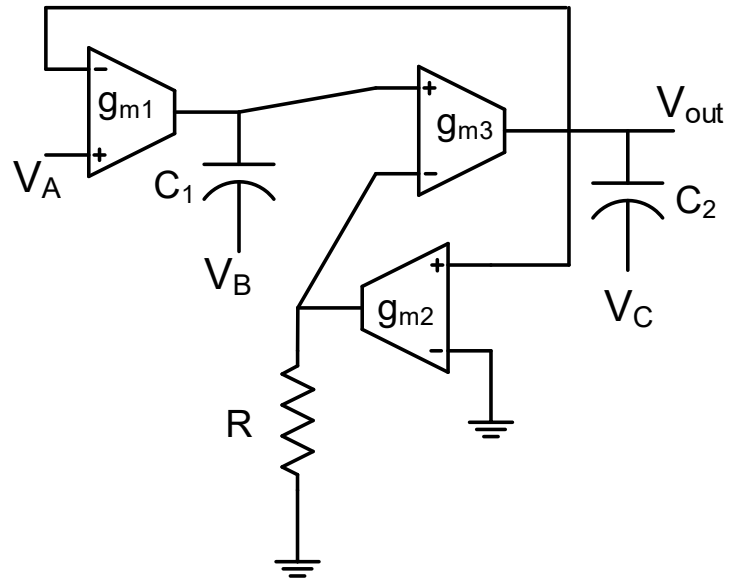It will be assumed that the transconductance gain can be programmed with either a dc current or a dc voltage



$$V_{OUT} = \frac{s^2 C_1 C_2 V_C + s C_1 g_{m2} V_B + g_{m1} g_{m2} V_A}{s^2 C_1 C_2 + s C_1 g_{m2} g_{m3} R + g_{m1} g_{m2}}$$


$$\omega_0 = \sqrt{\frac{g_{m1} g_{m2}}{C_1 C_2}}$$

$$Q = \frac{1}{g_{m3} R} \sqrt{\frac{C_2 g_{m1}}{C_1 g_{m2}}}$$

Programmable Second-Order Filter

Programmable Filter Structures

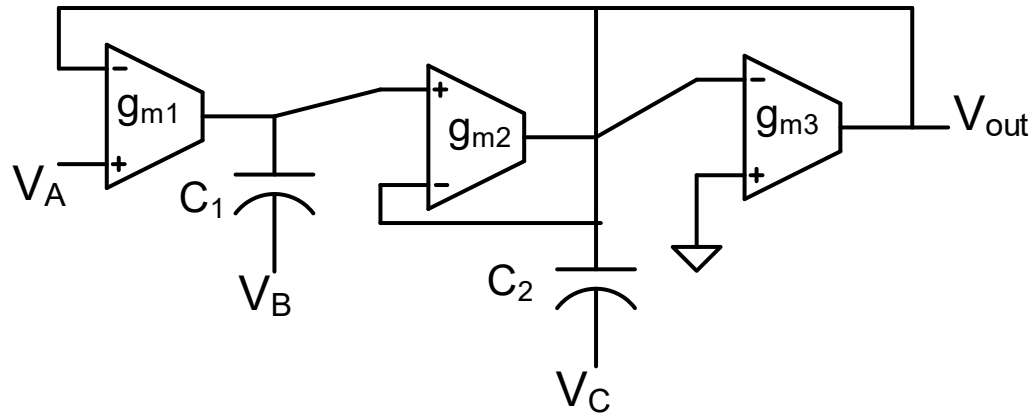It will be assumed that the transconductance gain can be programmed with either a dc current or a dc voltage



$$V_{\text{OUT}} = \frac{s^2 C_1 C_2 V_C + s C_1 g_{m2} V_B + g_{m1} g_{m2} V_A}{s^2 C_1 C_2 + s C_1 g_{m3} + g_{m1} g_{m2}}$$


$$\omega_0 = \sqrt{\frac{g_{m1} g_{m2}}{C_1 C_2}}$$

$$Q = \sqrt{\frac{C_2}{C_1}} \frac{\sqrt{g_{m1} g_{m2}}}{g_{m3}}$$

Programmable Second-Order Filter

Programmable Filter Structures

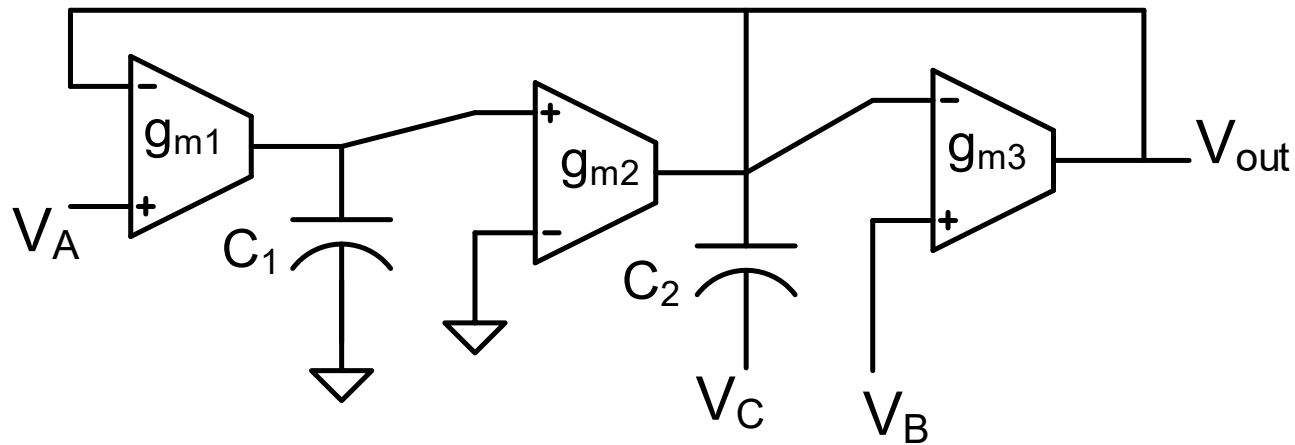It will be assumed that the transconductance gain can be programmed with either a dc current or a dc voltage




$$V_{OUT} = \frac{s^2 C_1 C_2 V_C + s C_1 g_{m3} V_B + g_{m1} g_{m2} V_A}{s^2 C_1 C_2 + s C_1 g_{m3} + g_{m1} g_{m2}}$$

$$\omega_0 = \sqrt{\frac{g_{m1} g_{m2}}{C_1 C_2}}$$
$$Q = \sqrt{\frac{C_2}{C_1}} \frac{\sqrt{g_{m1} g_{m2}}}{g_{m3}}$$

Programmable Second-Order Filter

Programmable Filter Structures

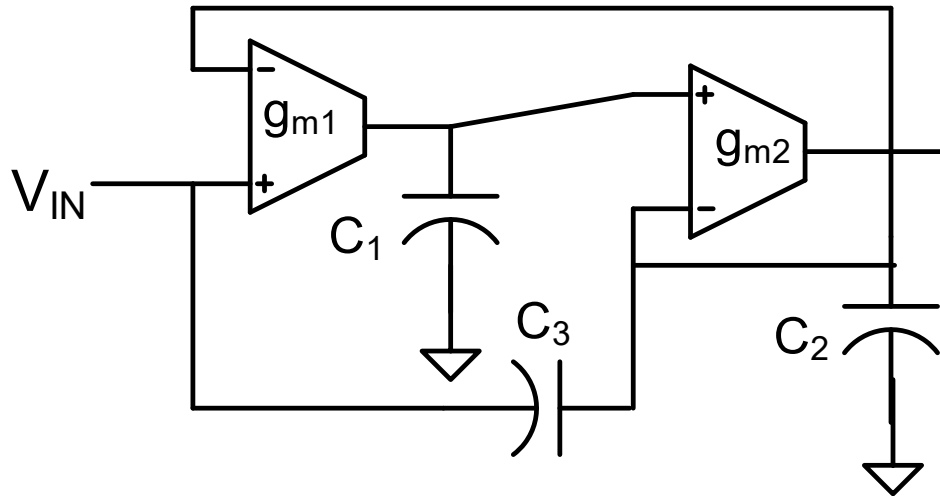It will be assumed that the transconductance gain can be programmed with either a dc current or a dc voltage



$$T(s) = \frac{C_2}{C_2 + C_3} \frac{s^2 C_1 C_2 + g_{m1} g_{m2}}{s^2 C_1 C_2 + s g_{m2} \frac{C_1 C_2}{C_2 + C_3} + g_{m1} g_{m2} \frac{C_2}{C_2 + C_3}}$$


$$\omega_0 = \sqrt{\frac{g_{m1} g_{m2}}{C_1 (C_2 + C_3)}}$$

$$Q = \sqrt{\frac{(C_2 + C_3)}{C_1}} \sqrt{\frac{g_{m1}}{g_{m2}}}$$


Programmable Notch Filter (Can be used as a programmable elliptic filter)

Programmable Filter Components

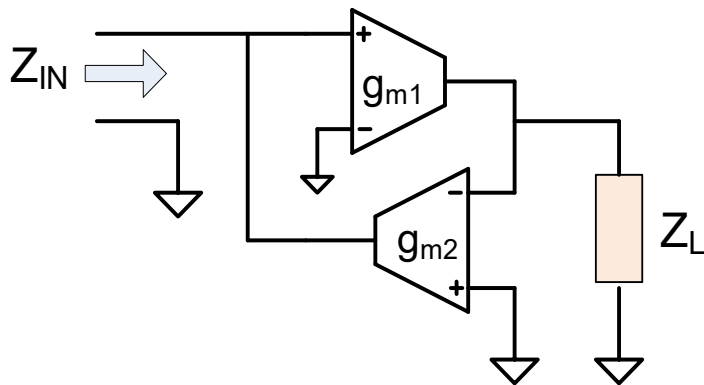It will be assumed that the transconductance gain can be programmed with either a dc current or a dc voltage



$$Z_{IN} = \frac{1}{g_{m1}g_{m2}Z_L}$$

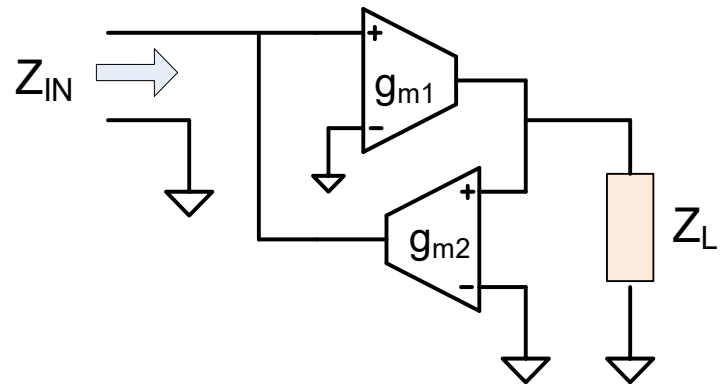



$$Z_{IN} = -\frac{1}{g_{m1}g_{m2}Z_L}$$

If Z_L is a capacitor serve as either positive or negative programmable inductors


Many other useful programmable filter components and filter structures possible

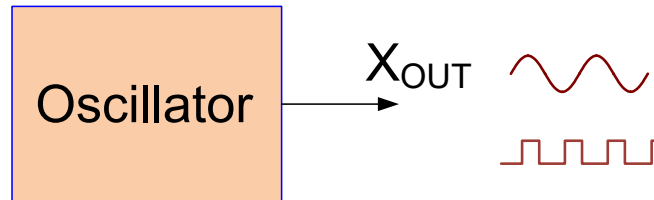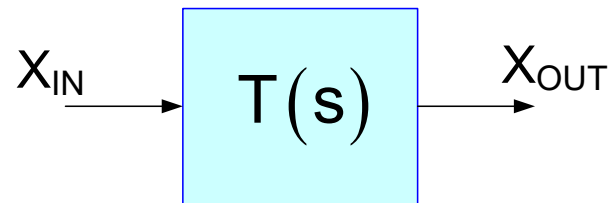Question:


What is the relationship, if any, between a filter and an oscillator or VCO?



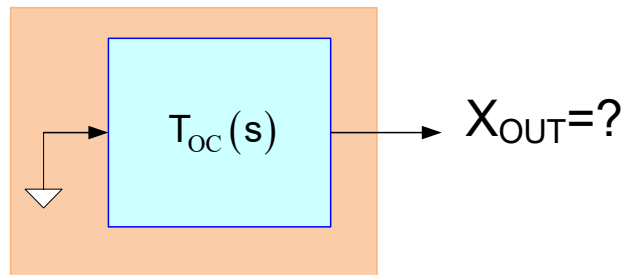i.e. Can an oscillator be viewed as a filter with no input?



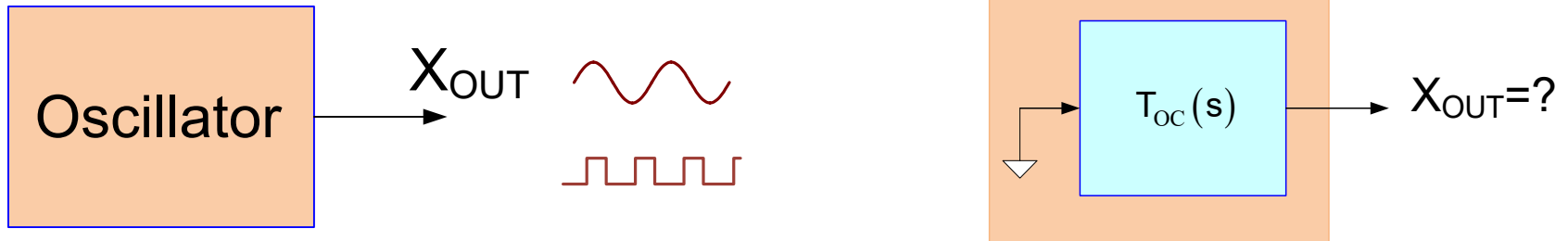What is the relationship, if any, between a filter and an oscillator or VCO?




Will focus on modifying oscillator structures to form high frequency narrow-band filters

Claim: Narrow band filters are dependent primarily on the poles close to the imaginary axis and affected little by poles that are farther away

Goal: Obtain very high frequency filter structures

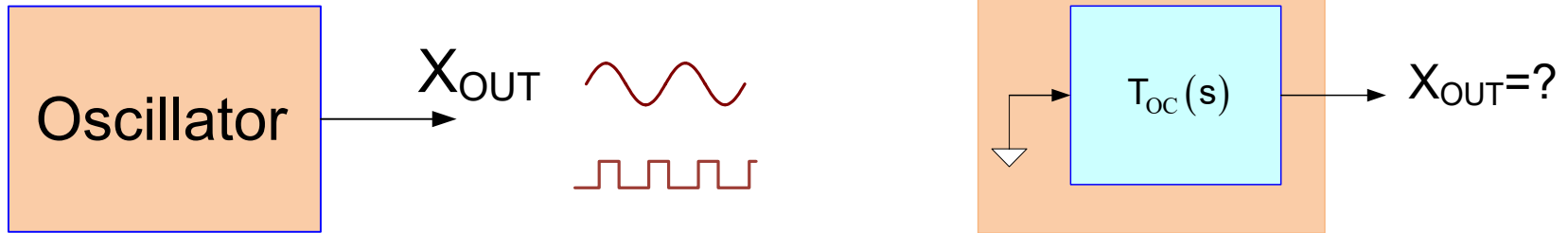What is the relationship, if any, between a filter and an oscillator or VCO?




- When power is applied to an oscillator, it initially behaves as a small-signal linear network
- When operating linearly, the oscillator has poles (but no zeros)
- Poles are ideally on the imaginary axis or appear as cc pairs in the RHP
- There is a wealth of literature on the design of oscillators
- Oscillators often are designed to operate at very high frequencies
- If cc poles of a filter are moved to RHP it will become an oscillator
- If RHP poles of an oscillator are moved to the LHP it will become a filter if an input is applied
- **Can oscillators be modified to become filters?**


Oscillator Background:

Consider a cascaded integrator loop comprised of n integrators

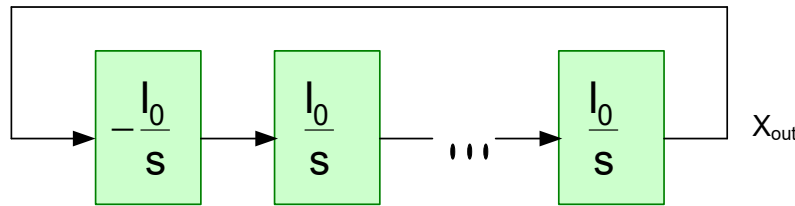This structure is often used to build oscillators



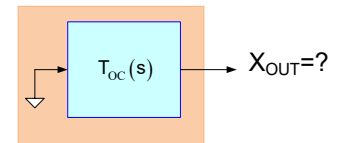(assume an odd number of inverting integrators)



$$X_{OUT} = -\left(\frac{I_0}{s}\right)^n X_{OUT}$$

$$X_{OUT} (s^n + I_0^n) = 0$$

$$D(s) = s^n + I_0^n$$

Consider the poles of $D(s) = s^n + I_0^n$

$$s^n + I_0^n = 0$$

$$s^n = -I_0^n$$



$$s = \left[-I_0^n \right]^{\frac{1}{n}}$$

$$s = \left[-1 \right]^{\frac{1}{n}} \left[I_0^n \right]^{\frac{1}{n}}$$

$$s = I_0 \left[-1 \right]^{\frac{1}{n}}$$





Poles are the n roots of -1 scaled by I_0

Roots of -1 :

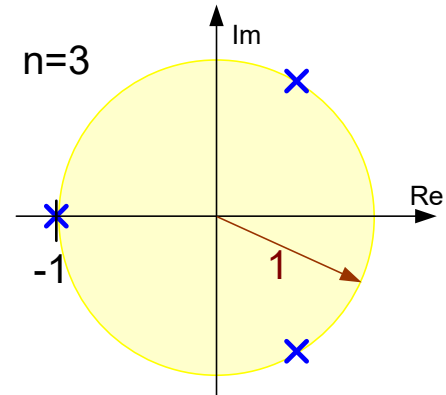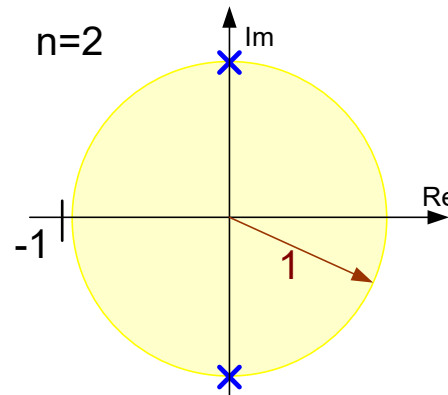


Roots are uniformly spaced on a unit circle

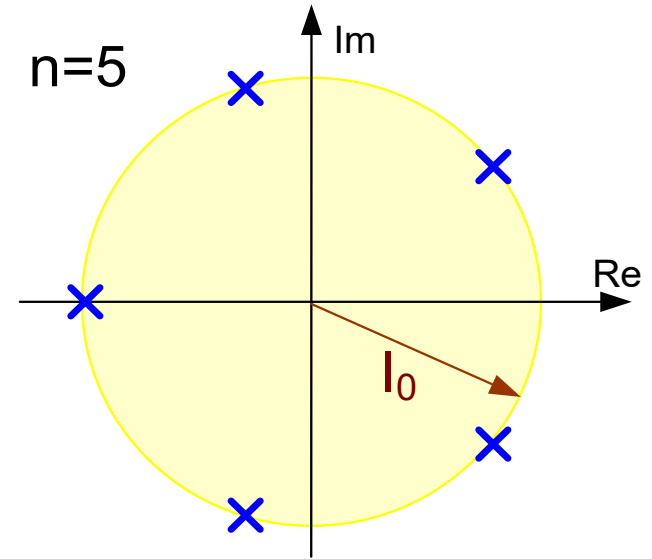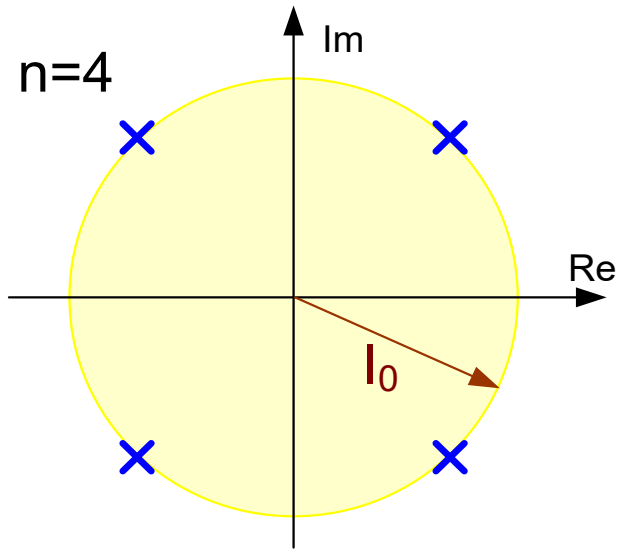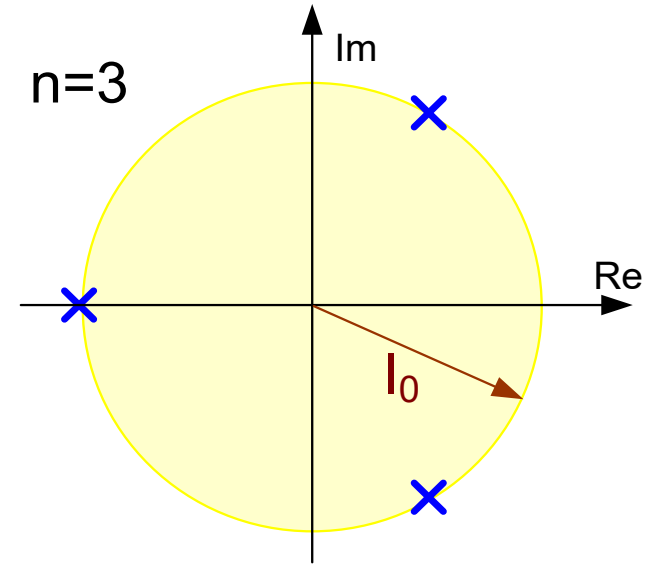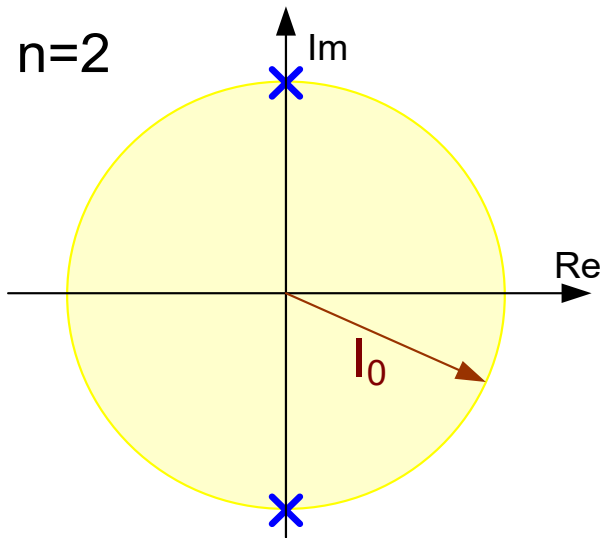
Consider the poles of $D(s) = s^n + I_0^n$




$n=6$

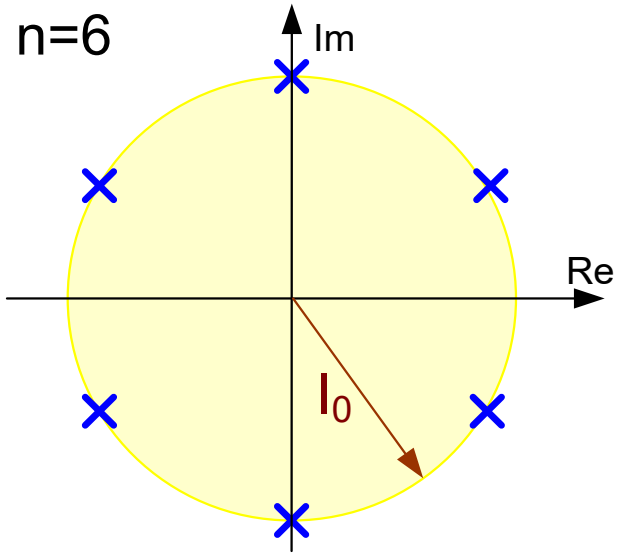

$n=7$

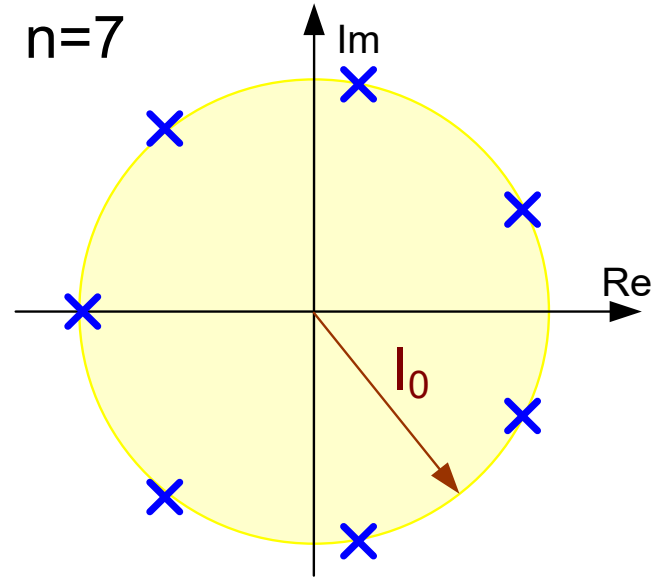

$n=8$

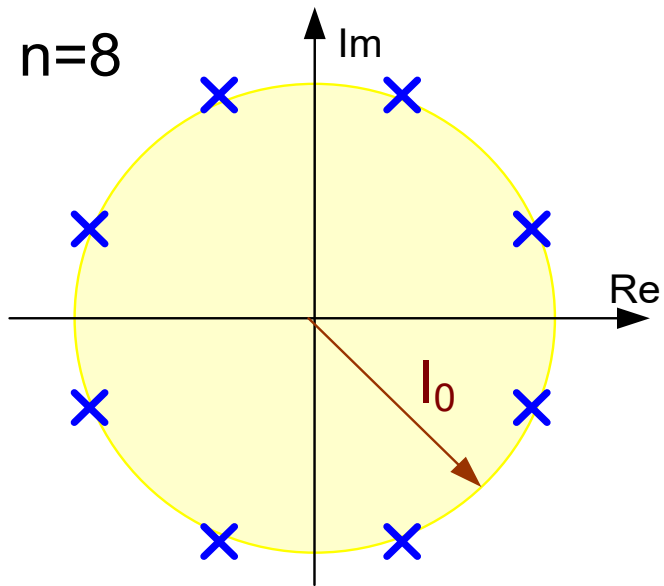

Some useful theorems

Theorem: A rational fraction $T(s) = \frac{N(s)}{\prod_{i=1}^n (s-p_i)}$ with simple poles can be expressed

in partial fraction form as $T(s) = \sum_{i=1}^n \frac{A_i}{s-p_i}$

where $A_i = (s-p_i)T(s)|_{s=p_i}$ for $1 \leq j \leq n$

Theorem: The impulse response of a rational fraction $T(s)$ with simple poles can be expressed as $r(t) = \sum_{i=1}^n A_i e^{p_i t}$ where the numbers A_i are the coefficients

in the partial fraction expansion of $T(s)$

Theorem: If p_i is a simple complex pole of the rational fraction $T(s)$, then the partial fraction expansion terms in the impulse response corresponding to p_i and p_i^* can be expressed as $\frac{A_i}{s-p_i} + \frac{A_i^*}{s-p_i^*}$

Theorem: If $p_i = \alpha_i + j\beta_i$ is a simple pole with non-zero imaginary part of the rational fraction $T(s)$, then the impulse response terms corresponding to the poles p_i and p_i^* in the partial fraction expansion can be expressed as

$$|A_i| e^{\alpha_i t} \cos(\beta_i t + \theta_i)$$

where θ_i is the angle of the complex quantity A_i

Observe $r(t)$ term corresponding to any complex pole pair is real !

Theorem: If all poles of an n-th order rational fraction T(s) are simple and have a non-zero Imaginary part, then the impulse response can be expressed as

$$\sum_{i=1}^{n/2} |A_i| e^{\alpha_i t} \cos(\beta_i t + \theta_i)$$

where θ_i , A_i , α_i , and β_i are as defined before

Theorem: If an odd-order rational fraction has one pole on the negative real axis at α_0 and n simple poles that have a non-zero Imaginary part, then the impulse response can be expressed as

$$A_0 e^{\alpha_0 t} + \sum_{i=1}^{n/2} |A_i| e^{\alpha_i t} \cos(\beta_i t + \theta_i)$$


where θ_i , A_i , α_i , and β_i are as defined before

Observe r(t) is real for both even and odd n !

Consider the following 3-pole situation

Poles of $D(s) = s^n + I_0^n$

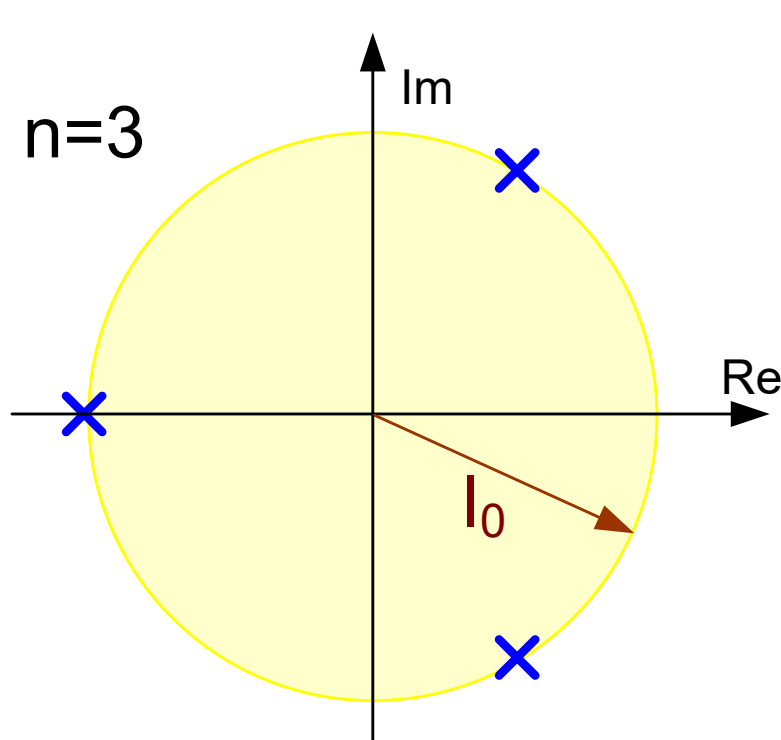0.5 -0.866025404
 0.5 0.866025404
 -1 3.67545E-16



$\theta = 60^\circ$
 $\alpha = I_0 \cos(60^\circ)$
 $\beta = I_0 \sin(60^\circ)$

for cc pole pair:

$\alpha = 0.5 I_0$

$\beta = 0.866 I_0$

Oscillatory output at startup with any small impulse input $\varepsilon \delta(t)$:

$\varepsilon \bullet |A_i| e^{\alpha_i t} \cos(\beta_i t + \theta_i)$

Starts at $\omega = \beta = 0.866 I_0$ and will slow down as nonlinearities limit amplitude

Consider the following 3-pole situation


Poles of $D(s) = s^n + I_0^n$

Consider moving all poles to left by $\Delta\alpha$

$$\beta = 0.866 I_0$$

$$\alpha = 0.5 I_0 - \Delta\alpha$$

$$\omega_0 = \sqrt{\alpha^2 + \beta^2}$$

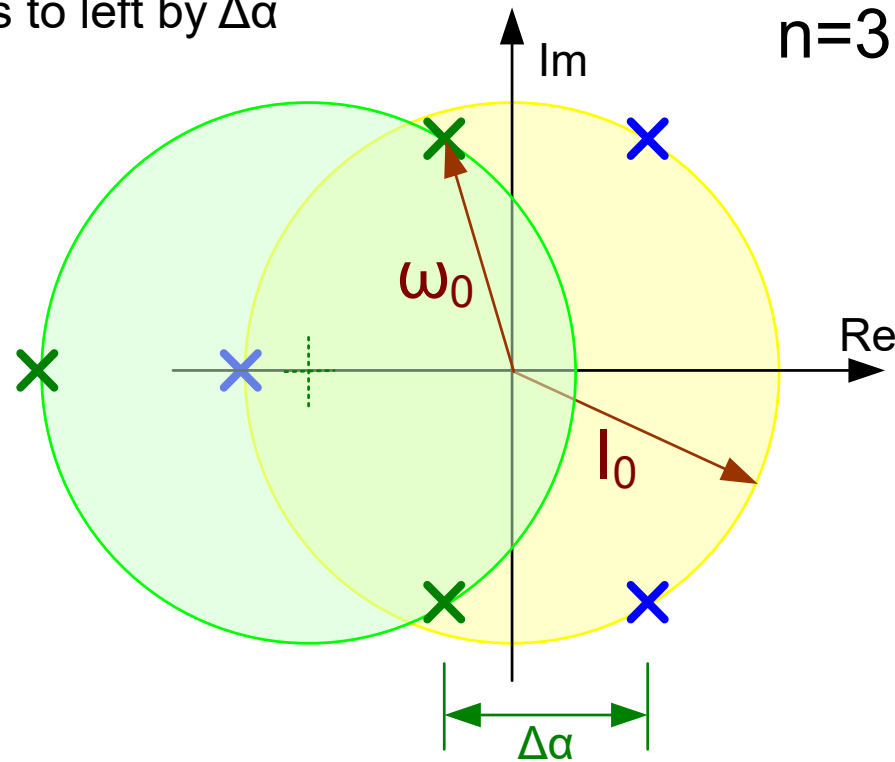

So since α is fixed, to get a high ω_0 , want β as large as possible



Stay Safe and Stay Healthy !

End of Lecture 36

Consider now the filter obtained by adding a loss of α_L to the integrators

Will now determine α_L and I_0 needed to get a desired pole Q and ω_0 by moving all poles so that right-most pole pair is the dominant high-frequency pole pair of the filter

The values of α and β are dependent upon I_0 but the angle θ is only dependent upon the number of integrators in the oscillator or VCO


$$\alpha + j\beta = I_0 (\cos\theta + j\sin\theta)$$

Define the location of the filter pole to be

$$\alpha_F + j\beta_F$$

It follows that
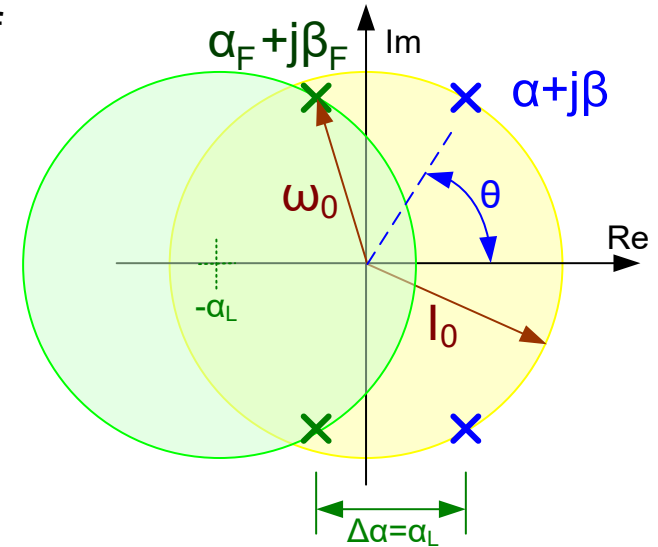
$$\beta_F = \beta \quad \alpha_F = \alpha - \alpha_L$$



The relationship between the filter parameters is well known

$$\beta_F = \frac{\omega_0}{2Q} \sqrt{4Q^2 - 1}$$


$$\alpha_F = -\frac{\omega_0}{2Q}$$

Thus for any n ↓

$$I_0 = \frac{\omega_0}{(\sin\theta)2Q} \sqrt{4Q^2 - 1}$$

$$\alpha_L = \frac{\omega_0}{2Q} + I_0 \cos\theta = \frac{\omega_0}{2Q} + \frac{\omega_0}{2Q(\tan\theta)} \sqrt{4Q^2 - 1}$$

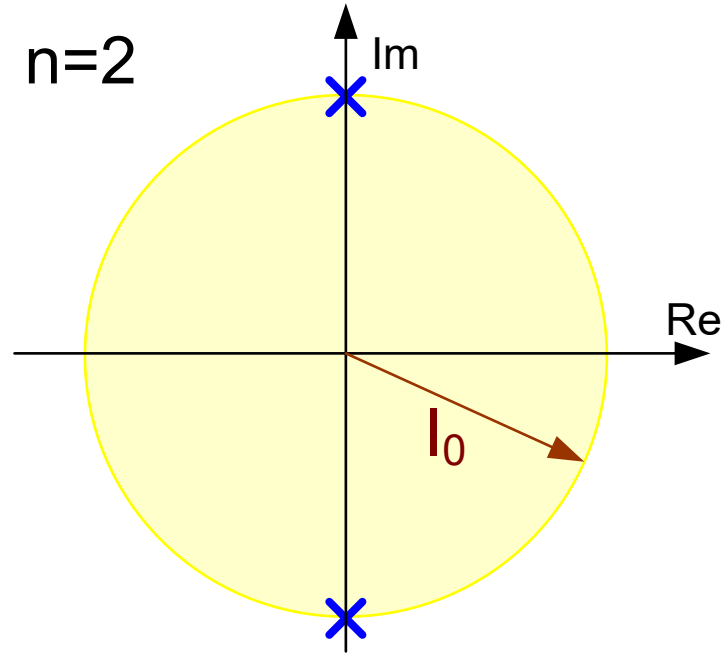Will a two-stage structure give the highest frequency of operation for integrators with unity gain frequency I_0 ?




$$\omega_0 = \sqrt{(\alpha - \Delta\alpha)^2 + \beta^2} \quad \longrightarrow \quad \omega_0 = \sqrt{(-\Delta\alpha)^2 + \beta^2}$$

- Even though the two-stage structure may not oscillate, can work as a filter!
- Need odd number of inversions in integrators
- Can add phase lead if necessary

Oscillator Background:

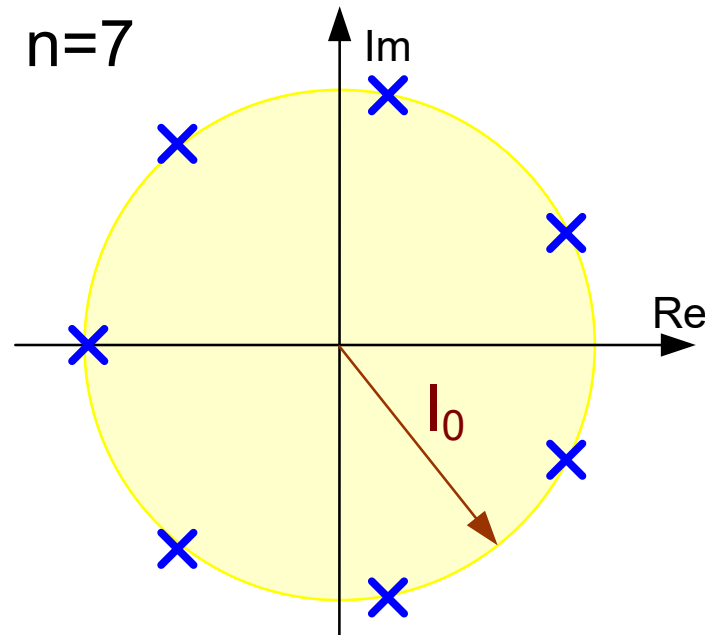What will happen with a circuit that has two pole-pairs in the RHP?




General form of response for odd number of poles:

$$A_0 e^{\alpha_0 t} + \sum_{i=1}^{n/2} |A_i| e^{\alpha_i t} \cos(\beta_i t + \theta_i)$$

The impulse response (for $n=7$) will have two decaying exponential terms and two growing exponential terms

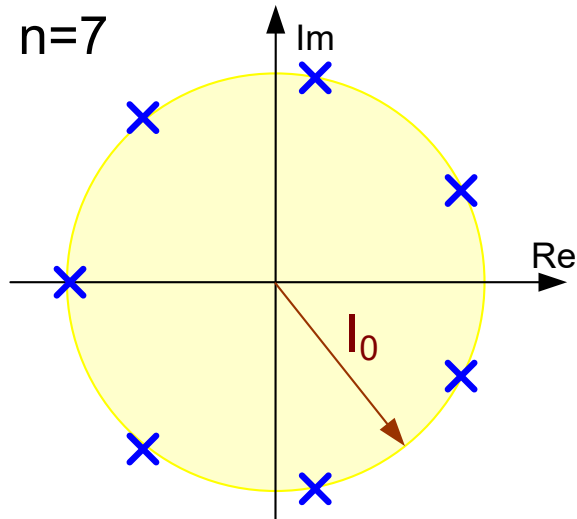What will happen with a circuit that has two pole-pairs in the RHP?



-0.62349	-0.781831482
0.222521	-0.974927912
0.900969	-0.433883739
0.900969	0.433883739
0.222521	0.974927912
-0.62349	0.781831482
-1	3.67545E-16

$$\alpha_1=0.2225 \quad \beta_1=0.974$$

$$\alpha_2=0.9009 \quad \beta_2=0.4338$$

Consider the growing exponential terms and normalize to $I_0=1$



$$|A_1| e^{\alpha_1 t} \cos(\beta_1 t + \theta_1) + |A_2| e^{\alpha_2 t} \cos(\beta_2 t + \theta_2)$$

At $t=145$ (after only 10 periods of the lower frequency signal)

$$r = \frac{e^{\alpha_2 t}}{e^{\alpha_1 t}} \Big|_{t=145} = \frac{e^{.9009 \cdot 145}}{e^{.2225 \cdot 145}} = 5.2 \times 10^{42}$$

The lower frequency oscillation will completely dominate !

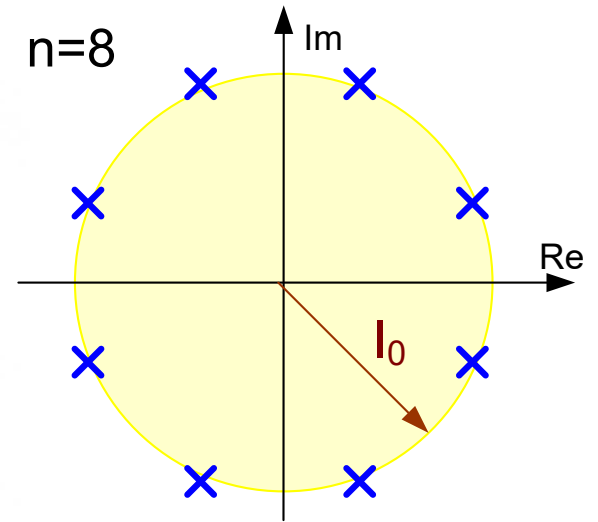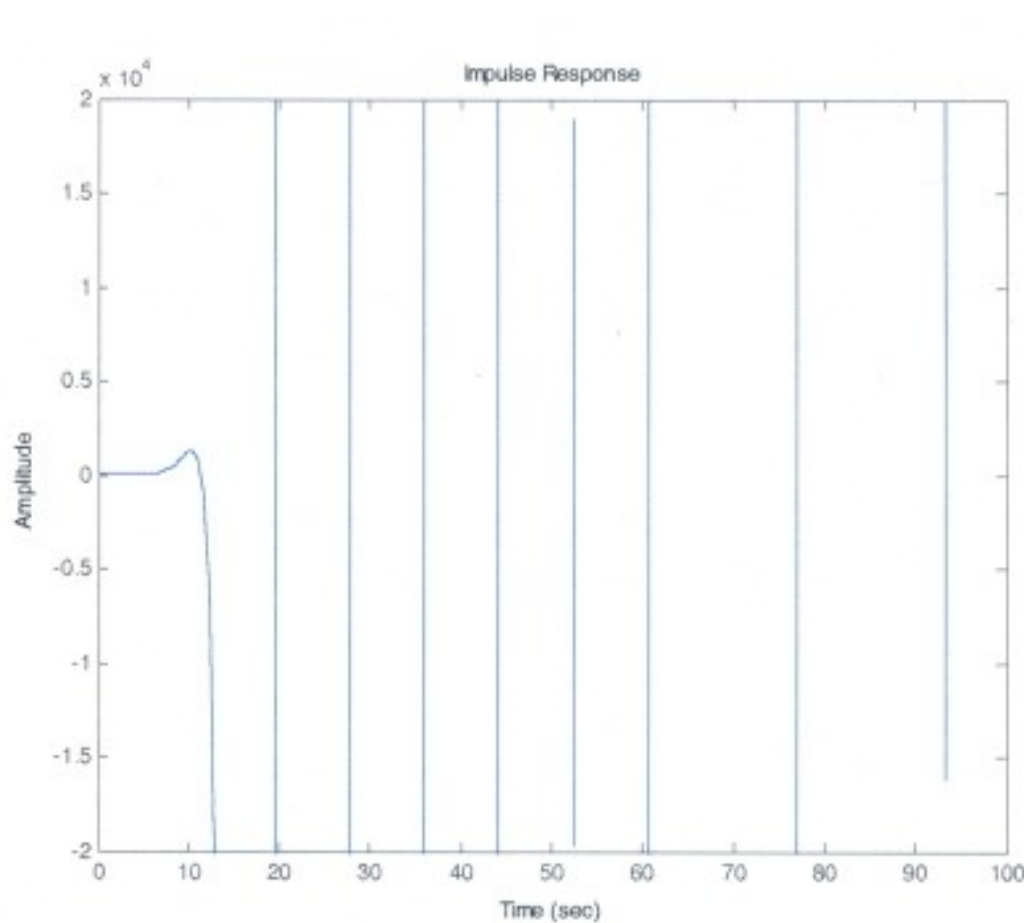What will happen with a circuit that has two pole-pairs in the RHP?



Thanks to Chen for these plots

Figure 14 N=8 impulse response

Can only see the lower frequency component !

What will happen with a circuit that has two pole-pairs in the RHP?

Thanks to Chen for these plots

image1.jpg
Type: JPEG Image
Size: 2.71 MB
Dimension: 5008 x 6608 pixels

$-0.9239i$

$0.9239 + 0.3827i$


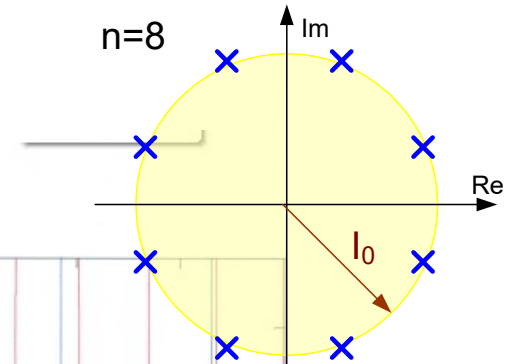
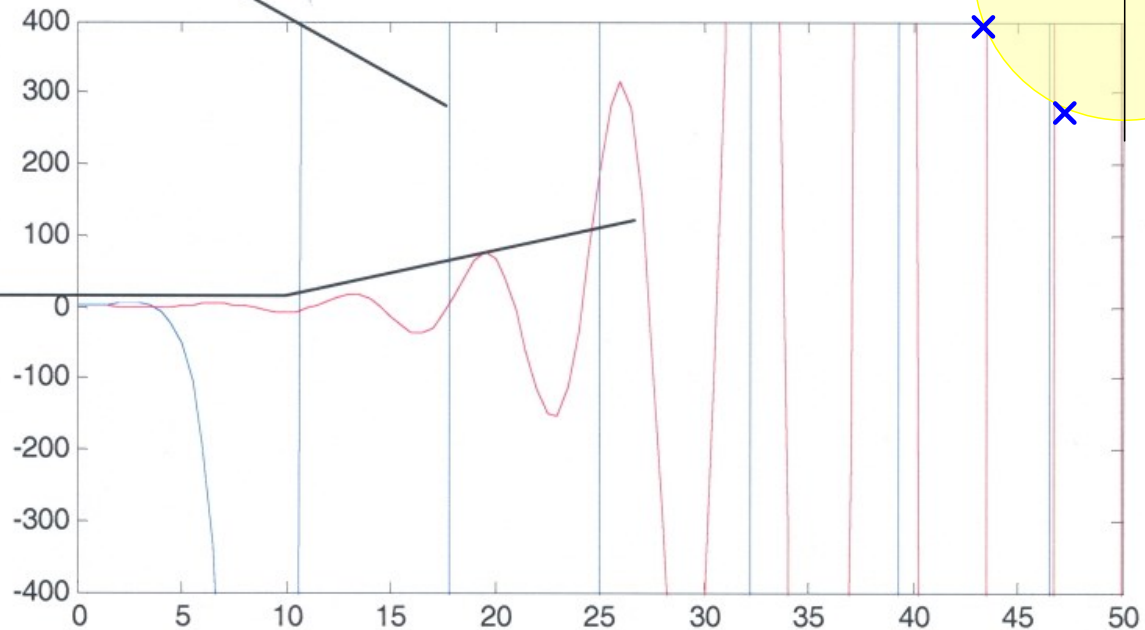


Figure 7 N=8 the impulse response of two poles

After even only two periods of the lower frequency waveform, it completely dominates !

How do we guarantee that we have a net coefficient of +1 in $D(s)$?

$$D(s) = s^n + I_0^n$$

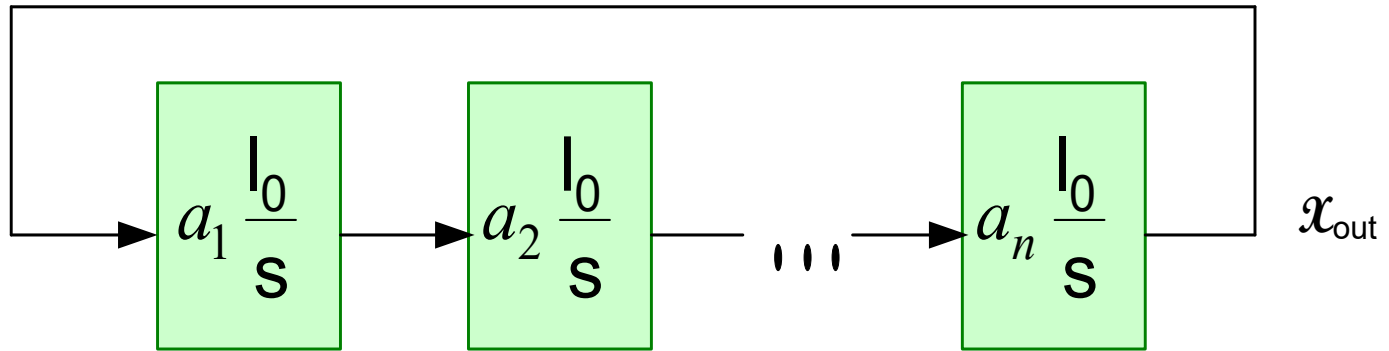

$$x_{out} = \left(\prod_{i=1}^n a_i \left(\frac{I_0}{s} \right) \right) x_{out} \quad a_i \in \{-1, 1\}$$


$$D(s) = s^n - \left(\prod_{i=1}^n a_i \right) I_0^n \quad \longrightarrow \quad \prod_{i=1}^n a_i = -1$$

Must have an odd number of inversions in the loop !

If n is odd, all stages can be inverting and identical !

How do we guarantee that we have a net coefficient of +1 in $D(s)$?

$$D(s) = s^n + I_0^n$$

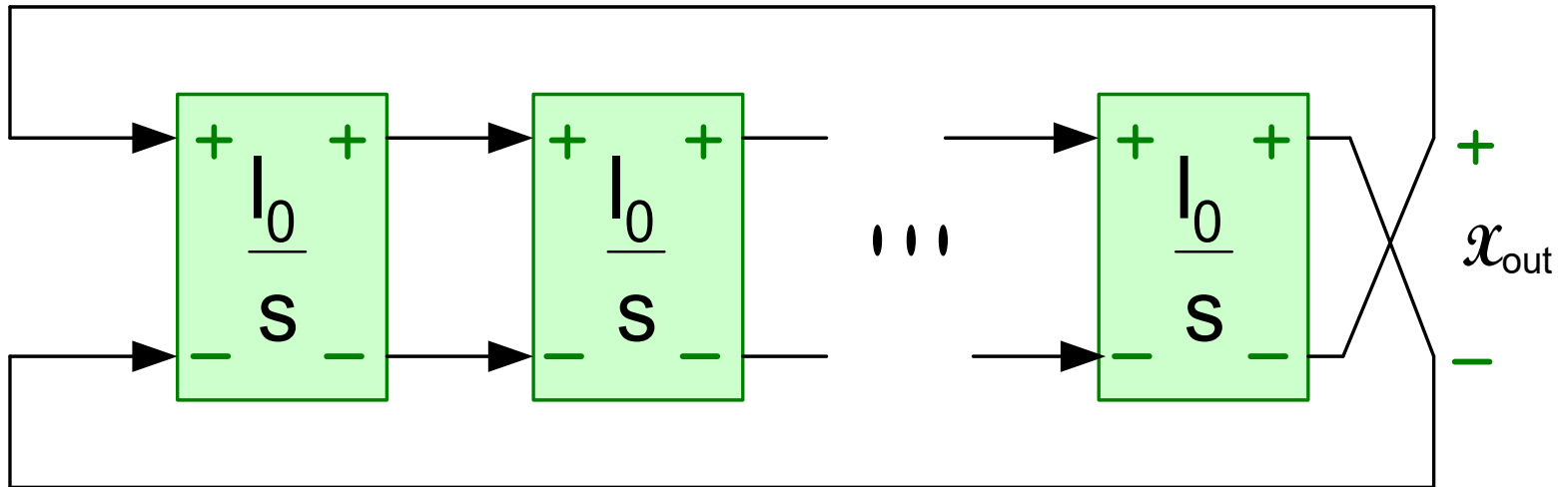



If fully differential or fully balanced, must have an odd number of crossings of outputs

Applicable for both even and odd order loops


Inputs to Oscillator-Derived Filters:

Most applicable to designing 2nd-order high frequency narrow band bandpass filters

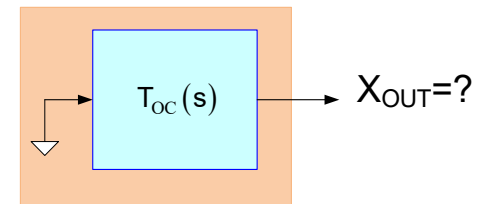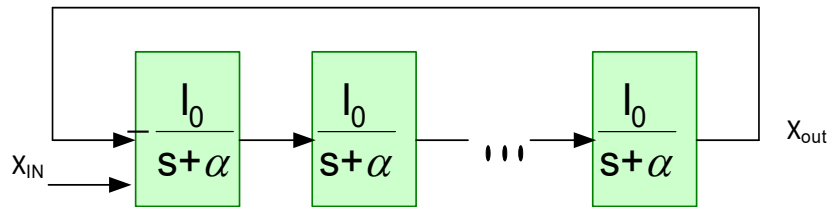- Add loss to delay stages
- Multiple Input Locations Often Possible
- Natural Input is Input to delay stage



A lossy integrator stage

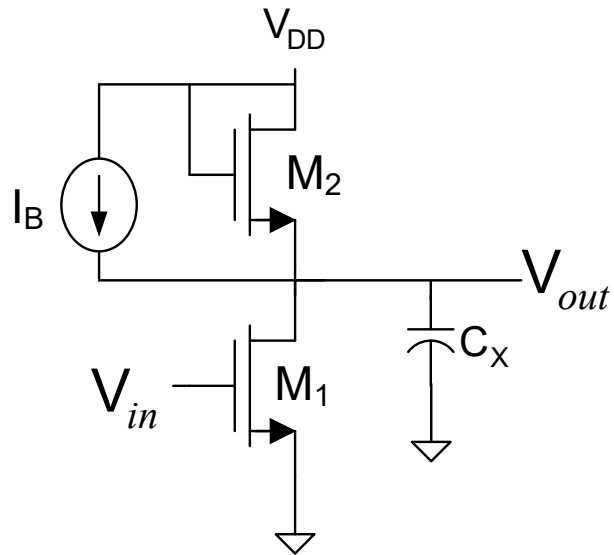


$$I(s) = \frac{-g_{m1}/C_X}{s + g_{m2}/C_X}$$

$$I_0 = g_{m1}/C_X$$

$$\alpha_L = g_{m2}/C_X$$

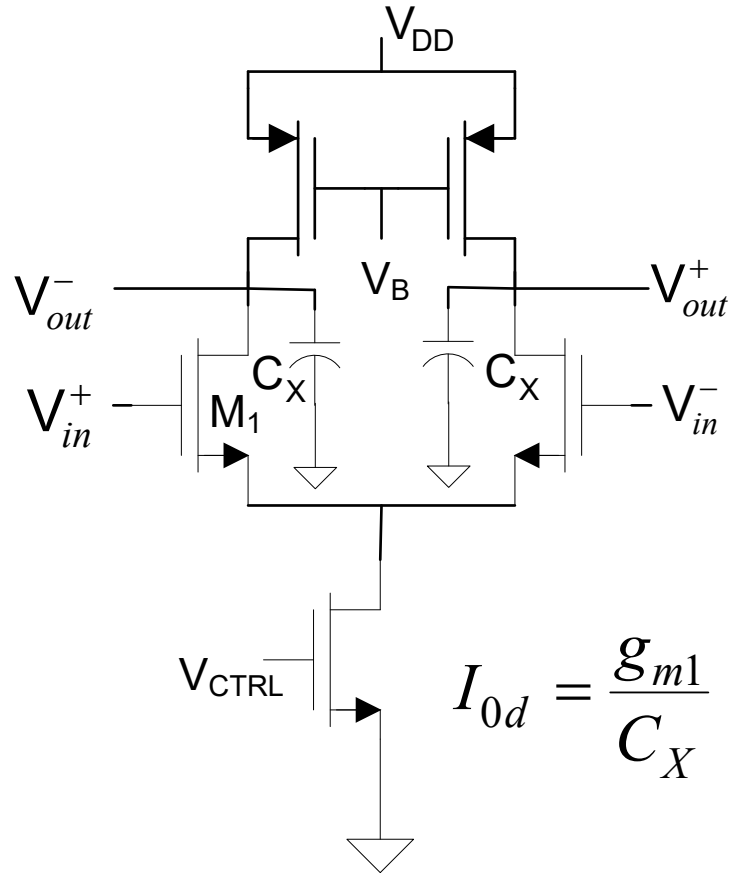A fully-differential voltage-controlled integrator stage



Will need CMFB circuit

Example:

Using the single-stage lossy integrator, design the integrator to meet a given ω_0 and Q requirement

Recall:


$$I_0 = \frac{\omega_0}{(\sin\theta)2Q} \sqrt{4Q^2 - 1} \quad (1)$$

$$\alpha_L = \frac{\omega_0}{2Q} + \frac{\omega_0}{2Q(\tan\theta)} \sqrt{4Q^2 - 1} \quad (2)$$

Substituting for I_0 and α_L we obtain:

$$\frac{g_{m1}}{C_X} = \frac{\omega_0}{(\sin\theta)2Q} \sqrt{4Q^2 - 1} \quad (3)$$
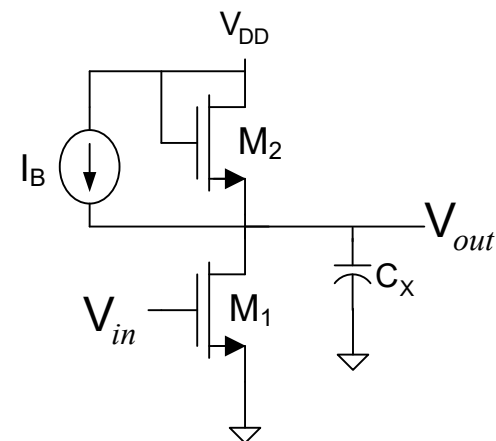
$$\frac{g_{m2}}{C_X} = \frac{\omega_0}{2Q} + \frac{\omega_0}{2Q(\tan\theta)} \sqrt{4Q^2 - 1} \quad (4)$$



$$V_{OUT}(sC_X + g_{m2}) + g_{m1} V_{IN} = 0$$

$$\frac{V_{OUT}}{V_{IN}} = - \frac{g_{m1}}{sC_X + g_{m2}}$$

$$I_0 = g_{m1}/C_X$$

$$\alpha_L = g_{m2}/C_X$$

Unknowns: $I_B, V_{EB1}, W_1/L_1, W_2/L_2, C_X$

Example:

Using the single-stage lossy integrator, design the integrator to meet a given ω_0 and Q requirement

Expressing g_{m1} and g_{m2} in terms of design parameters:

$$\frac{\mu C_{OX} W_1 V_{EB1}}{L_1 C_X} = \frac{\omega_0}{(\sin\theta) 2Q} \sqrt{4Q^2 - 1} \quad (5)$$

$$\frac{\mu C_{OX} W_2 V_{EB2}}{L_2 C_X} = \frac{\omega_0}{2Q} + \frac{\omega_0}{2Q(\tan\theta)} \sqrt{4Q^2 - 1} \quad (6)$$


If we assume $I_B=0$, equating drain currents obtain:

$$V_{EB2} = V_{EB1} \sqrt{\frac{W_1 L_2}{W_2 L_1}} \quad (7)$$

Thus the previous two expressions can be rewritten as :

$$\frac{\mu C_{OX} V_{EB1}}{C_X} \left[\frac{W_1}{L_1} \right] = \frac{\omega_0}{(\sin\theta) 2Q} \sqrt{4Q^2 - 1} \quad (8)$$
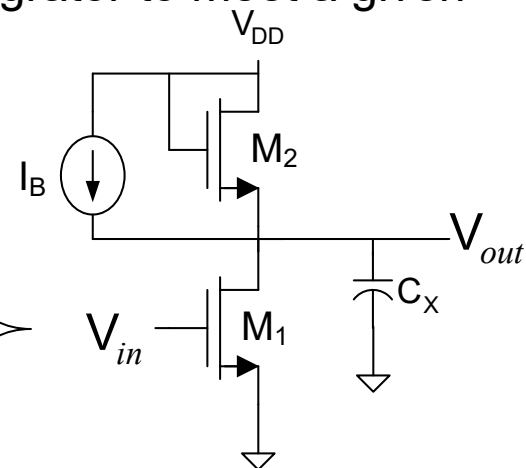
$$\frac{\mu C_{OX} V_{EB1}}{C_X} \left[\frac{W_1 W_2}{L_1 L_2} \right] = \frac{\omega_0}{2Q} + \frac{\omega_0}{2Q(\tan\theta)} \sqrt{4Q^2 - 1} \quad (9)$$



$$I_0 = g_{m1}/C_X$$

$$\alpha_L = g_{m2}/C_X$$

Example:


Using the single-stage lossy integrator, design the integrator to meet a given ω_0 and Q requirement

$$\frac{\mu C_{OX} V_{EB1}}{C_X} \left[\frac{W_1}{L_1} \right] = \frac{\omega_0}{(\sin\theta) 2Q} \sqrt{4Q^2 - 1}$$

$$\frac{\mu C_{OX} V_{EB1}}{C_X} \left[\frac{W_1 W_2}{L_1 L_2} \right] = \frac{\omega_0}{2Q} + \frac{\omega_0}{2Q(\tan\theta)} \sqrt{4Q^2 - 1}$$

Taking the ratio of these two equations we obtain:
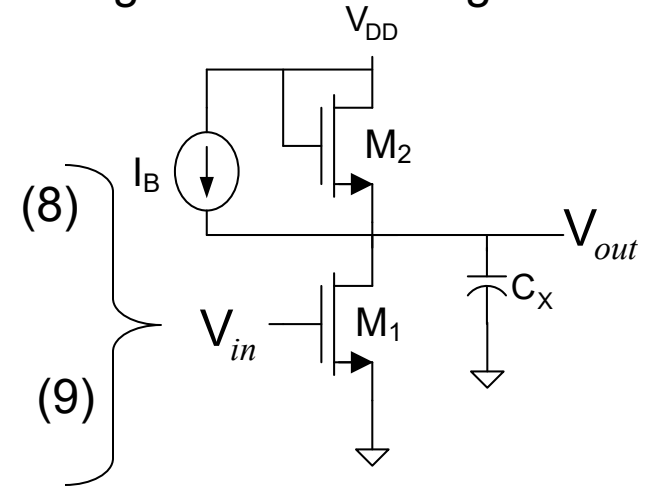
$$\frac{W_2}{L_2} = \frac{\sin\theta + \cos\theta \sqrt{4Q^2 - 1}}{\sqrt{4Q^2 - 1}} \quad (10)$$



$$I_0 = g_{m1}/C_X$$

$$\alpha_L = g_{m2}/C_X$$


Observe that the pole Q is determined by the dimensions of the lossy device !

Example:

Using the single-stage lossy integrator, design the integrator to meet a given ω_0 and Q requirement

$$\frac{\mu C_{OX} V_{EB1}}{C_X} \left[\frac{W_1}{L_1} \right] = \frac{\omega_0}{(\sin\theta) 2Q} \sqrt{4Q^2 - 1} \quad (8)$$
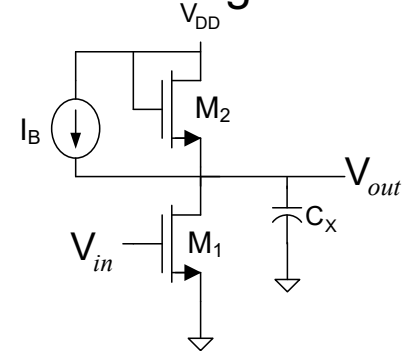
$$\frac{W_2}{L_2} = \frac{\sin\theta + \cos\theta \sqrt{4Q^2 - 1}}{\sqrt{4Q^2 - 1}} \quad (10)$$



Still must obtain W_1/L_1 , V_{EB1} , and C_X from either of these equations

Although it appears that there might be 3 degrees of freedom left and only one constraint (one of these equations), if these integrators are connected in a loop, the operating point (Q-point) will be the same for all stages and will be that value where $V_{out} = V_{in}$. So, this adds a second constraint.

Setting $V_{out} = V_{in}$, and assuming $V_{T1} = V_{T2}$, we obtain from KVL

$$V_{DD} = V_{EB1} + V_{EB2} + 2V_T \quad (11)$$


But V_{EB1} and V_{EB2} are also related in (7)

Example:

Using the single-stage lossy integrator, design the integrator to meet a given ω_0 and Q requirement

$$\frac{\mu C_{OX} V_{EB1}}{C_X} \left[\frac{W_1}{L_1} \right] = \frac{\omega_0}{(\sin\theta) 2Q} \sqrt{4Q^2 - 1} \quad (8)$$
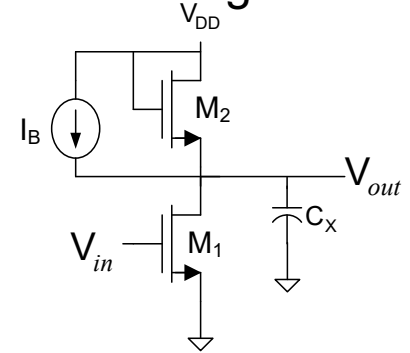
$$\frac{W_2}{L_2} = \frac{\sin\theta + \cos\theta \sqrt{4Q^2 - 1}}{\sqrt{4Q^2 - 1}} \quad (10)$$



Still must obtain W_1/L_1 , V_{EB1} , and C_X from either of these equations

$$V_{DD} = V_{EB1} + V_{EB2} + 2V_T \quad (11)$$

$$V_{EB2} = V_{EB1} \sqrt{\frac{W_1 L_2}{W_2 L_1}} \quad (7)$$

$$V_{EB1} = \frac{V_{DD} - 2V_T}{1 + \sqrt{\frac{W_2 L_1}{W_1 L_2}}} \quad (12)$$

Substituting (10) into (12) and then into (8) we obtain


$$\frac{\mu C_{OX}}{C_X} \left[\frac{W_1}{L_1} \right] \left(\frac{V_{DD} - 2V_T}{1 + \sqrt{\left(\frac{W_1}{L_1} \right)^{-1} \left(\frac{\sin\theta + \cos\theta \sqrt{4Q^2 - 1}}{\sqrt{4Q^2 - 1}} \right)}} \right) = \frac{\omega_0}{(\sin\theta) 2Q} \sqrt{4Q^2 - 1} \quad (13)$$

Example:

Using the single-stage lossy integrator, design the integrator to meet a given ω_0 and Q requirement

$$\frac{W_2}{L_2} = \frac{\sin\theta + \cos\theta\sqrt{4Q^2-1}}{\sqrt{4Q^2-1}}$$
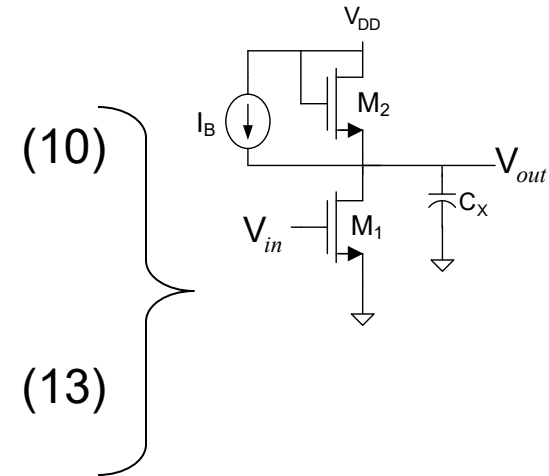
$$\frac{\mu C_{OX}}{C_X} \left[\frac{W_1}{L_1} \right] \left(\frac{V_{DD} - 2V_T}{1 + \sqrt{\left(\frac{W_1}{L_1}\right)^{-1} \left(\frac{\sin\theta + \cos\theta\sqrt{4Q^2-1}}{\sqrt{4Q^2-1}} \right)}} \right) = \frac{\omega_0}{(\sin\theta)2Q} \sqrt{4Q^2-1}$$



There is still one degree of freedom remaining. Can either pick W_1/L_1 and solve for C_X or pick C_X and solve for W_1/L_1 .

Explicit expression for W_1/L_1 not available

Tradeoffs between C_X and W_1/L_1 will often be made

Since $V_{OUTQ} = V_T + V_{EB1}$, it may be preferred to pick V_{EB1} , then solve (12) for W_1/L_1 and then solve (13) for C_X

Adding I_B will provide one additional degree of freedom (we arbitrarily set it to 0 in this analysis) and will relax the relationship between V_{OUTQ} and W_1/L_1 since (7) will be modified



Stay Safe and Stay Healthy !

End of Lecture 36