

# EE 508


## Lecture 37

### Oscillator/VCO-Derived Filters

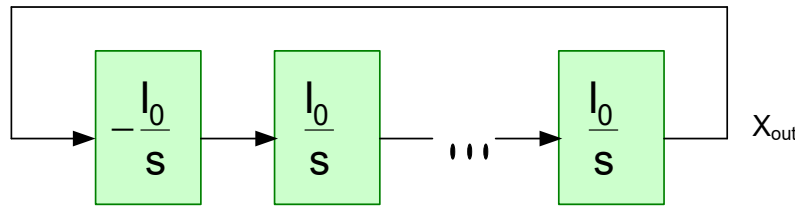
# Oscillator Background:

Consider a cascaded integrator loop comprised of  $n$  integrators

This structure is often used to build oscillators



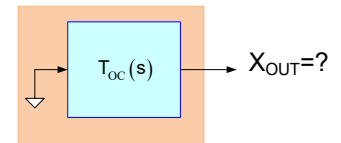(assume an odd number of inverting integrators)



$$X_{OUT} = -\left(\frac{I_0}{s}\right)^n X_{OUT}$$

$$X_{OUT} (s^n + I_0^n) = 0$$

$$D(s) = s^n + I_0^n$$

Review from last lecture:

# Consider the following 3-pole situation


Poles of  $D(s) = s^n + I_0^n$

Consider moving all poles to left by  $\Delta\alpha$

$$\beta = 0.866 I_0$$

$$\alpha = 0.5 I_0 - \Delta\alpha$$

$$\omega_0 = \sqrt{\alpha^2 + \beta^2}$$

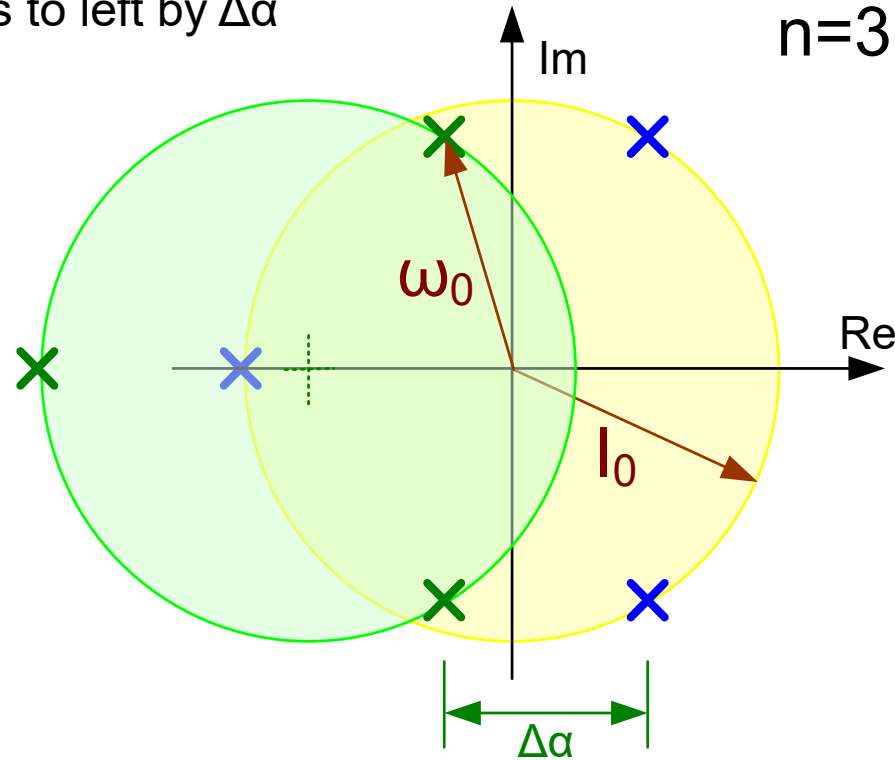

So since  $\alpha$  is fixed, to get a high  $\omega_0$ , want  $\beta$  as large as possible

## Consider now the filter obtained by adding a loss of $\alpha_L$ to the integrators

Will now determine  $\alpha_L$  and  $I_0$  needed to get a desired pole Q and  $\omega_0$  by moving all poles so that right-most pole pair is the dominant high-frequency pole pair of the filter

The values of  $\alpha$  and  $\beta$  are dependent upon  $I_0$  but the angle  $\theta$  is only dependent upon the number of integrators in the oscillator or VCO


$$\alpha + j\beta = I_0 (\cos\theta + j\sin\theta)$$

Define the location of the filter pole to be

$$\alpha_F + j\beta_F$$

It follows that
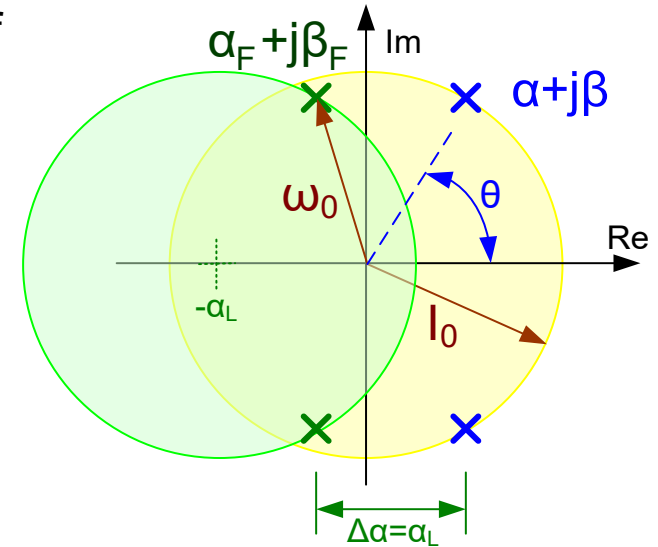
$$\beta_F = \beta \quad \alpha_F = \alpha - \alpha_L$$



The relationship between the filter parameters is well known

$$\beta_F = \frac{\omega_0}{2Q} \sqrt{4Q^2 - 1}$$


$$\alpha_F = -\frac{\omega_0}{2Q}$$

Thus for any n ↓

$$I_0 = \frac{\omega_0}{(\sin\theta)2Q} \sqrt{4Q^2 - 1}$$

$$\alpha_L = \frac{\omega_0}{2Q} + I_0 \cos\theta = \frac{\omega_0}{2Q} + \frac{\omega_0}{2Q(\tan\theta)} \sqrt{4Q^2 - 1}$$

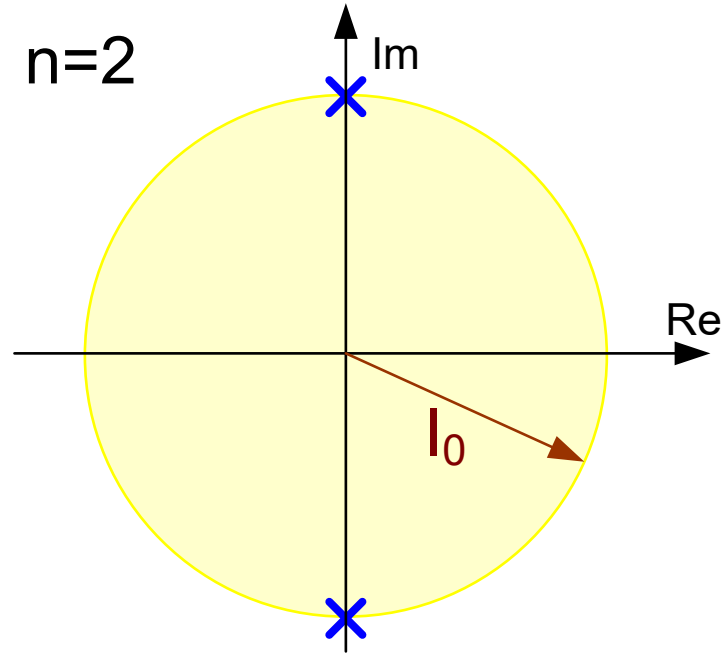**Will a two-stage structure give the highest frequency of operation for integrators with unity gain frequency  $I_0$ ?**




$$\omega_0 = \sqrt{(\alpha - \Delta\alpha)^2 + \beta^2} \quad \longrightarrow \quad \omega_0 = \sqrt{(-\Delta\alpha)^2 + \beta^2}$$

- Even though the two-stage structure may not oscillate, can work as a filter!
- Need odd number of inversions in integrators
- Can add phase lead if necessary
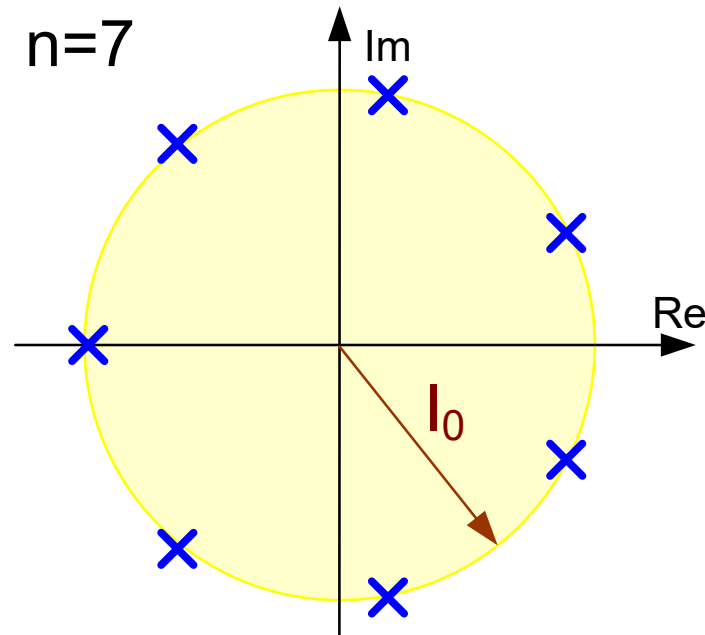
# Oscillator Background:

What will happen with a circuit that has two pole-pairs in the RHP?




General form of response for odd number of poles:

$$A_0 e^{\alpha_0 t} + \sum_{i=1}^{n/2} |A_i| e^{\alpha_i t} \cos(\beta_i t + \theta_i)$$

The impulse response (for  $n=7$ ) will have two decaying exponential terms and two growing exponential terms
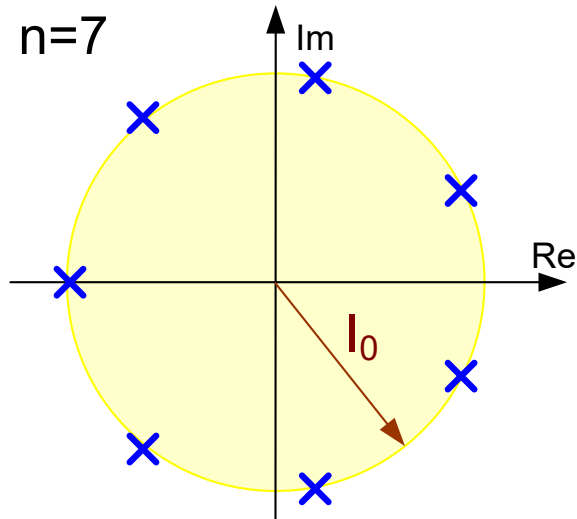
## What will happen with a circuit that has two pole-pairs in the RHP?



-0.62349	-0.781831482
0.222521	-0.974927912
0.900969	-0.433883739
0.900969	0.433883739
0.222521	0.974927912
-0.62349	0.781831482
-1	3.67545E-16

$$\alpha_1=0.2225 \quad \beta_1=0.974$$

$$\alpha_2=0.9009 \quad \beta_2=0.4338$$

Consider the growing exponential terms and normalize to  $I_0=1$



$$|A_1| e^{\alpha_1 t} \cos(\beta_1 t + \theta_1) + |A_2| e^{\alpha_2 t} \cos(\beta_2 t + \theta_2)$$

At  $t=145$  (after only 10 periods of the lower frequency signal)

$$r = \frac{e^{\alpha_2 t}}{e^{\alpha_1 t}} \Big|_{t=145} = \frac{e^{.9009 \cdot 145}}{e^{.2225 \cdot 145}} = 5.2 \times 10^{42}$$

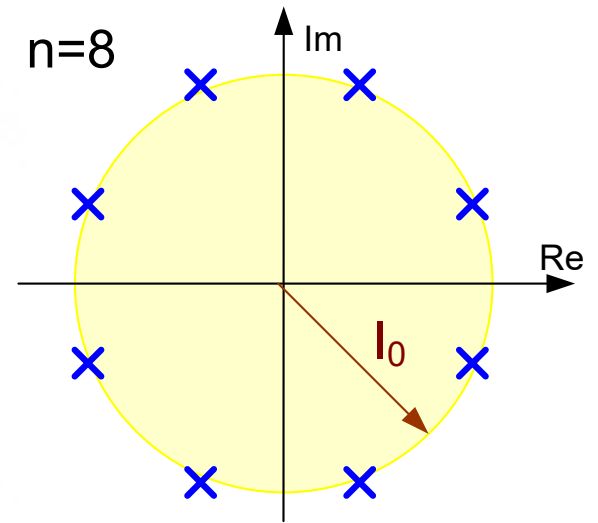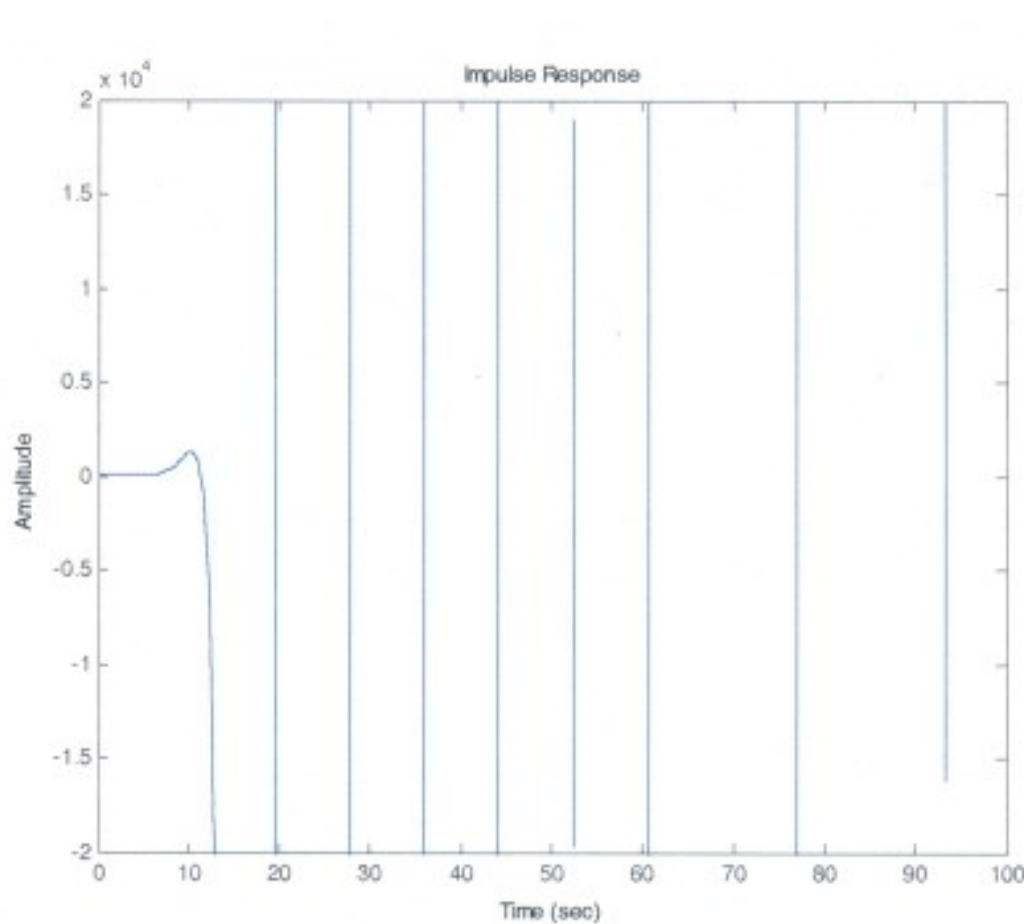**The lower frequency oscillation will completely dominate !**

What will happen with a circuit that has two pole-pairs in the RHP?



Thanks to Chen for these plots

Figure 14 N=8 impulse response

Can only see the lower frequency component !



# What will happen with a circuit that has two pole-pairs in the RHP?

Thanks to Chen for these plots

image1.jpg  
Type: JPEG Image  
Size: 2.71 MB  
Dimension: 5008 x 6608 pixels

$-0.9239i$

$0.9239 + 0.3827i$


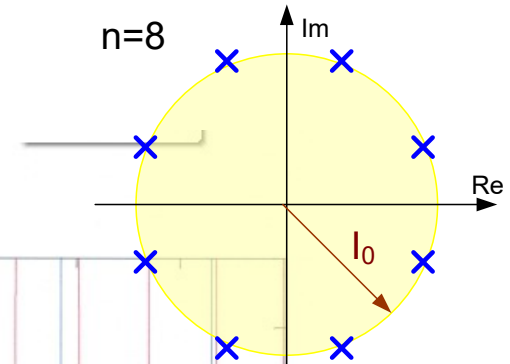
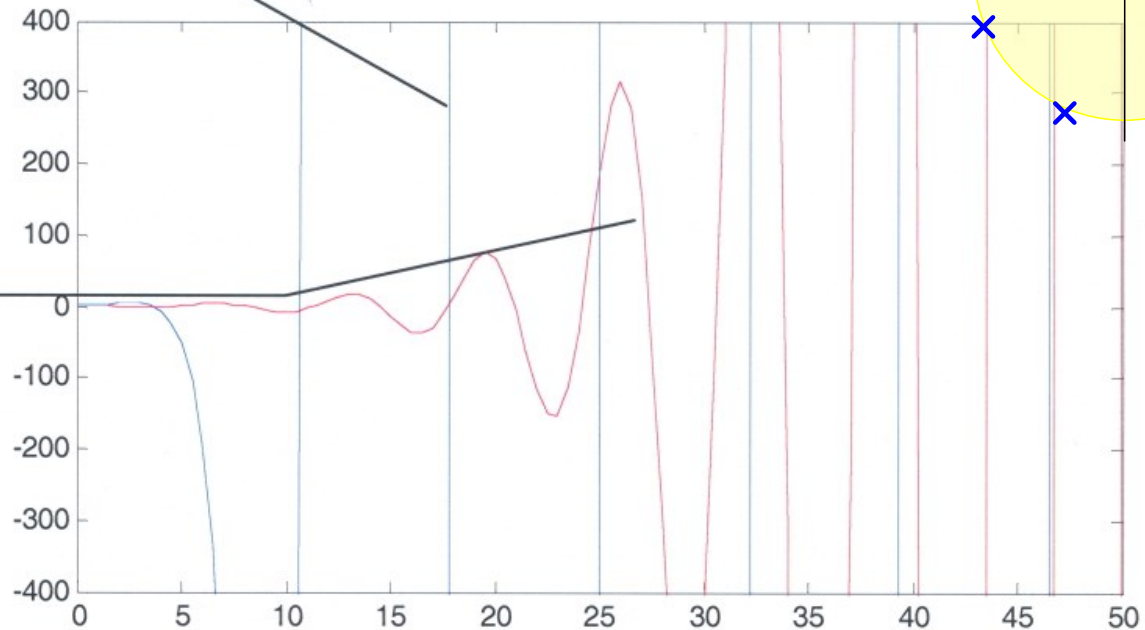


Figure 7 N=8 the impulse response of two poles

**After even only two periods of the lower frequency waveform, it completely dominates !**

How do we guarantee that we have a net coefficient of +1 in  $D(s)$ ?

$$D(s) = s^n + I_0^n$$

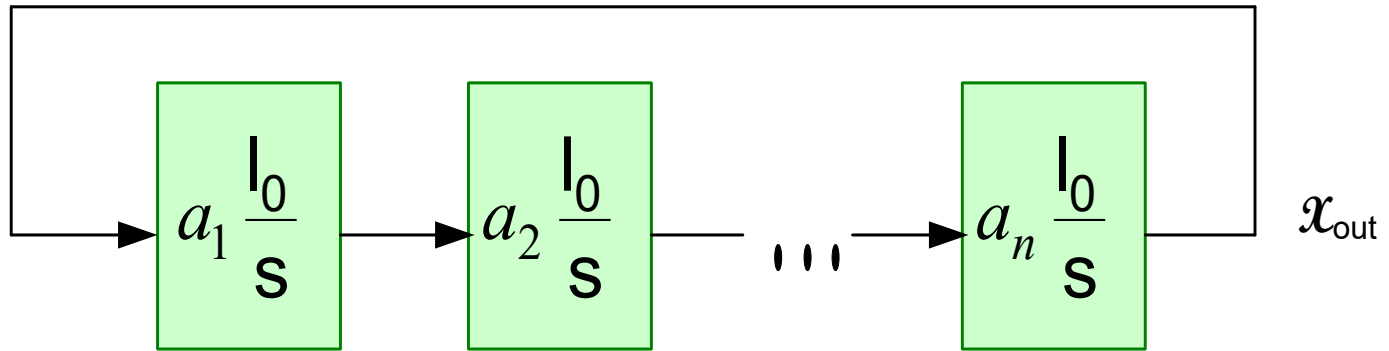

$$x_{out} = \left( \prod_{i=1}^n a_i \left( \frac{I_0}{s} \right) \right) x_{out} \quad a_i \in \{-1, 1\}$$


$$D(s) = s^n - \left( \prod_{i=1}^n a_i \right) I_0^n \quad \longrightarrow \quad \prod_{i=1}^n a_i = -1$$

Must have an odd number of inversions in the loop !

If  $n$  is odd, all stages can be inverting and identical !

How do we guarantee that we have a net coefficient of +1 in  $D(s)$ ?

$$D(s) = s^n + I_0^n$$

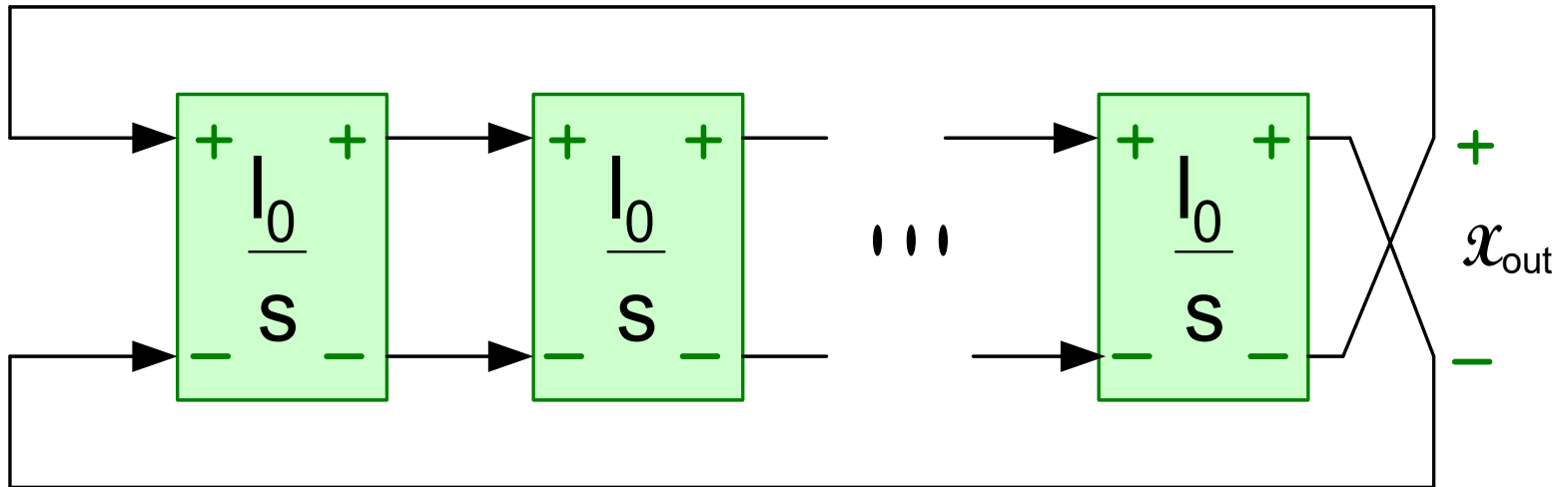



If fully differential or fully balanced, must have an odd number of crossings of outputs

Applicable for both even and odd order loops

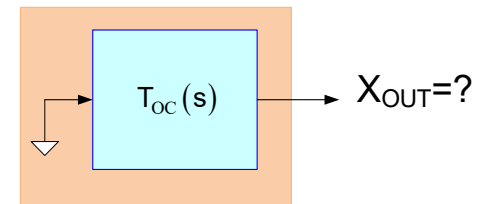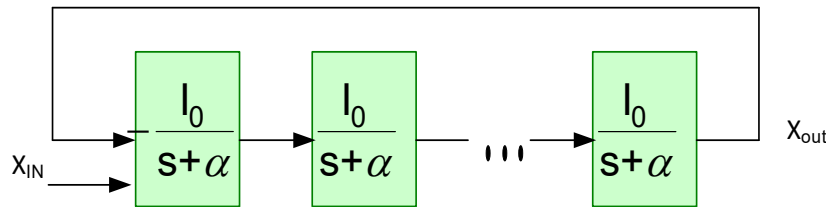
# Inputs to Oscillator-Derived Filters:

Most applicable to designing 2<sup>nd</sup>-order high frequency narrow band bandpass filters

- Add loss to delay stages
- Multiple Input Locations Often Possible
- Natural Input is Input to delay stage



## A lossy integrator stage

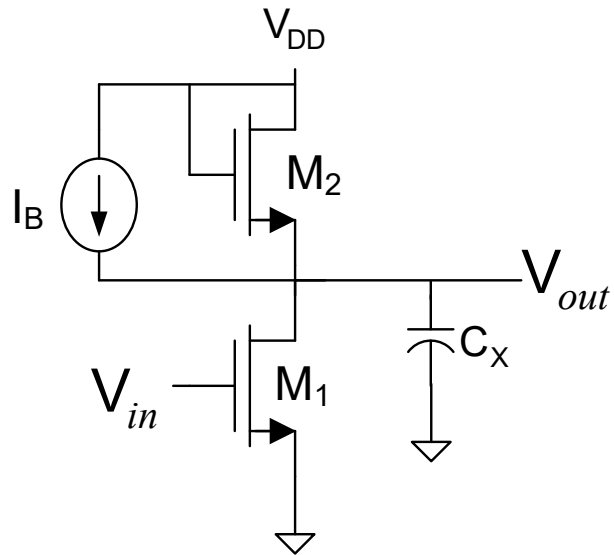


$$I(s) = \frac{-g_{m1}/C_X}{s + g_{m2}/C_X}$$

$$I_0 = g_{m1}/C_X$$


$$\alpha_L = g_{m2}/C_X$$
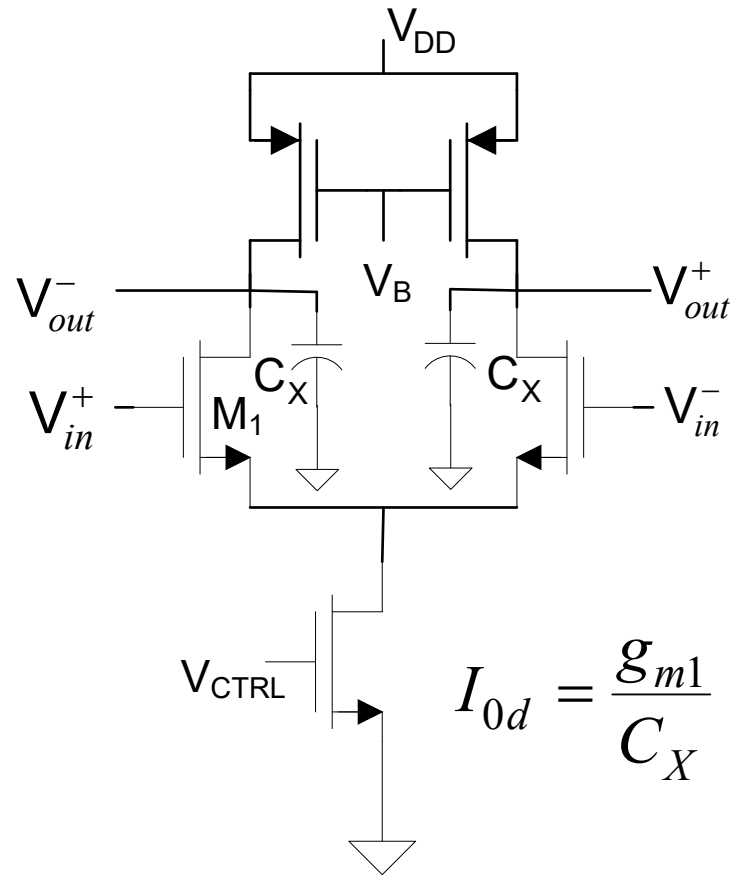
## A fully-differential voltage-controlled integrator stage



Will need CMFB circuit

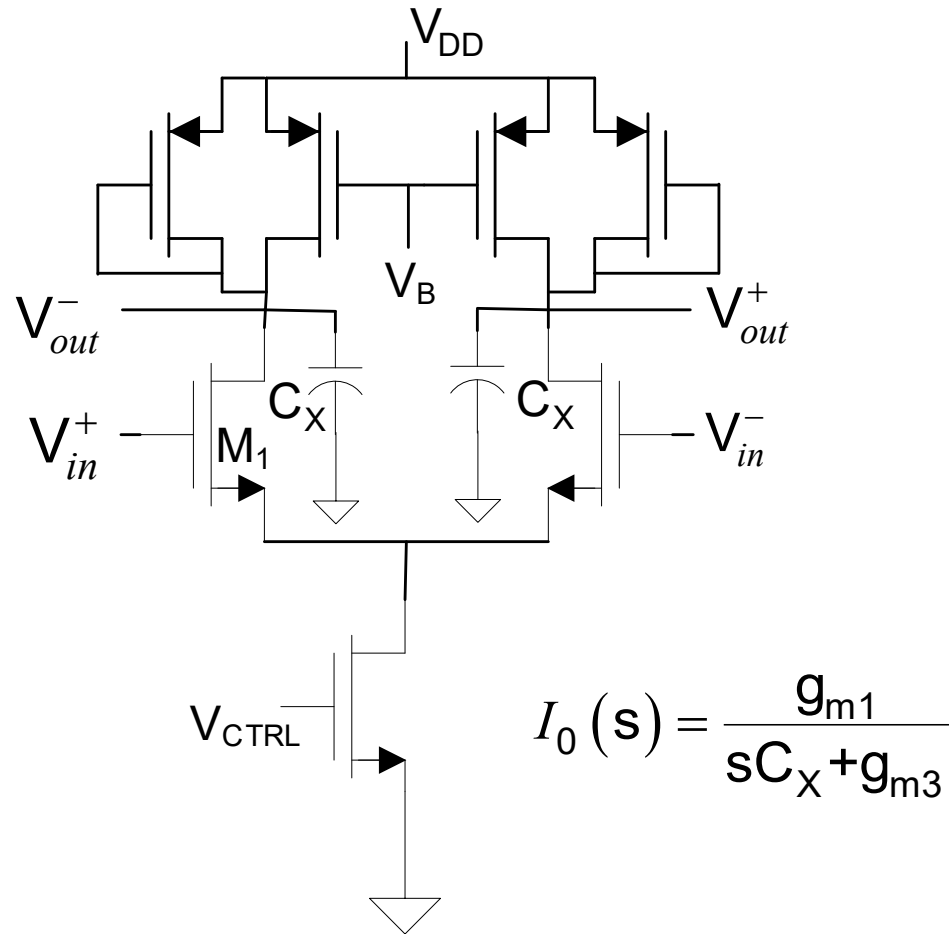
## A fully-differential voltage-controlled integrator stage with loss



Will need CMFB circuit

# A fully-differential voltage-controlled integrator stage with loss

(almost same as previous)

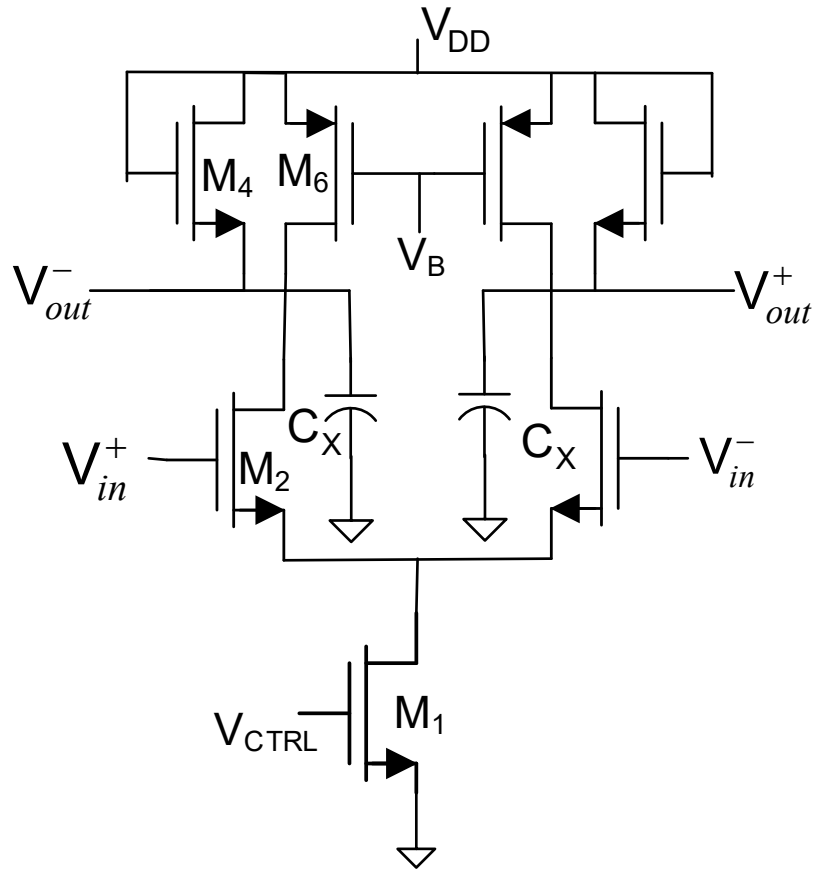

$$I_0 (s) = \frac{g_{m1}}{sC_X + g_{m3}}$$

Will need CMFB circuit



# Example:

Using the single-stage lossy integrator, design the integrator to meet a given  $\omega_0$  and  $Q$  requirement

Recall:


$$I_0 = \frac{\omega_0}{(\sin\theta)2Q} \sqrt{4Q^2 - 1} \quad (1)$$

$$\alpha_L = \frac{\omega_0}{2Q} + \frac{\omega_0}{2Q(\tan\theta)} \sqrt{4Q^2 - 1} \quad (2)$$

Substituting for  $I_0$  and  $\alpha_L$  we obtain:

$$\frac{g_{m1}}{C_X} = \frac{\omega_0}{(\sin\theta)2Q} \sqrt{4Q^2 - 1} \quad (3)$$
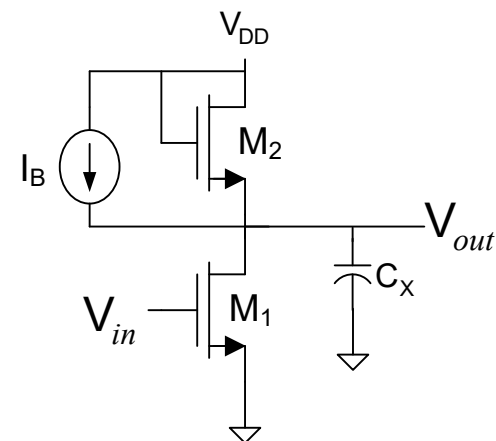
$$\frac{g_{m2}}{C_X} = \frac{\omega_0}{2Q} + \frac{\omega_0}{2Q(\tan\theta)} \sqrt{4Q^2 - 1} \quad (4)$$



$$V_{OUT}(sC_x + g_{m2}) + g_{m1} V_{IN} = 0$$

$$\frac{V_{OUT}}{V_{IN}} = - \frac{g_{m1}}{sC_x + g_{m2}}$$

$$I_0 = g_{m1}/C_X$$

$$\alpha_L = g_{m2}/C_X$$

Unknowns:  $I_B, V_{EB1}, W_1/L_1, W_2/L_2, C_X$

# Example:

Using the single-stage lossy integrator, design the integrator to meet a given  $\omega_0$  and  $Q$  requirement

Expressing  $g_{m1}$  and  $g_{m2}$  in terms of design parameters:

$$\frac{\mu C_{OX} W_1 V_{EB1}}{L_1 C_X} = \frac{\omega_0}{(\sin\theta) 2Q} \sqrt{4Q^2 - 1} \quad (5)$$

$$\frac{\mu C_{OX} W_2 V_{EB2}}{L_2 C_X} = \frac{\omega_0}{2Q} + \frac{\omega_0}{2Q(\tan\theta)} \sqrt{4Q^2 - 1} \quad (6)$$


If we assume  $I_B=0$ , equating drain currents obtain:

$$V_{EB2} = V_{EB1} \sqrt{\frac{W_1 L_2}{W_2 L_1}} \quad (7)$$

Thus the previous two expressions can be rewritten as :

$$\frac{\mu C_{OX} V_{EB1}}{C_X} \left[ \frac{W_1}{L_1} \right] = \frac{\omega_0}{(\sin\theta) 2Q} \sqrt{4Q^2 - 1} \quad (8)$$
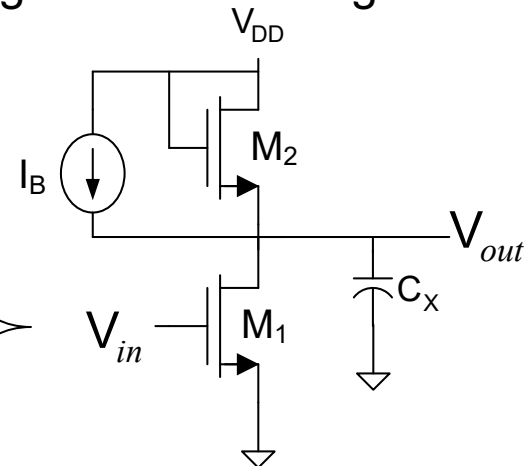
$$\frac{\mu C_{OX} V_{EB1}}{C_X} \left[ \frac{W_1 W_2}{L_1 L_2} \right] = \frac{\omega_0}{2Q} + \frac{\omega_0}{2Q(\tan\theta)} \sqrt{4Q^2 - 1} \quad (9)$$



$$I_0 = g_{m1}/C_X$$

$$\alpha_L = g_{m2}/C_X$$

# Example:


Using the single-stage lossy integrator, design the integrator to meet a given  $\omega_0$  and  $Q$  requirement

$$\frac{\mu C_{OX} V_{EB1}}{C_X} \left[ \frac{W_1}{L_1} \right] = \frac{\omega_0}{(\sin\theta) 2Q} \sqrt{4Q^2 - 1}$$

$$\frac{\mu C_{OX} V_{EB1}}{C_X} \left[ \frac{W_1 W_2}{L_1 L_2} \right] = \frac{\omega_0}{2Q} + \frac{\omega_0}{2Q(\tan\theta)} \sqrt{4Q^2 - 1}$$

Taking the ratio of these two equations we obtain:
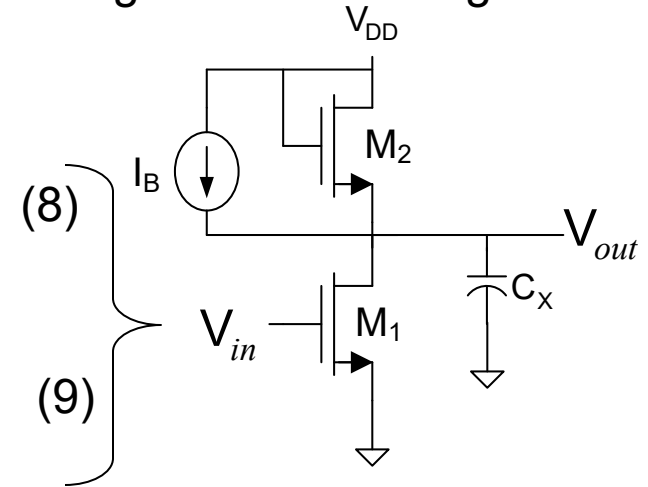
$$\frac{W_2}{L_2} = \frac{\sin\theta + \cos\theta \sqrt{4Q^2 - 1}}{\sqrt{4Q^2 - 1}} \quad (10)$$



$$I_0 = g_{m1}/C_X$$

$$\alpha_L = g_{m2}/C_X$$


Observe that the pole  $Q$  is determined by the dimensions of the lossy device !

# Example:

Using the single-stage lossy integrator, design the integrator to meet a given  $\omega_0$  and  $Q$  requirement

$$\frac{\mu C_{OX} V_{EB1}}{C_X} \left[ \frac{W_1}{L_1} \right] = \frac{\omega_0}{(\sin\theta) 2Q} \sqrt{4Q^2 - 1} \quad (8)$$
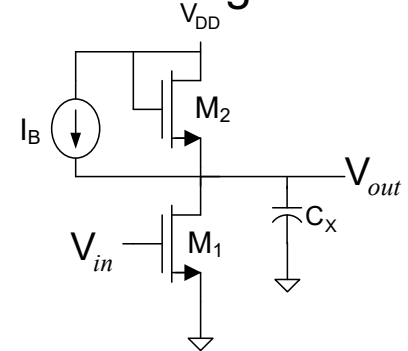
$$\frac{W_2}{L_2} = \frac{\sin\theta + \cos\theta \sqrt{4Q^2 - 1}}{\sqrt{4Q^2 - 1}} \quad (10)$$



Still must obtain  $W_1/L_1$ ,  $V_{EB1}$ , and  $C_X$  from either of these equations

Although it appears that there might be 3 degrees of freedom left and only one constraint (one of these equations), if these integrators are connected in a loop, the operating point (Q-point) will be the same for all stages and will be that value where  $V_{out} = V_{in}$ . So, this adds a second constraint.

Setting  $V_{out} = V_{in}$ , and assuming  $V_{T1} = V_{T2}$ , we obtain from KVL

$$V_{DD} = V_{EB1} + V_{EB2} + 2V_T \quad (11)$$


But  $V_{EB1}$  and  $V_{EB2}$  are also related in (7)

# Example:

Using the single-stage lossy integrator, design the integrator to meet a given  $\omega_0$  and  $Q$  requirement

$$\frac{\mu C_{OX} V_{EB1}}{C_X} \left[ \frac{W_1}{L_1} \right] = \frac{\omega_0}{(\sin\theta) 2Q} \sqrt{4Q^2 - 1} \quad (8)$$
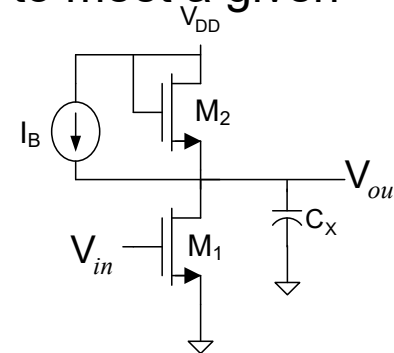
$$\frac{W_2}{L_2} = \frac{\sin\theta + \cos\theta \sqrt{4Q^2 - 1}}{\sqrt{4Q^2 - 1}} \quad (10)$$



Still must obtain  $W_1/L_1$ ,  $V_{EB1}$ , and  $C_X$  from either of these equations

$$V_{DD} = V_{EB1} + V_{EB2} + 2V_T \quad (11)$$

$$V_{EB2} = V_{EB1} \sqrt{\frac{W_1 L_2}{W_2 L_1}} \quad (7)$$

$$V_{EB1} = \frac{V_{DD} - 2V_T}{1 + \sqrt{\frac{W_2 L_1}{W_1 L_2}}} \quad (12)$$

Substituting (10) into (12) and then into (8) we obtain


$$\frac{\mu C_{OX}}{C_X} \left[ \frac{W_1}{L_1} \right] \left( \frac{V_{DD} - 2V_T}{1 + \sqrt{\left( \frac{W_1}{L_1} \right)^{-1} \left( \frac{\sin\theta + \cos\theta \sqrt{4Q^2 - 1}}{\sqrt{4Q^2 - 1}} \right)}} \right) = \frac{\omega_0}{(\sin\theta) 2Q} \sqrt{4Q^2 - 1} \quad (13)$$

# Example:

Using the single-stage lossy integrator, design the integrator to meet a given  $\omega_0$  and  $Q$  requirement

$$\frac{W_2}{L_2} = \frac{\sin\theta + \cos\theta\sqrt{4Q^2-1}}{\sqrt{4Q^2-1}}$$
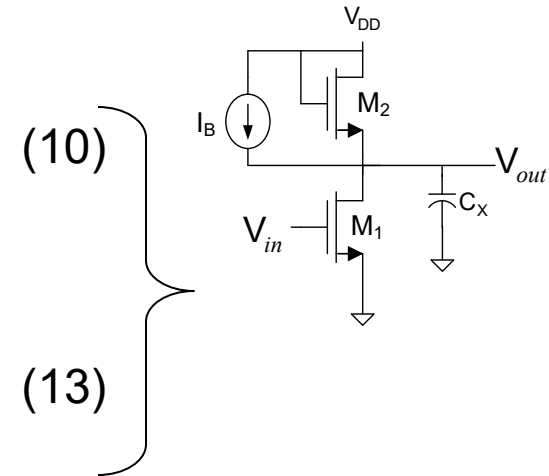
$$\frac{\mu C_{OX}}{C_X} \left[ \frac{W_1}{L_1} \right] \left( \frac{V_{DD} - 2V_T}{1 + \sqrt{\left(\frac{W_1}{L_1}\right)^{-1} \left( \frac{\sin\theta + \cos\theta\sqrt{4Q^2-1}}{\sqrt{4Q^2-1}} \right)}} \right) = \frac{\omega_0}{(\sin\theta)2Q} \sqrt{4Q^2-1}$$



There is still one degree of freedom remaining. Can either pick  $W_1/L_1$  and solve for  $C_X$  or pick  $C_X$  and solve for  $W_1/L_1$ .

Explicit expression for  $W_1/L_1$  not available

Tradeoffs between  $C_X$  and  $W_1/L_1$  will often be made

Since  $V_{OUTQ} = V_T + V_{EB1}$ , it may be preferred to pick  $V_{EB1}$ , then solve (12) for  $W_1/L_1$  and then solve (13) for  $C_X$

Adding  $I_B$  will provide one additional degree of freedom (we arbitrarily set it to 0 in this analysis) and will relax the relationship between  $V_{OUTQ}$  and  $W_1/L_1$  since (7) will be modified



Stay Safe and Stay Healthy !

**End of Lecture 36**