

EE 508

Lecture 19

Basic Biquadratic Active Filters


Sensitivity Functions

- Comparison of Filter Structures
- Performance Prediction
- Design Characterization

Filter Design/Synthesis Considerations


Most odd-ordered designs today use one of the following three basic architectures

Cascaded Biquads

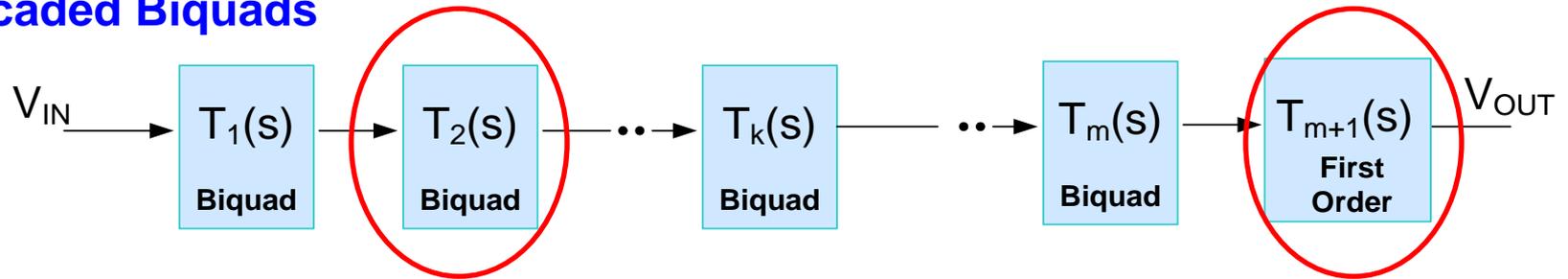


$$T(s) = T_1 T_2 \dots T_m$$

Leapfrog

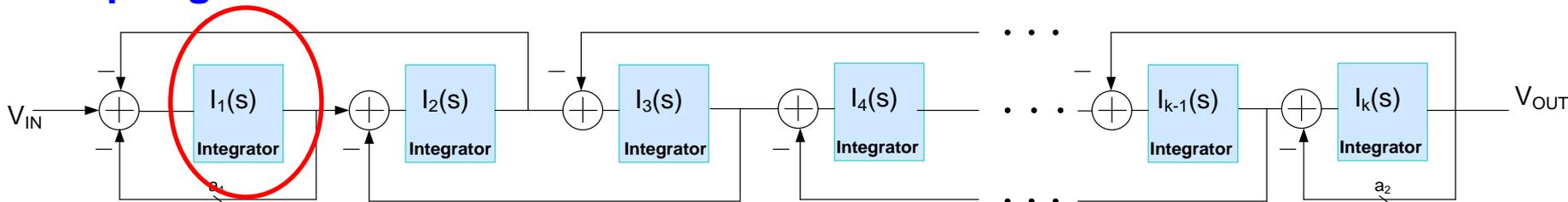


Multiple-loop Feedback (less popular)

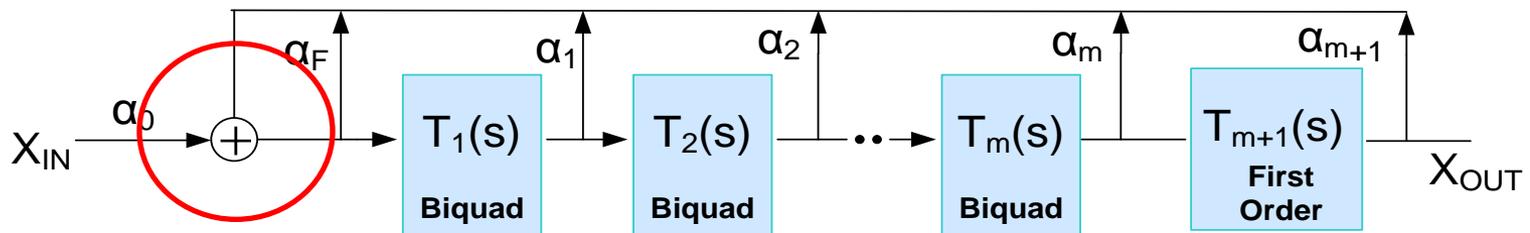

What's unique in all of these approaches?

Filter Design/Synthesis Considerations

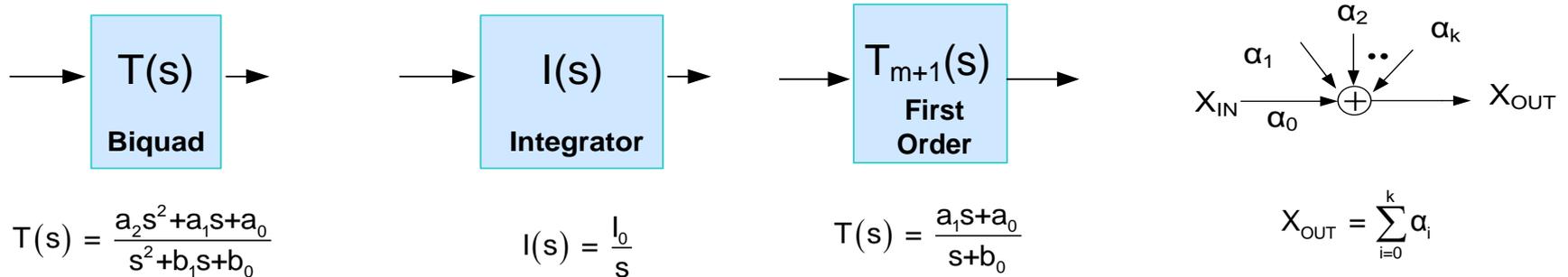What's unique in all of these approaches?




- Most effort on synthesis can focus on synthesizing these four blocks
 - (the summing function is often incorporated into the Biquad or Integrator)
 - (the first-order block is much less challenging to design than the biquad)
- Some issues associated with their interconnections

- And, in many integrated structures, the biquads are made with integrators
 - (thus, much filter design work simply focuses on the design of integrators)

Filter Design/Synthesis Considerations

There are many different filter architectures that can realize a given transfer function

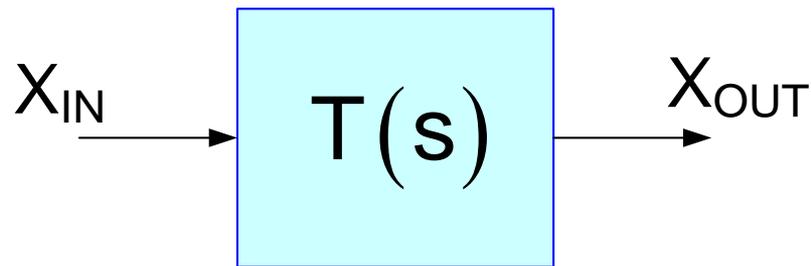Will first consider second-order Bandpass filter structures




$$|T(s)| = H \frac{s \left(\frac{\omega_0}{Q} \right)}{s^2 + s \left(\frac{\omega_0}{Q} \right) + \omega_0^2}$$

$$BW = \omega_B - \omega_A = \frac{\omega_0}{Q}$$

$$\omega_{PEAK} = \omega_0$$

Review from last time

Example 1:

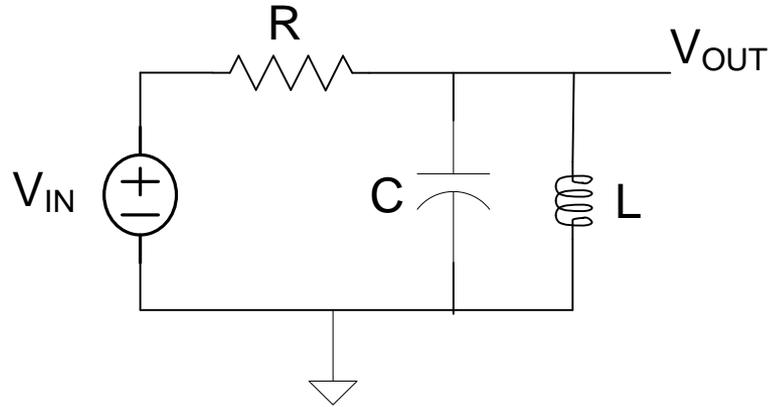

$$\frac{V_{\text{OUT}}}{V_{\text{IN}}} = T(s) = \frac{1}{RC} \frac{s}{s^2 + s\left(\frac{1}{RC}\right) + \frac{1}{LC}}$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

$$Q = R\sqrt{\frac{C}{L}}$$


$$BW = \frac{1}{RC}$$

Can realize an arbitrary 2nd order bandpass function within a gain factor

Simple design process (sequential but not independent control of ω_0 and Q)

Review from last time

Example 2:

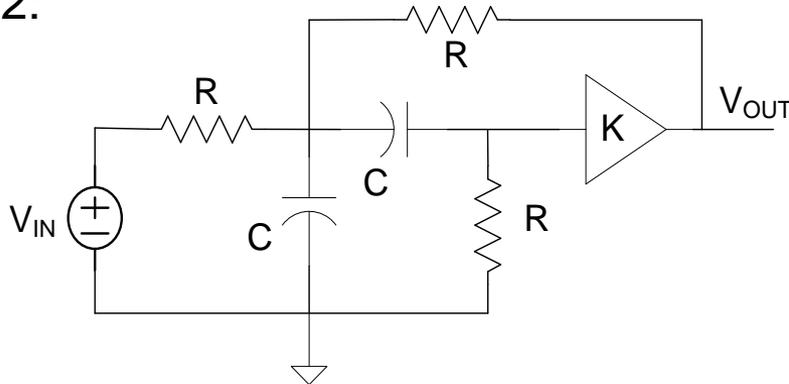

Equal R, Equal C Realization

$$\frac{V_{OUT}}{V_{IN}} = T(s) = \frac{K}{RC} \frac{s}{s^2 + s \left(\frac{4-K}{RC} \right) + \frac{2}{(RC)^2}}$$

$$\omega_0 = \frac{\sqrt{2}}{RC} \quad Q = \frac{\sqrt{2}}{4-K} \quad BW = \frac{4-K}{RC}$$

3 degrees of freedom (effectively 2 since dimensionless)


Can satisfy arbitrary 2nd-order BP constraints within a gain factor with this circuit
Very simple circuit structure

Independent control of ω_0 and Q but requires tuning more than one component

Can actually move poles in RHP by making $K > 4$

Review from last time

Example 3:

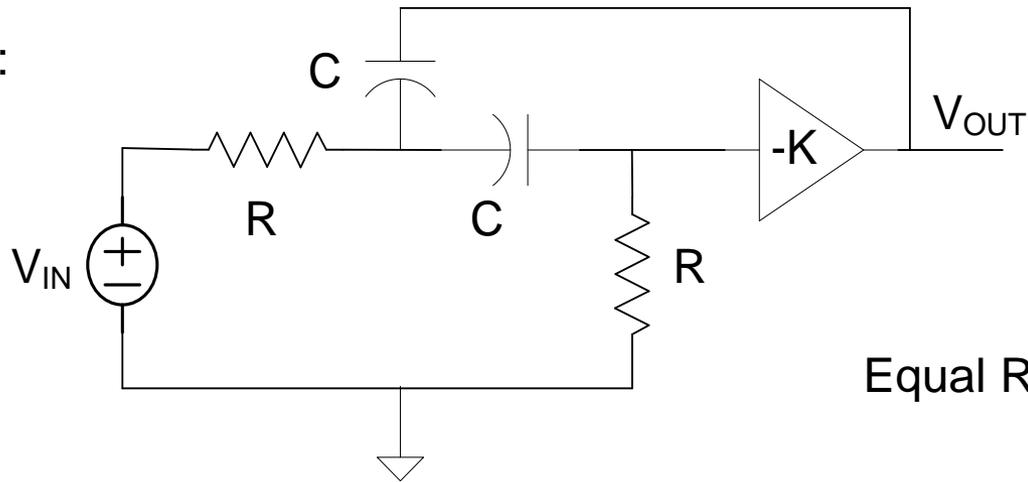

$$\frac{V_{OUT}}{V_{IN}} = T(s) = -\frac{K}{(1+K)RC} \frac{s}{s^2 + s \left(\left[\frac{3}{RC} \right] \frac{1}{(1+K)} \right) + \frac{1}{(1+K)(RC)^2}}$$

$$\omega_0 = \frac{1}{RC\sqrt{1+K}} \quad Q = \frac{\sqrt{1+K}}{3} \quad BW = \frac{3}{RC(1+K)}$$

3 degrees of freedom (2 effective since dimensionless)


Can satisfy arbitrary 2nd-order BP constraints within a gain factor with this circuit

Very simple circuit structure


Simple design process (sequential but not independent control of ω_0 and Q , requires tuning of more than 1 component if Rs used)

Review from last time


Example 4:

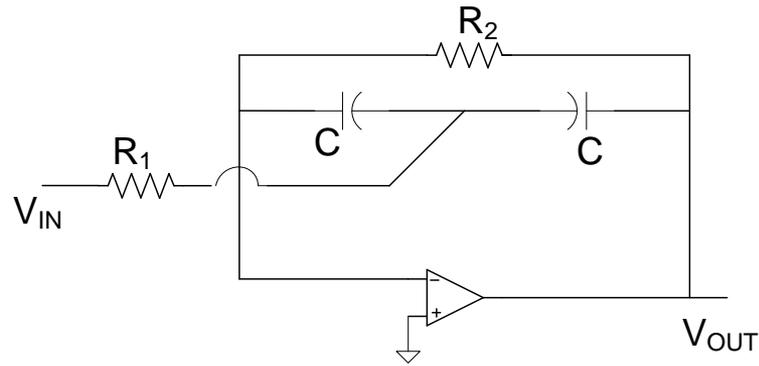

Some variants of the bridged-T feedback structure

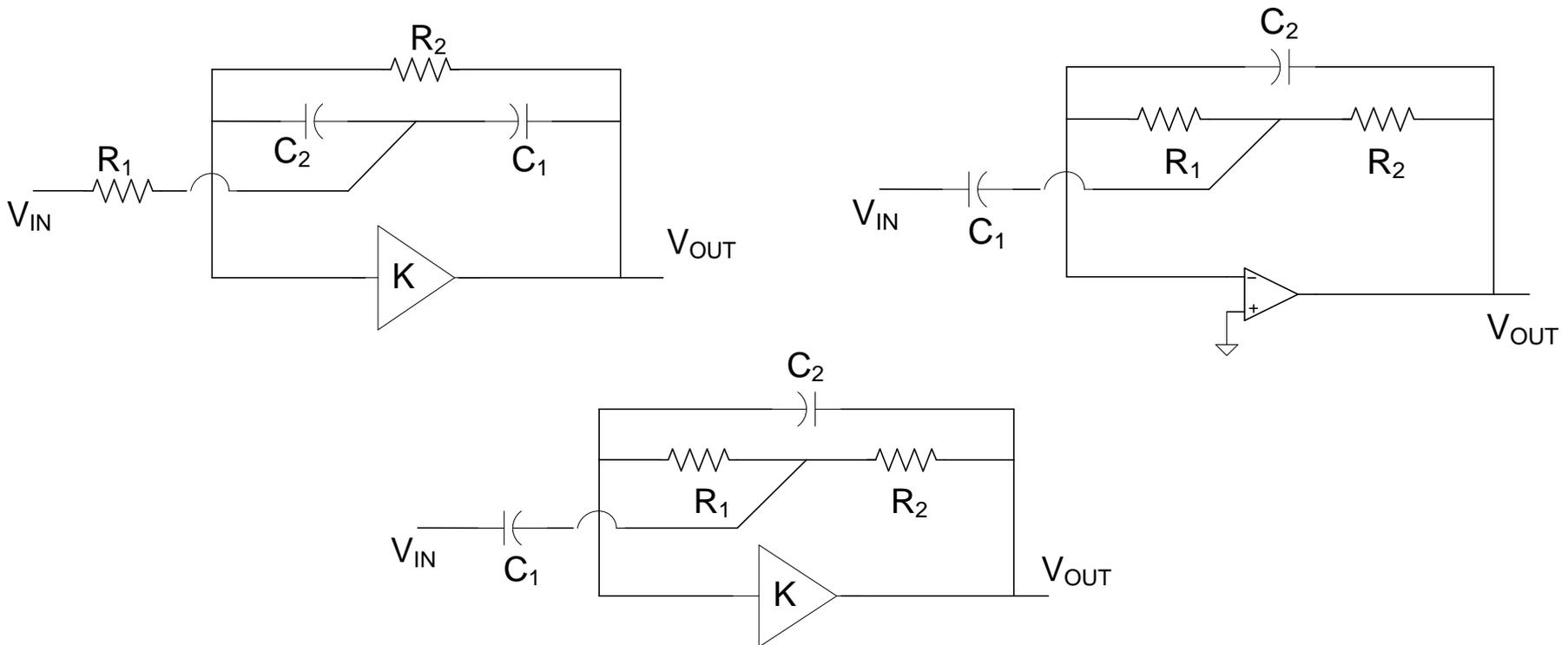

Example 5:

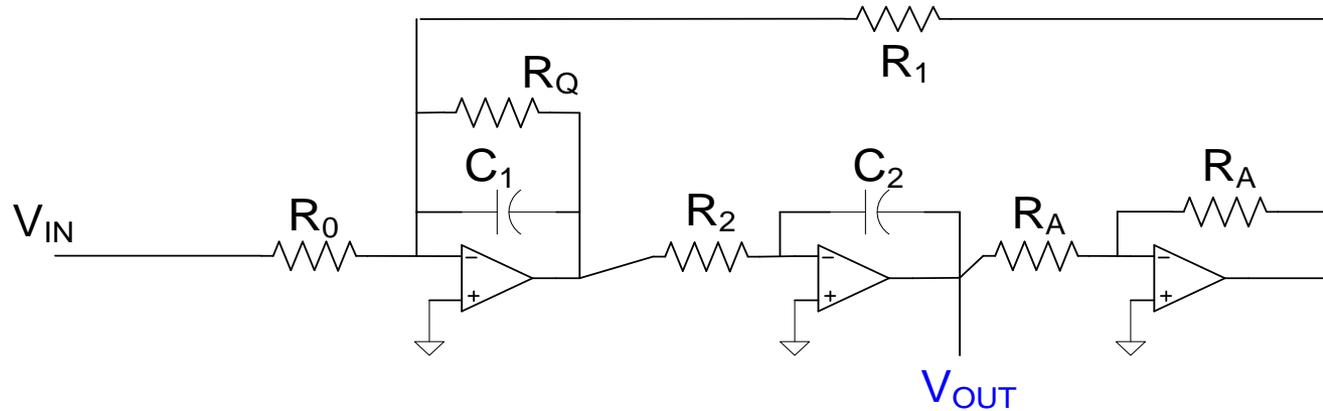


$$\frac{V_{OUT}}{V_{IN}} = T(s) = -\frac{1}{R_0 C_2} \frac{s}{s^2 + s \left(\frac{1}{R_Q C_2} \right) + \frac{1}{R_1 R_2 C_1 C_2}}$$

Second-order Bandpass Filter

8 degrees of freedom (effectively 7 since dimensionless)

Denote as a two-integrator-loop structure

Example 5:

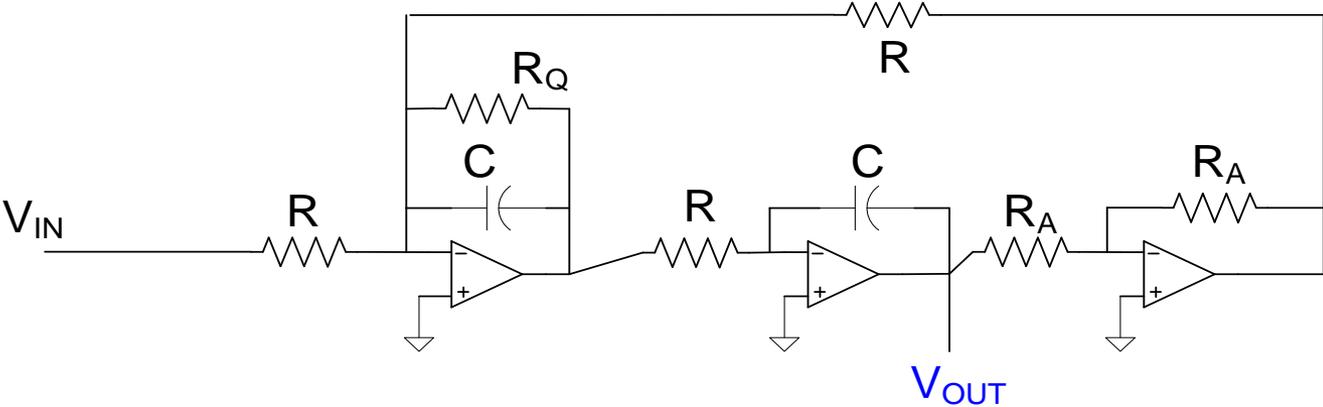

Equal R Equal C
(except R_Q)

$$\frac{V_{OUT}}{V_{IN}} = T(s) = -\frac{1}{RC} \frac{s}{s^2 + s \left(\left[\frac{R}{R_Q} \right] \frac{1}{RC} \right) + \frac{1}{(RC)^2}}$$


3 degrees of freedom (effectively 2 since dimensionless)

$\omega_0 = ?$

$Q = ?$

$BW = ?$

Example 5:

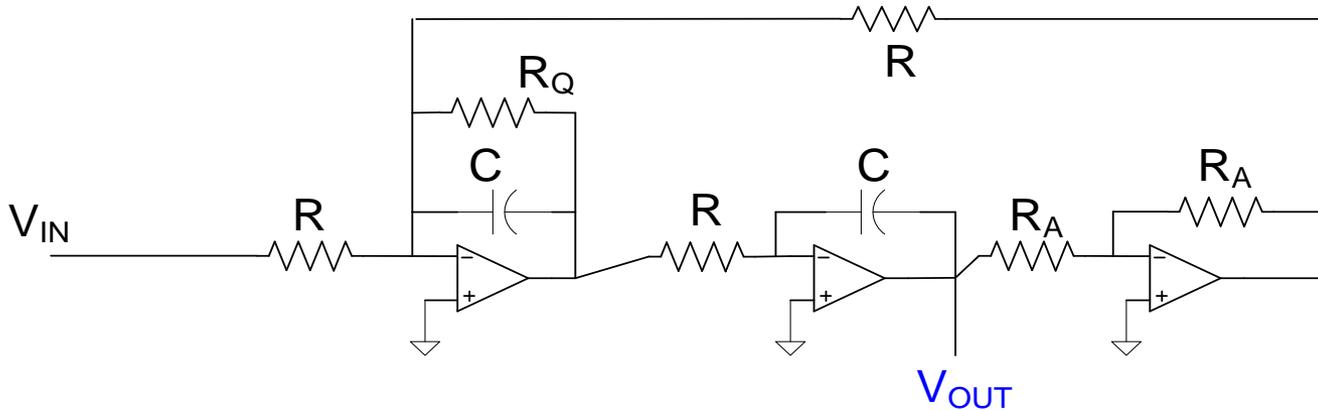

Equal R Equal C
(except R_Q)

$$\frac{V_{OUT}}{V_{IN}} = T(s) = -\frac{1}{RC} \frac{s}{s^2 + s \left(\left[\frac{R}{R_Q} \right] \frac{1}{RC} \right) + \frac{1}{(RC)^2}}$$

3 degrees of freedom (effectively 2 since dimensionless)

$$\omega_0 = \frac{1}{RC}$$




$$Q = \frac{R_Q}{R}$$

$$BW = \left[\frac{R}{R_Q} \right] \frac{1}{RC}$$

Simple design process (sequential but not independent control of ω_0 and Q with R_s , requires more tuning more than one R if C_s fixed)

Modest component spread even for large Q



Example 5:

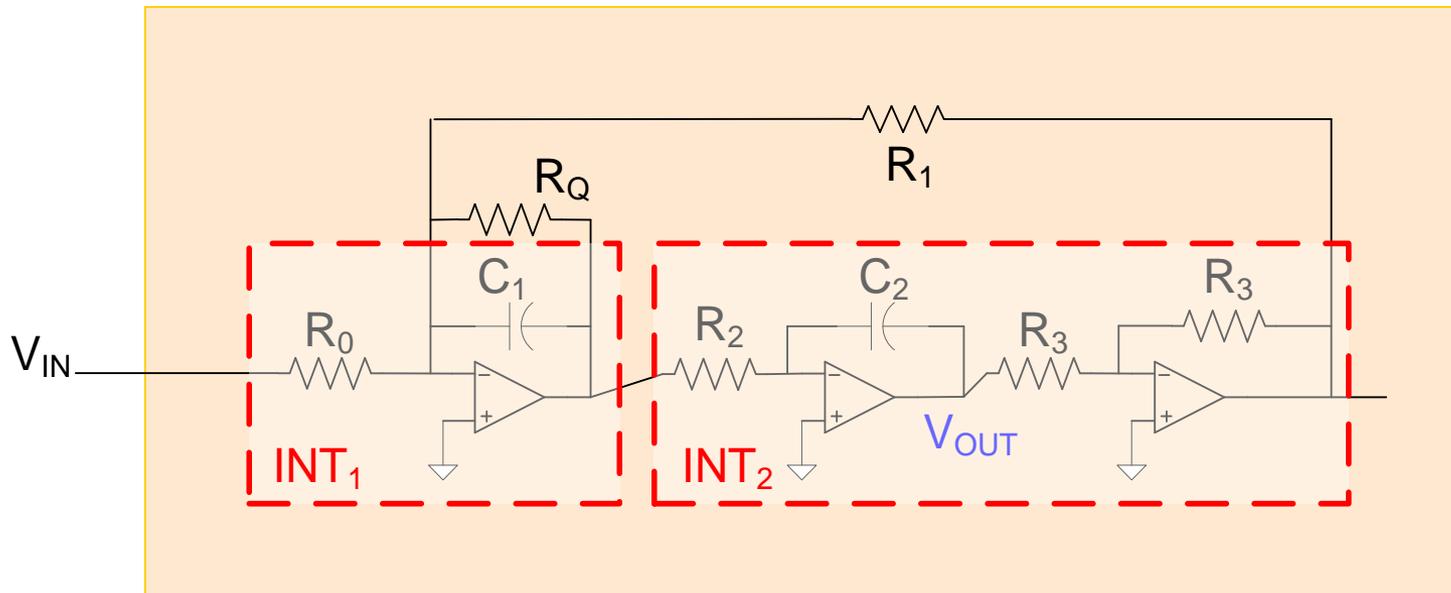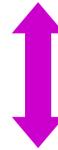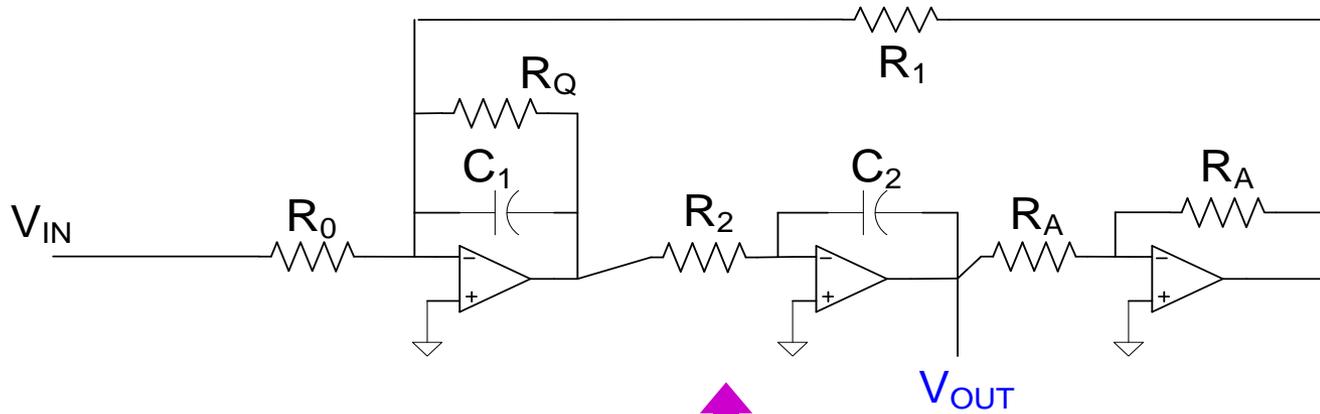


Two Integrator Loop Representation

Example 5:


Two Integrator Loop Representation

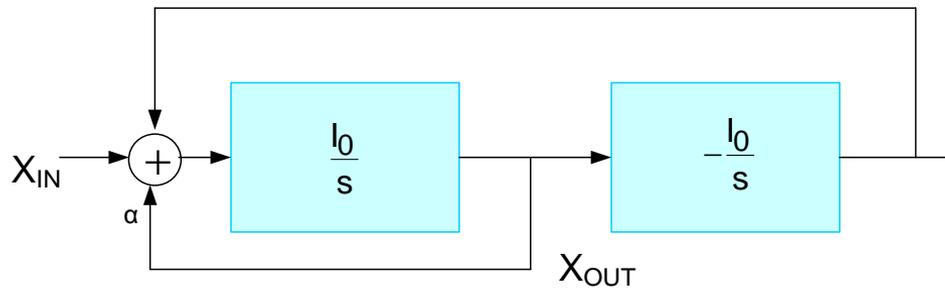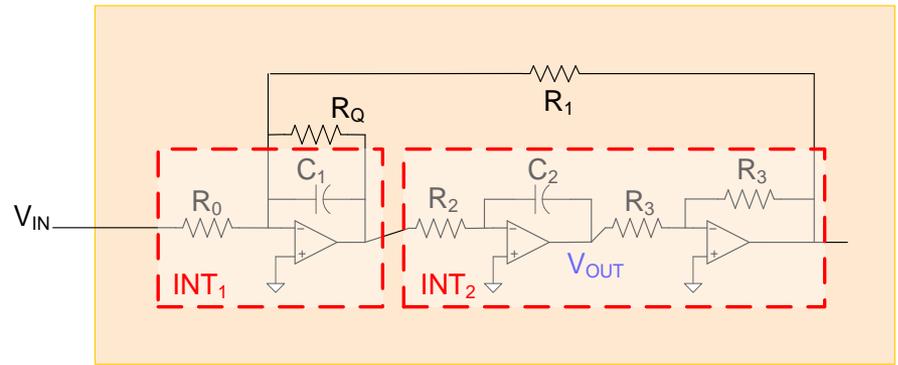

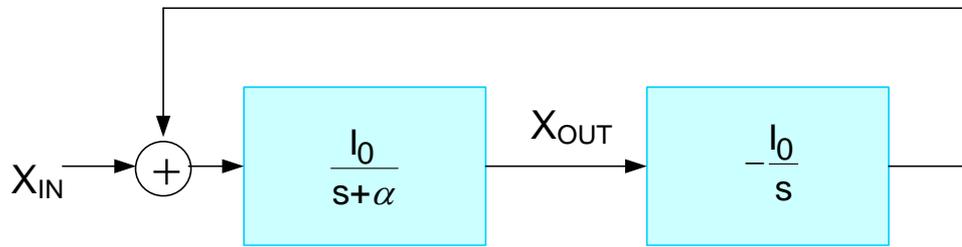Inverting and Noninverting Integrator Loop








Integrator and Lossy Integrator Loop

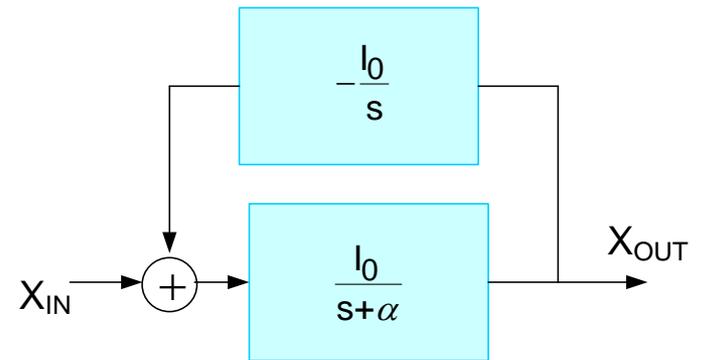




Integrator and Lossy Integrator Loop

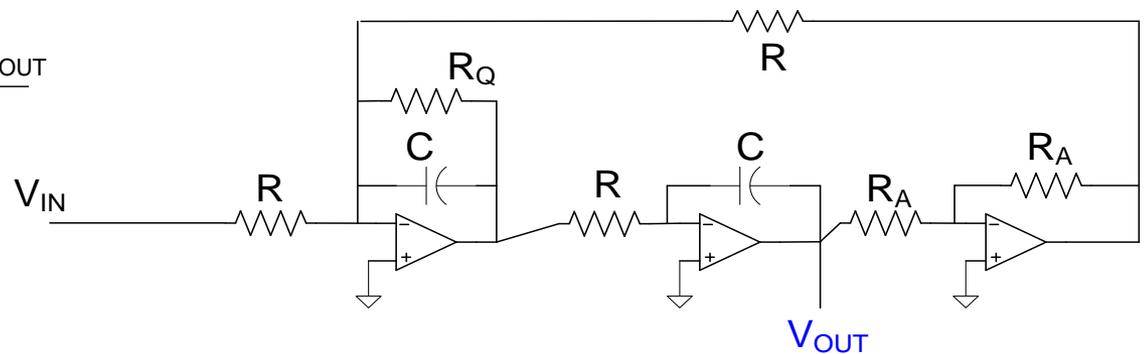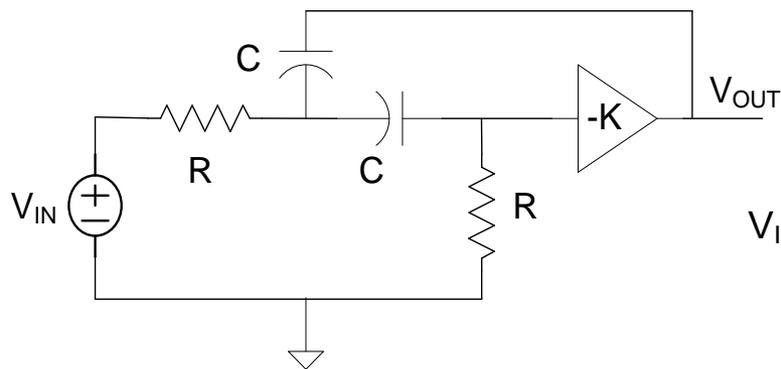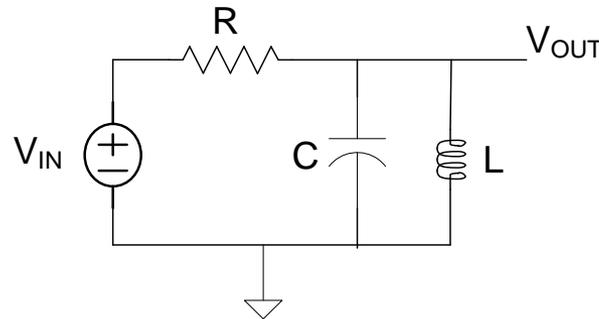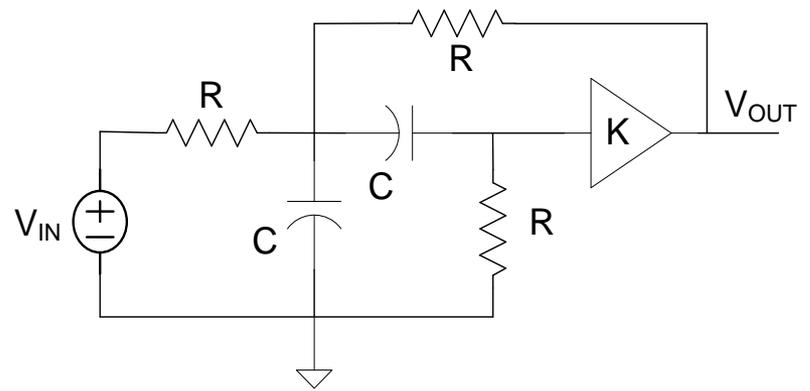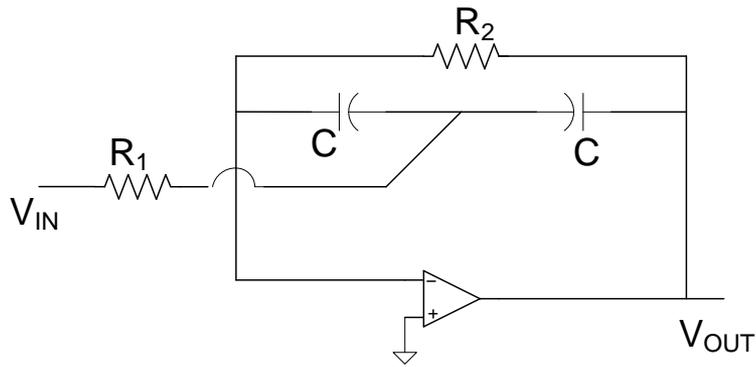How does the performance of these bandpass filters compare?





Ideally, all give same performance (within a gain factor)

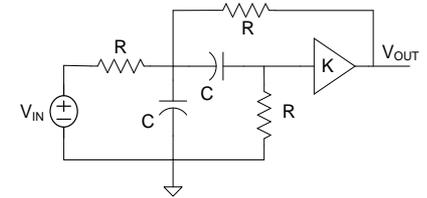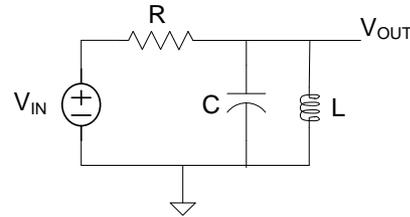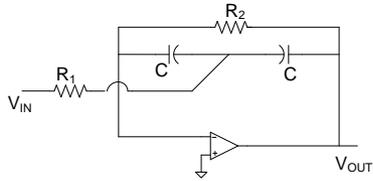How does the performance of these bandpass filters compare?



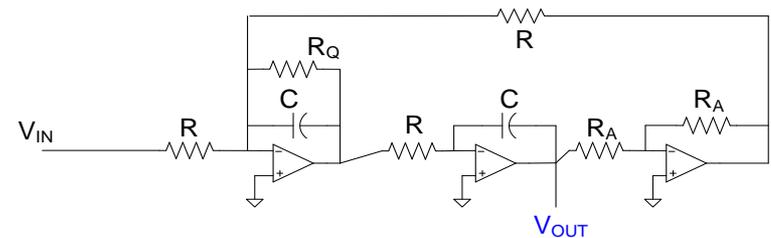
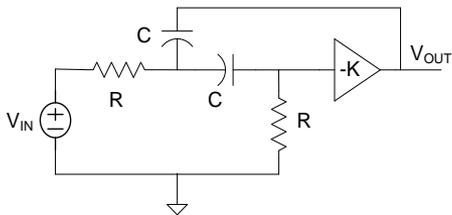
- Component Spread
- Number of Op Amps
- Is the performance strongly dependent upon how DOF are used?
- Ease of tunability/calibration (but practical structures often are not calibrated)
- Total capacitance or total resistance
- Power Dissipation
- Sensitivity
- Effects of Op Amps



Consider effects of Op Amp on +KRC Bandpass with Equal R, Equal C

$$\omega_0 = \frac{\sqrt{2}}{RC} \quad Q = \frac{\sqrt{2}}{4-K}$$

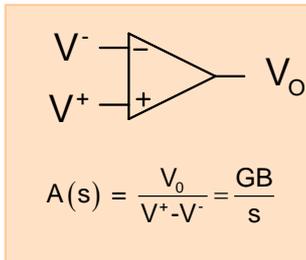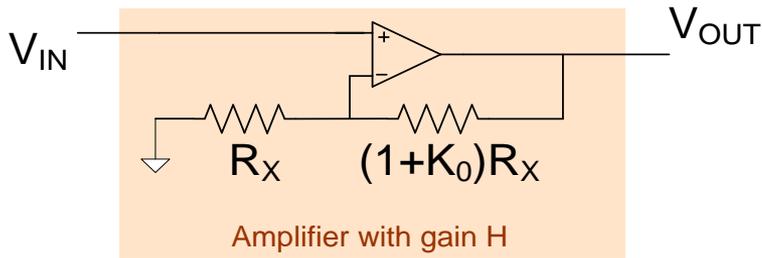Assume K realized with standard Op Amp Circuit



$$K(s) = \frac{K_0}{1 + \frac{K_0}{GB} s}$$

- Significant shift in peak frequency
- BW does not change very much
- Some drop in gain at peak frequency


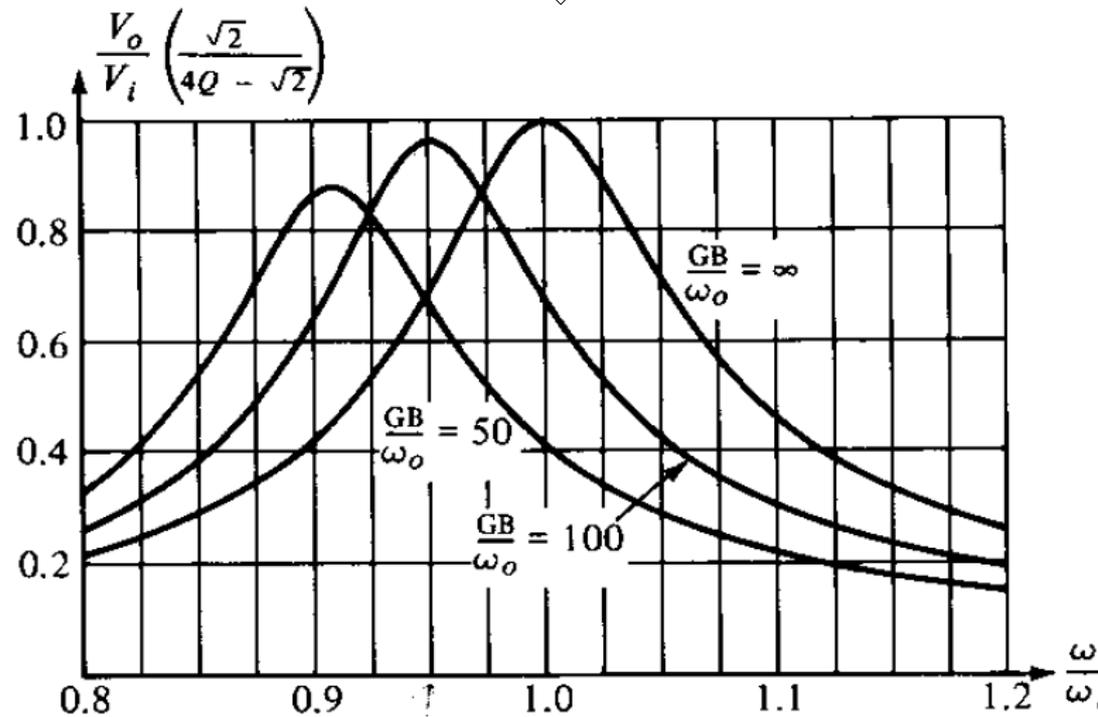
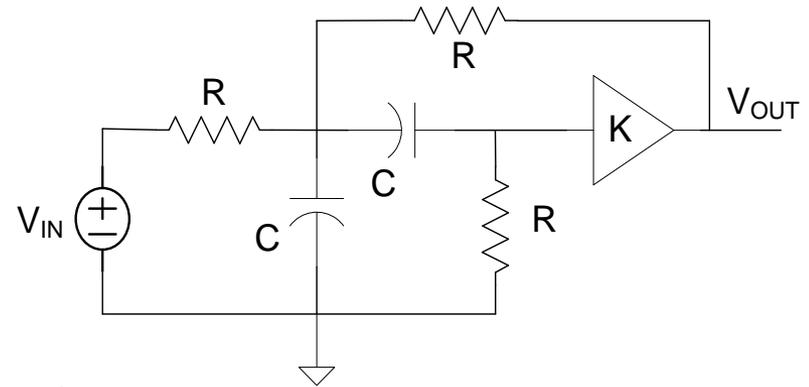


Fig. 11-4 Effect of GB on the magnitude curve for $Q = 10$

Practically, GB/ω_0 must be less than 100

Consider 2nd Order Lowpass Biquads

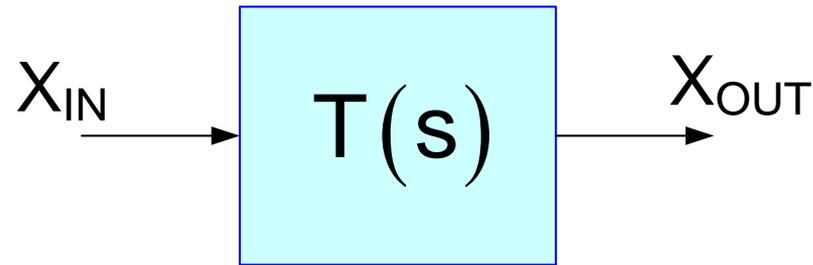


$$|T(s)| = H \frac{\omega_0^2}{s^2 + s \left(\frac{\omega_0}{Q} \right) + \omega_0^2}$$


$$BW = \omega_B - \omega_A \neq \frac{\omega_0}{Q}$$

$$\omega_{PEAK} \neq \omega_0$$

Consider 2nd Order Lowpass Biquads

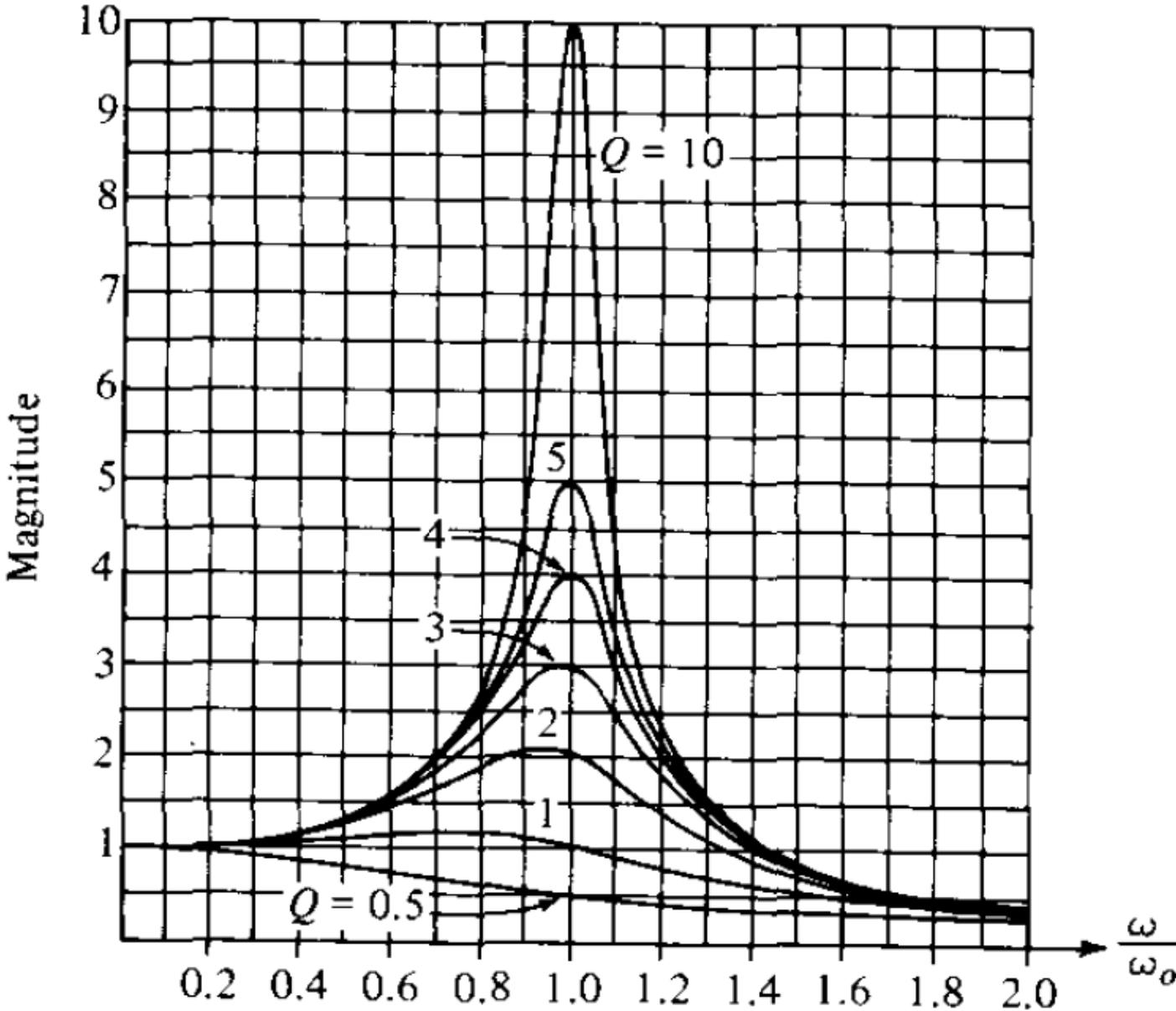


Example: 2nd Order +KRC Lowpass

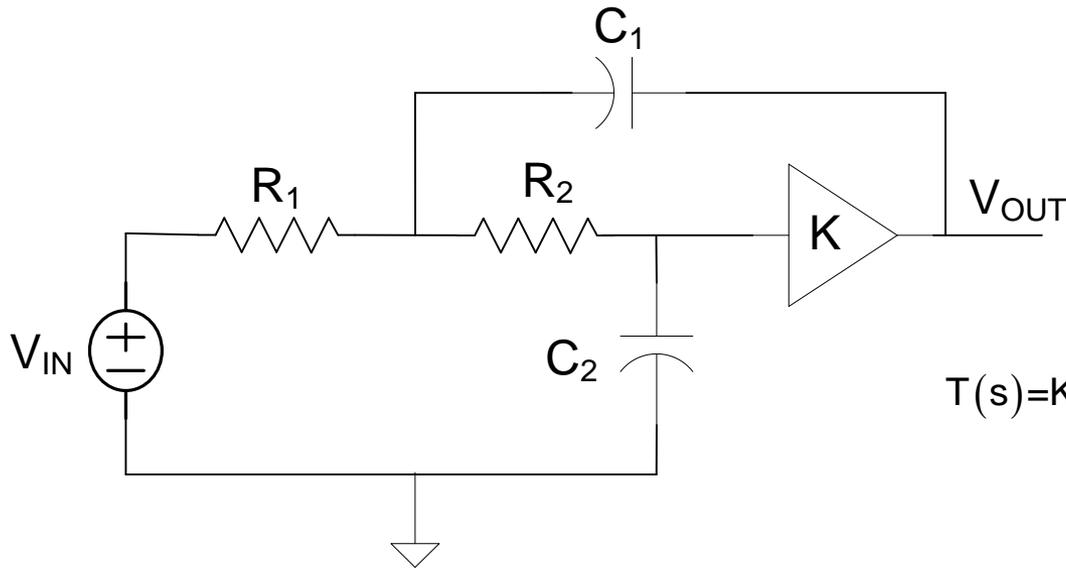

$$T(s) = K \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{s^2 + s \left[\frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$

Equal R, Equal C

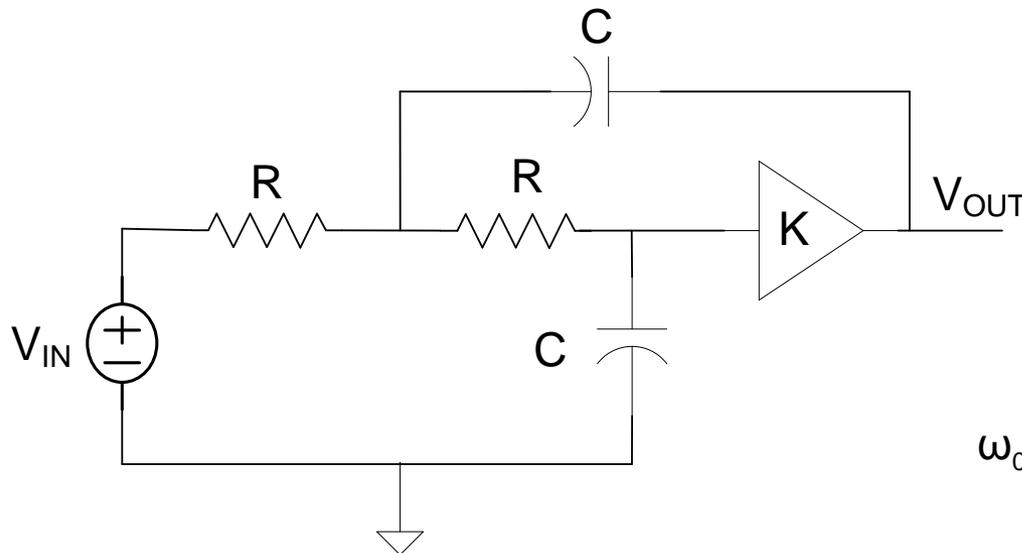


$$T(s) = K \frac{1}{R^2 C^2} \frac{1}{s^2 + s \left[\frac{(3-K)}{RC} \right] + \frac{1}{R^2 C^2}}$$

$$\omega_0 = \frac{1}{RC}$$

$$Q = \frac{1}{3-K}$$

Example: 2nd Order +KRC Lowpass



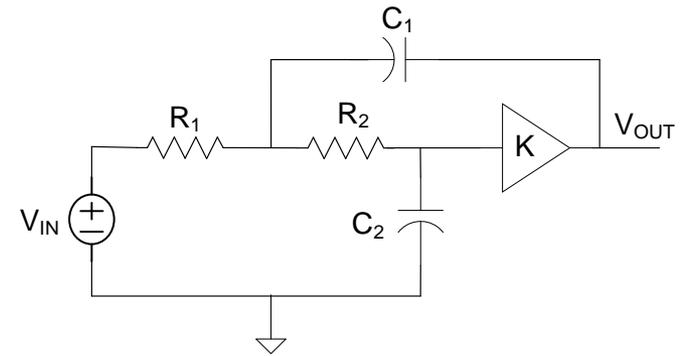


Equal R, K=1

$$T(s) = K \frac{1}{s^2 + s \left[\frac{2}{RC_1} \right] + \frac{1}{R^2 C_1 C_2}}$$

$$\omega_0 = \frac{1}{R \sqrt{C_1 C_2}}$$

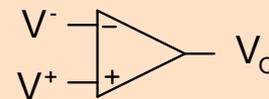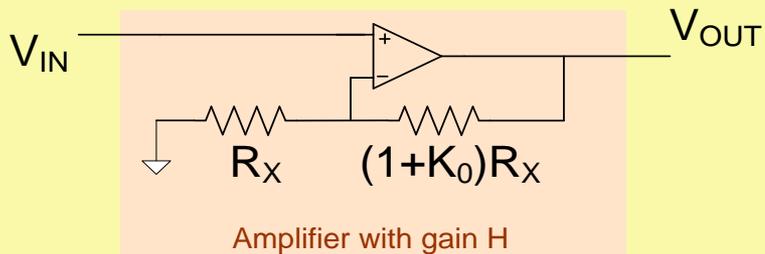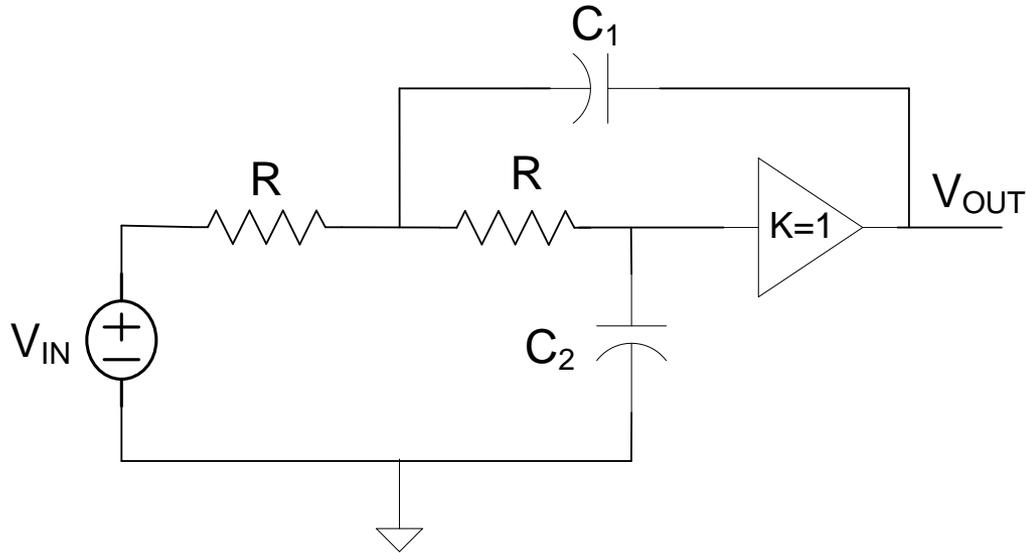
$$Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}}$$



$$A(s) = \frac{V_o}{V^+ - V^-} = \frac{GB}{s}$$

$$K(s) = \frac{K_0}{1 + \frac{K_0}{GB} s}$$


Example: 2nd Order +KRC Lowpass

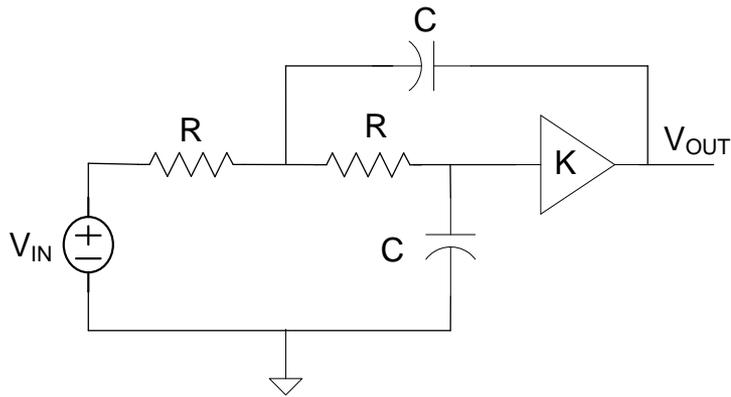



Equal R, Equal C

consider

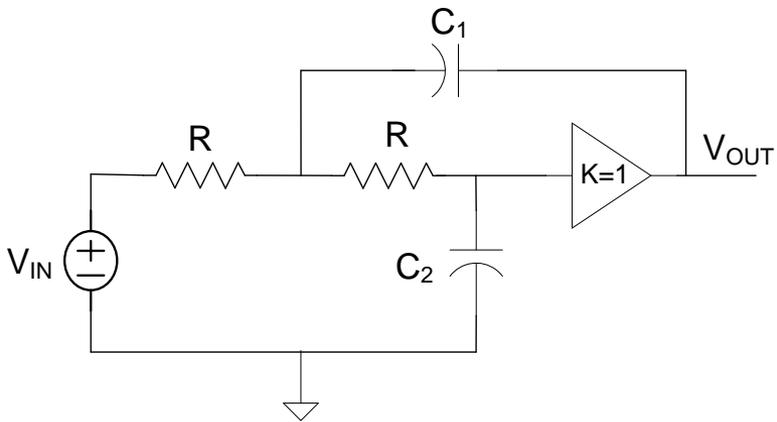
$$\bullet \longleftrightarrow GB_n = \frac{GB}{\omega_0} = .01$$




Equal R, K=1

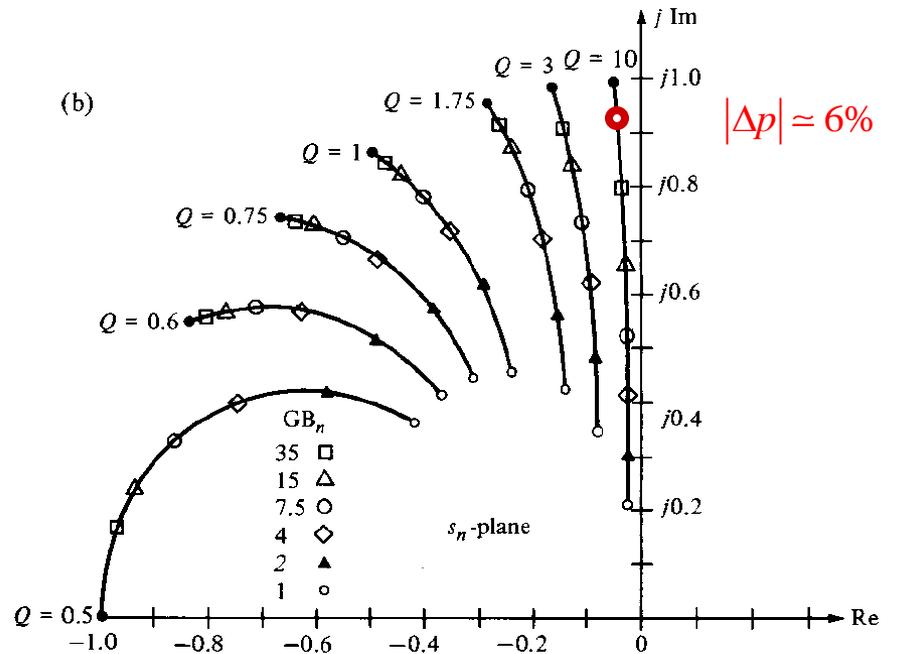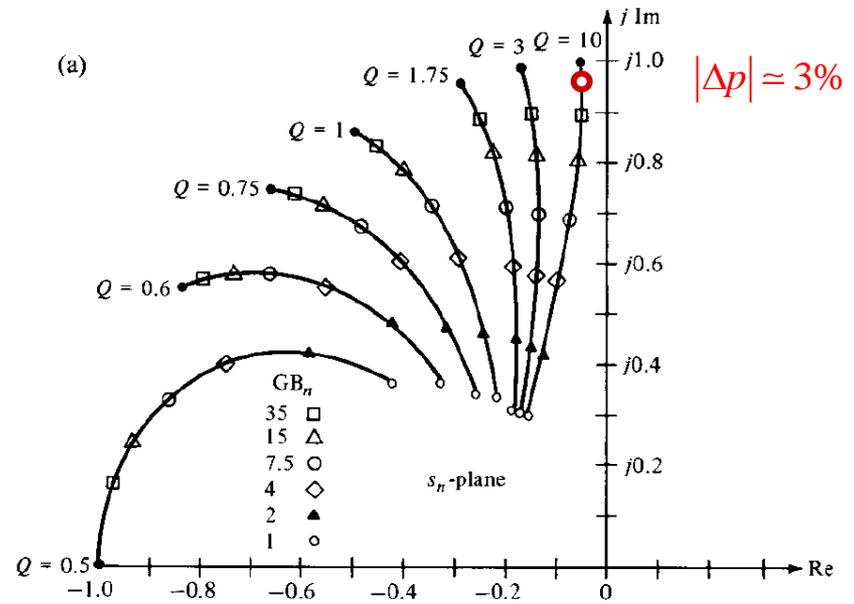

Example: 2nd Order -KRC Lowpass

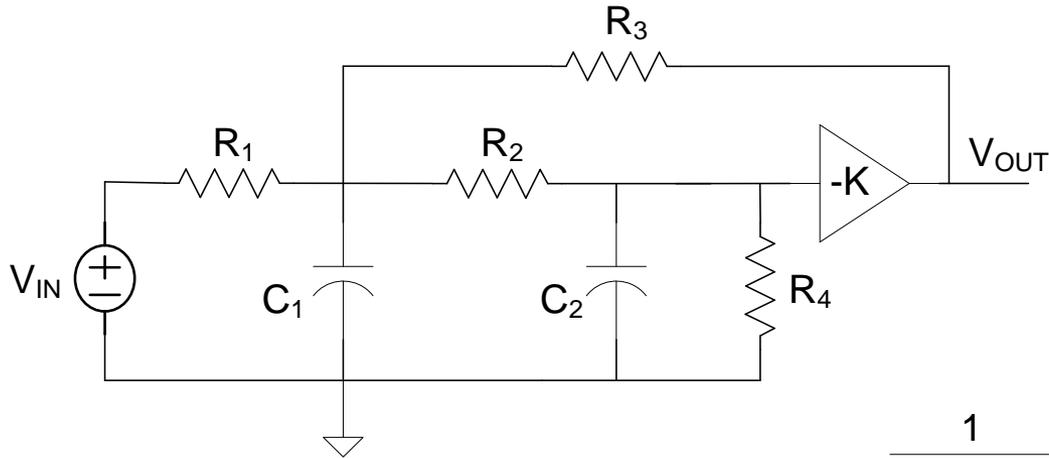
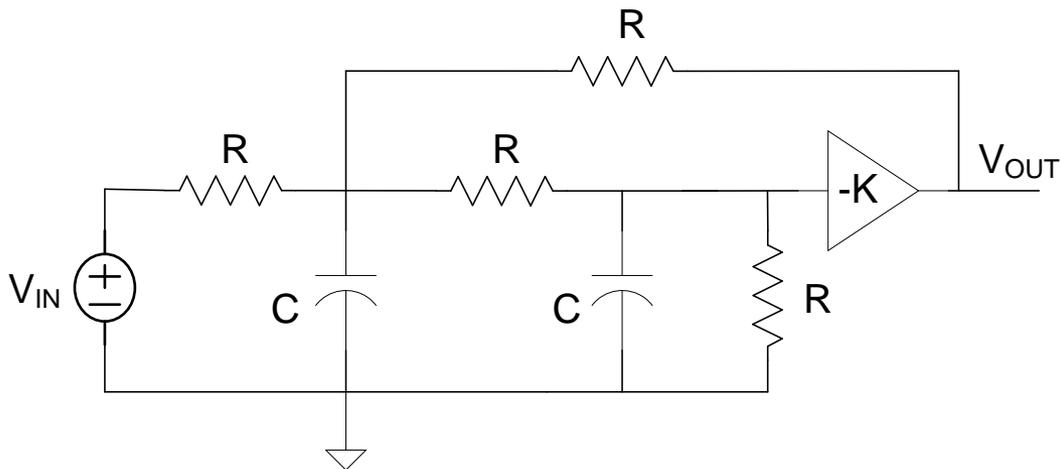
$$T(s) = -K \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{s^2 + s \left[\frac{1}{R_1 C_1} \left(1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left(1 + \frac{C_2}{C_1} \right) \right] + \left[\frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2} \right]}$$




Equal R, Equal C

$$T(s) = -K \frac{1}{R^2 C^2} \frac{1}{s^2 + s \left[\frac{5}{RC} \right] + \left[\frac{5+K}{R^2 C^2} \right]}$$



$$\omega_0 = \frac{\sqrt{5+K}}{RC}$$

$$Q = \frac{\sqrt{5+K}}{5}$$

Example: 2nd Order -KRC Lowpass

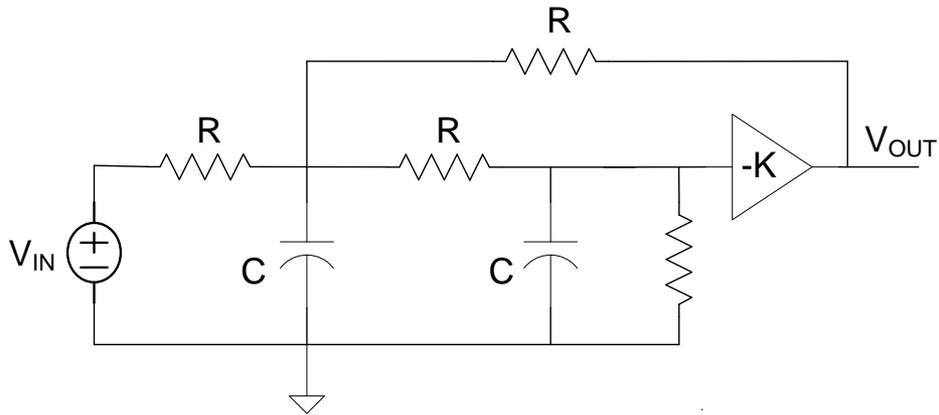

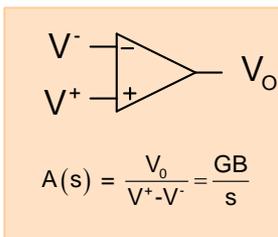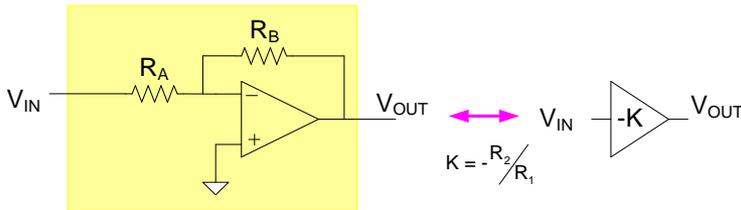
$$\omega_0 = \frac{\sqrt{5+K}}{RC} \quad Q = \frac{\sqrt{5+K}}{5}$$




$$K(s) = -\frac{K_0}{1 + \frac{(1+K_0)s}{GB}}$$

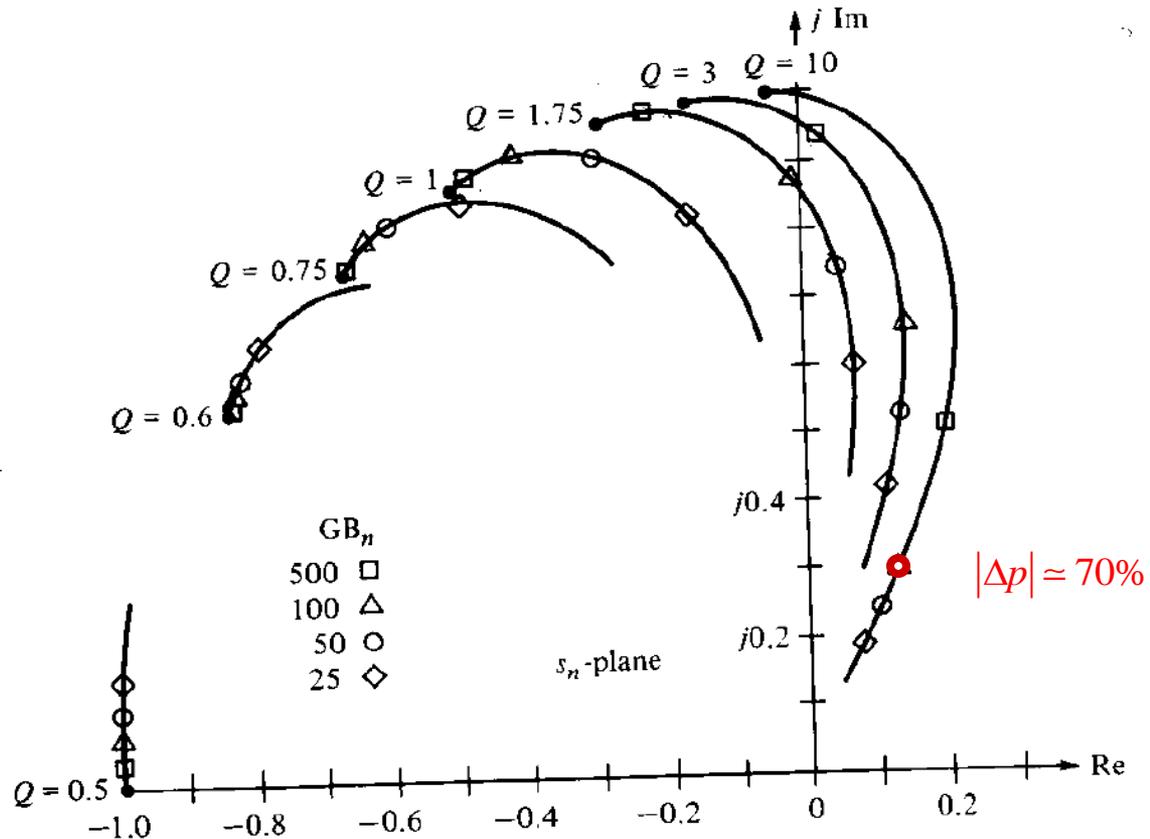consider $\bullet \longleftrightarrow GB_n = \frac{GB}{\omega_0} = .01$




Poles "move" towards RHP as GB degrades
Even very large values of GB will cause instability

Example: 2nd Bridged-T FB Lowpass

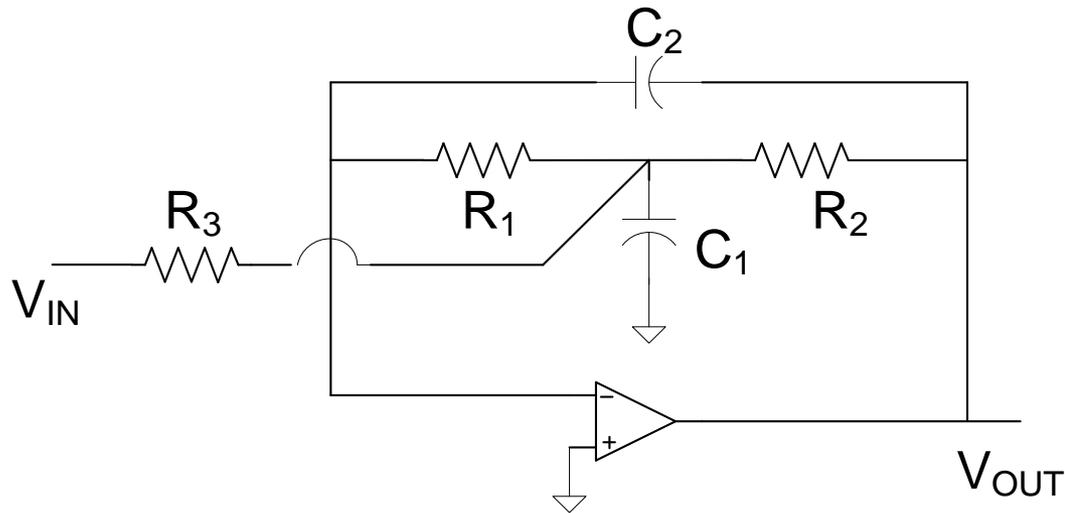
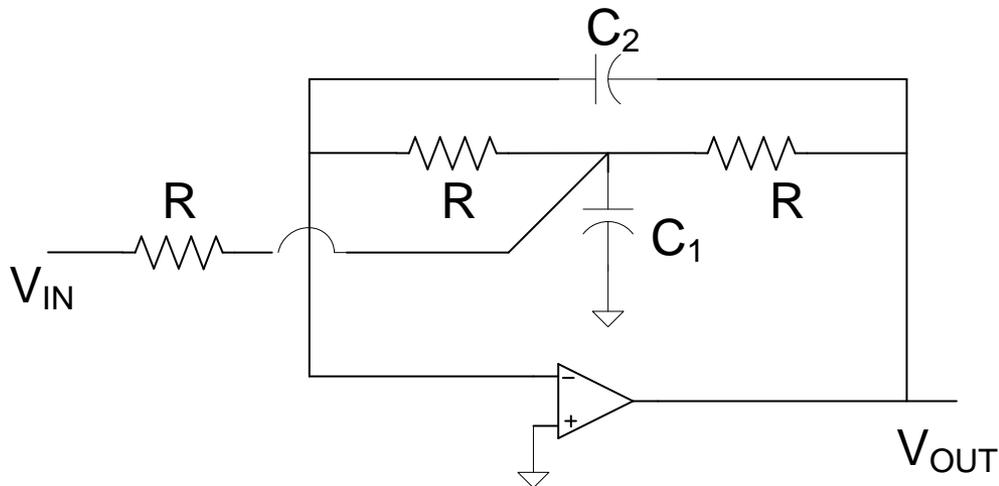
$$T(s) = - \frac{\frac{1}{R_2 R_3 C_1 C_2}}{s^2 + s \frac{1}{C_1} \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$




Equal R

$$T(s) = - \frac{\frac{1}{R^2 C_1 C_2}}{s^2 + s \left(\frac{3}{RC_1} \right) + \frac{1}{R^2 C_1 C_2}}$$

$$\omega_0 = \frac{1}{R \sqrt{C_1 C_2}} \quad Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}}$$



Example: 2nd Bridged-T FB Lowpass

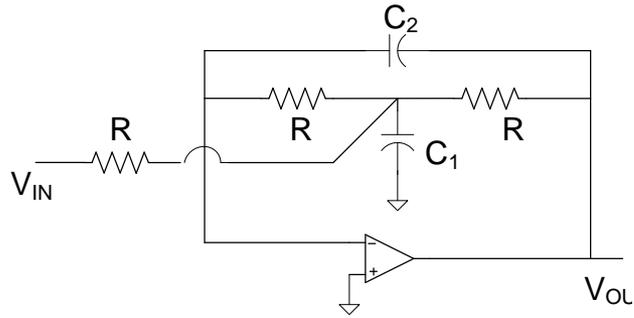


$$\omega_0 = \frac{1}{R\sqrt{C_1 C_2}} \quad Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}}$$

consider

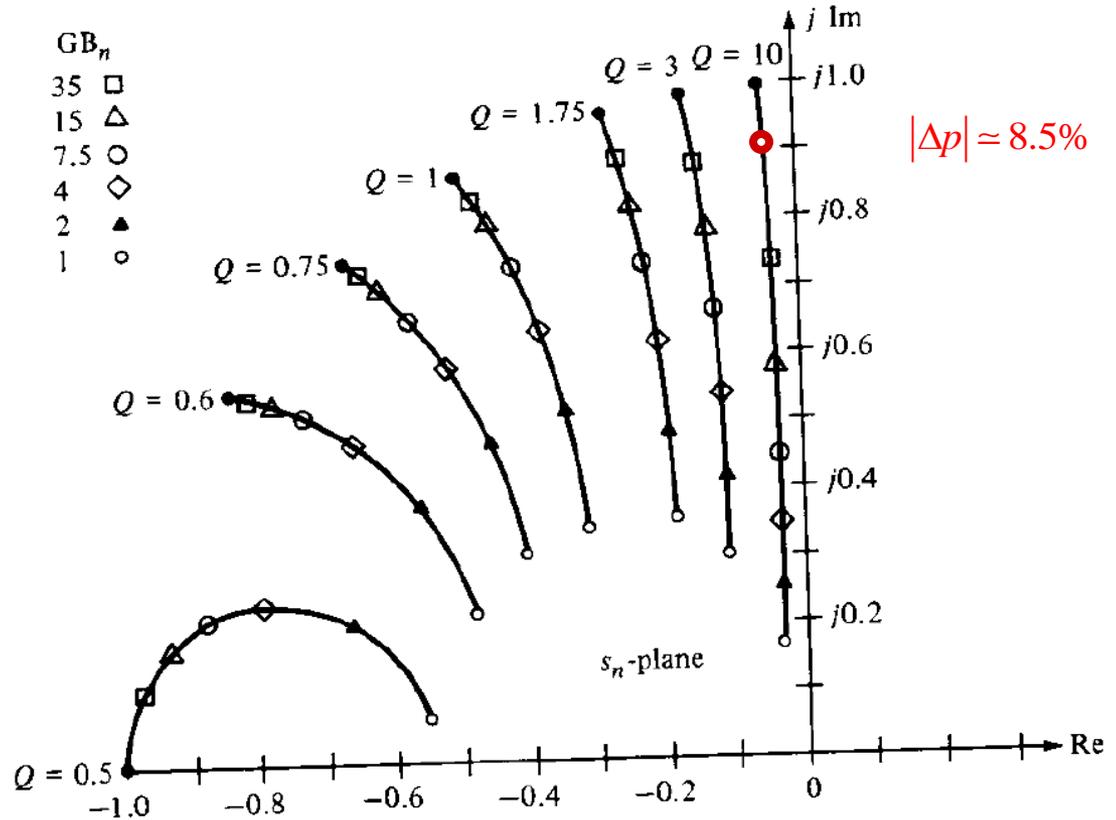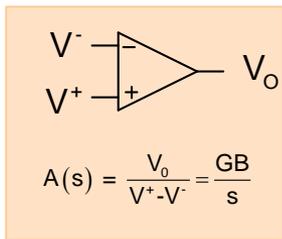
$$\bullet \longleftrightarrow GB_n = \frac{GB}{\omega_0} = .01$$



Example: 2nd Two-Integrator-Loop Lowpass

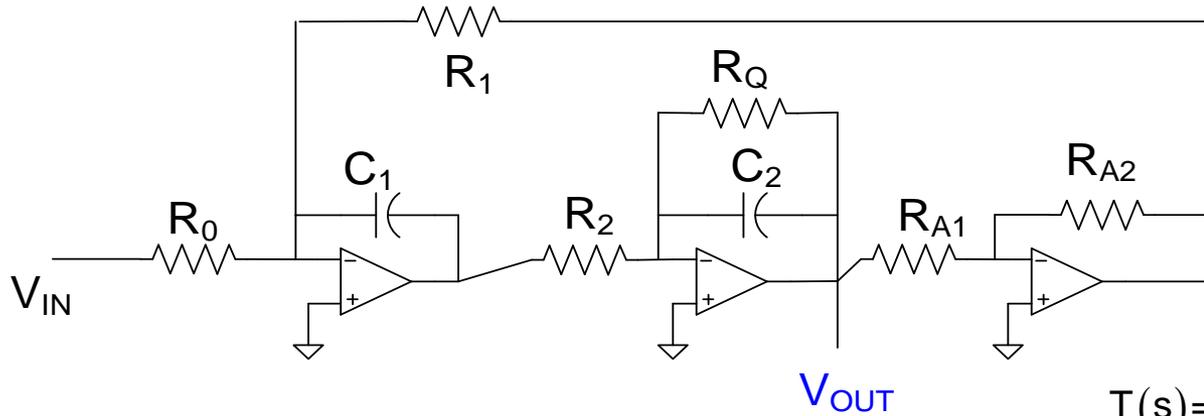
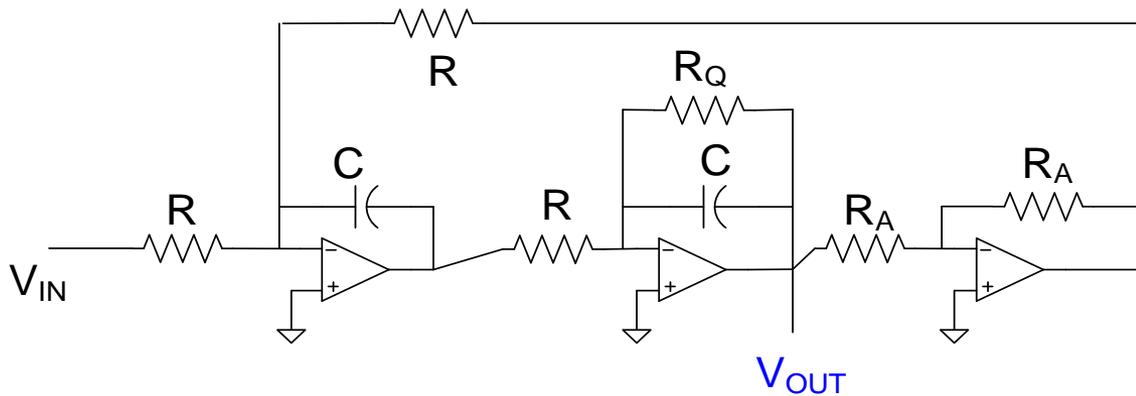
$$T(s) = - \frac{1}{R_0 R_2 C_1 C_2} \frac{1}{s^2 + s \left(\frac{1}{C_2 R_Q} \right) + \frac{R_{A2}/R_{A1}}{R_1 R_2 C_1 C_2}}$$




Equal R, Equal C
(except R_Q)

$$T(s) = - \frac{1}{R^2 C^2} \frac{1}{s^2 + s \left(\frac{1}{C R_Q} \right) + \frac{1}{R^2 C^2}}$$



$$\omega_0 = \frac{1}{RC} \quad Q = \frac{R_Q}{R}$$

Example: 2nd Two-Integrator-Loop Lowpass

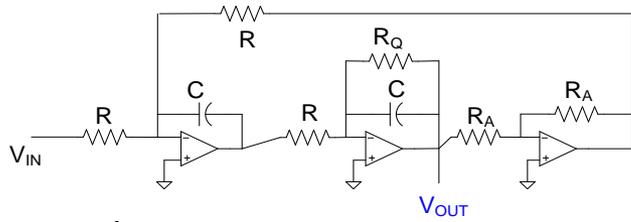








$$\omega_0 = \frac{1}{RC} \quad Q = \frac{R_Q}{R}$$

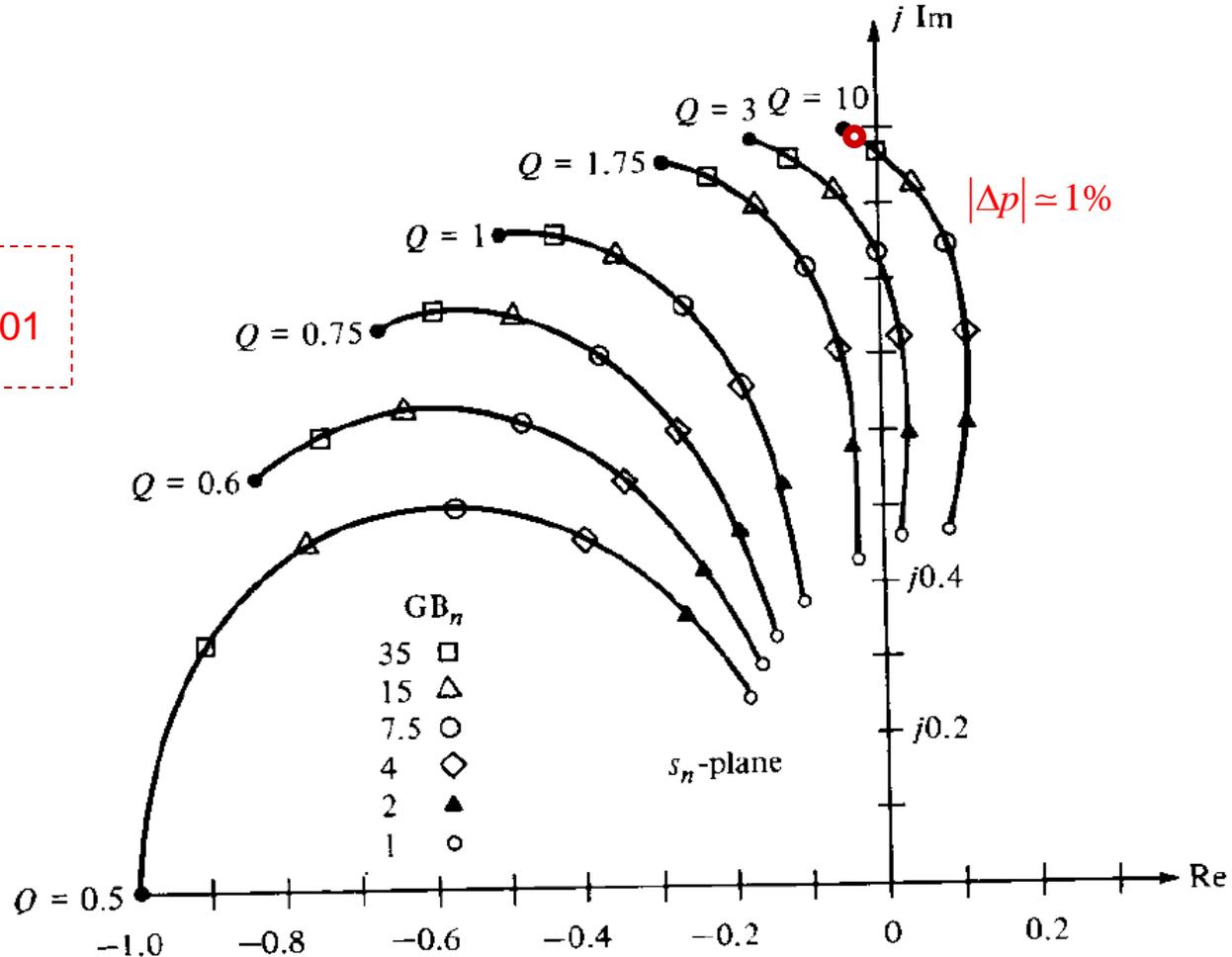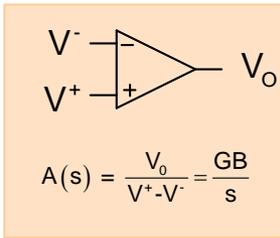consider $\bullet \longleftrightarrow GB_n = \frac{GB}{\omega_0} = .01$




Poles "move" towards RHP as GB degrades

Comparison of 4 second-order LP filters

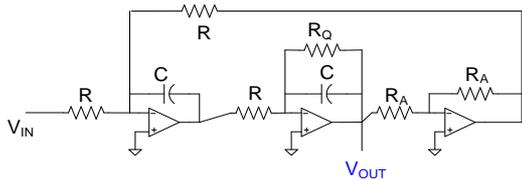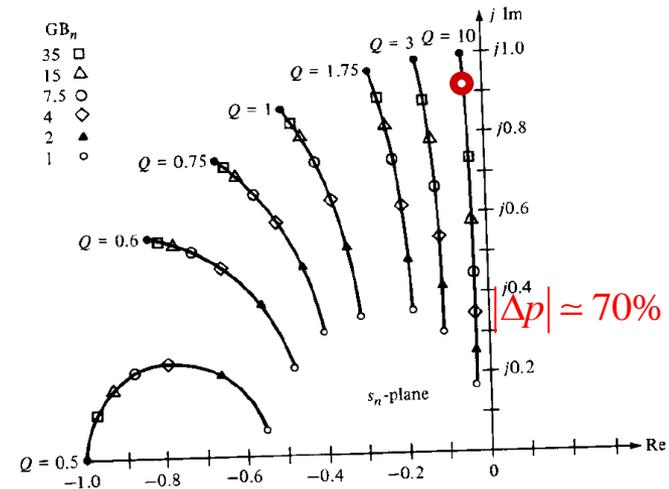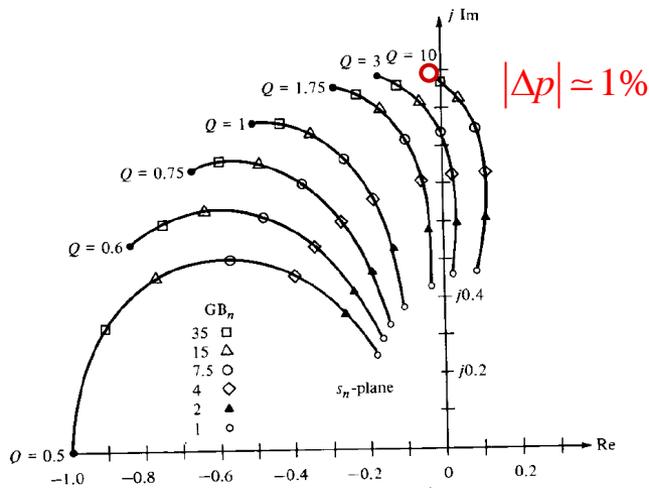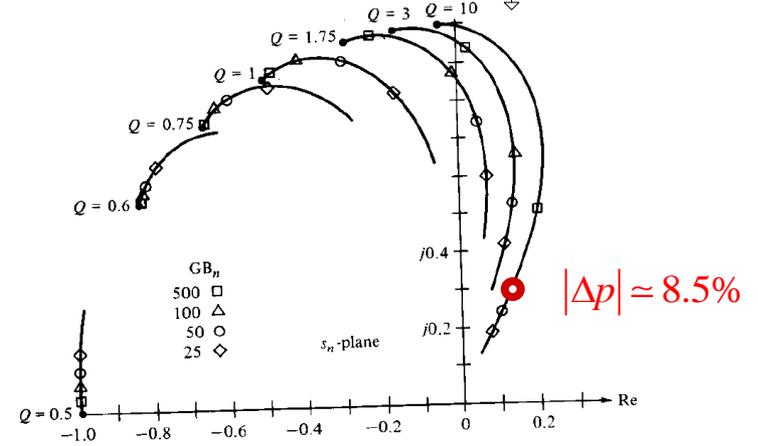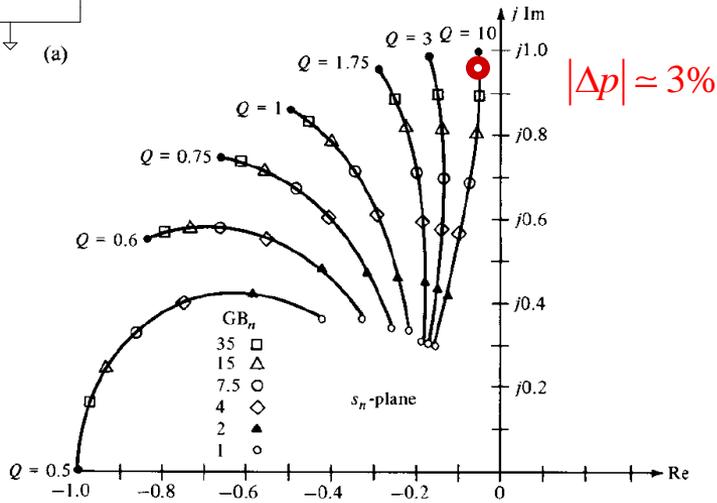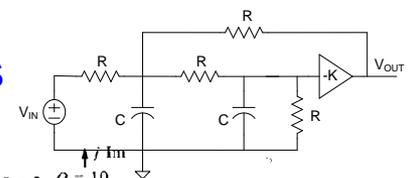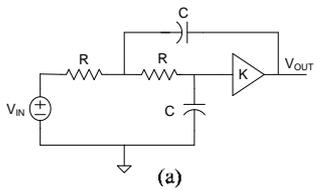

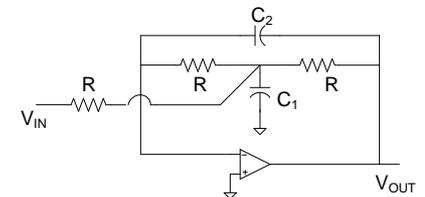consider $\bullet \longleftrightarrow GB_n = \frac{GB}{\omega_0} = .01$



Some Observations

- Seemingly similar structures have dramatically different sensitivity to frequency response of the Op Amp
- Critical to have enough GB if filter is to perform as desired
- Performance strongly affected by both magnitude and direction of pole movement
- Some structures appear to be totally impractical – at least for larger Q
- Different use of the Degrees of Freedom produces significantly different results

Sensitivity analysis is useful for analytical characterization of the performance of a filter

