





# EE 508

## Lecture 20




### Sensitivity Functions

- Comparison of Filter Structures
- Performance Prediction
- Design Characterization

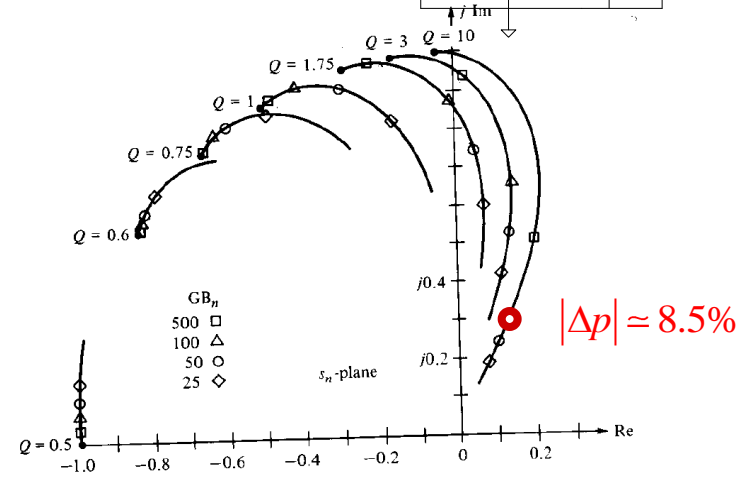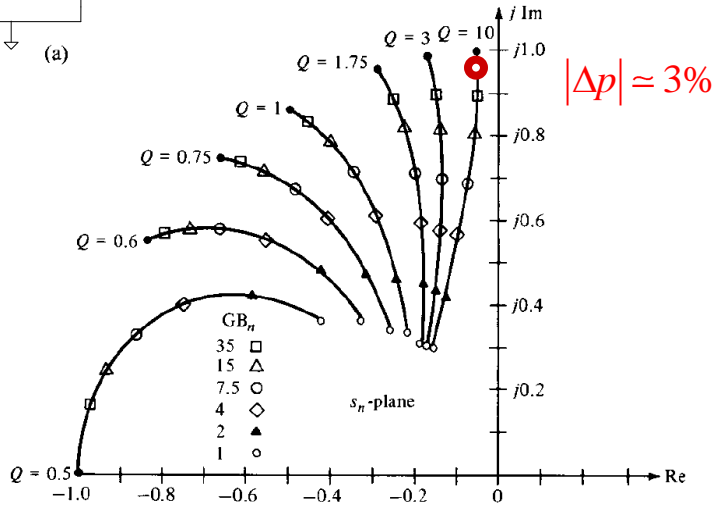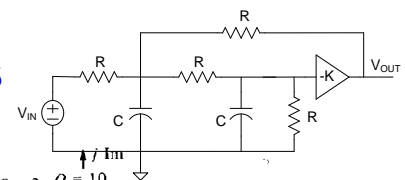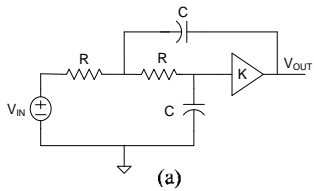
# Comparison of 4 second-order LP filters




Review from last time

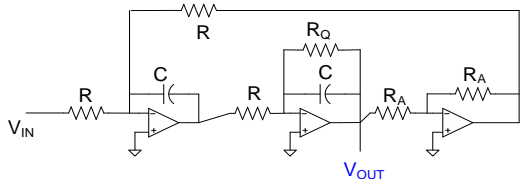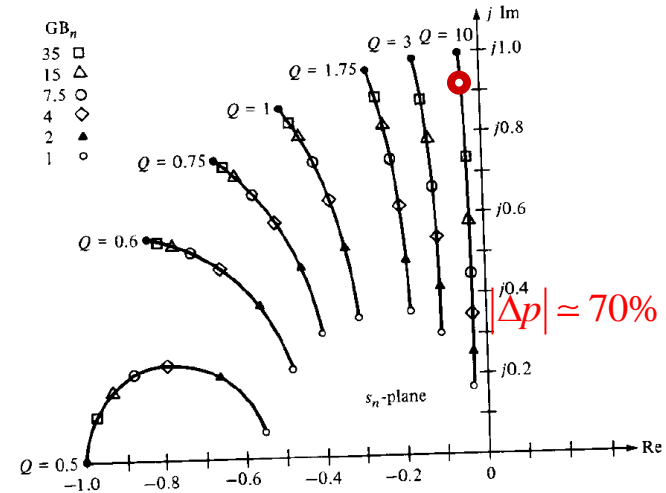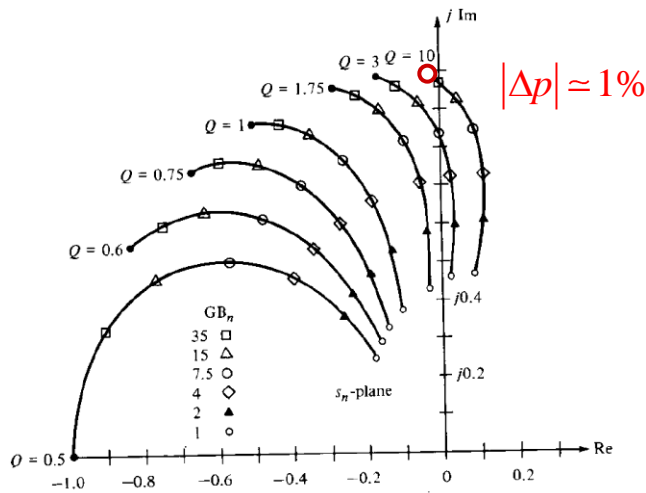

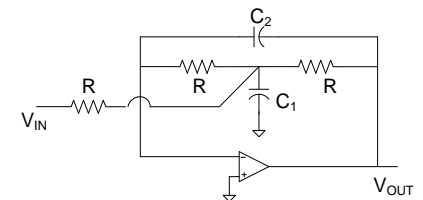
consider  $\bullet \longleftrightarrow GB_n = \frac{GB}{\omega_0} = .01$



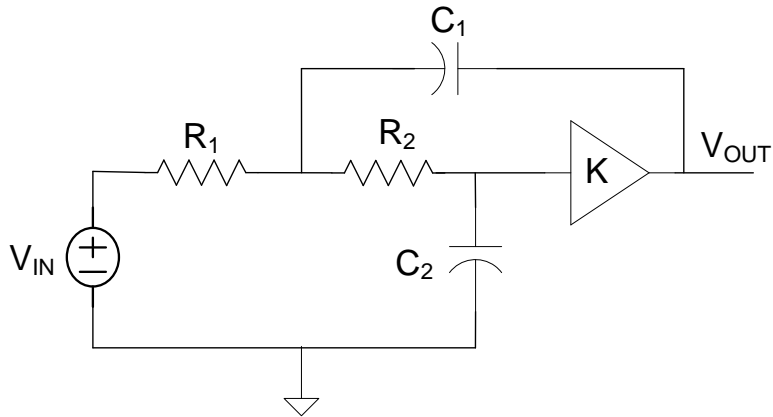
What causes the dramatic differences in performance between these two structures?  
 How can the performance of different structures be compared in general?



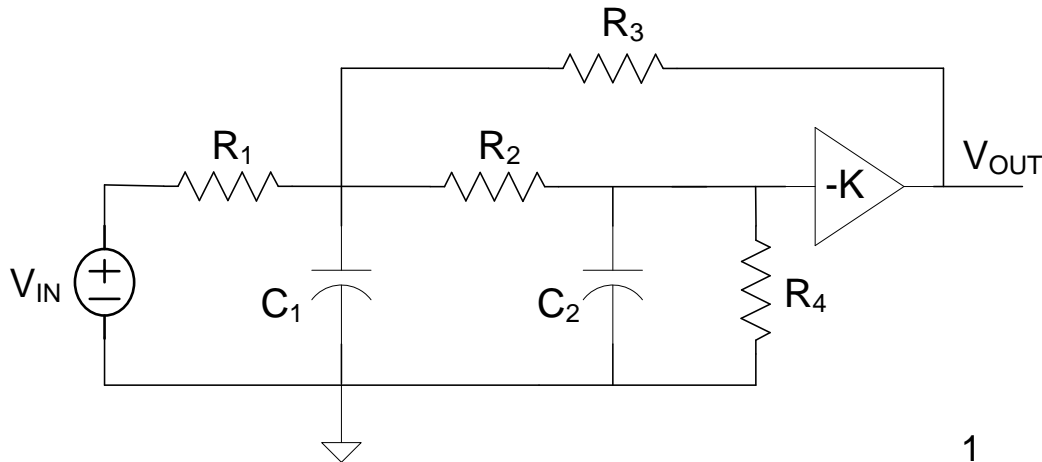
$$T(s) = K \frac{1}{s^2 + s \left[ \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$




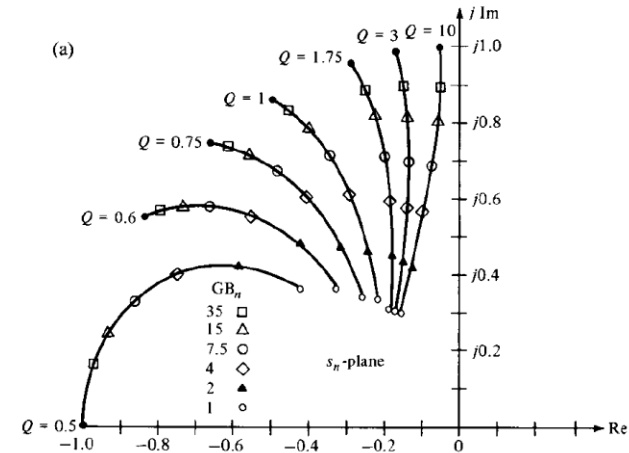
$$T(s) = -K \frac{1}{s^2 + s \left[ \frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right) \right] + \left[ \frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2} \right]}$$



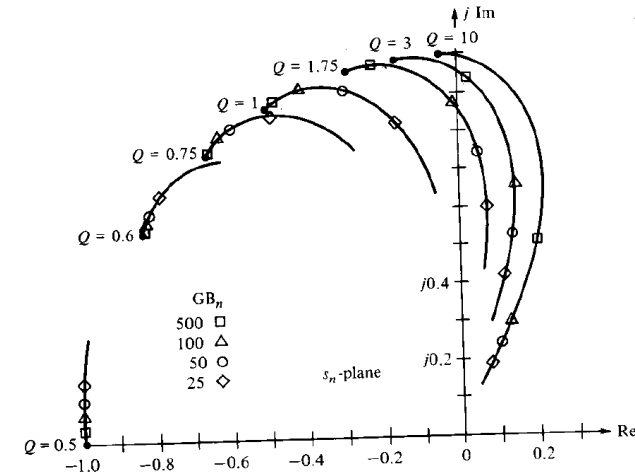Equal R, Equal C, Q=10 Pole Locus vs GB<sub>N</sub>



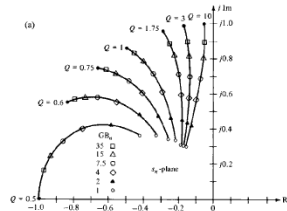
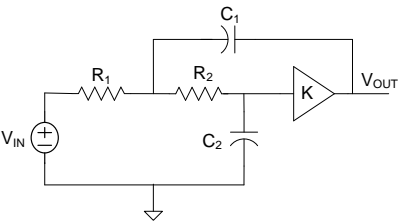
# How can the performance of different structures be compared in general?



$$T(s) = K \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{s^2 + s \left[ \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$Q = \frac{1}{\sqrt{\frac{R_2 C_2}{R_1 C_1}} + \sqrt{\frac{R_1 C_2}{R_2 C_1}} + (1-K) \sqrt{\frac{R_1 C_1}{R_2 C_2}}}$$
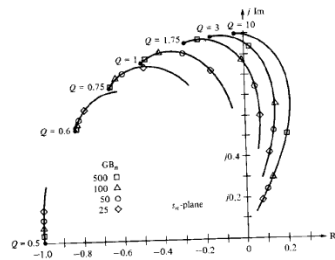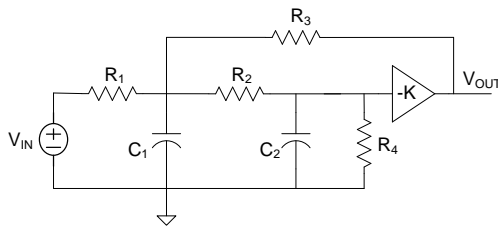
$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$



$$T(s) = -K \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{s^2 + s \left[ \frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right) \right] + \left[ \frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2} \right]}$$



$$\omega_0 = \sqrt{\frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2}}$$

$$Q = \sqrt{\frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2} \frac{1}{\frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right)}}$$

- Equations for key performance parameters give little insight into the differences
- Expressions for key performance parameters quite complicated



# How can the performance of different structures be compared in general?

## Equal R, Equal C implementations

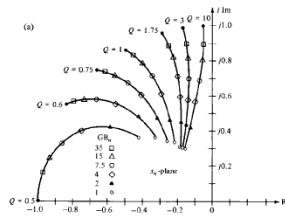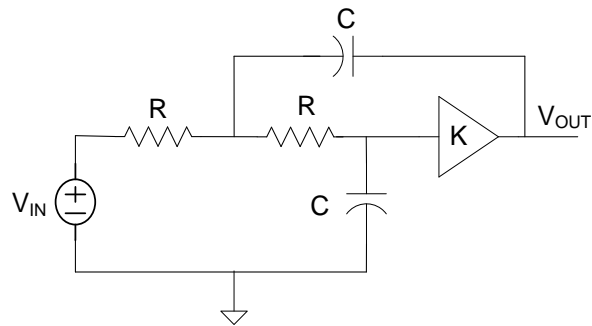

$$T(s) = K \frac{1}{R^2 C^2} \frac{1}{s^2 + s \left[ \frac{(3-K)}{RC} \right] + \frac{1}{R^2 C^2}}$$
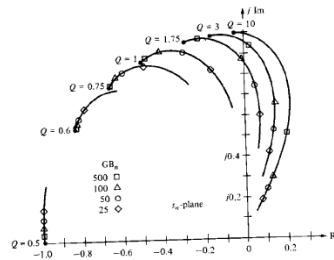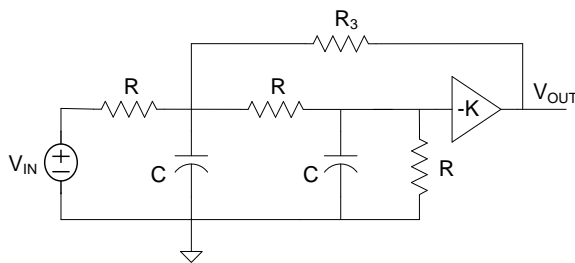
$$Q = \frac{1}{3-K} \quad \omega_0 = \frac{1}{RC}$$





$$T(s) = -K \frac{1}{R^2 C^2} \frac{1}{s^2 + s \left[ \frac{5}{RC} \right] + \left[ \frac{5+K}{R^2 C^2} \right]}$$

$$Q = \frac{\sqrt{5+K}}{5} \quad \omega_0 = \frac{\sqrt{5+K}}{RC}$$


- Analytical expressions for  $\omega_0$  and  $Q$  much simpler
- Equations for key performance parameters give little insight into the differences
- Effects of individual components is obscured in these expressions
- GB effects absent in this analytical formulation

# Modeling of the Amplifiers

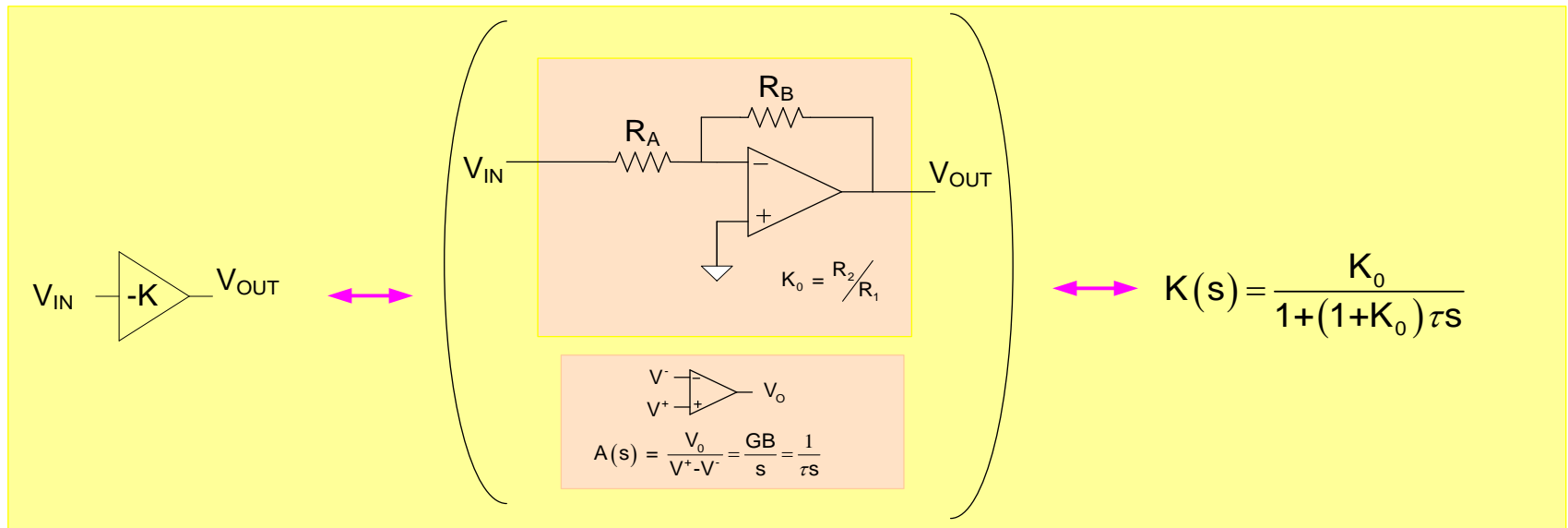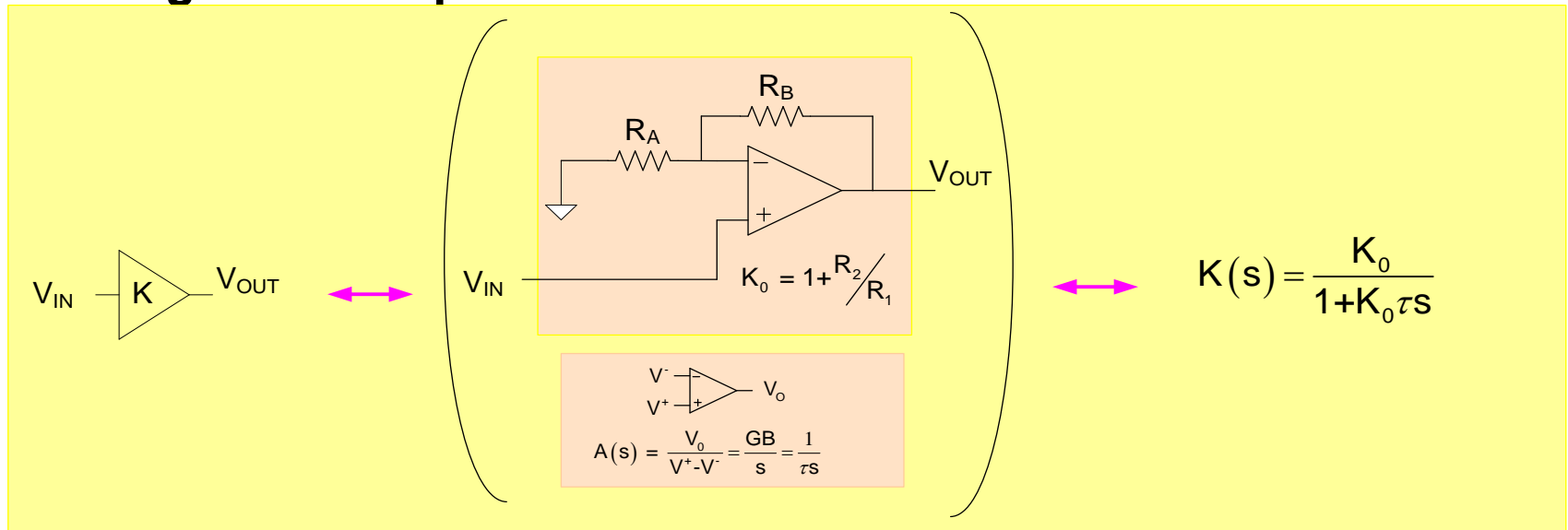

**Different implementations of the amplifiers are possible**  
**Have used the op amp time constant in these models  $\tau = GB^{-1}$**

## GB effects in +KRC Lowpass Filter

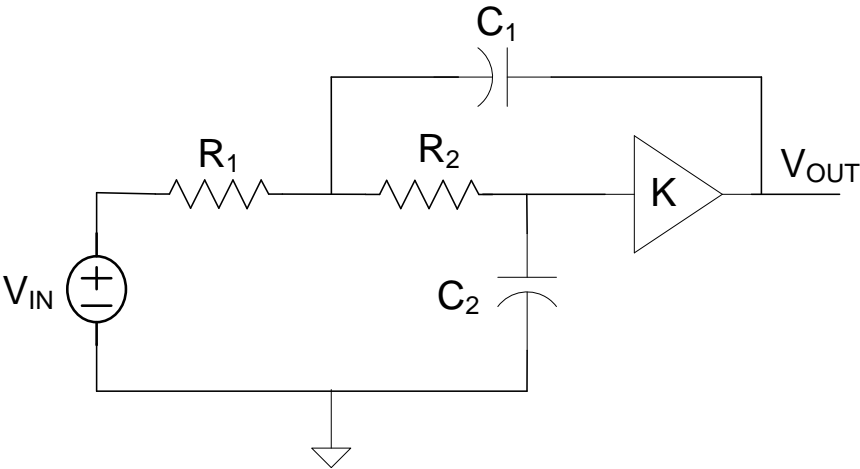

$$T(s) = K \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{s^2 + s \left[ \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$K(s) = \frac{K_0}{1 + K_0 \tau s}$$

$$T(s) = \frac{\frac{K_0}{R_1 R_2 C_1 C_2}}{s^2 + s \left[ \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{(1-K_0)}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2} + K_0 \tau s \left( s^2 + s \left[ \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2} \right)}$$

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$Q = \frac{1}{\sqrt{\frac{R_2 C_2}{R_1 C_1} + \sqrt{\frac{R_1 C_2}{R_2 C_1}} + (1-K) \sqrt{\frac{R_1 C_1}{R_2 C_2}}}}$$

$\omega_0$  and  $Q$  in these expressions are for ideal op amp


$$T(s) = \frac{K_0 \omega_0^2}{s^2 + s \left[ \frac{\omega_0}{Q} \right] + \omega_0^2 + K_0 \tau s \left( s^2 + s \left[ \frac{\omega_0}{Q} \left( 1 + K_0 Q \sqrt{\frac{R_1 C_1}{R_2 C_2}} \right) \right] + \omega_0^2 \right)}$$

$$T(s) = \frac{\frac{K_0}{R_1 R_2 C_1 C_2}}{D_1(s) + K_0 \tau s (D_{RC0}(s))}$$

$D_1(s)$  is the  $D(s)$  if the OA is ideal

$D_{RC0}(s)$  is the  $D(s)$  of RC circuit with  $K=0$

# GB effects in -KRC Lowpass Filter

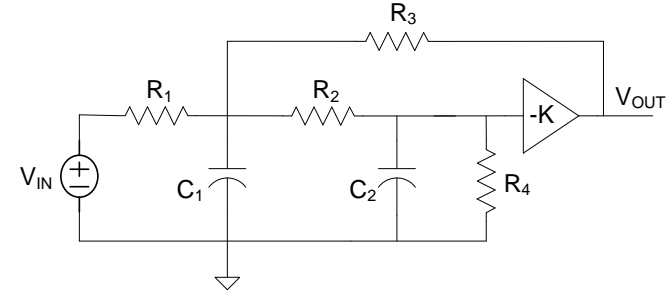

$$T(s) = -K \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{s^2 + s \left[ \frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right) \right] + \left[ \frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2} \right]}$$

$$K(s) = \frac{K_0}{1 + (1 + K_0) \tau s}$$

$$Q = \sqrt{\frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2} \frac{1}{\frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right)}}$$

$$\omega_0 = \sqrt{\frac{1 + (R_1/R_3)(1+K) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2}}$$


$\omega_0$  and  $Q$  in these expressions are for ideal op amp

$$T(s) = -K_0 \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{\left( s^2 + s \left[ \frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right) \right] + \left[ \frac{1 + (R_1/R_3)(1+K_0) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2} \right] \right) + \tau s (1+K_0) \left( s^2 + s \left[ \frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right) \right] + \left[ \frac{1 + (R_1/R_3) + (R_1/R_4)(1 + (R_2/R_3) + (R_2/R_1))}{R_1 R_2 C_1 C_2} \right] \right)}$$


$$T(s) = \frac{-K_0}{D_1(s) + (1+K_0) \tau s (D_{RC0}(s))}$$


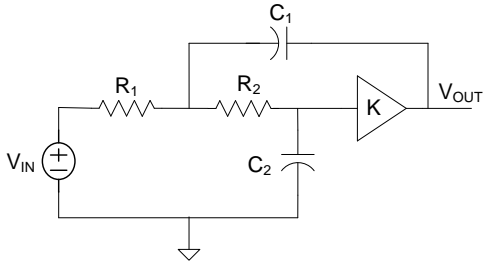
## GB effects in KRC and -KRC Lowpass Filter


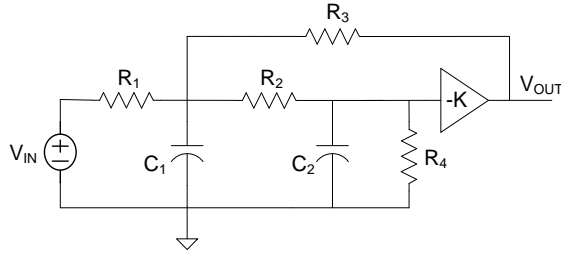
$$T(s) = \frac{K_0 \omega_0^2}{s^2 + s \left[ \frac{\omega_0}{Q} \right] + \omega_0^2 + K_0 \tau s \left( s^2 + s \left[ \frac{\omega_0}{Q} \left( 1 + K_0 Q \sqrt{\frac{R_1 C_1}{R_2 C_2}} \right) \right] + \omega_0^2 \right)}$$



$$T(s) = \frac{K_0}{R_1 R_2 C_1 C_2 D_I(s) + K_0 \tau s (D_{RCO}(s))}$$


$$T(s) = -K_0 \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{\left( s^2 + s \left[ \frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right) \right] + \left[ \frac{1 + (R_1/R_3)(1+K_0) + (R_1/R_4)(1+(R_2/R_3)+(R_2/R_1))}{R_1 R_2 C_1 C_2} \right] \right)} + \tau s (1+K_0) \left( s^2 + s \left[ \frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right) \right] + \left[ \frac{1 + (R_1/R_3) + (R_1/R_4)(1+(R_2/R_3)+(R_2/R_1))}{R_1 R_2 C_1 C_2} \right] \right)}$$

$$T(s) = \frac{-K_0}{R_1 R_2 C_1 C_2 D_I(s) + (1+K_0) \tau s (D_{RCO}(s))}$$

All linear performance effects can be obtained from this formulation

Op amp introduced an additional pole and moves the desired poles
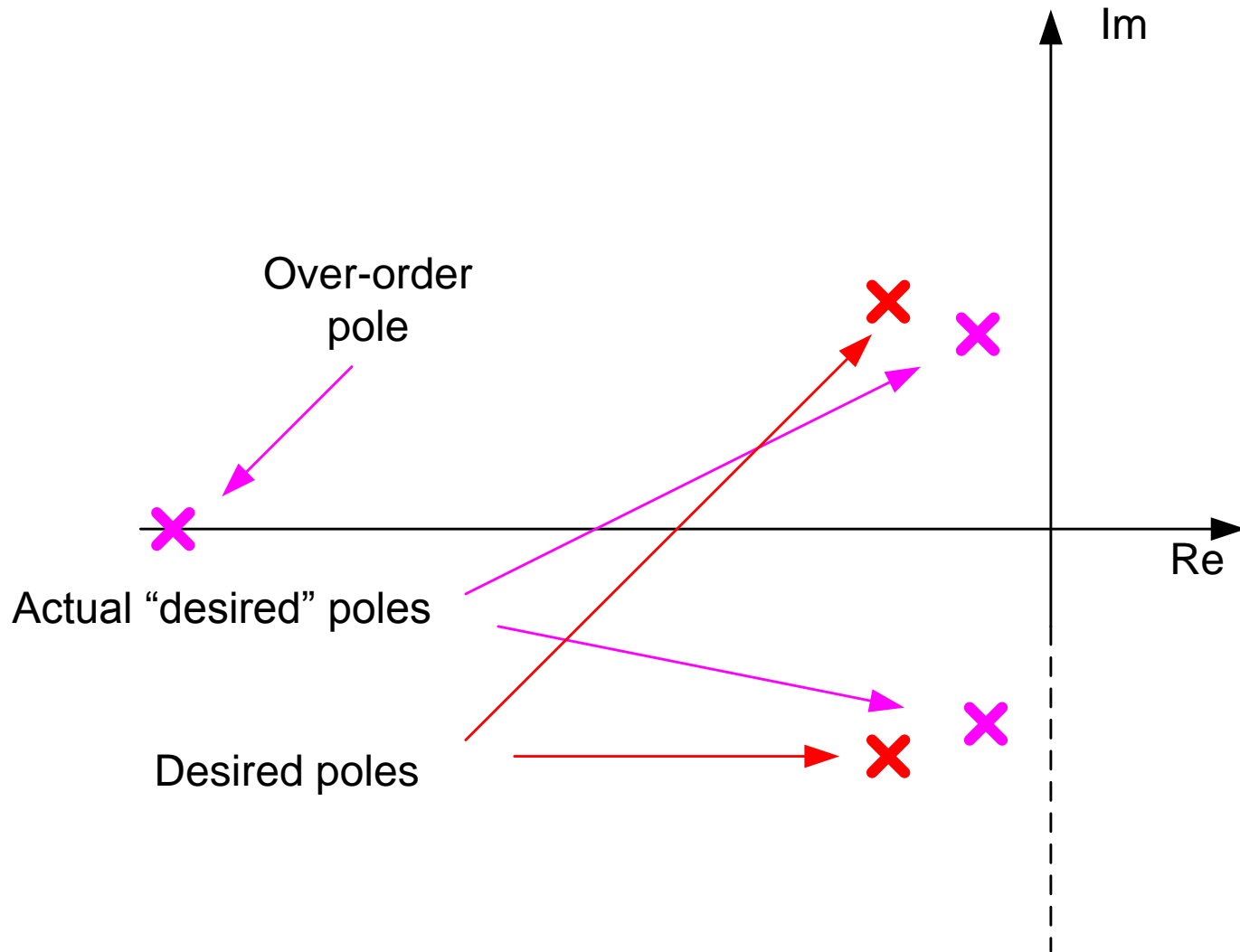
# Effects of GB on poles of KRC and -KRC Lowpass Filters



## GB effects in KRC and -KRC Lowpass Filter

$$T(s) = \frac{K_0 \omega_0^2}{s^2 + s \left[ \frac{\omega_0}{Q} \right] + \omega_0^2 + K_0 \tau s \left( s^2 + s \left[ \frac{\omega_0}{Q} \left( 1 + K_0 Q \sqrt{\frac{R_1 C_1}{R_2 C_2}} \right) \right] + \omega_0^2 \right)}$$

$$T(s) = -K_0 \frac{\frac{1}{R_1 R_2 C_1 C_2}}{\left( s^2 + s \left[ \frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right) \right] + \left[ \frac{1 + (R_1/R_3)(1+K_0) + (R_1/R_4)(1+(R_2/R_3)+(R_2/R_1))}{R_1 R_2 C_1 C_2} \right] \right) + \tau s (1+K_0) \left( s^2 + s \left[ \frac{1}{R_1 C_1} \left( 1 + \frac{R_1}{R_3} \right) + \frac{1}{R_4 C_2} + \frac{1}{R_2 C_2} \left( 1 + \frac{C_2}{C_1} \right) \right] + \left[ \frac{1 + (R_1/R_3) + (R_1/R_4)(1+(R_2/R_3)+(R_2/R_1))}{R_1 R_2 C_1 C_2} \right] \right)}$$

- Analytical expressions for  $\omega_0$ ,  $Q$ , poles, zeros, and other key parameters are unwieldy in these circuits and as bad or worse in many other circuits
- Sensitivity metrics give considerable insight into how filters perform and widely used to assess relative performance
- Need sensitivity characterization of real numbers as well as complex quantities such as poles and zeros
- **Since analytical expressions for key parameters are unwieldy in even simple circuits, obtaining expressions for the purpose of calculating sensitivity appears to be a formidable task !**

# Sensitivity Characterization of Filter Structures

Let  $F$  be a filter characteristic of interest

$F$  might be  $\omega_0$  or  $Q$  of a pole or zero, a band edge, a peak frequency, a BW,  $T(s)$ ,  $|T(j\omega)|$ , a coefficient in  $T(s)$ , etc

Can express  $F$  in terms of all components and model parameters as

$$F=f(R_1, \dots, R_{k1}, C_1, \dots, C_{k2}, L_{11}, \dots, L_{lk3}, T_1, \dots, T_{k4}, W_1, \dots, W_{k5}, L_1, \dots, L_{k5}, \dots)$$

$$F=f(x_1, x_2, \dots, x_k)$$

The differential  $dF$  of the multivariate function  $F$  can be expressed as

$$\begin{aligned}dF &= \frac{\partial F}{\partial R_1} dR_1 + \frac{\partial F}{\partial R_2} dR_2 + \dots + \frac{\partial F}{\partial R_{k1}} dR_{k1} \\ &+ \frac{\partial F}{\partial C_1} dC_1 + \frac{\partial F}{\partial C_2} dC_2 + \dots + \frac{\partial F}{\partial C_{k2}} dC_{k2} \\ &+ \dots\end{aligned}$$

$$dF = \sum_{i=1}^k \frac{\partial F}{\partial x_i} dx_i$$

Define the standard sensitivity function as

$$S_{x}^f = \frac{\partial f}{\partial x} \bullet \frac{x}{f}$$

$S_{x}^f$  Is widely used except when  $x$  or  $f$  assume extreme values of 0 or  $\infty$

Define the derivative sensitivity function as

$$D_{x}^f = \frac{\partial f}{\partial x}$$

$D_{x}^f$  Is more useful when  $x$  or  $f$  ideally assume extreme values of 0 or  $\infty$

Consider the normalized differential  $\frac{dF}{F}$

$$\frac{dF}{F} \approx \frac{\Delta F}{F}$$

This approximates the percent change in F due to changes in ALL components

$$\frac{dF}{F} = \frac{\sum_{i=1}^k \frac{\partial F}{\partial x_i} dx_i}{F} = \sum_{i=1}^k \frac{\partial F}{\partial x_i} \cdot \frac{dx_i}{F} \stackrel{\text{All } x_i \neq 0, \infty}{=} \sum_{i=1}^k \left( \frac{\partial F}{\partial x_i} \cdot \frac{x_i}{F} \right) \cdot \frac{dx_i}{x_i}$$

This can be expressed in terms of the standard sensitivity function as

$$\frac{dF}{F} \stackrel{\text{All } x_i \neq 0, \infty}{=} \sum_{i=1}^k \left( S_{x_i}^f \cdot \frac{dx_i}{x_i} \right)$$

This relates the percent change in F to the sensitivity function and the percent change in each component

Consider the normalized differential

$$\frac{dF}{F} = \sum_{i=1}^k \left( S_{x_i}^f \bullet \frac{dx_i}{x_i} \right)$$

This can be expressed as

$$\frac{dF}{F} = \left( \sum_{\text{all resistors}} S_{R_i}^f \bullet \frac{dR_i}{R_i} \right) + \left( \sum_{\text{all capacitors}} S_{C_i}^f \bullet \frac{dC_i}{C_i} \right) + \left( \sum_{\text{all opamps}} S_{\tau_i}^f \bullet \frac{d\tau_i}{\tau_i} \right) + \dots$$

Often interested in  $\frac{dF}{F}$  evaluated at the ideal (or nominal value)

If the nominal values are all not extreme (0 or  $\infty$ ), then

$$\frac{dF}{F} = \sum_{i=1}^k \left( S_{x_i}^f \Big|_{\bar{X}_N} \bullet \frac{dx_i}{x_{iN}} \right)$$

The normalized differential – a different perspective

$$\frac{dF}{F} = \sum_{i=1}^k \left( \mathbf{S}_{x_i}^f \Big|_{\bar{X}_N} \bullet \frac{dx_i}{x_{iN}} \right)$$

Consider the multivariate Taylor's series expansion of F

$$F(\bar{X}) = F(\bar{X}_N) + \sum_{i=1}^k \frac{\partial F}{\partial x_i} \Big|_{\bar{X}_N} (x_i - x_{iN}) + \left[ \frac{1}{2!} \sum_{i=1}^k \frac{\partial^2 F}{\partial x_i^2} \Big|_{\bar{X}_N} (x_i - x_{iN})^2 + \sum_{\substack{i=1, \\ j=1, \\ i \neq j}}^{k,k} \frac{\partial^2 F}{\partial x_i \partial x_j} \Big|_{\bar{X}_N} (x_i - x_{iN})(x_j - x_{jN}) \right] + \dots$$

$$F(\bar{X}) \approx F(\bar{X}_N) + \sum_{i=1}^k \frac{\partial F}{\partial x_i} \Big|_{\bar{X}_N} (x_i - x_{iN}) +$$

$$F(\bar{X}) - F(\bar{X}_N) \approx + \sum_{i=1}^k \frac{\partial F}{\partial x_i} \Big|_{\bar{X}_N} (x_i - x_{iN})$$

$$\Delta F(\bar{X}) \approx \sum_{i=1}^k \frac{\partial F}{\partial x_i} \Big|_{\bar{X}_N} \Delta x_i$$



The normalized differential – a different perspective

$$\frac{dF}{F} = \sum_{i=1}^k \left( S_{x_i}^f \Big|_{\bar{X}_N} \bullet \frac{dx_i}{x_{iN}} \right)$$

Consider the multivariate Taylor's series expansion of F

$$\Delta F(\bar{X}) \approx \sum_{i=1}^k \frac{\partial F}{\partial x_i} \Big|_{\bar{X}_N} \Delta x_i$$

$$\frac{\Delta F(\bar{X})}{F} \approx \sum_{i=1}^k \frac{\partial F}{\partial x_i} \Big|_{\bar{X}_N} \frac{\Delta x_i}{F} = \sum_{i=1}^k \frac{\partial F}{\partial x_i} \Big|_{\bar{X}_N} \frac{x_i}{x_i} \frac{\Delta x_i}{F} = \sum_{i=1}^k \left( \frac{\partial F}{\partial x_i} \Big|_{\bar{X}_N} \frac{x_i}{F} \right) \frac{\Delta x_i}{x_i}$$

$$\frac{\Delta F}{F} \approx \sum_{i=1}^k \left( S_{x_i}^f \Big|_{\bar{X}_N} \right) \frac{\Delta x_i}{x_i}$$

**Note this is essentially the same expression that was arrived at from the sensitivity analysis approach**

$$\frac{dF}{F} = \sum_{i=1}^k \left( S_{x_i}^f \Big|_{\bar{X}_N} \cdot \frac{dx_i}{x_{iN}} \right)$$

Dependent only on components  
(not circuit structure)

Dependent on circuit structure (for some  
circuits, also not dependent on components)

**The sensitivity functions are thus useful for comparing  
different circuit structures**

**The variability which is the product of the sensitivity  
function and the normalized component differential is  
more important for predicting circuit performance**

# Variability Formulation

$$V_{x_i}^f = S_{x_i}^f \Big|_{\vec{X}_N} \bullet \frac{dx_i}{x_{iN}}$$


$$\frac{dF}{F} = \sum_{i=1}^k V_{x_i}^f \Big|_{\vec{X}_N}$$

Variability includes effects of both circuit structure and components on performance

If component variations are small, high sensitivities are acceptable

If component variations are large, low sensitivities are critical

Example

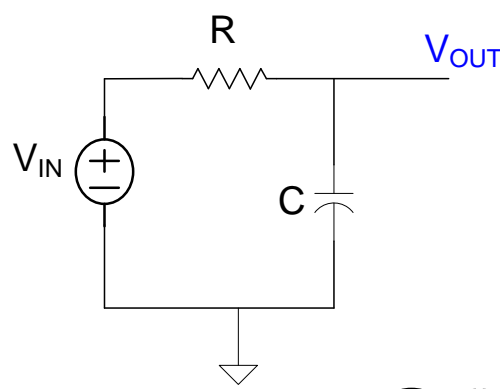

$$T(s) = \frac{1}{1+RCs} = \frac{\omega_0}{s+\omega_0}$$

If  $\omega_0 = 1/RC$ , determine  $S_R^{\omega_0}$  and  $S_C^{\omega_0}$

$$S_R^{\omega_0} = \frac{\partial \omega_0}{\partial R} \bullet \frac{R}{\omega_0}$$


$$S_R^{\omega_0} = \left( \frac{-1}{R^2 C} \right) \bullet \frac{R}{\omega_0}$$

$$S_R^{\omega_0} = -\frac{1}{R} \left( \frac{1}{RC} \right) \bullet \frac{R}{\omega_0} = -\frac{1}{R} (\omega_0) \bullet \frac{R}{\omega_0} = -1$$

Likewise

$$S_C^{\omega_0} = -1$$

## Example

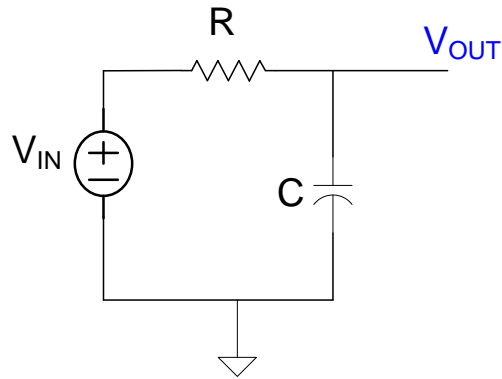

$$T(s) = \frac{1}{1+RCs} = \frac{\omega_0}{s+\omega_0}$$

$$\omega_0 = 1/RC$$

$$S_R^{\omega_0} = -1$$

$$S_C^{\omega_0} = -1$$


$$\frac{d\omega_0}{\omega_0} = \sum_{i=1}^k v_{x_i}^{\omega_0} \Big|_{\bar{X}_N}$$

Thus a 1% increase in  $R$  will cause approximately a 1% decrease in  $\omega_0$

a 1% increase in  $C$  will cause approximately a 1% decrease in  $\omega_0$

a 1% increase in both  $C$  and  $R$  will cause approximately a 2% decrease in  $\omega_0$

# Example

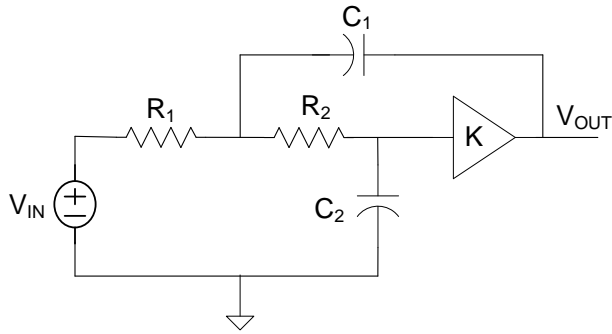

$$T(s) = K \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{s^2 + s \left[ \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$Q = \frac{1}{\sqrt{\frac{R_2 C_2}{R_1 C_1} + \sqrt{\frac{R_1 C_2}{R_2 C_1} + (1-K) \frac{R_1 C_1}{R_2 C_2}}}}$$

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

Determine  $S_{C_1}^{\omega_0}$   $S_{C_2}^{\omega_0}$   $S_{R_1}^{\omega_0}$   $S_{R_2}^{\omega_0}$

$$S_{C_1}^{\omega_0} = \frac{\partial \left[ \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \right]}{\partial C_1} \frac{C_1}{\omega_0}$$

$$S_{C_1}^{\omega_0} = -\frac{1}{2} \frac{1}{\sqrt{R_1 R_2 C_2}} \left( \frac{1}{\sqrt{C_1 C_1}} \right) \frac{C_1}{\omega_0}$$

$$S_{C_1}^{\omega_0} = \frac{1}{\sqrt{R_1 R_2 C_2}} \frac{\partial \left[ \frac{1}{\sqrt{C_1}} \right]}{\partial C_1} \frac{C_1}{\omega_0}$$


$$S_{C_1}^{\omega_0} = -\frac{1}{2} \frac{1}{\sqrt{R_1 R_2 C_2 C_1}} \left( \frac{1}{C_1} \right) \frac{C_1}{\omega_0}$$

$$S_{C_1}^{\omega_0} = -\frac{1}{2} \omega_0 \left( \frac{1}{C_1} \right) \frac{C_1}{\omega_0}$$

$$S_{C_1}^{\omega_0} = \frac{1}{\sqrt{R_1 R_2 C_2}} \left( -\frac{1}{2} C_1^{-3/2} \right) \frac{C_1}{\omega_0}$$

$$S_{C_1}^{\omega_0} = -\frac{1}{2}$$

# Example

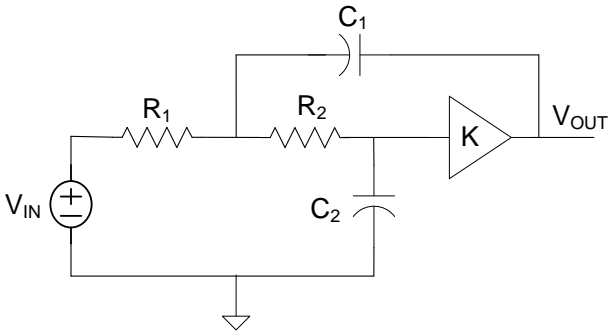

$$T(s) = K \frac{1}{R_1 R_2 C_1 C_2} \frac{1}{s^2 + s \left[ \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} + \frac{1-K}{R_2 C_2} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$Q = \frac{1}{\sqrt{\frac{R_2 C_2}{R_1 C_1}} + \sqrt{\frac{R_1 C_2}{R_2 C_1}} + (1-K) \sqrt{\frac{R_1 C_1}{R_2 C_2}}}$$

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$


Determine  $S_{C_1}^{\omega_0}$   $S_{C_2}^{\omega_0}$   $S_{R_1}^{\omega_0}$   $S_{R_2}^{\omega_0}$

$$S_{C_1}^{\omega_0} = -\frac{1}{2}$$

Likewise

$$S_{C_2}^{\omega_0} = S_{R_1}^{\omega_0} = S_{R_2}^{\omega_0} = -\frac{1}{2}$$

# Observation:

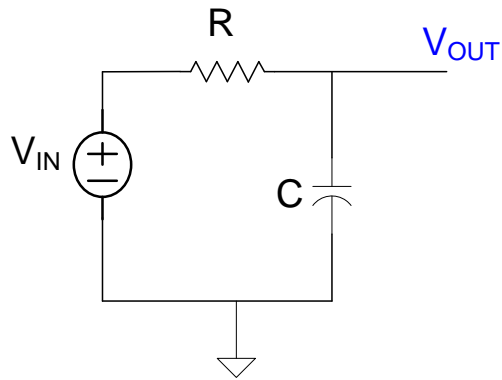


$$\omega_0 = 1/RC$$

$$S_R^{\omega_0} = -1$$

$$S_C^{\omega_0} = -1$$

$$\sum_{\text{All resistors}} S_{R_i}^{\omega_0} = -1$$
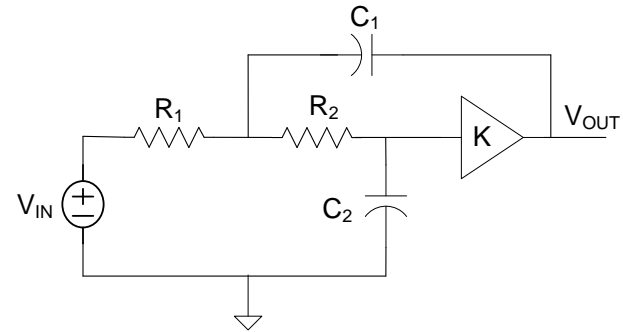
$$\sum_{\text{All capacitors}} S_{C_i}^{\omega_0} = -1$$



$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$S_{R_1}^{\omega_0} = -1/2$$

$$S_{C_1}^{\omega_0} = -1/2$$

$$S_{R_2}^{\omega_0} = -1/2$$

$$S_{C_2}^{\omega_0} = -1/2$$

$$\sum_{\text{All resistors}} S_{R_i}^{\omega_0} = -1$$

$$\sum_{\text{All capacitors}} S_{C_i}^{\omega_0} = -1$$

At this stage, this is just an observation about summed sensitivities but later will establish some fundamental properties of summed sensitivities



**End of Lecture 20**