

# EE 508

## Lecture 24

### Sensitivity Functions


- Predistortion and Calibration

Review from last time

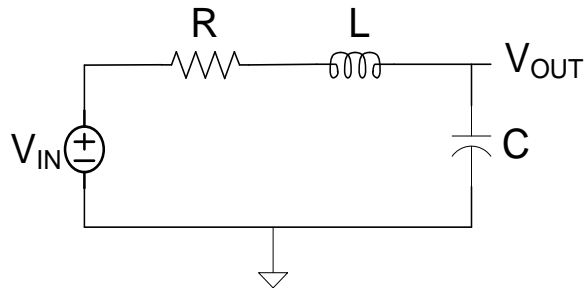
# Sensitivity Comparisons

Consider 5 second-order lowpass filters


(all can realize same  $T(s)$  within a gain factor)




Passive RLC

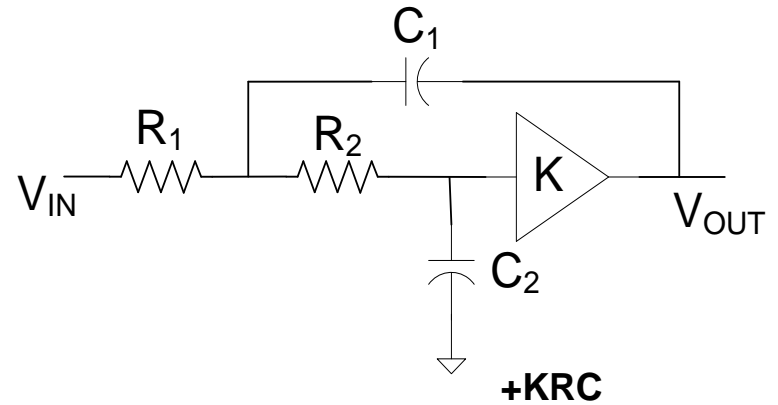

+KRC

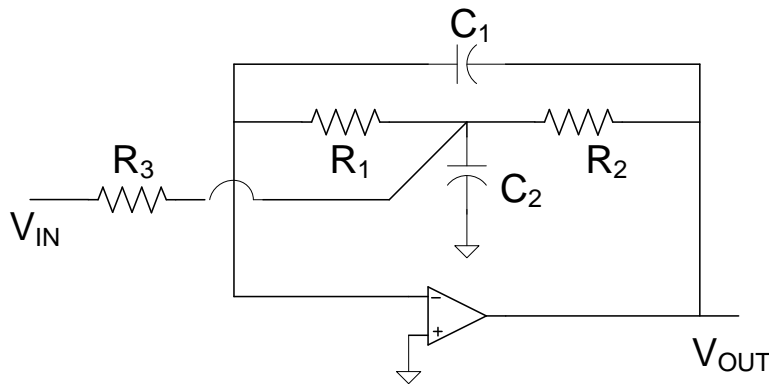

Bridged-T Feedback

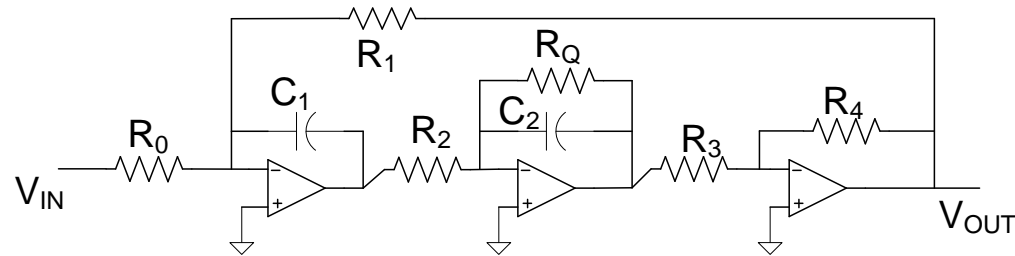


Two-Integrator Loop

Review from last time
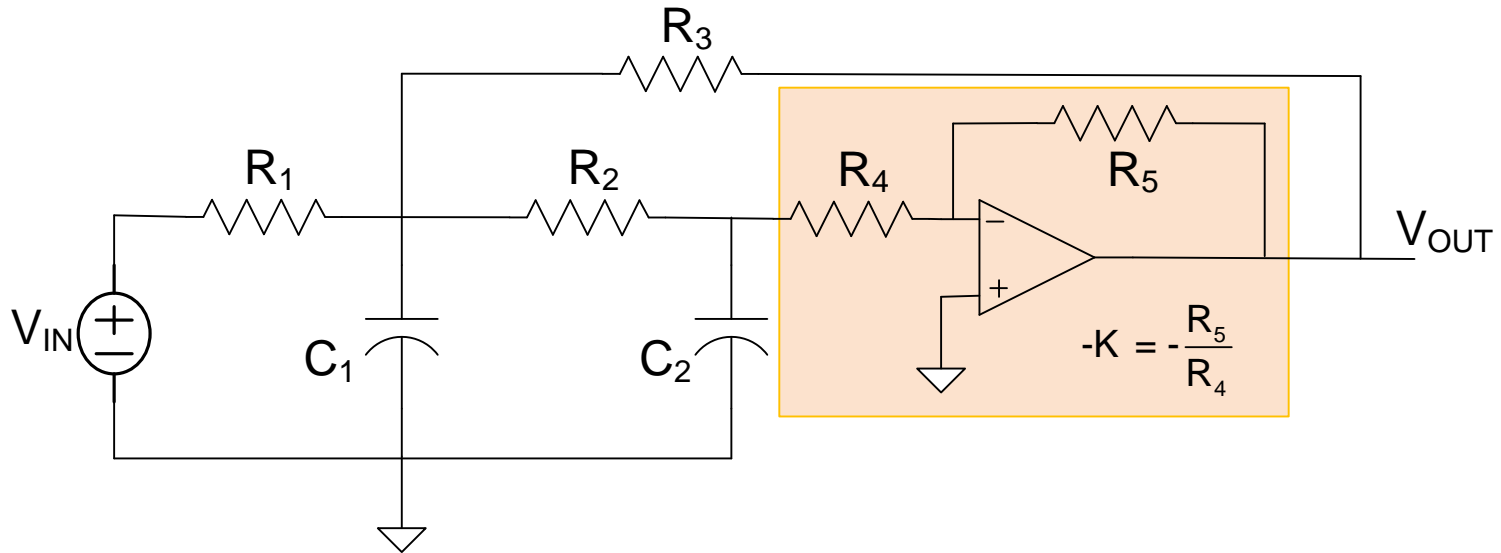
# Sensitivity Comparisons

Consider 5 second-order lowpass filters

(all can realize same  $T(s)$  within a gain factor)



**-KRC Lowpass**

Review from last time

# Passive Sensitivity Comparisons




	$\left  S_x^{\omega_0} \right $	$\left  S_x^Q \right $
Passive RLC	$\leq \frac{1}{2}$	1, 1/2
+KRC		
Equal R, Equal C (K=3-1/Q)	0, 1/2	Q, 2Q, 3Q
Equal R, K=1 (C <sub>1</sub> =4Q <sup>2</sup> C <sub>2</sub> )	0, 1/2	0, 1/2, 2Q <sup>2</sup>
Bridged-T Feedback	0, 1/2	1/3, 1/2, 1/6
Two-Integrator Loop	0, 1/2	1, 1/2, 0
-KRC	less than or equal to 1/2	less than or equal to 1/2

Substantial Differences Between (or in) Architectures

# Where we are at with sensitivity analysis:

Considered a group of five second-order filters

## Passive Sensitivity Analysis

- Closed form expressions were obtained for  $\omega_0$  and Q 
- Tedious but straightforward calculations provided passive sensitivities directly from the closed form expressions  ??? 

## Active Sensitivity Analysis

- Closed form expressions for  $\omega_0$  and Q are very difficult or impossible to obtain 

If we consider higher-order filters

## Passive Sensitivity Analysis

- Closed form expressions for  $\omega_0$  and Q are very difficult or impossible to obtain for many useful structures 

## Active Sensitivity Analysis

- Closed form expressions for  $\omega_0$  and Q are very difficult or impossible to obtain 

Need some better method for obtaining sensitivities when closed-form expressions are difficult or impractical to obtain or manipulate !!

# Relationship between active pole sensitivities and $\omega_0$ and Q sensitivities

Define  $D(s) = D_0(s) + t D_1(s)$  (from bilinear form of  $T(s)$ )

Recall: 
$$s_\tau^p = \frac{-D_1(p)}{\left. \frac{\partial D(s)}{\partial s} \right|_{s=p, t=0}}$$

Theorem: 
$$\Delta p \approx \tau s_\tau^p$$

Theorem: 
$$\Delta \alpha \approx \tau \operatorname{Re}(s_\tau^p)$$
  

$$\Delta \beta \approx \tau \operatorname{Im}(s_\tau^p)$$

Theorem:

$$\frac{\Delta \omega_0}{\omega_0} \approx \frac{1}{2Q} \frac{\Delta \alpha}{\omega_0} + \sqrt{1 - \frac{1}{4Q^2}} \frac{\Delta \beta}{\omega_0} \qquad \frac{\Delta Q}{Q} \approx -2Q \left( 1 - \frac{1}{4Q^2} \right) \frac{\Delta \alpha}{\omega_0} + \sqrt{1 - \frac{1}{4Q^2}} \frac{\Delta \beta}{\omega_0}$$

Claim: These theorems, with straightforward modification, also apply to other parameters (R, C, L, K, ...) where,  $D_0(s)$  and  $D_1(s)$  will change since the parameter is different

Review from last time

# Active Sensitivity Comparisons

	$\frac{\Delta\omega_0}{\omega_0}$	$\frac{\Delta Q}{Q}$
Passive RLC		
+KRC		
Equal R, Equal C (K=3-1/Q)	$-\frac{1}{2}\left(3-\frac{1}{Q}\right)^2 \tau\omega_0$	$-\frac{1}{2}\left(3-\frac{1}{Q}\right)^2 \tau\omega_0$
Equal R, K=1 (C <sub>1</sub> =4Q <sup>2</sup> C <sub>2</sub> )	$-Q \tau\omega_0$	$Q \tau\omega_0$
Bridged-T Feedback	$-\frac{3}{2} Q \tau\omega_0$	$\frac{1}{2} Q \tau\omega_0$
Two-Integrator Loop	$-\tau\omega_0$	$4Q \tau\omega_0$
-KRC	$\frac{5}{2} Q \tau\omega_0$	$25Q^3 \tau\omega_0$

Substantial Differences Between Architectures

## Review from last time

Are these passive sensitivities acceptable?

$$\left| S_x^{\omega_0} \right|$$

$$\left| S_x^Q \right|$$

Passive RLC

$$\leq \frac{1}{2}$$

1, 1/2

+KRC

Equal R, Equal C ( $K=3-1/Q$ )

0, 1/2

Q, 2Q, 3Q

Equal R,  $K=1$  ( $C_1=4Q^2C_2$ )

0, 1/2

0, 1/2, 2Q<sup>2</sup>

Bridged-T Feedback

0, 1/2

1/3, 1/2, 1/6

Two-Integrator Loop

0, 1/2

1, 1/2, 0

-KRC

less than or equal to 1/2

less than or equal to 1/2



Review from last time  
Are these sensitivities acceptable?

**Passive Sensitivities:**

$$\frac{\Delta\omega_0}{\omega_0} \simeq S_x^{\omega_0} \frac{\Delta x}{x}$$

In integrated circuits,  $\Delta R/R$  and  $\Delta C/C$  due to process variations can be K 30% or larger due to process variations

Many applications require  $\Delta\omega_0/\omega_0 < .001$  or smaller and similar requirements on  $\Delta Q/Q$

Even if sensitivity is around  $\frac{1}{2}$  or 1, variability is often orders of magnitude too large

**Active Sensitivities:**

All are proportional to  $\tau\omega_0$

Some architectures much more sensitive than others

Can reduce  $\tau\omega_0$  by making GB large but this is at the expense of increased power and even if power is not of concern, process presents fundamental limits on how large GB can be made

# What can be done to address these problems?

## 1. Predistortion

Design circuit so that after component shift, correct pole locations are obtained

Predistortion is generally used in integrated circuits to remove the bias associated with inadequate amplifier bandwidth

Tedious process after fabrication since depends on individual components

Temperature dependence may not track

Difficult to maintain over time and temperature

Over-ordering will adversely affect performance



Seldom will predistortion alone be adequate to obtain acceptable performance

Bell Labs did to this in high-volume production (STAR Biquad)

# What can be done to address these problems?
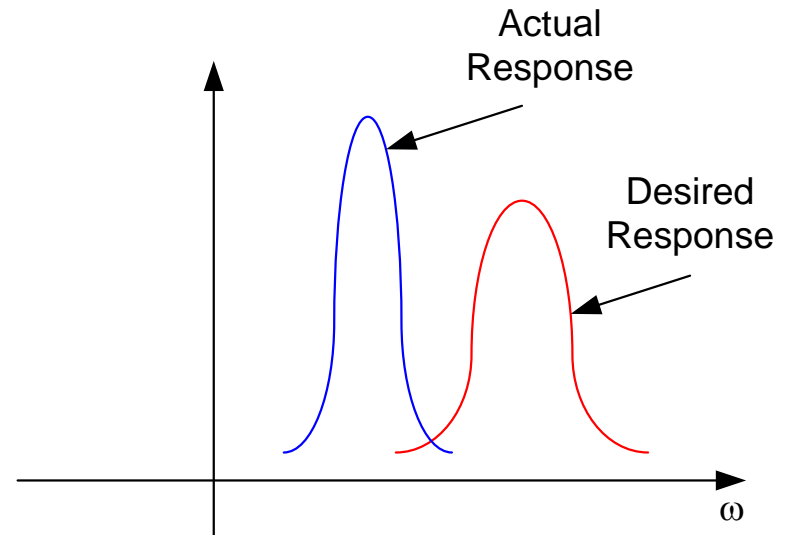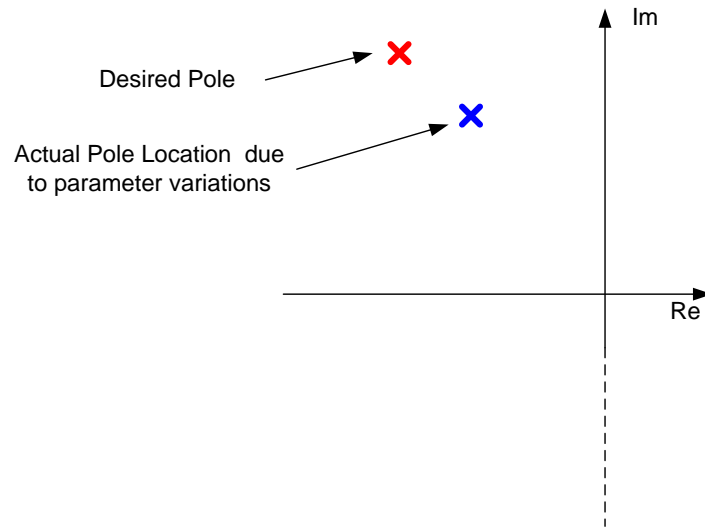
## 1. Predistortion

Design circuit so that after component shift, correct pole locations are obtained





Pole shift due to parametric variations (e.g. inadequate GB)

# What can be done to address these problems?
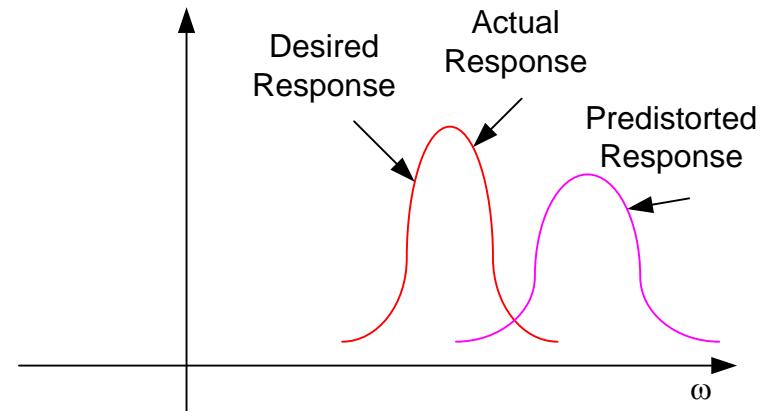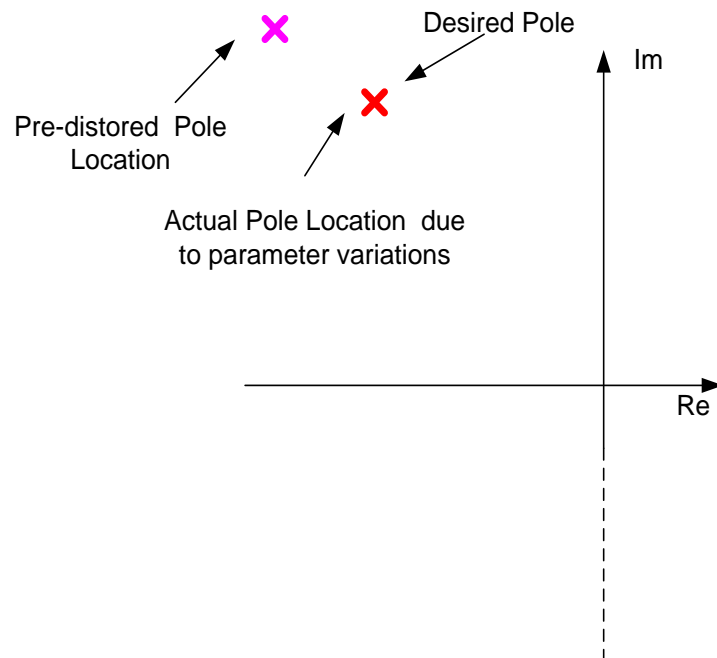
## 1. Predistortion

Design circuit so that after component shift, correct pole locations are obtained





Pre-distortion concept

# What can be done to address these problems?
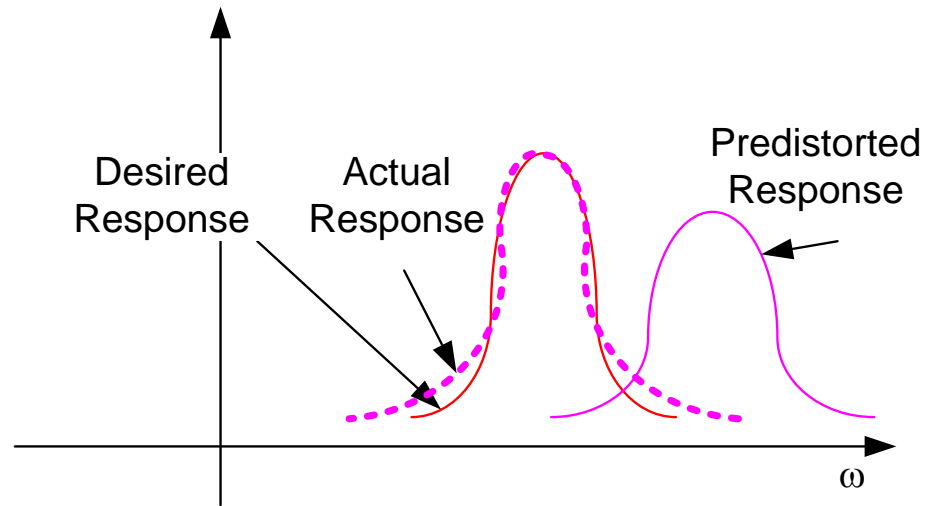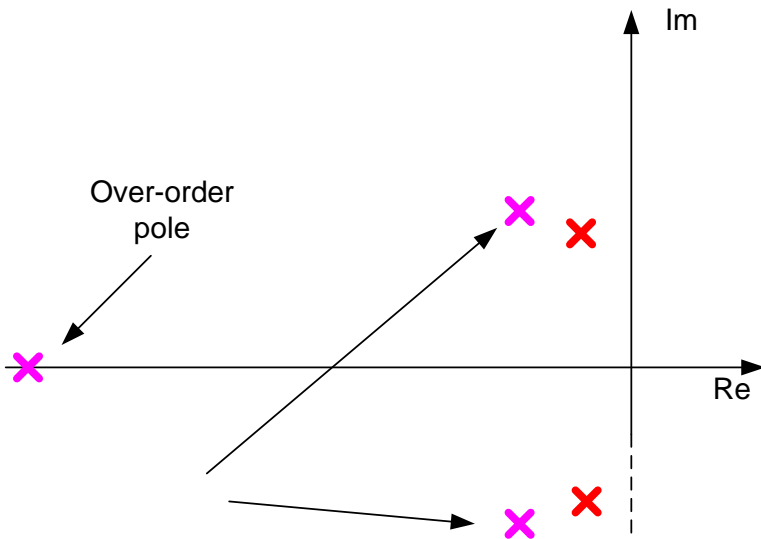
## 1. Predistortion

Design circuit so that after component shift, correct pole locations are obtained



Over-ordering Limitations with Pre-distortion

Parasitic Pole Affects Response

Predistortion almost always done even if benefits only modest

Not effective if significant deviations exist before predistortion

# What can be done to address these problems?

## 2. Trimming

### a) **Functional Trimming**

- trim parameters of actual filter based upon measurements
- difficult to implement in many structures
- manageable for cascaded biquads


### b) **Deterministic Trimming (much preferred)**

- Trim component values to their ideal value
  - Continuous-trims of resistors possible in some special processes
  - Continuous-trim of capacitors is more challenging
  - Link trimming of Rs or Cs is possible with either metal or switches
- If all components are ideal, the filter should also be ideal
  - R-trimming algorithms easy to implement
  - Limited to unidirectional trim
  - Trim generally done at wafer level for laser trimming, package for link trims
- Filter shifts occur due to stress in packaging and heat cycling

### c) **Master-slave reference control (depends upon matching in a process)**


- Can be implemented in discrete or integrated structures
- Master typically frequency or period referenced
- Most effective in integrated form since good matching possible
- Widely used in integrated form
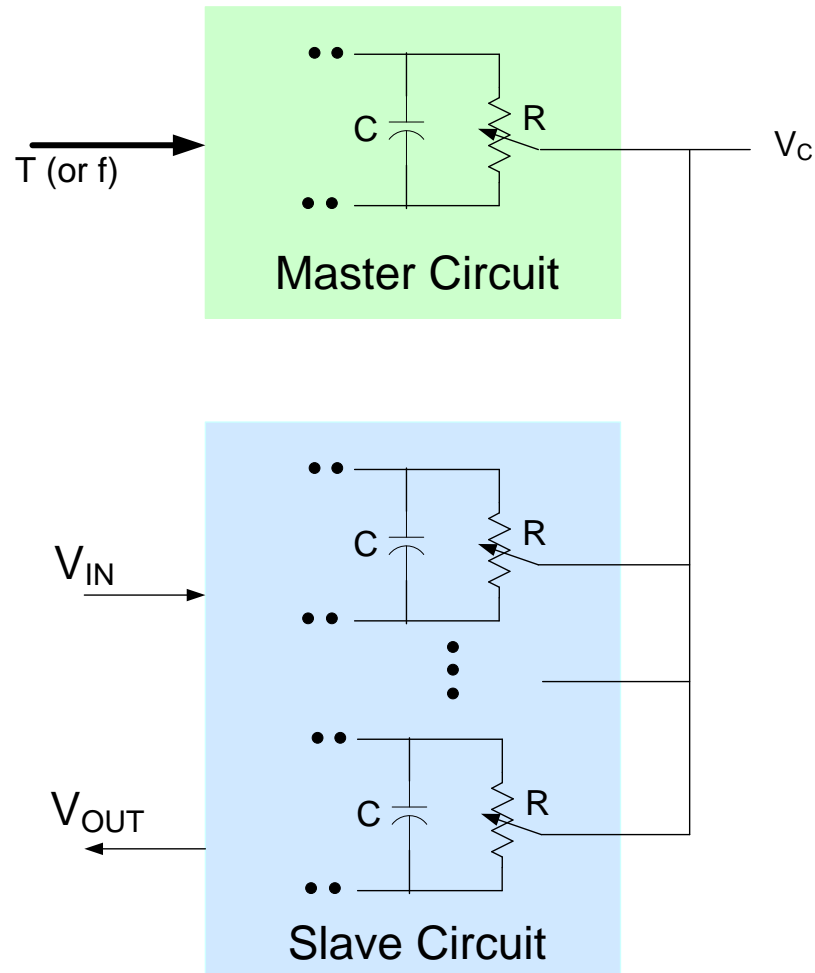
## Master-slave Control (depends upon matching in a process)



- Automatically adjust  $R$  in the Master Circuit to match  $RC$  to  $T$
- Rely on matching to match  $RC$  products in Slave Circuit to  $T$
- Matching can be very good (1% or 0.1% or better)

## Master-slave Example:

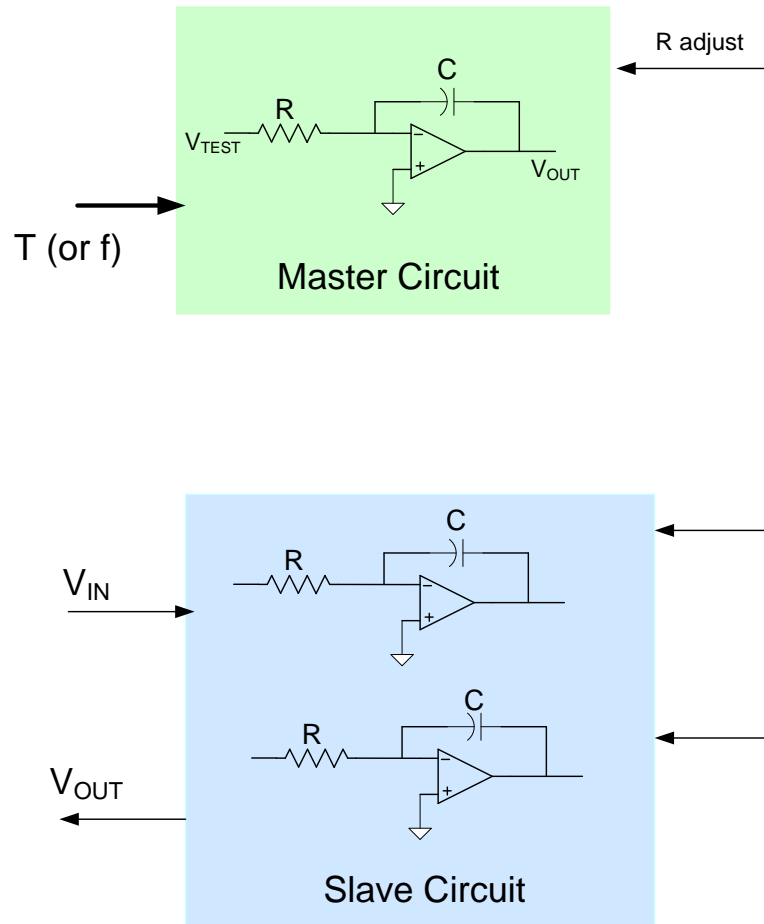


$$T(s) = \frac{V_{OUT}}{V_{TEST}} = - \frac{1}{RCs}$$

- Key parameter of integrator is unity gain frequency  $I_0=1/RC$
- Adjust  $R$  in Master Circuit so that  $I_0=1$  at the input frequency  $f$
- With matching, unity gain frequency of all integrators in Slave Circuit will also be 1



## Master-slave Example:

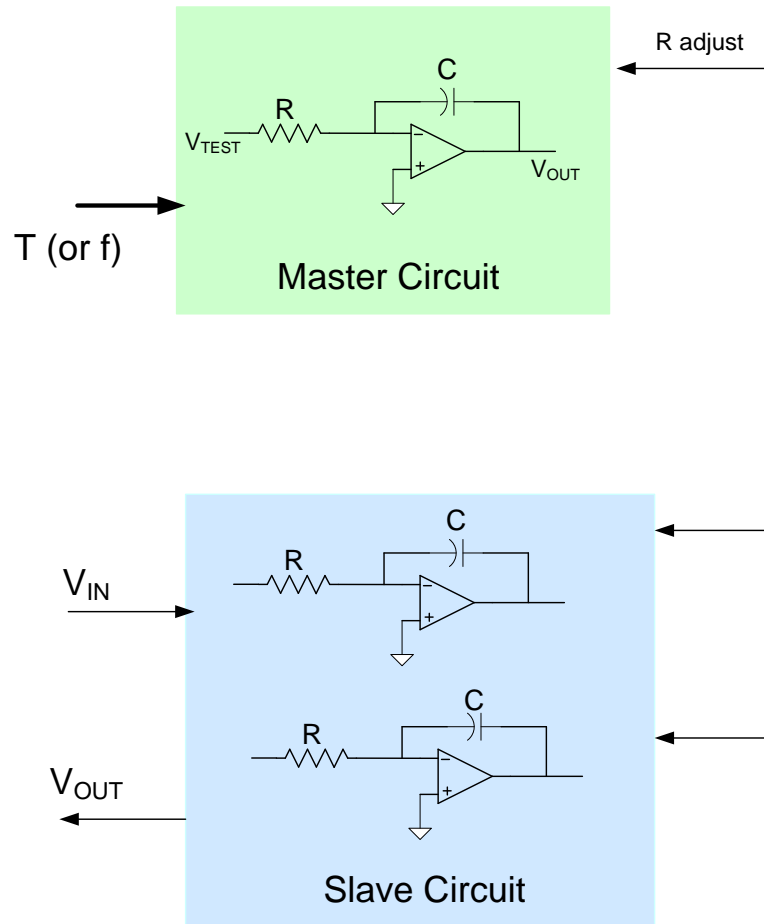

$$T(s) = \frac{V_{OUT}}{V_{TEST}} = - \frac{1}{RCs}$$

$$T_{ACT}(s) = \frac{V_{OUT}}{V_{TEST}} = - \frac{1}{RCs + \tau(s + RCs^2)}$$

- Over-ordering will limit accuracy of master-slave approach even if unity gain frequency of master circuit is precisely obtained
- Technique is often used to maintain good control of effective RC products

What can be done to address these problems?

### 3. Select Appropriate Architecture

**Helps a lot**

**Best architectures are not known**

**Performance of good architectures often not good enough**

What can be done to address these problems?


## 4. Different Approach for Filter Implementation

- **Frequency Referenced Filters**
  - **Switched-Capacitor Filters**
- **DSP- Based Filter Implementation**
- **Other Niche Methods**

# Summary of Sensitivity Observations

- Sensitivity varies substantially from one implementation to another
- Variability too high, even with low sensitivity, for more demanding applications
- Methods of managing high variability
  - Select good structures
  - Trimming
    - Functional
    - Deterministic
  - Predistortion
    - In particular, for active sensitivities
    - Useful but not a total solution
  - Frequency Referenced Techniques
    - Master-Slave Control
      - Depends upon matching
      - Can self-trim or self-compensate
    - Switched-Capacitor Filters
    - AD/digital filter/D/A
  - Alternate Design Approach
    - Other methods


# Filter Design Process

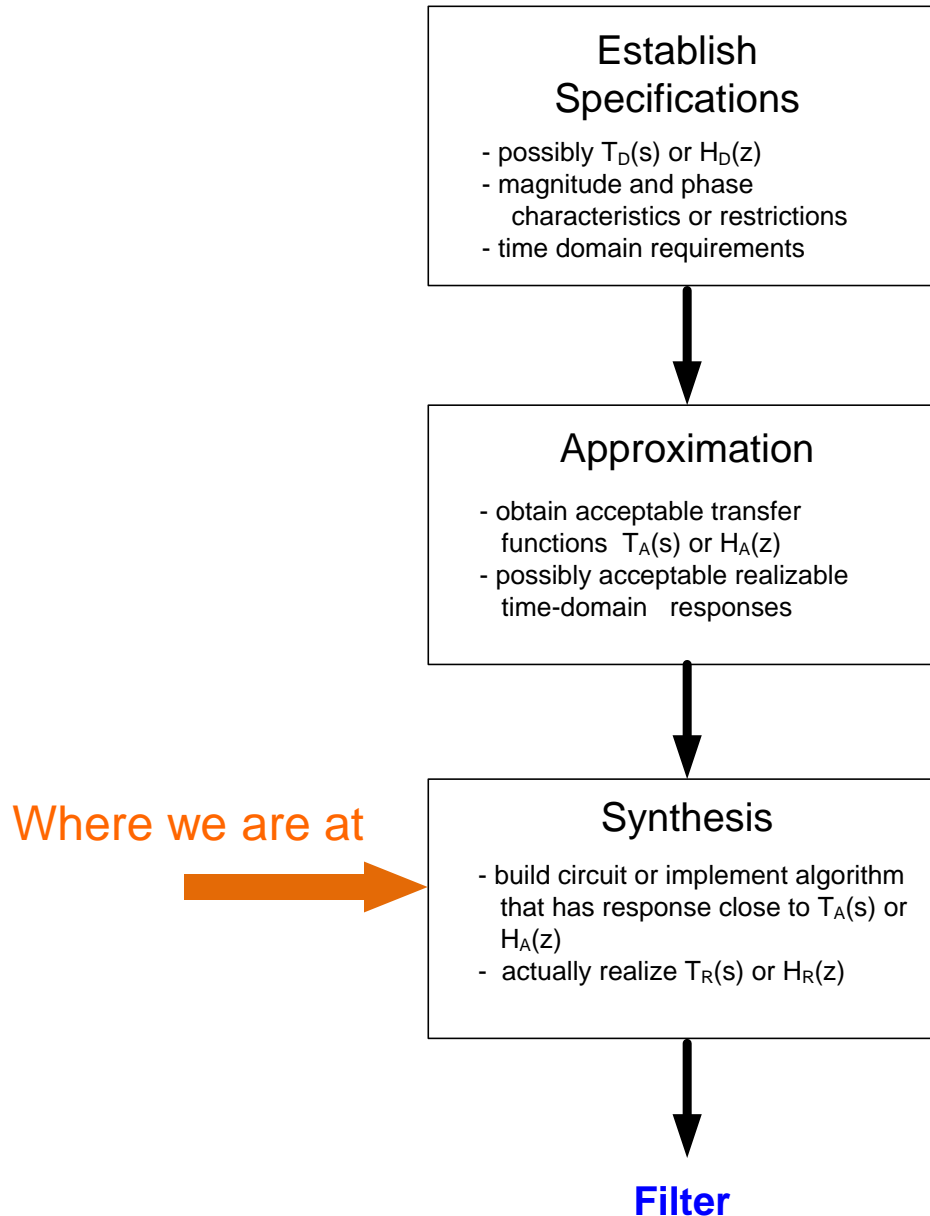

# Filter Design/Synthesis Considerations


Most designs today use one of the following three basic architectures

## Cascaded Biquads

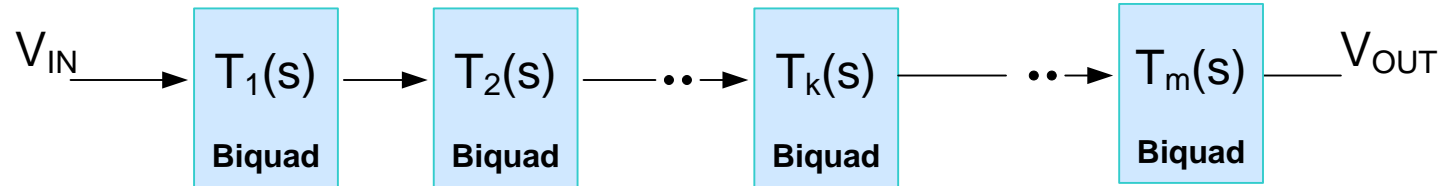


$$T(s) = T_1 T_2 \dots T_m$$

## Leapfrog

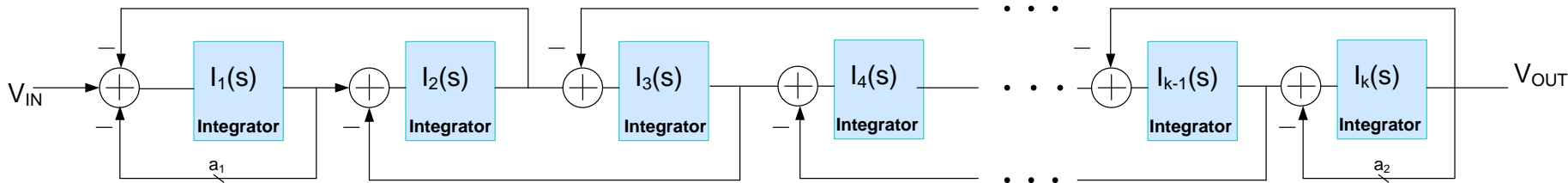

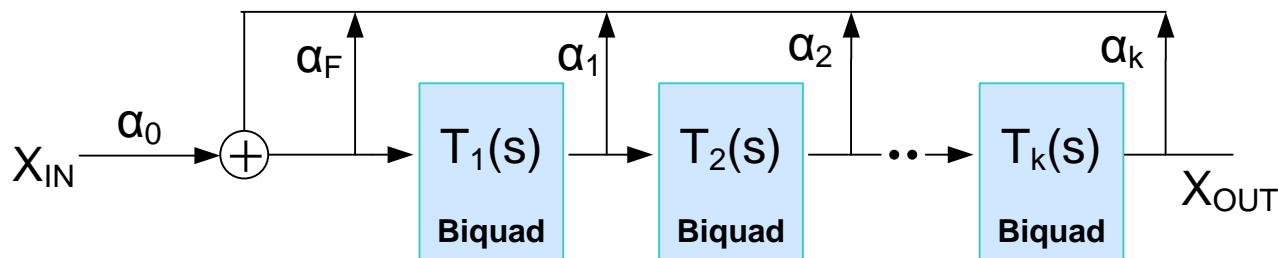
## Multiple-loop Feedback – One type shown (less popular)



# Filter Design/Synthesis Considerations

## Multiple-loop Feedback – Another type

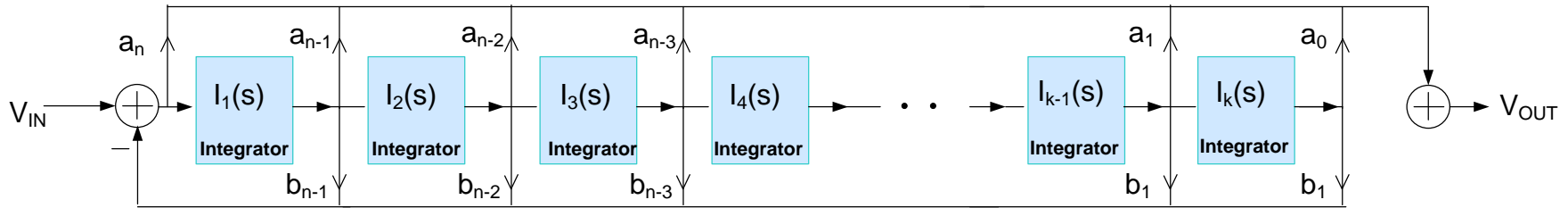

$$X = V_{IN} - X \bullet \sum_{k=1}^n b_{n-k} \left( \frac{I_0}{s} \right)^k$$

$$V_{OUT} = X \bullet \sum_{k=0}^n a_{n-k} \left( \frac{I_0}{s} \right)^k$$


$$T(s) = \frac{\sum_{k=0}^n a_{n-k} \left( \frac{I_0}{s} \right)^k}{1 + \sum_{k=1}^n b_{n-k} \left( \frac{I_0}{s} \right)^k}$$

$$T(s) = \frac{\sum_{k=0}^n a_{n-k} I_0^k s^{n-k}}{s^n + \sum_{k=1}^n b_{n-k} I_0^k s^{n-k}}$$

- Termed the direct synthesis method
- Directly implements the coefficients in the numerator and denominator
- Approach followed in the Analog Computers
- Not particularly attractive from an overall performance viewpoint


# Filter Design/Synthesis Considerations

## Cascaded Biquads

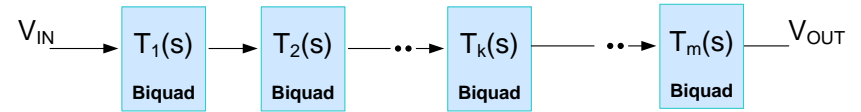


$$T(s) = T_1 T_2 \dots T_m$$

## Leapfrog

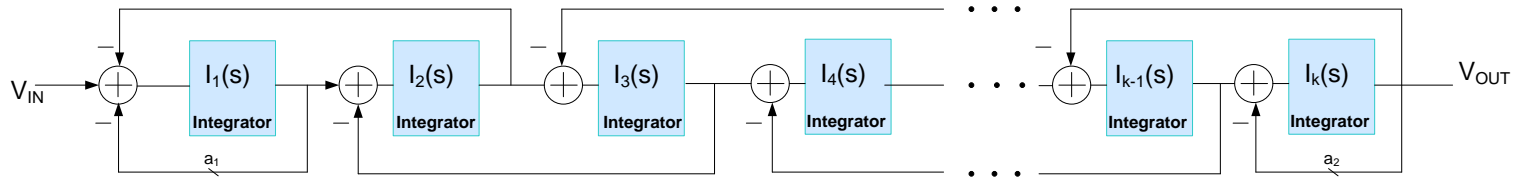
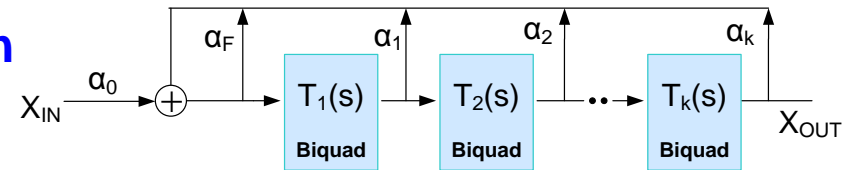
## Multiple-loop Feedback – One type shown



Will study details of all three types of architectures later


Observation: All filters are comprised of summers, biquads and integrators

Consider now the biquads




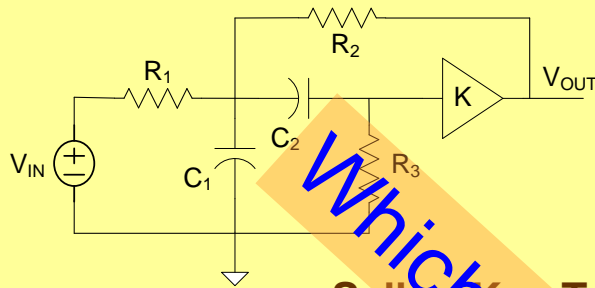
# Biquad Filters Design Considerations


Several different Biquads were considered and other implementations exist



**Sallen-Key Type (Dependent Sources)**

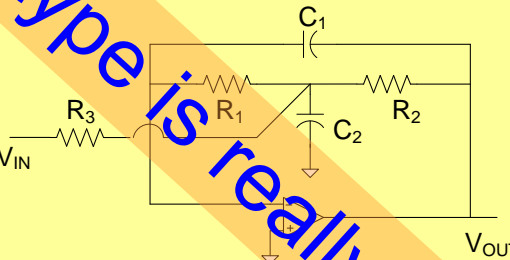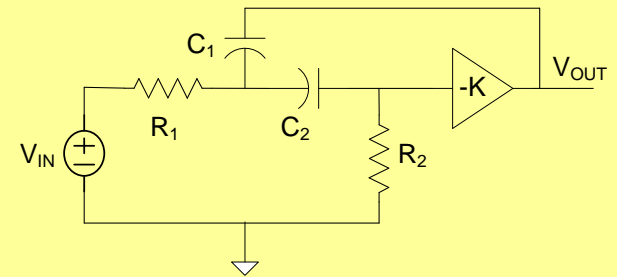

**Infinite Gain Amplifiers**

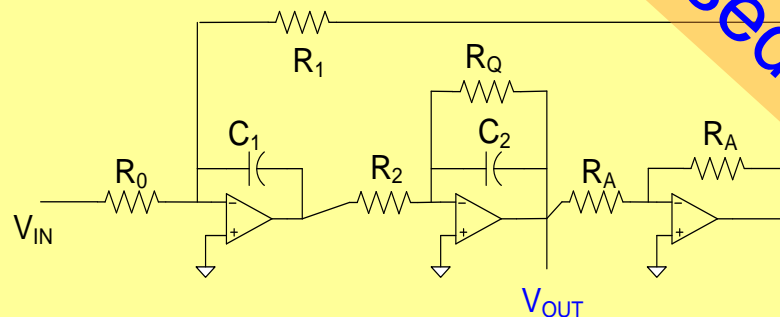

**Integrator Based Structures**


Which type is really used?

# Floating Nodes


A node in a circuit is termed a **floating node** if it is not an output node of a ground-referenced voltage-output amplifier (dependent or independent), not connected to a ground-referenced voltage source, or not connected to a ground-referenced null-port

● Floating Node

● Not Floating Node

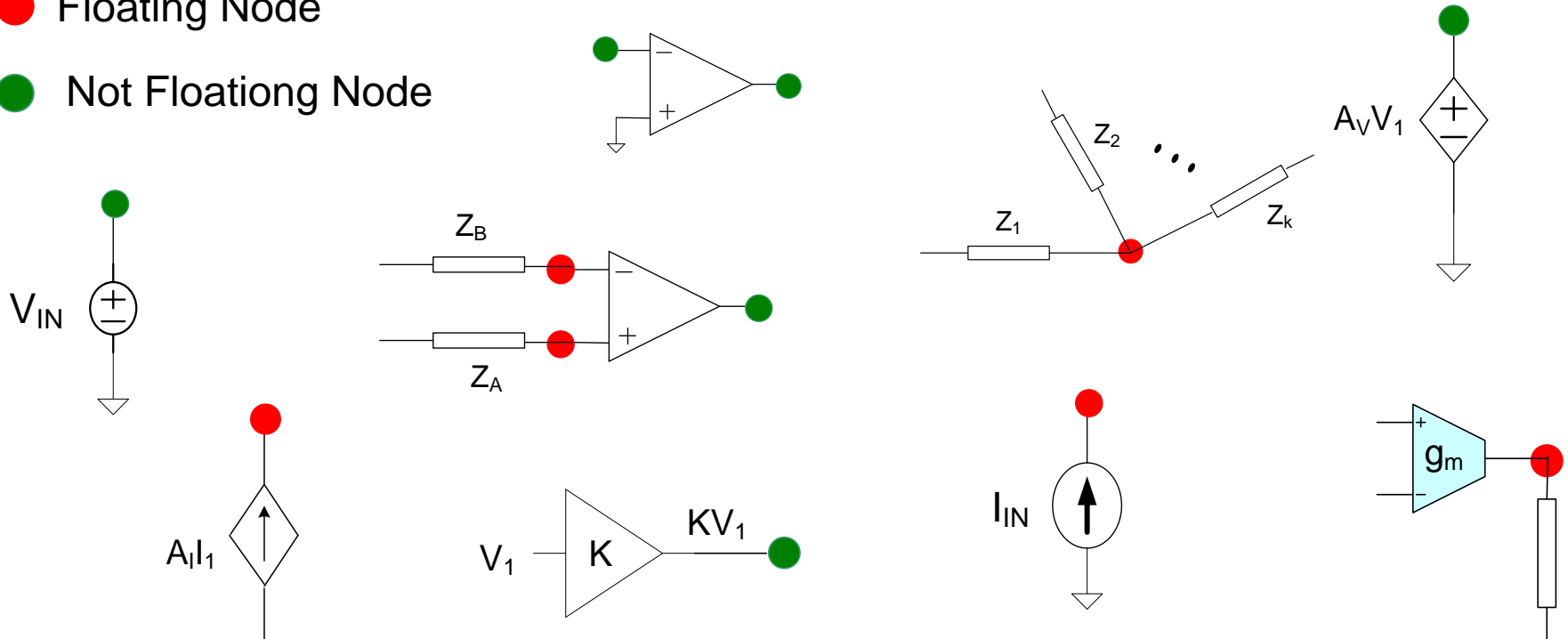
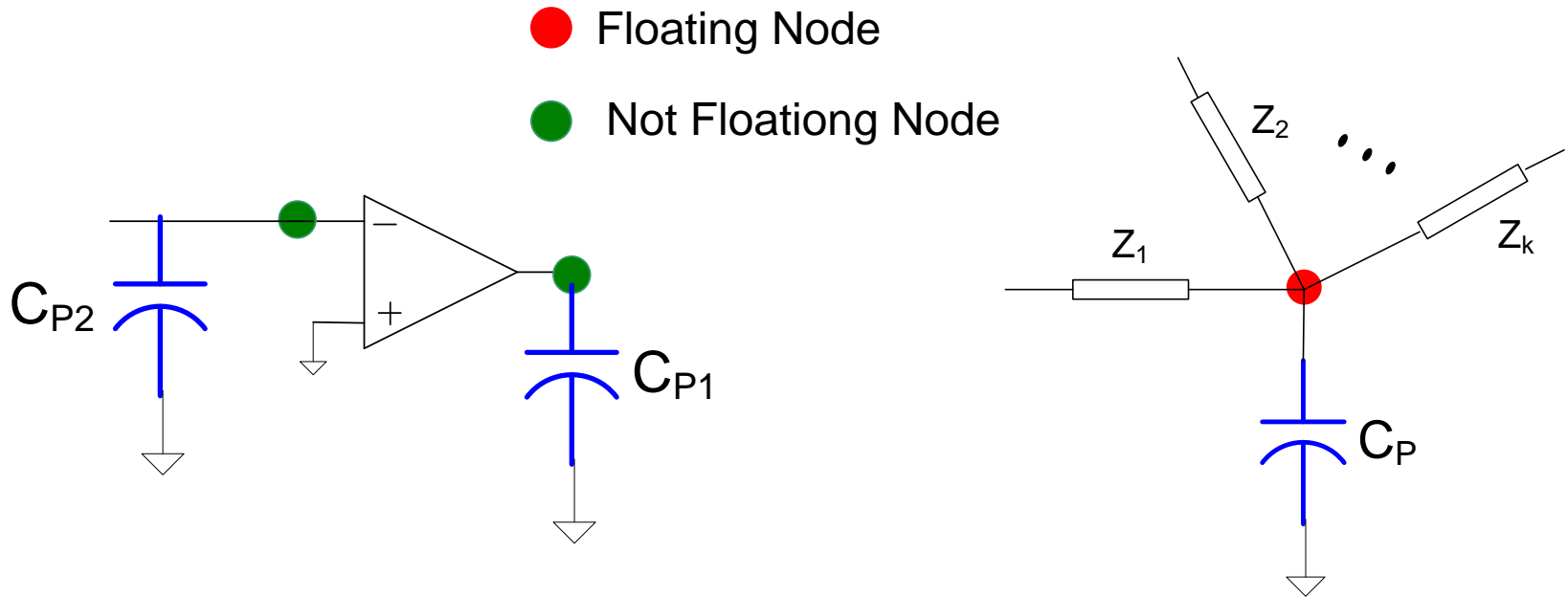
# Parasitic Capacitances on Floating Nodes



Parasitic capacitances ideally have no effect on filter when on a non-floating node but directly affect transfer function when they appear on a floating node



Parasitic capacitances are invariably large, nonlinear, and highly process dependent in integrated filters. Thus, it is difficult to build accurate integrated filters if floating nodes are present

Generally avoid floating nodes, if possible, in integrated filters


# Which type of Biquad is really used?

● Not Floating Node


● Floating Node

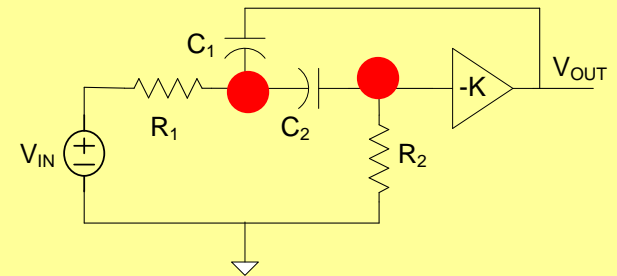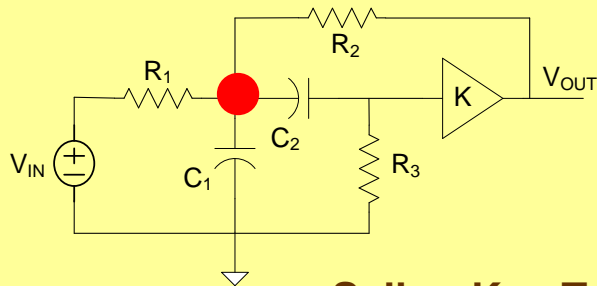

**Sallen-Key Type (Dependent Sources)**

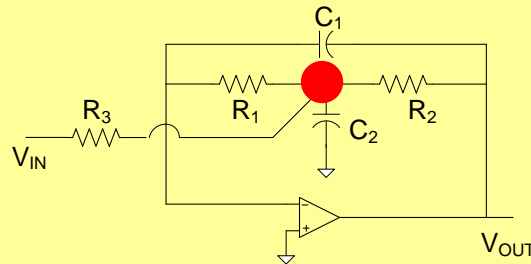

**Infinite Gain Amplifiers**

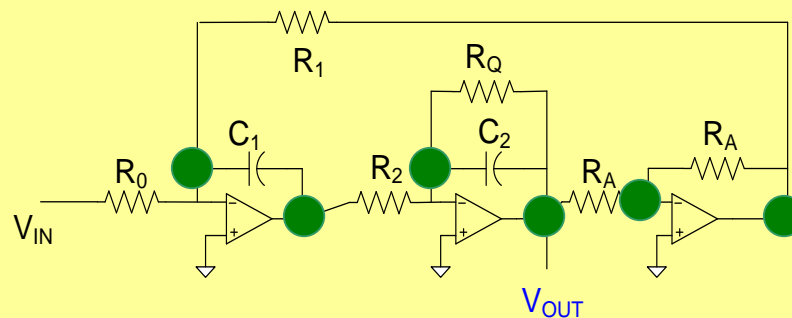




**Integrator Based Structures**

# Which type of Biquad is really used?




● Not Floating Node

● Floating Node

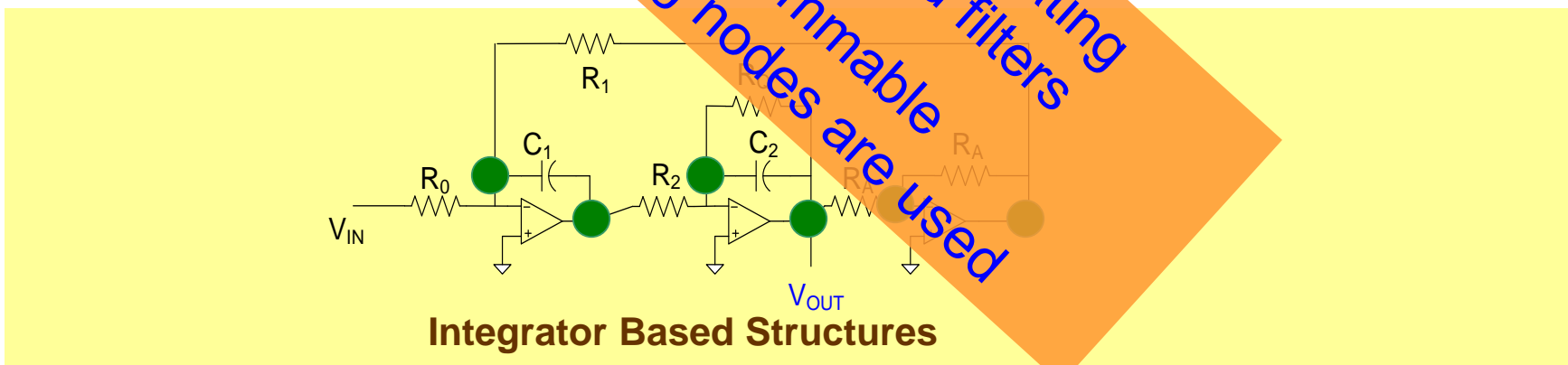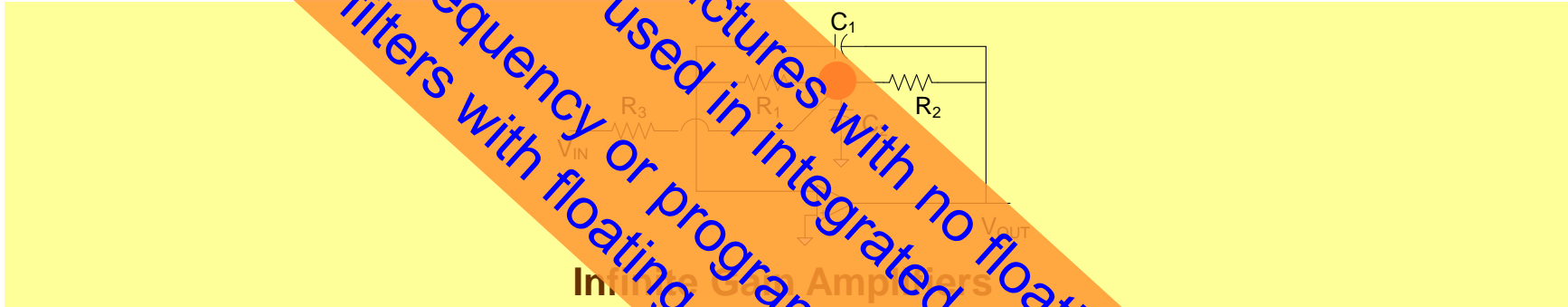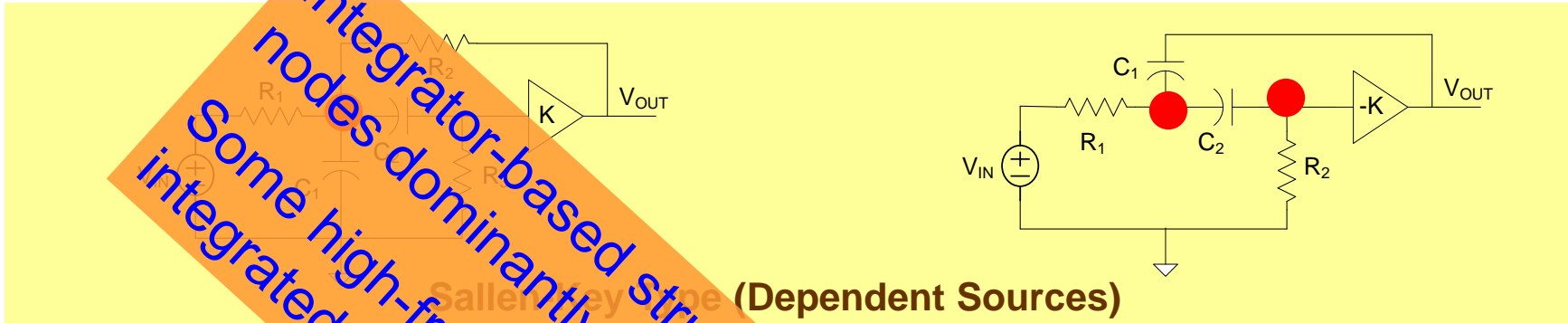
Integrator-based structures with no floating nodes dominantly used in integrated filters with floating nodes are used




# Integrator-based Biquads

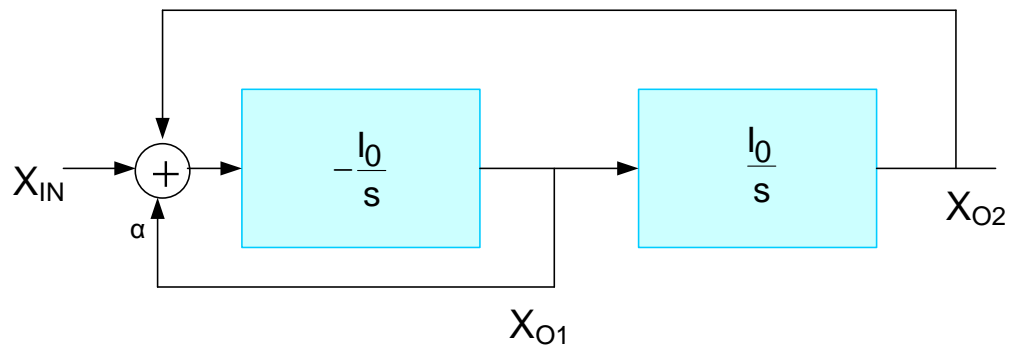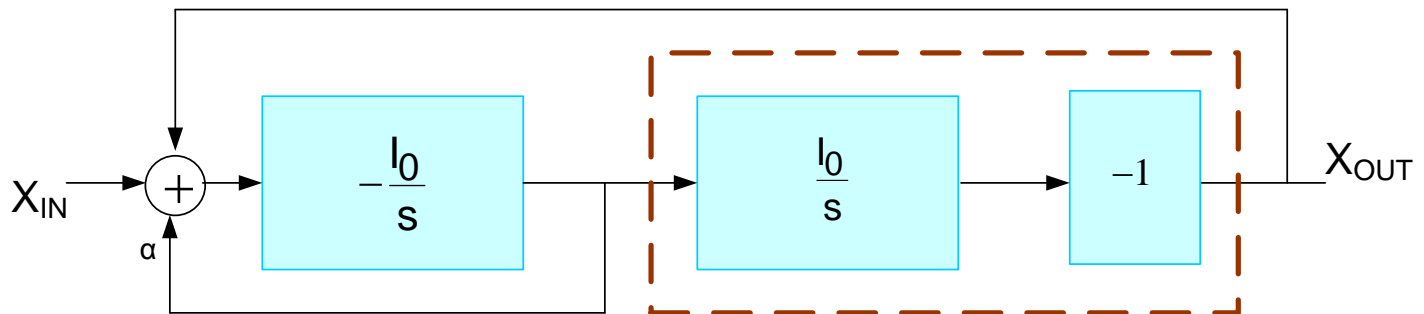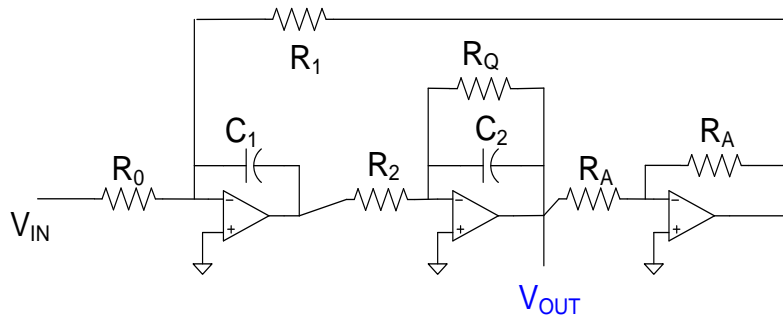

# Integrator-based Biquads

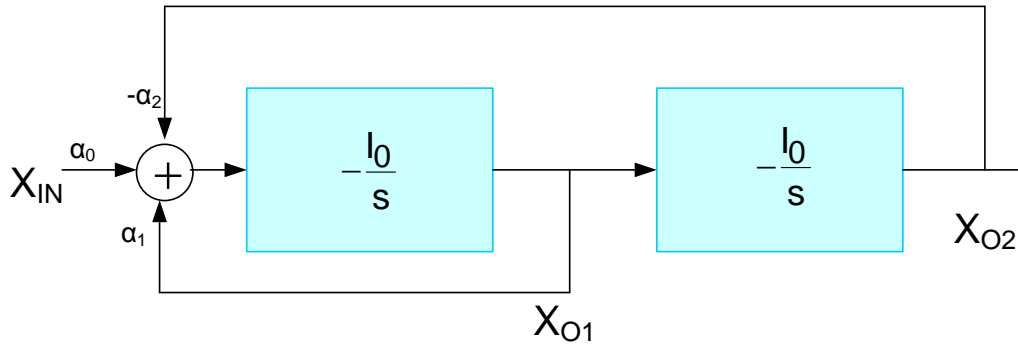


State Variable Biquad  
(Alt KHN Biquad)

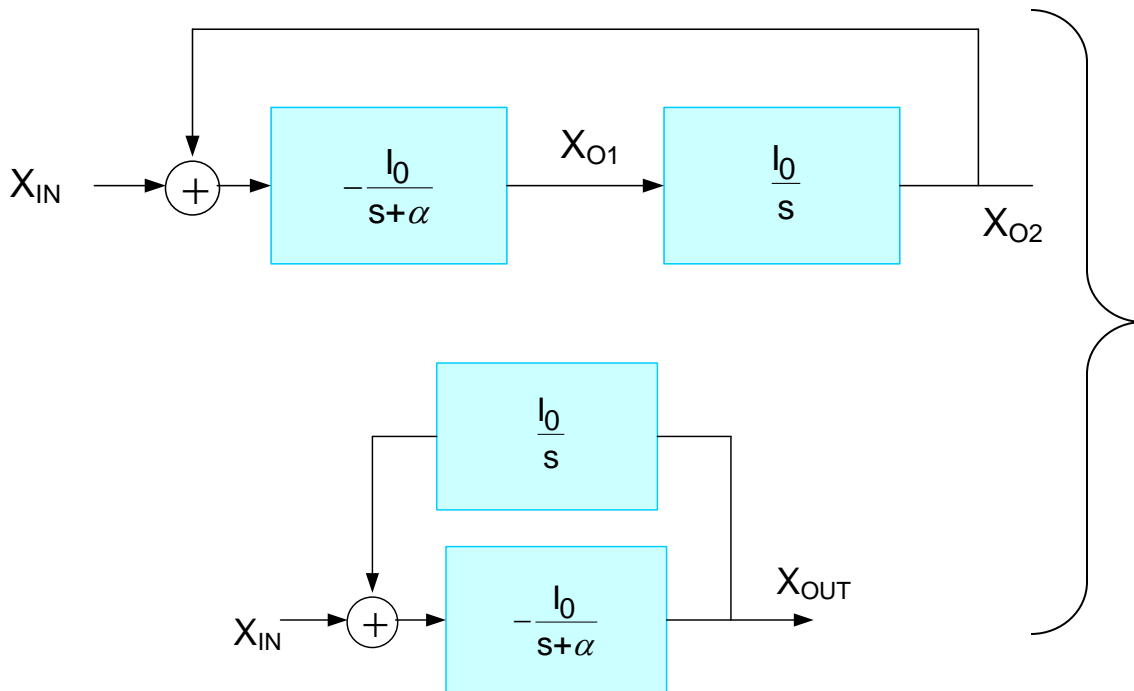


Integrator and lossy  
integrator in a loop

# Integrator-based Biquads

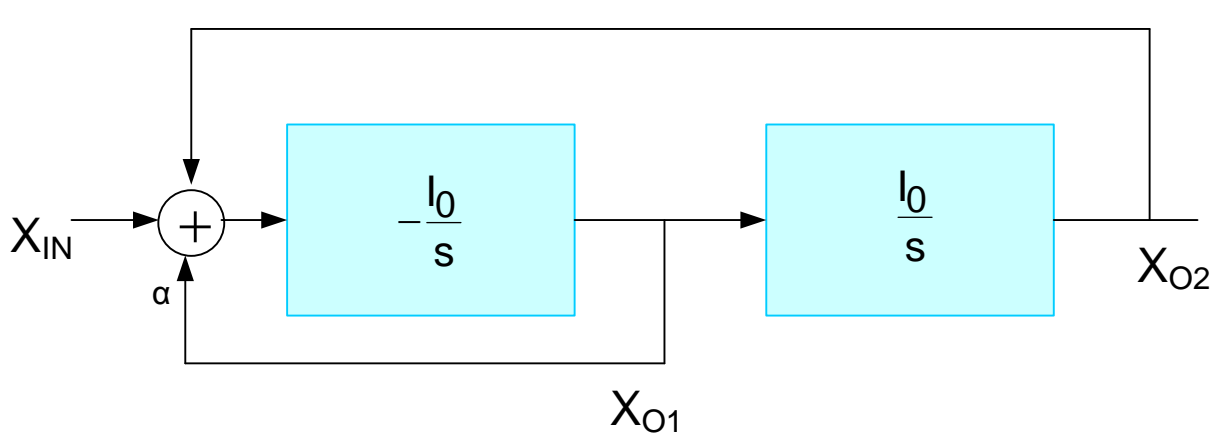



Tow-Thomas Biquad

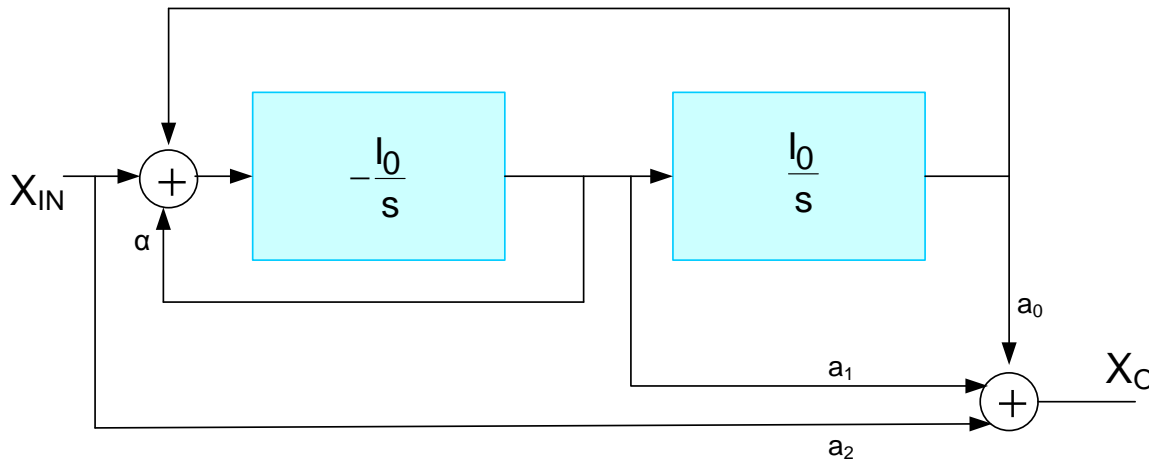

With arbitrary zero locations



# Integrator-based Biquads

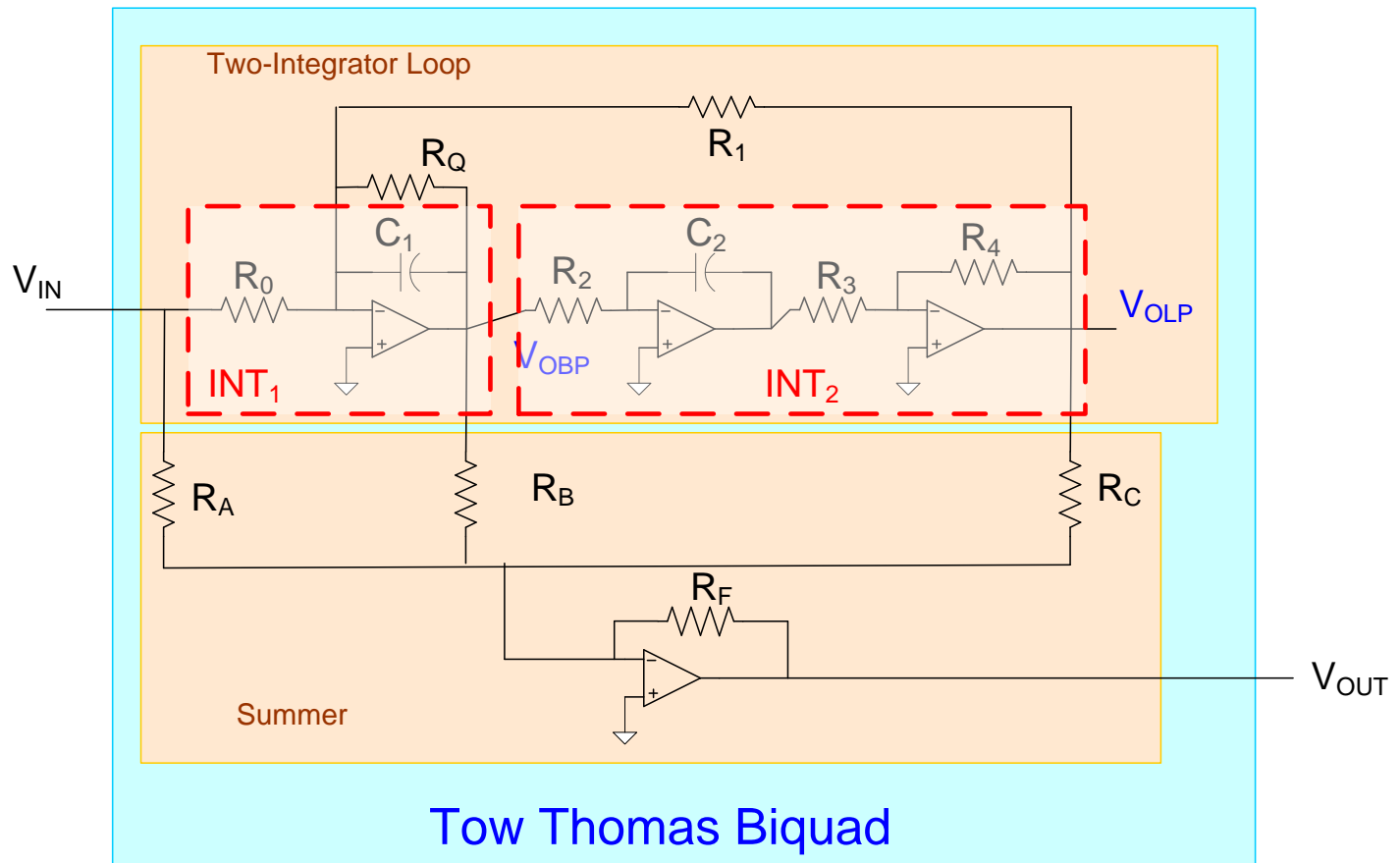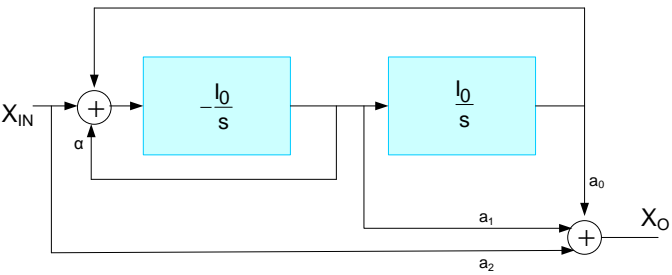


# Integrator-based Biquads


- Integrator-based biquads all involve two integrators in a loop
- All integrator-based biquads discussed have no floating nodes
- Most biquads in integrated filters are based upon two integrator loop structures
- The summers are usually included as summing inputs on the integrators
- The loss can be combined with the integrator to form a lossy integrator
- Performance of the minor variants of the two integrator loop structures are comparable

# Filter Design/Synthesis Considerations


## Cascaded Biquads

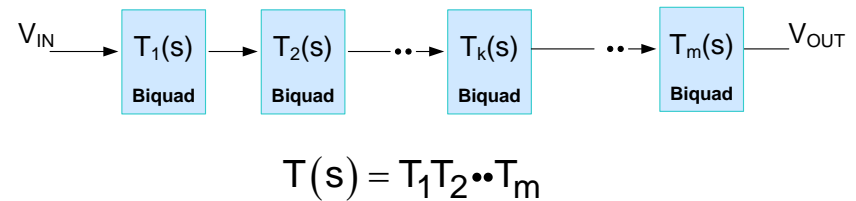

## Leapfrog

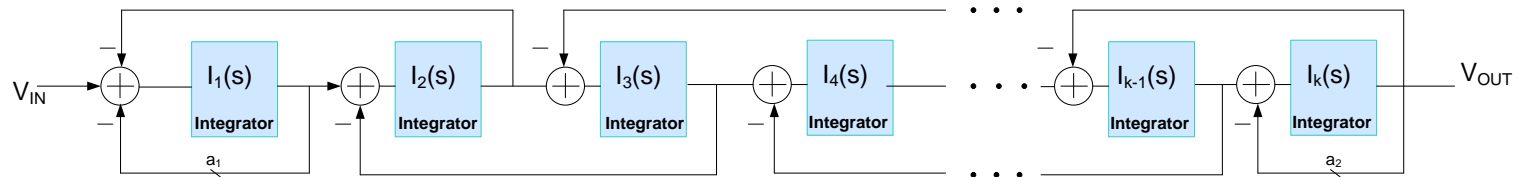
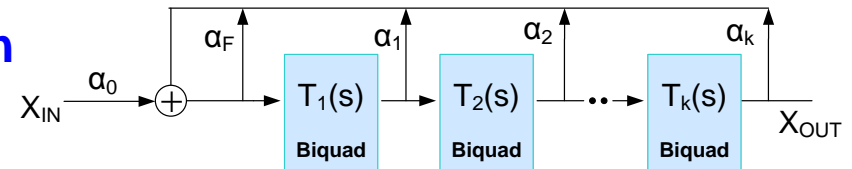
## Multiple-loop Feedback – One type shown



Observation: All filters are comprised of summers, biquads and integrators

And biquads usually made with summers and integrators

Integrated filter design generally focused on design of integrators, summers, and amplifiers (Op Amps)

**Will now focus on the design of integrators, summers, and op amps**

**End of Lecture 24**