### EE 508 Lecture 25

### **Integrator Design**

#### Review from last time

### Parasitic Capacitances on Floating Nodes



Parasitic capacitances ideally have no affect on filter when on a non-floating node but directly affect transfer function when they appear on a floating node

Parasitic capacitances are invariably large, nonlinear, and highly process dependent in integrated filters. Thus, it is difficult to build accurate integrated filters if floating nodes are present

Generally avoid floating nodes, if possible, in integrated filters

#### Review from last time

### Which type of Biquad is really used?



#### Review from last time Filter Design/Synthesis Considerations



Observation: All filters are comprised of summers, biquads and integrators

And biquads usually made with summers and integrators

Integrated filter design generally focused on design of integrators, summers, and amplifiers (Op Amps)

# Will now focus on the design of integrators, summers, and op amps

# Basic Filter Building Blocks

(particularly for integrated filters)



- Summers
- Operational Amplifiers

### **Integrator Characteristics of Interest**

$$X_{IN} = \frac{I_0}{s}$$

$$X_{OUT}$$

$$I(s) = \frac{I_0}{s}$$

Properties of an ideal integrator:

$$|I(j\omega)| = \frac{I_0}{\omega}$$
$$\angle I(j\omega) = -90^0$$
$$|I(jI_0)| = 1$$

Gain decreases with  $1/\omega$ 

Phase is a constant -90°

Unity Gain Frequency = 1

How important is it that an integrator have all 3 of these properties?

### **Integrator Characteristics of Interest**



How important is it that an integrator have all 3 of these properties?

Consider a filter example:



Band edges proportional to  $I_0$ Phase critical to make Q expression valid

In many (most) applications it is critical that an integrator be very nearly ideal

(in the frequency range of interest)





$$s_{s}^{2} + s_{s}^{2} \left( \frac{1}{2} + \frac{1}{Q} + \frac{GB_{s}}{4} \right) + s_{s} \frac{1}{4Q} \left( 1 + GB_{s} \right) + \frac{GB_{s}}{4} = 0$$



Inverting Active RC Integrator

Are there other integrator structures?



Termed an OTA-C or a gm-C integrator





Termed a TA-C integrator



Termed MOSFET-C integrator





Are there other integrator structures?



- Output current is independent of Z<sub>L</sub>
- Thus output impedance is  $\infty$  so provides current output

Termed active RC current-mode integrator



There are many different ways to build an inverting integrator

### **Integrator Functionality**



**Basic Active RC Inverting Integrator** 





**Summing Integrator** 



Many different types of functionality from basic inverting integrator Same modifications exist for other integrator architectures

### **Integrator-Based Filter Design**



Any of these different types of integrators can be used to build integrator-based filters

# Are new integrators still being invented?

USPTO PATENT FULL-TEXT AND IMAGE DATABASE



Searching US Patent Collection ...

-

Results of Search in US Patent Collection db for: TTL/integrator: 419 patents. Hits 1 through 50 out of 419 PAT. NO. Title

1 8,290,897 System integrator and method for mapping dynamic COBOL constructs to object instances for the automatic integration to object-oriented computing systems

- 2 <u>8,283,966</u> Integrator circuit
- 3 <u>8,275,307</u> Vehicle audio integrator
- 4 8,264,388 <sup>■</sup> Frequency integrator with digital phase error message for phase-locked loop applications
- 5 8,258,990 Integrator, resonator, and oversampling A/D converter
- 6 8,253,473 Integrated circuit of an integrator with enhanced stability and related stabilization method
- 7 8,199,038 Active resistance-capacitor integrator and continuous-time sigma-delta modulator with gain control function
- 8 8,164,873 Integrator and circuit-breaker having an integrator
- 9 8,145,597 System integrator and method for mapping dynamic COBOL constructs to object instances for the automatic integration to object-oriented computing systems
- 10 8,129,972 T Single integrator sensorless current mode control for a switching power converter
- 11 8,125,262 Low power and low noise switched capacitor integrator with flexible input common mode range
- 12 8,098,377 Electric gated integrator detection method and device thereof
- 13 8,081,098 Integrator, delta-sigma modulator, analog-to-digital converter and applications thereof
- 14 8,035,439 Multi-channel integrator
- 15 8,031,404 T Fly's eye integrator, illuminator, lithographic apparatus and method
- 16 8,029,144 Color mixing rod integrator in a laser-based projector
- 17 8,028,304 Component integrator
- 18 8,013,657 Temperature compensated integrator
- 19 8,011,810 Light integrator for more than one lamp
- 20 <u>7,997,740</u> Integrator unit
- 21 7,965,795 Prevention of integrator wind-up in PI type controllers
- 22 7,965,151 Pulse width modulator with two-way integrator
- 23 7,954,962 🔳 Laser image display, and optical integrator and laser light source package used in such laser image display
- 24 7,943,893 Illumination optical system and image projection device having a rod integrator uniformizing spatial energy distribution of diffused illumination beam
- 25 7,933,812 System integrator and commodity roll-up

- 26 7,932,960 Integrator array for HUD backlighting
- 27 7,911,256 **Dual integrator circuit for analog front end (AFE)**
- 28 7.907.115 Digitally synchronized integrator for noise rejection in system using PWM dimming signals to control brightness of cold cathode fluorescent lamp for backlighting liquid crystal display.
- 29 7,905,631 Illumination system having coherent light source and integrator rotatable transverse the illumination axis
- 30 7,884,662 Multi-channel integrator
- 31 7,880,969 Deptical integrator for an illumination system of a microlithographic projection exposure apparatus
- 32 7,873,223 Cognition integrator and language
- 33 7,834,963 Deptical integrator
- 34 7,830,197 Adjustable integrator using a single capacitance
- 35 <u>RE41,792</u> Controllable integrator
- 36 7,788,309 TInterleaved comb and integrator filter structures
- 37 7,773,730 Voice record integrator
- 38 7,729,577 T Waveguide-optical Kohler integrator utilizing geodesic lenses
- 39 7,726,819 T Structure for protecting a rod integrator having a light shield plate with an opening
- 40 7.724.063 Integrator-based common-mode stabilization technique for pseudo-differential switched-capacitor circuits
- 41 7,714,634 Pseudo-differential active RC integrator
- 42 7,706,072 Deptical integrator, illumination optical device, photolithograph, photolithography, and method for fabricating device
- 43 7,696,913 I Signal processing system using delta-sigma modulation having an internal stabilizer path with direct output-to-integrator connection
- 44 7,693,430 Burst optical receiver with AC coupling and integrator feedback network
- 45 7,679,540 Double sampling DAC and integrator
- 46 7,671,774 Analog-to-digital converter with integrator circuit for overload recovery
- 47 7,658,497 Rod integrator holder and projection type video display
- 48 7.629,917 Integrator and cyclic AD converter using the same
- 49 7,619,550 Delta-sigma AD converter apparatus using delta-sigma modulator circuit provided with reset circuit resetting integrator
- 50 7,611,246 Trojection display and optical integrator

	PAT. NO.	Title
51	<u>7,605,645</u>	Transconductor, integrator, and filter circuit
52	7,599,631	Burst optical receiver with AC coupling and integrator feedback network
53	<u>7,575,159</u>	Point of sale integrator
54	<u>7,570,032</u>	Regulator with integrator in feedback signal
55	<u>7,565,326</u>	Dialect independent multi-dimensional integrator using a normalized language platform and secure controlled access
56	<u>7,554,400</u>	TIntegrator and error amplifier
57	<u>7,543,945</u>	Integrator module with a collimator and a compact light source and projection display having the same
58	7,532,145	THigh resolution and wide dynamic range integrator
59	7,528,818	<sup>T</sup> Digitally synchronized integrator for noise rejection in system using PWM dimming signals to control brightness of light source
60	<u>7,511,648</u>	Integrating/SAR ADC and method with low integrator swing and low complexity
61	<u>7,474,241</u>	Delta-sigma modulator provided with a charge sharing integrator
62	<u>7,471,456</u>	Optical integrator, illumination optical device, exposure device, and exposure method
63	<u>7,454,750</u>	Integrator adaptor and proxy based composite application provisioning method and apparatus
64	<u>7,447,049</u>	<sup>T</sup> Single ended flyback power supply controllers with integrator to integrate the difference between feedback signal a reference signal
65	<u>7,423,729</u>	Method of monitoring the light integrator of a photolithography system
66	<u>7,417,485</u>	Differential energy difference integrator
67	<u>7,415,716</u>	Component integrator
68	<u>7,411,534</u>	Analog-to-digital converter (ADC) having integrator dither injection and quantizer output compensation
69	<u>7,411,198</u>	Integrator circuitry for single channel radiation detector
70	<u>7,395,090</u>	Personal portable integrator for music player and mobile phone
71	<u>7,385,426</u>	Low current offset integrator with signal independent low input capacitance buffer circuit
72	<u>7,379,160</u>	Optical integrator, illumination optical device, exposure apparatus, and exposure method
73	<u>7,352,510</u>	Light-pipe integrator for uniform irradiance and intensity
74	<u>7.345,285</u>	Spectra acquisition system with threshold adaptation integrator
75	<u>7,333,626</u>	Arbitrary coverage angle sound integrator
		Received and the second s

- 76 <u>7,324,654</u> Arbitrary coverage angle sound integrator
- 77 7.324,025 Non-integer interpolation using cascaded integrator-comb filter
- 78 7,315,268 Integrator current matching
- 79 7,304,592 TMethod of adding a dither signal in output to the last integrator of a sigma-delta converter and relative sigma-delta converter
- 80 7,280,405 Integrator-based current sensing circuit for reading memory cells
- 81 7,262,056 Enhancing intermolecular integration of nucleic acids using integrator complexes
- 82 7,243,844 Point of sale integrator
- 83 7,242,333 Alternate sampling integrator
- 84 7,205,849 Phase locked loop including an integrator-free loop filter
- 85 7,187,948 Personal portable integrator for music player and mobile phone
- 86 7,182,468 Dual lamp illumination system using multiple integrator rods
- 87 7,180,357 T Operational amplifier integrator
- 88 7,170,959 Tailored response cascaded integrator comb digital filter and methodology for parallel integrator processing
- 89 7,155,470 Variable gain integrator
- 90 7,152,981 Projection illumination system with tunnel integrator and field lens
- 91 7,152,084 Parallelized infinite impulse response (IIR) and integrator filters
- 92 7,150,968 Bridging INtegrator-2 (Bin2) nucleic acid molecules and proteins and uses therefor
- 93 7,138,848 Switched capacitor integrator system
- 94 7,130,764 Robust DSP integrator for accelerometer signals
- 95 7,102,844 Dual direction integrator for constant velocity control for an actuator using sampled back EMF control
- 96 7,102,548 Cascaded integrator comb filter with arbitrary integer decimation value and scaling for unity gain
- 97 7,098,845 Apparatus for generating an integrator timing reference from a local oscillator signal
- 98 7,098,827 Integrator circuit
- 99 7,098,718 Tunable current-mode integrator for low-frequency filters
- 100 7,087,881 Solid state image pickup device including an integrator with a variable reference potential

### Example – OTA-C Tow Thomas Biquad







$$\frac{V_{OUT}}{V_{IN}} = \frac{g_{m3}g_{m2}}{\left(s^{2}C_{1}C_{2} + sg_{m4}C_{2} + g_{m1}g_{m2}\right)}$$
Assume  $g_{m1} = g_{m2} = g_{m}$ ,  $C_{1} = C_{2} = C$ 

$$\frac{V_{OUT}}{V_{IN}} = \frac{\left(\frac{g_{m3}}{g_{m}}\right)\frac{g_{m}^{2}}{C^{2}}}{\left(s^{2} + s\left(\frac{g_{m4}}{g_{m}}\right)\frac{g_{m}}{C} + \frac{g_{m}^{2}}{C^{2}}\right)}$$

express as



 $\omega_0 = \frac{g_m}{C} \qquad Q = \frac{g_m}{g_{m4}}$ 

#### **Basic Integrator Functionality**



Summing (Multiple-Input) Inverting/Noninverting



Summing (Multiple-Input) Lossy Inverting/Noninverting





**Balanced Differential** 



#### **Basic Integrator Functionality**



- An inverting/noninverting integrator pair define a family of integrators
- All integrator functional types can usually be obtained from the inverting/noninverting integrator pair
- Suffices to focus primarily on the design of the inverting/noninverting integrator pair since properties of class primarily determined by properties of integrator pair





Summing Inverting Integrator



Lossy Summing Inverting Integrator



Lossy Inverting Integrator



Balanced Differential Inverting Integrator



Fully Differential Inverting Integrator

## **Integrator Types**



#### Will consider first the Voltage Mode type of integrators

# Voltage Mode Integrators

- Active RC (Feedback-based)
- MOSFET-C (Feedback-based)
- OTA-C
- TA-C Sometimes termed "current mode"
- Switched CapacitorSwitched Resistor

Will discuss later

### Active RC Voltage Mode Integrator



- Limited to low frequencies because of Op Amp limitations
- No good resistors for monolithic implementations
   Area for passive resistors is too large at low frequencies
   Some recent work by Haibo Fei shows promise for some audio frequency applications
- · Capacitor area too large at low frequencies for monolithic implementatins
- Active devices are highly temperature dependent, proc. dependent, and nonlinear
- No practical tuning or trimming scheme for integrated applications with passive resistors

# MOSFET-C Voltage Mode Integrator



- Limited to low frequencies because of Op Amp limitations
- Area for R<sub>MOS</sub> is manageable !
- Active devices are highly temperature dependent, process dependent
- Potential for tuning with  $\mathrm{V}_\mathrm{C}$
- Highly Nonlinear (can be partially compensated with cross-coupled input

#### A Solution without a Problem

## MOSFET-C Voltage Mode Integrator





- Improved Linearity
- Some challenges for implementing  $\mathrm{V}_{\mathrm{C}}$

#### Still A Solution without a Problem

### OTA-C Voltage Mode Integrator





#### Inverting

- Requires only two components
- Inverting and Noninverting structures of same complexity
- Good high-frequency performance
- Small area
- Linearity is limited (no feedback in integrator)
- Susceptible to process and temperature variations
- Tuning control can be readily added

#### Widely used in high frequency applications

### OTA-C Voltage Mode Integrator



#### Programmable Integrator

### OTA-C Voltage Mode Integrator



Lossy Integrator

But R<sub>F</sub> is typically too large for integrated applications

# End of Lecture 25