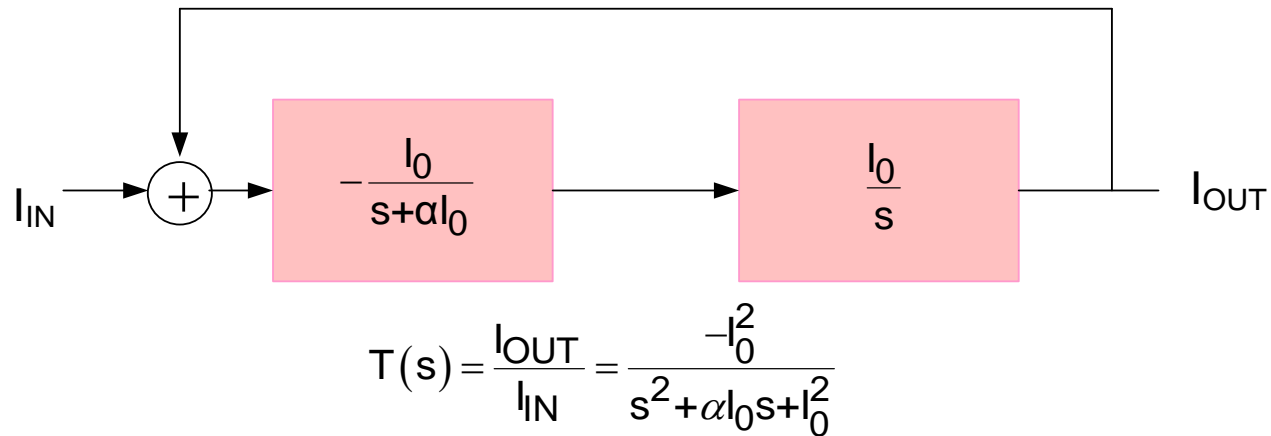


EE 508

Lecture 31

Switched Current Filters



Current-Mode Filters



Basic Concepts of Benefits of Current-Mode Filters:

- Large voltage swings difficult to maintain in integrated processes because of linearity concerns
- Large voltage swings slow a circuit down because of time required to charge capacitors
- Voltage swings can be very small when currents change
- Current swings are not inherently limited in integrated circuits (only voltage swings)
- With low voltage swings, current-mode circuits should dissipate little power

Current-Mode Filters

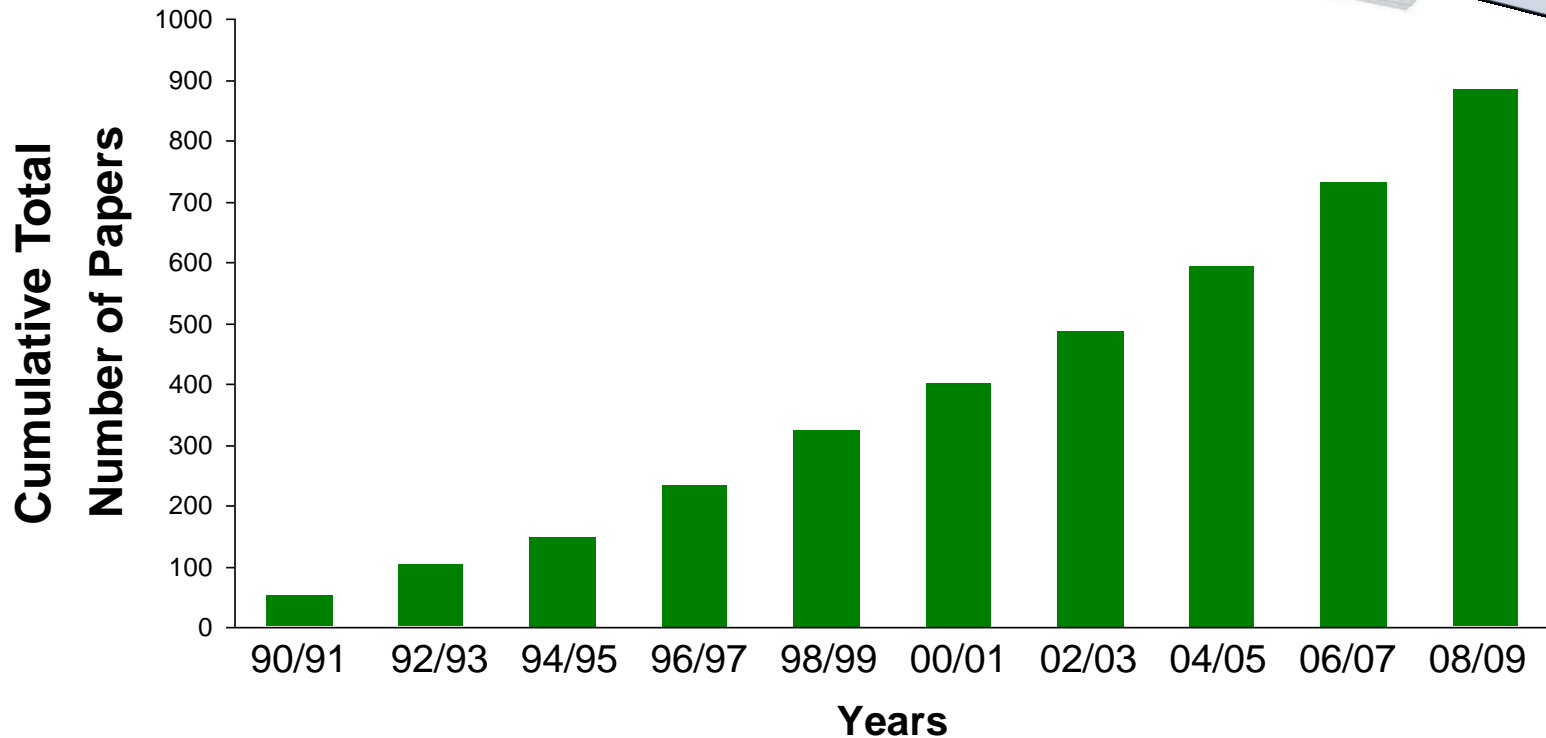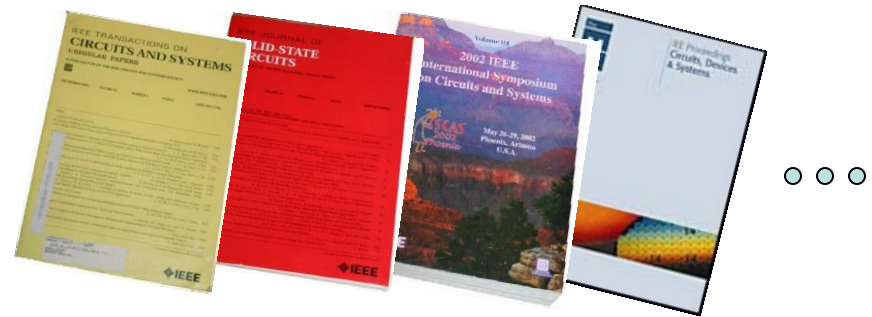

Steady growth in research in the area since 1990 and publication rate is growing with time !!

Current-Mode Filters


The Conventional Wisdom:

- Current-Mode circuits operate at higher-frequencies than voltage-mode counterparts
- Current-Mode circuits operate at lower supply voltages and lower power levels than voltage-mode counterparts
- Current-Mode circuits are simpler than voltage-mode counterparts
- Current-Mode circuits offer better linearity than voltage-mode counterparts

This represents four really significant benefits of current-mode circuits!


Some Current-Mode Integrators

OTA-C

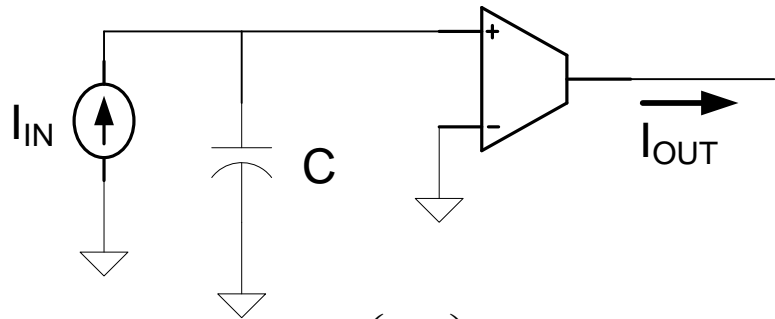

$$I_{OUT} = \left(\frac{g_m}{C_s} \right) I_{IN}$$

Noninverting

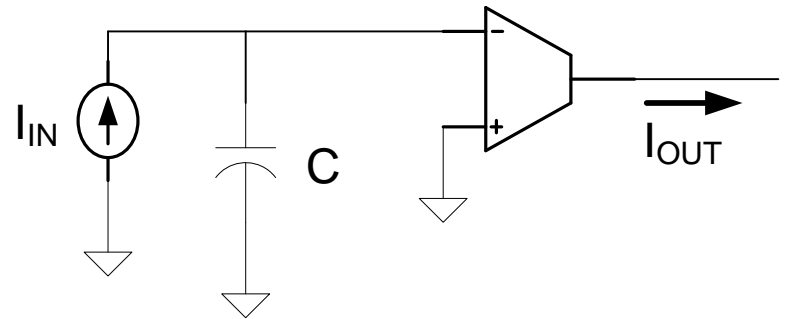


$$I_{OUT} = \left(\frac{-g_m}{C_s} \right) I_{IN}$$

Inverting

- Summing inputs really easy to obtain
- Loss is easy to add
- Same component count as voltage-mode integrators
- Many argue that since only interested in currents, can operate at lower voltages and higher frequencies

Current-Mode Two Integrator Loop



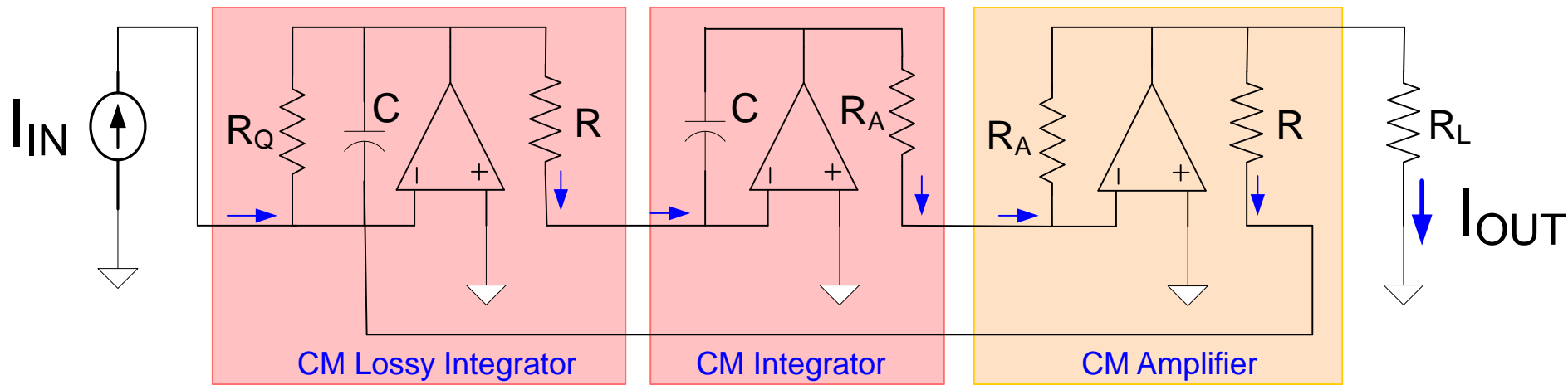


- Straightforward implementation of the two-integrator loop
- Simple structure

Review from last time

Current-Mode Two Integrator Loop

An Observation:

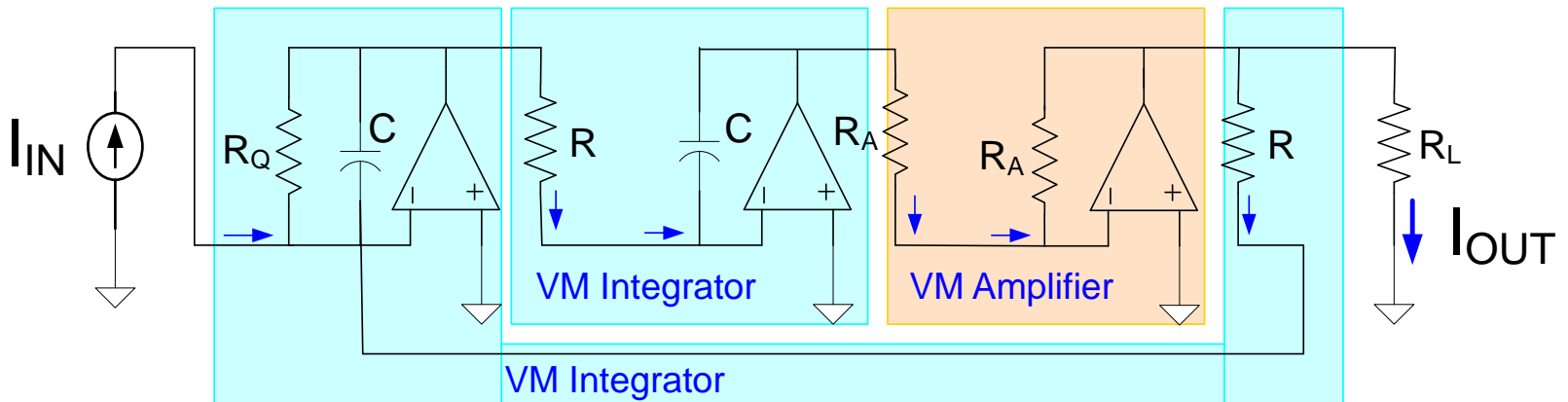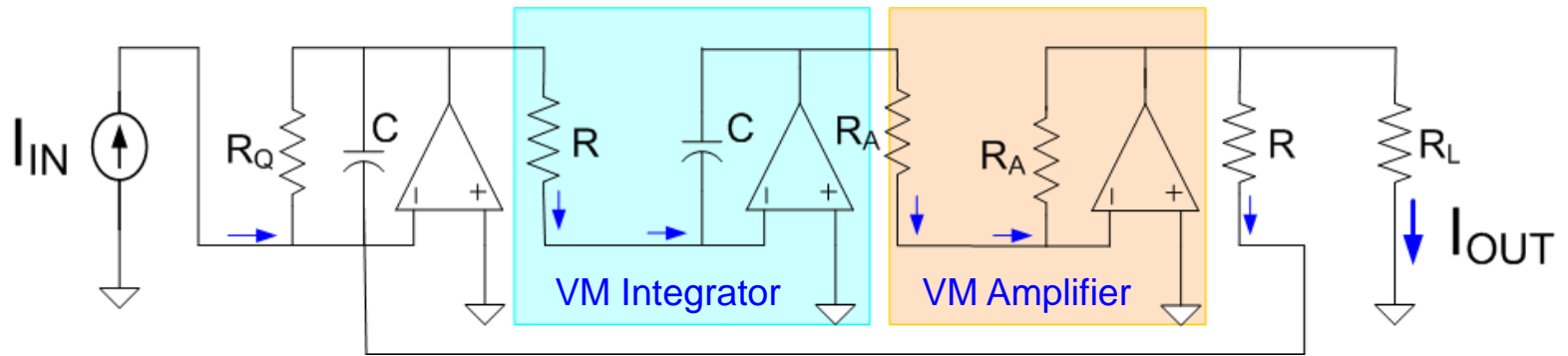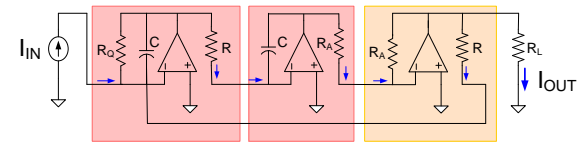

This circuit is identical to another one with two voltage-mode integrators and a voltage-mode amplifier !

Observation

- Many papers have appeared that tout the performance advantages of current-mode circuits
- In all of the current-mode papers that this instructor has seen, no attempt is made to provide a quantitative comparison of the key performance features of current-mode circuits with voltage-mode counterparts
- All justifications of the advantages of the current-mode circuits this instructor has seen are based upon qualitative statements

Observations (cont.)

- It appears easy to get papers published that have the term “current-mode” in the title
- Over 900 papers have been published in IEEE forums alone !
- Some of the “current-mode” filters published perform better than other “voltage-mode” filters that have been published
- We are still waiting for even one author to quantitatively show that current-mode filters offer even one of the claimed four advantages over their voltage-mode counterparts

Will return to a discussion of Current-Mode filters later

Switched-Current Filters

Basic idea introduced by Hughes and Bird at ISCAS 1989

[Switched currents-a new technique for analog sampled-data signal processing](#)

JB Hughes, NC Bird... - Circuits and Systems, 1989 ... , 2002 - ieeexplore.ieee.org


INTRODUCTION The enormous complexity available in state-of-the-art CMOS processing has made possible the integration of complete systems, including both digital and analog signal processing functions, within the same chip Through the last decade, the **switched** capacitor technique ...

[Cited by 151](#) - [Related articles](#)

Technique introduced directly in the z-domain

Switched-Current Filters

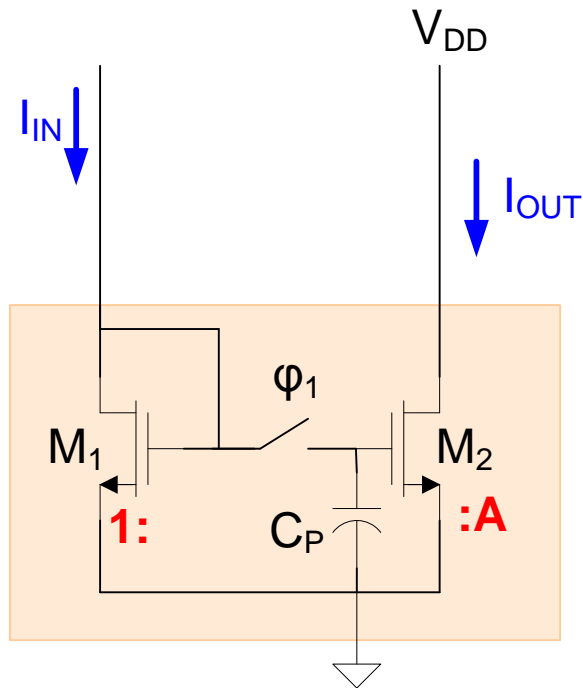Basic idea introduced by Hughes and Bird at ISCAS 1989



$$I_{OUT} = \begin{cases} AI_{IN}(t) & \text{for } \phi_1 \text{ closed} \\ AI_{IN}(T_{SW}) & \text{for } \phi_1 \text{ open} \end{cases}$$

If Φ_1 is a periodic signal and if I_{IN} is also appropriately clocked, the input/output currents of this circuit can be represented with the difference equation

$$I_{OUT}(nT) = AI_{IN}(nT-T)$$

This switched mirror becomes a delay element

“Gain” A is that of a current mirror

A can be accurately controlled

Circuit is small and very fast

Concept can be extended to implement arbitrary difference equation

Difference equation characterizes filter $H(z)$

Need only current mirrors and switches


Truly a “current-mode” circuit

Review from last time

Switched-Current Filters

Basic idea introduced by Hughes and Bird at ISCAS 1989

$$I_{OUT}(nT) = A I_{IN}(nT-T)$$

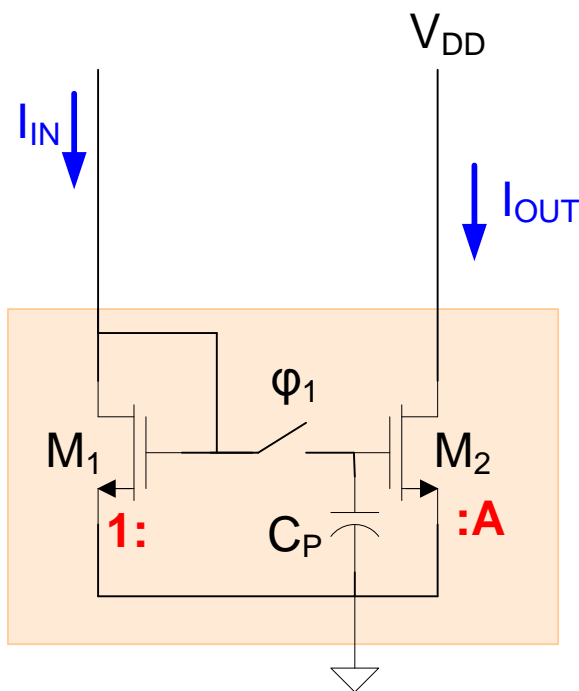

C_p is parasitic gate capacitance on M_2

Very low power dissipation

Potential to operate at very low voltages


Potential for accuracy of a SC circuit at both low and high frequencies but without the Op Amp and large C ratios

Neither capacitor or resistor values needed to do filtering!

A completely new approach to designing filters that offers potential for overcoming most of the problems plaguing filter designers for decades !

Before developing Switch-Current concept, need to review background information in s to z domain transformations

s-domain to z-domain transformations

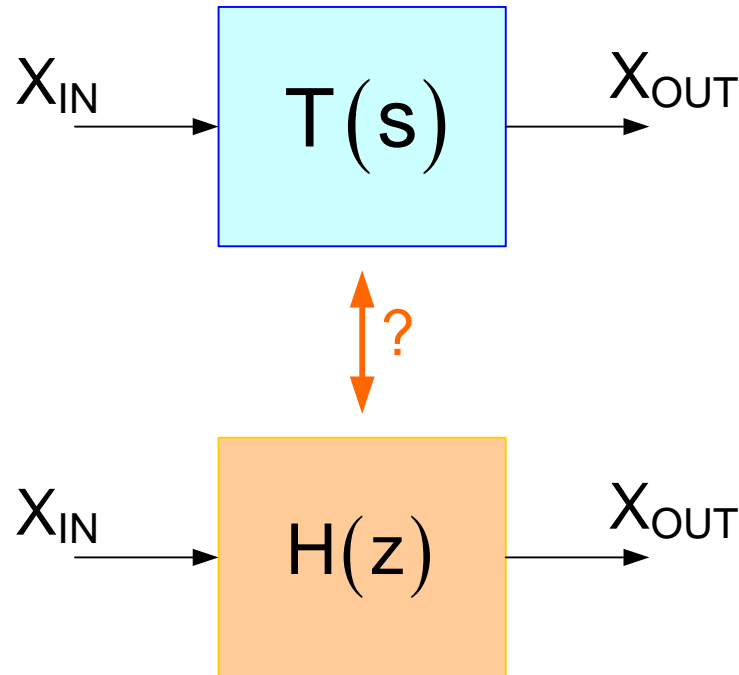


For a given $T(s)$ would like to obtain a function $H(z)$ or for a given $H(z)$ would like to obtain a $T(s)$ such that preserves the magnitude and phase response

Mathematically, would like to obtain the relationship:

$$T(s) \Big|_{s=j\omega} = H(z) \Big|_{z=e^{j\omega T}}$$

s-domain to z-domain transformations

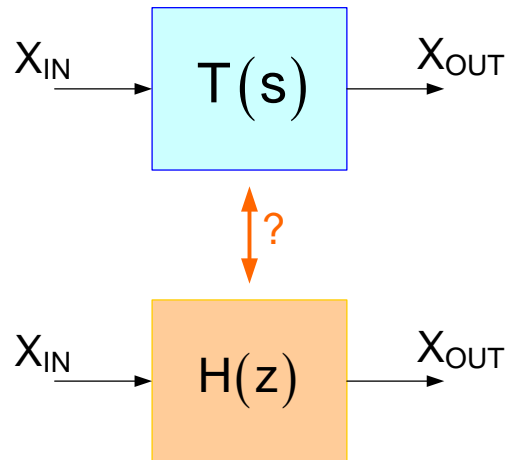

want:
$$T(s)|_{s=j\omega} = H(z)|_{z=e^{j\omega T}}$$


equivalently, want:

$$T(s) = H(z)|_{z=e^{sT}}$$

But if this were to happen, $T(s)$ would not be a rational fraction in s with real coeff.

Thus, it is impossible to obtain this mapping between $T(s)$ and $H(z)$

s-domain to z-domain transformations

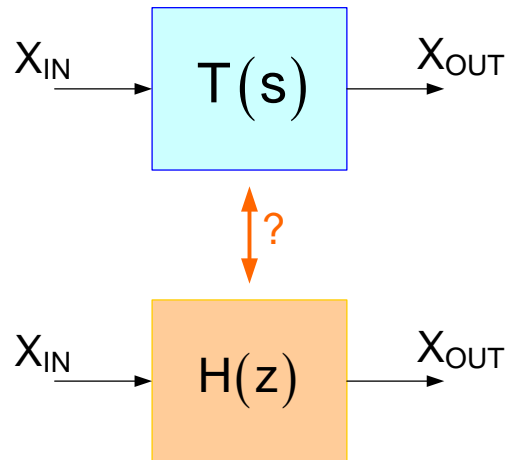

goal: $T(s) = H(z) \Big|_{z=e^{sT}}$

If can't achieve this goal, would like to map imaginary axis to unit circle and map stable filters to stable filters


consider: $z = e^{sT}$

Case 1: $z = e^{sT} \approx \sum_{i=0}^{\infty} \frac{1}{i!} (sT)^i$
 $z = \sum_{i=0}^{\infty} \frac{1}{i!} (sT)^i \approx 1 + sT$

$$s = \frac{z-1}{T}$$

Termed the Forward Euler transformation

s-domain to z-domain transformations

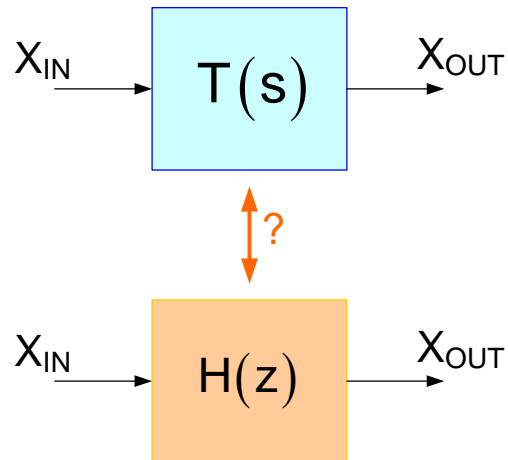


$$s = \frac{z-1}{T}$$

Forward Euler transformation

- Doesn't map imaginary axis in s-plane to unit circle in z-plane
- Doesn't guarantee stable filter will map to stable filter
- But mapping may give stable filter with good frequency response

s-domain to z-domain transformations

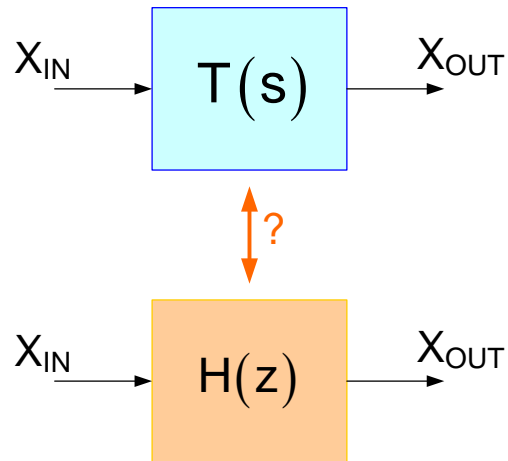

consider: $z = e^{sT}$


Case 2:
$$z = e^{sT} = \frac{1}{e^{-sT}} = \frac{1}{\sum_{i=0}^{\infty} \frac{1}{i!} (-sT)^i} \approx \frac{1}{1-sT}$$

$$z \approx \frac{1}{1-sT}$$

$$s = \left(\frac{1}{T} \right) \frac{z-1}{z}$$

Termed the Backward Euler transformation

s-domain to z-domain transformations

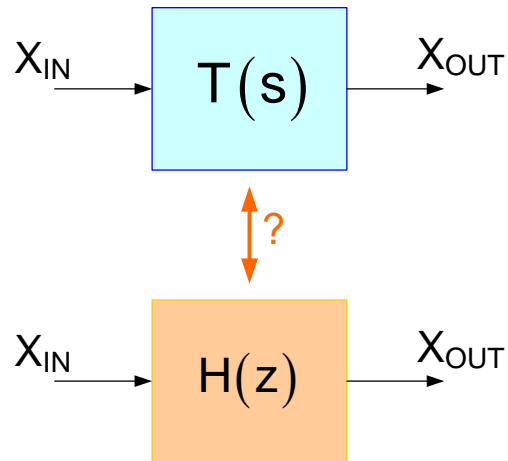


$$s = \left(\frac{1}{T} \right) \frac{z-1}{z}$$

Backward Euler transformation

- Doesn't map imaginary axis in s-plane to unit circle in z-plane
- Does guarantee stable filter will map to stable filter

s-domain to z-domain transformations

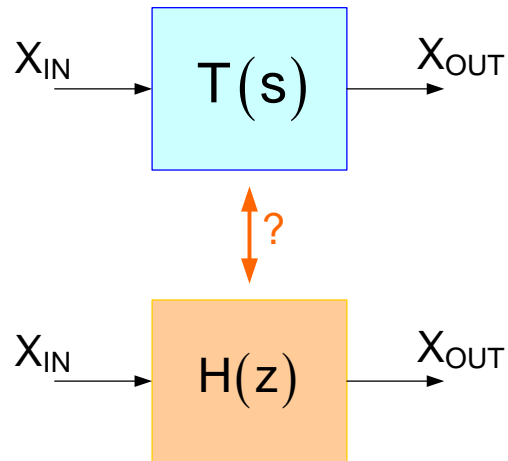

consider: $z = e^{sT}$

Case 3:


$$z = e^{sT} = \frac{e^{\frac{sT}{2}}}{e^{-\frac{sT}{2}}} = \frac{\sum_{i=0}^{\infty} \frac{1}{i!} \left(\frac{sT}{2}\right)^i}{\sum_{i=0}^{\infty} \frac{1}{i!} \left(-\frac{sT}{2}\right)^i} \approx \frac{1 + s\frac{T}{2}}{1 - s\frac{T}{2}}$$

solving for s, obtain

$$s = \frac{2}{T} \bullet \frac{z-1}{z+1}$$

Termed the Bilinear z transformation

s-domain to z-domain transformations

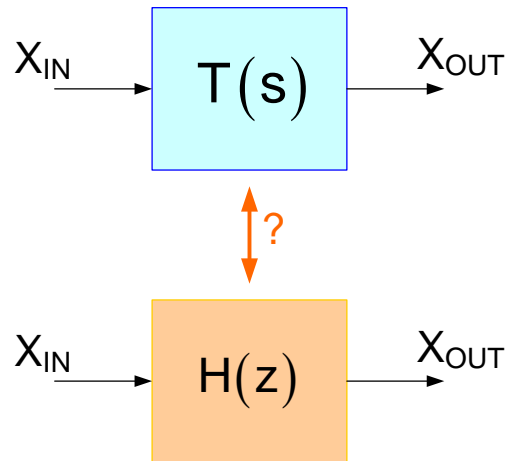


$$s = \frac{2}{T} \cdot \frac{z-1}{z+1}$$

Bilinear z transformation

- Maps imaginary axis in s-plane to unit circle in z-plane (preserves shape, distorts frequency axis)
- Does guarantee stable filter will map to stable filter
- Bilinear z transformation is widely used

s-domain to z-domain transformations

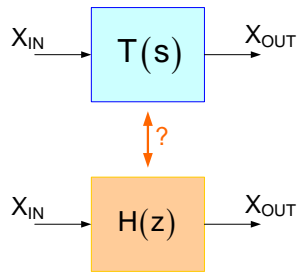

consider: $z = e^{sT}$

Three Popular Transformations

$$s = \frac{z-1}{T}$$

Forward Euler

$$s = \frac{1-z^{-1}}{Tz^{-1}}$$

$$s = \frac{z-1}{Tz}$$

Backward Euler


$$s = \frac{1-z^{-1}}{T}$$

$$s = \frac{2}{T} \cdot \frac{z-1}{z+1}$$

Bilinear z
transform

$$s = \frac{2}{T} \cdot \frac{1-z^{-1}}{1+z^{-1}}$$

s-domain to z-domain transformations

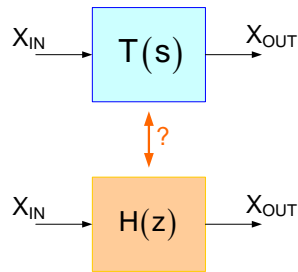

Three Popular Transformations

$$s = \frac{z-1}{T}$$

Forward Euler

$$s = \frac{1-z^{-1}}{Tz^{-1}}$$

$$s = \frac{z-1}{Tz}$$

Backward Euler

$$s = \frac{1-z^{-1}}{T}$$


$$s = \frac{2}{T} \cdot \frac{z-1}{z+1}$$

Bilinear z transform

$$s = \frac{2}{T} \cdot \frac{1-z^{-1}}{1+z^{-1}}$$

- Transformations of standard approximations in s-domain are the corresponding transformations in the z-domain
- Transformations are not unique
- Transformations cause warping of the imaginary axis and may cause change in basic shape
- Transformations do not necessarily guarantee stability
- These transformations preserve order

z-domain integrators

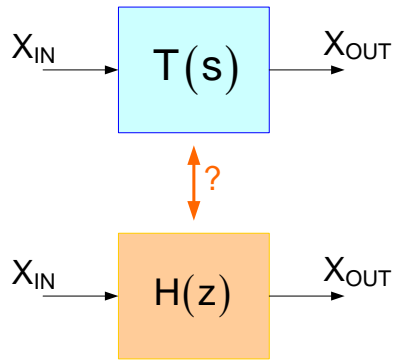

$$T(s) = \frac{I_0}{s}$$

Some z-domain integrators

$$H(z) = \begin{cases} \frac{T I_0}{z-1} & \text{Forward Euler} \\ \frac{I_0 T z}{z-1} & \text{Backward Euler} \\ \frac{T I_0}{2} \left(\frac{z+1}{z-1} \right) & \text{Bilinear z} \end{cases}$$

Three Popular Transformations

$$s = \frac{z-1}{T}$$

Forward Euler

$$s = \frac{1-z^{-1}}{T z^{-1}}$$

$$s = \frac{z-1}{T z}$$

Backward Euler

$$s = \frac{1-z^{-1}}{T}$$

$$s = \frac{2}{T} \cdot \frac{z-1}{z+1}$$

Bilinear z transform

$$s = \frac{2}{T} \cdot \frac{1-z^{-1}}{1+z^{-1}}$$

Corresponding difference equations:

$$V_{OUT}(nT+T) = T I_0 V_{IN}(nT) + V_{OUT}(nT)$$

Forward Euler



$$V_{OUT}(nT+T) = I_0 T V_{IN}(nT+T) + V_{OUT}(nT)$$

Backward Euler

$$V_{OUT}(nT+T) = \frac{T I_0}{2} (V_{IN}(nT+T) + V_{IN}(nT)) + V_{OUT}(nT)$$

Bilinear z

z-domain lossy integrators

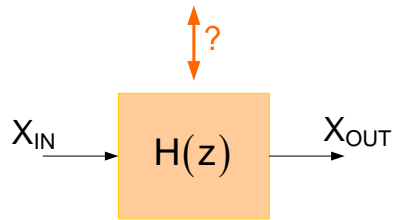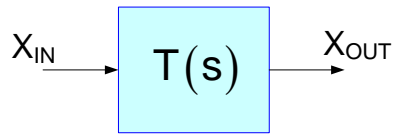

$$T(s) = \frac{l_0}{s + \alpha}$$

Three Popular Transformations

$$s = \frac{z-1}{T}$$

Forward Euler

$$s = \frac{1-z^{-1}}{Tz^{-1}}$$

$$s = \frac{z-1}{Tz}$$

Backward Euler

$$s = \frac{1-z^{-1}}{T}$$

$$s = \frac{2}{T} \cdot \frac{z-1}{z+1}$$

Bilinear z transform

$$s = \frac{2}{T} \cdot \frac{1-z^{-1}}{1+z^{-1}}$$

Some z-domain lossy integrators

$$H(z) = \begin{cases} \frac{Tl_0}{z-1+\alpha T} & \text{Forward Euler} \\ \frac{l_0 T z}{z(1+\alpha T)-1} & \text{Backward Euler} \\ \frac{Tl_0}{2} \left(\frac{z+1}{z \left(1 + \frac{\alpha T}{2} \right) + \left(\frac{\alpha T}{2} - 1 \right)} \right) & \text{Bilinear z} \end{cases}$$


Corresponding difference equations:

$$V_{OUT}(nT+T) = Tl_0 V_{IN}(nT) + [1-\alpha T] V_{OUT}(nT) \quad \text{Forward Euler}$$

$$(1+\alpha T) V_{OUT}(nT+T) = l_0 T V_{IN}(nT+T) + V_{OUT}(nT) \quad \text{Backward Euler}$$

$$\left(1 + \frac{\alpha T}{2} \right) V_{OUT}(nT+T) = \frac{Tl_0}{2} (V_{IN}(nT+T) + V_{IN}(nT)) + \left[1 - \frac{\alpha T}{2} \right] V_{OUT}(nT) \quad \text{Bilinear z}$$

z-domain lossy integrators

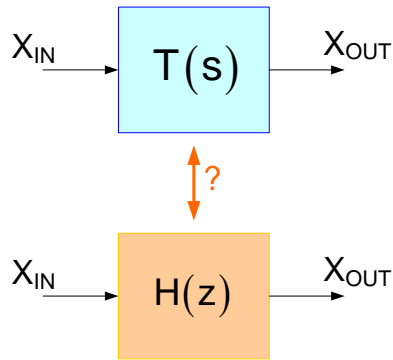

Some z-domain lossy integrators

$$T(s) = \frac{I_0}{s + \alpha}$$

$$H(z) = \begin{cases} \frac{TI_0}{z - 1 + \alpha T} \\ \frac{I_0 T z}{z(1 + \alpha T) - 1} \\ \frac{TI_0}{2} \left(\frac{z + 1}{z \left(1 + \frac{\alpha T}{2} \right) + \left(\frac{\alpha T}{2} - 1 \right)} \right) \end{cases}$$

Functional Form

$$\frac{G}{z - H}$$

Forward Euler

$$\frac{Gz}{zH - 1}$$

Backward Euler

$$G \left(\frac{z + 1}{z - H} \right)$$

Bilinear z

Corresponding difference equations:

$$V_{OUT}(nT + T) = G V_{IN}(nT) + H V_{OUT}(nT)$$

Forward Euler

$$H V_{OUT}(nT + T) = G V_{IN}(nT + T) + V_{OUT}(nT)$$



Backward Euler

$$V_{OUT}(nT + T) = G (V_{IN}(nT + T) + V_{IN}(nT)) + H V_{OUT}(nT)$$

Bilinear z

Switched-Current Integrator


Consider this circuit

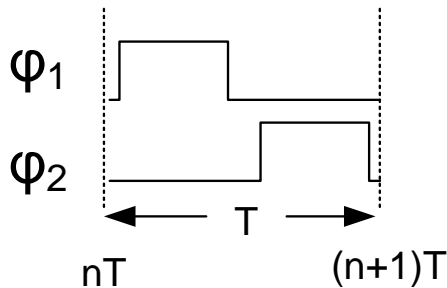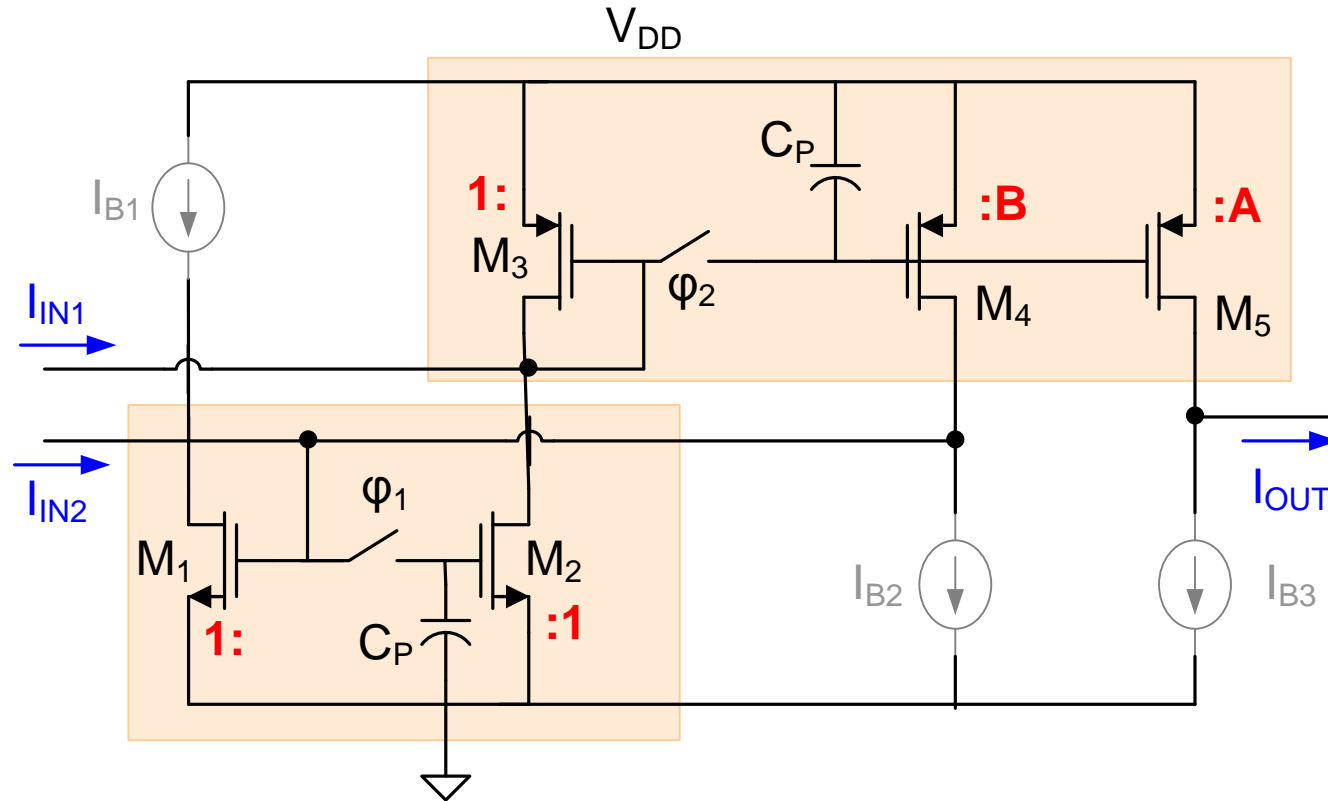

- Clocks complimentary, nonoverlapping
- Phase not critical

Assume inputs change only during phase Φ_2
(may be outputs from other like stages)

Switched-Current Integrator

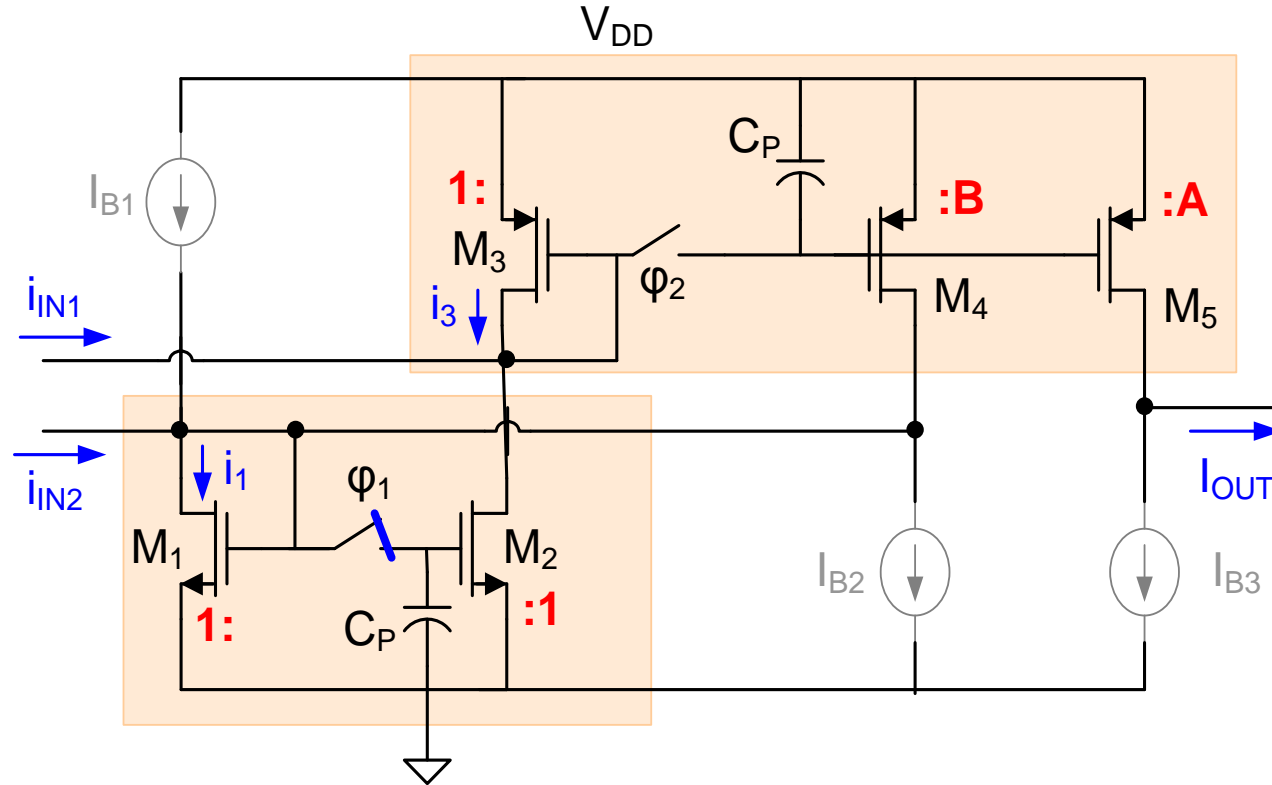


Consider Φ_1 closed, Φ_2 open ($nT-T < t < nT-T/2$)

$$i_1(t) = Bi_3(nT-T) + i_{iN2}(t)$$

Since current does not change during this interval

$$i_1(nT-T) = Bi_3(nT-T) + i_{iN2}(nT-T)$$

Switched-Current Integrator

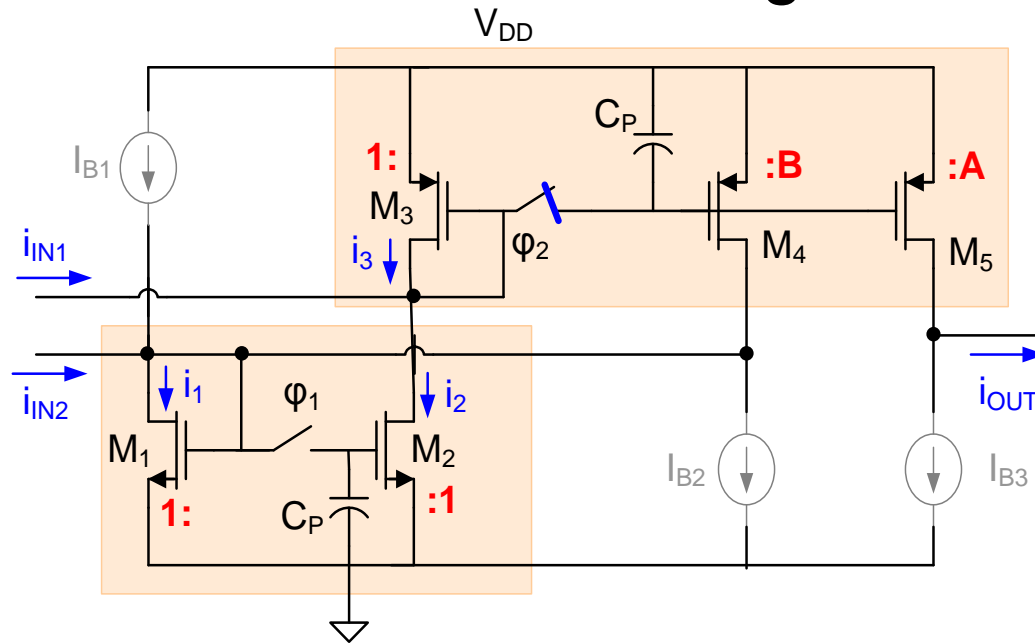

Consider Φ_2 closed, Φ_1 open ($nT - T/2 < t < nT$)

$$i_2(t) = i_1(nT - T)$$


$$i_2(t) = i_3(t) + i_{IN1}(t)$$

$$i_{OUT}(t) = Ai_3(t)$$

$$i_1(nT - T) = Bi_3(nT - T) + i_{IN2}(nT - T) \quad (\text{from first phase})$$

$$\left(\frac{1}{A}\right)i_{OUT}(t) + i_{IN1}(t) = \frac{B}{A}i_{OUT}(nT - T) + i_{IN2}(nT - T)$$

Switched-Current Integrator

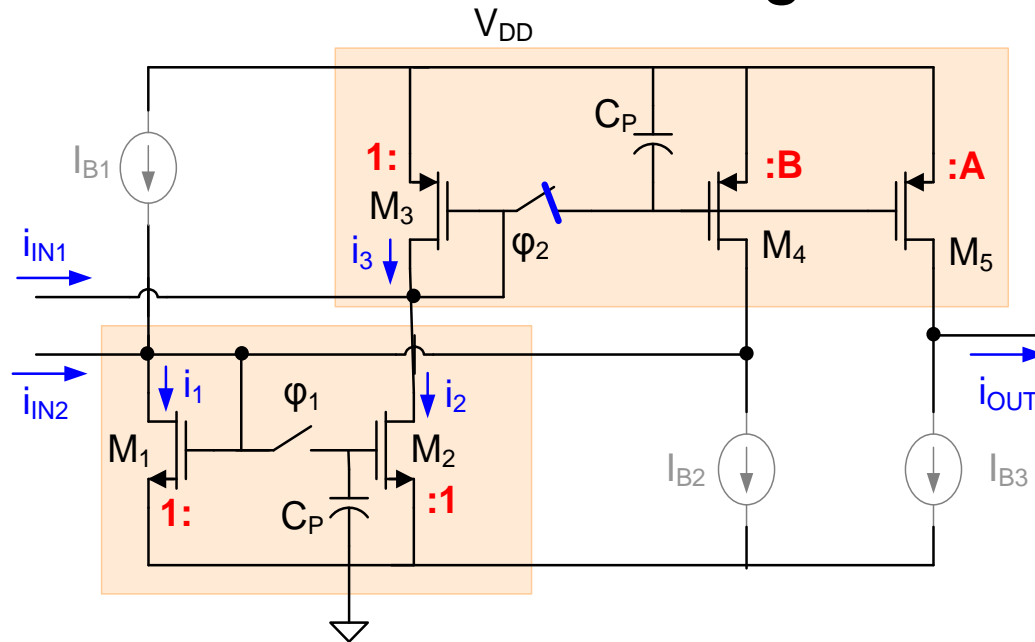

Consider Φ_2 closed, Φ_1 open ($nT - T/2 < t < nT$)

$$\left(\frac{1}{A}\right) i_{\text{OUT}}(t) + i_{\text{IN1}}(t) = \frac{B}{A} i_{\text{OUT}}(nT - T) + i_{\text{IN2}}(nT - T)$$


Evaluating at $t = nT$, we have

$$\left(\frac{1}{A}\right) i_{\text{OUT}}(nT) + i_{\text{IN1}}(nT) = \frac{B}{A} i_{\text{OUT}}(nT - T) + i_{\text{IN2}}(nT - T)$$

Taking z-transform, obtain

$$I_{\text{OUT}}(z) = \left(\frac{Az^{-1}}{1 - Bz^{-1}}\right) I_{\text{IN2}}(z) - \left(\frac{A}{1 - Bz^{-1}}\right) I_{\text{IN1}}(z)$$

Switched-Current Integrator

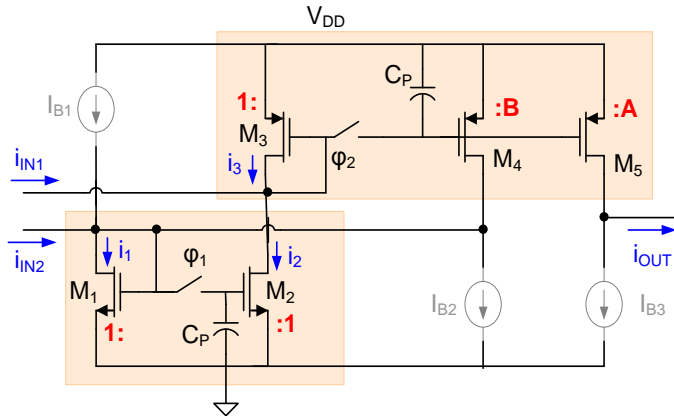

Recall lossy integrators:

$$H(z) = \begin{cases} \frac{Gz^{-1}}{1 - Hz^{-1}} & \text{Forward Euler} \\ \frac{G}{1 - Hz^{-1}} & \text{Backward Euler} \\ G \left(\frac{1 + z^{-1}}{1 - Hz^{-1}} \right) & \text{Bilinear } z \end{cases}$$

For H=1 becomes lossless


$$I_{OUT}(z) = \left(\frac{Az^{-1}}{1 - Bz^{-1}} \right) I_{IN2}(z) - \left(\frac{A}{1 - Bz^{-1}} \right) I_{IN1}(z)$$

If $I_{IN1}=0$, becomes Forward Euler integrator

If $I_{IN2}=0$, becomes Backward Euler integrator

If $I_{IN1} = -I_{IN2}$, becomes Bilinear Integrator

Switched-Current Integrator

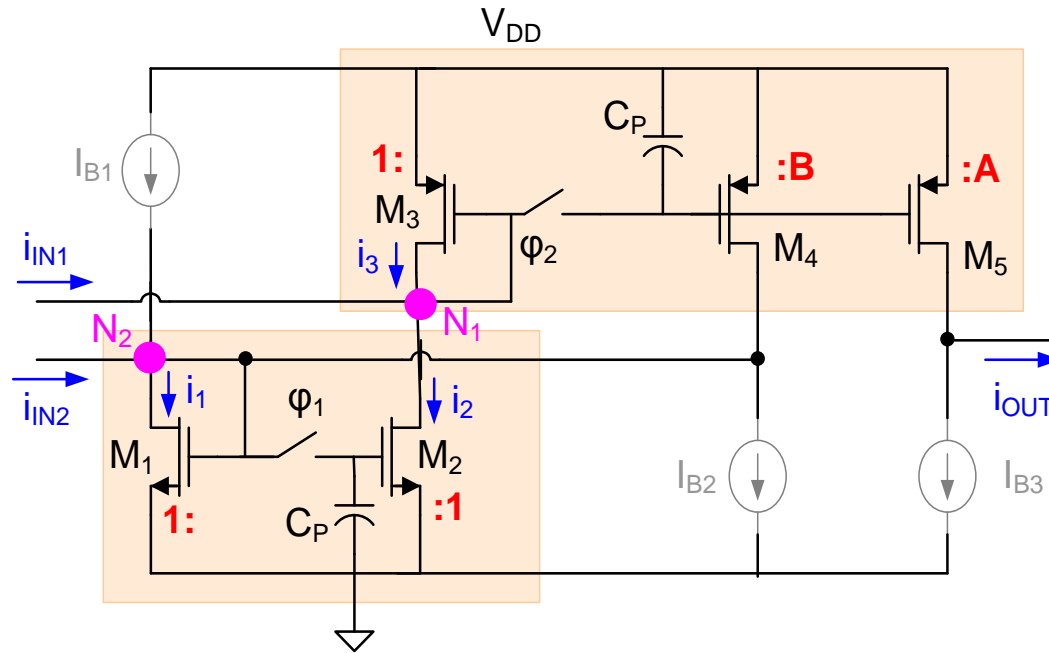


$$I_{OUT}(z) = \left(\frac{Az^{-1}}{1-Bz^{-1}} \right) I_{IN2}(z) - \left(\frac{A}{1-Bz^{-1}} \right) I_{IN1}(z)$$

- Summing inputs can be provided by summing currents on N_1 or N_2 or both
- Multiple outputs can be provided by adding outputs to upper mirror
- Amount of loss determined by mirror gain B

Switched-Current Integrator

Sensitivity Analysis

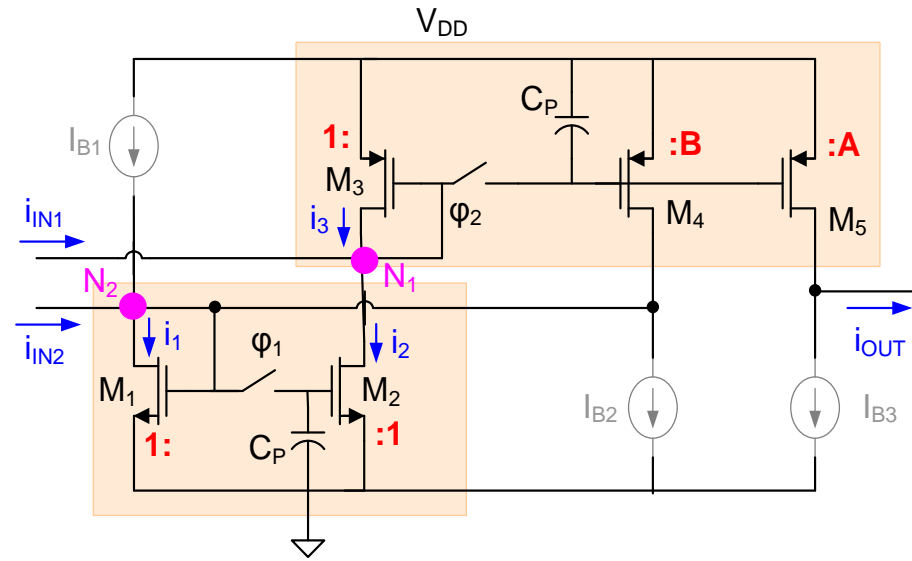

Consider Forward Euler

$$I_{\text{OUT}}(z) = \left(\frac{Az^{-1}}{1-Bz^{-1}} \right) I_{\text{IN2}}(z)$$

$$H(z) = \frac{TI_0}{z-1+\alpha T}$$

$$I_0 = \frac{A}{T} \quad \frac{1-B}{T} = \alpha$$


$$S_A^{I_0} = 1$$

$$S_B^\alpha = \frac{-B}{1-B}$$

For low loss integrator (e.g. ideal integrator), the sensitivity of α is very large!

Switched-Current Integrator

Sensitivity Analysis

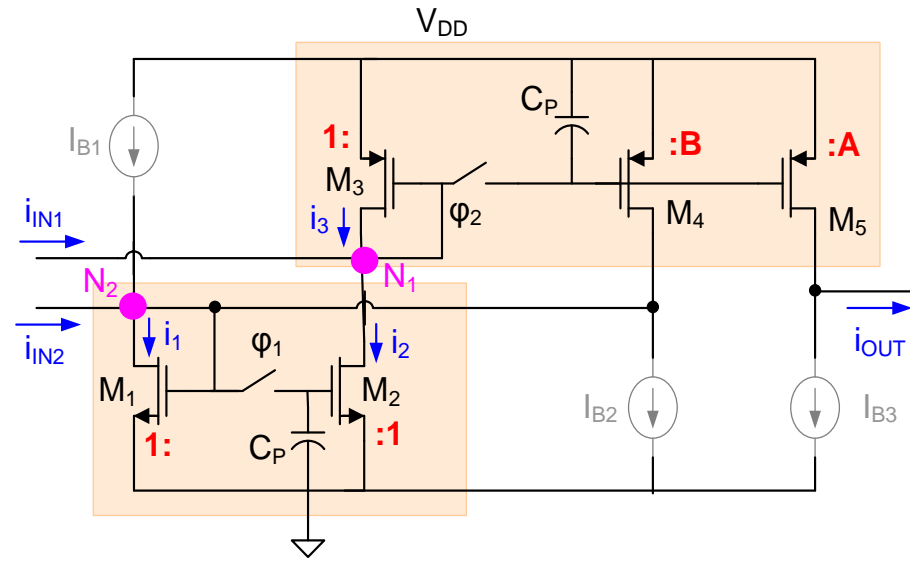

Consider Bilinear z

$$I_{OUT}(z) = A \left(\frac{z^{-1} + 1}{1 - Bz^{-1}} \right) I_{IN}(z)$$

$$H(z) = \frac{TI_0}{2} \left(\frac{z+1}{z \left(1 + \frac{\alpha T}{2} \right) + \left(\frac{\alpha T}{2} - 1 \right)} \right)$$

$$I_0 = A \frac{2}{T(1+B)} \quad \alpha = \frac{2}{T} \frac{1-B}{1+B}$$

$$S_A^{I_0} = 1$$

$$S_B^\alpha = \frac{-B}{(1-B)(1+B)}$$


For low loss integrator (e.g. ideal integrator), the sensitivity of α is very large!

What about the sensitivity to the gain of the lower current mirror?

Switched-Current Integrator

Define A_1 to be the gain of the lower mirror

Sensitivity to A_1 ?

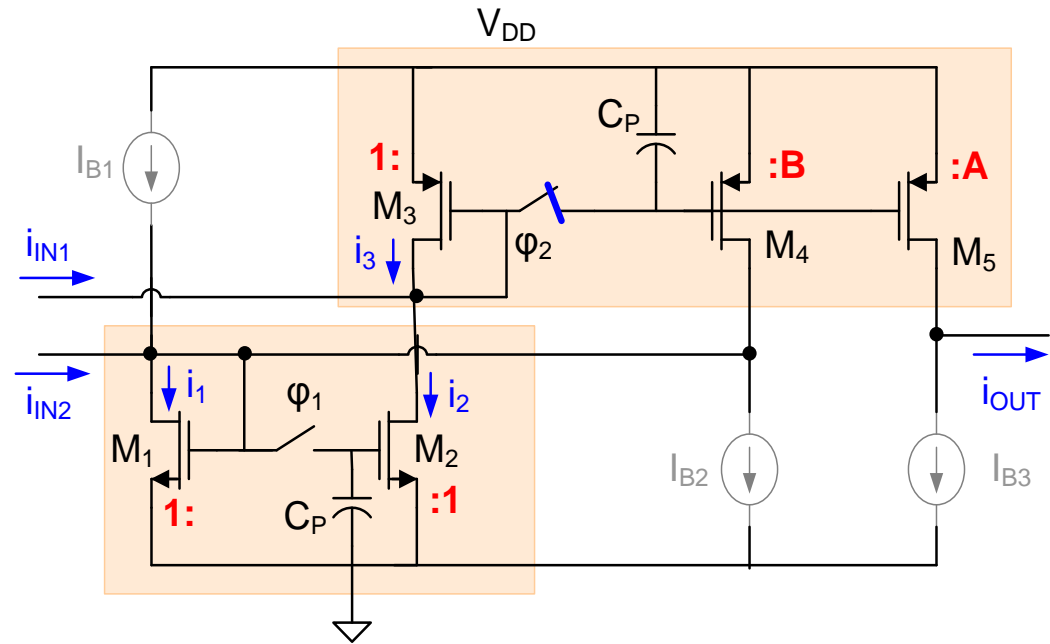

Consider Φ_2 closed, Φ_1 open ($nT - T/2 < t < nT$)

$$i_2(t) = A_1 i_1(nT - T)$$

$$i_2(t) = i_3(t) + i_{IN1}(t)$$

$$i_{OUT}(t) = A i_3(t)$$


$$i_1(nT - T) = B i_3(nT - T) + i_{IN2}(nT - T) \quad (\text{from first phase})$$

$$\left(\frac{1}{A}\right) i_{OUT}(t) + i_{IN1}(t) = \frac{A_1 B}{A} i_{OUT}(nT - T) + A_1 i_{IN2}(nT - T)$$

Switched-Current Integrator

Define A_1 to be the gain of the lower mirror

Sensitivity to A_1 ?

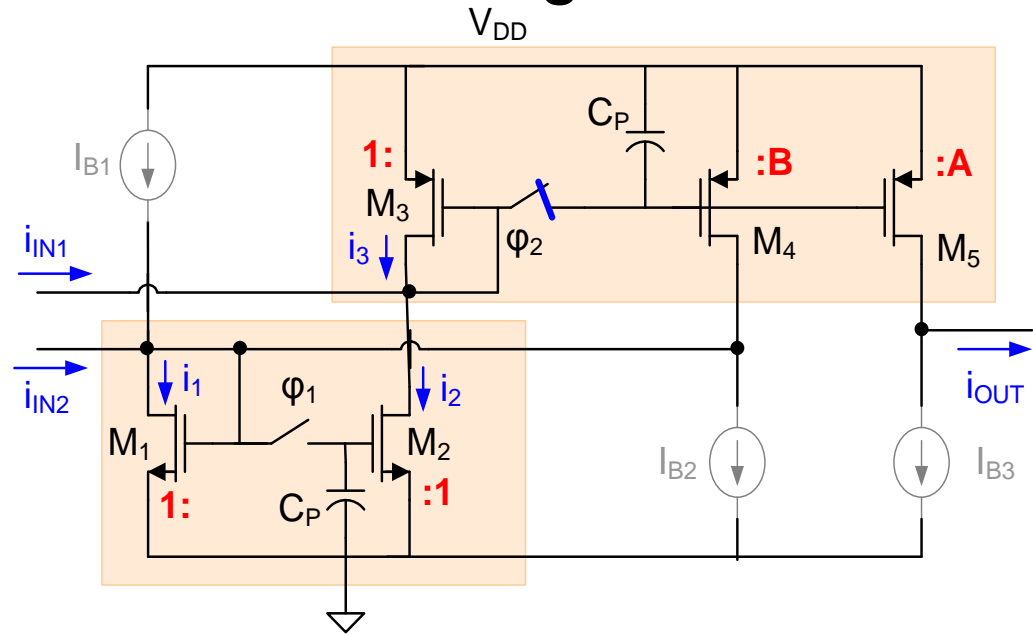

$$\left(\frac{1}{A}\right) i_{\text{OUT}}(nT) + i_{\text{IN1}}(nT) = \frac{A_1 B}{A} i_{\text{OUT}}(nT-T) + A_1 i_{\text{IN2}}(nT-T)$$

Taking z-transform, obtain

$$I_{\text{OUT}}(z) = \left(\frac{A_1 A z^{-1}}{1 - B A_1 z^{-1}}\right) I_{\text{IN2}}(z) - \left(\frac{A}{1 - B A_1 z^{-1}}\right) I_{\text{IN1}}(z)$$

Consider Forward Euler

$$\frac{1 - B A_1}{T} = \alpha \quad S_B^\alpha = \frac{-B A_1}{1 - B A_1} \quad S_{A_1}^\alpha = \frac{-B A_1}{1 - B A_1}$$

Sensitivity to A_1 is also large for low-loss or lossless integrator

