




# EE 508

## Lecture 36


### Oscillators, VCOs, and Oscillator/VCO-Derived Filters
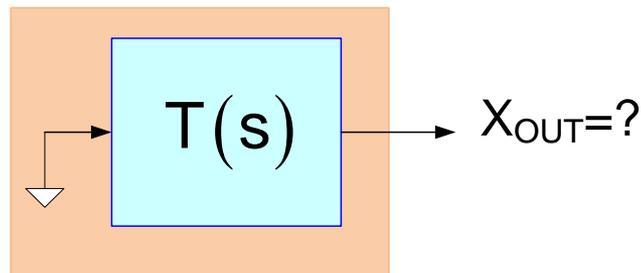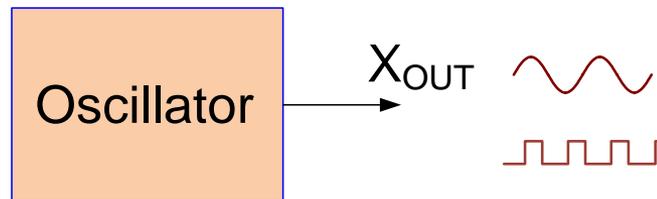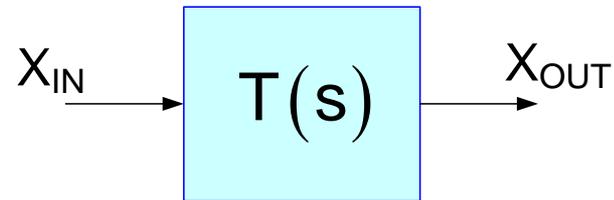
# Question:

What is the relationship, if any, between a filter and an oscillator or VCO?



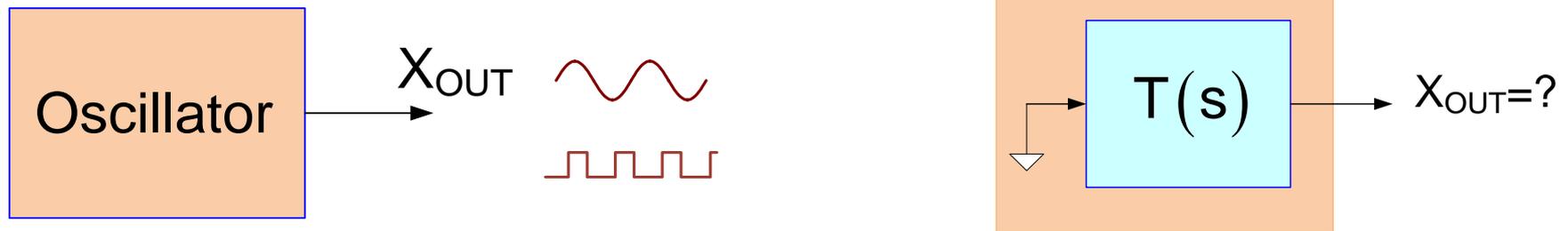
# What is the relationship, if any, between a filter and an oscillator or VCO?





- When power is applied to an oscillator, it initially behaves as a small-signal linear network
- When operating linearly, the oscillator has poles (but no zeros)
- Poles are ideally on the imaginary axis or appear as cc pairs in the RHP
- There is a wealth of literature on the design of oscillators
- Oscillators often are designed to operate at very high frequencies
- If cc poles of a filter are moved to RHP it will become an oscillator
- **Can oscillators be modified to become filters?**

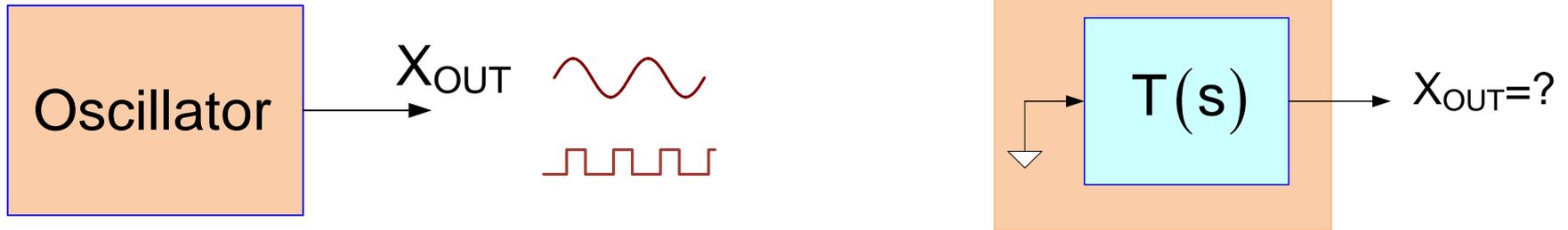What is the relationship, if any, between a filter and an oscillator or VCO?



Will focus on modifying oscillator structures to form high frequency narrow-band filters

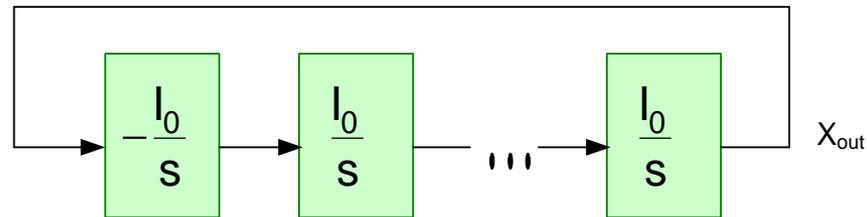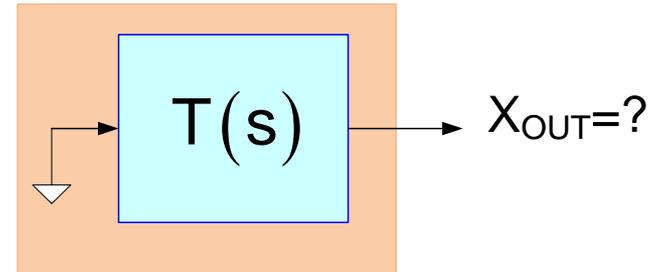Consider a cascaded integrator loop comprised of  $n$  integrators



$$X_{OUT} = -\left(\frac{I_0}{s}\right)^n X_{OUT}$$

$$X_{OUT} (s^n + I_0^n) = 0$$

$$D(s) = s^n + I_0^n$$

Consider the poles of  $D(s) = s^n + I_0^n$

$$s^n + I_0^n = 0$$

$$s^n = -I_0^n$$



$$s = \left[ -I_0^n \right]^{\frac{1}{n}}$$

$$s = \left[ -1 \right]^{\frac{1}{n}} \left[ I_0^n \right]^{\frac{1}{n}}$$

$$s = I_0 \left[ -1 \right]^{\frac{1}{n}}$$





Poles are the n roots of -1 scaled by  $I_0$

Roots of -1:

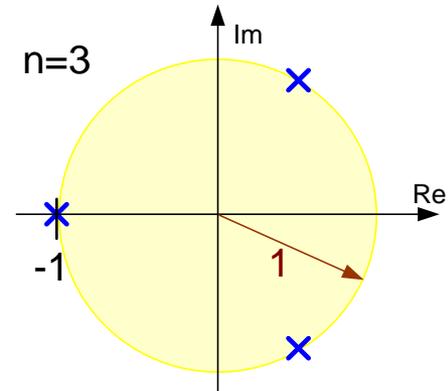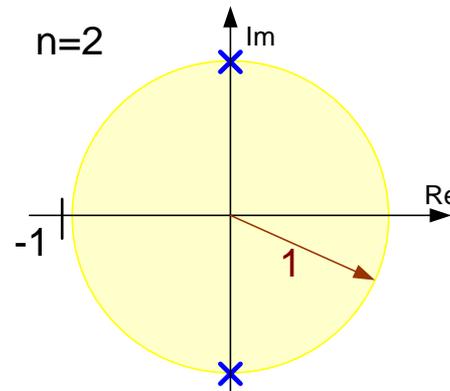


Roots are uniformly spaced on a unit circle

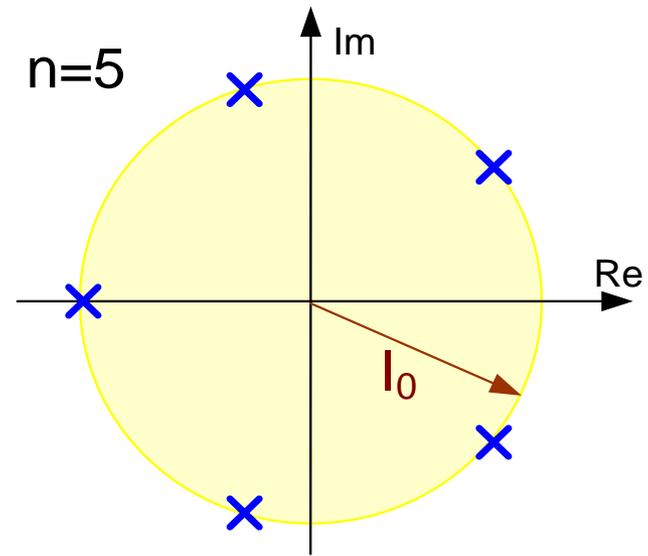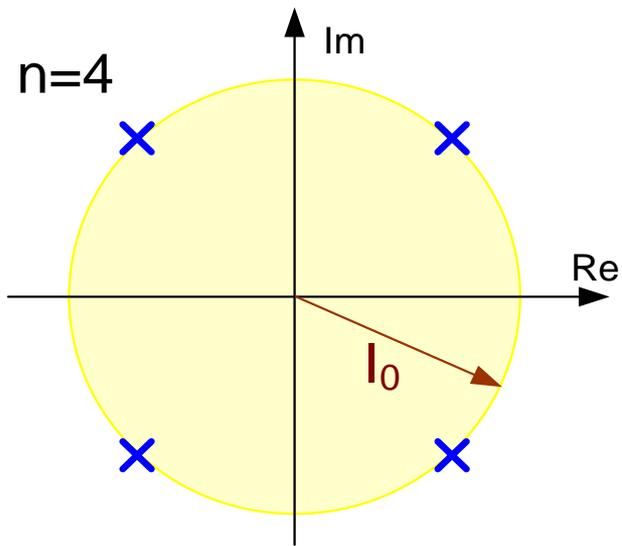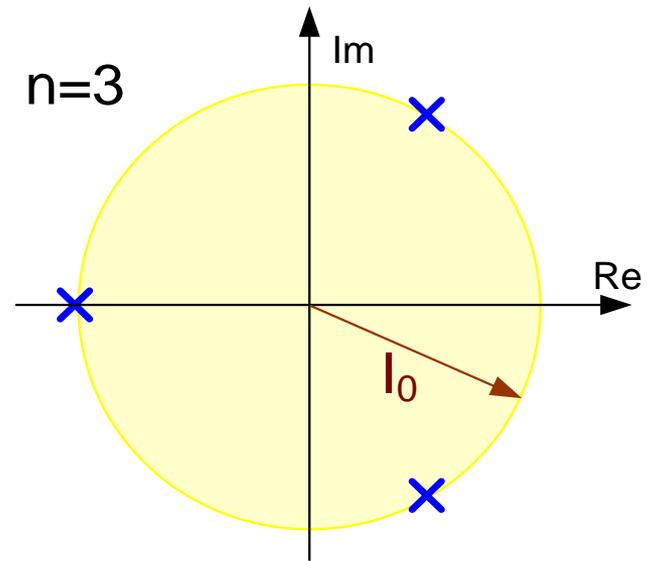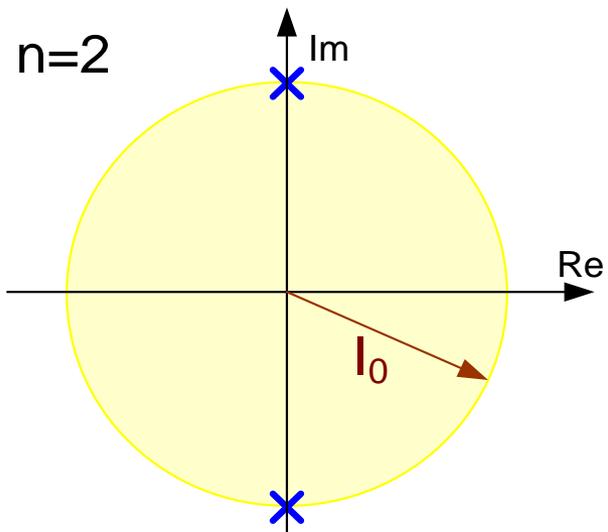
Consider the poles of  $D(s) = s^n + I_0^n$




$n=6$

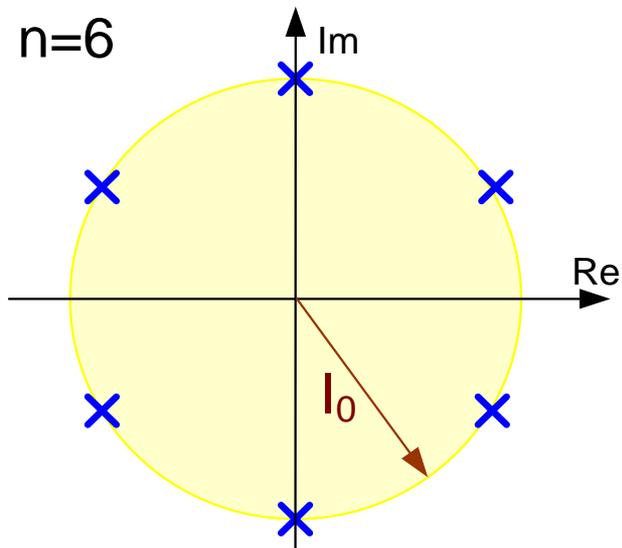

$n=7$

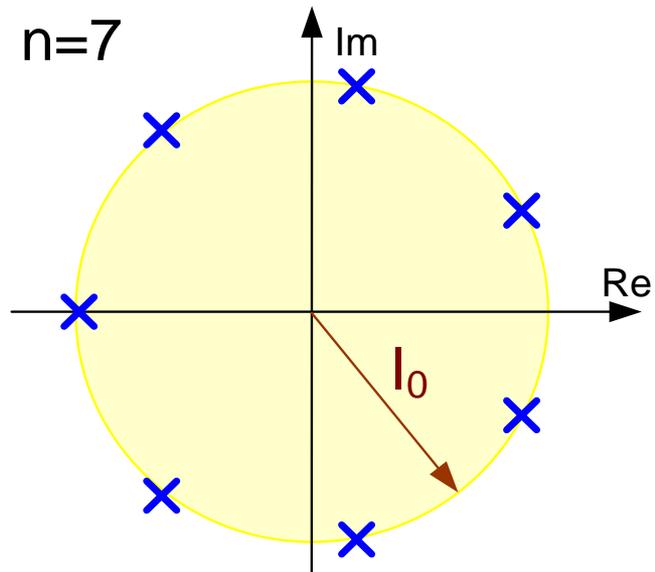

$n=8$

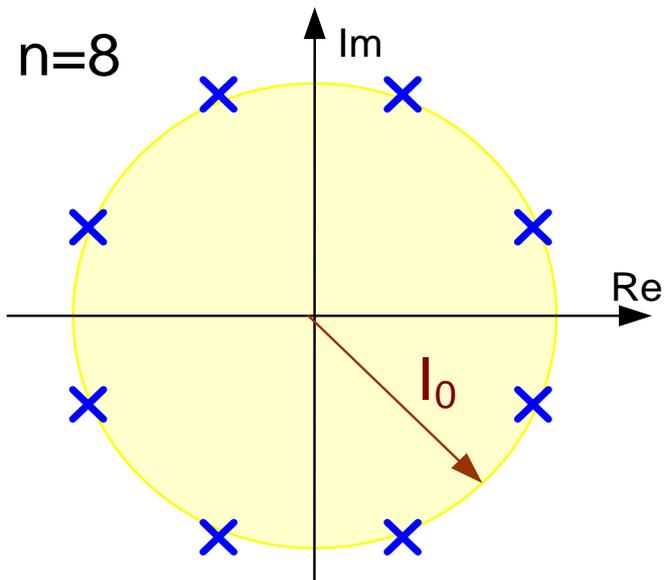

# Some useful theorems

Theorem: A rational fraction  $T(s) = \frac{N(s)}{\prod_{i=1}^n (s-p_i)}$  with simple poles can be expressed

in partial fraction form as  $T(s) = \sum_{i=1}^n \frac{A_i}{s-p_i}$

where  $A_i = (s-p_i)T(s)|_{s=p_i}$  for  $1 \leq j \leq n$

Theorem: The impulse response of a rational fraction  $T(s)$  with simple poles can be expressed as  $T(s) = \sum_{i=1}^n A_i e^{p_i t}$  where the numbers  $A_i$  are the coefficients

in the partial fraction expansion of  $T(s)$

Theorem: If  $p_i$  is a simple complex pole of the rational fraction  $T(s)$ , then the partial fraction expansion terms in the impulse response corresponding to  $p_i$  and  $p_i^*$  can be expressed as

$$\frac{A_i}{s-p_i} + \frac{A_i^*}{s-p_i^*}$$

Theorem: If  $p_i = \alpha_i + j\beta_i$  is a simple pole with non-zero imaginary part of the rational fraction  $T(s)$ , then the impulse response terms corresponding to the poles  $p_i$  and  $p_i^*$  in the partial fraction expansion can be expressed as

$$|A_i| e^{\alpha_i t} \cos(\beta_i t + \theta_i)$$

where  $\theta_i$  is the angle of the complex quantity  $A_i$

Theorem: If all poles of an n-th order rational fraction T(s) are simple and have a non-zero Imaginary part, then the impulse response can be expressed as

$$\sum_{i=1}^{n/2} |A_i| e^{\alpha_i t} \cos(\beta_i t + \theta_i)$$

where  $\theta_i$ ,  $A_i$ ,  $\alpha_i$ , and  $\beta_i$  are as defined before

Theorem: If an odd-order rational fraction has one pole on the negative real axis at  $\alpha_0$  and n simple poles that have a non-zero Imaginary part, then the impulse response can be expressed as


$$A_0 e^{\alpha_0 t} + \sum_{i=1}^{n/2} |A_i| e^{\alpha_i t} \cos(\beta_i t + \theta_i)$$

where  $\theta_i$ ,  $A_i$ ,  $\alpha_i$ , and  $\beta_i$  are as defined before

Poles of  $D(s) = s^n + I_0^n$

Consider the following

0.5	-0.866025404
0.5	0.866025404
-1	3.67545E-16

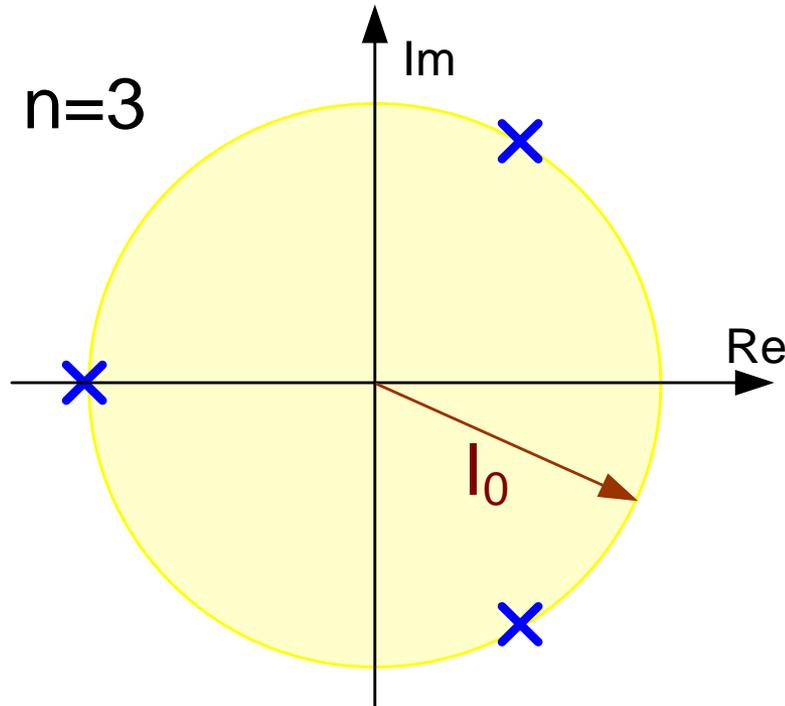

$$\alpha = 0.5 I_0$$

$$\beta = 0.866 I_0$$

frequency of oscillation:  $|A_i| e^{\alpha t} \cos(\beta_i t + \theta_i)$

Starts at  $\omega = 0.866 I_0$  and will slow down as nonlinearities limit amplitude

Poles of  $D(s) = s^n + I_0^n$


$n=3$

Consider the following

$$\beta = 0.866 I_0$$

$$\alpha = 0.5 I_0 - \Delta\alpha$$
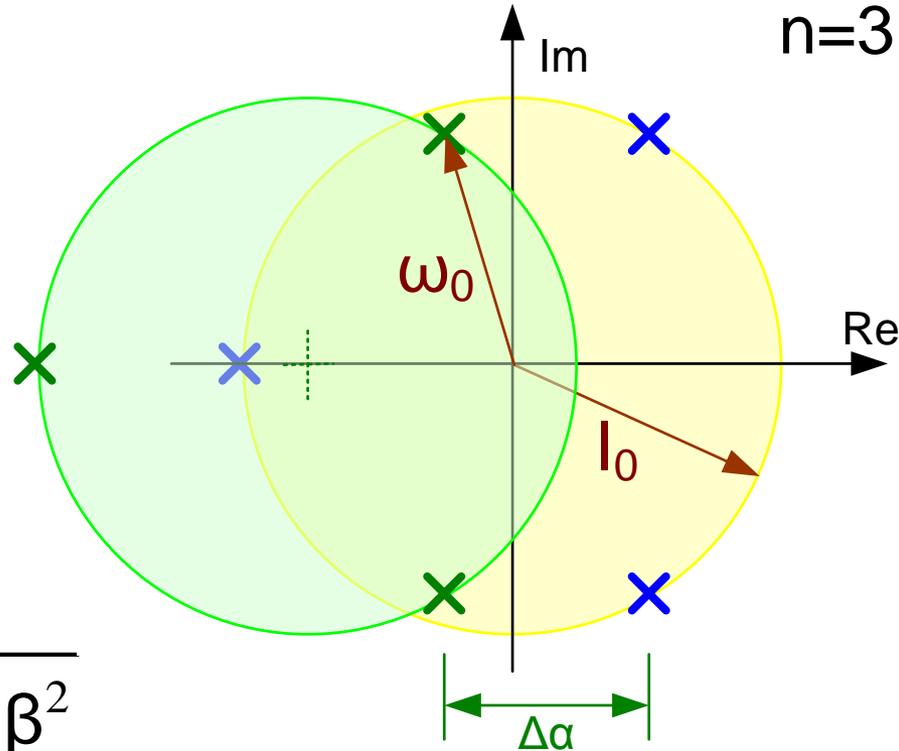
$$\omega_0 = \sqrt{(\alpha - \Delta\alpha)^2 + \beta^2}$$



So, to get a high  $\omega_0$ , want  $\beta$  as large as possible

## Consider now the filter by adding a loss of $\alpha_L$ to the integrator

Will now determine  $\alpha_L$  and  $I_0$  needed to get a desired pole  $Q$  and  $\omega_0$

The values of  $\alpha$  and  $\beta$  are dependent upon  $I_0$  but the angle  $\theta$  is only dependent upon the number of integrators in the VCO


$$\alpha + j\beta = I_0 (\cos\theta + j\sin\theta)$$

Define the location of the filter pole to be

$$\alpha_F + j\beta_F$$

It follows that
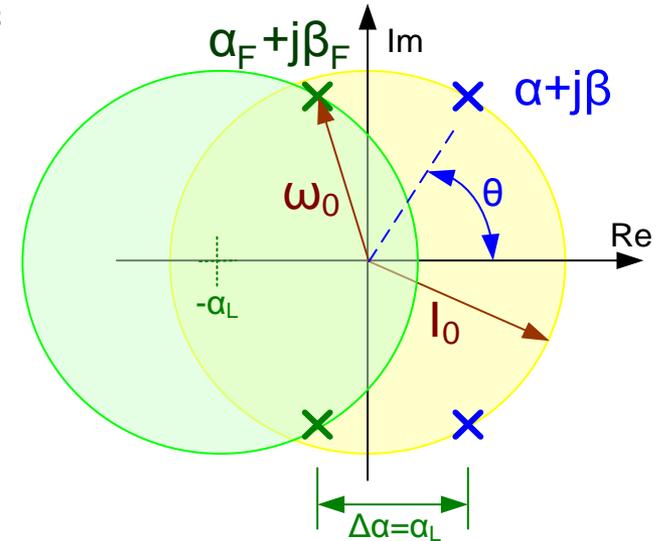
$$\beta_F = \beta \quad \alpha_F = \alpha - \alpha_L$$



The relationship between the filter parameters is well known

$$\beta_F = \frac{\omega_0}{2Q} \sqrt{4Q^2 - 1}$$


$$\alpha_F = -\frac{\omega_0}{2Q}$$

Thus

$$I_0 = \frac{\omega_0}{(\sin\theta)2Q} \sqrt{4Q^2 - 1}$$

$$\alpha_L = \frac{\omega_0}{2Q} + I_0 \cos\theta = \frac{\omega_0}{2Q} + \frac{\omega_0}{2Q(\tan\theta)} \sqrt{4Q^2 - 1}$$

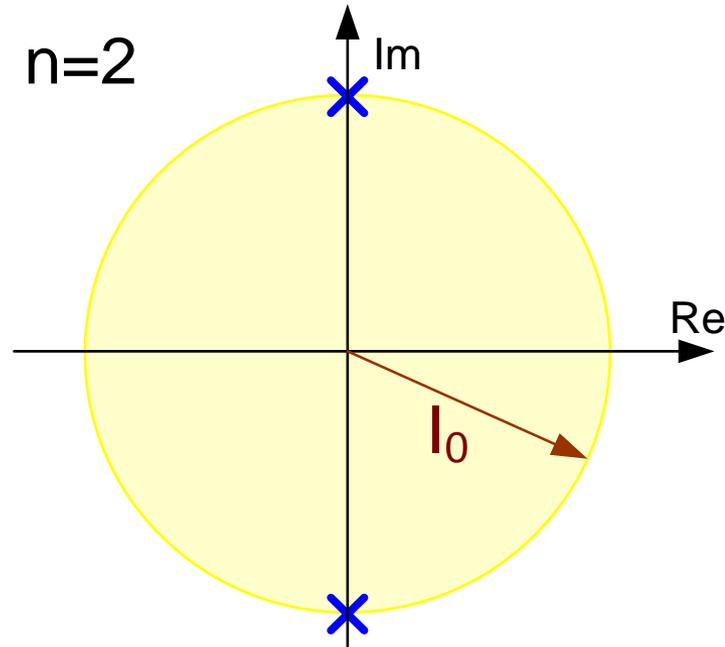
**Will a two-stage structure give the highest frequency of operation?**



$$\omega_0 = \sqrt{(\alpha - \Delta\alpha)^2 + \beta^2} \quad \longrightarrow \quad \omega_0 = \sqrt{(-\Delta\alpha)^2 + \beta^2}$$

- Even though the two-stage structure may not oscillate, can work as a filter!
- Can add phase lead if necessary

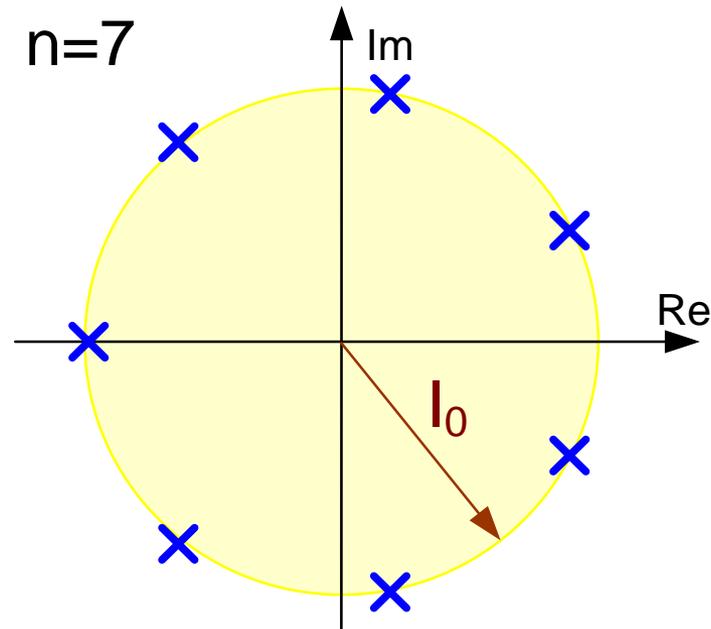
What will happen with a circuit that has two pole-pairs in the RHP?



The impulse response will have three decaying exponential terms and two growing exponential terms

$$A_0 e^{\alpha_0 t} + \sum_{i=1}^{n/2} |A_i| e^{\alpha_i t} \cos(\beta_i t + \theta_i)$$
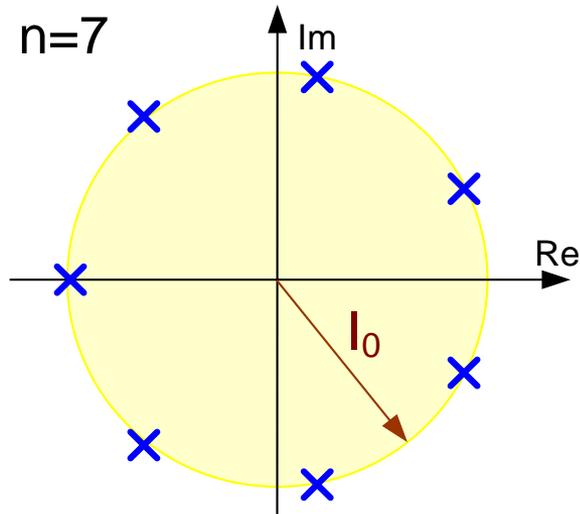
## What will happen with a circuit that has two pole-pairs in the RHP?



-0.62349	-0.781831482
0.222521	-0.974927912
0.900969	-0.433883739
0.900969	0.433883739
0.222521	0.974927912
-0.62349	0.781831482
-1	3.67545E-16

$$\alpha_1=0.2225 \quad \beta_1=0.974$$

$$\alpha_2=0.9009 \quad \beta_2=0.4338$$

Consider the growing exponential terms and normalize to  $I_0=1$



$$|A_1| e^{\alpha_1 t} \cos(\beta_1 t + \theta_1) + |A_2| e^{\alpha_2 t} \cos(\beta_2 t + \theta_2)$$

At  $t=145$  (after only 10 periods of the lower frequency signal)

$$r = \frac{e^{\alpha_2 t}}{e^{\alpha_1 t}} \Big|_{t=145} = \frac{e^{0.9009 \cdot 145}}{e^{0.2225 \cdot 145}} = 5.2 \times 10^{42}$$

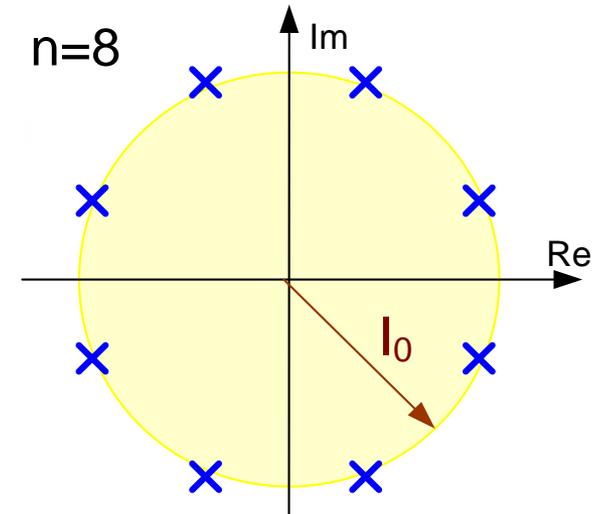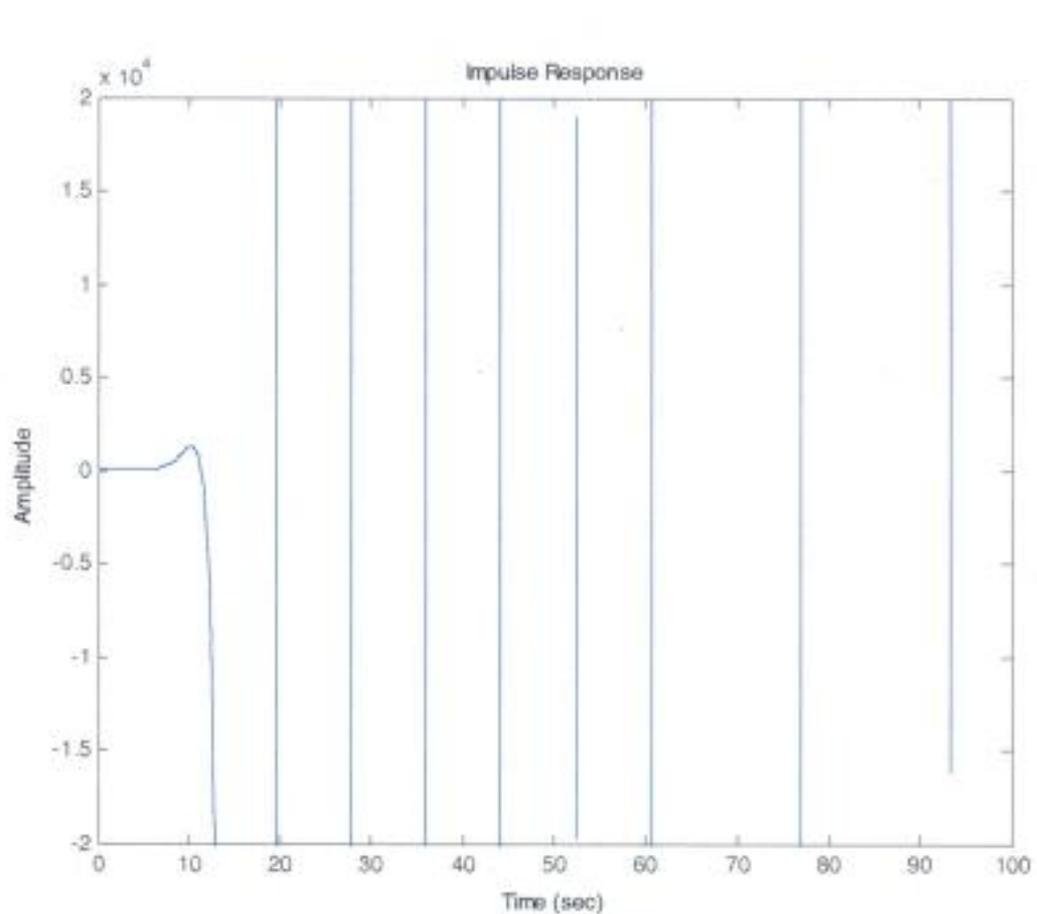**The lower frequency oscillation will completely dominate !**

What will happen with a circuit that has two pole-pairs in the RHP?



Thanks to Chen for these plots

Figure 14 N=8 impulse response

Can only see the lower frequency component !

# What will happen with a circuit that has two pole-pairs in the RHP?

Thanks to Chen for these plots

image1.jpg  
Type: JPEG Image  
Size: 2.71 MB  
Dimension: 5008 x 6608 pixels

$-0.9239i$

$0.9239 + 0.3827i$


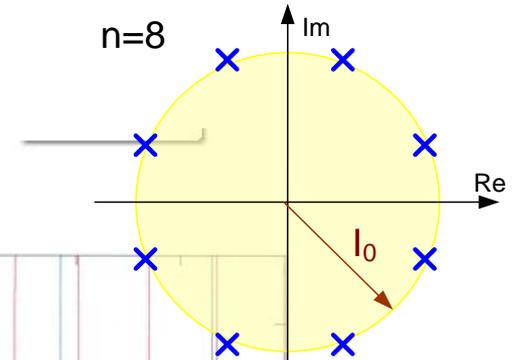
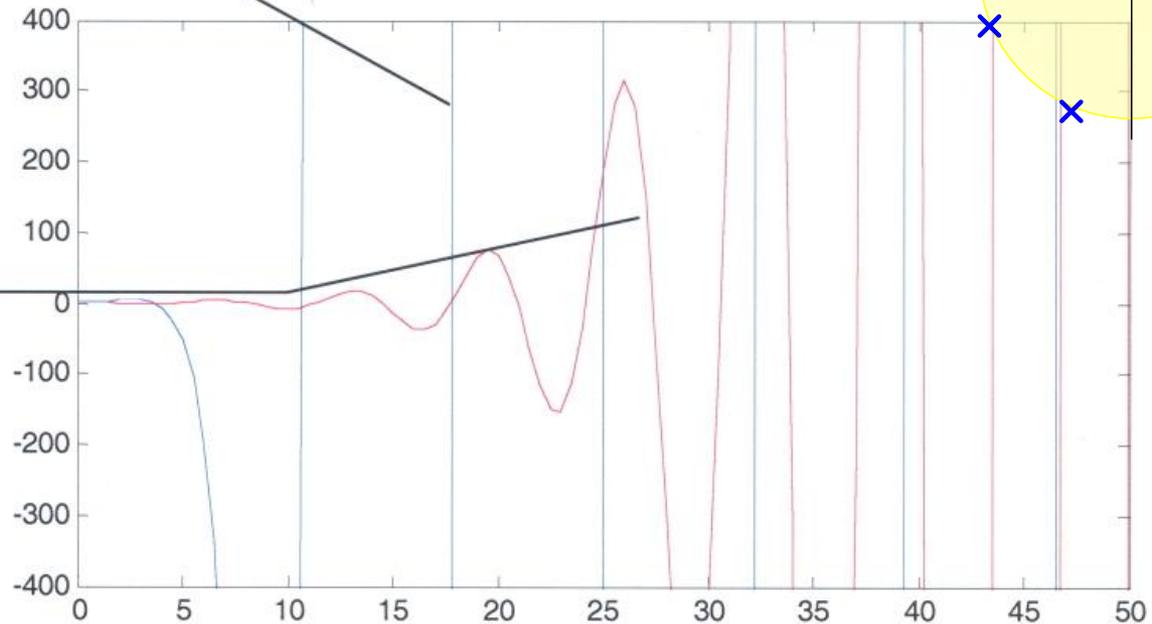


Figure 7 N=8 the impulse response of two poles

**After even only two periods of the lower frequency waveform, it completely dominates !**

How do we guarantee that we have a net coefficient of +1 in  $D(s)$ ?

$$D(s) = s^n + I_0^n$$

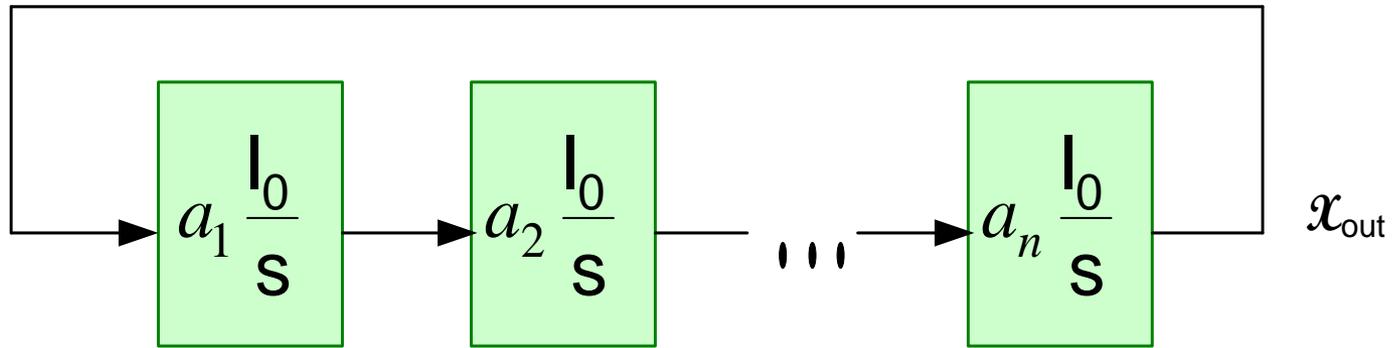

$$x_{out} = \left( \prod_{i=1}^n a_i \left( \frac{I_0}{s} \right) \right) x_{out} \quad a_i \in \{-1, 1\}$$


$$D(s) = s^n - \left( \prod_{i=1}^n a_i \right) I_0^n \quad \longrightarrow \quad \prod_{i=1}^n a_i = -1$$

Must have an odd number of inversions in the loop !

If  $n$  is odd, all stages can be inverting and identical !

How do we guarantee that we have a net coefficient of +1 in  $D(s)$ ?


$$D(s) = s^n + I_0^n$$

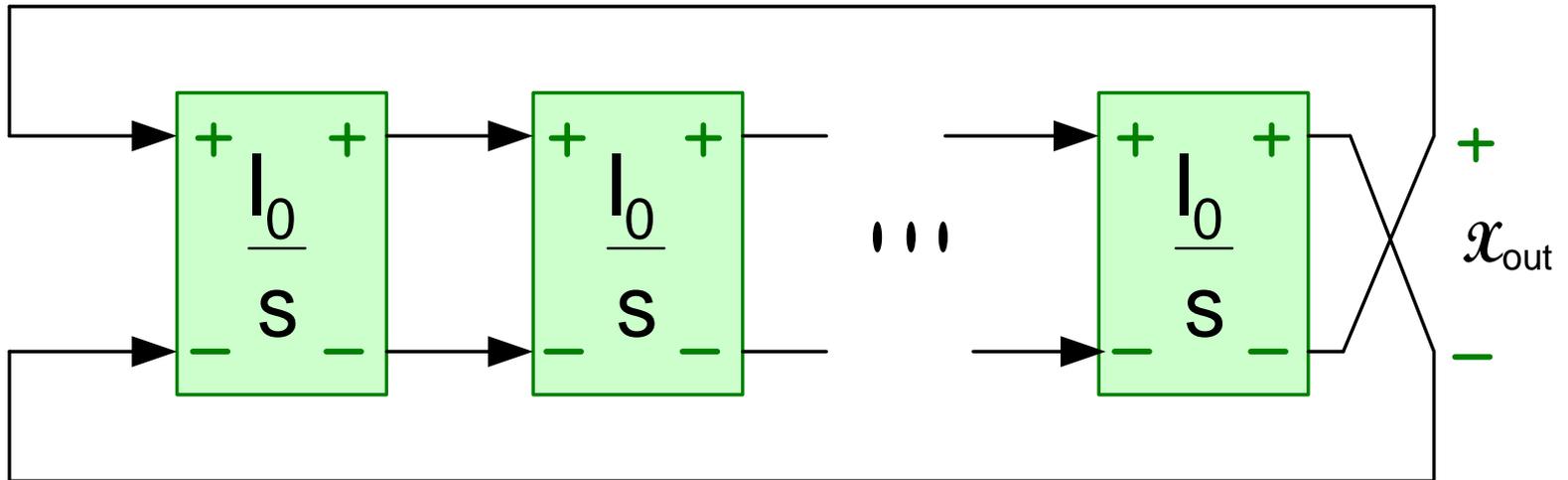

If fully differential or fully balanced, must have an odd number of crossings of outputs

Applicable for both even and odd order loops

## A lossy integrator stage

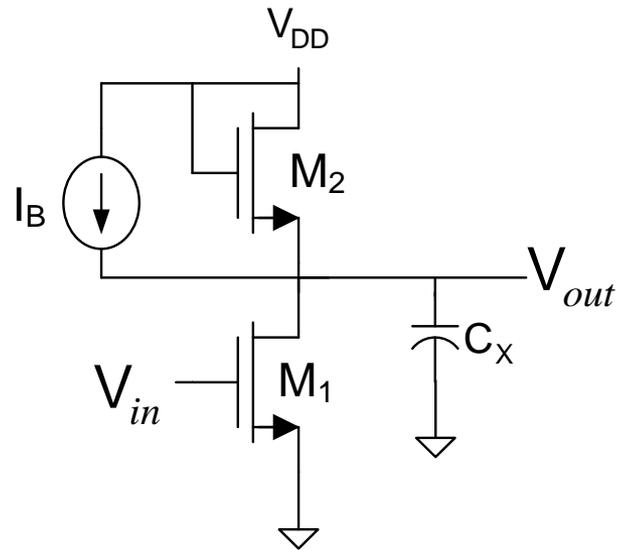


$$I(s) = \frac{-g_{m1}/C_X}{s + g_{m2}/C_X}$$

$$I_0 = g_{m1}/C_X$$


$$\alpha_L = g_{m2}/C_X$$
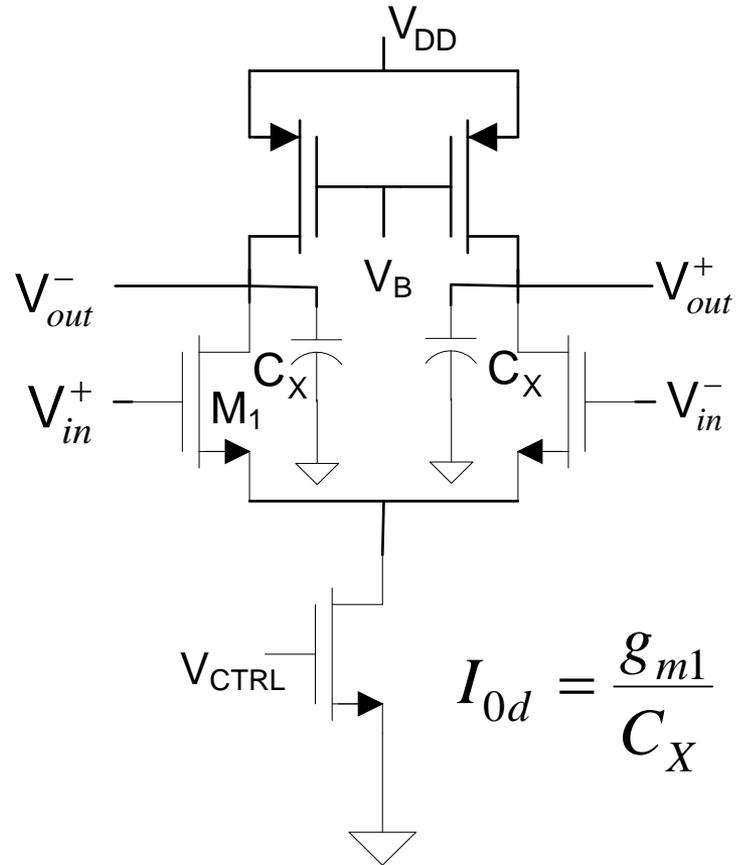
## A fully-differential voltage-controlled integrator stage



Will need CMFB circuit
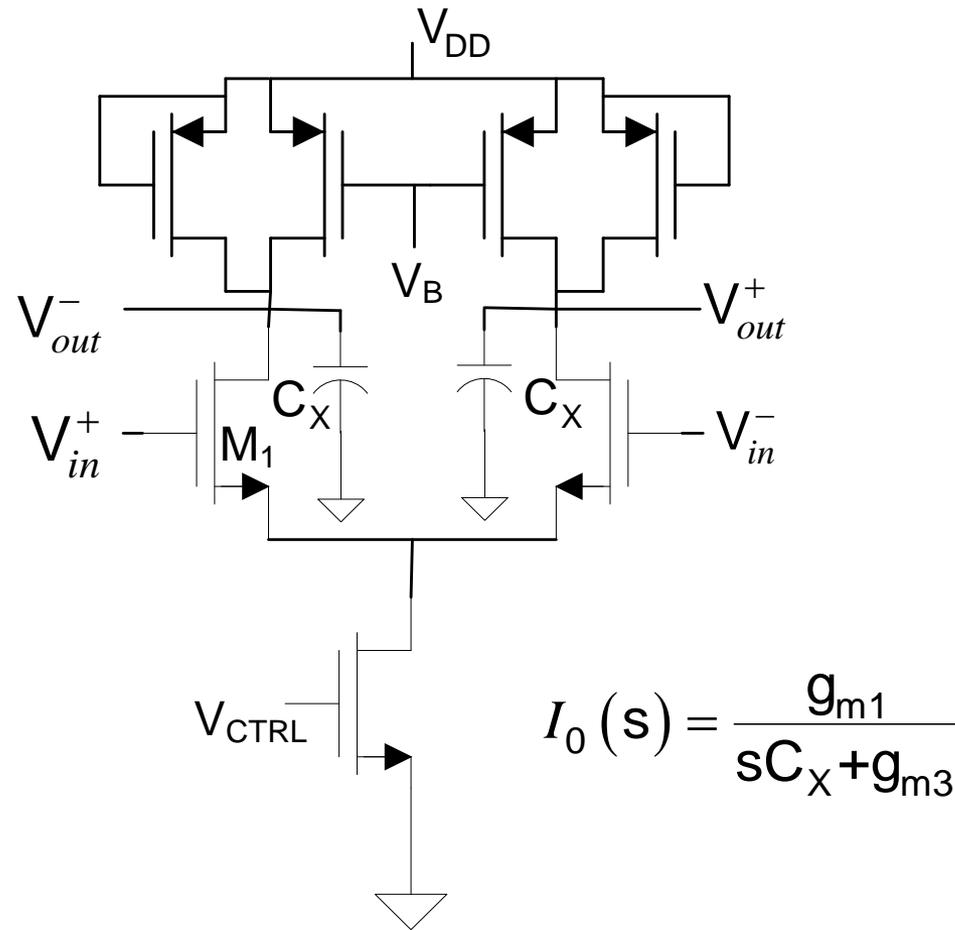
## A fully-differential voltage-controlled integrator stage with loss



Will need CMFB circuit

# Example:

Using the single-stage lossy integrator, design the integrator to meet a given  $\omega_0$  and  $Q$  requirement

Recall:


$$I_0 = \frac{\omega_0}{(\sin\theta)2Q} \sqrt{4Q^2 - 1} \quad (1)$$

$$\alpha_L = \frac{\omega_0}{2Q} + \frac{\omega_0}{2Q(\tan\theta)} \sqrt{4Q^2 - 1} \quad (2)$$

Substituting for  $I_0$  and  $\alpha_L$  we obtain:

$$\frac{g_{m1}}{C_X} = \frac{\omega_0}{(\sin\theta)2Q} \sqrt{4Q^2 - 1} \quad (3)$$
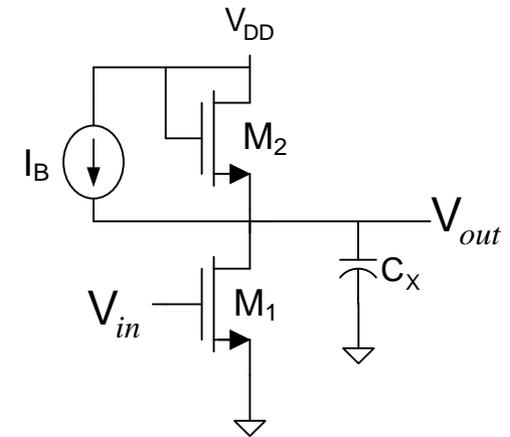
$$\frac{g_{m2}}{C_X} = \frac{\omega_0}{2Q} + \frac{\omega_0}{2Q(\tan\theta)} \sqrt{4Q^2 - 1} \quad (4)$$



$$I_0 = g_{m1}/C_X$$

$$\alpha_L = g_{m2}/C_X$$

# Example:

Using the single-stage lossy integrator, design the integrator to meet a given  $\omega_0$  and  $Q$  requirement

Expressing  $g_{m1}$  and  $g_{m2}$  in terms of design parameters:

$$\frac{\mu C_{OX} W_1 V_{EB1}}{L_1 C_X} = \frac{\omega_0}{(\sin\theta) 2Q} \sqrt{4Q^2 - 1} \quad (5)$$

$$\frac{\mu C_{OX} W_2 V_{EB2}}{L_2 C_X} = \frac{\omega_0}{2Q} + \frac{\omega_0}{2Q(\tan\theta)} \sqrt{4Q^2 - 1} \quad (6)$$


If we assume  $I_B=0$ , equating drain currents obtain:

$$V_{EB2} = V_{EB1} \sqrt{\frac{W_1 L_2}{W_2 L_1}} \quad (7)$$

Thus the previous two expressions can be rewritten as :

$$\frac{\mu C_{OX} V_{EB1}}{C_X} \left[ \frac{W_1}{L_1} \right] = \frac{\omega_0}{(\sin\theta) 2Q} \sqrt{4Q^2 - 1} \quad (8)$$
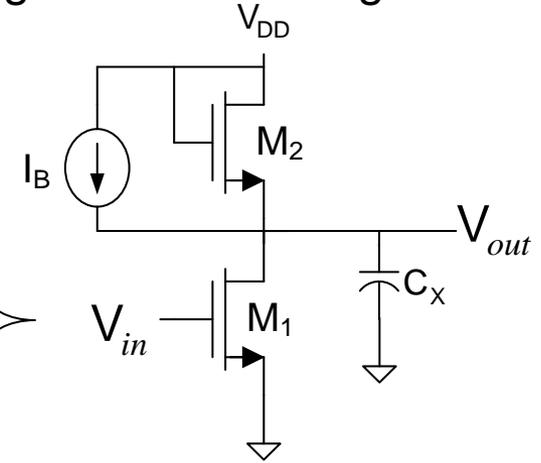
$$\frac{\mu C_{OX} V_{EB1}}{C_X} \left[ \frac{W_1 W_2}{L_1 L_2} \right] = \frac{\omega_0}{2Q} + \frac{\omega_0}{2Q(\tan\theta)} \sqrt{4Q^2 - 1} \quad (9)$$



$$I_0 = g_{m1}/C_X$$

$$\alpha_L = g_{m2}/C_X$$

# Example:


Using the single-stage lossy integrator, design the integrator to meet a given  $\omega_0$  and  $Q$  requirement

$$\frac{\mu C_{OX} V_{EB1}}{C_X} \left[ \frac{W_1}{L_1} \right] = \frac{\omega_0}{(\sin\theta) 2Q} \sqrt{4Q^2 - 1}$$

$$\frac{\mu C_{OX} V_{EB1}}{C_X} \left[ \frac{W_1 W_2}{L_1 L_2} \right] = \frac{\omega_0}{2Q} + \frac{\omega_0}{2Q(\tan\theta)} \sqrt{4Q^2 - 1}$$

Taking the ratio of these two equations we obtain:
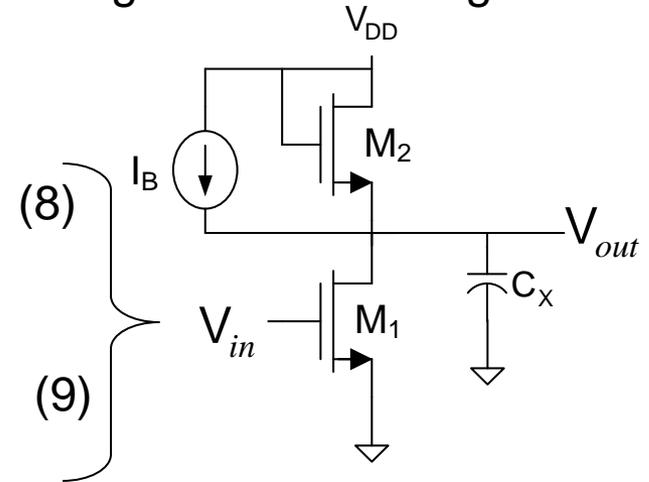
$$\frac{W_2}{L_2} = \frac{\sin\theta + \cos\theta \sqrt{4Q^2 - 1}}{\sqrt{4Q^2 - 1}} \quad (10)$$



$$I_0 = g_{m1}/C_X$$

$$\alpha_L = g_{m2}/C_X$$


Observe that the pole  $Q$  is determined by the dimensions of the lossy device !

# Example:

Using the single-stage lossy integrator, design the integrator to meet a given  $\omega_0$  and  $Q$  requirement

$$\frac{\mu C_{OX} V_{EB1}}{C_X} \left[ \frac{W_1}{L_1} \right] = \frac{\omega_0}{(\sin\theta) 2Q} \sqrt{4Q^2 - 1} \quad (8)$$
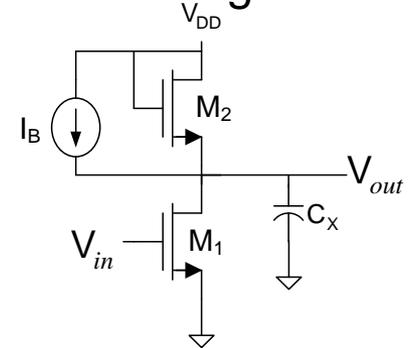
$$\frac{W_2}{L_2} = \frac{\sin\theta + \cos\theta \sqrt{4Q^2 - 1}}{\sqrt{4Q^2 - 1}} \quad (10)$$



Still must obtain  $W_1/L_1$ ,  $V_{EB1}$ , and  $C_X$  from either of these equations

Although it appears that there might be 3 degrees of freedom left and only one constraint (one of these equations), if these integrators are connected in a loop, the operating point (Q-point) will be the same for all stages and will be that value where  $V_{out} = V_{in}$ . So, this adds a second constraint.

Setting  $V_{out} = V_{in}$ , and assuming  $V_{T1} = V_{T2}$ , we obtain from KVL

$$V_{DD} = V_{EB1} + V_{EB2} + 2V_T \quad (11)$$


But  $V_{EB1}$  and  $V_{EB2}$  are also related in (7)

# Example:

Using the single-stage lossy integrator, design the integrator to meet a given  $\omega_0$  and  $Q$  requirement

$$\frac{\mu C_{OX} V_{EB1}}{C_X} \left[ \frac{W_1}{L_1} \right] = \frac{\omega_0}{(\sin\theta) 2Q} \sqrt{4Q^2 - 1} \quad (8)$$
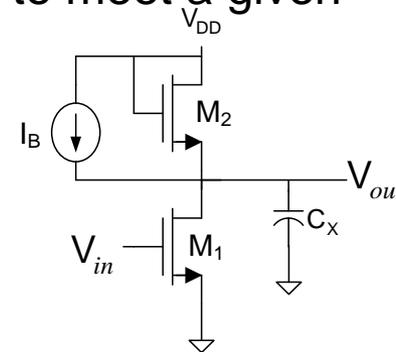
$$\frac{W_2}{L_2} = \frac{\sin\theta + \cos\theta \sqrt{4Q^2 - 1}}{\sqrt{4Q^2 - 1}} \quad (10)$$



Still must obtain  $W_1/L_1$ ,  $V_{EB1}$ , and  $C_X$  from either of these equations

$$V_{DD} = V_{EB1} + V_{EB2} + 2V_T \quad (11)$$

$$V_{EB2} = V_{EB1} \sqrt{\frac{W_1 L_2}{W_2 L_1}} \quad (7)$$

$$V_{EB1} = \frac{V_{DD} - 2V_T}{1 + \sqrt{\frac{W_2 L_1}{W_1 L_2}}} \quad (12)$$

Substituting (10) into (12) and then into (8) we obtain


$$\frac{\mu C_{OX}}{C_X} \left[ \frac{W_1}{L_1} \right] \left( \frac{V_{DD} - 2V_T}{1 + \sqrt{\left(\frac{W_1}{L_1}\right)^{-1} \left( \frac{\sin\theta + \cos\theta \sqrt{4Q^2 - 1}}{\sqrt{4Q^2 - 1}} \right)}} \right) = \frac{\omega_0}{(\sin\theta) 2Q} \sqrt{4Q^2 - 1} \quad (13)$$

# Example:

Using the single-stage lossy integrator, design the integrator to meet a given  $\omega_0$  and  $Q$  requirement

$$\frac{W_2}{L_2} = \frac{\sin\theta + \cos\theta\sqrt{4Q^2-1}}{\sqrt{4Q^2-1}}$$
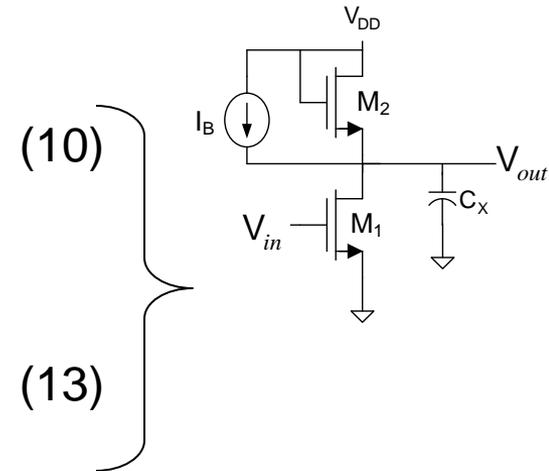
$$\frac{\mu C_{OX}}{C_X} \left[ \frac{W_1}{L_1} \right] \left( \frac{V_{DD} - 2V_T}{1 + \sqrt{\left(\frac{W_1}{L_1}\right)^{-1} \left( \frac{\sin\theta + \cos\theta\sqrt{4Q^2-1}}{\sqrt{4Q^2-1}} \right)}} \right) = \frac{\omega_0}{(\sin\theta)2Q} \sqrt{4Q^2-1}$$



There is still one degree of freedom remaining. Can either pick  $W_1/L_1$  and solve for  $C_X$  or pick  $C_X$  and solve for  $W_1/L_1$ .

Explicit expression for  $W_1/L_1$  not available

Tradeoffs between  $C_X$  and  $W_1/L_1$  will often be made

Since  $V_{OUTQ} = V_T + V_{EB1}$ , it may be preferred to pick  $V_{EB1}$ , then solve (12) for  $W_1/L_1$  and then solve (13) for  $C_X$

Adding  $I_B$  will provide one additional degree of freedom and will relax the relationship between  $V_{OUTQ}$  and  $W_1/L_1$  since (7) will be modified

