EE 508

Lecture 39

Current Mode Filters

Current-Mode Filters have become a topic of considerable interest in recent years

Consider first a brief background about filters

Recall:

John Hughes introduced the concept of the switched-current filter in 1989

This was considered a revolutionary concept since it offered potential for operating at very high frequencies with simple amplifiers (current mirrors) but no operational amplifiers. Some properties of Hughes's current-mode filters

- 1. Filter parameters dependend only on geometric ratios and clock frequency
- 2. Insensitive to value of parasitic capacitors
- 3. Operates at both low and high frequencies
- 4. Very small
- 5. Can operate at very low voltages (one $V_{\rm T}$ and one $V_{\rm EB}$ between rails if switches are neglected)

Others argued that these properties were inherent in the current-mode of operation and that continuous-time structures may perform even better !

A current-conveyor community had been struggling for years to get any adoption and this seemed to propel them to the forefront of the technology field

Literally hundreds of researchers jumped on the current-mode filter bandwagon

Recall:

John Hughes introduced the concept of the switched-current filter in 1989 Hughes has been recognized as a renowned filter design expert for many years and has had the benefits of an industrial research environment to support his work

Update on Hughes Work

Recall the Hughes integrator:

$$H(z) = \frac{B}{1 + Az^{-1}}$$

Hughes found the sensitivity of the parameter A was too large in his original structure to make an acceptable lossless integrator

He made some modifications to this approach to improve the sensitivity problem

He worked for about another 10 years to develop practical switchedcurrent filters at Phillips but struggled to get good practical experimental results. He retired several years ago

There appears to be little work going on today on the switched-current filter and there appears to be little adoption of the concept

Conventional Wisdom:

- A current-mode filter is a filter where the input and output variables are currents
- A voltage-mode filter is a filter where the input and output variables are voltages



- Most higher-order filters today are built around one of the following architectures
- These basic structures have evolved because of their performance capabilities (e.g. sensitivities, component spread, ...)
- These basic structures are used irrespective of whether the filter is a "voltage mode" or a "current mode" filter



Most filters today, particularly integrated structures, are built with integrators



Biquads are usually built with integrators !

Most filters today, particularly integrated structures, are built with integrators

Typical integrator-based biquadratic structure (shown LP only)



Tow-Thomas Biquad

- State Variable Biquad
- Two Integrator Loop

Similar to:

- KHN Biquad
- Lead and Lag in a Loop

Most filters today, particularly integrated structures, are built with integrators

Variants of two integrator loop



9

Voltage-Mode Biquad



Current-Mode Biquad



Voltage-Mode Biquad



Current-Mode Biquad



Notice considerable differences in the circuit-level implementations



Observations:

- Structures for voltage mode and current mode Integrators are often the same
- Structures for voltage mode and current mode filters are often the same
- Circuit-level implementations appear to be quite different



Concept of Current-Mode Filters is Somewhat Recent:

Key paper that generated interest in current-mode filters:

Switched currents-a new technique for analog sampled-data signal processing JB Hughes, NC Bird, IC Macbeth - Circuits and Systems, 1989., ..., 1989 - ieeexplore.ieee.org Abstract A technique calledswitched currents, 'for analog sampled-data signal processing in the current domain, is introduced. A family of modules that are capable of various computational and memory functions is described. The modules are well suited to system ... Cited by 193 Related articles All 2 versions Cite

(from Google Scholar Nov 25, 2012)







rate is growing with time !!

Current-Mode Filters The Conventional Wisdom:

TSP 2012:

RECENTLY, current-mode circuits have been receiving considerable attention due to their potential advantages such as inherently wide bandwidth, higher slew-rate, greater linearity, wider dynamic range, simpler circuitry and lower power consumption [1].

CECNet 2012

In analog circuit design, many researches have been performed on current-mode active filters using different active elements [1–22]. The use of current-mode active devices has many other advantages such as larger dynamic, higher bandwidth, greater linearity, simple circuitry and low power consumption compared to that of voltage-mode counterparts for example operational amplifiers [1–2].

Current-Mode Filters The Conventional Wisdom:



Proc. IEE Dec 2006:

1 Introduction

Current-mode circuits have been proven to offer advantages over their voltage-mode counterparts [1, 2]. They possess wider bandwidth, greater linearity and wider dynamic range. Since the dynamic range of the analogue circuits using low-voltage power supplies will be low, this problem can be solved by employing current-mode operation.



Proc. SICE-ICASE, Oct. 2006

1. INTRODUCTION

It is well known that current-mode circuits have been receiving significant attention owing to its advantage over the voltage-mode counterpart, particularly for higher frequency of operation and simpler filtering structure [1].

The Conventional Wisdom:



JSC April 1998:

"... current-mode functions exhibit higher frequency potential, simpler architectures, and lower supply voltage capabilities than their voltage mode counterparts."



CAS June 1992

"Current-mode signal processing is a very attractive approach due to the simplicity in implementing operations such as ... and the potential to operate at higher signal bandwidths than their voltage mode analogues" ... "Some voltage-mode filter architectures using transconductance amplifiers and capacitors (TAC) have the drawback that ..."

The Conventional Wisdom:

ISCAS 1993:



"In this paper we propose a fully balanced high frequency currentmode integrator for low voltage high frequency filters. Our use of the term current mode comes from the use of current amplifiers as the basic building block for signal processing circuits. This fully differential integrator offers significant improvement even over recently introduced circuit with respect to accuracy, high frequency response, linearity and power supply requirements. Furthermore, it is well suited to standard digital based CMOS processes."

The Conventional Wisdom:

Two key publications where benefits of the current-mode circuits are often referenced:



<u>All current-mode frequency selective circuits</u> **GW Roberts**, AS **Sedra** - Electronics Letters, June 1989 - pp. 759-761 <u>Cited by 161</u>

"To make greatest use of the available transistor bandwidth f_{T} , and operate at low voltage supply levels, it has become apparent that analogue signal processing can greatly benefit from processing current signals rather than voltage signals. Besides this, it is well known by electronic circuit designers that the mathematical operations of adding, subtracting or multiplying signals represented by currents are simpler to perform than when they are represented by voltages. This also means that the resulting circuits are simpler and require less silicon area."

The Conventional Wisdom:

Two key publications where benefits of the current-mode circuits are often referenced:



Recent developments in current conveyors and current-mode circuits **B Wilson** - Circuits, Devices and Systems, IEE Proceedings G, pp. 63-77, Apr. 1990 <u>Cited by 203</u>

"The **use** of current rather than voltage as the active parameter can result in higher usable gain, accuracy and bandwidth due to reduced voltage excursion at sensitive nodes. A current-mode approach is not just restricted to current processing, but also offers certain important advantages when interfaced to voltage-mode circuits."

Conventional Wisdom:

- Current-Mode filters operate at higher-frequencies than voltage-mode counterparts
- Current-Mode filters operate at lower supply voltages and lower power levels than voltage-mode counterparts
- Current-Mode filters are simpler than voltage-mode counterparts
- Current-Mode filters offer better linearity than voltagemode counterparts
- Integrated Current-Mode filters require less area

Observation

- Many papers have appeared that tout the performance advantages of current-mode circuits
- In all of the current-mode papers that this author has seen, no attempt is made to provide a quantitative comparison of the key performance features of current-mode circuits with voltage-mode counterparts
- All justifications of the advantages of the current-mode circuits this author has seen are based upon qualitative statements

Observations (cont.)

- In selected comparisons this author has made, performance characteristics of current-mode filters do not appear to be substantially better than those reported for "other" approaches
- It appears easy to get papers published that have the term "current-mode" in the title
- Over 1200 papers have been published in IEEE forums alone !

Research Opportunity (for academia)

- Provide a formal justification of the high frequency, low voltage and low power benefits of current-mode circuits
- Gain insight into how these benefits can be further exploited
- Sounds like a simple problem



- Why does a current-mode circuit work better at high frequencies?
- Why is a current-mode circuit better suited for low frequencies?
- Why do some "voltage"-mode circuits have specs that are as good as the current-mode circuits?

- Why are most of the papers on current-mode circuits coming from academia?
- Why haven't current-mode circuits replaced "voltage"-mode circuits in industrial applications?

- Are current-mode circuits really better than their "voltage-mode" counterparts?
- What is a current-mode circuit?

 Must have a simple answer since so many authors use the term
- Do all agree on the definition of a current-mode circuit?

What is a current-mode circuit?

- Everybody seems to know what it is
- Few have tried to define it
- Is a current-mode circuit not a voltagemode circuit?

What is a current-mode circuit?

"Several analog CMOS continuous-time filters for high frequency applications have been reported in the literature... Most of these filters were designed to process voltage signals. It results in high voltage power supply and large power dissipation. To overcome these drawbacks of the voltage-mode filters, the current-mode filters circuits , which process current signals have been developed"

A **3V-50MHz Analog CMOS Current-Mode High Frequency Filter with a Negative Resistance Load**, pp. 260...,,IEEE Great Lakes Symposium March 1996.

Conventional Wisdom Definition:

- A current-mode circuit is a circuit that processes current signals
- A current-mode circuit is one in which the defined state variables are currents

Example:

Is this a current-mode circuit?



Is this a voltage-mode circuit?



Conventional Wisdom Definition:

A current-mode circuit is a circuit that processes current signals



- One is obtained from the other by a Norton to Thevenin Transformation
- The poles and the BW of the two circuits are identical !



Is the following circuit a voltage mode-circuit or a current-mode circuit?





Is the following circuit a voltage mode-circuit or a current-mode circuit?



Question?

Is the following circuit a voltage mode-circuit or a current-mode circuit?



Observations:

- Voltage-Mode or Current-Mode Operation of a Given Circuit is not Obvious
- All electronic devices have a voltage-current relationship between the port variables that characterizes the device
- The "solution" of all circuits is identical independent of whether voltages or currents are used as the state variables
- The poles of any circuit are independent of whether the variables identified for analysis are currents or voltages or a mixture of the two
Questions about the Conventional Wisdom

Is it possible that there are really no benefits from frequency response, supply voltage and power dissipation viewpoints for "current-mode" circuits?



JSC April 1998:

"... current-mode functions exhibit higher frequency potential, simpler architectures, and lower supply voltage capabilities than their voltage mode counterparts."

Questions about the Conventional Wisdom

Is it possible that there are really no benefits from a frequency response, supply voltage and power dissipation viewpoints for "current-mode" circuits?

Observation: If any so-called current-mode circuit is analyzed using voltages as the port variables, the poles, sensitivities, frequency response, power dissipation, supply voltage requirements and the power dissipation will all be the same!

Questions about the Conventional Wisdom

Since a given structure can be implemented with either current-mode or voltage-mode circuits, is there a fundamental relationship between the performance of so-called currentmode circuits and their "voltage-mode" counterparts? Comparison of Continuous-Time Current-Mode and Voltage-Mode Filters

- Current-Mode and Voltage-Mode Integrators
 - Op-amp based current-mode and voltage-mode integrators
 - $-g_mC$ current-mode and voltage-mode integrators
 - High frequency current-mode and voltage-mode integrators
- Structure Comparisons
 - Two integrator loop filters
 - Leapfrog filters

Basic Feedback Inverting Integrators

Voltage-Mode





$$\frac{V_{OUT}}{V_{IN}} = -\frac{1}{sRC}$$

$$\frac{I_{OUT}}{I_{IN}} = -\frac{1}{sRC}$$

Basic Feedback Non-Inverting Integrators

Voltage-Mode

Current-Mode



 $\frac{V_{OUT}}{V_{IN}} = \frac{1}{sRC}$

 $\frac{I_{OUT}}{I_{IN}} = \frac{1}{sRC}$

Basic OL Non-Inverting Integrators

Voltage-Mode





$$\frac{V_{OUT}}{V_{IN}} = \frac{g_{m}}{sC}$$

$$\frac{I_{OUT}}{I_{IN}} = \frac{g_{m}}{sC}$$

Basic OL Inverting Integrators

Voltage-Mode





$$\frac{V_{OUT}}{V_{IN}} = \frac{-g_{m}}{sC}$$

$$\frac{I_{OUT}}{I_{IN}} = \frac{-g_{m}}{sC}$$

High-Frequency Non-Inverting Integrators

Voltage-Mode



 $\frac{V_{OUT}}{V_{IN}} = \frac{M \bullet g_{m}}{sC}$





High-Frequency Non-Inverting Integrators

Voltage-Mode





$$\frac{V_{OUT}}{V_{IN}} = \frac{M \bullet g_m}{sC}$$

 $\frac{I_{OUT}}{I_{IN}} = \frac{M \bullet g_{m}}{sC}$

High-Frequency Inverting Integrators

Voltage-Mode



 $\frac{V_{OUT}}{V_{IN}} = \frac{-g_{m}}{sC}$

Current-Mode



 $\frac{I_{OUT}}{I_{IN}} = \frac{-g_{m}}{sC}$

Lossy Integrators

Well-known Property:

All voltage-mode and current-mode integrators can be made lossy by placing a resistor in shunt with the capacitor



Basic Feedback Lossy Inverting Integrators





How does the performance of filters that use the current-mode and voltage-mode integrators compare?

A fair comparison should be within a common structure and with a common integrator type

How does the performance of filters that use the current-mode and voltagemode integrators compare?

Will compare the filter performance of

- a two-integrator loop biquad
- a leapfrog filter



"Integrator and Lossy Integrator in a Loop"

Lowpass output to X_{OUT}
$$T(s) = \frac{-l_0^2}{s^2 + \alpha l_0 s + l_0^2}$$

Bandass output to X_{OUT1}

$$T_{1}(s) = \frac{-sI_{0}}{s^{2} + \alpha I_{0}s + I_{0}^{2}}$$



Alternate Equivalent Representation: $I_0 \leftrightarrow \omega_0 = \alpha_0 \leftrightarrow \omega_0$





Alternate implementation of Lossy Integrator





- For notational convenience, the input signal can be suppressed and output will not be designated
- This forms the "dead network"
- Poles for dead network are identical to original network as are key sensitivities



Two Integrator Loop Biquad



Consider a current-mode implementation:





Consider the corresponding voltage-mode implementation:













How does the performance of filters that use the current-mode and voltagemode integrators compare?

How does the performance of filters that use the current-mode and voltagemode integrators compare?

The corresponding current-mode and the voltage-mode two integrator loop biquad filters are identical!

How does the performance of filters that use the current-mode and voltagemode integrators compare?

The performance (speed, signal swing, sensitivity, linearity, power dissipation, etc.) of these circuits is identical !



Current-mode:



Standard OTA



Voltage-mode:



Standard OTA

Current-mode



Consider lower OTA in stage k-2, capacitor in stage k-1 and upper OTA in stage k



Current-mode

Consider upper OTA in stage k-1, capacitor in stage k and lower OTA in stage k+1





Consider lower OTA in stage k, capacitor in stage k+1 and upper OTA in stage k+2



g_m

C_{k-2}

 g_{m}

C_{k-1}

 \forall

Current-mode



g_m

C_k

gm

C_{k+1}

72

3-08

Terminated Leap-Frog Filter (3-rd order lowpass)



Current-mode implementation



Current-mode implementation



Current-mode implementation


Current-mode implementation



I/O Source Transformation



Current-mode implementation



Redraw as:



Current-mode implementation



This is a voltage-mode implementation of the Leap-Frog Circuit !

SUMMARY

Current-mode implementation



Voltage-mode implementation





Comment

The current-mode and voltage-mode equivalence also exists for the high-frequency single transistor twointegrator loop filters and leapfrog filter structures

Question:

How does the performance of filters that use the current-mode and voltagemode integrators compare?



Question:

How does the performance of filters that use the current-mode and voltagemode integrators compare?

The current-mode and the voltagemode leapfrog filters are identical!

Question:

How does the performance of filters that use the current-mode and voltagemode integrators compare?

The performance (speed, signal swing, sensitivity, linearity, etc.) of these circuits is identical !

Current-Mode Filters

Conventional Wisdom

- Current-Mode circuits operate at higher-frequencies than voltage-mode counterparts
- Current-Mode circuits operate at lower supply voltages and lower power levels than voltage-mode counterparts
- Current-Mode circuits are simpler than voltage-mode counterparts
- Current-Mode circuits offer better linearity than voltage-mode counterparts

Reconciliation of Conventional Wisdom and Fundamental Concepts

- The choice of state (or stated) port variables plays no role on the fundamental performance characteristics of a filter
- Many current-mode and voltage-mode filters that have appeared in the literature are identical
- The issue of whether there are any performance advantages from the viewpoint of supply voltage, speed of operation and linearity of continuous-time current-mode filters over voltmode counterparts is in question

