

2) ① Chapter 7

② Quiz

③ Test

④ Next Week

⑤ Lab

⑥ Grading & Records

⑦ evaluations

T Chapter 7

W → Chapter 7 + Quiz

Th → Chapter 7 + Review

F → Test Chapter 7

⇒ M → Review / self evaluation. how did you do, what should you do to get the grade you want.

W → ~~Evaluation & Per.~~

Makeup (comp., optional)

Th Evaluation & Per.

F Final (all chapters everything)

⇒ all chapter 7 HW is due Fri with the test

⇒ Make up for Test 3 is due Monday 3rd.

⇒ Make up for Test 4 is due Final.

- (a) The source voltage in the circuit in Fig. P7.21 is $v_s = 96 \cos 10,000t$ V. Find the values of L such that i_s is in phase with v_s when the circuit is operating in the steady state.
- (b) For the values of L found in (a), find the steady-state expressions for i_s .

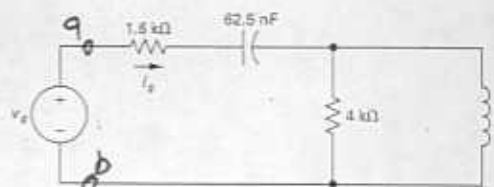


Figure P7.21

$$v_s(t) = 96 \cos 10000t \text{ V}$$


↓

$$V_s = 96 \angle 0^\circ \text{ V} = 96 e^{j(0)}$$

$$V_{sm} = 96$$

$$\omega = 10000 \text{ rad/s}$$

Find L so that i_s is in phase with V_s

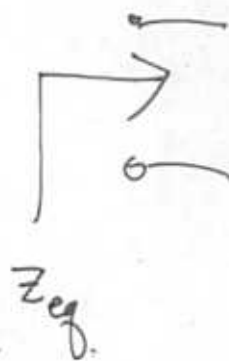

$$I_s = \frac{V_s}{Z_{eq}}$$

The only way I_s will be in phase

$$\theta_v = \theta_i$$

with $V_s \Rightarrow$ is to have

$$Z_{eq} = |Z_{eq}| \angle 0^\circ$$

for Z_{eq} to have 0 angle



all real! $\Rightarrow$ Kill the imag. part!!

- (a) The source voltage in the circuit in Fig. P7.21 is $v_s = 96 \cos 10,000t$ V. Find the values of L such that i_g is in phase with v_s when the circuit is operating in the steady state.
- (b) For the values of L found in (a), find the steady-state expressions for i_g .

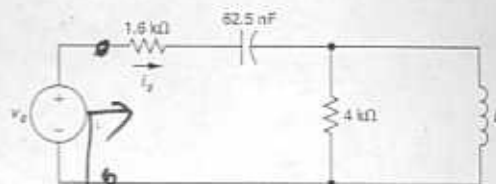


Figure P7.21

what is Z_{eq}

This can be viewed as Th. in complex domain.

$$Z_{eq} = 1.6K + \frac{1}{j(10000) 62.5n} + \left[\frac{1}{4K} + \frac{1}{j\omega L} \right]^{-1}$$

$$= 1.6K + \frac{1}{j\omega C} + \left[\frac{j\omega L + 4K}{(4K)(j\omega L)} \right]^{-1}$$

$$Z_{eq} = 1.6K + \frac{1}{j\omega C} + \frac{(4K)(j\omega L)}{j\omega L + 4K}$$

$$\rightarrow \frac{(4K)(j\omega L)}{j\omega L + 4K} \cdot \frac{-j\omega L + 4K}{-j\omega L + 4K}$$

$$\frac{(4K)\omega^2 L^2 + 16 \times 10^6 j\omega L}{\omega^2 L^2 + 16 \times 10^6}$$

look at the imag. part

$$0 = \frac{1}{j\omega C} + \frac{16 \times 10^6 j\omega L}{\omega^2 L^2 + 16 \times 10^6} \Rightarrow 0$$

$$L = \begin{cases} 0.8H \\ \text{or} \\ 0.2H \end{cases}$$

$$\omega = 10000$$

$$L = ?$$

$$C = 62.5 \times 10^{-9}$$

- (a) The source voltage in the circuit in Fig. P7.21 is $v_s = 96 \cos 10,000t$ V. Find the values of L such that i_g is in phase with v_s when the circuit is operating in the steady state.
- (b) For the values of L found in (a), find the steady-state expressions for i_g .

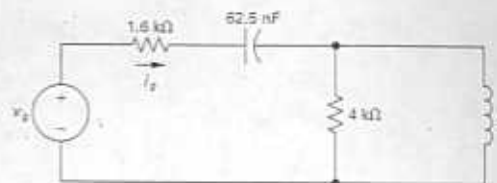


Figure P7.21

$$L = 0.8 \text{ H}$$

$$Z_{eq} = 4800 \Omega$$

$$I_g = \frac{V_0}{Z_{eq}} = \frac{96 \angle 0^\circ}{4800 \angle 0^\circ} = 20 \angle 0^\circ \text{ mA}$$

$$i_g(t) = \text{Re} \left\{ I_g e^{j\omega t} \right\}$$

$$i_g(t) = 20 \cos(10000t) \text{ mA}$$


$$L = 0.2 \text{ H}$$

$$\oplus Z_{eq} = 2400 \Omega$$

$$I_g = 40 \angle 0^\circ \text{ mA}$$

$$i_g(t) = 40 \cos(10000t) \text{ mA}$$

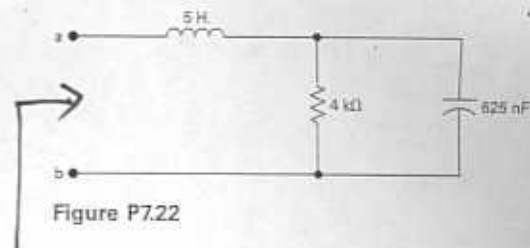- (a) For the circuit shown in Fig. P7.22, find the frequency (in radians per second) at which the impedance Z_{ab} is purely resistive.
 (b) Find the value of Z_{ab} at the frequency of (a).



$$Z_{ab} \triangleq \text{purely resistive} \Rightarrow \angle 0^\circ$$

$$\triangleq \text{purely reactive} \Rightarrow \angle 90^\circ$$


$$i_g = 50 \sin(\omega t - \frac{\pi}{4})$$

no phase diff

for

V_g

1st go to imped. plane.

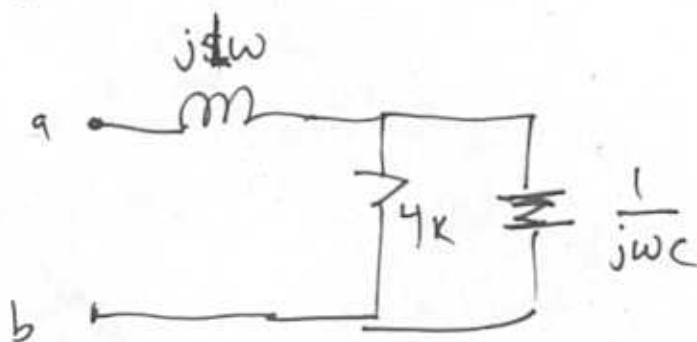

$$Z_{ab} = j\omega L + \left[\frac{1}{4k} + j\omega C \right]^{-1}$$

$$= j\omega L + \left[\frac{1 + j\omega C(4 \times 10^3)}{4k} \right]^{-1}$$

$$= j\omega L + \frac{4 \times 10^3}{1 + j\omega C(4 \times 10^3)} \cdot \frac{1 - j\omega C(4 \times 10^3)}{1 - j\omega C(4 \times 10^3)}$$

$$= j\omega L + \frac{4 \times 10^3 - j\omega C(16 \times 10^6)}{1 + \omega^2 C^2 (16 \times 10^6)}$$

- (a) For the circuit shown in Fig. P7.22, find the frequency (in radians per second) at which the impedance Z_{ab} is purely resistive.
 (b) Find the value of Z_{ab} at the frequency of (a).

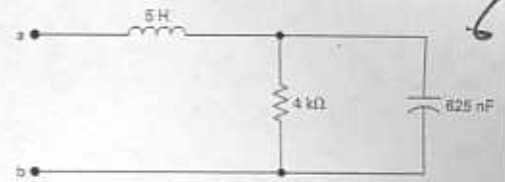


Figure P7.22

$$Z_{ab} = \frac{4 \times 10^3}{1 + \omega^2 L^2 (16 \times 10^6)} + j \left[\omega L - \frac{\omega L \times 16 \times 10^6}{1 + \omega^2 L^2 (16 \times 10^6)} \right]$$

for purely resistive
 This "imag. part"
 should go to zero

$$C = 625 \text{ nF}$$

$$L = 5 \text{ H}$$

$$\omega = ? \Rightarrow \omega = 400 \text{ rad/s}$$

$$Z_{ab} = 2600 \Omega$$

$$\omega L = \frac{\text{rad}}{\text{s}} \text{ H} \triangleq \Omega$$

$$\frac{1}{\omega C} = \frac{1}{\frac{\text{rad}}{\text{s}} \text{ F}} \triangleq \Omega$$

$$V = L \frac{di}{dt} \Rightarrow \text{⓪}$$

$$V = L \frac{A}{s} \Rightarrow \frac{V}{A} = \frac{\text{H}}{\text{s}} = \Omega$$

$$i = C \frac{dV}{dt}$$

$$A = \text{F} \frac{\text{V}}{\text{s}} \Rightarrow \frac{V}{A} = \frac{\text{s}}{\text{F}}$$

(7)

$$\sqrt{\frac{L}{C}} \rightarrow \sqrt{\frac{j\omega L}{j\omega C}} = \sqrt{\frac{\Omega}{\frac{1}{\Omega}}} = \Omega$$

$$\frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{V}{A} s \frac{A}{V} s}} = \frac{1}{s}$$

L?

$$V = L \frac{di}{dt}$$

$$\frac{V}{A} s = H$$

$$i = C \frac{dV}{dt}$$

$$\frac{A}{V} s = F$$

dim. f & ω are the same $\frac{1}{s}$

but

$f \equiv$ cyl. per second.

$$2\pi f = \omega = \frac{\text{rad}}{s}.$$

7.29 p379

$$v_g = 150 \cos(8000\pi t + 20^\circ) \text{ V}$$

a)

$$i_g = 30 \sin(8000\pi t + 38^\circ) \text{ A}$$

$$V_g = 150 \angle 20^\circ = 150 e^{j 20 (\frac{\pi}{180})}$$

$$I_g = -j 30 \angle 38^\circ = 30 e^{j 38 \frac{\pi}{180}} e^{-j \frac{\pi}{2}}$$

$$= 30 \angle 38^\circ - 90^\circ = 30 \angle -52^\circ = 30 e^{-j 52 (\frac{\pi}{180})}$$

$$Z = \frac{V_g}{I_g} = \frac{150 \angle 20^\circ}{30 \angle -52^\circ} = 5 \angle 20^\circ + 52^\circ$$

$$= 5 \angle 72^\circ \Omega$$

b)

i_g lags v_g by 72°

72

$$2\pi f = 8000\pi \Rightarrow f = 4000$$

$$\frac{72}{360} (250) = 50\mu\text{s}$$

$$T = 250\mu\text{s}$$

i_g lags v_g ~~with~~ by $50\mu\text{s}$

$$\omega (\frac{\text{rad}}{\text{s}}) \left(\frac{180 \text{ deg}}{\pi \text{ rad}} \right) = \frac{\omega}{\pi} 180 \frac{\text{deg}}{\text{s}}$$


7.36 P380

90

$$\omega = 25 \text{ krad/s}$$

$$C \rightarrow \frac{1}{j\omega C} =$$
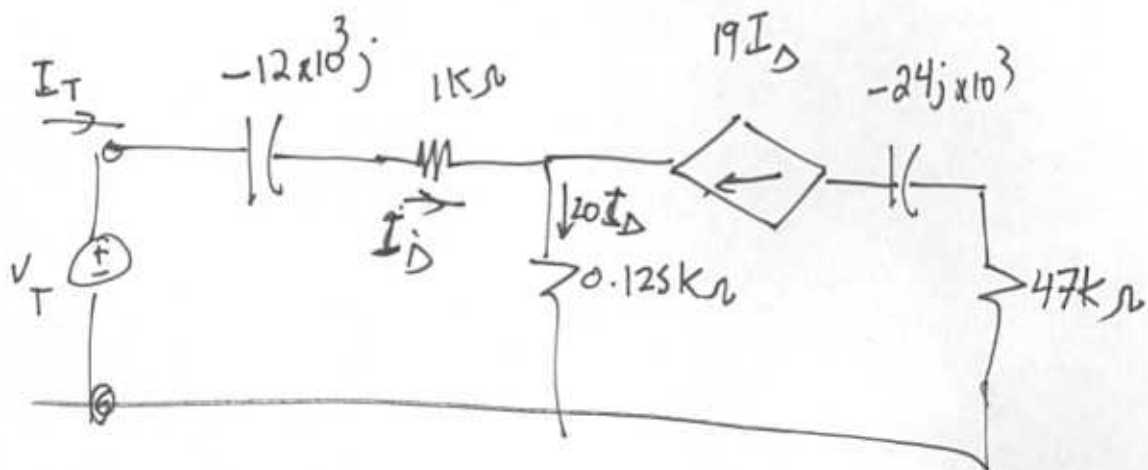
$$\begin{aligned} \frac{10}{3} \text{ nF} &\downarrow \frac{5}{3} \text{ nF} \longrightarrow -j \frac{1}{\omega C} = -j \frac{1}{(25 \times 10^3)(\frac{5}{3} \times 10^{-9})} \\ &= -j(12 \text{ k}\Omega) \end{aligned}$$



$$I_D \triangleq I_T$$

$$V_T = (1 - 12j) \times 10^3 I_D + 20 I_D (0.125) \times 10^3 \Omega$$

$$\frac{V_T}{I_T} = 1 - 12j + 20(0.125) \text{ K}$$

$$Z_y = 3.5 - 12j \text{ k}\Omega$$