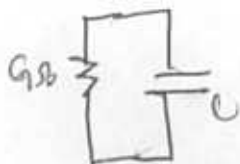


- ① chapter 7
- ② Quiz → wedid
- ③ Test #3 → nr. is about 79-80%
- ④ - Pspice → remember
- ⑤ self evaluation
 ↳ will talk about NEXT time



For self evaluation
 please look at your work
 For 201 in detail. How have
 you been doing? what grade would
 you give yourself? How could
 you improve & how could you
 get an A? what should you do?
 You need to do the above for your self evaluation.

Find the complex impedance in polar form of the network shown in Figure P5.23 for $\omega = 500$. Repeat for $\omega = 1000$ and $\omega = 2000$.

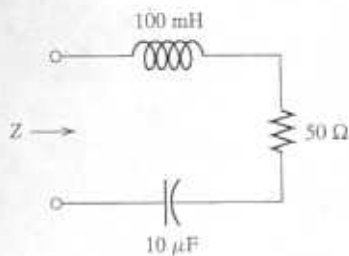


Figure P5.23

$$Z = j\omega L + R + \frac{1}{j\omega C}$$


$$= j\omega(100 \times 10^{-3}) + 50 + \frac{1}{j\omega 10 \times 10^{-6}}$$

$$\omega = 500 \quad Z = 50 - j150 = 158.1 \angle -71.57^\circ = 158.1 e^{-j71.57 \frac{\pi}{180}}$$

$$\omega = 1000 \quad Z = 50 = 50 \angle 0^\circ = 50 e^{j(0)}$$

$$\omega = 2000 \quad Z = 50 + j150 = 158.1 \angle 71.57^\circ = 158.1 e^{j71.57 \frac{\pi}{180}}$$

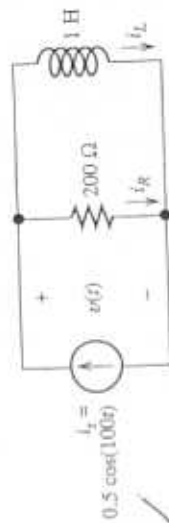P5.29. Find the phasors for the voltage and the currents of the circuit shown in Figure P5.29. Construct a phasor diagram showing I_s , V , I_R , and I_L . What is the phase relationship between V and I_s ?



$$I_R = \frac{V}{200} = 0.224 \angle 63.44^\circ$$

$$I_L = \frac{V}{j(100)} = 0.447 \angle -26.56^\circ$$

or

$$I_R = 0.5 \angle 0^\circ \frac{j100}{200 + j100}$$

$$I_L = 0.5 \angle 0^\circ \frac{200}{200 + j100}$$

$$I_s = 0.5 \angle 0^\circ \text{ A}$$

$$V = I_R \left(\frac{1}{200} + \frac{1}{j\omega L} \right)^{-1}$$

$$= 0.5 \angle 0^\circ \left[\frac{1}{200} + \frac{1}{j(100)(1)} \right]^{-1}$$

$$V = 0.5 \angle 0^\circ \left[\frac{1}{200} - \frac{j}{100} \right]^{-1}$$

$$V = 44.7 \angle 63.44^\circ \text{ V}$$

$$v(t) = \operatorname{Re} \{ e^{j\omega t} V \} = 44.7 \cos(100t + 63.44^\circ) \text{ V}$$

4. Consider the circuit shown in Figure P5.33. Find the phasors V_1 , V_2 , V_R , V_L , and I . Draw the phasor diagram to scale. What is the phase relationship between I and V_1 ? Between I and V_L ?

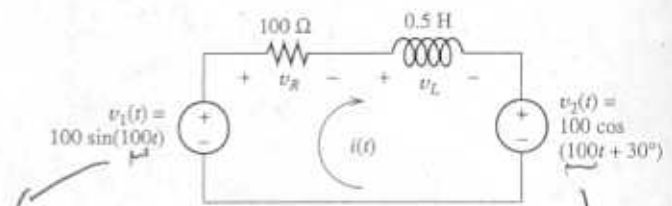


Figure P5.33

$$\omega = 100 \text{ rad/s}$$

$$V_2 = 100 \angle 30^\circ$$

$$V_2 = 100 e^{j\frac{\pi}{6}}$$

$$-j100 \angle 0^\circ$$

$$V_1 = 100 \angle -90^\circ$$

$$\text{Re} \left\{ e^{j\omega t} 100 e^{-j\frac{\pi}{2}} \right\} = 100 e^{j(\omega t - \frac{\pi}{2})}$$

$$100 \cos(\omega t - \frac{\pi}{2})$$

$$100 \left[\cos(\omega t) \cos \frac{\pi}{2} + \sin \omega t \sin \frac{\pi}{2} \right]$$

$$100 \sin \omega t = 100 \sin 100t$$

$$I = ?$$

$$-V_1 + [100 + j(100)(0.5)] I + V_2 = 0$$

$$I = \frac{V_1 - V_2}{100 + j50} = \frac{100 \angle -90^\circ - 100 \angle 30^\circ}{100 + j50}$$

$$= \frac{-j100 - (86.6 + j50)}{100 + j50}$$

$$\Rightarrow I = 1.55 \angle -146.6^\circ$$

$$i(t) = 1.55 \cos(100t - 146.6^\circ)$$

5. Consider the circuit shown in Figure P5.33. Find the phasors V_1 , V_2 , V_R , V_L , and I . Draw the phasor diagram to scale. What is the phase relationship between I and V_1 ? Between I and V_L ?

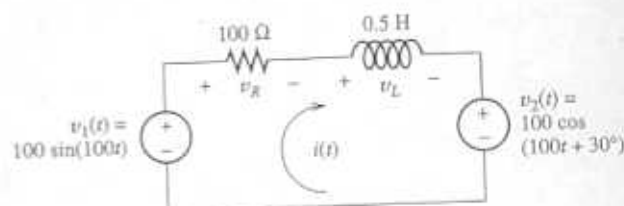


Figure P5.33

$$V_R = I(100) \approx 155 \angle -146.6^\circ$$

$$V_L = I(j\omega L) = 155 \angle -146.6^\circ [j50]$$

$$V_L = 77.5 \angle -56.6^\circ$$

$$v_L(t) = 77.5 \cos(100t - 56.6^\circ)$$

is this the same as

$$L \frac{di(t)}{dt} = ? \quad \text{it should be!}$$

P5.38. Solve for the mesh currents shown in Figure P5.38.

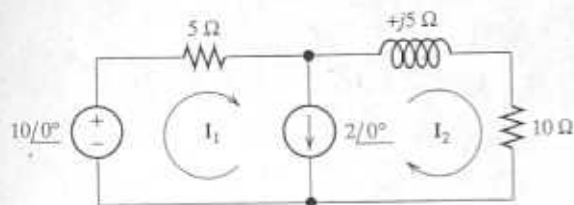


Figure P5.38

Super mesh condition

$$\begin{cases} I_1 - I_2 = 2\angle 0^\circ \\ -10\angle 0^\circ + 5I_1 + 5jI_2 + 10I_2 = 0 \end{cases}$$

$$I_1 = 2\angle 0^\circ \rightarrow i_1(t) = 2 \cos(\omega t)$$

$$I_2 = 0$$

↓
do you know
this?

if somewhere in the
problem they would say

$L = 0.2 \text{ mH} \Rightarrow$ then you
know ω .

P5.34. Consider the circuit shown in Figure P5.34. Find the phasors I , I_R , and I_C . Construct the phasor diagram.


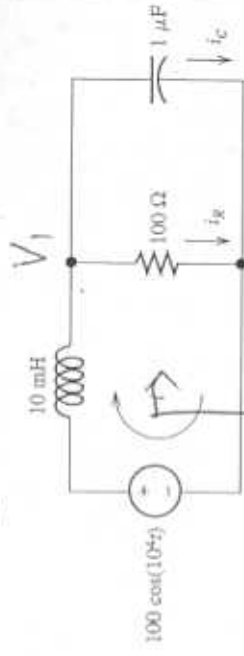


Figure P5.34

Imp-
phasor

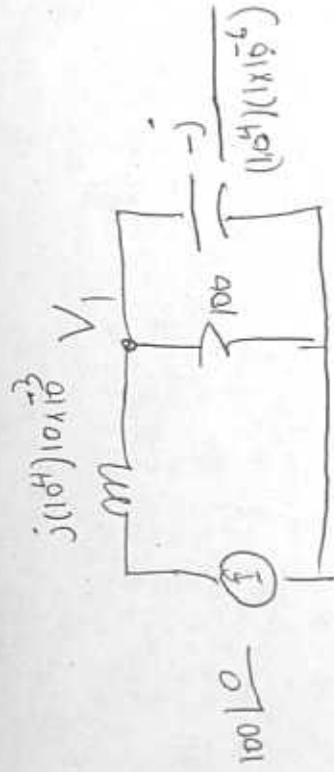

$$\frac{V_1 - 100I}{100j} + \frac{V_1}{100} + \frac{V_1}{100} = 0$$

$$Z_C = \frac{-j}{10^4 \times 10^{-6}} = -j100$$

$$\frac{V_1 - 100I}{100j} + \frac{V_1}{100} + \frac{V_1}{-j100} = 0$$

$$I_R = \frac{V_1}{100} \quad \& \quad I_C = \frac{V_1}{-j100}$$

easy way

$$Z_Y = j100 + \frac{1}{\frac{1}{R} + \frac{1}{j\omega C}} = j100 + \frac{1}{0.01 + j0.01}$$

$$Z_Y = 50 + j50$$

$$I = \frac{100 \angle 0^\circ}{Z_Y} = \frac{100 \angle 0^\circ}{50 + j50}$$

$$I = 1.414 \angle -45^\circ$$

$$I_R = I \frac{\frac{1}{j\omega C}}{100 + \frac{1}{j\omega C}} = I \frac{Z_C}{R + Z_C} \quad Z_C = \frac{1}{j\omega C}$$

$$I_R = -j = 1 \angle -90^\circ$$

$$I_C = I \frac{R}{R + Z_C} = I \frac{100}{100 + \frac{1}{j10^4 \times 10^{-6}}} = 1 \angle 0^\circ$$

$$I = I_R + I_C = -j + 1 = 1.414 \angle -45^\circ$$

1

Find the average power dissipated in the $20\ \Omega$ resistor in the circuit seen in Fig. P7.68 if $i_g = 15 \cos 10,000t$ A.

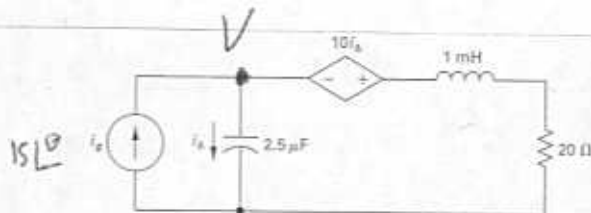


Figure P7.68

$$j\omega L = j(10000)1 \times 10^{-3} = 10j\ \Omega$$

$$\frac{1}{j\omega C} = \frac{1}{j(10000)(2.5 \times 10^{-6})} = -40j\ \Omega$$

$$\begin{cases} -15\angle 0^\circ + \frac{V}{-40j} + \frac{V + 10I_\Delta}{20 + 10j} = 0 \\ I_\Delta = \frac{V}{-j40} \end{cases}$$

$$V = 300 - j100\text{ V}$$

$$I_\Delta = 2.5 + j7.5\text{ A}$$

$$I_R = 15\angle 0^\circ - I_\Delta = 15\angle 0^\circ - 2.5 - j7.5$$

$$\boxed{I_R = 14.58\angle -30.9^\circ\text{ A}}$$

$$P_{20\Omega} = \frac{\text{Re}}{2} [V_R I_R^*] = \frac{\text{Re}}{2} [I_R R I_R^*]$$

$$\frac{\text{Re}}{2} \left[V_R \left(\frac{V_R}{R} \right)^* \right] = \frac{\text{Re}}{2} \left[\frac{|V_R|^2}{R} \right] \quad I_R I_R^* = |I_R|^2$$

$$P_{20} = \frac{1}{2} |14.58|^2 (20\ \Omega) = 2125\text{ W}$$

Complex Pow

$$= \frac{1}{2} V I^*$$

Ave power

$$\text{Re} \left[\frac{1}{2} V I^* \right]$$

Reactive Pow

$$\text{Im} \left[\frac{1}{2} V I^* \right]$$