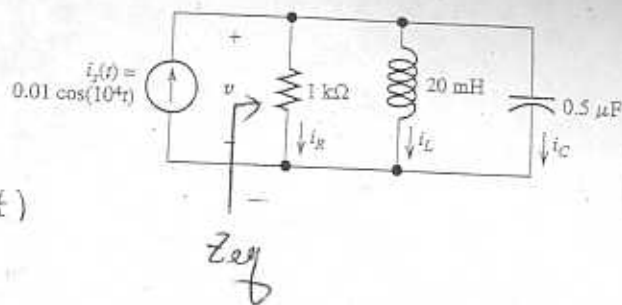


① Find i_R, i_L, i_C
in phasor form



①

② Use i_C in phasor form to find $i_C(t)$

① Z_{eq}

② $V = I Z_{eq}$

③ $\frac{V}{R} = I_R$ $\frac{V}{\frac{1}{j\omega L}} = I_L$ $\frac{V}{\frac{1}{j\omega C}} = I_C$

④ $i_C(t) = \text{Re}\{e^{j\omega t} \bar{I}_C\}$

$$Z_{eq} = \left[\frac{1}{1k} + \frac{1}{j(10^4)(20 \times 10^{-3})} + j(10^4)(0.5 \times 10^{-6}) \right]^{-1}$$

$\left(\frac{1}{\frac{1}{j\omega C}} \right)$

$\rightarrow Z_{eq} = 1000$

$V = I_g Z_{eq} = 0.01 \angle 0 \cdot 1000 = 10 \angle 0 \text{ Volts}$

$I_R = \frac{10 \angle 0}{1k} = 10 \angle 0 \text{ mA}$

$I_C = \frac{10 \angle 0}{\frac{1}{j\omega C}} = 10 \angle 0 (j 10^4)(0.5 \times 10^{-6}) = 0.05 \angle 90^\circ \text{ A}$

$I_L = \frac{10 \angle 0}{j\omega L} = 0.05 \angle -90^\circ \text{ A}$

$i_C(t) = 0.05 \cos(10^4 t + 90^\circ)$

The voltage V_g in the frequency-domain circuit shown in Fig. P7.70 is $340 \angle 0^\circ$ V (rms).

- Find the average and reactive power delivered by the voltage source.
- Is the voltage source absorbing or delivering average power?
- Is the voltage source absorbing or delivering magnetizing vars?
- Find the average and reactive powers associated with each impedance branch in the circuit.
- Check the balance between delivered and absorbed average power.
- Check the balance between delivered and absorbed magnetizing vars.

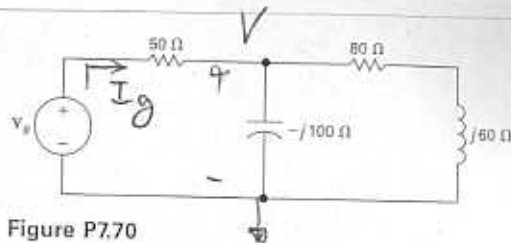


Figure P7.70

$$\frac{V}{-j100} + \frac{V}{80 + j60} + \frac{V - 340 \angle 0^\circ}{50} = 0$$

$$V = 238 - j34 \text{ V}$$

$$I_g = \frac{V_g - V}{50} = \frac{340 \angle 0^\circ - 238 + j34}{50} = 2.04 + j0.68 \text{ A}$$

$$S_g = V_g I_g^* = 340 \angle 0^\circ (2.04 - j0.68)$$

$$S = 693.6 - j231.2 \text{ VA}$$

693.6 W avg. power

b) → Source is delivering

231.2 Vars reactive pow

c) The source is absorbing 231.2 Vars

d)

The voltage V_s in the frequency-domain circuit shown in Fig. P7.70 is $340 \angle 0^\circ$ V (rms).

- Find the average and reactive power delivered by the voltage source.
- Is the voltage source absorbing or delivering average power?
- Is the voltage source absorbing or delivering magnetizing vars?
- Find the average and reactive powers associated with each impedance branch in the circuit.
- Check the balance between delivered and absorbed average power.
- Check the balance between delivered and absorbed magnetizing vars.

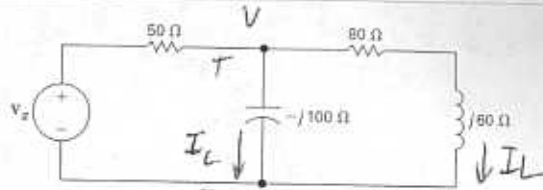


Figure P7.70

$$I_C = \frac{V}{-j100} = \frac{238 - j34}{-j100}$$

$$= 0.34 + j2.38 \text{ A}$$

$$S_C = V I_C^* = (238 - j34)(0.34 - j2.38 \text{ A})$$

$$S_C = 0 - j578 \text{ VA}$$

$$\rightarrow 578 \text{ vars}$$

$$I_L = \frac{V}{80 + j60} = 1.7 - j1.7 \text{ A}$$

$$S_L = V I_L^* = (238 - j34)(1.7 + j1.7)$$

$$S_L = \underbrace{462.4}_{\text{watts}} + j \underbrace{346.8}_{\text{vars}} \text{ VA}$$

average power
diss in the resist.

$$S_{50\Omega} = V_{50} I_0^* = \begin{cases} I_0 R I_0^* = |I_0|^2 R \xrightarrow{50} = 231.2 \text{ W} \\ V_{50} \frac{V_{50}^*}{R} = \frac{|V_0|^2}{R} \xrightarrow{50} \end{cases}$$

The voltage V_s in the frequency-domain circuit shown in Fig. P7.70 is $340 \angle 0^\circ$ V (rms).

- Find the average and reactive power delivered by the voltage source.
- Is the voltage source absorbing or delivering average power?
- Is the voltage source absorbing or delivering magnetizing vars?
- Find the average and reactive powers associated with each impedance branch in the circuit.
- Check the balance between delivered and absorbed average power.
- Check the balance between delivered and absorbed magnetizing vars.

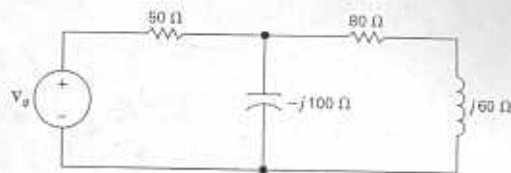


Figure P7.70

$$\begin{aligned}
 S_L &= V I_L^* \\
 &= I_L (-j100) I_L^* \\
 &= |I_L|^2 (-j100)
 \end{aligned}$$

or

$$\begin{aligned}
 &= V \left(\frac{V}{-j100} \right)^* \\
 &= |V|^2 \frac{1}{j100} = -j \frac{|V|^2}{100}
 \end{aligned}$$

Consider the circuit shown in Figure P5.43. Find the phasor current I . Find the power, reactive power, and apparent power delivered by the source. Find the power factor and state whether it is lagging or leading.

5

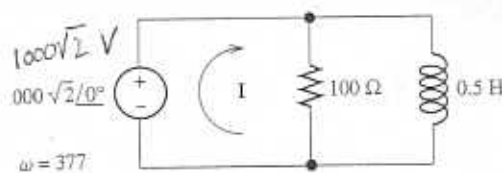


Figure P5.43

$$I = \frac{1000\sqrt{2}}{100 + j(377)(0.5)} = 16.01 \angle -27.95^\circ$$

$$\left[\frac{1}{100} + \frac{1}{j(377)(0.5)} \right]^{-1}$$

$$i(t) = 16.01 \cos(377t - 27.95^\circ)$$

$$P = V_{rms} I_{rms}^* = \frac{1}{2} V I^* = P + jQ$$

$\swarrow$ 10 k Watts $\searrow$ $j(5.3) \text{ k VARs}$

$$\text{Apparent power} = \sqrt{P^2 + Q^2} = V_{rms} I_{rms}$$

$$= 11.32 \text{ k VA}$$

$$\text{Power factor} = \tan^{-1} \frac{Q}{P}$$


$$S = S_1 e^{j\theta} = \underbrace{S_1 \cos \theta}_P + j \underbrace{S_1 \sin \theta}_Q$$

this will work.


$$\text{pf} = \cos(\theta_v - \theta_i) = \cos(0 - (-27.95)) = \cos(27.95) = 0.883$$

88.3% lagging.

(6)

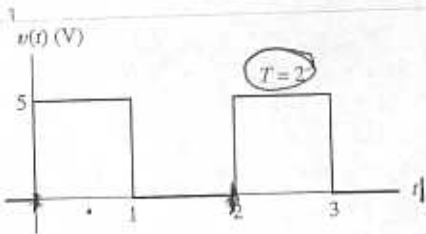
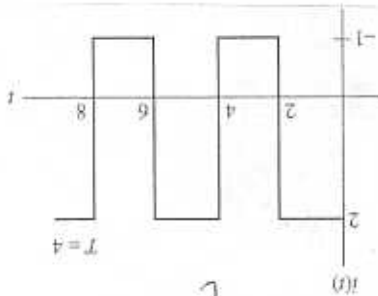
$$= \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$



$$= \sqrt{\frac{1}{2} \int_0^2 2^2 dt + \int_2^4 0 dt} = \sqrt{\int_0^2 2^2 dt + \int_2^4 0 dt}$$


$$= \sqrt{\frac{2 \cdot 2}{2}} = \frac{2}{\sqrt{2}}$$

$$= \sqrt{12.5} =$$

$$V_{rms} \approx 3.536 V$$



$$\sqrt{\frac{1}{4} \int_0^4 i^2 dt} = \sqrt{\frac{1}{4} \left[\int_0^2 2^2 dt + \int_2^4 (-1)^2 dt \right]}$$

$$i_{rms} = 1.58 A$$


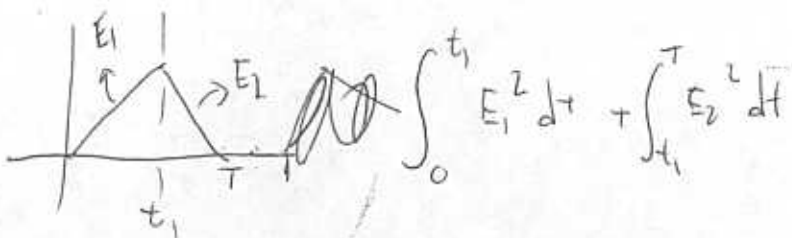


or Carefully
use area under the
curve for V^2

7

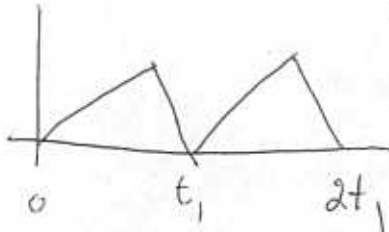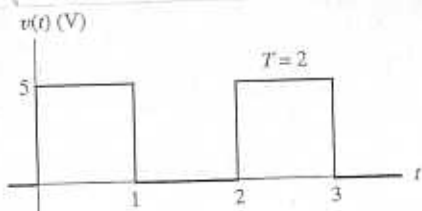

$$T = t_1$$

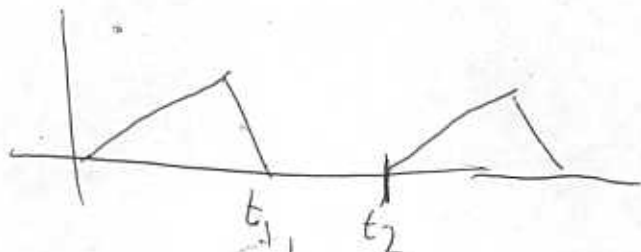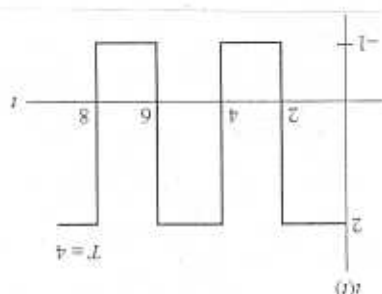

$$T = t_2$$

becareful
with choosing
the right period