EE 505

Lecture 15

String DACs Current Steering DACs

General Performance Concerns: 1.Glitch

2.Ringing

3.Incomplete Settling

4.Kickback

1. Output feeding back to the input due to gate to drain capacitance 5.Mismatch

- 1. Local Random Variations (Handled with area)
- 2. Gradient Effects (Handled with Common Centroid)

String DACs:

1.Large number of elements

2.Routing is significant for decoder

- 1. Matrix Decoder dramatically simplifies routing
 - 1. Severe previous code dependance (Can have memory)
- 2. Tree Decoder with Pass Transistor Logic can help as well
- 3. Row and Column Decoder can be used to decrease area
- 4. Fine String Interpolator
 - 1. Reduces decoder complexity
 - 2. Reduces number of switches and resistors
 - 3. Could use 2 interpolators for when interpolator is near VDD or near 0
 - 4. Switch resistance determines tap voltages

3.Fairly Large INL

4. Significant Previous Code Dependance (Large Parasitic Capacitance)

5. Gradient Effects can cause trouble (Common Centroid Difficult)

1. Include a course string to dump most of the area into for common centroid layout

6.Settling time dependant on Thevenin impedance

Current Steering DACs:



Note Dual Ladder is used !

AND pixel sensor gate32x32 Matrix

A 10-b 50-MHz CMOS D/A converter with 75- ω buffer

MJM **Pelgrom** - Solid-State Circuits, IEEE Journal of, 1990 - ieeexplore.ieee.org Abstracf-A 10-b 50-MHz digital-to-analog (D/A) converter is pre-sented which is based on a dual-ladder resistor string. This approach allows the linearity requirements to be met without the need for selection or trimming. The D/A decoding scheme reduces the glitch energy, ... Cited by 109 Related articles All 3 versions Cite Save

Review from Last Lecture

Common-Centroid Anti-Parallel Ladder Layout



Review from Last Lecture

Common-Centroid Anti-Parallel Ladder Layout



Interconnects Not Shown





Sometimes termed sub-divider, sub-range or dual-string DAC

R-String DAC Buffered Fine String Interpolator





 $N_2 = 2^{n_2}$

Paralleling each R will be either the interpolator or a resistor of value N_2R_F

Area of N_2R_F resistors may be very small

Tap voltages on coarse R-string should not change with X_{IN}



Basic R-String DAC









Transfer	

Latching Boolean Signal Can Reduce/Eliminate Logic Transients which Cause Distortion



Dither DAC



For all b_1 and b_2 , $R_U+R_L=R$

- Another Segmented DAC structure
- Can be viewed as a "dither" DAC
- Often n₁ is smaller than n₂
- Dither can be used in other applications as well

Basic R-String DAC



Impedance facing V_{OUT} is code dependent



No loading of V_{REF} Kickback to V_{REF} removed



 $d_{k} = \begin{cases} 1 & \text{if } S_{k} \text{ closed} \\ 0 & \text{if } S_{k} \text{ open} \end{cases}$

$$V_{OUT} = \left[\sum_{l=1}^{k} \mathbf{d}_{i} \mathbf{l}_{i}\right] (-\mathbf{R})$$

- Current sources usually unary or binary-bundled unary
- Termed bottom-plate switching
- Can eliminate resistors from DAC core
- Op Amp and resistor R can be external
- Can use all same type of switches
- Switch impedance not critical nor is switch matching
- Popular MDAC approach



Inherently Insensitive to Nonlinearities in Switches and Resistors

- Termed "top plate switching"
- Thermometer coding (routing challenge!)
- Excellent DNL properties
- INL may be poor, typically near mid range
- Switch kickback to V_{REF}
- Not suitable for use as MDAC

Unary Current Sources



- Inherently Insensitive to Nonlinearities in Switches and Resistors
- Smaller ON resistance and less phase-shift from clock edges
 - Termed "bottom plate switching"
 - Thermometer coded
 - Can be used as MDAC
 - Reduced kickback to V_{REF}



- All single-transistor n-channel devices for switcher
- Unary R:switch cells
- Parasitic capacitances on drain nodes of switches cause transient settling delays
- R+Rsw is nonlinear (so nonlinear relationship between I_k and V_{REF}) but does not affect linearity of DAC
- Resistor and switch impedance matching important
- **Previous code dependent transient** (parasitic capacitances on drains of switches)



Stay Safe and Stay Healthy !

End of Lecture 15