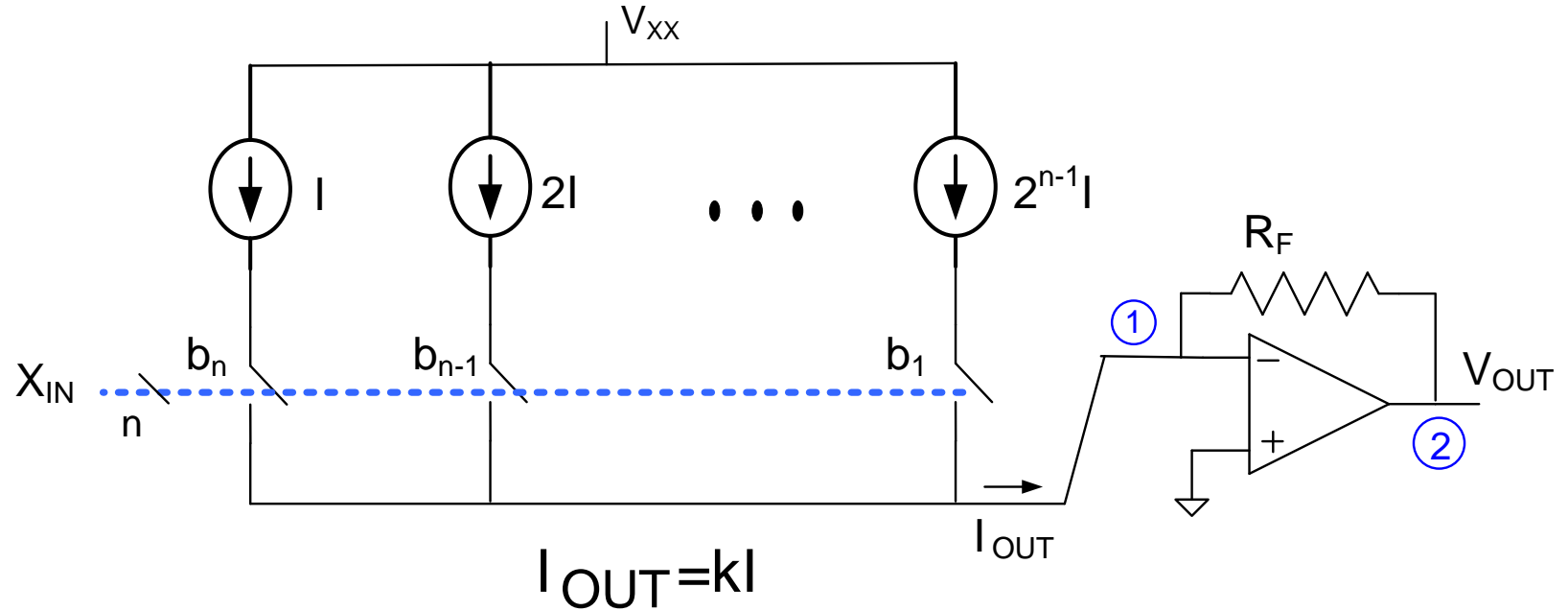


# EE 505


## Lecture 18

Dynamic Current Source Matching  
Charge Redistribution DACs

# Current Steering DAC



## Sub-radix Array

 

Typically  $2.1 < \theta < 2.5$


Termination resistor must be selected so that same attenuation is maintained

Often only the first  $n_1$  MSB “slices” will be sub-radix



Effective number of bits when using sub-radix array will be less than  $k$

Can be calibrated to obtain very low DNL (and maybe INL) with small area


# Current Steering DAC

 

# Current Steering DAC

  
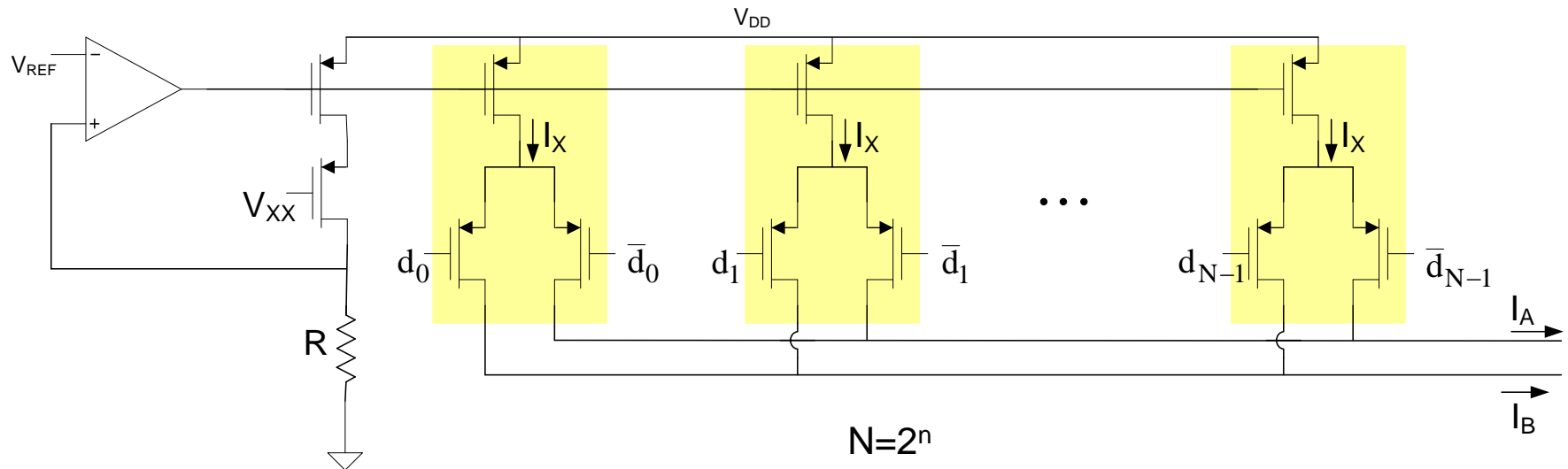
# Current Steering DAC with Supply Independent Biasing




If transistors on top row are all matched,  $I_X = V_{REF}/R$

Thermometer coded structure (requires binary to thermometer decoder)

$$I_A = \left( \frac{V_{REF}}{R} \right) \sum_{i=0}^{N-1} d_i$$

Provides Differential Output Currents
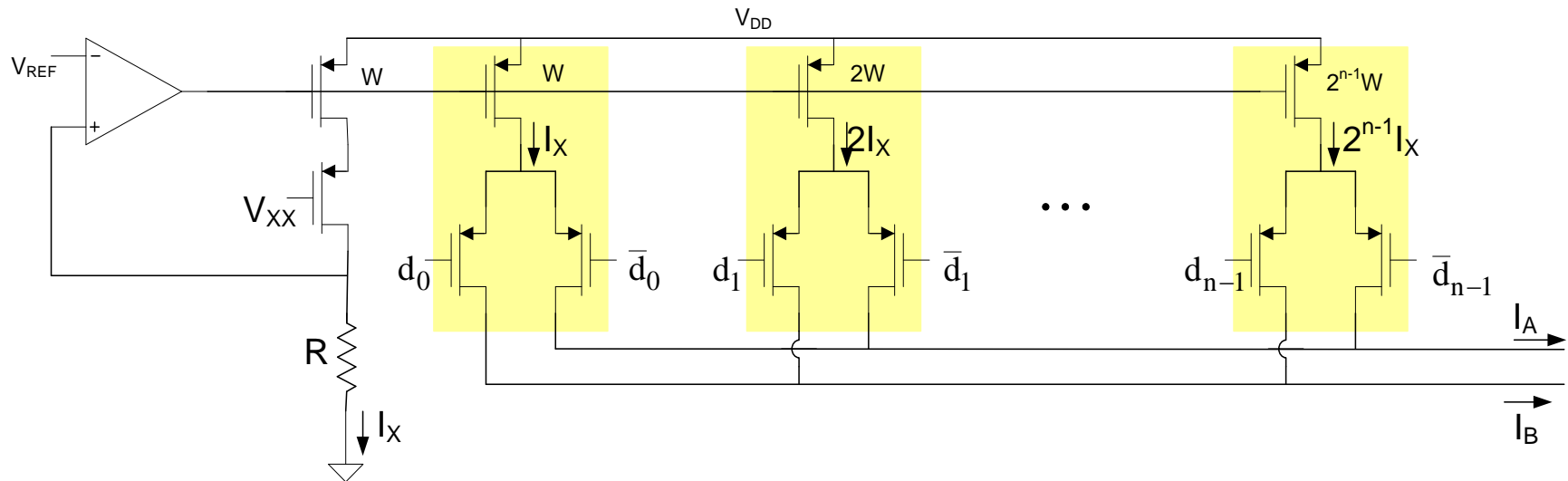
# Current Current Steering DAC with Supply Independent Biasing




If transistors on top row are binary weighted

$$I_A = \left( \frac{V_{REF}}{R} \right) \sum_{i=0}^{n-1} \frac{d_i}{2^{n-i}}$$


Provides Differential Output Currents
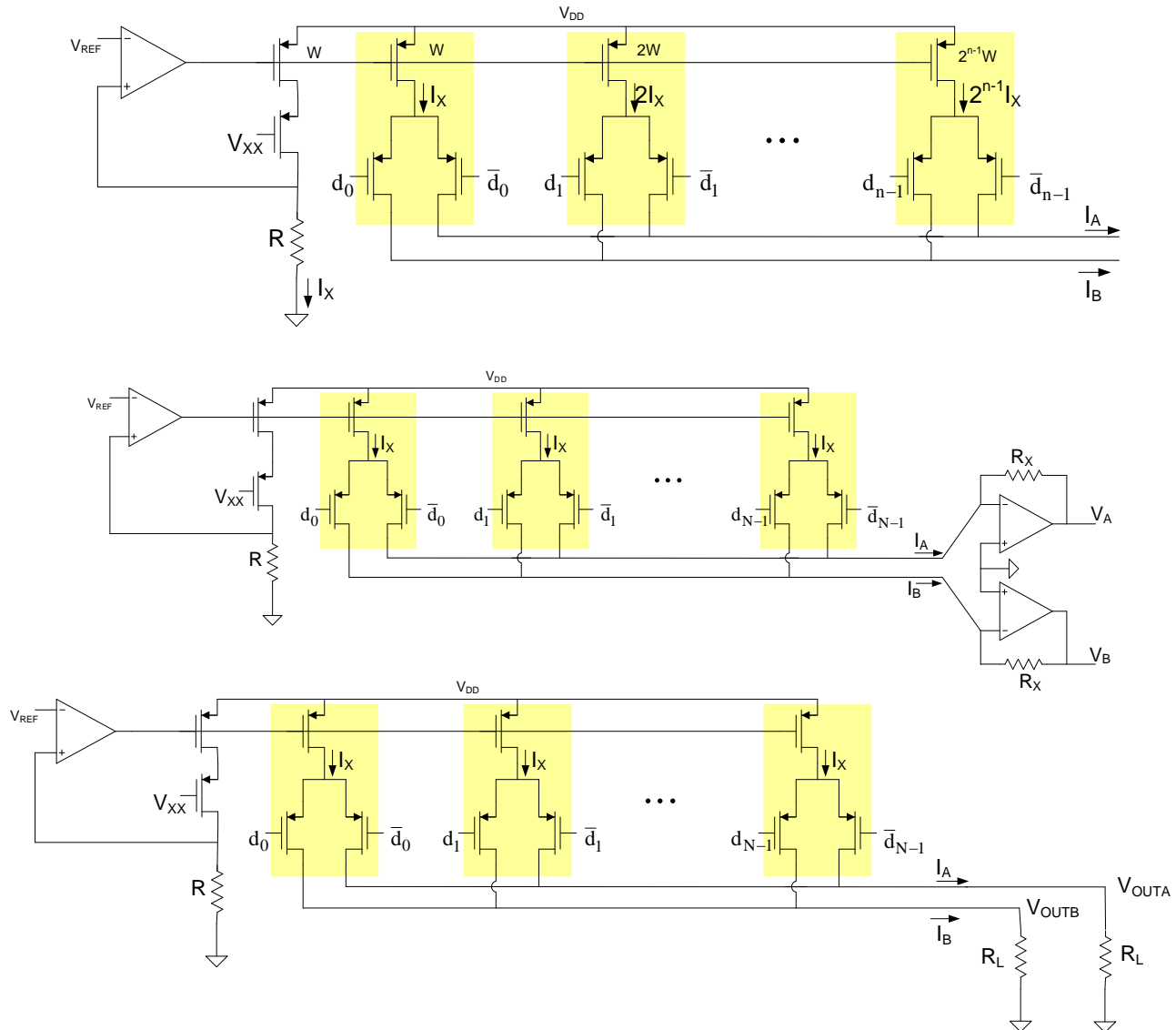
# Current Steering DAC with current output, buffered output, resistor load





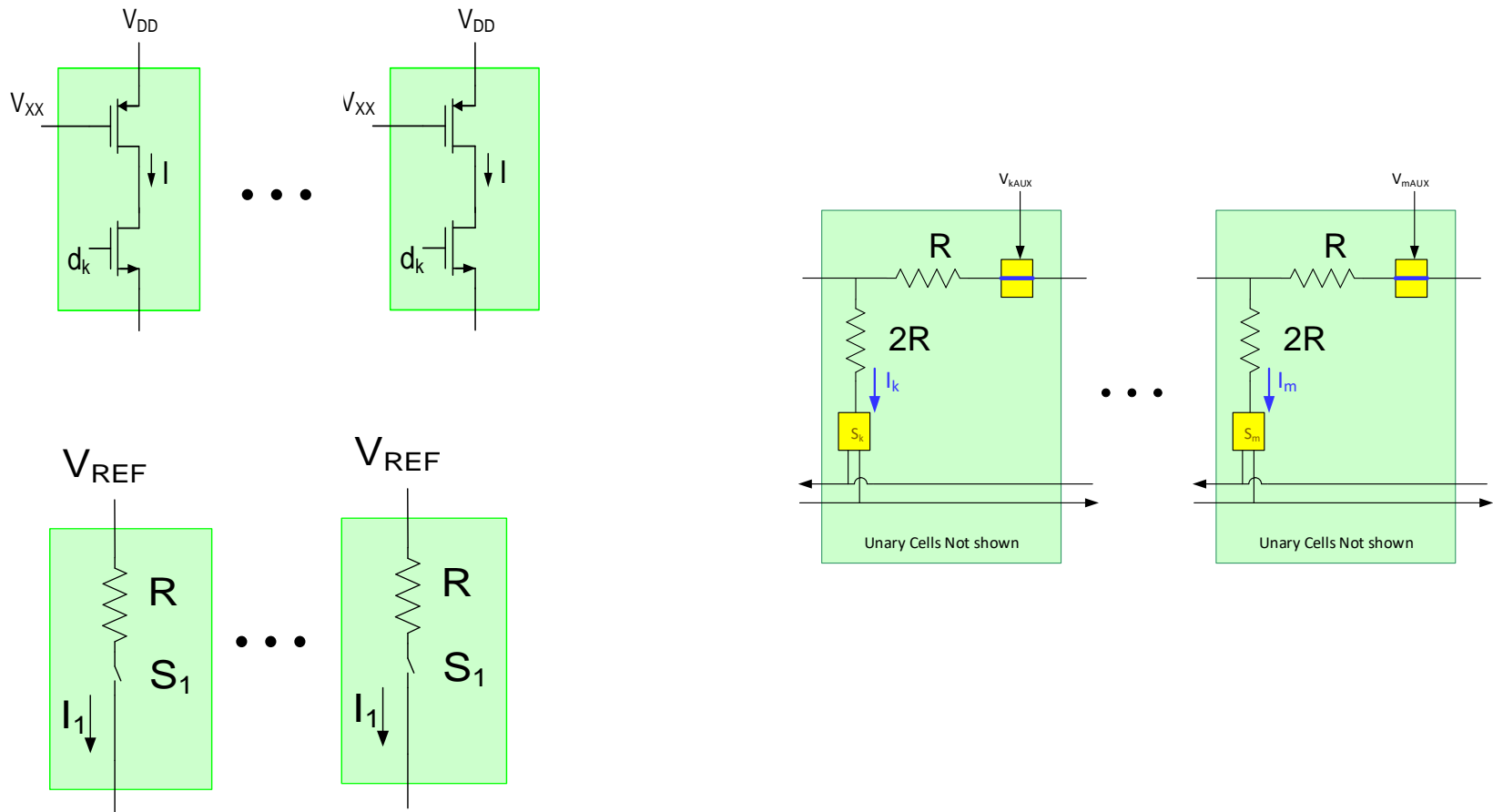
# Matching is Critical in all DAC Considered



Obtaining adequate matching remains one of the major challenges facing the designer!


# Dynamic Current Source Matching

 

- Correct charge is stored on  $C$  to make all currents equal to  $I_{REF}$
- Does not require matching of transistors or capacitors
- Requires refreshing to keep charge on  $C$
- Form of self-calibration
- Calibrates current sources one at a time
- Current source unavailable for use while calibrating
- Can be directly used in DACs (thermometer or binary coded)
- Still use steering rather than switching in DAC


Often termed “Current Copier” or “Current Replication” circuit

# Dynamic Current Source Matching

 

Extra current source can be added to facilitate background calibration

# Charge Redistribution Principle

 

$$\sum_{i=1}^k C_i (V_i - V_X) = Q_X$$


Charge on capacitors is preserved if there is no loss element on any of the capacitors

$$\sum_{i=1}^k C_i V_i - V_X \sum_{i=1}^k C_i = Q_X$$

Thus for any time-dependent voltages  $V_1, \dots, V_k$

$$V_X = \frac{\sum_{i=1}^k C_i V_i - Q_X}{\sum_{i=1}^k C_i}$$

# Charge Redistribution Principle

 


$$V_X = \frac{\sum_{i=1}^k C_i V_i - Q_X}{\sum_{i=1}^k C_i}$$

All capacitors will have some gradual leakage thus causing  $Q_T$  to change

How long will charge on a simple M-SiO<sub>2</sub>-M capacitor be retained in a standard semiconductor process?


Decades !

 

# DAC Architectures



## Charge Redistribution

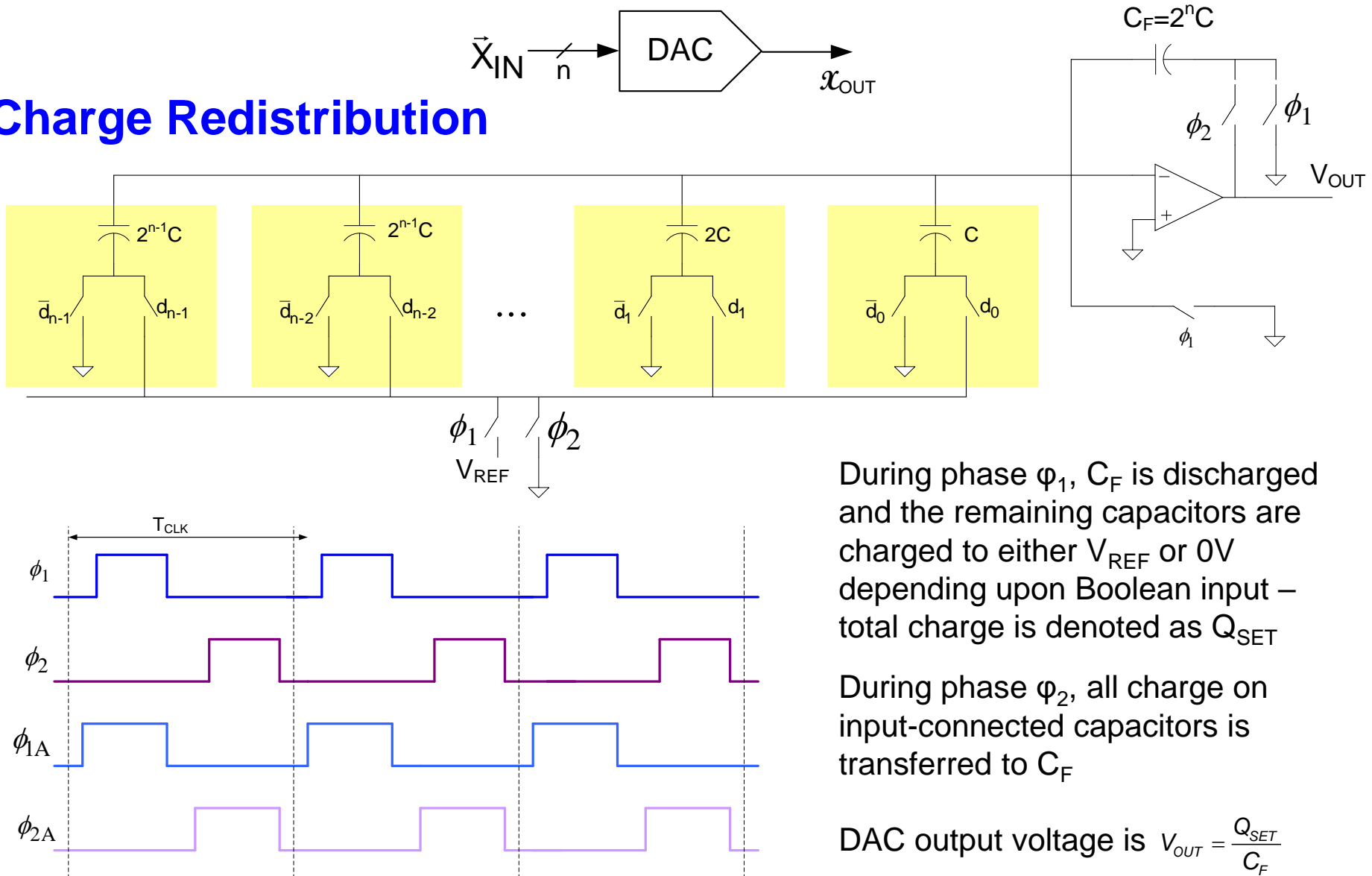

During phase  $\phi_1$ ,  $C_F$  is discharged and the remaining capacitors are charged to either  $V_{REF}$  or  $0V$  depending upon Boolean input – total charge is denoted as  $Q_{SET}$



During phase  $\phi_2$ , all charge on input-connected capacitors is transferred to  $C_F$

DAC output voltage is  $V_{OUT} = \frac{Q_{SET}}{C_F}$

# DAC Architectures



## Charge Redistribution

 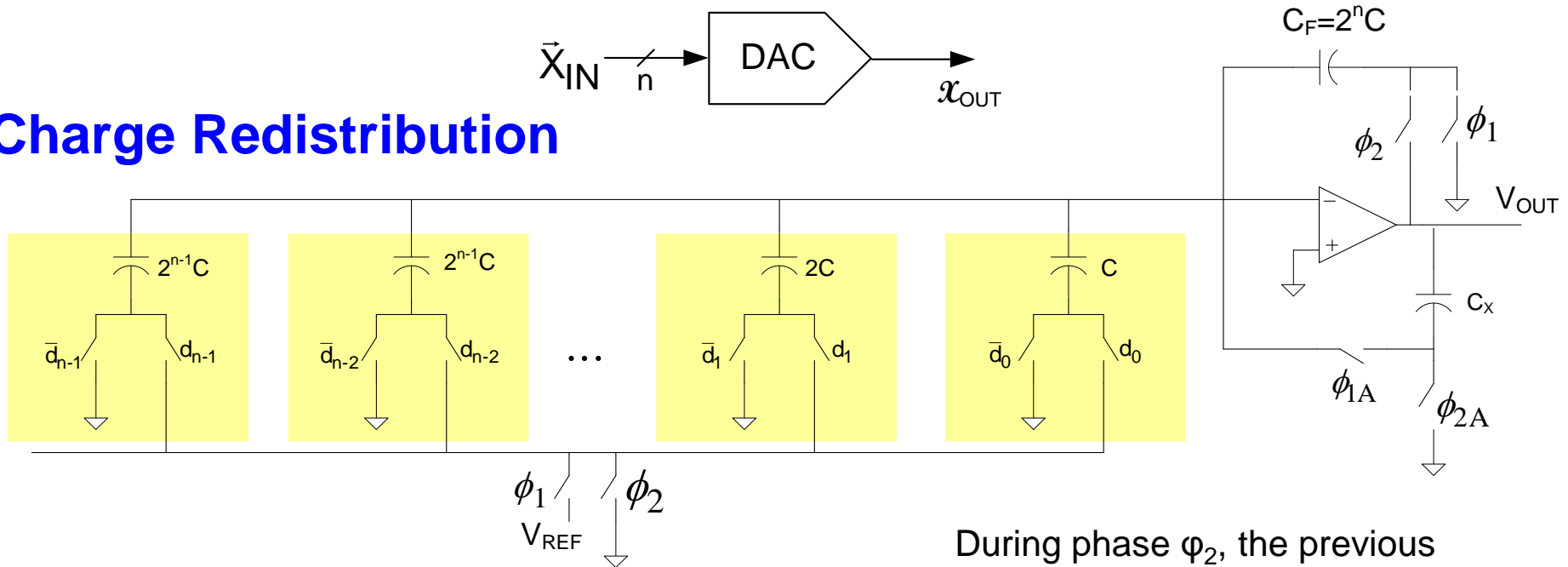


During phase  $\phi_2$ , the previous output voltage is sampled on  $C_X$

During phase  $\phi_1$ , the Op Amp has feedback through  $C_X$  thus establishing a null-port at the input so voltage on selected sampling capacitors is  $V_{REF}$

$C_X$  does some good things (mitigates  $V_{OS}$ ,  $1/f$  noise and finite gain errors)


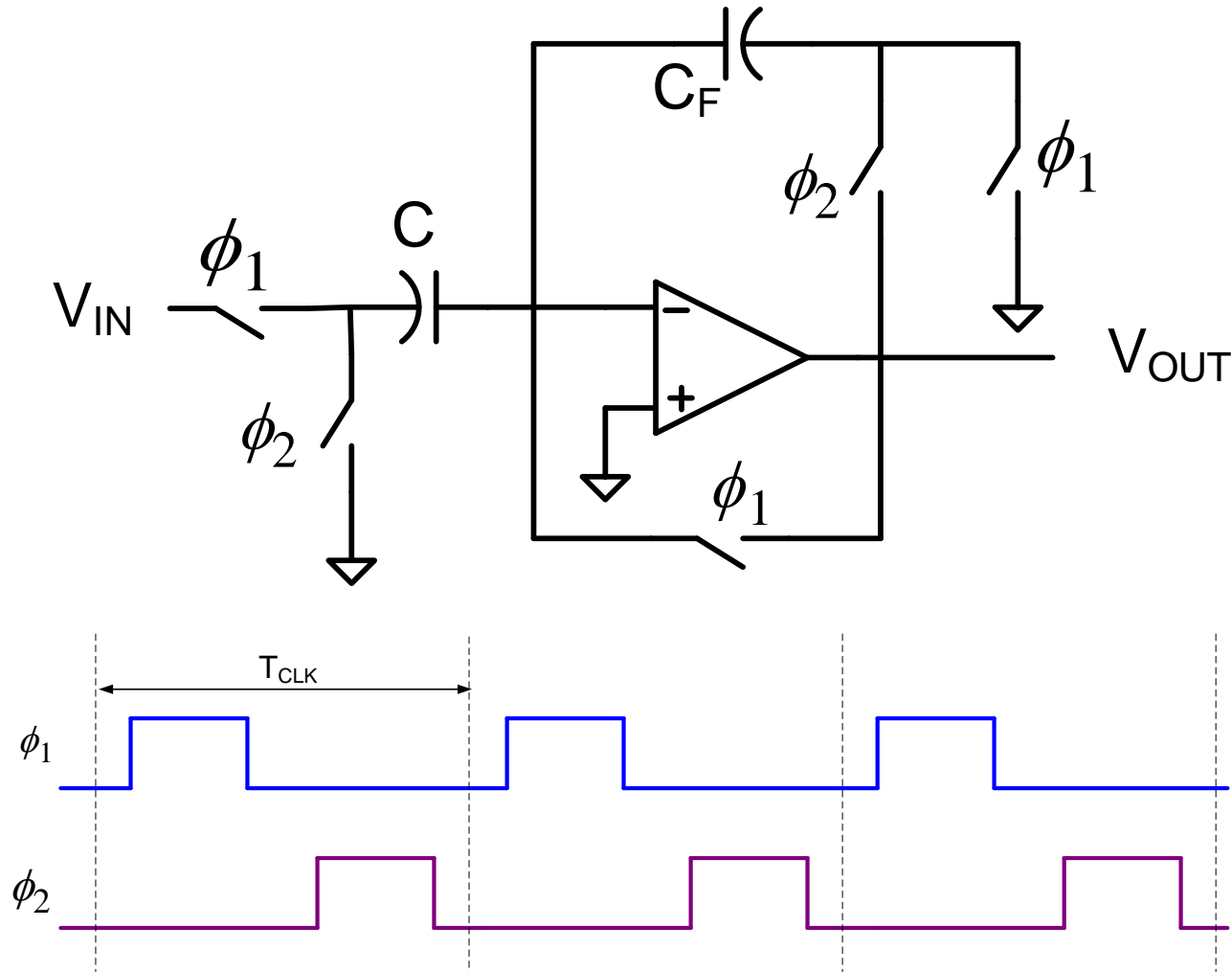
# Consider basic charge redistribution circuit



Clocks are complimentary non-overlapping



# Basic charge redistribution circuit

 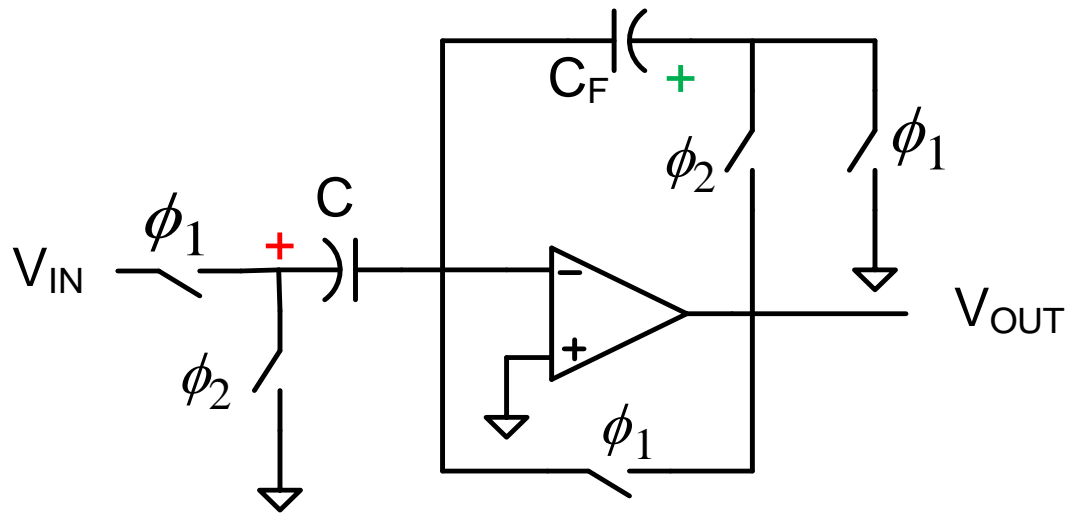

During phase  $\phi_1$

$$Q_{\phi_1} = CV_{IN}$$

$$Q_{CF} = 0$$

During phase  $\phi_2$



$$\frac{Q_{\phi_1}}{C_F} = V_{OUT}$$

$$\frac{CV_{IN}}{C_F} = V_{OUT}$$

$$\frac{V_{OUT}}{V_{IN}} = \frac{C}{C_F}$$

Serves as a noninverting amplifier  
Gain can be very accurate  
Output valid only during  $\Phi_2$

# Another charge redistribution circuit

 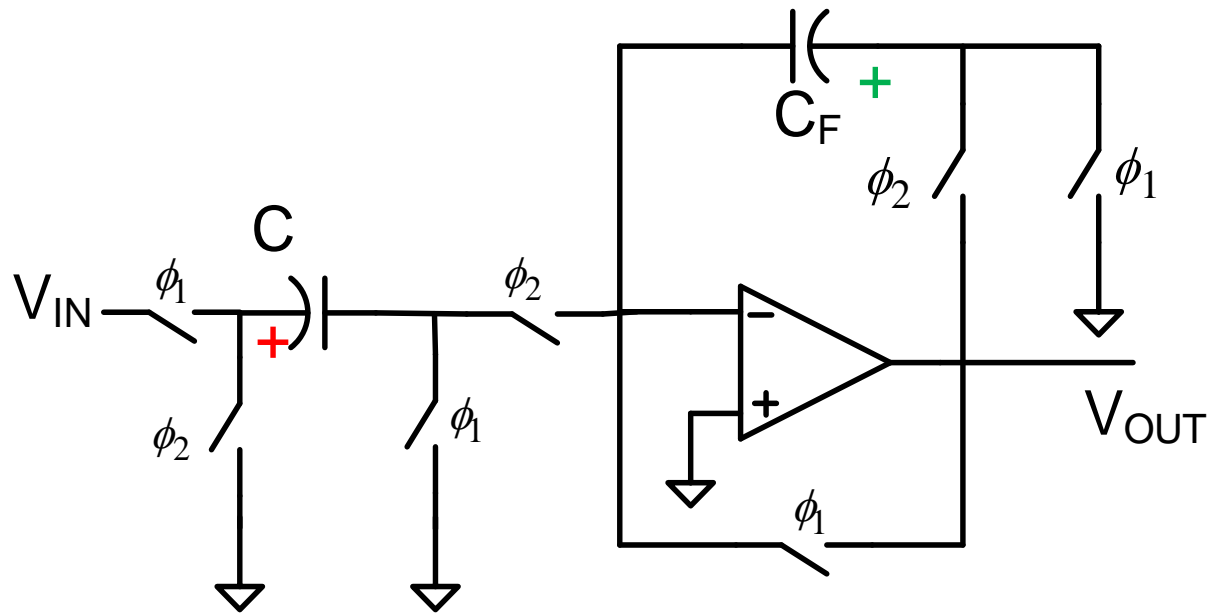

# Another charge redistribution circuit

During phase  $\phi_1$

$$Q_{\phi_1} = CV_{IN}$$

$$Q_{CF} = 0$$



During phase  $\phi_2$

$$\frac{-Q_{\phi_1}}{C_F} = V_{OUT}$$



$$\frac{-CV_{IN}}{C_F} = V_{OUT}$$

$$\frac{V_{OUT}}{V_{IN}} = -\frac{C}{C_F}$$

 
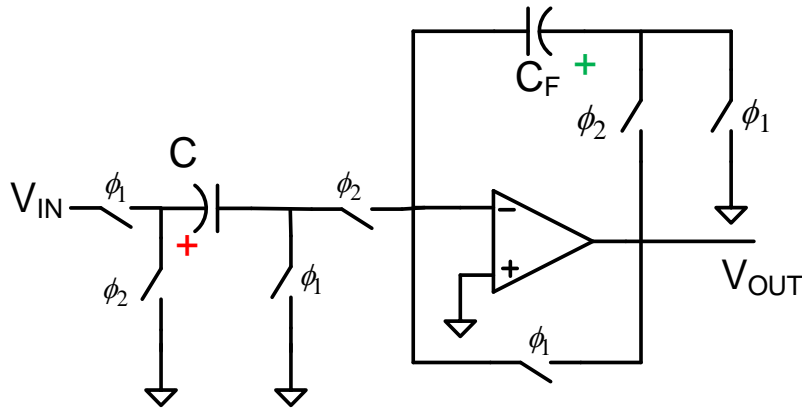
Serves as a noninverting amplifier  
Gain can be very accurate  
Output valid only during  $\Phi_2$



# Another charge redistribution circuit

 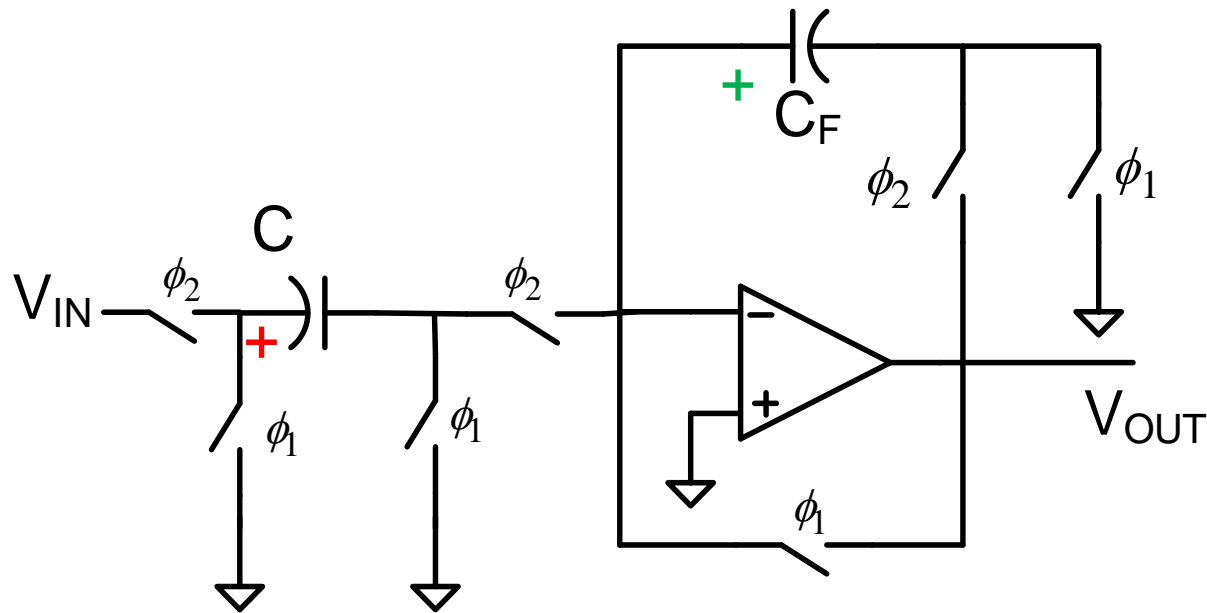

# Another charge redistribution circuit

 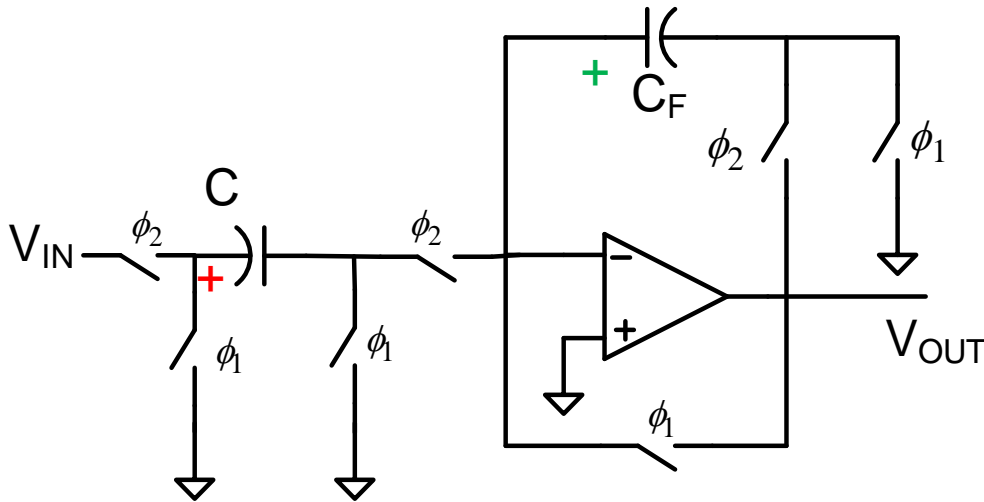

$$\frac{-Q_{\phi 1}}{C_F} = V_{OUT}$$

During phase  $\phi_1$

$$Q_{\phi 1} = 0$$

$$Q_{CF} = 0$$

During phase  $\phi_2$

$$Q_{\phi 2} = CV_{IN}$$


$$Q_{CF} = C_F V_{OUT}$$

$$Q_{CF} = -Q_{\phi 1}$$

$$\frac{V_{OUT}}{V_{IN}} = -\frac{C}{C_F}$$

Serves as an inverting amplifier  
Gain can be very accurate  
Output valid only during  $\phi_2$

# Charge Redistribution DAC

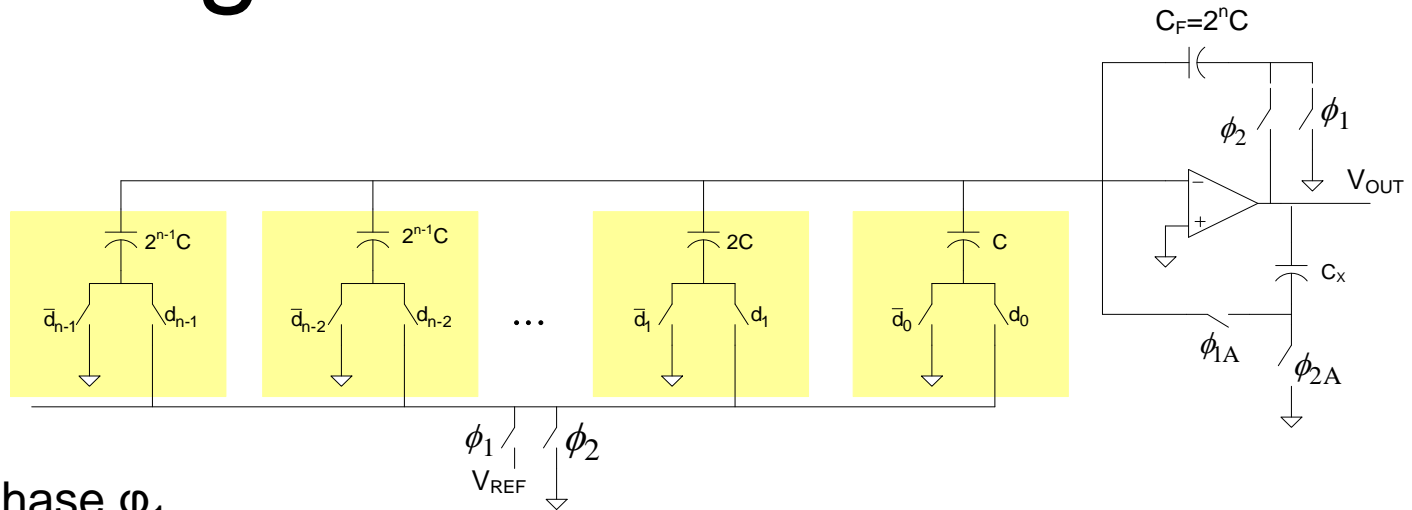

During phase  $\phi_1$

$$Q_{SET} = V_{REF} \sum_{i=0}^{n-1} d_i 2^i C$$


During phase  $\phi_2$

Charge  $Q_{SET}$  is all transferred to  $C_F$


$$Q_{CF} = V_{OUT} 2^n C$$

but  $Q_{SET} = Q_{CF}$
 
$$V_{REF} \sum_{i=0}^{n-1} d_i 2^i C = V_{OUT} 2^n C \longrightarrow V_{OUT} = V_{REF} \sum_{i=0}^{n-1} \frac{d_i}{2^{n-i}}$$



# Another Redistribution DAC

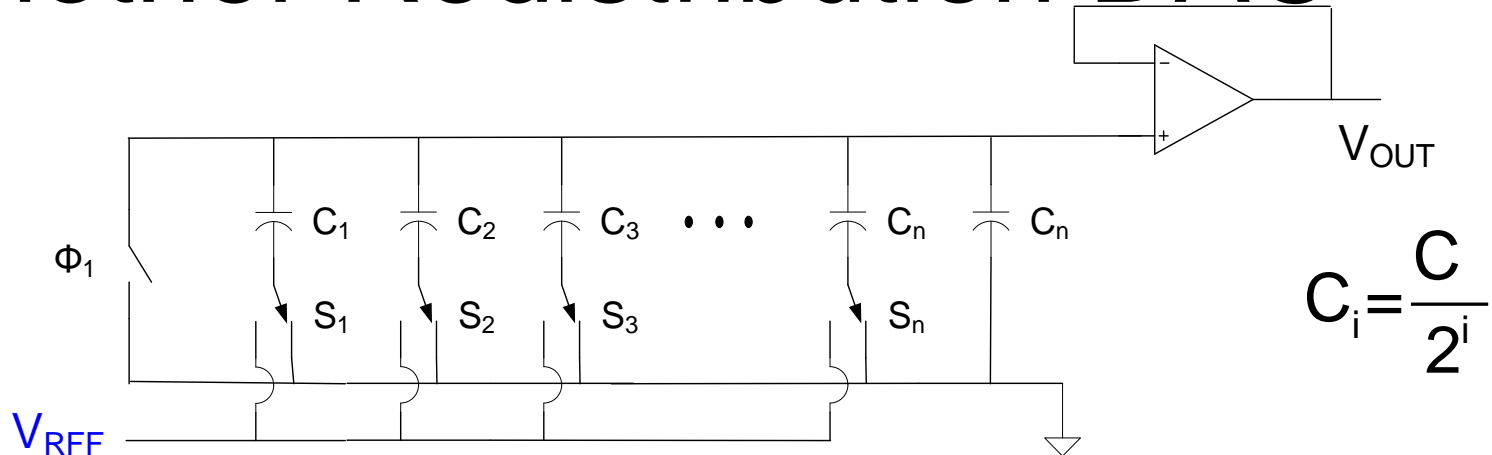

During phase  $\phi_1$  selected switches set to  $V_{REF}$   $Q_{SET} = V_{REF} \sum_{i=0}^n d_i C_i = V_{REF} \sum_{i=0}^n d_i \frac{C}{2^{n-i}}$

During phase  $\phi_2$  all switches connected to GND

Charge  $Q_{SET}$  is all redistributed among the capacitors


$$Q_{SET} = V_{OUT} \left( \sum_{i=1}^n C_i + C_n \right)$$

but

$$\sum_{i=1}^n C_i + C_n = \left( \sum_{i=1}^n \frac{C}{2^i} + C_n \right) = C$$




$$Q_{SET} = V_{OUT} C$$
 
$$V_{REF} \sum_{i=0}^{n-1} d_i \frac{C}{2^{n-i}} = V_{OUT} C \quad \longrightarrow \quad V_{OUT} = V_{REF} \sum_{i=0}^{n-1} \frac{d_i}{2^{n-i}}$$


 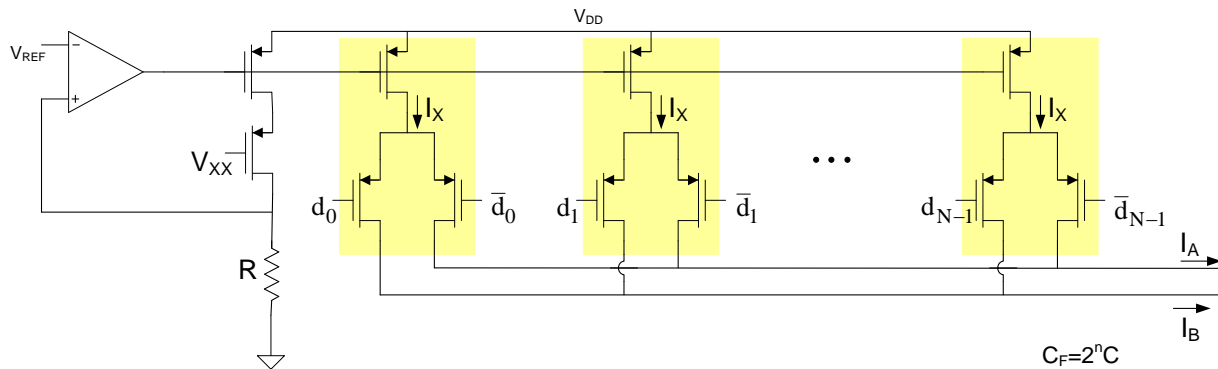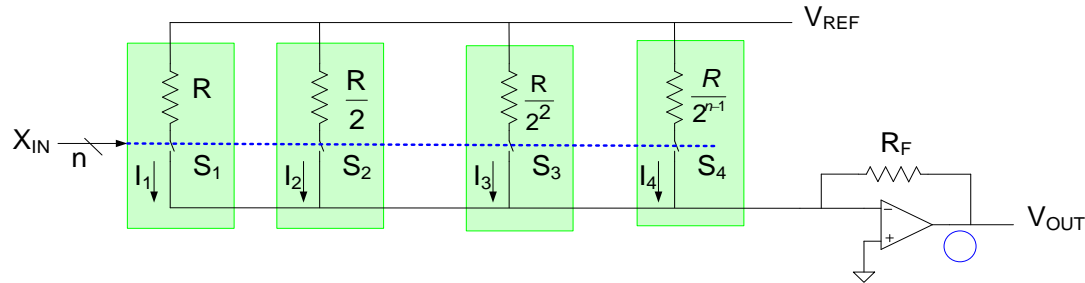
# Noise in DACs

Resistors and transistors contribute device noise but  
what about charge redistribution DACs ?






# Noise in DACs

Resistors and transistors contribute device noise but  
what about charge redistribution DACs ?

Noise in resistors:

 

Noise spectral density of  $v_n(t)$  at all frequencies  $S = 4kTR$

This is white noise !

k: Boltzmann's Constant

T: Temperature in Kelvin


$$k = 1.38064852 \times 10^{-23} \text{ m}^2 \text{ kg s}^{-2} \text{ K}^{-1}$$

$$\text{At } 300\text{K}, kT = 4.14 \times 10^{-21}$$

# Noise in DACs

Resistors and transistors contribute device noise but  
what about charge redistribution DACs ?

Noise in linear circuits:

 


Due to any noise voltage source:

$$S_{V_{OUT}} = S_{V_n} |T(j\omega)|^2$$

$$v_{OUT_{RMS}} = \sqrt{\int_{f=0}^{\infty} S_{V_{OUT}} df} = \sqrt{\int_{f=0}^{\infty} S_{V_n} |T(j\omega)|^2 df}$$

## Example: First-Order RC Network

 


$$T(s) = \frac{1}{1+RCs}$$

$$S_{VOUT} = 4kTR \left( \frac{1}{1+(RC\omega)^2} \right)$$

$$v_{n_{RMS}} = \sqrt{\int_{f=0}^{\infty} S_{VOUT} df} = \sqrt{\int_{f=0}^{\infty} \frac{4kTR}{1+\omega^2 R^2 C^2} df}$$

## Example: First-Order RC Network

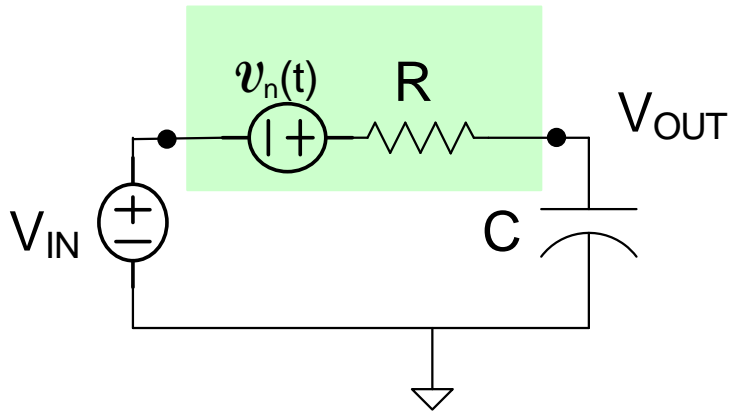


$$v_{n_{RMS}} = \sqrt{\int_{f=0}^{\infty} S_{V_{OUT}} df} = \sqrt{\int_{f=0}^{\infty} \frac{4kTR}{1 + \omega^2 R^2 C^2} df}$$

From a standard change of variable with a trig identity, it follows that


$$v_{n_{RMS}} = \sqrt{\int_{f=0}^{\infty} S_{V_{OUT}} df} = \sqrt{\frac{kT}{C}}$$

- The continuous-time noise voltage has an RMS value that is independent of  $R$
- Noise contributed by the resistor is dependent only upon the capacitor value  $C$
- This is often referred to as  $kT/C$  noise and it can be decreased at a given  $T$  only by increasing  $C$



**"kT/C" Noise at T=300K**

 


**"kT/C" Noise at T=300K**

 

## Example: Switched Capacitor Sampler

 
 


Track mode

 


Hold mode

## Example: Switched Capacitor Sampler

  



Track mode

 

Hold mode

## Example: Switched Capacitor Sampler


$T$  is the period of the sampler

  

$v_n(mT)$  is a discrete-time sequence obtained by sampling continuous-time noise waveform



## Characterization of a noise sequence



 


$$\hat{v}_{\text{RMS}} = E \left( \sqrt{\lim_{N \rightarrow \infty} \left( \frac{1}{N} \sum_{m=1}^N v^2(mT) \right)} \right) \underset{N \text{ large}}{\approx} \sqrt{\frac{1}{N} \sum_{m=1}^N v^2(mT)}$$


**Theorem** If  $\mathcal{V}(t)$  is a continuous-time zero-mean noise source and  $\langle \mathcal{V}(kT) \rangle$  is a sampled version of  $\mathcal{V}(t)$  sampled at times  $T, 2T, \dots$  then the RMS value of the continuous-time waveform is the same as that of the sampled version of the waveform. This can be expressed as  $\mathcal{V}_{\text{RMS}} = \hat{\mathcal{V}}_{\text{RMS}}$

**Theorem** If  $\mathcal{V}(t)$  is a continuous-time zero-mean noise signal and  $\langle \mathcal{V}(kT) \rangle$  is a sampled version of  $\mathcal{V}(t)$  sampled at times  $T, 2T, \dots$  then the standard deviation of the random variable  $\mathcal{V}(kT)$ , denoted as  $\sigma_{\hat{\mathcal{V}}}$  satisfies the expression  $\sigma_{\hat{\mathcal{V}}} = \mathcal{V}_{\text{RMS}} = \hat{\mathcal{V}}_{\text{RMS}}$

# Example: Switched Capacitor Sampler

   

Track mode

 

Hold mode

$$v_{n_{RMS}} = \sqrt{\frac{kT}{C}}$$

k: Boltzmann's constant  
T: temperature in Kelvin

**End of Lecture 18**