 


EE 505

Lecture 18

Architectural Performance Comparisons
ADC Design


Dynamic Current Source Matching




- Correct charge is stored on C to make all currents equal to I_{REF}
- Does not require matching of transistors or capacitors
- Requires refreshing to keep charge on C
- Form of self-calibration
- Calibrates current sources one at a time
- Current source unavailable for use while calibrating
- Can be directly used in DACs (thermometer or binary coded)
- Still use steering rather than switching in DAC

Often termed “Current Copier” or “Current Replication” circuit


Floating Current Source

 

Floating Current Copier

 

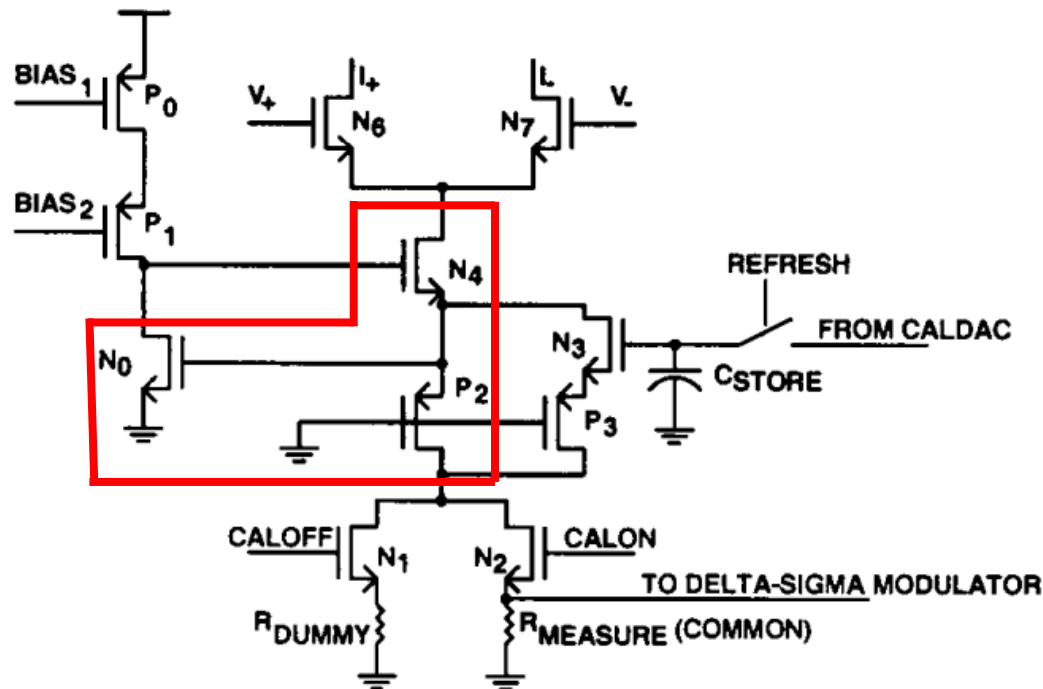Another Dynamic Current Source Matching Structure




Floating Current Source

Voltage Copier

Eliminates need to remove current source from circuit during cal

Noise in DACs

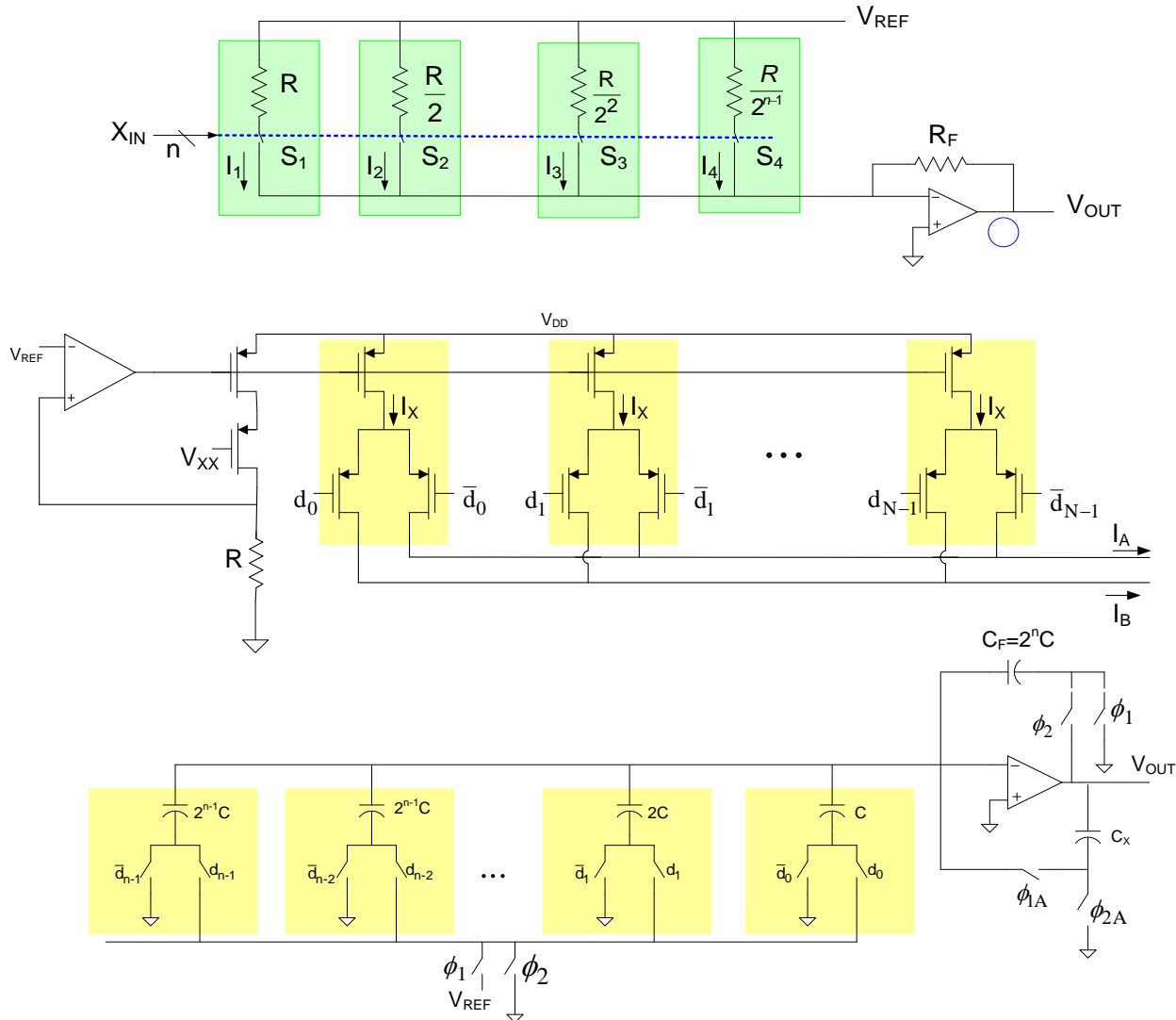
Resistors and transistors contribute device noise but
what about charge redistribution DACs ?



Noise in DACs

Resistors and transistors contribute device noise but
what about charge redistribution DACs ?

Noise in resistors:

 

Noise spectral density of $v_n(t)$ at all frequencies $S = 4kTR$

This is white noise !

k: Boltzmann's Constant

T: Temperature in Kelvin


$$k = 1.38064852 \times 10^{-23} \text{ m}^2 \text{ kg s}^{-2} \text{ K}^{-1}$$

$$\text{At } 300\text{K}, kT = 4.14 \times 10^{-21}$$

Noise in DACs

Resistors and transistors contribute device noise but
what about charge redistribution DACs ?

Noise in linear circuits:

 


Due to any noise voltage source:

$$S_{V_{OUT}} = S_{V_n} |T(j\omega)|^2$$

$$v_{OUT_{RMS}} = \sqrt{\int_{f=0}^{\infty} S_{V_{OUT}} df} = \sqrt{\int_{f=0}^{\infty} S_{V_n} |T(j\omega)|^2 df}$$

Example: First-Order RC Network

 

$$T(s) = \frac{1}{1+RCs}$$

$$S_{VOUT} = 4kTR \left(\frac{1}{1+(RC\omega)^2} \right)$$

$$v_{n_{RMS}} = \sqrt{\int_{f=0}^{\infty} S_{VOUT} df} = \sqrt{\int_{f=0}^{\infty} \frac{4kTR}{1+\omega^2 R^2 C^2} df}$$

Useful Trig Identity:


$$v_{n_{RMS}} = \sqrt{\int_{f=0}^{\infty} S_{V_{OUT}} df} = \sqrt{\int_{f=0}^{\infty} \frac{4kTR}{1 + \omega^2 R^2 C^2} df} = \sqrt{\frac{4kT}{RC^2} \int_{f=0}^{\infty} \frac{1}{\left(\frac{1}{RC}\right)^2 + \omega^2} df}$$

$$\int_{x=0}^{\infty} \frac{1}{a^2 + x^2} dx = \frac{\pi}{2a}$$

If $\omega = 2\pi f$ this can be rewritten as

$$\int_{f=0}^{\infty} \frac{1}{b^2 + \omega^2} df = \frac{1}{4b}$$

Example: First-Order RC Network

 


$$v_{n_{RMS}} = \sqrt{\int_{f=0}^{\infty} S_{V_{OUT}} df} = \sqrt{\int_{f=0}^{\infty} \frac{4kTR}{1 + \omega^2 R^2 C^2} df}$$

From a standard change of variable with a trig identity, it follows that


$$v_{n_{RMS}} = \sqrt{\int_{f=0}^{\infty} S_{V_{OUT}} df} = \sqrt{\frac{kT}{C}}$$

- The continuous-time noise voltage has an RMS value that is independent of R
- Noise contributed by the resistor is dependent only upon the capacitor value C
- This is often referred to as kT/C noise and it can be decreased at a given T only by increasing C



"kT/C" Noise at T=300K

 


"kT/C" Noise at T=300K

 

Example: Switched Capacitor Sampler

 
 


Track mode

 


Hold mode

Example: Switched Capacitor Sampler

  



Track mode

 

Hold mode


Example: Switched Capacitor Sampler

T is the period of the sampler

  

$v_n(mT)$ is a discrete-time sequence obtained by sampling continuous-time noise waveform

Characterization of a noise sequence

 


$$\hat{v}_{\text{RMS}} = E \left(\sqrt{\lim_{N \rightarrow \infty} \left(\frac{1}{N} \sum_{m=1}^N v^2(mT) \right)} \right) \underset{N \text{ large}}{\approx} \sqrt{\frac{1}{N} \sum_{m=1}^N v^2(mT)}$$

Theorem If $\mathcal{V}(t)$ is a continuous-time zero-mean noise source and $\langle \mathcal{V}(kT) \rangle$ is a sampled version of $\mathcal{V}(t)$ sampled at times $T, 2T, \dots$ then the RMS value of the continuous-time waveform is the same as that of the sampled version of the waveform. This can be expressed as $\mathcal{V}_{\text{RMS}} = \hat{\mathcal{V}}_{\text{RMS}}$

Theorem If $\mathcal{V}(t)$ is a continuous-time zero-mean noise signal and $\langle \mathcal{V}(kT) \rangle$ is a sampled version of $\mathcal{V}(t)$ sampled at times $T, 2T, \dots$ then the standard deviation of the random variable $\mathcal{V}(kT)$, denoted as $\sigma_{\hat{\mathcal{V}}}$ satisfies the expression $\sigma_{\hat{\mathcal{V}}} = \mathcal{V}_{\text{RMS}} = \hat{\mathcal{V}}_{\text{RMS}}$

Example: Switched Capacitor Sampler

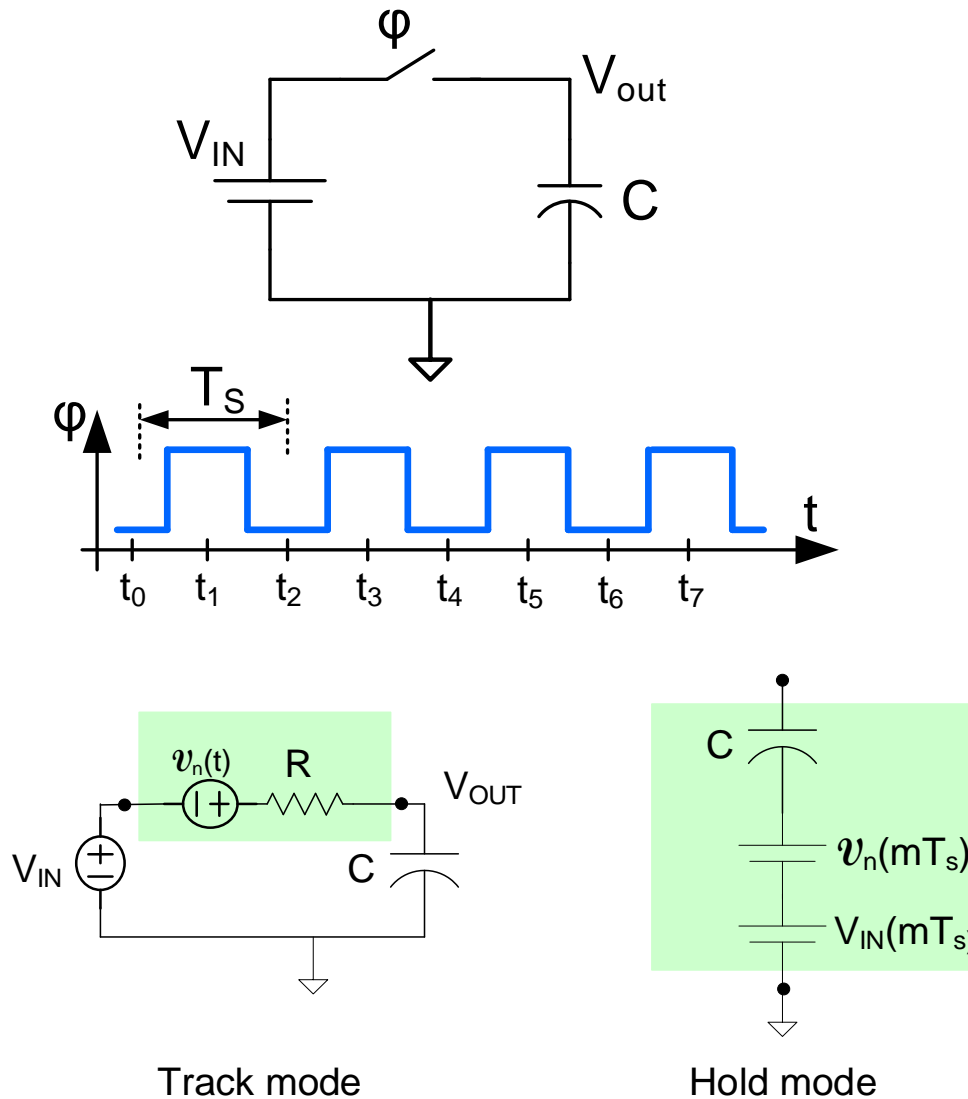


$$v_{n_{RMS}} = \sqrt{\frac{kT}{C}}$$


k : Boltzmann's constant
 T : temperature in Kelvin

Architectural Performance Characterizations

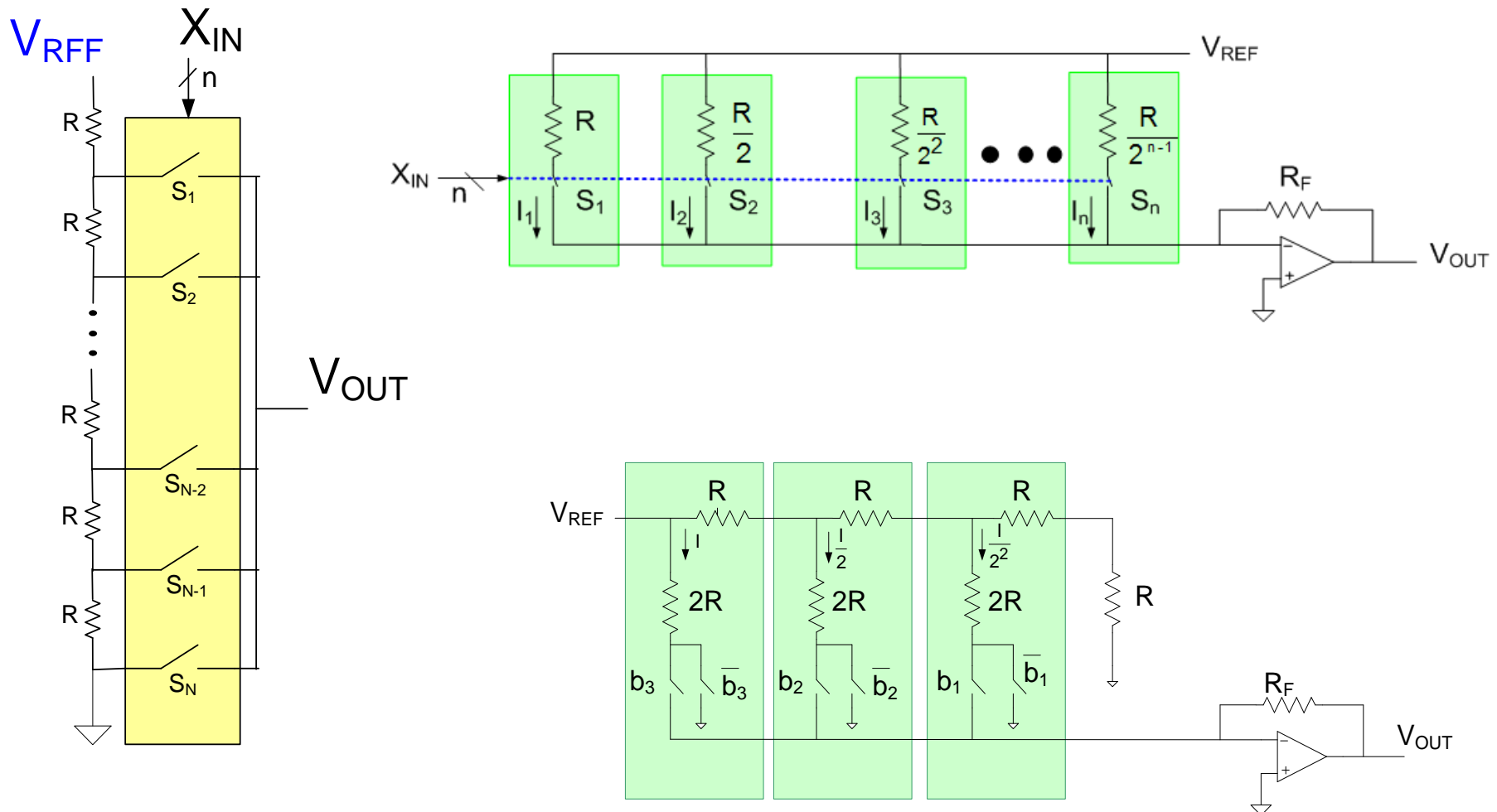For the same total resistor area and the same resolution, how do these structures compare from a statistical characterization viewpoint?



 Relative Statistical Characterization of R-based DACs



$$A = WL$$

$$\sigma_{\frac{R}{R_N}} = \frac{A_{pR}}{\sqrt{A}}$$

Relative Statistical Characterization of R-based DACs

For the same total area and the same resolution, how do these structures compare from a statistical characterization viewpoint?

Simulation environment:

Resolution = 10

$A_{pR} = 0.02\mu\text{m}$

Rnom = 1000

Area Unit Resistor = $2\mu\text{m}^2$






Resistor Sigma= 14.1421

INLtarget = 0.5000 LSB

Yield: Must meet INL target


Relative Statistical Characterization of R-based DACs

INL_k for four random implementations

     


Relative Statistical Characterization of R-based DACs

 INL histogram for 100,000 random implementations




String DAC

 


Relative Statistical Characterization of R-based DACs

 INL_{kMAX} histogram for 100,000 random implementations




String DAC

 


Relative Statistical Characterization of R-based DACs

 DNL histogram for 100,000 random implementations




String DAC

 

Relative Statistical Characterization of R-based DACs

Summary

 

String DAC

Resolution = 10

$A_{\rho R} = 0.02 \mu\text{m}$

$R_{\text{nom}} = 1000$

Area Unit Resistor = $2 \mu\text{m}^2$

Resistor Sigma = 14.1421

$\text{INL}_{\text{mean}} = 0.385 \text{ LSB}$

$\text{INL}_{\text{sigma}} = 0.118 \text{ LSB}$






$\text{DNL}_{\text{mean}} = 0.049 \text{ LSB}$

$\text{DNL}_{\text{sigma}} = 0.0047 \text{ LSB}$

Yield (%) = 84.0

Relative Statistical Characterization of R-based DACs



INL_k for four random implementations

     

Binary Weighted DAC

Relative Statistical Characterization of R-based DACs

 
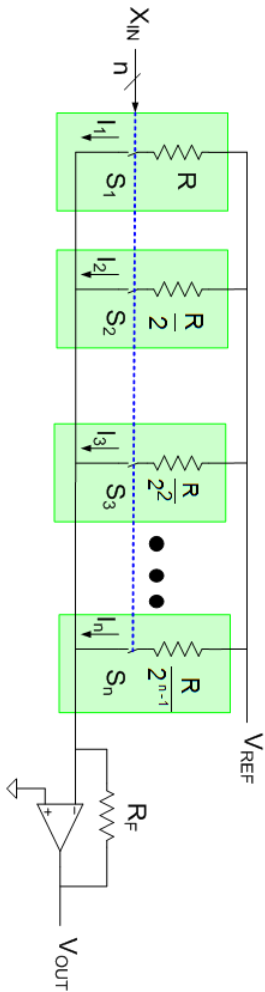
INL histogram for 100,000 random implementations



Binary Weighted DAC

Relative Statistical Characterization of R-based DACs

 
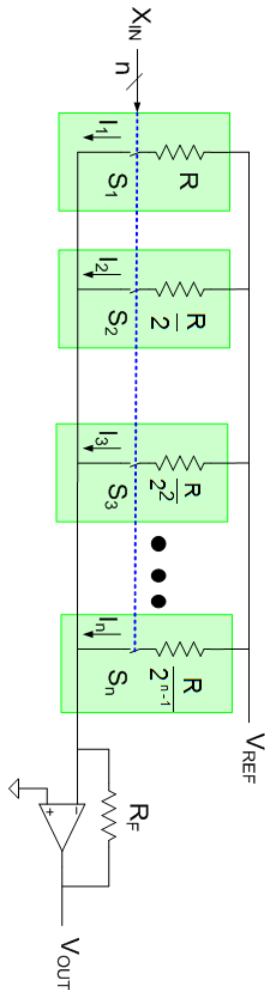
INL_{kMAX} histogram for 100,000 random implementations



Binary Weighted DAC

Relative Statistical Characterization of R-based DACs

  
DNL histogram for 100,000 random implementations



Binary Weighted DAC

Relative Statistical Characterization of R-based DACs

Summary

 

Binary Weighted DAC

Resolution = 10

$A_{pR} = 0.02\mu\text{m}$

$R_{\text{nom}} = 1000$

Area unit resistor = $2\mu\text{m}^2$

Resistor Sigma = 14.1421

$\text{INL}_{\text{mean}} = 0.367\text{LSB}$

$\text{INL}_{\text{sigma}} = 0.128\text{LSB}$

$\text{INL}_{\text{kmax_mean}} = 0.00013\text{LSB}$

$\text{INL}_{\text{kmax_sigma}} = 0.226\text{LSB}$

$\text{DNL}_{\text{mean}} = 0.470\text{LSB}$


$\text{DNL}_{\text{sigma}} = 0.228\text{LSB}$

$\text{INL}_{\text{target}} = 0.500\text{LSB}$


Yield (%) = 84.9

Relative Statistical Characterization of R-based DACs

Popular Area Allocation Strategies





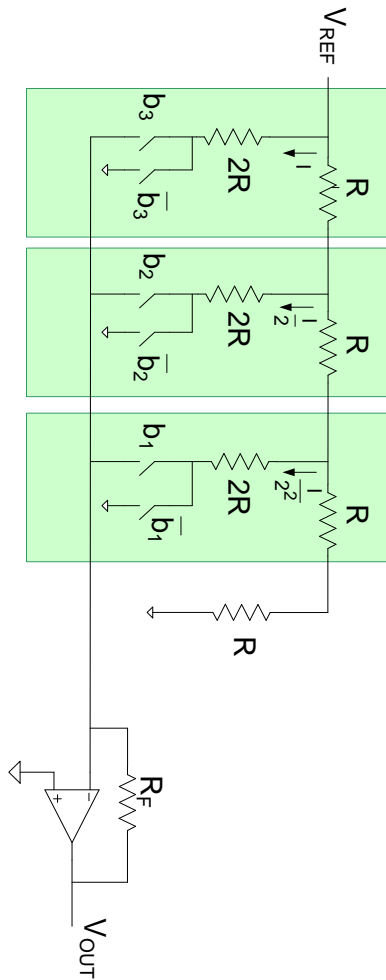


R-2R DAC

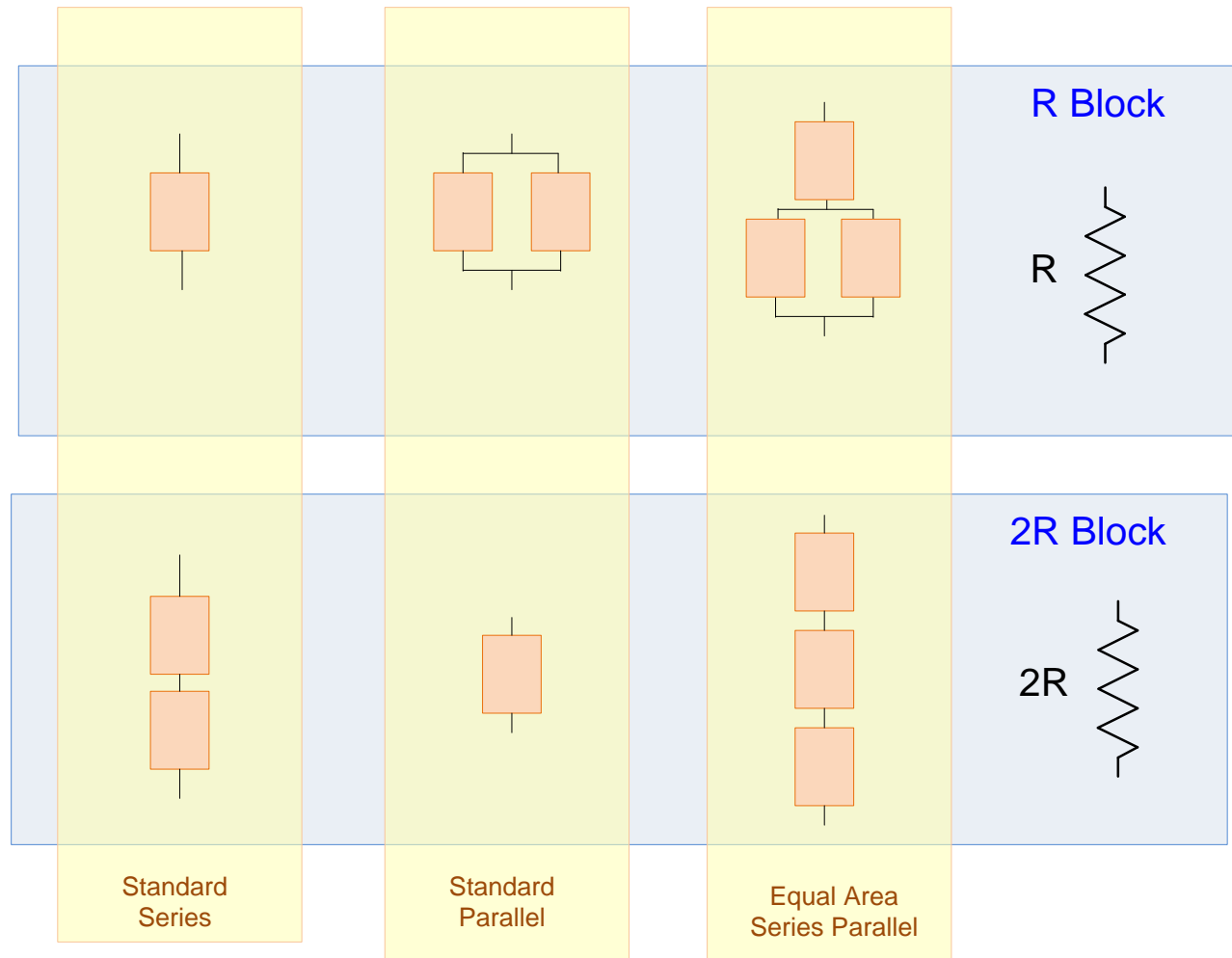

Relative Statistical Characterization of R-based DACs

    
 
INL_k for four random standard series implementations



R-2R DAC

Relative Statistical Characterization of R-based DACs

 
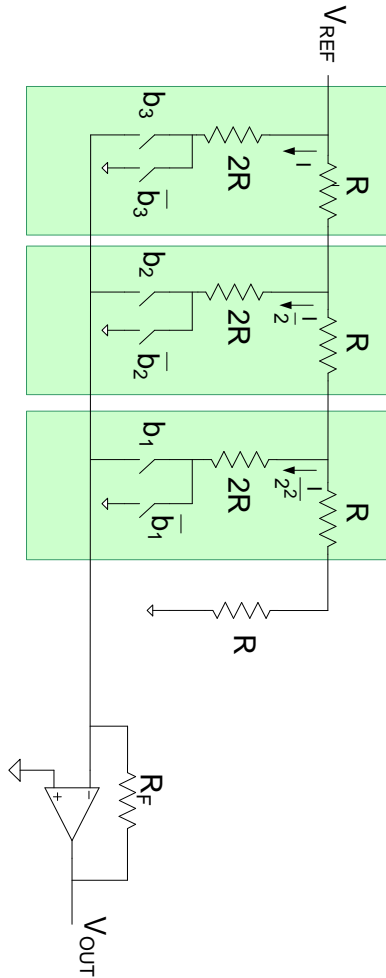
INL histogram for 15,000 random implementations Standard Series



R-2R DAC

Relative Statistical Characterization of R-based DACs

  
DNL histogram for 15,000 random implementations Standard Series



R-2R DAC

Relative Statistical Characterization of R-based DACs

Summary Standard Series

 

R-2R DAC

Resolution=10

$A_{pR} = 0.02 \mu\text{m}$

$R_{\text{nom}} = 1000$

Base Res Area(μm^2)=2

Res Sigma=14.1421

$\text{INL}_{\text{mean}} = 0.609 \text{ LSB}$

$\text{INL}_{\text{sigma}} = 0.295 \text{ LSB}$

$\text{DNL}_{\text{mean}} = 1.021 \text{ LSB}$

$\text{DNL}_{\text{sigma}} = 0.610 \text{ LSB}$

$\text{INL}_{\text{kmax_mean}} = 0.00017 \text{ LSB}$






$\text{INL}_{\text{kmax_sigma}} = 0.566 \text{ LSB}$

Yield INL Bound=0.5 LSB

Yield= 41.4%

Relative Statistical Characterization of R-based DACs

    
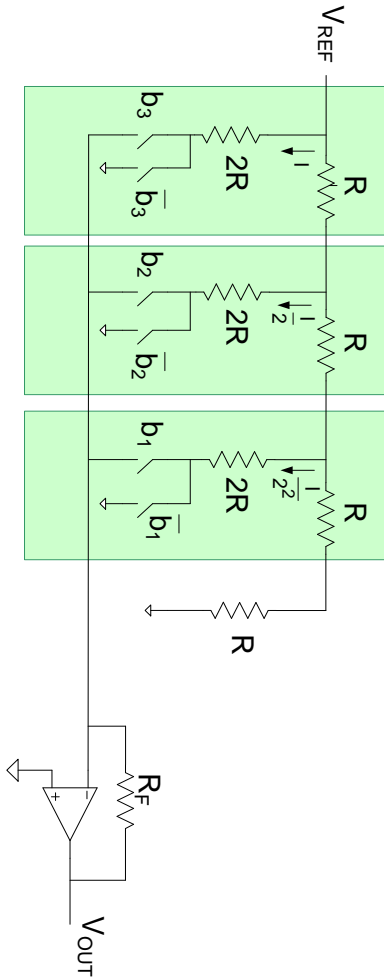
INL_k for four random standard parallel implementations



R-2R DAC

Relative Statistical Characterization of R-based DACs

 
 
INL histogram for 100,000 random implementations Standard Parallel



R-2R DAC

Relative Statistical Characterization of R-based DACs

 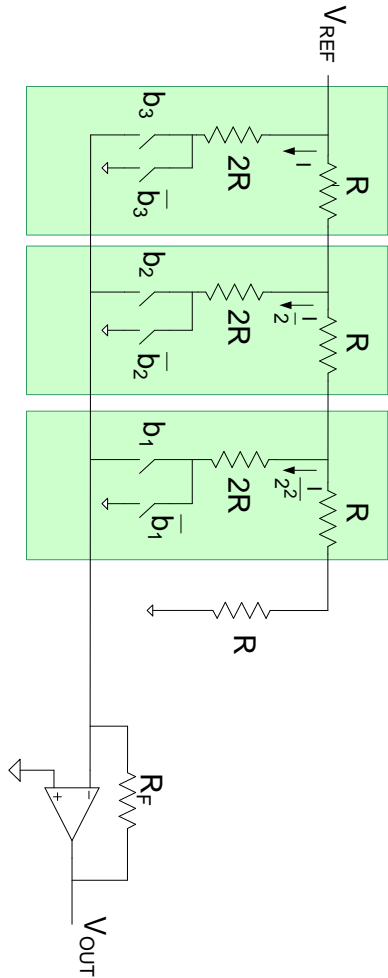
DNL histogram for 100,000 random implementations Standard Parallel



R-2R DAC

Relative Statistical Characterization of R-based DACs

Summary Standard Parallel

 

Resolution = 10

$A_{pR} = 0.02\mu\text{m}$

$R_{\text{nom}} = 1000$

Base Resistor Area(μm^2) = 2

Resistor Sigma = 14.1421

$\text{INL}_{\text{mean}} = 0.737 \text{ LSB}$

$\text{INL}_{\text{sigma}} = 0.357 \text{ LSB}$

$\text{INL}_{\text{kmax_mean}} = 0.0045 \text{ LSB}$

$\text{INL}_{\text{kmax_sigma}} = 0.680 \text{ LSB}$

$\text{DNL}_{\text{mean}} = 1.225 \text{ LSB}$

$\text{DNL}_{\text{sigma}} = 0.732 \text{ LSB}$

$\text{INL}_{\text{target}} = 0.5 \text{ LS}$

Yield = 28.5%

R-2R DAC


Why is the Standard Series yield significantly larger than the Standard Parallel?

Standard Parallel

Yield = 28.5%

Standard Series


Yield = 41.4%

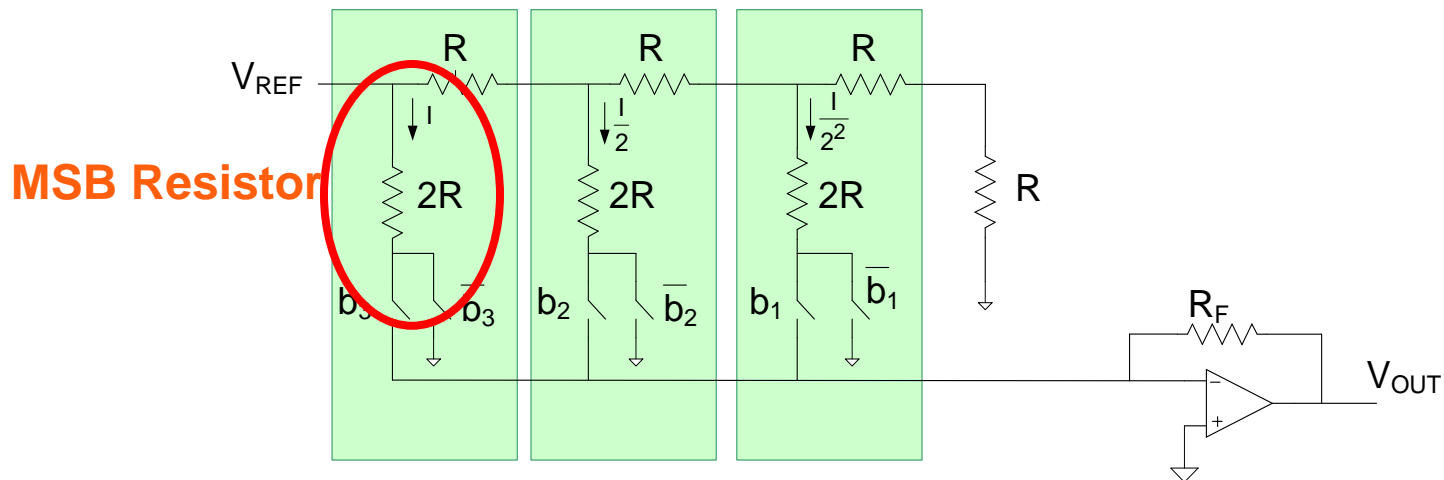


Each bit slice has the same area

MSB resistor has higher percentage of area in Standard Series

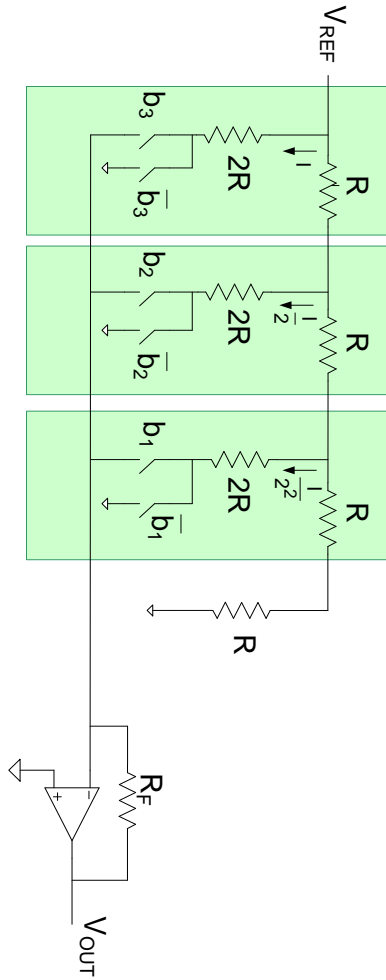Relative Statistical Characterization of R-based DACs



Standard Series Slice Area Scaled


 


R-2R DAC

Relative Statistical Characterization of R-based DACs

DNL histogram for 15,000 random implementations Standard Series Area Scaled

Scaling Factor: 1.7

 
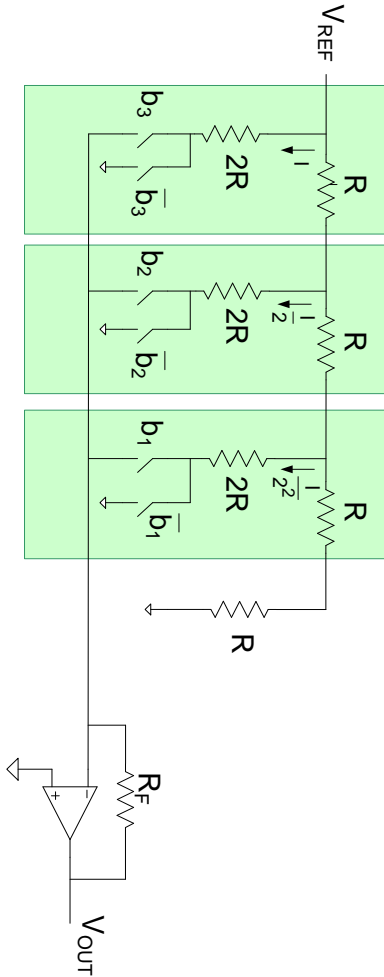


R-2R DAC

Relative Statistical Characterization of R-based DACs

INL histogram for 15,000 random implementations Standard Series Area Scaled

Scaling Factor: 1.7

 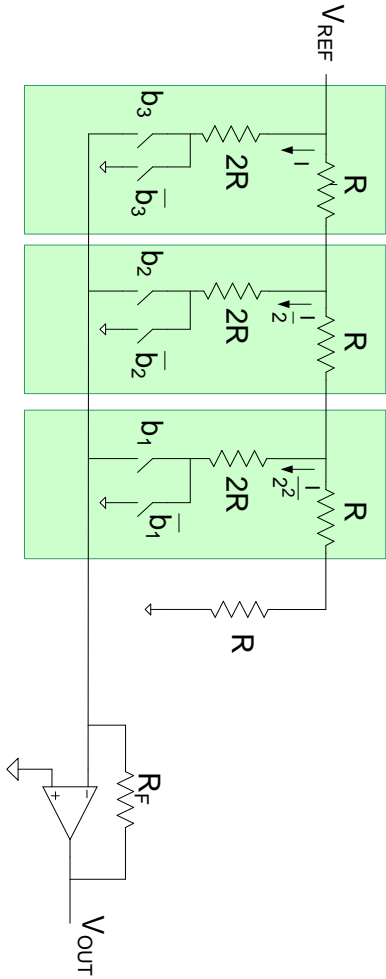

R-2R DAC

Relative Statistical Characterization of R-based DACs

Resolution = 10

$A_{pR} = 0.02\mu\text{m}$

$R_{\text{nom}} = 1000$

Total Area $2048\mu\text{m}^2$

Resistor Sigma= 14.1421

$\text{INL}_{\text{target}} = 0.5\text{ LSB}$

Yield =28.5%

Architecture	INL(LSB)		DNL(LSB)		INL Yield
	Mean	Sigma	Mean	Sigma	
String	0.385	0.118	0.049	0.0047	84.0
Binary Weighted	0.367	0.128	0.470	0.228	84.9
R-2R Series	0.609	0.295	1.021	0.610	41.4
R-2R Parallel	0.737	0.357	1.225	0.732	28.5
Slice Scaled (1.7) Series R-2R	0.399	0.153	0.556	0.286	76.4


Calibration of DACs

- The area required to get acceptable performance of a DAC is often too large to be practical
- Large DAC area invariably increased power dissipation
- Large DAC area invariably limits speed of a DAC
- Calibration is often used to improve the linearity of a DAC
- Calibration requires area overhead but it is often less than the area overhead that is required to improve yield using area alone

$$\sigma_{\frac{x}{x_N}} = \frac{A_x}{\sqrt{A}}$$

- Benefits of using calibration are limited to the inherent noise in a DAC and calibration does not improve random noise (but can reduce quantization noise)

Calibration of DACs

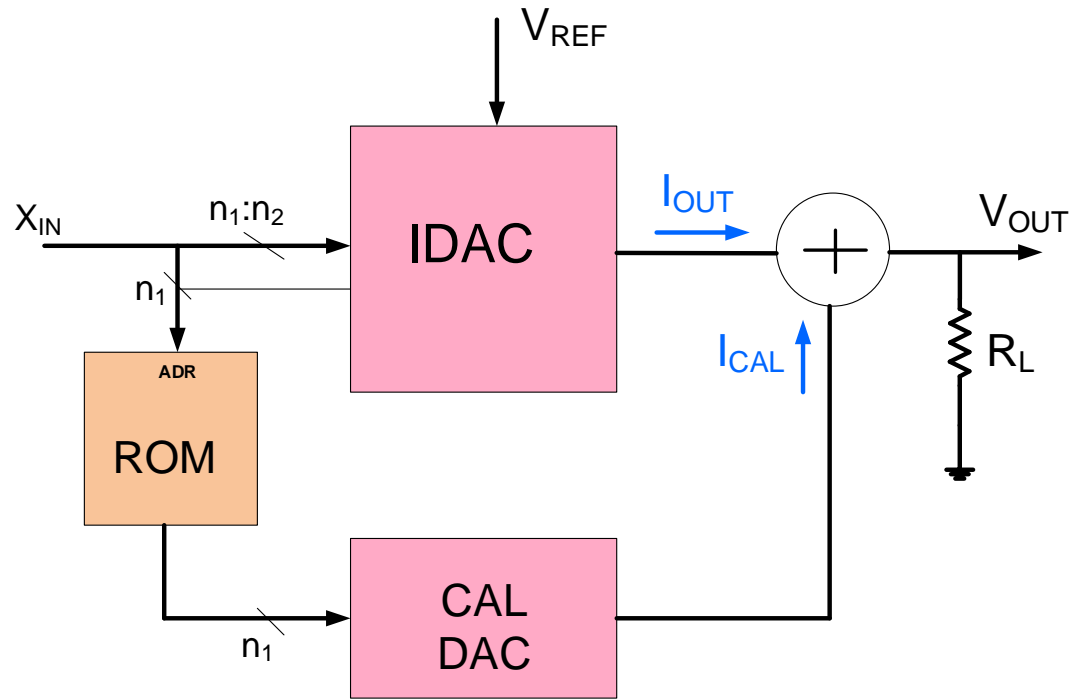


- If CAL DAC is driven by appropriate information in RAM, it can correct for nonlinearities in IDAC
- Resolution of CAL DAC can be small if IDAC is modestly linear
- Code in ROM can be programmed at test or during production

5

- use a slow-speed APC to determine actual output of IDAC & then add approp. output from CALDAC to obtain desired curve

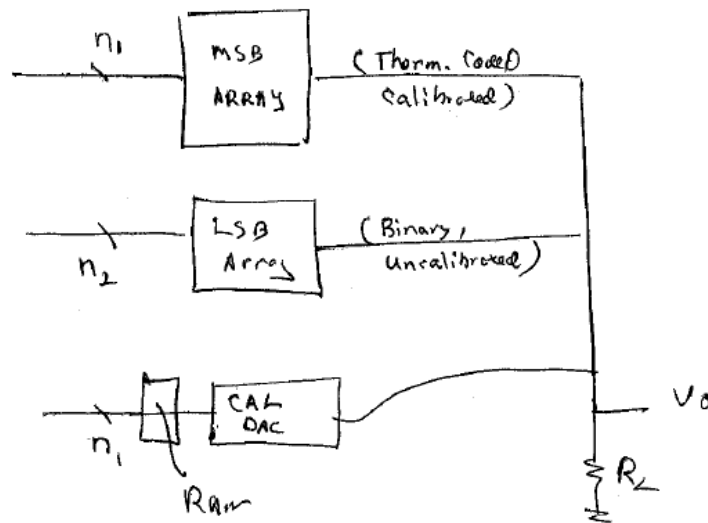
Dramatic Reduction Potential in Area for
Higher-Resolution DACs



Higher-resolution DACs make extensive use of calibration or self-calibration

- Calibration corrects for nonlinearities (either discontinuities or smooth nonlinearities)
- Better high frequency performance
- Smaller die area
- Lower power dissipation
- Often more practical to calibrate for combined effects of all nonlinearities rather than correct the source of individual nonlinearities

Recall the MDAC

 


$$I_1 = (D V_{REF})(K)$$

$$V_O = -I_1 R$$

$$\begin{aligned} V_O &= -R K D V_{REF} \\ &= D [-R K] V_{REF} \end{aligned}$$

Dividing DACs

 

$$I_2 = \frac{V_o D k}{R}$$


$$V_i = -I_2 R$$

$$V_i = -V_o D k$$

$$V_o = + V_i \left(\frac{1}{D} \right) \left(\frac{-1}{k R} \right)$$

could call this D DAC

Multiplying and Dividing DACs

 


$$\begin{cases} I_1 = K_1 V_i D_1 \\ I_2 = V_o D_2 K_2 \end{cases}$$

$$\therefore V_o = \frac{D_1}{D_2} \left[\frac{-K_1 V_i}{K_2} \right]$$

Can create various nonlinear relationships with MDACs and Op Amps



ADC Design

Analog to Digital Converters

 


Analog to Digital Converters

  The conversion from analog to digital in ALL ADCs is done with comparators




ADC design is primarily involved with designing comparators and embedding these into circuits that are robust to nonideal effects


Nyquist Rate

 

Nyquist Rate

 


Over-Sampled

 

Over-sampling ratios of 128:1 or 64:1 are common
Dramatic reduction in quantization noise effects
Limited to relatively low frequencies

Data Converter Type Chart

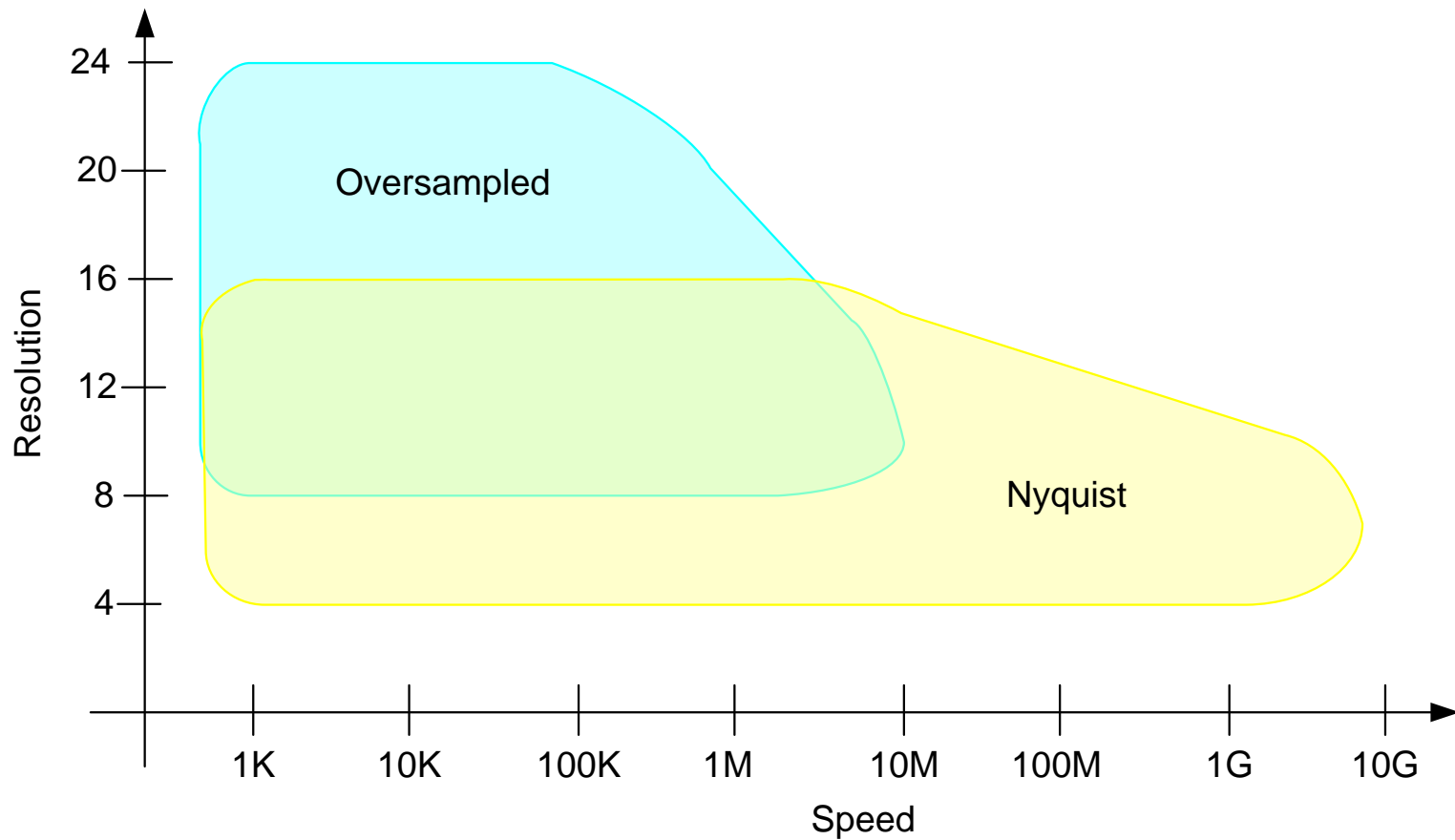

ADC Types


Nyquist Rate

- Flash
- Pipeline
- Two-Step Flash
- Multi-Step Flash
- Cyclic (algorithmic)
- Successive Approximation
- Folded
- Dual Slope

Over-Sampled

- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time

Nyquist Rate Usage Structures

 

Flash is the least used as a stand-alone structure but widely used as a subcomponent in SAR and Pipelined Structures

ADC Types

Nyquist Rate

- Flash
- Pipeline
- Two-Step Flash
- Multi-Step Flash
- Cyclic (algorithmic)
- Successive Approximation
- Folded
- Dual Slope

Over-Sampled



- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time



**All have comparable
conversion rates**

**Basic approach in all is very
similar**


Flash ADC

 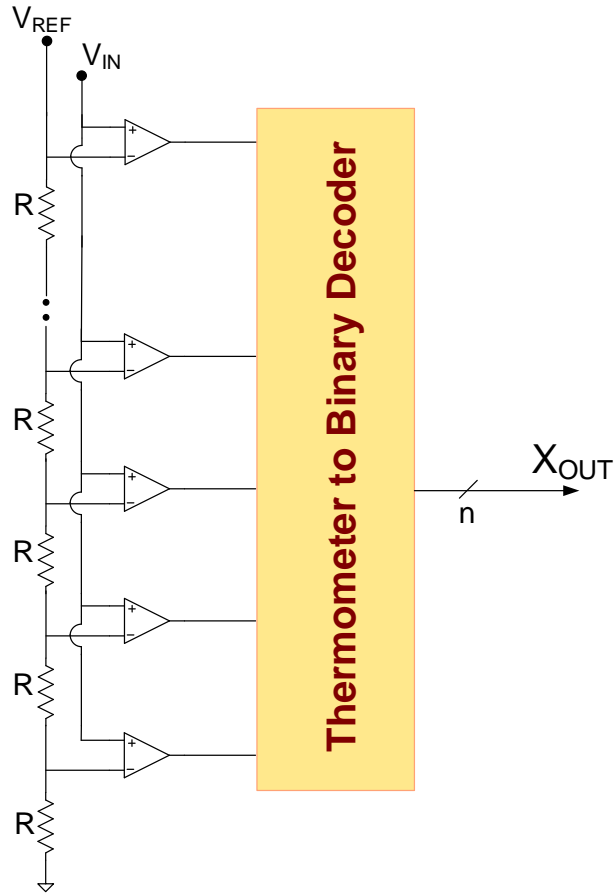

Flash ADC


Basic structure has thermometer code at output

Performance Issues:

 


- + Very fast
- + Simple architecture
- + Instantaneous output
- ➡ Bubble vulnerability
 - Input change during conversion
 - Offset of comparators
 - Number of components and area (for large n)
 - Speed of comparators
 - Loading of V_{REF} and V_{IN}
 - Propagation of V_{IN} and Kickback
 - Power dissipation (for large n)
 - Layout of resistors
 - Voltage and temperature dependence of R 's
 - Matching of R 's

Flash ADC

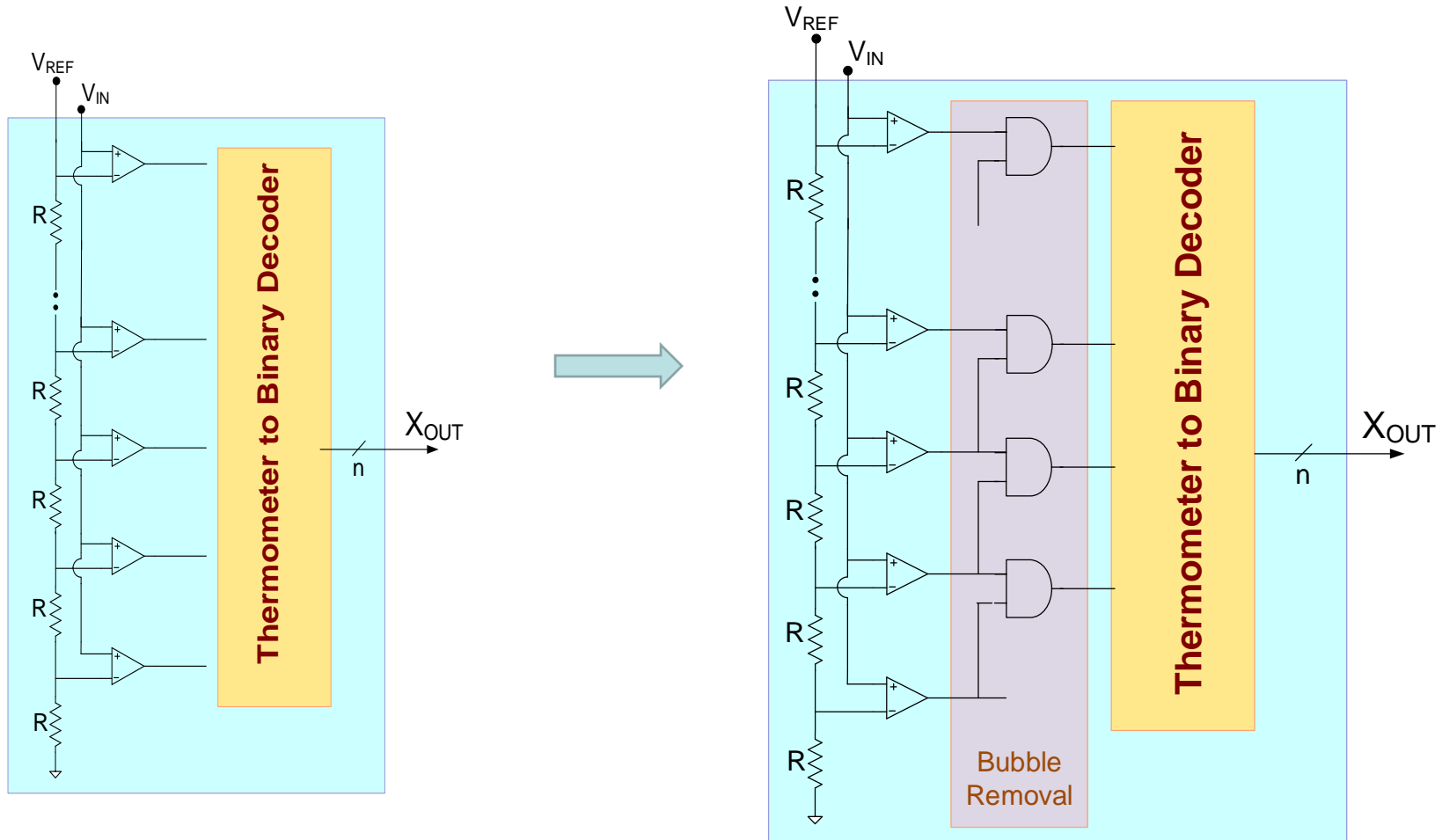

Bubble Removal Approach

Flash ADC

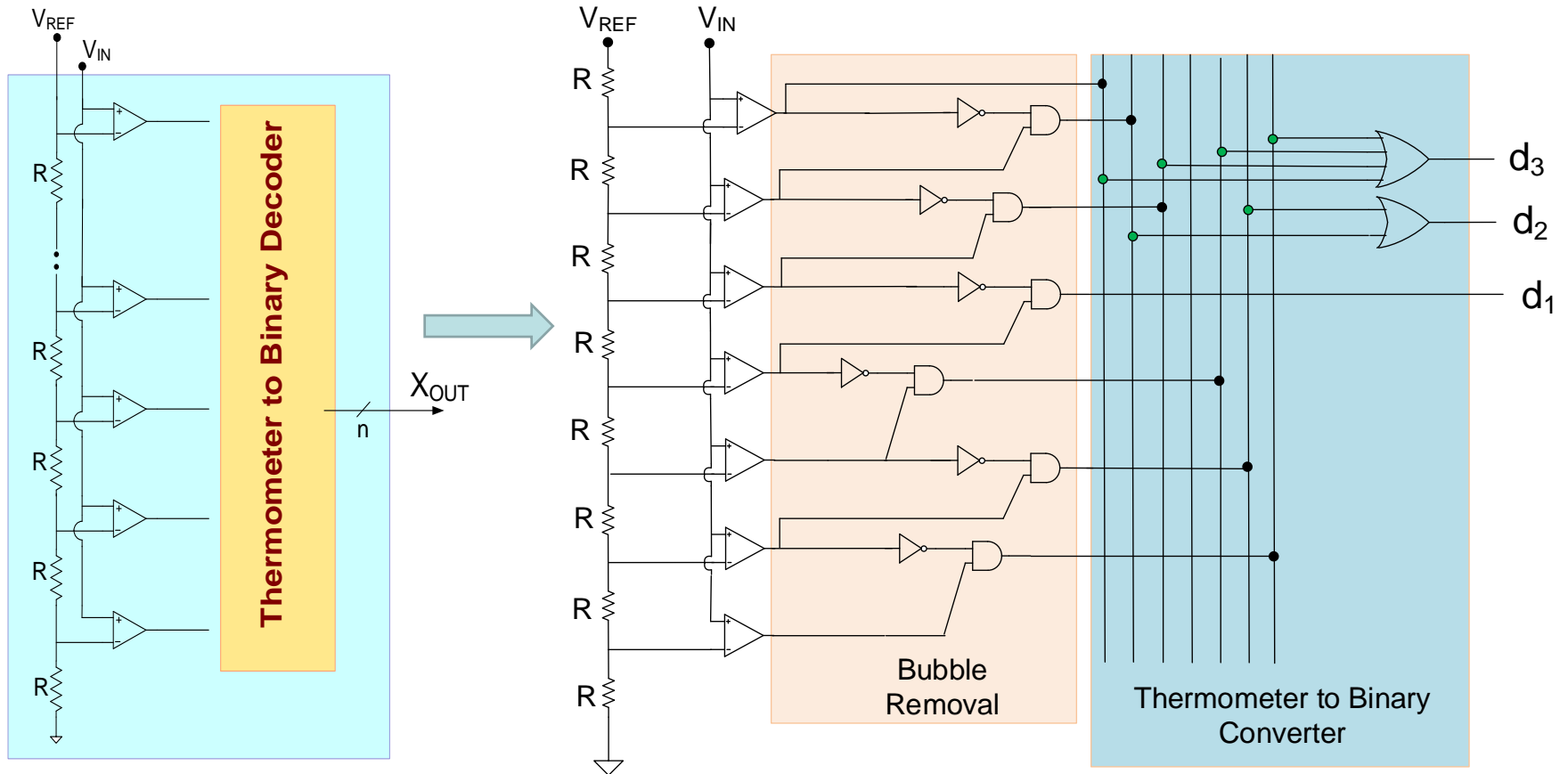

Another Bubble Removal Approach



Stay Safe and Stay Healthy !

End of Lecture 18