 


# EE 505

## Lecture 19

Architectural Performance Comparisons  
ADC Design

# Dynamic Current Source Matching






- Correct charge is stored on  $C$  to make all currents equal to  $I_{REF}$
- Does not require matching of transistors or capacitors
- Requires refreshing to keep charge on  $C$
- Form of self-calibration
- Calibrates current sources one at a time
- Current source unavailable for use while calibrating
- Can be directly used in DACs (thermometer or binary coded)
- Still use steering rather than switching in DAC

Often termed “Current Copier” or “Current Replication” circuit

 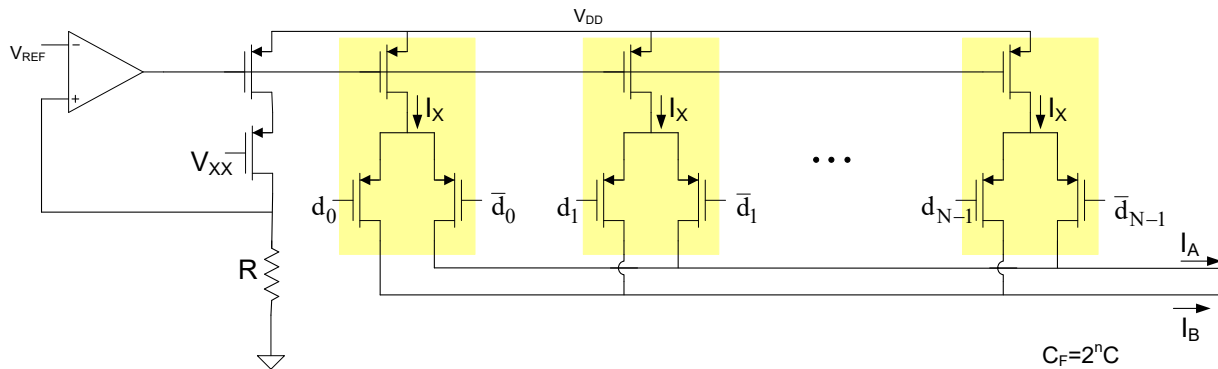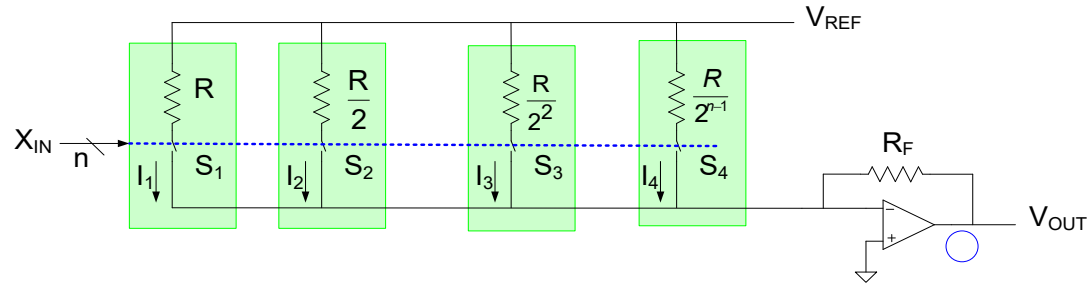
# Noise in DACs

Resistors and transistors contribute device noise but  
what about charge redistribution DACs ?



## Review from Last Lecture

Example: First-Order RC Network

 


$$T(s) = \frac{1}{1+RCs}$$

$$S_{VOUT} = 4kTR \left( \frac{1}{1+(RC\omega)^2} \right)$$

$$v_{n_{RMS}} = \sqrt{\int_{f=0}^{\infty} S_{VOUT} df} = \sqrt{\int_{f=0}^{\infty} \frac{4kTR}{1+\omega^2 R^2 C^2} df}$$

## Review from Last Lecture

### Example: First-Order RC Network

 

$$v_{n_{RMS}} = \sqrt{\int_{f=0}^{\infty} S_{V_{OUT}} df} = \sqrt{\int_{f=0}^{\infty} \frac{4kTR}{1 + \omega^2 R^2 C^2} df}$$


From a standard change of variable with a trig identity, it follows that

$$v_{n_{RMS}} = \sqrt{\int_{f=0}^{\infty} S_{V_{OUT}} df} = \sqrt{\frac{kT}{C}}$$


- Note the continuous-time noise voltage has an RMS value that is independent of  $R$
- The noise contributed by the resistor is dependent only upon the capacitor value  $C$
- This is often referred to as  $kT/C$  noise and it can be decreased at a given  $T$  only by increasing  $C$

# Review from Last Lecture

"kT/C" Noise at T=300K


 


"kT/C" Noise at T=300K

 


## Review from Last Lecture

### Example: Switched Capacitor Sampler

  



Track mode

 

Hold mode

## Review from Last Lecture

### Example: Switched Capacitor Sampler

  


$v_n(kT)$  is a discrete-time sequence obtained by sampling a continuous-time noise wave



## Review from Last Lecture

Characterization of a noise sequence

 

$$\hat{v}_{\text{RMS}} = E \left( \sqrt{\lim_{N \rightarrow \infty} \left( \frac{1}{N} \sum_{k=1}^N v^2(kT) \right)} \right) \underset{N \text{ large}}{\approx} \sqrt{\frac{1}{N} \sum_{k=1}^N v^2(kT)}$$


## Review from Last Lecture

**Theorem** If  $\mathcal{V}(t)$  is a continuous-time zero-mean noise source and  $\langle \mathcal{V}(kT) \rangle$  is a sampled version of  $\mathcal{V}(t)$  sampled at times  $T, 2T, \dots$  then the RMS value of the continuous-time waveform is the same as that of the sampled version of the waveform. This can be expressed as  $\mathcal{V}_{\text{RMS}} = \hat{\mathcal{V}}_{\text{RMS}}$

**Theorem** If  $\mathcal{V}(t)$  is a continuous-time zero-mean noise signal and  $\langle \mathcal{V}(kT) \rangle$  is a sampled version of  $\mathcal{V}(t)$  sampled at times  $T, 2T, \dots$  then the standard deviation of the random variable  $\mathcal{V}(kT)$ , denoted as  $\sigma_{\hat{\mathcal{V}}}$  satisfies the expression  $\sigma_{\hat{\mathcal{V}}} = \mathcal{V}_{\text{RMS}} = \hat{\mathcal{V}}_{\text{RMS}}$


## Review from Last Lecture

### Example: Switched Capacitor Sampler

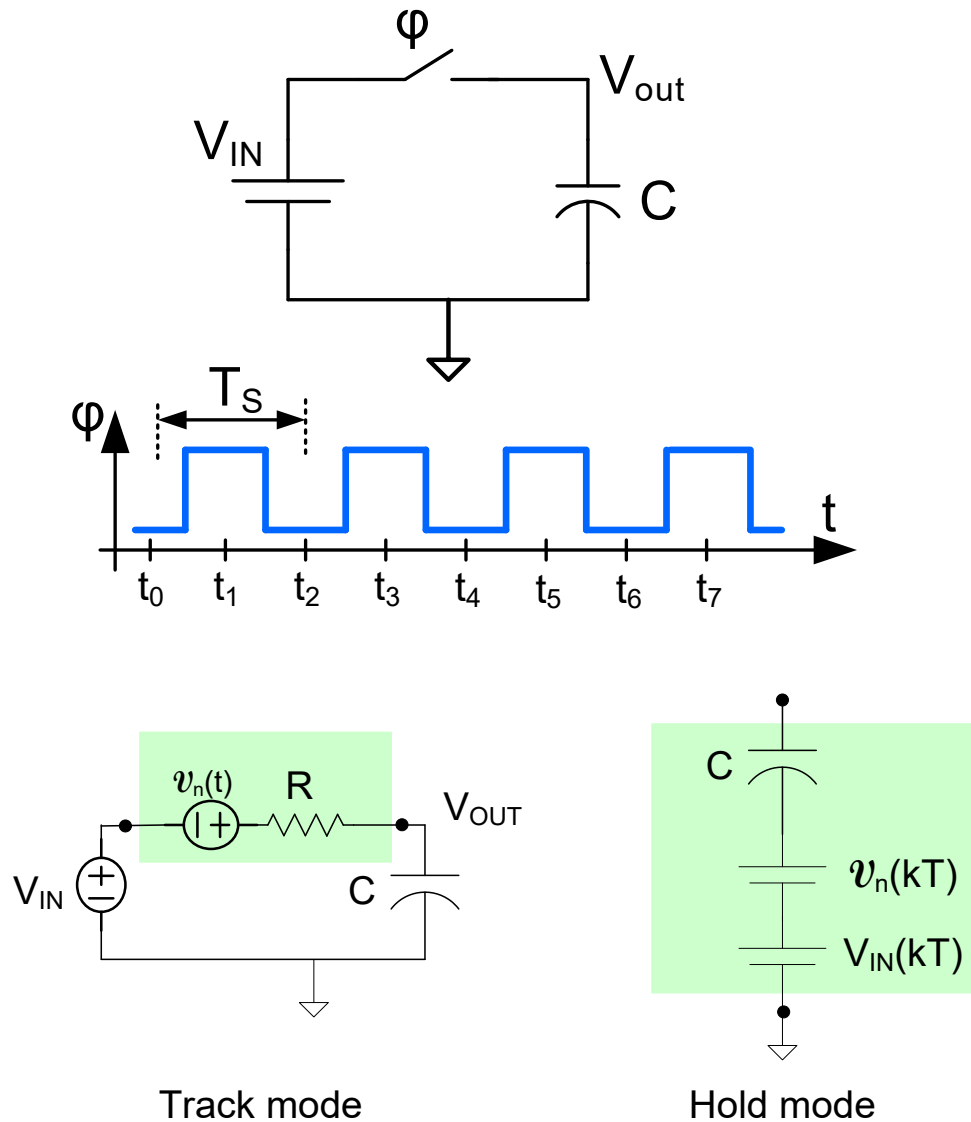

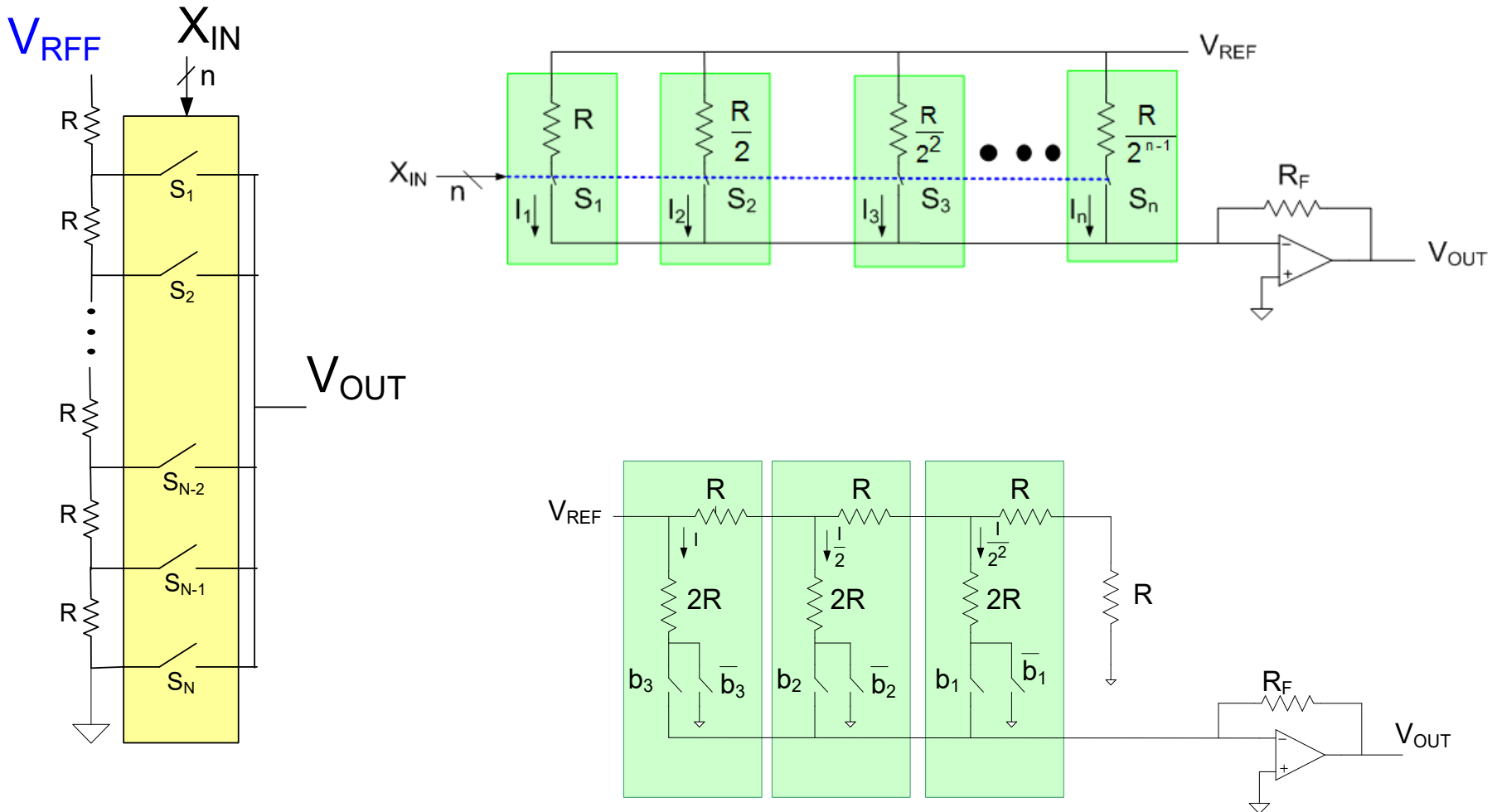
# Architectural Performance Characterizations

For the same total resistor area and the same resolution, how do these structures compare from a statistical characterization viewpoint?


 
# Relative Statistical Characterization of R-based DACs



$$A = WL$$

$$\sigma_{\frac{R}{R_N}} = \frac{A_{\rho R}}{\sqrt{A}}$$

# Relative Statistical Characterization of R-based DACs

For the same total area and the same resolution, how do these structures compare from a statistical characterization viewpoint?

## Simulation environment:

Resolution = 10

$A_{\rho R} = 0.02\mu\text{m}$

Rnom = 1000

Area Unit Resistor =  $2\mu\text{m}^2$


Resistor Sigma= 14.1421

INLtarget = 0.5000 LSB





Yield: Must meet INL target

# Relative Statistical Characterization of R-based DACs

$INL_k$  for four random implementations

 


String DAC

    

 
# Relative Statistical Characterization of R-based DACs

INL histogram for 100,000 random implementations




String DAC

 



 
# Relative Statistical Characterization of R-based DACs

$INL_{kMAX}$  histogram for 100,000 random implementations




String DAC

 

 
# Relative Statistical Characterization of R-based DACs

DNL histogram for 100,000 random implementations




String DAC

 

# Relative Statistical Characterization of R-based DACs

## Summary

 

String DAC

Resolution = 10

$A_{\rho R} = 0.02 \mu\text{m}$

$R_{\text{nom}} = 1000$

Area Unit Resistor =  $2 \mu\text{m}^2$

Resistor Sigma = 14.1421

$\text{INL}_{\text{mean}} = 0.385 \text{ LSB}$

$\text{INL}_{\text{sigma}} = 0.118 \text{ LSB}$






$\text{DNL}_{\text{mean}} = 0.049 \text{ LSB}$

$\text{DNL}_{\text{sigma}} = 0.0047 \text{ LSB}$

Yield (%) = 84.0

# Relative Statistical Characterization of R-based DACs



$INL_k$  for four random implementations

    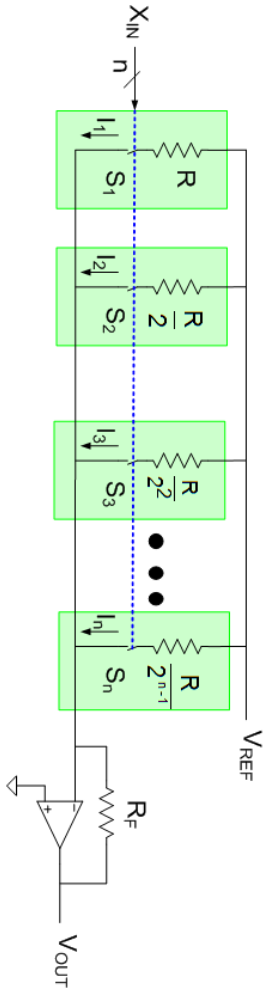

Binary Weighted DAC
 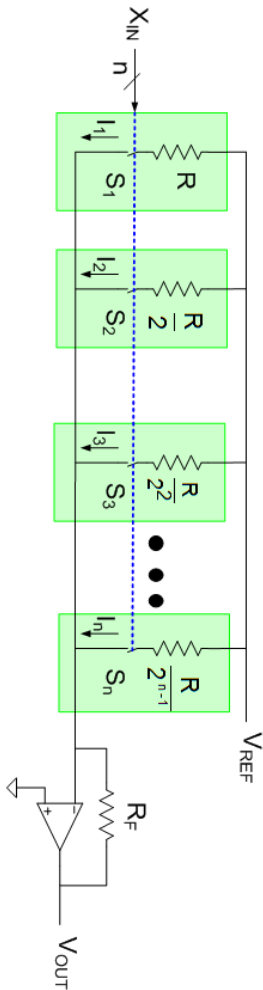
# Relative Statistical Characterization of R-based DACs



INL histogram for 100,000 random implementations



Binary Weighted DAC
  
# Relative Statistical Characterization of R-based DACs



$INL_{kMAX}$  histogram for 100,000 random implementations



Binary Weighted DAC
  
# Relative Statistical Characterization of R-based DACs


DNL histogram for 100,000 random implementations



Binary Weighted DAC

# Relative Statistical Characterization of R-based DACs

## Summary

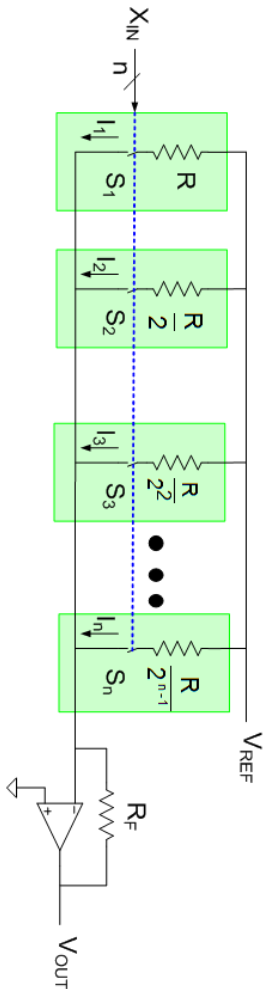

Binary Weighted DAC

Resolution = 10

$A_{pR} = 0.02\mu\text{m}$

$R_{\text{nom}} = 1000$

Area unit resistor =  $2\mu\text{m}^2$

Resistor Sigma = 14.1421

$\text{INL}_{\text{mean}} = 0.367\text{LSB}$

$\text{INL}_{\text{sigma}} = 0.128\text{LSB}$

$\text{INL}_{\text{kmax\_mean}} = 0.00013\text{LSB}$

$\text{INL}_{\text{kmax\_sigma}} = 0.226\text{LSB}$

$\text{DNL}_{\text{mean}} = 0.470\text{LSB}$

$\text{DNL}_{\text{sigma}} = 0.228\text{LSB}$


$\text{INL}_{\text{target}} = 0.500\text{LSB}$

Yield (%) = 84.9




# Relative Statistical Characterization of R-based DACs

## Popular Area Allocation Strategies





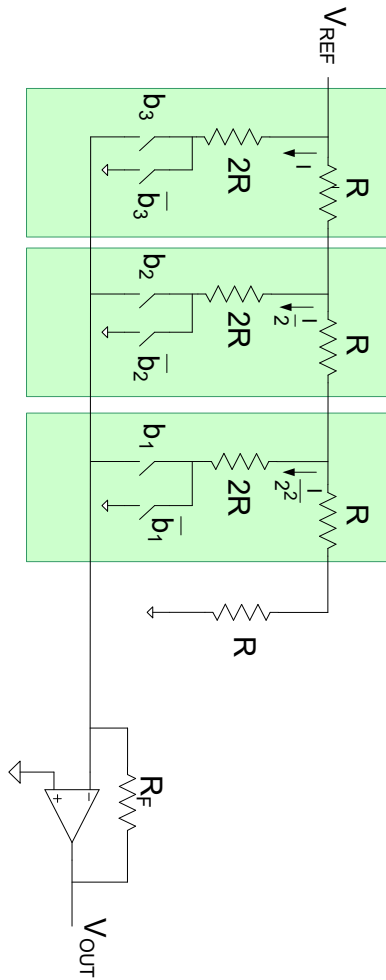


R-2R DAC

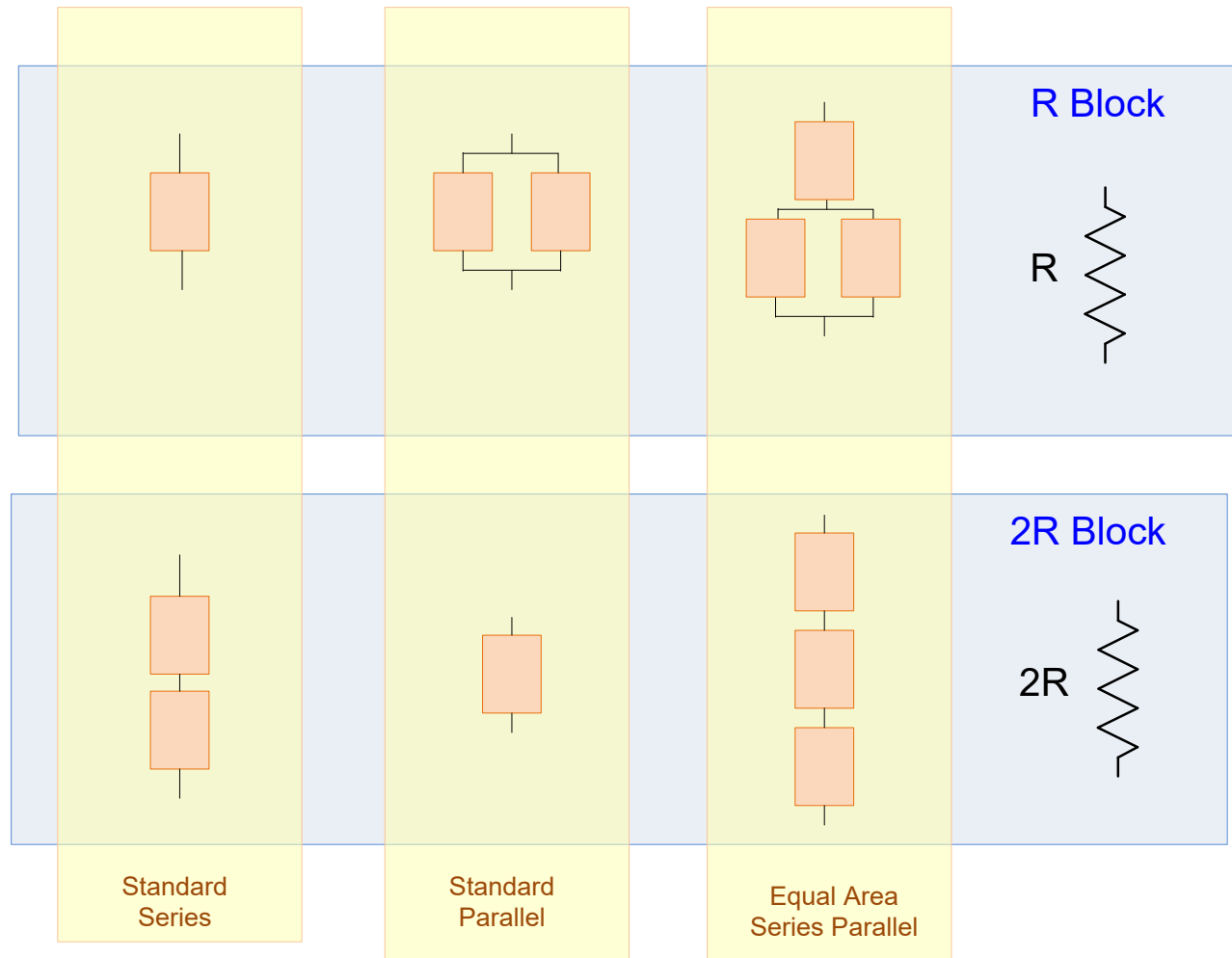
     
# Relative Statistical Characterization of R-based DACs



$INL_k$  for four random standard series implementations



R-2R DAC
  
# Relative Statistical Characterization of R-based DACs



INL histogram for 15,000 random implementations Standard Series



R-2R DAC
  
# Relative Statistical Characterization of R-based DACs


DNL histogram for 15,000 random implementations Standard Series



R-2R DAC

# Relative Statistical Characterization of R-based DACs

## Summary Standard Series

 

R-2R DAC

Resolution=10

$A_{pR}=0.02 \mu\text{m}$

$R_{\text{nom}} = 1000$

Base Res Area( $\mu\text{m}^2$ )=2

Res Sigma=14.1421

$\text{INL}_{\text{mean}} = 0.609 \text{ LSB}$

$\text{INL}_{\text{sigma}} = 0.295 \text{ LSB}$

$\text{DNL}_{\text{mean}} = 1.021 \text{ LSB}$

$\text{DNL}_{\text{sigma}} = 0.610 \text{ LSB}$

$\text{INL}_{\text{kmax\_mean}} = 0.00017 \text{ LSB}$


$\text{INL}_{\text{kmax\_sigma}} = 0.566 \text{ LSB}$

Yield INL Bound=0.5 LSB





Yield= 41.4%
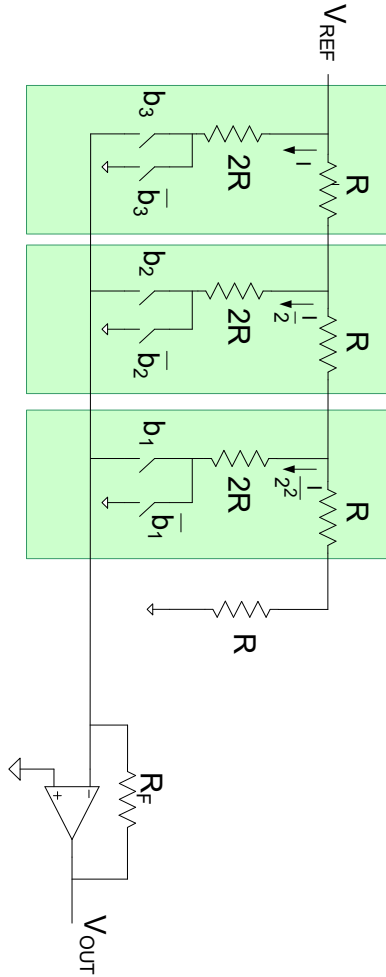
# Relative Statistical Characterization of R-based DACs

$INL_k$  for four random standard parallel implementations





R-2R DAC

    
 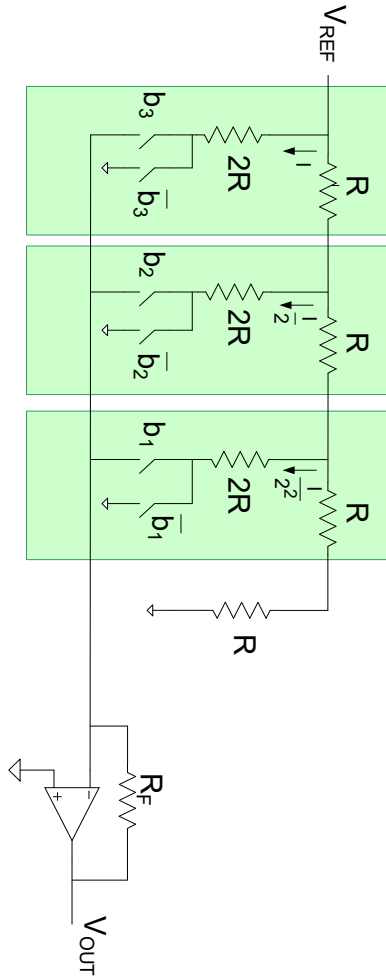
# Relative Statistical Characterization of R-based DACs



INL histogram for 100,000 random implementations Standard Parallel



R-2R DAC
  
# Relative Statistical Characterization of R-based DACs

DNL histogram for 100,000 random implementations Standard Parallel




R-2R DAC



# Relative Statistical Characterization of R-based DACs

## Summary Standard Parallel

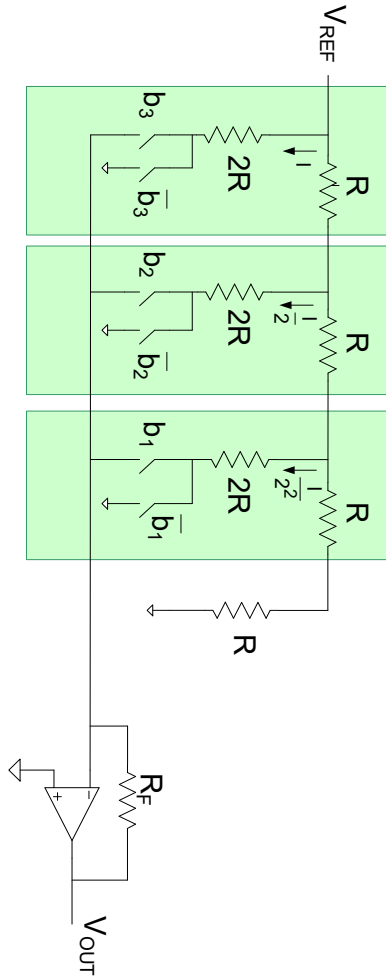

Resolution = 10

$A_{pR} = 0.02\mu\text{m}$

$R_{\text{nom}} = 1000$

Base Resistor Area( $\mu\text{m}^2$ ) = 2

Resistor Sigma = 14.1421

$\text{INL}_{\text{mean}} = 0.737 \text{ LSB}$

$\text{INL}_{\text{sigma}} = 0.357 \text{ LSB}$

$\text{INL}_{\text{kmax\_mean}} = 0.0045 \text{ LSB}$

$\text{INL}_{\text{kmax\_sigma}} = 0.680 \text{ LSB}$

$\text{DNL}_{\text{mean}} = 1.225 \text{ LSB}$

$\text{DNL}_{\text{sigma}} = 0.732 \text{ LSB}$

$\text{INL}_{\text{target}} = 0.5 \text{ LS}$

Yield = 28.5%

R-2R DAC


Why is the Standard Series yield significantly larger than the Standard Parallel?

Standard Parallel

Yield = 28.5%

Standard Series


Yield = 41.4%

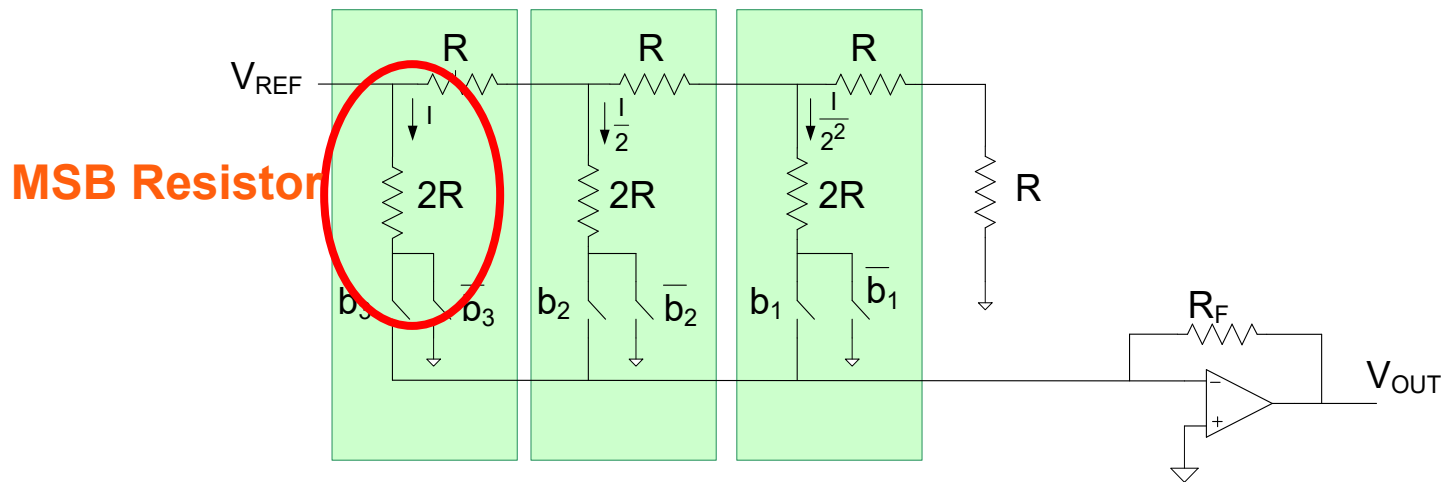


Each bit slice has the same area

MSB resistor has higher percentage of area in Standard Series
 
# Relative Statistical Characterization of R-based DACs



Standard Series Slice Area Scaled


 


R-2R DAC

# Relative Statistical Characterization of R-based DACs

DNL histogram for 15,000 random implementations Standard Series Area Scaled

Scaling Factor: 1.7

 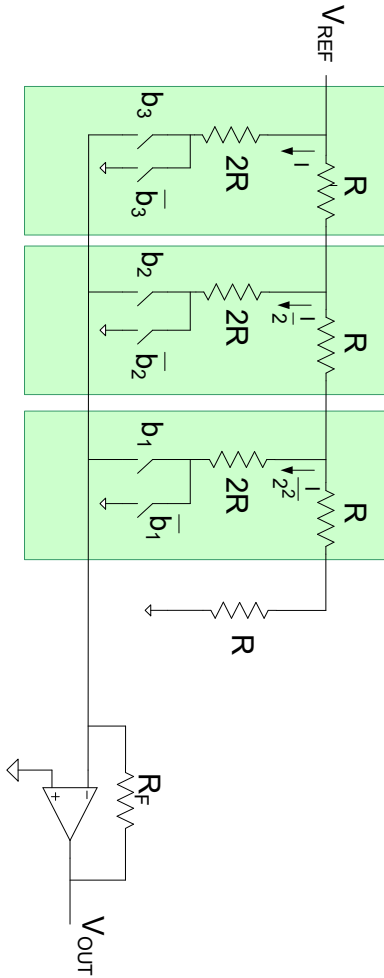


R-2R DAC


# Relative Statistical Characterization of R-based DACs

INL histogram for 15,000 random implementations Standard Series Area Scaled

Scaling Factor: 1.7

 

R-2R DAC

 

# Relative Statistical Characterization of R-based DACs

Resolution = 10

$A_{pR} = 0.02\mu\text{m}$

$R_{\text{nom}} = 1000$

Total Area  $2048\mu\text{m}^2$

Resistor Sigma= 14.1421

$\text{INL}_{\text{target}} = 0.5\text{ LSB}$

Yield =28.5%

Architecture	INL(LSB)		DNL(LSB)		INL Yield
	Mean	Sigma	Mean	Sigma	
String	0.385	0.118	0.049	0.0047	84.0
Binary Weighted	0.367	0.128	0.470	0.228	84.9
R-2R Series	0.609	0.295	1.021	0.610	41.4
R-2R Parallel	0.737	0.357	1.225	0.732	28.5
Slice Scaled (1.7) Series R-2R	0.399	0.153	0.556	0.286	76.4


# Calibration of DACs

- The area required to get acceptable performance of a DAC is often too large to be practical
- Large DAC area invariably increased power dissipation
- Large DAC area invariably limits speed of a DAC
- Calibration is often used to improve the linearity of a DAC
- Calibration requires area overhead but it is often less than the area overhead that is required to improve yield using area alone

$$\sigma_{\frac{x}{x_N}} = \frac{A_x}{\sqrt{A}}$$

- Benefits of using calibration are limited to the inherent noise in a DAC and calibration does not improve random noise (but can reduce quantization noise)

# Calibration of DACs

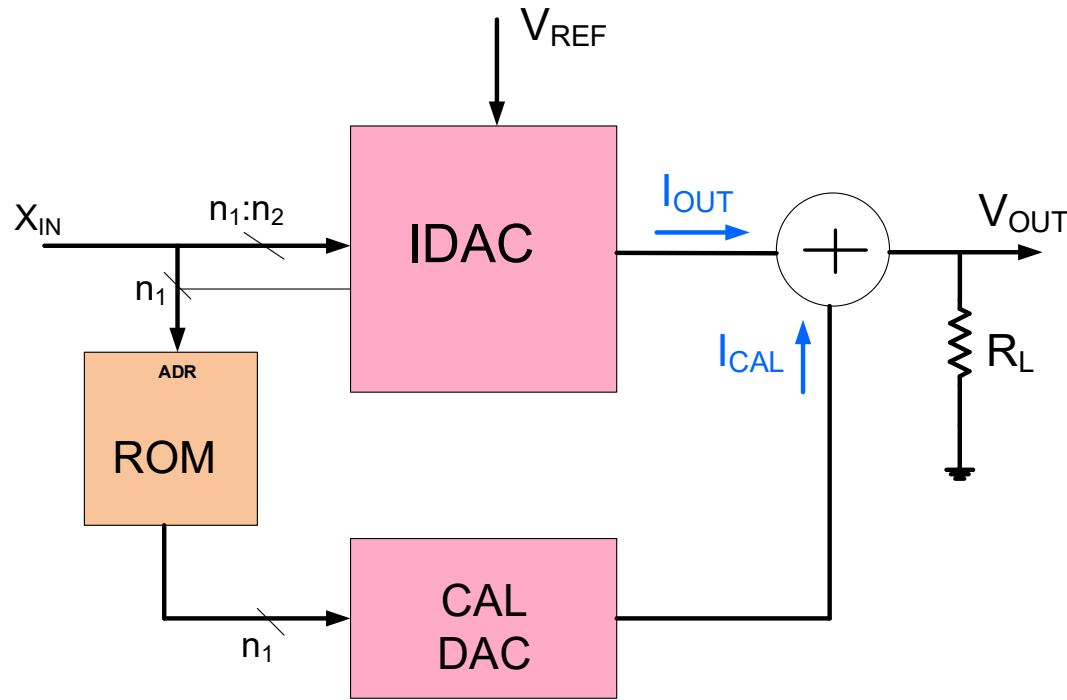


- If CAL DAC is driven by appropriate information in RAM, it can correct for nonlinearities in ADC
- Resolution of CAL DAC can be small if IDAC is modestly linear
- Code in ROM can be programmed at test or during production



5

- use a slow-speed APC to determine actual output of IDAC & then add approp. output from CALDAC to obtain desired curve

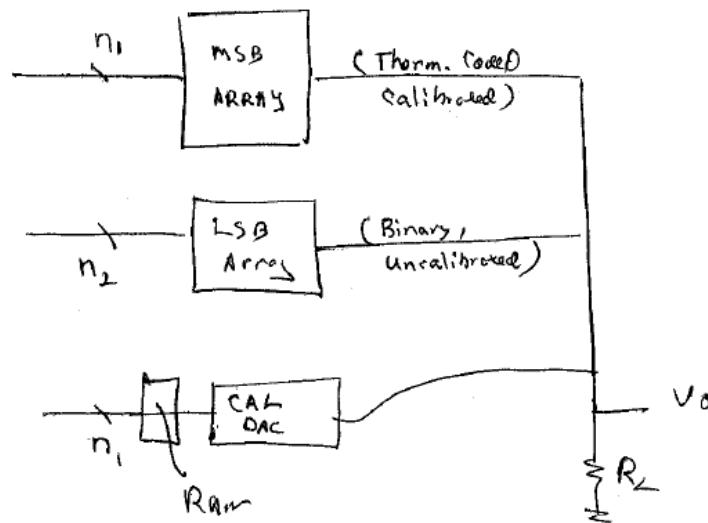
Dramatic Reduction Potential in Area for Higher-Resolution ADCs,



Higher-resolution DACs make extensive use of calibration or self-calibration

- Calibration corrects for nonlinearities (either discontinuities or smooth nonlinearities)
- Better high frequency performance
- Smaller die area
- Lower power dissipation
- Often more practical to calibrate for combined effects of all nonlinearities rather than correct the source of individual nonlinearities

# Recall the MDAC

 


$$I_1 = (D V_{REF})(K)$$

$$V_O = -I_1 R$$

$$\begin{aligned} V_O &= -R K D V_{REF} \\ &= D [-R K] V_{REF} \end{aligned}$$

# Dividing DACs

 

$$I_2 = \frac{V_o D k}{R}$$


$$V_i = -I_2 R$$

$$V_i = -V_o D k$$

$$V_o = + V_i \left( \frac{1}{D} \right) \left( \frac{-1}{k R} \right)$$

could call this D DAC

# Multiplying and Dividing DACs

 


$$\begin{cases} I_1 = K_1 V_i D_1 \\ I_2 = V_o D_2 K_2 \end{cases}$$

$$\therefore V_o = \frac{D_1}{D_2} \left[ \frac{-K_1 V_i}{K_2} \right]$$

Can create various nonlinear relationships with MDACs and Op Amps



# ADC Design

# Analog to Digital Converters

 
  
# Analog to Digital Converters


The conversion from analog to digital in ALL ADCs is done with comparators




ADC design is primarily involved with designing comparators and embedding these into circuits that are robust to nonideal effects




# Nyquist Rate

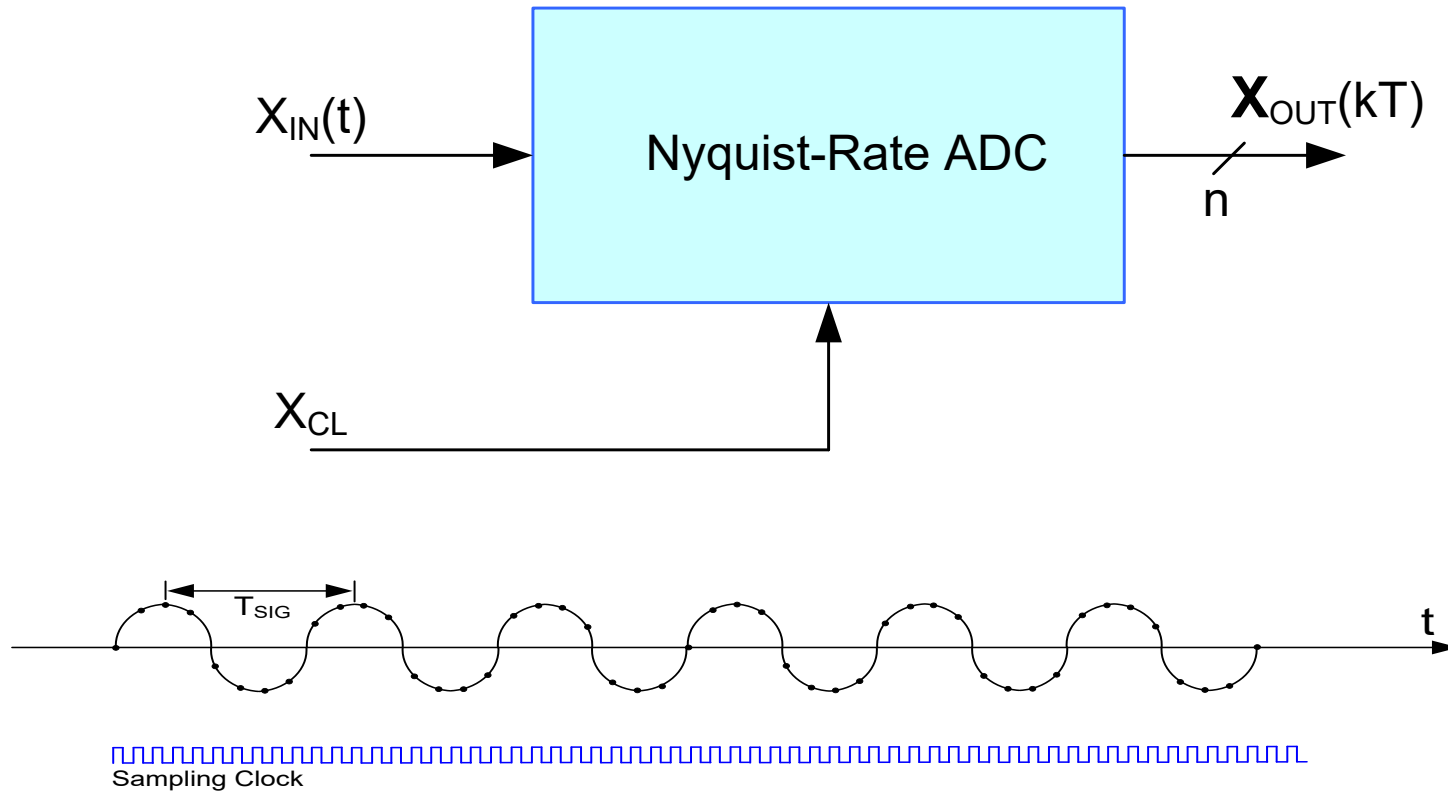

# Nyquist Rate

 


# Over-Sampled

 

Over-sampling ratios of 128:1 or 64:1 are common  
Dramatic reduction in quantization noise effects  
Limited to relatively low frequencies

# Data Converter Type Chart

 

# ADC Types


## Nyquist Rate

- Flash
- Pipeline
- Two-Step Flash
- Multi-Step Flash
- Cyclic (algorithmic)
- Successive Approximation
- Folded
- Dual Slope

## Over-Sampled

- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time

# Nyquist Rate Usage Structures

 

Flash is the least used as a stand-alone structure but widely used as a subcomponent in SAR and Pipelined Structures

# ADC Types

## Nyquist Rate

- Flash
- Pipeline
- Two-Step Flash
- Multi-Step Flash
- Cyclic (algorithmic)
- Successive Approximation
- Folded
- Dual Slope

## Over-Sampled



- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time



**All have comparable  
conversion rates**


**Basic approach in all is very  
similar**

# Flash ADC

  



# Flash ADC

 


Basic structure has thermometer code at output

## Performance Issues:


- + Very fast
- + Simple architecture
- + Instantaneous output
- ➡ Bubble vulnerability
  - Input change during conversion
  - Offset of comparators
  - Number of components and area (for large  $n$ )
  - Speed of comparators
  - Loading of  $V_{REF}$  and  $V_{IN}$
  - Propagation of  $V_{IN}$  and Kickback
  - Power dissipation (for large  $n$ )
  - Layout of resistors
  - Voltage and temperature dependence of  $R$ 's
  - Matching of  $R$ 's

# Flash ADC

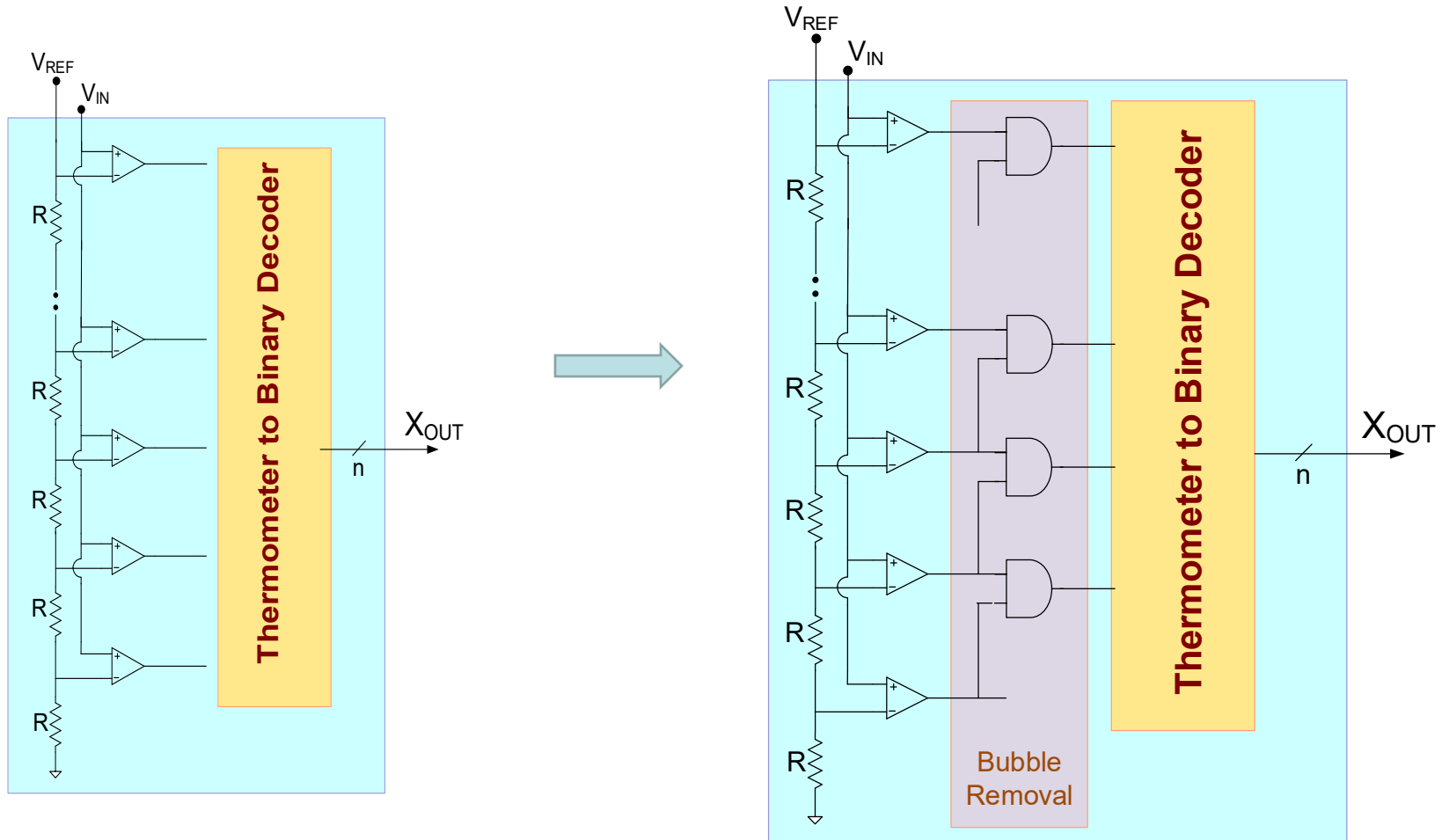


Bubble Removal Approach

# Flash ADC

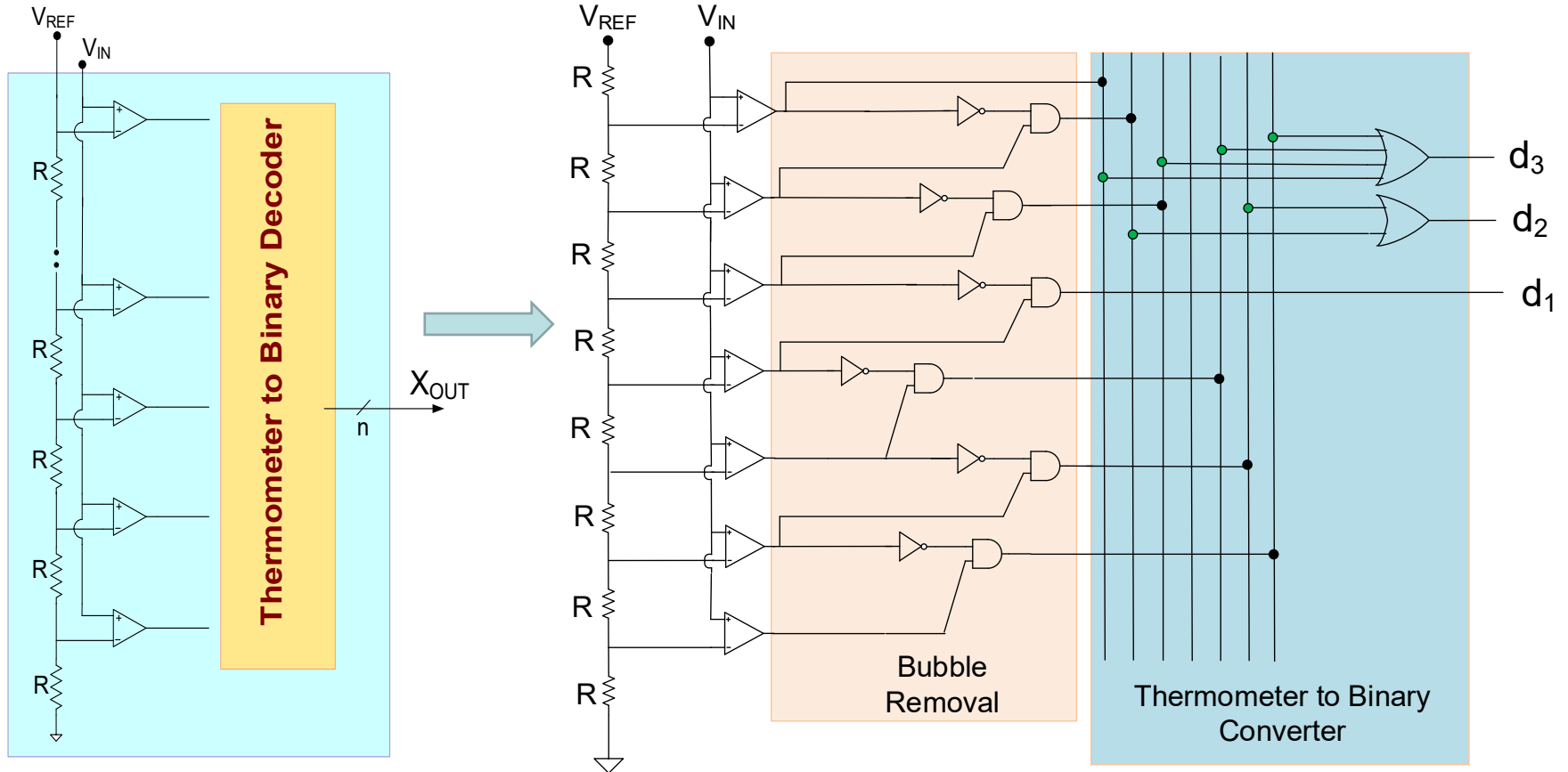

Another Bubble Removal Approach

# Flash ADC

 

Basic structure has thermometer code at output

## Performance Issues:

- + Very fast
- + Simple architecture
- + Instantaneous output



Bubble vulnerability



Input change during conversion



Offset of comparators




Number of components and area (for large  $n$ )

- Speed of comparators
- Loading of  $V_{REF}$  and  $V_{IN}$
- Propagation of  $V_{IN}$  and Kickback
- Power dissipation (for large  $n$ )
- Layout of resistors
- Voltage and temperature dependence of  $R$ 's
- Matching of  $R$ 's
 
# Input change during conversion


Front-End S/H can mitigate effects of input change during conversion



- Speed of sample/hold of concern
- Noise of S/H
- Nonlinearity of S/H
- Input range of S/H
- Power dissipation of S/H
- Loose asynchronous operation of ADC
- Widely used
- S/H may be most challenging part of design


# Input change during conversion

## Flash ADC with Front-End S/H

 


# Input change during conversion

## Flash ADC with Front-End S/H

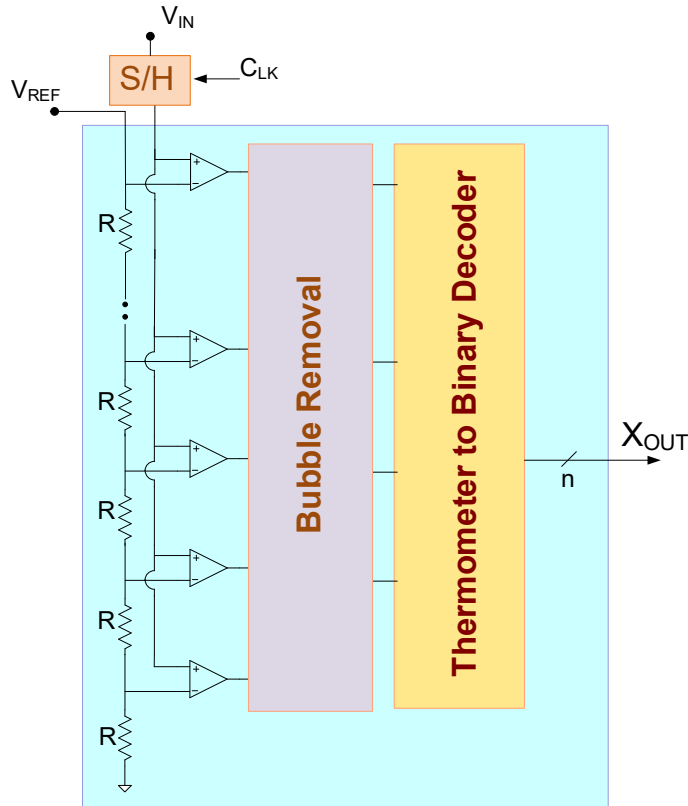

Input S/H with Clk

 


Input S/H with Clk and clocked comparators

**End of Lecture 19**



# Flash ADC

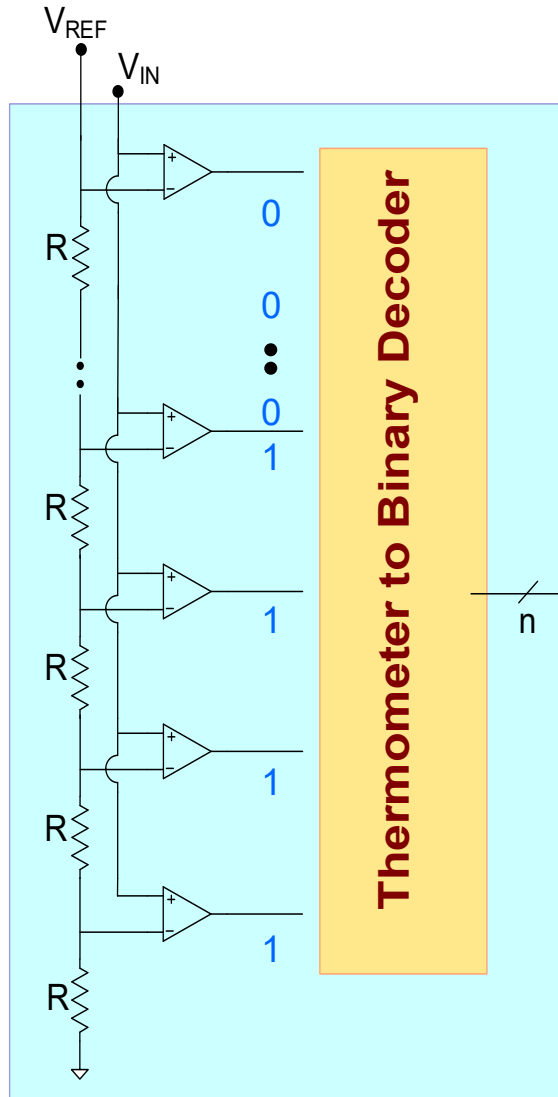


Basic structure has thermometer code at output

## Performance Issues:


- + Very fast
  - + Simple architecture
  - + Instantaneous (asynchronous output)
  - + Good DNL with low comparator offsets
- 
- ✓ Bubble vulnerability
  - ✓ Input change during conversion
  - ➡ Wide range of common-mode comparator inputs
    - Number of components and area (for large  $n$ )
    - Loading of  $V_{REF}$  and  $V_{IN}$
    - Propagation of  $V_{IN}$
    - Power dissipation (for large  $n$ )
    - Offset and speed of comparators
    - Layout of resistors
    - Voltage and temperature dependence of  $R$ 's
    - Matching of  $R$ 's
 
# Clocked Comparator with Regenerative Feedback




Regenerative Feedback

## Regenerative Comparators

 

Differential

 

Single-Ended

- Regenerative feedback often used to force decision when differential inputs are small
- Several variants of clocked comparators are available
- Important to not have trip point dependent upon previous comparison results
- Often one or more linear gain stages precede the regenerative stage
- Power dissipation can be small in regenerative feedback comparators
- Large offset voltage (100mV or more) common for regenerative feedback comparators

# Clocked Comparator with Regenerative Feedback

