 


EE 505

Lecture 27

Oversampled ADCs

Data Converter Type Chart




Over-Sampled Data Converters


General Classes

- Single-bit
- Multi-bit
- First-order
- Higher-order
- Continuous-time

Nyquist Rate

 

Over-Sampled

 

Over-sampling ratios of 128:1 or 64:1 are common
Dramatic reduction in quantization noise effects
Limited to relatively low frequencies


Recall with no quantization:

$$f_{\text{SIG}}=50\text{Hz}$$

$$f_{\text{NYQ}}=100\text{Hz}$$

$$f_{\text{SAMP}}=2.3\text{KHz}$$


Oversampled: 23:1

 

MatLab Results

Recall:

Quantization Effects

 


Simulation environment:

$$N_p = 23$$
$$f_{\text{SIG}} = 50\text{Hz}$$

Recall:

Quantization Effects

Res = 4 bits

 

$f_{\text{SIG}}=50\text{Hz}$
 $f_{\text{NYQ}}=100\text{Hz}$
 $f_{\text{SAMP}}=1113\text{KHz}$
Oversampled: 11:1


RMS Quantization Noise: $E_{\text{RMS}} = \frac{x_{\text{LSB}}}{\sqrt{12}}$

Lets now increase resolution

Recall:

Quantization Effects

Res = 10 bits

 

$f_{\text{SIG}}=50\text{Hz}$
 $f_{\text{NYQ}}=100\text{Hz}$
 $f_{\text{SAMP}}=1113\text{KHz}$
Oversampled: 11:1

$$E_{\text{RMS}} = \frac{x_{\text{LSB}}}{\sqrt{12}}$$


Quantization noise is much lower but still significant

Lets now increase oversampling ratio (i.e. number of samples)

Recall:

Quantization Effects

Res = 10 bits

 

$f_{\text{SIG}} = 50\text{Hz}$

$f_{\text{NYQ}} = 100\text{Hz}$

$f_{\text{SAMP}} = 8904\text{KHz}$

Oversampled: 89:1

$$E_{\text{RMS}} = \frac{x_{\text{LSB}}}{\sqrt{12}}$$


Compared to the previous slide, it appears that the quantization noise has gone down

But has it ? Magnitude of quantization DFT terms decreased but E_{RMS} unchanged

Recall:

Quantization Effects

Res = 10 bits

 

$$f_{\text{SIG}} = 50\text{Hz}$$

$$f_{\text{NYQ}} = 100\text{Hz}$$


$$f_{\text{SAMP}} = 8904\text{KHz}$$

Oversampled: 89:1

$$E_{\text{RMS}} = \frac{x_{\text{LSB}}}{\sqrt{12}}$$

Can any additional useful information about the input be obtained since we have many more samples than are needed?

Over-Sampling

 

Res = 10 bits

$$f_{\text{SIG}} = 50\text{Hz}$$

$$f_{\text{NYQ}} = 100\text{Hz}$$

$$f_{\text{SAMP}} = 8904\text{KHz}$$

Oversampled: 89:1



$$E_{\text{RMS}} = \frac{x_{\text{LSB}}}{\sqrt{12}}$$


What would happen if we break the 4096 samples into groups of 20 samples and form?

$$\hat{x}_{\text{OUT}}(k \cdot 20T_{\text{SAMP}}) = \frac{1}{20} \sum_{j=1}^{20} x_{\text{OUT}}(jT_{\text{SAMP}} + 20kT_{\text{SAMP}})$$

$$E_{\text{RMS}} = ?$$

- Though the individual samples have been quantized to 10 bits, the arithmetic operations will have many more bits
- The effective sampling rate has been reduced by a factor of 20 but is still over 4 times the Nyquist rate
- Has the quantization noise been reduced (or equivalently has the resolution of the ADC been improved?)
- Is there more information available about the signal?

Over-Sampling

 

Res = 10 bits

$$f_{\text{SIG}} = 50\text{Hz}$$

$$f_{\text{NYQ}} = 100\text{Hz}$$


$$f_{\text{SAMP}} = 8904\text{KHz}$$

Oversampled: 89:1



$$E_{\text{RMS}} = \frac{x_{\text{LSB}}}{\sqrt{12}}$$

 Since the quantization noise is at high frequencies, what would happen if filtered the Boolean output signal?




$$E_{\text{RMS}} = ?$$

$$Y_{\text{OUT}}(kT_{\text{SAMP}}) = \sum_{j=0}^m a_j x_{\text{OUT}}(k - jT_{\text{SAMP}})$$

Or

$$Y_{\text{OUT}}(kT_{\text{SAMP}}) = \sum_{j=0}^m a_j x_{\text{OUT}}(k - jT_{\text{SAMP}}) + \sum_{j=1}^h b_j Y_{\text{OUT}}(k - jT_{\text{SAMP}})$$

Over-Sampling

 

Res = 10 bits

$f_{SIG}=50\text{Hz}$

$f_{NYQ}=100\text{Hz}$

$f_{SAMP}=8904\text{KHz}$

Oversampled: 89:1

What does this difference equation represent?

$$Y_{OUT}(kT_{SAMP}) = \sum_{j=0}^m a_j x_{OUT}(k - jT_{SAMP})$$

- Moving Average (MA) Digital Filter
- Filter shape (e.g. low-pass, band-pass, high-pass, ... dependent upon $\langle a_i \rangle$ coefficients)



$$E_{RMS} = \frac{x_{LSB}}{\sqrt{12}}$$

$$H(z) = \sum_{i=1}^m a_i z^i$$

What does this difference equation represent?


$$Y_{OUT}(kT_{SAMP}) = \sum_{j=0}^m a_j x_{OUT}(k - jT_{SAMP}) + \sum_{j=1}^h b_j Y_{OUT}(k - jT_{SAMP})$$

- Auto Regressive Moving Average (ARMA) Digital Filter
- Filter shape (e.g. low-pass, band-pass, high-pass, ... dependent upon $\langle a_i \rangle$ and $\langle b_j \rangle$ coefficients)



$$H(z) = \frac{\sum_{i=1}^m a_i z^i}{\sum_{i=0}^n b_i z^i}$$

Over-Sampling

 

Res = 10 bits

$$f_{\text{SIG}} = 50\text{Hz}$$

$$f_{\text{NYQ}} = 100\text{Hz}$$

$$f_{\text{SAMP}} = 8904\text{KHz}$$

Oversampled: 89:1




$$E_{\text{RMS}} = \frac{x_{\text{LSB}}}{\sqrt{12}}$$

Since the quantization noise is at high frequencies, what would happen if filtered and decimated the Boolean output signal?


$$Y_{\text{OUT}}(kT_{\text{SAMP}}) = \sum_{j=0}^m a_j x_{\text{OUT}}(k - jT_{\text{SAMP}})$$
 
$$Y_{\text{OUT}}(kT_{\text{SAMP}}) = \sum_{j=0}^m a_j x_{\text{OUT}}(k - jT_{\text{SAMP}}) + \sum_{j=1}^h b_j Y_{\text{OUT}}(k - jT_{\text{SAMP}})$$




$$E_{\text{RMS}} = ?$$

Over-Sampling

 

$$E_{RMS} = \frac{x_{LSB}}{\sqrt{12}}$$

 


$$E_{RMS} = ?$$



$$E_{RMS} = ?$$


- What is the overhead?
- What is the performance potential?
- How can these or related over-sampling approaches be designed?
- Though this approach may help quantization noise, will not improve ADC linearity

Over-Sampling

 


$$f_s = f_{\text{SAMP}}$$

$$OSR = \frac{f_s}{2 f_0}$$

 

With ideal lowpass filter with band-edge at f_0

 
$$V_{\text{Rms}} = \frac{V_{\text{LSB}}}{\sqrt{12}} \frac{1}{\sqrt{OSR}}$$



For sinusoidal input with p-p value V_{REF}


$$SNR = 6.02n + 1.76 + 10\log(OSR)$$

 Improvement of 3dB/octave or 0.5bits/octave




Oversampling increases resolution and if followed by LP filter Reduces Quantization Noise!

Over-Sampling

 

 Example: If we sample a sinusoidal waveform at a rate of 1000 samples/period with a 4-bit ADC and at each time we create a 16-point moving sum, how many digits will we have at each sample point?



What is the quantization noise of the 4-bit ADC?

$$V_{n_RMS} = \frac{V_{LSB_4}}{\sqrt{12}} = \frac{V_{REF}}{2^4 \sqrt{12}} = \frac{V_{REF}}{2^5 \sqrt{3}}$$

Have we created an 8-bit ADC by simply over sampling?

What is the quantization noise of an 8-bit ADC?


$$V_{n_RMS} = \frac{V_{LSB_8}}{\sqrt{12}} = \frac{V_{REF}}{2^8 \sqrt{12}} = \frac{V_{REF}}{2^9 \sqrt{3}} \quad \text{of this ADC (w/o decimation)?}$$

If the 4-bit ADC has INL at the 16-bit level, what will be the INL of the 8-bit ADC?

How many digital output codes will be present with the 4-bit ADC ? 16

How many digital output codes will be present in the 8-bit ADC ? 256

Over-Sampling

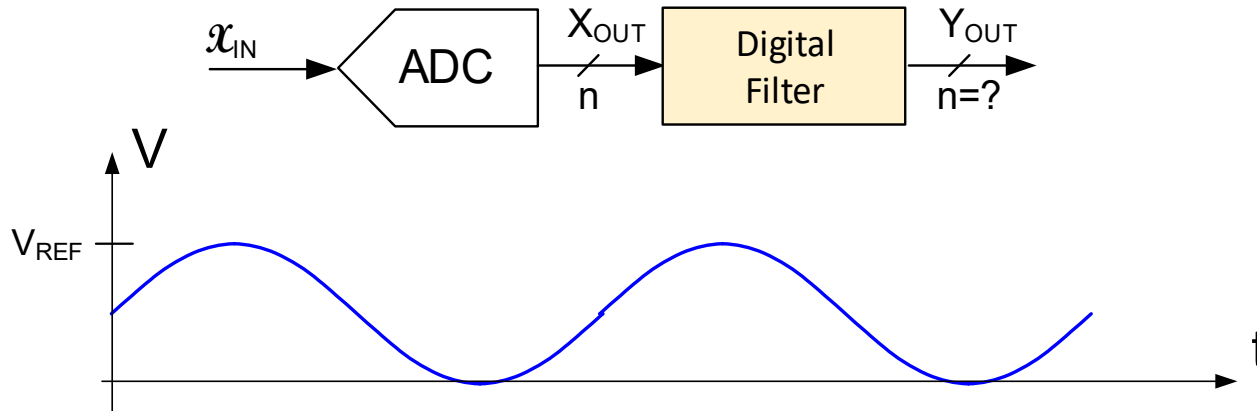


In the previous example, the Digital Filter was a MA filter, other Digital Filters could be used

Is over-sampling followed by digital filtering a practical way to increase the effective resolution of an ADC?


Is the digital computation overhead acceptable?

One limitation of this approach is that to get a major increase in effective resolution, the over-sampling ratio gets very large since ENOB varies with the square root of the OSR


Over-Sampling

 

 Consider same 4-bit ADC with 16-point Moving Average digital filter



 
What will be the output if a constant input is applied ?




Will it still be an 8-bit output?

If a large number of constant input signals are applied, how many output codes will there be? 16

Over-Sampling

 

 Consider same 4-bit ADC with 16-point Moving Average digital filter




Be careful about performance relative to speckmanship !

Is there some way to actually take advantage of the over-sampling to increase the apparent resolution without facing the static resolution problem?


Can add random noise, or dither, or use $\Delta\Sigma$ modulation or other ways as well

Over-sampled ADC

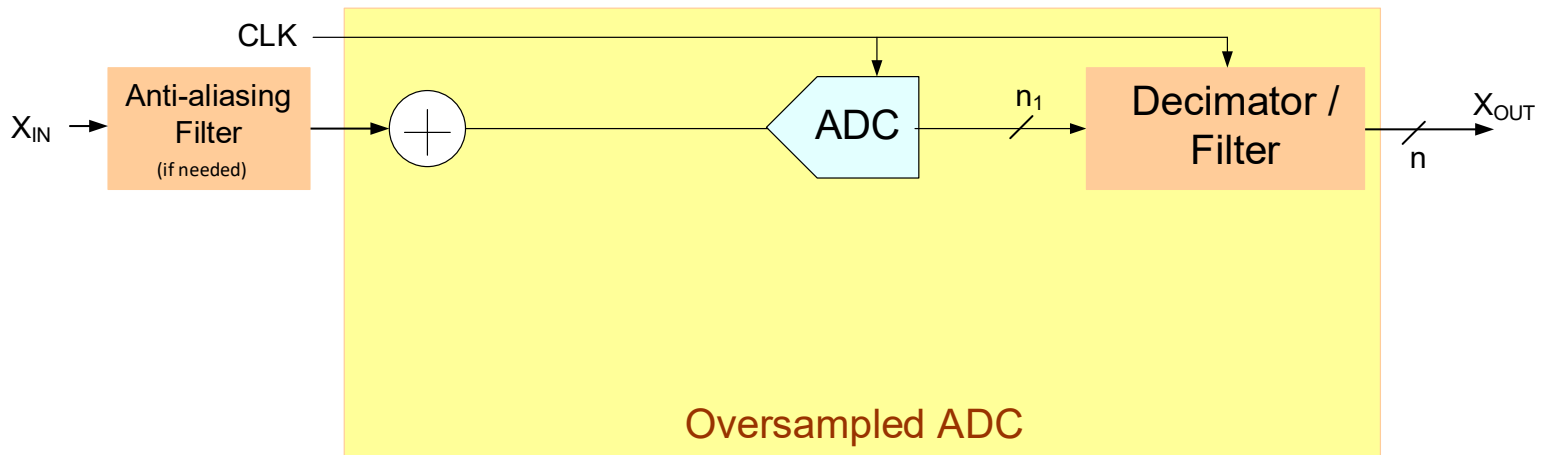

- Anti-aliasing filter at the input (if needed) to limit bandwidth of input signal
- ADC is often simply a comparator
- CLK is much higher in frequency than effective sampling rate (maybe 128:1 though lower OSR also widely used)
- Can obtain very high resolution but effective sampling rate is small
- **With clever design, this approach can reduce quantization effects and improve linearity**

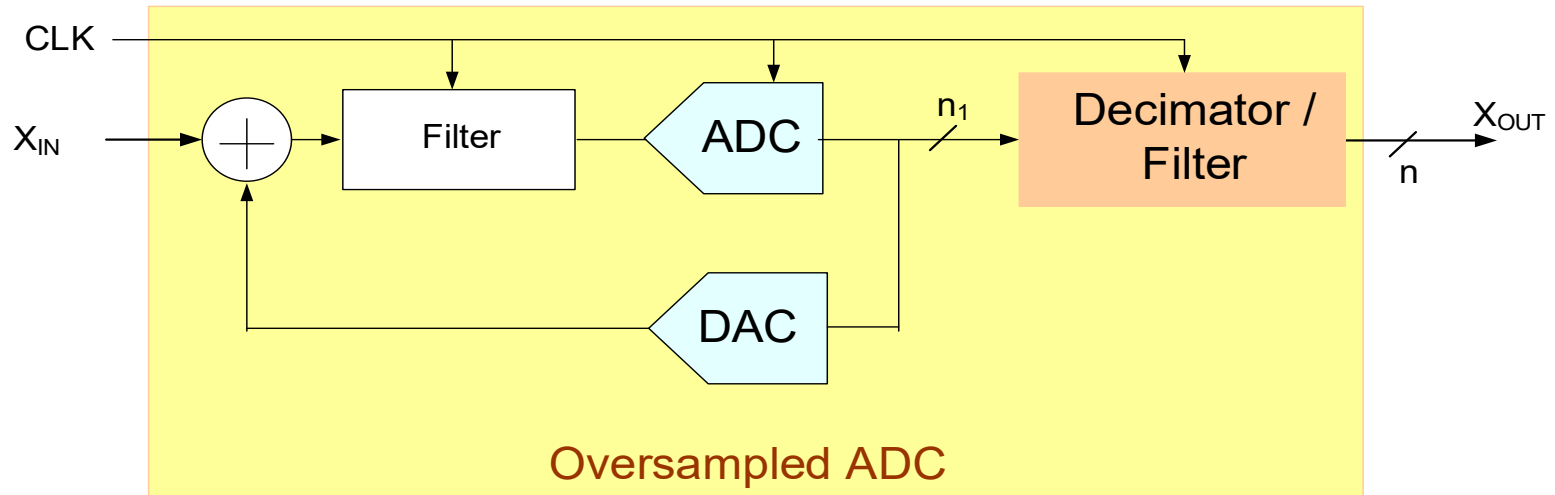Over-sampled $\Delta\Sigma$ ADC (Delta-Sigma)




If Modulator is added, the over-sampled ADC becomes a $\Delta\Sigma$ ADC

Δ modulation introduced by Deloraine in 1946

$\Delta\Sigma$ ADC concept introduced by Yasuhiko Yasuda in the early 1960's while he was a student at [the University of Tokyo](#)

Candy (1974) and Temes credited with incorporating the concept in integrated data converters

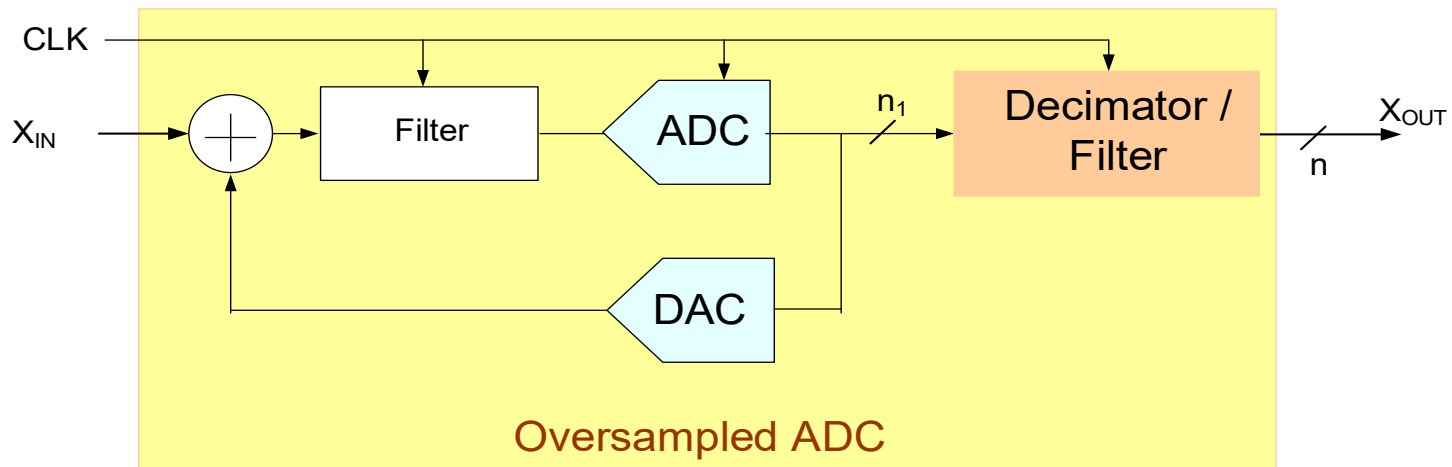Over-sampled $\Delta\Sigma$ ADC (Delta-Sigma)




- Linearity performance almost entirely determined by that of the DAC
- 1-bit DAC (i.e. only a comparator for ADC) is inherently linear and widely used
- 20-bit linearity is achievable without any trimming using 1-bit DAC

Example: To obtain 16-bit linearity with a 10-bit DAC, the 10-bit DAC must be linear to at least the 16-bit level. This would usually require tedious trimming of the DAC

Analysis of Delta-Sigma ADC

(big benefit is noise shaping)

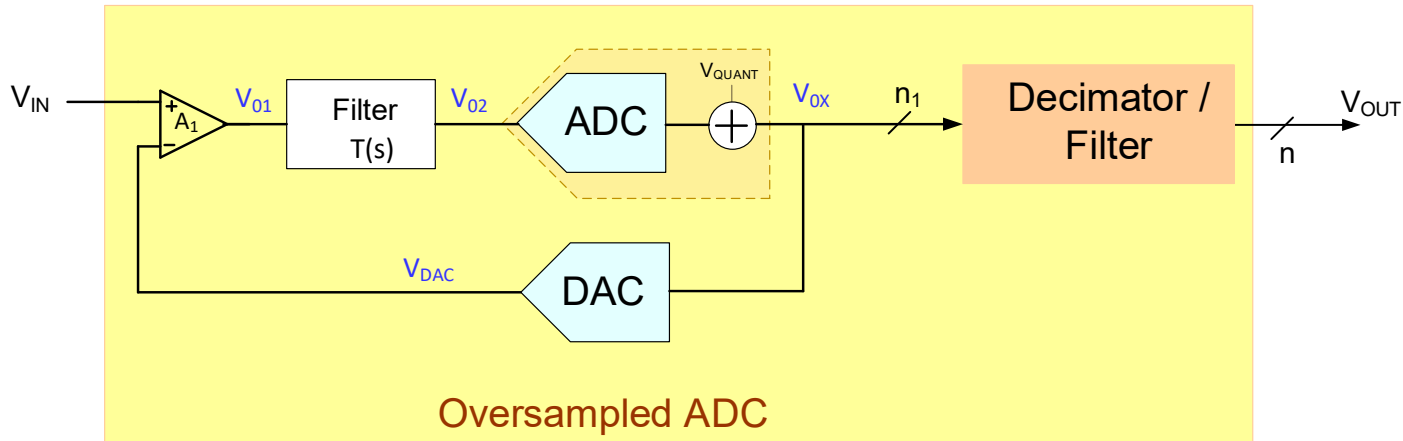


Assume ADC and DAC have unity gain (for convenience only)

Model the ADC as an ideal ADC with a quantization noise source

Decimator/Filter follow the modulator so can be neglected in analysis of modulator

Analysis of Delta-Sigma ADC

(big benefit is noise shaping)

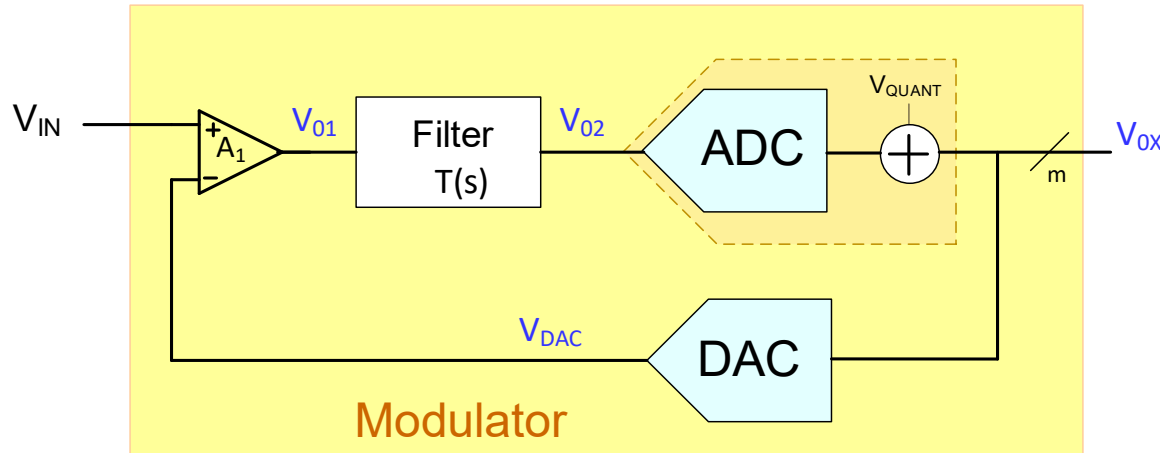

$$V_{O1} = A_1 (V_{IN} - V_{DAC})$$

$$V_{O2} = T(s) V_{O1}$$

$$V_{OX} = V_{O2} + V_{QUANT}$$

$$V_{DAC} = V_{OX}$$

Solving, we obtain


$$V_{OX} = \frac{T(s)A_1}{1 + T(s)A_1} V_{IN} + V_{QUANT} \frac{1}{1 + T(s)A_1}$$

Note: Significantly different transfer functions for V_{IN} and V_{QUANT}

Analysis of Delta-Sigma ADC

(big benefit is noise shaping)
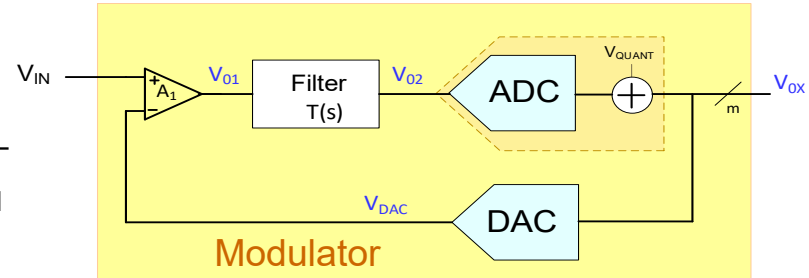
$$V_{OX} = \frac{T(s)A_1}{1 + T(s)A_1} V_{IN} + V_{QUANT} \frac{1}{1 + T(s)A_1}$$



Consider using an integrator for $T(s)$

$$T(s) = \frac{I_{01}}{s}$$

I_{01} is the unity gain frequency of the integrator and is a critical parameter in the modulator

Thus

$$V_{OX} = \frac{I_{01}A_1}{s + I_{01}A_1} V_{IN} + V_{QUANT} \frac{s}{s + I_{01}A_1}$$


Note V_{IN} is low-pass filtered and V_{QUANT} is high-pass filtered and both are first-order with the same poles

Analysis of Delta-Sigma ADC


(big benefit is noise shaping)

$$V_{OX} = \frac{I_{01}A_1}{s + I_{01}A_1} V_{IN} + V_{QUANT} \frac{s}{s + I_{01}A_1}$$

With integrator for $T(s)$

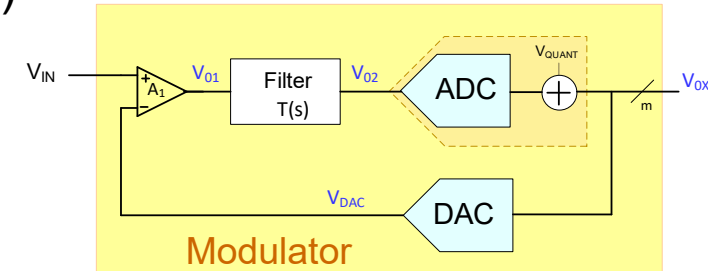

 Signal and Noise Transfer Function Magnitudes




- Noise filtering will remove most of the noise from the signal band if the pole placed around signal band edge
- Signal band will not be significantly affected
- Filtering the noise is termed “noise shaping” in the vernacular of the delta-sigma community
- Since gain is 1 at high frequencies, HP filter does not increase spectral magnitude of noise at high frequencies

Analysis of Delta-Sigma ADC

(big benefit is noise shaping)


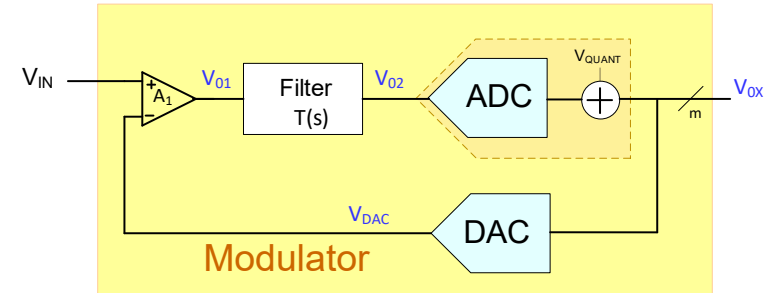
$$V_{OX} = \frac{I_{01}A_1}{s + I_{01}A_1} V_{IN} + V_{QUANT} \frac{s}{s + I_{01}A_1}$$



Consider the noise output first

$$V_{OX-noise} = V_{QUANT} \frac{s}{s + I_{01}A_1}$$

$$f_{3dB} = I_{01}A_1$$

  


Major change in quantization noise spectral density at output

Analysis of Delta-Sigma ADC

(big benefit is noise shaping)

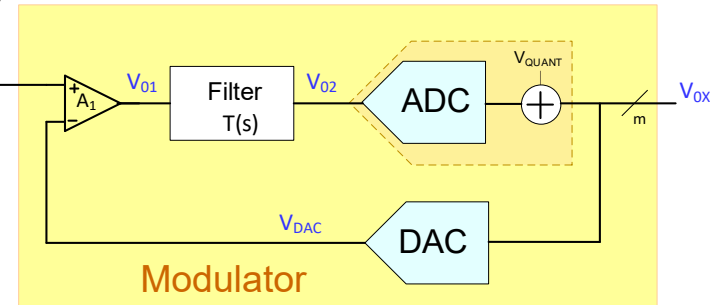
$$V_{OX} = \frac{I_{01}A_1}{s + I_{01}A_1} V_{IN} + V_{QUANT} \frac{s}{s + I_{01}A_1}$$



Consider the input signal

$$V_{OX-IN} = V_{IN} \frac{I_{01}A_1}{s + I_{01}A_1}$$

$$f_{3dB} = I_{01}A_1$$

 


Little change in spectrum of input at the output


Analysis of Delta-Sigma ADC

(big benefit is noise shaping)
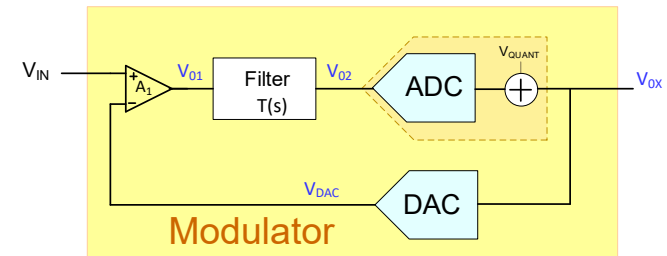
$$V_{OX} = \frac{I_{01}A_1}{s + I_{01}A_1} V_{IN} + V_{QUANT} \frac{s}{s + I_{01}A_1}$$



Combined effects

 


Remaining quantization noise can be dramatically reduced by a low-pass digital filter following modulator with band-edge around f_{3dB}

The low-pass digital filter would have little effect on the signal band


Analysis of Delta-Sigma ADC

(big benefit is noise shaping)
 
$$V_{OX} = \frac{T(s)A_1}{1 + T(s)A_1} V_{IN} + V_{QUANT} \frac{1}{1 + T(s)A_1}$$



 
Signal and Noise Transfer Function Magnitudes



- A more selective filter (of higher order) would shape the noise even more and affect the passband even less if band edges are coincident
- Ideal low-pass and high-pass filters with coincident band edges followed by digital filter at output would allow nearly complete removal of the quantization noise !!

Second-order Delta-Sigma ADC

(big benefit is noise shaping)

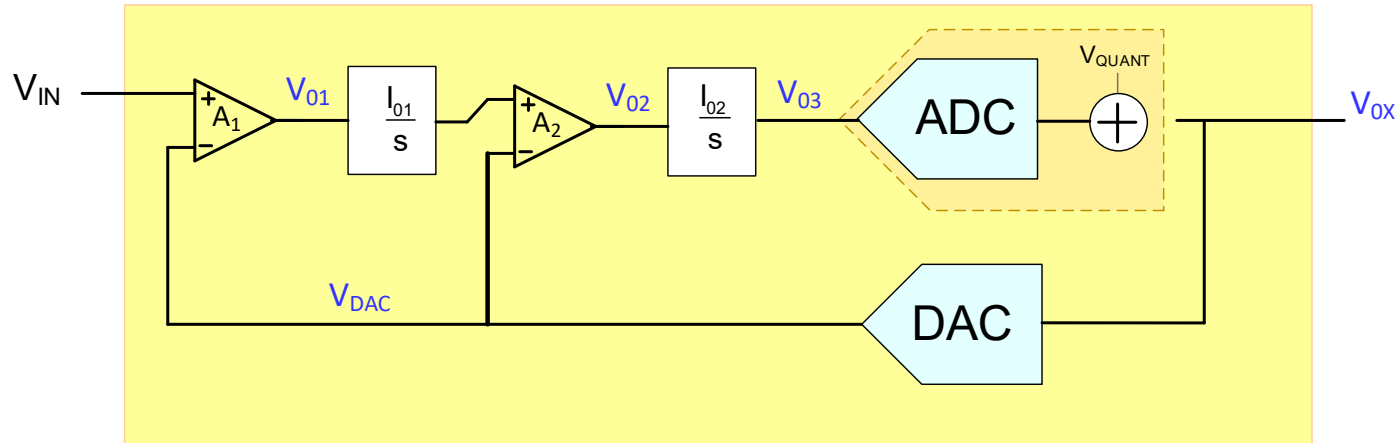

Modulator only shown with two integrators

$$V_{01} = A_1 (V_{IN} - V_{DAC})$$

$$V_{02} = A_2 \left[\frac{I_{01}}{s} V_{01} - V_{DAC} \right]$$

$$V_{03} = \frac{I_{02}}{s} V_{02}$$

$$V_{OX} = V_{03} + V_{QUANT}$$


$$V_{DAC} = V_{OX}$$

Solving, obtain


$$V_{OX} = \frac{I_{01} I_{02} A_1 A_2}{s^2 + s I_{02} A_2 + I_{01} I_{02} A_1 A_2} V_{IN} + \frac{s^2}{s^2 + s I_{02} A_2 + I_{01} I_{02} A_1 A_2} V_{QUANT}$$

Higher-order Delta-Sigma ADC

(big benefit is noise shaping)

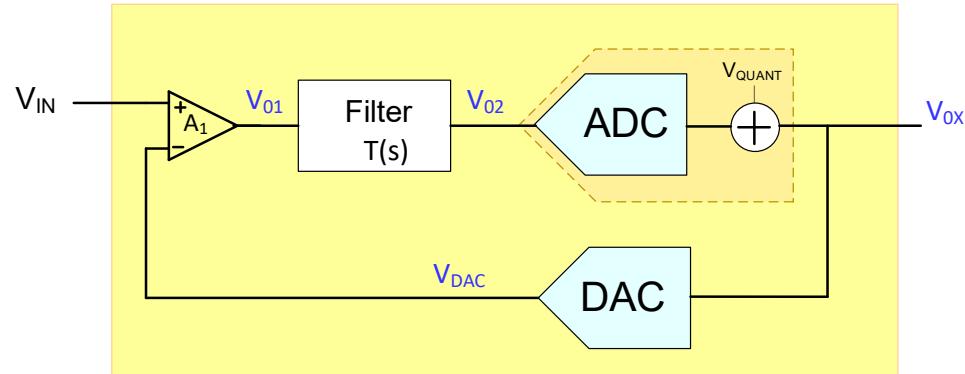

 Much sharper transition between noise pass-band and signal stop band



From SLYT423 by Texas Instruments (author Bonnie Baker)

Baker reported TI used up to 6th order filters in SLYT423

Behavioral Modeling of Switched-Capacitor Sigma-Delta Modulators

Piero Malcovati, *Member, IEEE*, Simona Brigati, *Member, IEEE*, Fabrizio Francesconi, *Member, IEEE*,
Franco Maloberti, *Fellow, IEEE*, Paolo Cusinato, and Andrea Baschiroto, *Senior Member, IEEE*

SC Circuits often used for Modulator

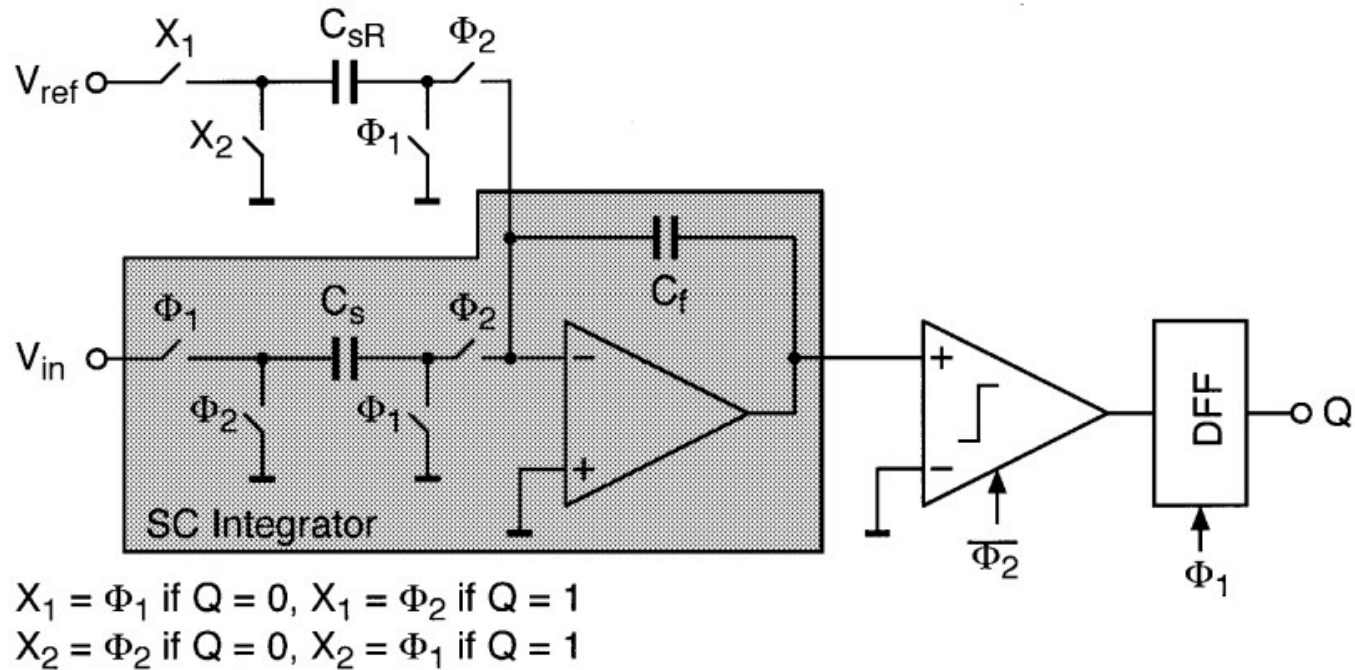


Fig. 1. Schematic of an SC first-order $\Sigma\Delta$ modulator.

Over-sampled $\Delta\Sigma$ ADC)

Oversampling Alone:

$$SNR = 6.02n + 1.76 + 10\log(OSR)$$

0.5 bits/octave

Oversampling and First-Order Modulator:

$$SNR = 6.02n + 1.76 - 5.17 + 30\log(OSR)$$

1.5 bits/octave



OSR		Log(OSR)
128		2.1
64		1.8
32		1.5
16		1.2
8		0.9

Oversampling and Second-Order Modulator:

$$SNR = 6.02n + 1.76 - 12.9 + 50\log(OSR)$$

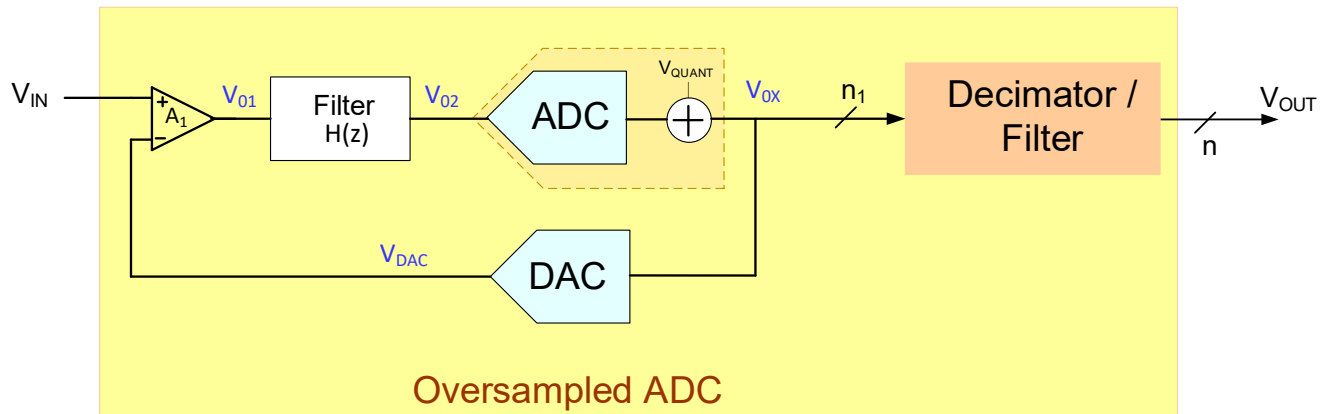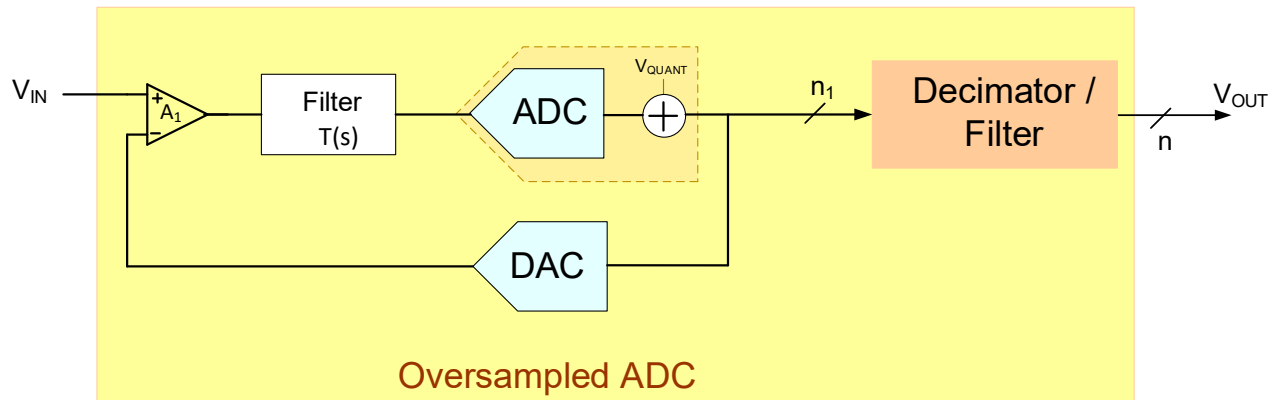
2.5 bits/octave

Continuous-Time vs Discrete-Time Delta-Sigma ADC



- Formulation was developed in the continuous-domain
- How does this map to a discrete-time domain?

s-domain to z-domain transformations

 

Goal: Obtain $H(z)$ so that $T(s) = H(z)|_{z=e^{sT}}$

Since can't achieve this goal, would like to map imaginary axis to unit circle and map stable filters to stable filters

consider: $z = e^{sT}$

$$z = e^{sT} \cong \sum_{i=0}^{\infty} \frac{1}{i!} (sT)^i$$

$$z = \sum_{i=0}^{\infty} \frac{1}{i!} (sT)^i \cong 1 + sT$$

Termed the Forward Euler transformation

$$s = \frac{z-1}{T}$$


If normalized to $T=1$, $s = z - 1$

(big benefit is noise shaping)

Consider using an integrator for $T(s)$ normalized to 1 rad/sec band edge

Discrete-Time Delta-Sigma ADC (normalized)

(big benefit is noise shaping)

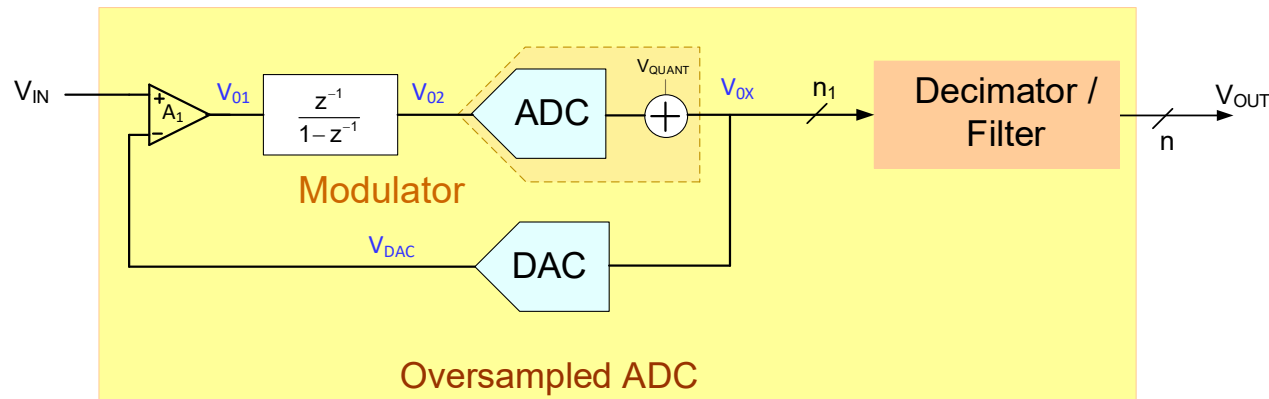

$$H(z) = \frac{1}{z-1} = \frac{z^{-1}}{1-z^{-1}}$$

$$V_{OX} = \frac{1}{z-1+1} V_{IN} + V_{QUANT} \frac{z-1}{z-1+1} = z^{-1} V_{IN} + V_{QUANT} (1-z^{-1})$$



Note V_{IN} is low-pass filtered and V_{QUANT} is high-pass filtered and both are first-order with the same poles

$$STF_{NORM} = z^{-1}$$

$$NTF_{NORM} = 1-z^{-1}$$

Discrete-Time Delta-Sigma ADC (normalized)



(big benefit is noise shaping)

 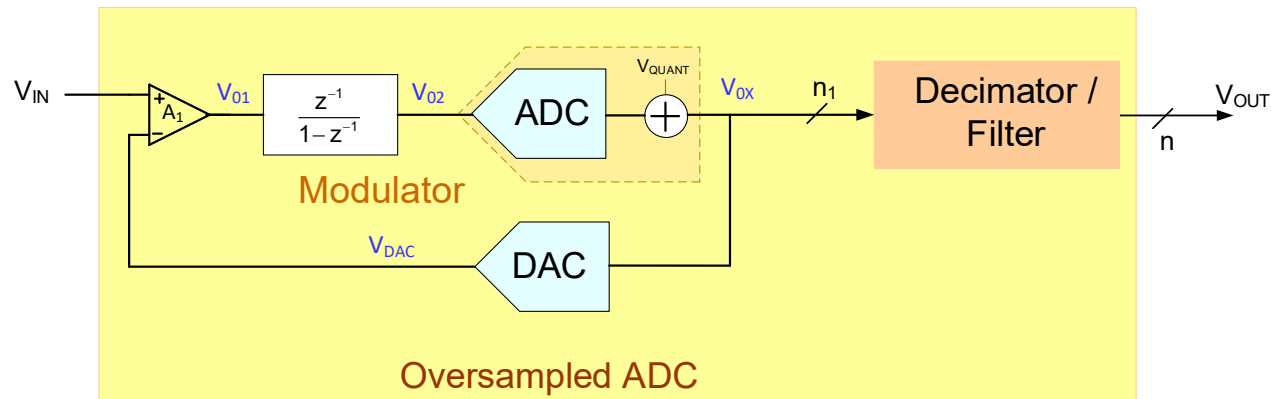

Spectral density of shaped quantization noise can be increased at higher frequencies with the high-pass noise filter



But steep cutoff in the digital filter output will still remove the high-frequency quantization noise

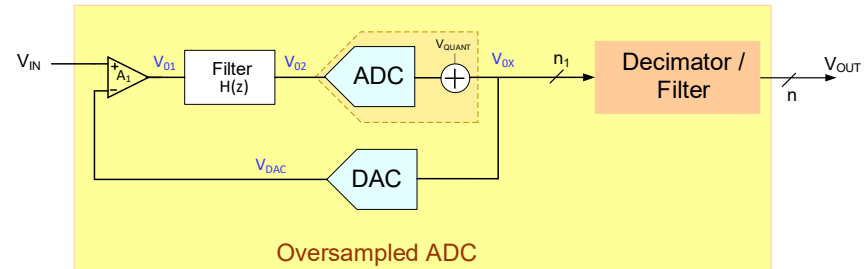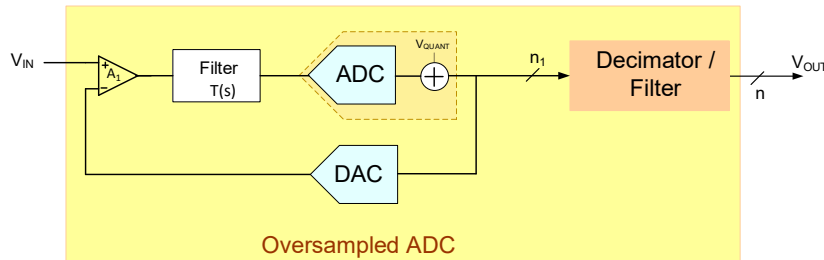Continuous-Time vs Discrete-Time Over-sampled Delta-Sigma ADCs



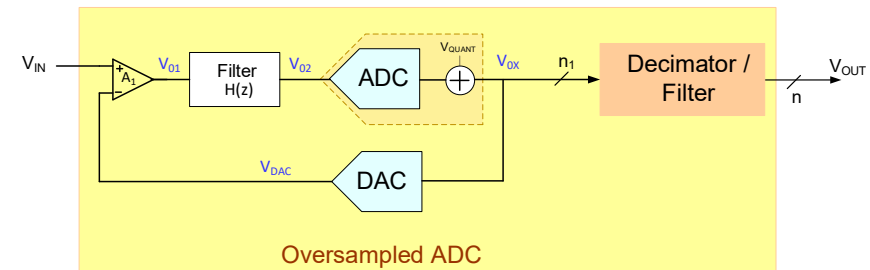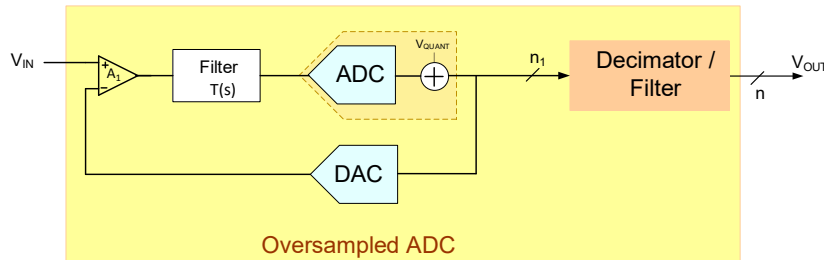1. Input sampling errors for DT structures are never recovered
2. Nonlinearity of switches of concern in DT structures
3. No good switches in bipolar processes
4. Clock jitter adversely affects performance of discrete-time structures
5. Slew-rate requirements higher for DT structures and signal swings generally higher too
6. DT structures need additional headroom for switch control
7. CT structures can operate at lower supply voltages and lower power levels
8. Linearity of filter of increased concern in CT structures (particularly when using gm-C filters)
9. Transient response of DAC of increased concern in CT structures


Peculiar Issues with Over-sampled Delta-Sigma ADCs



1. Increasing resolution of DAC, OSR, and filter order (in the right way) all offer potential for increasing ENOB
2. Output is not completely repeatable for a given input
3. Some dc inputs will introduce idle tones or spectral lines in the output
4. Dynamic range requirements for both the filter and the ADC may be high to avoid saturation
5. Stability analysis may be challenging and require extensive time-domain simulations (because of nonlinearities, analytically not practical)
6. OSDS-ADCs are insensitive to errors in ADC though ADC errors may increase the amount of over-range required for filter
7. Although nonlinearity in the signal-band of the filter is important, it is usually not difficult to obtain
8. Nonlinearity errors of the DAC directly introduce nonlinearity in the OSDS-ADC so excellent DAC linearity is generally required
9. Dead zones (input regions with no output) may exist

Higher-order Delta-Sigma ADC

(big benefit is noise shaping)

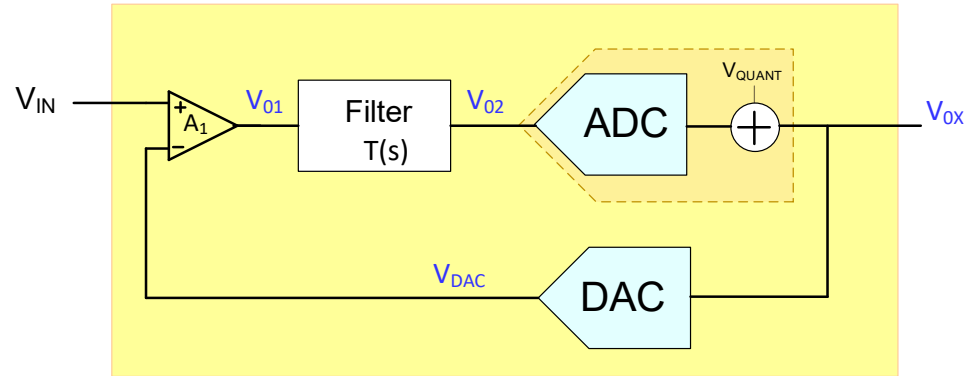

Excellent Material on Delta-Sigma ADCs

“How delta-sigma ADCs work (Part 1 and Part 2)”

Author: Bonnie Baker

SLYT423 Revised Sept 2016 by Texas Instruments

Demystifying Delta-Sigma ADCs

 


Figure 1. FFT diagram of a multi-bit ADC with a sampling frequency F_s .

Oversampling by K Times

 


Figure 2. FFT diagram of a multi-bit ADC with a sampling frequency kF_s .

- Removal of high-frequency quantization noise
- But noise is still a problem in signal band

 


Figure 3. Effect of the digital filter on the noise bandwidth.

Noise reduction (noise shaping) in signal band

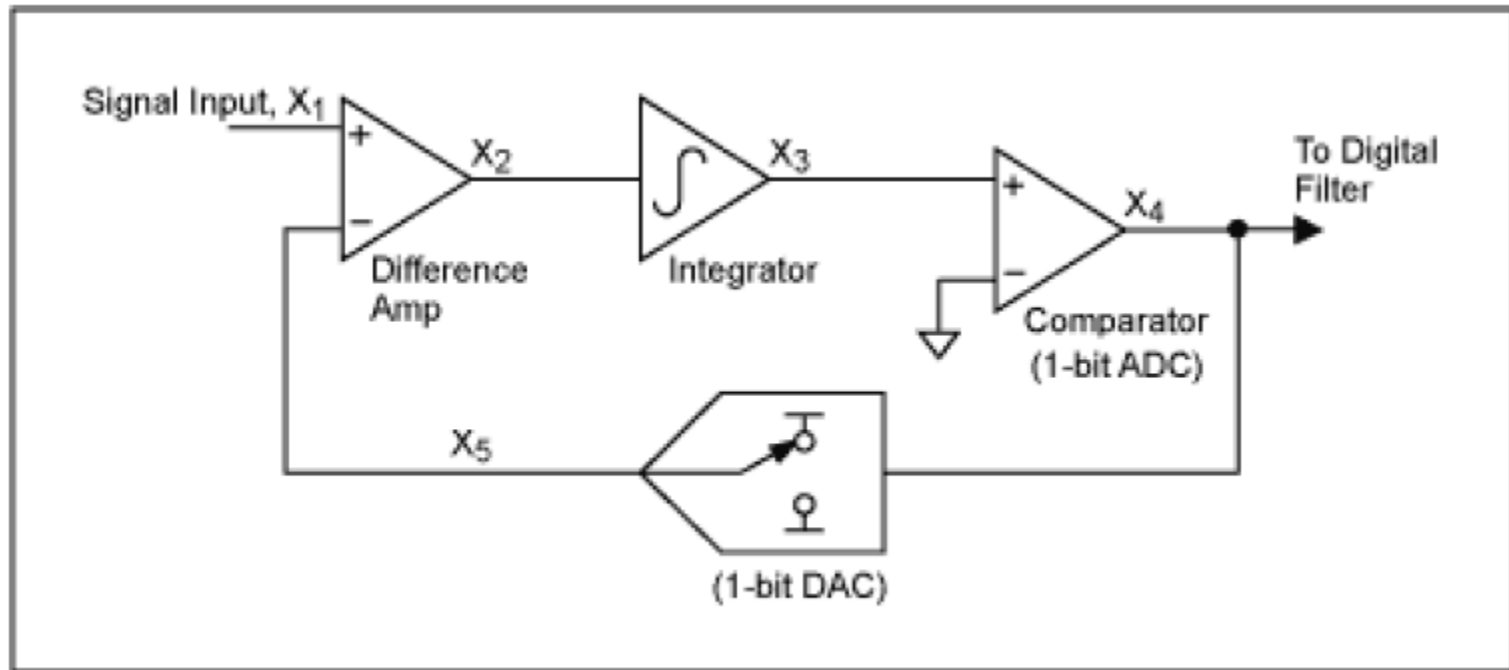


Figure 4. Block diagram of a sigma-delta modulator.

 


Figure 5. Affect of the integrator in the sigma-delta modulator.

Filtering the Shaped Noise

 


Figure 6. Effect of the digital filter on the shaped noise.


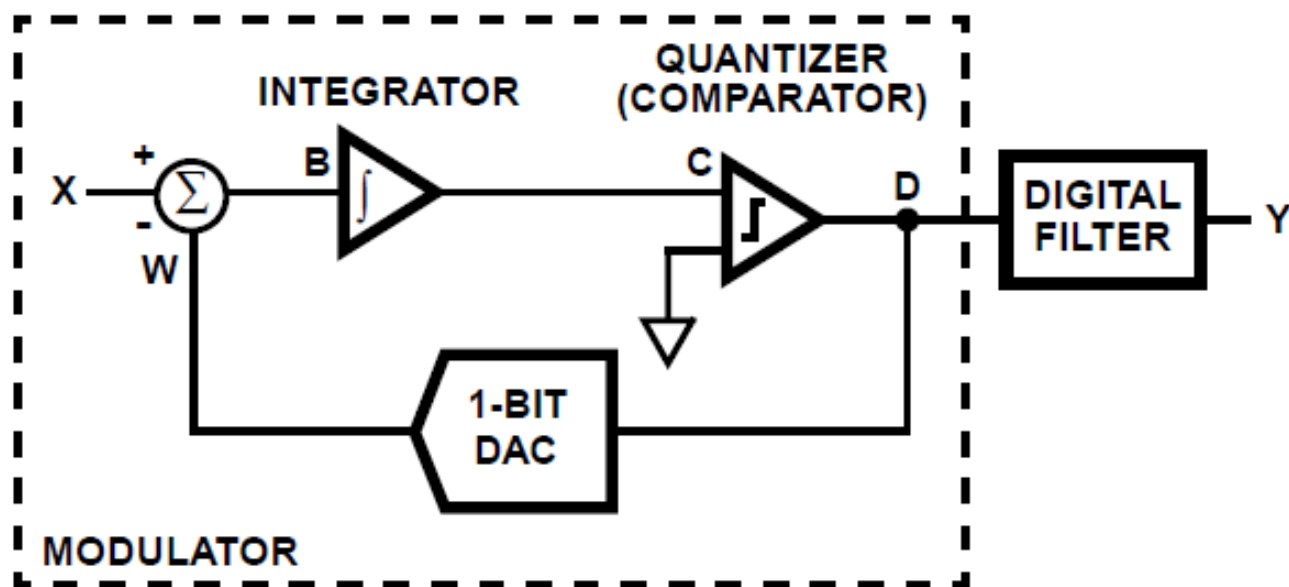


FIGURE 1. FIRST ORDER SIGMA DELTA ADC BLOCK DIAGRAM

SECOND-ORDER SIGMA-DELTA ADC

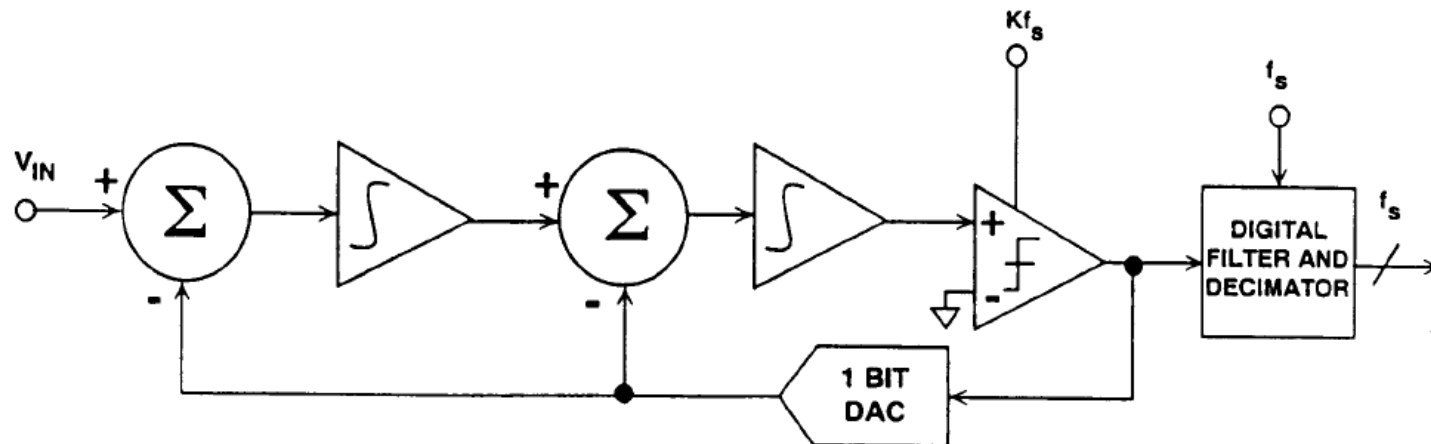

Behavioral Modeling of Switched-Capacitor Sigma-Delta Modulators

Piero Malcovati, *Member, IEEE*, Simona Brigati, *Member, IEEE*, Fabrizio Francesconi, *Member, IEEE*,
Franco Maloberti, *Fellow, IEEE*, Paolo Cusinato, and Andrea Baschirotto, *Senior Member, IEEE*

SC Circuits often used for Modulator

 


Fig. 1. Schematic of an SC first-order $\Sigma\Delta$ modulator.

Over-sampled $\Delta\Sigma$ ADC)

Oversampling Alone:

$$SNR = 6.02n + 1.76 + 10\log(OSR)$$

0.5 bits/octave

Oversampling and First-Order Modulator:

$$SNR = 6.02n + 1.76 - 5.17 + 30\log(OSR)$$


1.5 bits/octave


Oversampling and Second-Order Modulator:


$$SNR = 6.02n + 1.76 - 12.9 + 50\log(OSR)$$

 2.5 bits/octave


Noise reduction (noise shaping) in signal band



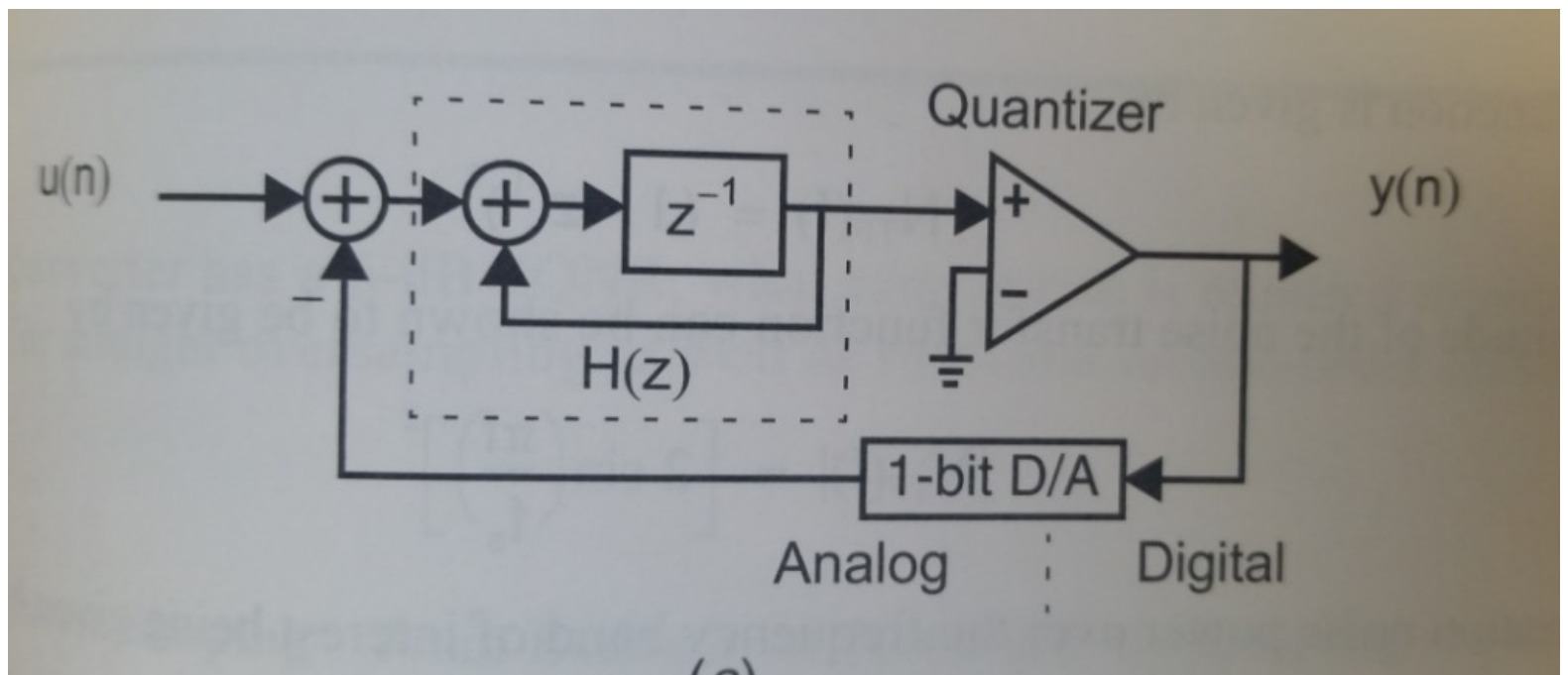

 

(a)

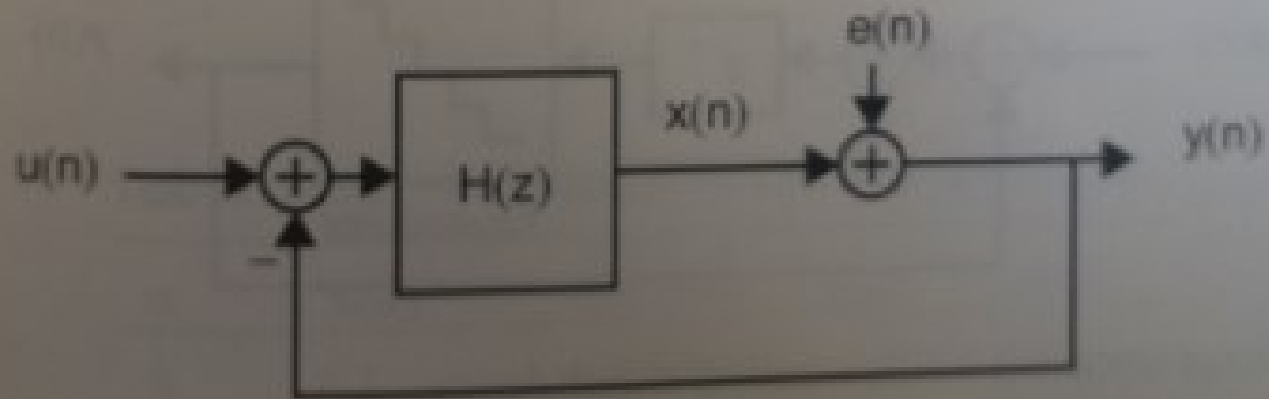



(b)


$$S_{TF}(z) = \frac{Y(z)}{U(z)} = \frac{1/(z-1)}{1 + 1/(z-1)} = z^{-1}$$

$S_{TF}(z)$, is given by

$$N_{TF}(z) = \frac{Y(z)}{E(z)} = \frac{1}{1 + 1/(z-1)} = (1 - z^{-1})$$

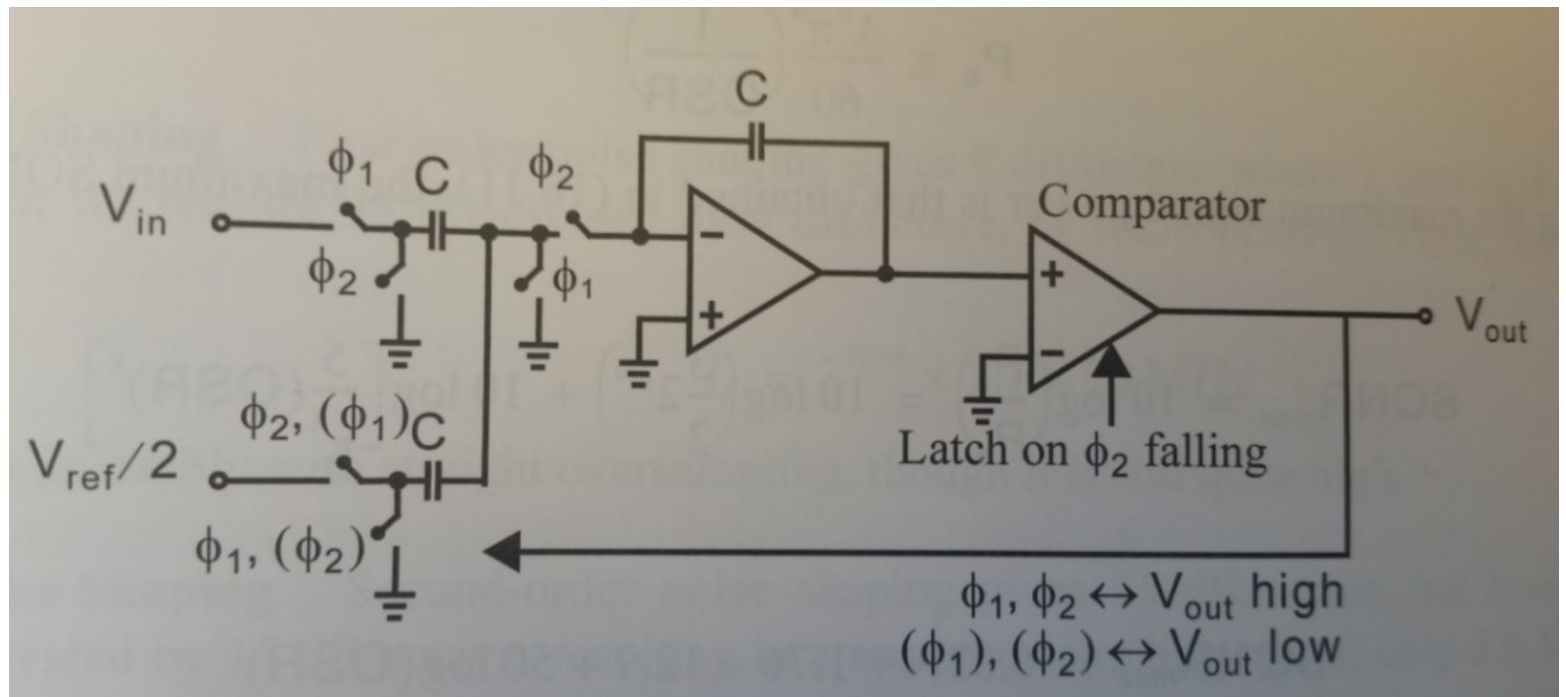

 

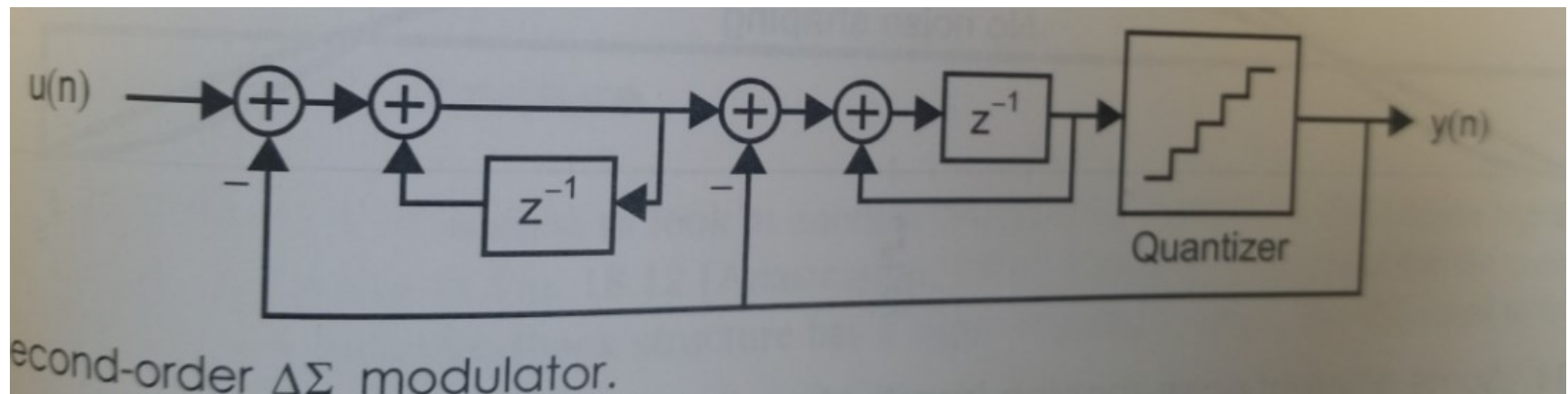

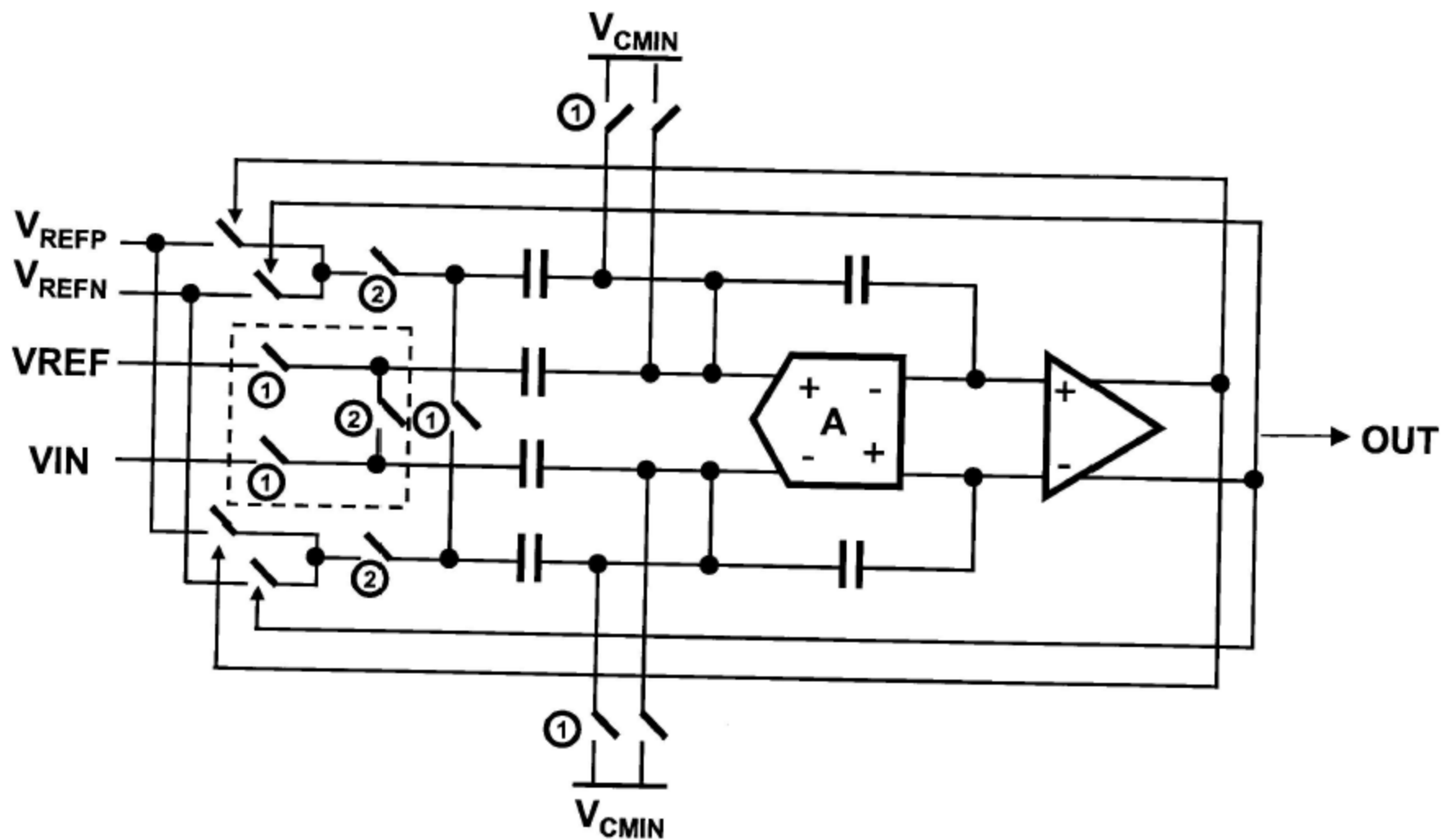


Figure 2: 1st Order Delta-Sigma ADC



Stay Safe and Stay Healthy !

End of Lecture 27


Layout Issues for Matching Critical Components

Layout plays a critical role in determining performance of most matching-critical circuits and is of particular concern in most data converters


Layout Issues for Matching Critical Components

- Matching is dominantly determined by local random variations and gradient effects – both of which are random variables at the design phase
- Mismatch induced by local random variations almost entirely determined by area allocated to matching-critical components
 - Good statistical analysis tools available for predicting mismatch induced by local random variations (Monte-Carlo analysis in SPECTRE)
 - Analytical formulations often (but not always) available for predicting effects of local random variations
 - At some resolution level, area required to maintain noise performance may dominate that required for matching due to local random variations
- Mismatch induced by gradient effects strongly affected by layout
 - Gradient effects will usually dominate mismatch concerns if not managed
 - No good statistical analysis tools available for predicting mismatch induced by local random variations
 - Area allocation often plays no direct role in managing gradients though total span may play a role and may increase with area
 - Conventional-wisdom used to guide layout to manage gradient effects
 - With good layout techniques, gradient effects can usually be reduced below level of local random variations

 Local Random Variations and Gradients in MOS Devices



n-channel MOSFET

 


n-channel MOSFET

Impurity density or layer thicknesses vary linearly through the channel

Model and design parameters vary throughout channel and thus the corresponding equivalent lumped model parameters will vary from device to device

Gradient and Local Random Effect

 

Gradient Effects : Locally Appear Linear

- Magnitude and Direction of Gradients are random
- Highly Correlated over Short Distances


Local Random Effects :
Vary Locally With No
Correlation

- **Both contribute to mismatch**
- **Both are random variables**
- **If not managed, both can cause large mismatch effects**
- **Strategies for minimizing their effects are different**
- **Will refer to the local random effects as “random” and the random gradient effects as “gradient” effects**

From a previous lecture

Resistor Characterization Concepts

 Assume lithography is perfect, no gradient effects, and no contact resistance



$R_{\square}(x, y)$: Sheet resistance at (x, y)

Most authors assume: $R_{\square EQ} = \frac{\int R_{\square}(x, y) dx dy}{A}$ $A = WL$

$$R_{Z_1 Z_2} = R_{\square EQ} \frac{L}{W}$$

We will make this same assumption

Model Parameter Variation

Define p to be a process parameter that varies with lateral position throughout the region defined by the channel of the transistor.

Almost Theorem:

If $p(x,y)$ varies throughout a two-dimensional region, then

$$p_{EQ} = \frac{1}{A} \int_A p(x,y) dx dy$$

Parameters such as V_T , μ and C_{OX} vary throughout a two-dimensional region

Local random variations introduce a random component in device model parameters which are uncorrelated but for ideally matched devices they are identically distributed

e.g. $V_{TEQi} = V_{TN} + V_{TRi}$

V_{TRi} and V_{TRj} due to local random variations are uncorrelated for $i \neq j$ but if ideally matched they are identically distributed

Model Parameter Variation



Define p to be a process parameter that varies with lateral position throughout the region defined by the channel of the transistor.

Almost Theorem:

If $p(x,y)$ varies throughout a two-dimensional region, then

$$p_{EQ} = \frac{1}{A} \int_A p(x,y) dx dy$$

Why almost?

  

Current densities dramatically different

Model Parameter Variation

Define p to be a process parameter that varies with lateral position throughout the region defined by the channel of the transistor.


Almost Theorem:

If $p(x,y)$ varies throughout a two-dimensional region, then

$$p_{EQ} = \frac{1}{A} \int_A p(x,y) dx dy$$

Why almost?

Reason 2

 

$$I_{D1} = \frac{\mu C_{OX} W}{2L} (V_{GS} - V_{TH1})^2$$

$$I_{D2} = \frac{\mu C_{OX} W}{2L} (V_{GS} - V_{TH2})^2$$


$$I_{DEQ} = \frac{\mu C_{OX} W}{2L} (V_{GS} - V_{THEQ})^2$$

$$I_{DEQ} = \frac{\mu C_{OX} 2W}{2L} \left[V_{GS}^2 - V_{GS} (V_{TH1} + V_{TH2}) + \frac{V_{TH1}^2 + V_{TH2}^2}{2} \right]$$

$$I_{DEQ} = \frac{\mu C_{OX} W}{2L} \left[(V_{GS} - V_{TH1})^2 + (V_{GS} - V_{TH2})^2 \right] \neq \frac{\mu C_{OX} W_{EQ}}{2L_{EQ}} \left(V_{GS} - \frac{V_{TH1} + V_{TH2}}{2} \right)^2$$

Models Inherently Different

Model Parameter Variation

 

$$p_{EQ} = \frac{1}{A} \int_A p(x, y) dx dy$$

Common Centroid Layouts

Define p to be a process parameter that varies linearly with lateral position throughout the region defined by the channel of the transistor.

Almost Theorem:

If $p(x,y)$ varies linearly throughout a two-dimensional region, then

$$p_{EQ} = \frac{1}{A} \int_A p(x,y) dx dy$$

Gradient effects cause parameters such as V_T , μ and C_{OX} to vary approximately linearly throughout a two-dimensional region as long as the “span” of the region is not too large

The direction and magnitude of gradients are random variables but are correlated and identical for closely-placed devices

Common Centroid Layouts


Almost Theorem:

If $p(x,y)$ varies linearly throughout a two-dimensional region, then $p_{EQ}=p(x_0,y_0)$ where x_0,y_0 is the geometric centroid to the region.

If a parameter varies linearly throughout a two-dimensional region, it is said to have a linear gradient.

Many parameters have a dominantly linear gradient over rather small regions but large enough to encompass layouts where devices are ideally matched

Common Centroid Layouts

 

(x_0, y_0) is geometric centroid

$$p_{EQ} = \frac{1}{A} \int_A p(x, y) dx dy$$

If $p(x, y)$ varies linearly in any direction, then the theorem states

$$p_{EQ} = \frac{1}{A} \int_A p(x, y) dx dy = p(x_0, y_0)$$

Common Centroid Layouts

Definition: A layout of two devices is termed a common-centroid layout if both devices have the same geometric centroid

Almost Theorem:

If $p(x,y)$ varies linearly throughout a two-dimensional region, then if two devices have the same centroid, the lateral-variable parameters are matched !

Note: This is true independent of the magnitude and direction of the gradient!



Almost Theorem:

If a common-centroid layout is used for the matching-critical part of an operational amplifier, the lateral-variable parameters (e.g. V_{TH} , μ , C_{OX}) will introduce no mismatch!

Common-centroid layouts almost always used for matching-critical components to eliminate linear gradients of critical parameters !



But local random variations will still affect matching even if gradient effects are eliminated

  Recall parallel combinations of transistors equivalent to a single transistor of appropriate W,L




Centroids of Segmented Geometries

× Denotes Geometric Centroid

  


 Common Centroid of Multiple Segmented Geometries




If these are layouts of gates of two transistors with two segments, M_1 and M_2 have common centroids. They are thus termed common-centroid layouts

 Common Centroid of Multiple Segmented Geometries



Common Centroid Layouts

 

Common centroid layouts widely (almost always) used where matching of devices or components is critical because these layouts will cancel all first-order gradient effects


Applies to resistors, capacitors, transistors and other components

Always orient all devices in the same way

Keep common centroid for interconnects, diffusions, and all features

Often dummy devices placed on periphery to improve matching !

 Common Centroid Layout Surrounded by Dummy Devices



More than one ring of dummy devices may be required


Dummy devices may be used for other purposes as well

e.g. bypass capacitors for capacitor arrays or binary-weighted LSB devices for segmented structures



Fingers and Multipliers

- Multiple fingers use shared diffusions
- Multipliers refer to multiple copies of transistors with individual drains and sources

 
Important to match orientation if overall device matching is required




Multiplier = 2

  

Fingers = 2

 

Fingers = 2

 


$L_{\text{eff}}=L, W_{\text{eff}}=2W$

$L_{\text{eff}}=2L, W_{\text{eff}}=W$

Fingers and Multipliers

Alternate Orientations

 

If matching is important, orientations should be identical



Stay Safe and Stay Healthy !

End of Lecture 27