

# EE 505

## Lecture 9

- Statistical Circuit Modeling

Review from last lecture

Recall from previous lecture

# How important is statistical analysis?

Example: 7-bit FLASH ADC with R-string DAC

Assume R-string is ideal,  $V_{REF}=1V$  and  $V_{OS}$  for each comparator must be at most  $\pm \frac{1}{2}$  LSB

Case 1

Standard deviation is 5mV

$$P_{COMP} = 0.565$$


$$Y_{ADC} = 3.2 \cdot 10^{-32}$$

Case 2

Standard deviation is 1mV

$$P_{COMP} = 0.999904$$

$$Y_{ADC} = 0.988$$

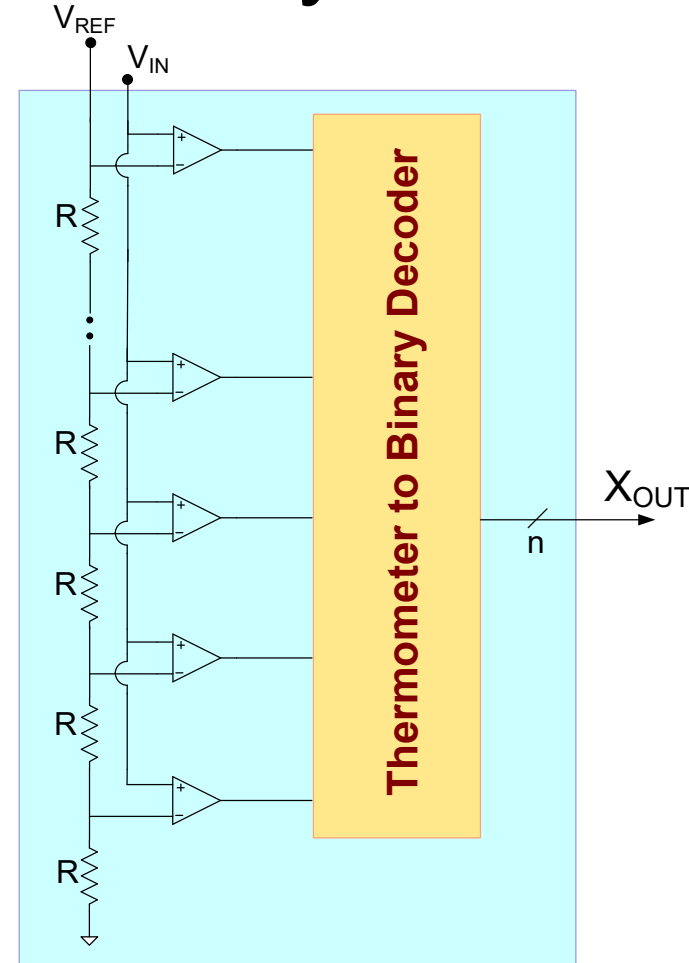

**Statistics play a key role in the performance and consequently yield of a data converter**

# Statistical Analysis Strategy

Will first focus on statistical characterization of resistors, then extend to capacitors and transistors

Every resistor  $R$  can be expressed as

$$R = R_N + R_{RP} + R_{RW} + R_{RD} + R_{RGRAD} + R_{RL}$$

where  $R_N$  is the nominal value of the resistor and the remaining terms are all random variables

$R_{RP}$ : Random process variations

$R_{RW}$ : Random wafer variations

$R_{RD}$ : Random die variations

$R_{RGRAD}$ : Random gradient variations

$R_{RL}$ : Local Random Variations

- Data Converters (ADCs and DACs) are ratiometric devices and performance often dominated by ratiometric device characteristics (e.g. matching)
- Many other AMS functions are dependent upon dimensioned parameters and often not dependent upon matching characteristics

# Statistical Analysis Strategy

$$R = R_N + R_{RP} + R_{RW} + R_{RD} + R_{RGRAD} + R_{RL}$$

$R_{RP}$ : Random process variations

$R_{RW}$ : Random wafer variations

$R_{RD}$ : Random die variations

$R_{RGRAD}$ : Random gradient variations

$R_{RL}$ : Local Random Variations

$$\sigma_{RP} \gg \sigma_{RW} \gg \sigma_{RD}$$


- All variables globally uncorrelated
- For good common-centroid layouts gradient effects can be neglected
- Local random variations often much smaller than  $R_{RP}$ ,  $R_{RW}$ , and  $R_{RD}$  though not necessarily
- Area dominantly determines  $\sigma_{RL}$ , but area has little effect on the other variables
- At the resistor-level on a die,  $R_{RP}$ ,  $R_{RW}$  and  $R_{RD}$  highly correlated thus cause no mismatch
- Major challenge in data converter design is managing  $R_{RL}$  effects
- All zero mean and approximately Gaussian (truncated)
- For dimensioned performance characteristics (e.g. band edge of filter),  $R_{RP}$ ,  $R_{RW}$  and  $R_{RD}$  are dominant and  $R_{RGRAD}$  and  $R_{RL}$  typically secondary

For notational convenience, assume  $R = R_N + R_R$

$R_N$  includes  $R_{RP}$ ,  $R_{RW}$  and  $R_{RD}$ ,  $R_{GRAD}$  neglected,  $R_R = R_{RL}$
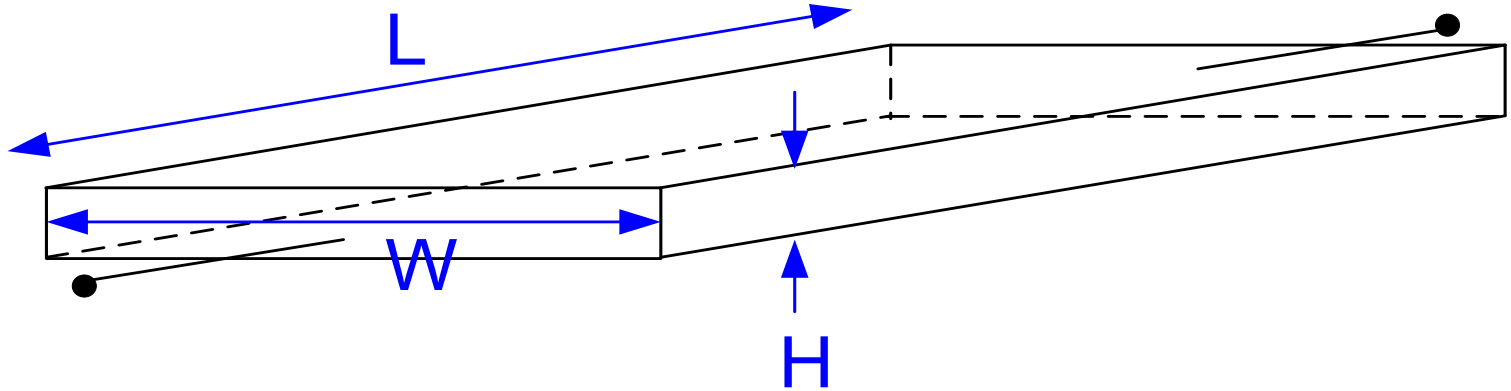
# Resistor Characterization

Resistors are generally made of thin films of conductive or semiconductor materials



Generally  $h$  is very small compared to  $L$  and  $W$


Films are often characterized by Sheet Resistance

In the ideal case

$$R = \rho \left( \frac{1}{H} \cdot \frac{L}{W} \right) = R_{\square} \left( \frac{L}{W} \right)$$
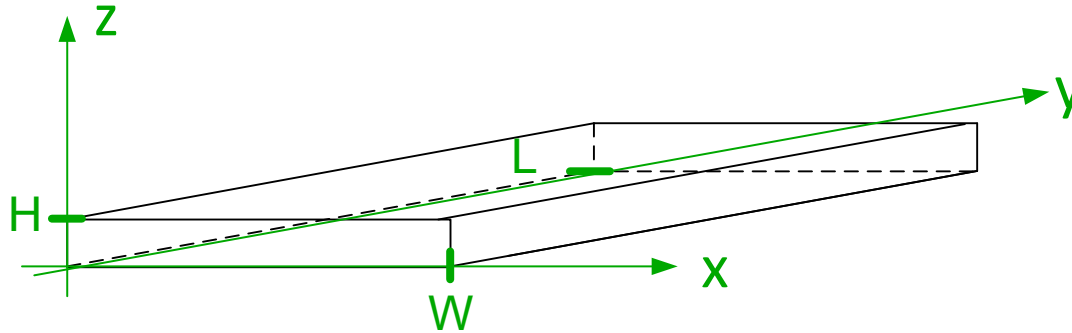
# Resistor Characterization

Resistors are generally made of thin films of conductive or semiconductor materials



Film Characterized by Resistivity :  $\rho(x,y,z)$

Films are often characterized by Sheet Resistance  $R_{\square}(x,y) = \frac{\rho(x,y,z)}{H(x,y)}$


Ideally  $\rho(x,y,z)$  is independent of position as is  $R_{\square}(x,y)$

In the ideal case  $R = \rho \left( \frac{1}{H} \bullet \frac{L}{W} \right) = R_{\square} \left( \frac{L}{W} \right)$

# Resistor Characterization

Resistors are generally made of thin films of conductive or semiconductor materials

Ideally




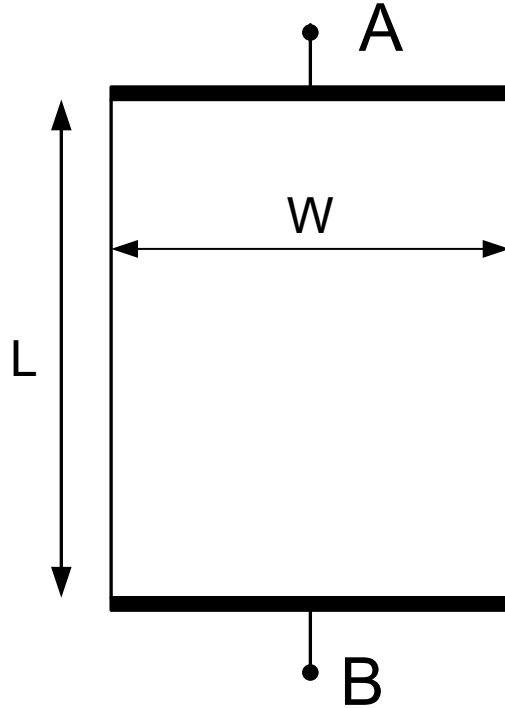


$$R = R_{\square} \left( \frac{L}{W} \right)$$

$$R_{\square} = \frac{\rho}{h}$$

# Resistor Characterization

Ideally

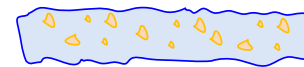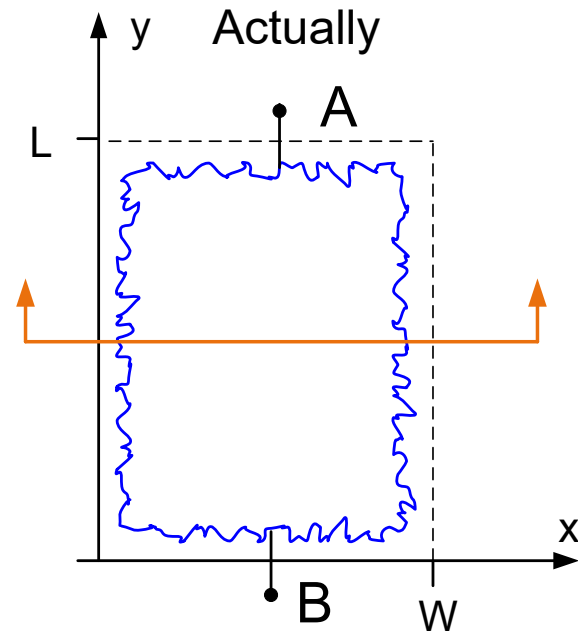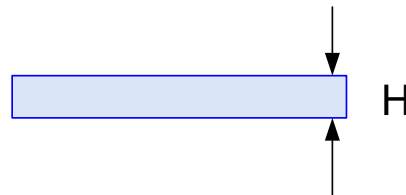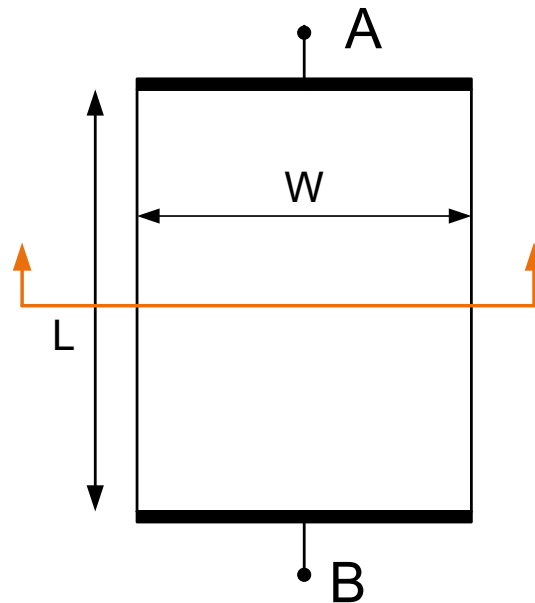


- Boundary of resistor varies with position
- $\rho(x,y,z)$  varies with position
- Thickness ( $H(x,y)$ ) varies with position
- Properties of resistor vary with position and temperature


# Resistor Characterization

• B

Ideally

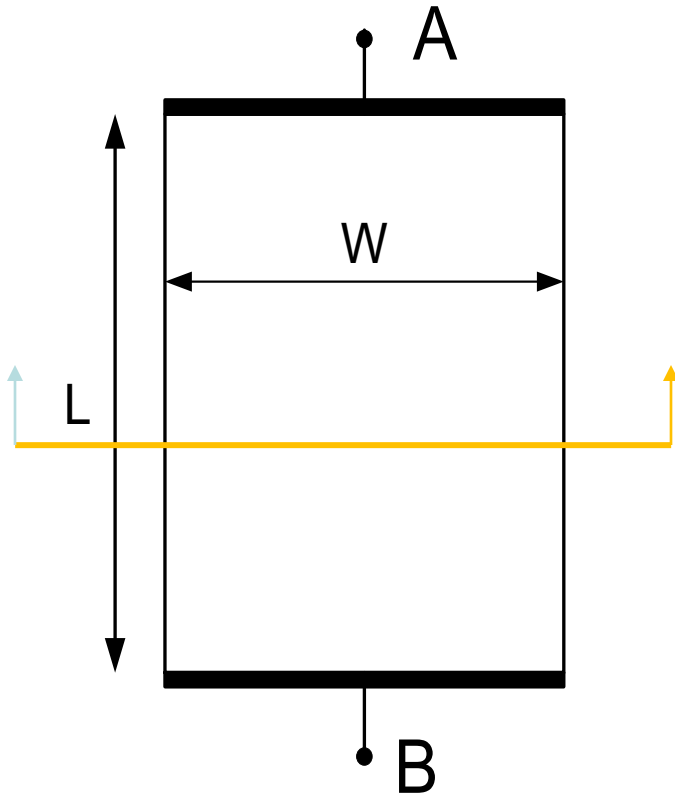


Actually

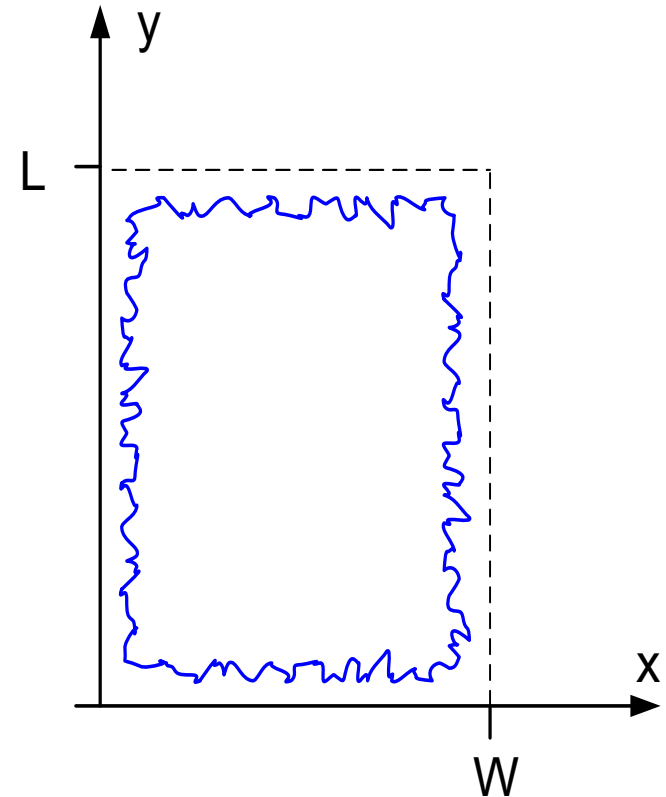

Boundary of resistor varies  
 $\rho(x,y,z)$  varies with position

These variations will define  $R_R$
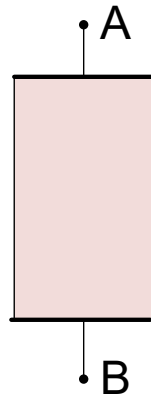
# Consider the following resistor circuits



$$R = R_N + R_R$$

Statistical  
Model


mean  $\mu_{R_R} = 0$

standard deviation  $\sigma_{R_R}$

Distribution: Truncated Gaussian

$$N \sim (0, \sigma_{R_R})$$

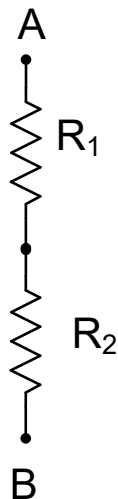Series Resistor Connection (of two nominally identical devices)



$$R_1 = R_N + R_{R1}$$

$$R_2 = R_N + R_{R2}$$

$$R_{Ser2} = 2R_N + R_{R1} + R_{R2}$$

Compare the standard deviation of the resistance of the series combination with that of a single resistor

Consider the following well-known Theorem:

Theorem: If  $X_1, \dots, X_n$  are uncorrelated random variables and  $a_1, \dots, a_n$  are real numbers, then the random variable  $Y$  defined by

$$Y = \sum_{i=1}^n a_i X_i$$

has mean and variance given by

$$\mu_Y = \sum_{i=1}^n a_i \mu_i$$

$$\sigma_Y = \sqrt{\sum_{i=1}^n (a_i \sigma_i)^2}$$

where  $\mu_i$  and  $\sigma_i$  are the mean and variance of  $X_i$  for  $i=1, \dots, n$ .

# Series Resistor Connection

(of nominally identical devices)

$$\left. \begin{aligned} R_1 &= R_N + R_{R1} \\ R_2 &= R_N + R_{R2} \end{aligned} \right\}$$

$$R_{Ser2} = 2R_N + R_{R1} + R_{R2}$$

From Theorem  $\sigma_{Ser2} = \sqrt{2}\sigma_{R_R}$



$$N \sim (0, \sqrt{2}\sigma_{R_R})$$

Extending to n-resistors that are nominally identical

$$R_{Ser n} = nR_N + \sum_{k=1}^n R_{Rk}$$

$$\sigma_{Ser n} = \sqrt{n}\sigma_{R_R}$$

$$N \sim (0, \sqrt{n}\sigma_{R_R})$$

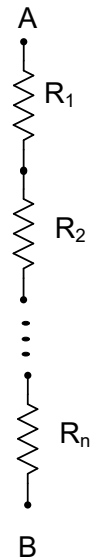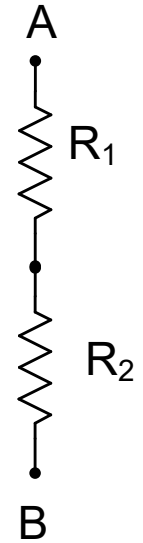

# Summary of Results

Structure	Nominal Resistance	Standard Deviation	Normalized Standard Deviation
R	$R_N$	$\sigma_{R_R}$	
Ser nR	$nR_N$	$\sqrt{n}\sigma_{R_R}$	

Note increasing the resistance by a factor of n increased the standard deviation by  $\sqrt{n}$

# Normalized Statistical Characterization

$$\sigma_{\frac{R}{R_N}} = ?$$

From previous theorem:

For single resistor R

$$\sigma_{\frac{R}{R_N}}^2 = \frac{1}{R_N^2} \sigma_{R_R}^2 \quad \rightarrow \quad \sigma_{\frac{R}{R_N}} = \frac{1}{R_N} \sigma_{R_R}$$

For series connection of n ideally identical resistors (identical in both value and structure)

$$R_{EQ} = nR_N + \sum_{k=1}^n R_{Rk}$$

$$R_{EQNor m} = \frac{R_{EQ}}{nR_N} = \frac{nR_N + \sum_{k=1}^n R_{Rk}}{nR_N} = 1 + \frac{1}{n} \sum_{k=1}^n \frac{R_{Rk}}{R_N}$$

$$\sigma_{\frac{R_{EQ}}{nR_N}}^2 = \frac{1}{n^2} \sum_{k=1}^n \frac{1}{R_N^2} \sigma_{R_R}^2 = \frac{1}{n^2} \sum_{k=1}^n \sigma_{\frac{R_R}{R_N}}^2 = \frac{1}{n} \sigma_{\frac{R_R}{R_N}}^2 \quad \rightarrow \quad \sigma_{\frac{R_{EQ}}{nR_N}} = \frac{1}{\sqrt{n}} \sigma_{\frac{R_R}{R_N}}$$

Note increasing the resistance by a factor of n dropped the normalized standard deviation by  $\sqrt{n}$

# Summary of Results

Structure	Nominal Resistance	Standard Deviation	Normalized Standard Deviation
R	$R_N$	$\sigma_R = \sigma_{R_R}$	$\sigma_{\frac{R_R}{R_N}}$
Ser nR	$nR_N$	$\sqrt{n}\sigma_{R_R}$	$\frac{1}{\sqrt{n}}\sigma_{\frac{R_R}{R_N}}$

Note increasing the resistance by a factor of n (identical in both value and structure) increased the standard deviation by  $\sqrt{n}$

Note increasing the resistance by a factor of n decreased the normalized standard deviation by  $\sqrt{n}$

# Parallel Resistor Connection


$$\left. \begin{aligned} R_1 &= R_N + R_{R1} \\ R_2 &= R_N + R_{R2} \end{aligned} \right\}$$

$$R_{Par2} = \frac{(R_N + R_{R1})(R_N + R_{R2})}{2R_N + R_{R1} + R_{R2}}$$

$$R_{Par2} = \frac{R_N^2 + R_N(R_{R1} + R_{R2}) + R_{R1}R_{R2}}{2R_N + R_{R1} + R_{R2}}$$

$$R_{Par2} \cong \frac{R_N^2}{2R_N} \frac{1 + \frac{R_{R1} + R_{R2}}{R_N}}{1 + \frac{R_{R1} + R_{R2}}{2R_N}}$$
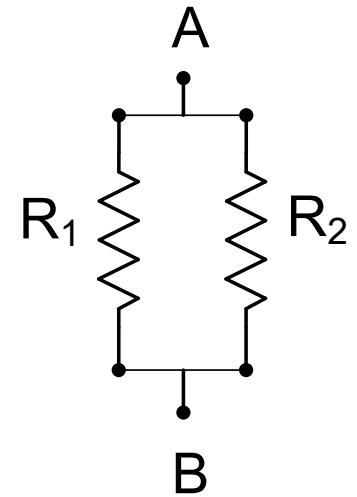
$$R_{Par2} \cong \frac{R_N}{2} \frac{1 + \frac{R_{R1} + R_{R2}}{R_N}}{1 + \frac{R_{R1} + R_{R2}}{2R_N}}$$




- The random variable  $R_{Par2}$  is highly nonlinear in  $R_{R1}$  and  $R_{R2}$
- Some very good approximations of  $R_{Par2}$  can be made that linearize the expression
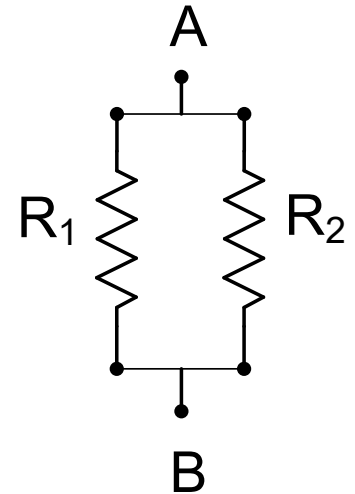
# Parallel Resistor Connection

$$\left. \begin{aligned} R_1 &= R_N + R_{R1} \\ R_2 &= R_N + R_{R2} \end{aligned} \right\}$$

$$R_{Par2} \cong \frac{R_N}{2} \frac{1 + \frac{R_{R1} + R_{R2}}{R_N}}{1 + \frac{R_{R1} + R_{R2}}{2R_N}}$$



Recall that for  $x$  small,

$$\frac{1}{1+x} \cong 1-x$$

Thus


$$R_{Par2} \cong \frac{R_N}{2} \left( 1 + \frac{R_{R1} + R_{R2}}{R_N} \right) \left[ 1 - \frac{R_{R1} + R_{R2}}{2R_N} \right] \cong \frac{R_N}{2} + \frac{1}{4} R_{R1} + \frac{1}{4} R_{R2}$$

From Theorem (identical in both value and structure)

$$\sigma_{R_{Par2}}^2 = \frac{1}{16} \sigma_{R_R}^2 + \frac{1}{16} \sigma_{R_R}^2 \cong \frac{1}{8} \sigma_{R_R}^2 \quad \longrightarrow \quad \sigma_{R_{Par2}} \cong \frac{1}{\sqrt{8}} \sigma_{R_R}$$

For  $n$  in parallel (identical in both value and structure), it follows that
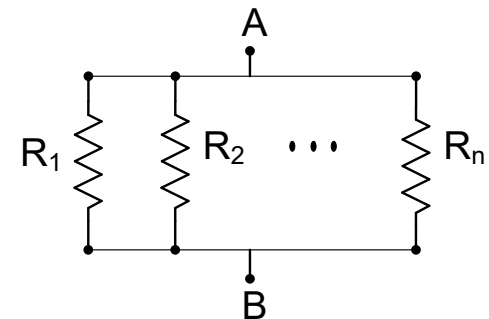
$$\sigma_{R_{Par n}} \cong \frac{1}{n^{3/2}} \sigma_{R_R}$$




# Parallel Resistor Connection

Consider normalized variance

$$R_{Par-2} = \frac{R_N}{2}$$
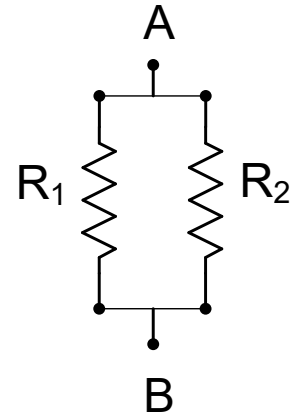
$$\frac{R_{Par2}}{R_{Par2-Norm}} \cong 1 + \frac{1}{2} \frac{R_{R1}}{R_N} + \frac{1}{2} \frac{R_{R2}}{R_N}$$




From Theorem

$$\sigma^2_{\frac{R_{Par2}}{R_{Par2-Norm}}} \cong \frac{1}{4} \sigma^2_{\frac{R_{R1}}{R_N}} + \frac{1}{4} \sigma^2_{\frac{R_{R2}}{R_N}} = \frac{1}{2} \sigma^2_{\frac{R_{R1}}{R_N}}$$

$$\sigma_{\frac{R_{Par2}}{R_{Par2-Norm}}} \cong \frac{1}{\sqrt{2}} \sigma_{\frac{R_{R1}}{R_N}}$$

And for n in parallel (identical in both value and structure)  $R_{Par-n} = \frac{R_N}{n}$
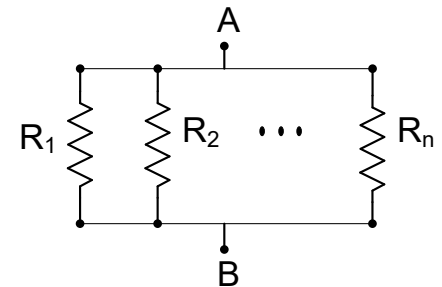
$$\sigma_{\frac{R_{Par}}{R_{Par-Norm}}} \cong \frac{1}{\sqrt{n}} \sigma_{\frac{R_R}{R_N}}$$



Note decreasing the resistance by a factor of n dropped the standard deviation by  $\sqrt{n}$

# Summary of Results

(for ideally identical in both value and structure)

Structure	Nominal Resistance	Standard Deviation	Normalized Standard Deviation
R	$R_N$	$\sigma_R = \sigma_{R_R}$	$\frac{\sigma_{R_R}}{R_N}$
Ser nR	$nR_N$	$\sqrt{n}\sigma_{R_R}$	$\frac{1}{\sqrt{n}}\sigma_{\frac{R_R}{R_N}}$
Par nR	$\frac{R_N}{n}$	$\frac{1}{n^{3/2}}\sigma_{R_R}$	$\frac{1}{\sqrt{n}}\sigma_{\frac{R_R}{R_N}}$


Note increasing or decreasing the resistance by a factor of n decreased the normalized standard deviation by  $\sqrt{n}$

Note increasing the area by a factor of n decreased the normalized standard deviation by  $\sqrt{n}$

What is the relationship between resistance, area, and standard deviation?

## Consider parallel/series combination of 4 nominally identical resistors

(identical in both value and structure)

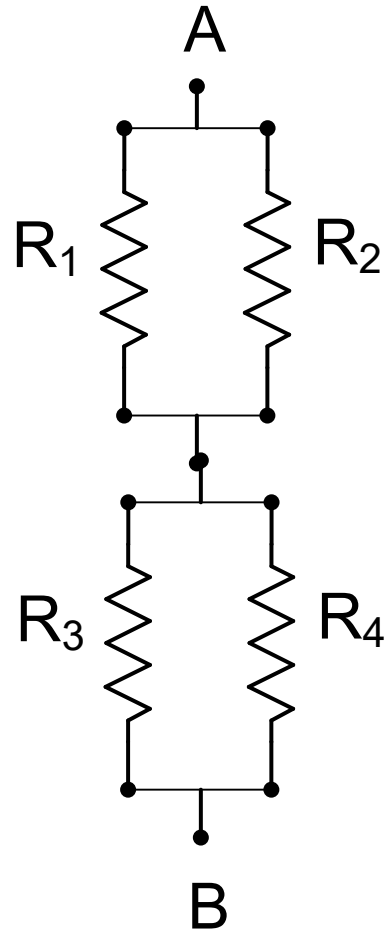

$$R_{EQ} = R_N$$

$$\sigma_{R_{EQ}} = \frac{\sigma_R}{2}$$

$$\sigma_{\frac{R_{EQ}}{R_N}} = \frac{1}{2} \sigma_{\frac{R}{R_N}}$$

Note making no change in the resistance reduced the standard deviation by 2

Note increasing the area by a factor of 4 dropped the standard deviation by 2


# Summary of Results

Structure	Nominal Resistance	Standard Deviation	Normalized Standard Deviation
R	$R_N$	$\sigma_{R_R}$	$\frac{\sigma_{R_R}}{R_N}$
Ser nR	$nR_N$	$\sqrt{n}\sigma_{R_R}$	$\frac{1}{\sqrt{n}} \frac{\sigma_{R_R}}{R_N}$
Par nR	$\frac{R_N}{n}$	$\frac{1}{n^{3/2}} \sigma_{R_R}$	$\frac{1}{\sqrt{n}} \frac{\sigma_{R_R}}{R_N}$
Ser 2R	$2R_N$	$\sqrt{2}\sigma_{R_R}$	$\frac{\sigma_{R_R}}{R_N} / \sqrt{2}$
Par 2R	$\frac{R_N}{2}$	$\frac{\sigma_{R_R}}{\sqrt{8}}$	$\frac{\sigma_{R_R}}{R_N} / \sqrt{2}$
Ser 4R	$4R_N$	$2\sigma_{R_R}$	$\frac{\sigma_{R_R}}{R_N} / 2$
Par 4R	$\frac{R_N}{4}$	$\frac{\sigma_{R_R}}{8}$	$\frac{\sigma_{R_R}}{R_N} / 2$
Par/Ser 4R	$R_N$	$\frac{\sigma_{R_R}}{2}$	$\frac{\sigma_{R_R}}{R_N} / 2$




# Observation:

- In all cases, increasing the area by a factor of  $n$  decreases the normalized standard deviation by  $\sqrt{n}$
- These structures were all configured to have the same nominal current density. Without the equal current density requirement, results would differ

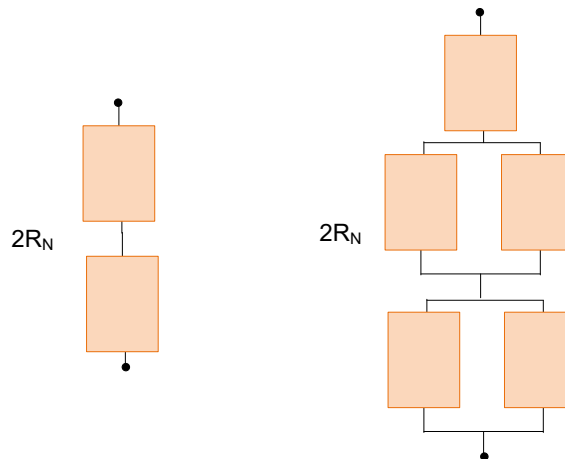Example: Same nominal resistance but different current density and different variances



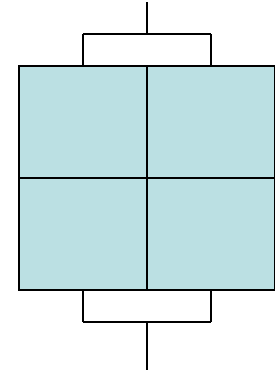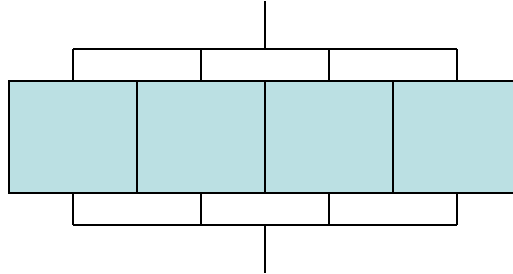 Have considered in previous examples the following scenarios




- Current density is uniform in each structure
- Aspect ratio plays no role in normalized performance
- Resistance value plays no role in normalized performance
- Only factor in normalized performance is area
- For a given resistance, each factor of 2 reduction in  $\sigma$  requires a factor of 4 increase in area

## Key Implications:

If yield of a data converter is determined by matching performance, then every bit increment in performance will require at least a factor of 2 reduction in  $\sigma$  and correspondingly a factor of 4 increase in the area for the matching critical components if the same yield is to be obtained.
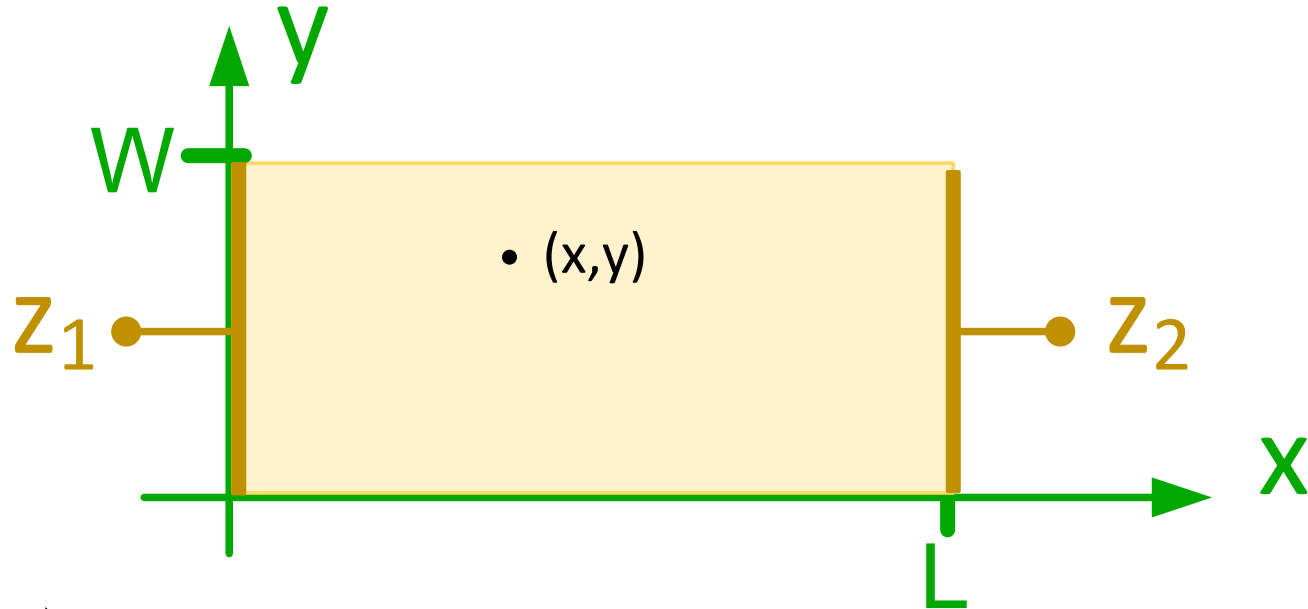
# Formalize Resistor Characterization Concepts

Assume lithography is perfect, no gradient effects, and no contact resistance



$R_{\square}(x, y)$ : Sheet resistance at  $(x, y)$


Most authors assume: 
$$R_{\square EQ} = \frac{\int R_{\square}(x, y) dx dy}{A} \quad A = WL$$

$$R_{Z_1 Z_2} = R_{\square EQ} \frac{L}{W}$$

We will make this same “standard” assumption
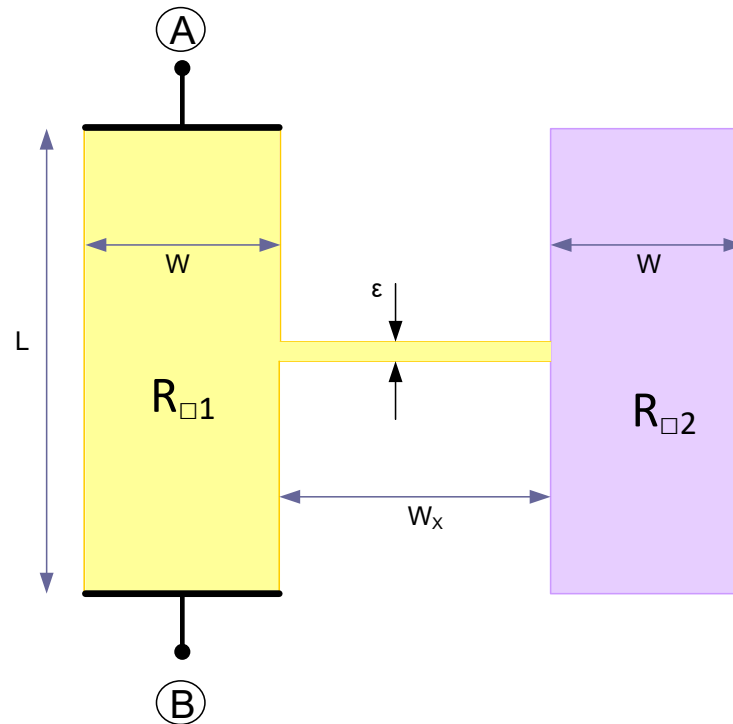
# Counter example showing limitations of standard assumption

Assume sheet resistance constant in yellow region of value  $R_{\square 1}$  and constant in purple region of value  $R_{\square 2}$



If  $\epsilon$  is small and  $W_x$  large  $R_{\square EQ} \cong R_{\square 1} \longrightarrow R_{AB} \cong R_{\square 1} \left( \frac{L}{W} \right)$

$$\text{but } R_{\square EQ} = \frac{\int R_{\square}(x,y) dx dy}{A} \underset{\text{model}}{\cong} \frac{R_{\square 1} + R_{\square 2}}{2}$$


If  $R_{\square 1}$  and  $R_{\square 2}$  are not equal, then  $R_{\square EQ} \neq R_{\square 1}$

Though errors can be big, in practical processes for structures with identical current density throughout, the assumptions are probably pretty good !
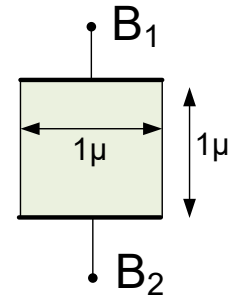
# Consider a square reference resistor of width $1\mu\text{m}$

Define REF to be the resistance of the reference resistor.  
Since it is square of area  $1\mu^2$ , the equivalent sheet resistance of the reference resistor is equal to REF

Assume the standard deviation of this reference resistor, due to local random variations, is  $\sigma_{\text{REF}}$




Consider now a resistor of length L and width W

Define the equivalent sheet resistance of this resistor:  $R_{\square\text{EQ}}$

$R_{\square\text{EQ}}$  is a random variable with a nominal value of  $R_{\square\text{N}}$  and standard deviation that satisfies the expression
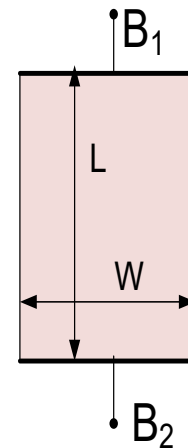
$$\sigma_{R_{\square\text{EQ}}}^2 = \frac{\sigma_{\text{REF}}^2}{W \bullet L} = \frac{\sigma_{\text{REF}}^2}{A}$$



$$A = W \bullet L$$

It follows that the value of the resistor R is given by the expression

$$R = R_{\square\text{EQ}} \bullet \frac{L}{W}$$

Thus

$$\sigma_R^2 = \left( \frac{L}{W} \right)^2 \bullet \sigma_{R_{\square\text{EQ}}}^2 \qquad \sigma_R^2 = \left( \frac{L}{W} \right)^2 \bullet \frac{\sigma_{\text{REF}}^2}{W \bullet L} = \sigma_{\text{REF}}^2 \bullet \frac{L}{W^3}$$

Consider a resistor of width  $W$  and length  $L$

$$\sigma_R^2 = \left( \frac{L}{W} \right)^2 \cdot \frac{\sigma_{REF}^2}{W \cdot L} = \sigma_{REF}^2 \cdot \frac{L}{W^3}$$

$$A = W \cdot L$$

Note  $\sigma_R$  is dependent on resistance value

Consider now the normalized resistance  $\frac{R}{R_N}$

where  $R_N = R_{\square N} \frac{L}{W}$

It follows that

$$\sigma_{\frac{R}{R_N}}^2 = \left( \frac{1}{R_N^2} \right) \left( \sigma_{REF}^2 \frac{L}{W^3} \right) = \left( \frac{W^2}{R_{\square N}^2 L^2} \right) \left( \sigma_{REF}^2 \frac{L}{W^3} \right) = \left( \frac{1}{WL} \right) \left[ \frac{\sigma_{REF}^2}{R_{\square N}^2} \right]$$

The term on the right in [ ] is the ratio of two process parameters so define the process parameter  $A_R$  by the expression  $A_R = \frac{\sigma_{REF}}{R_{\square N}}$


$A_R$  is more convenient to use than both  $\sigma_{REF}$  and  $R_{\square N}$

Thus the normalized resistance is given by the expression

$$\sigma_{\frac{R}{R_N}}^2 = \frac{A_R^2}{WL} = \frac{A_R^2}{A}$$


Note  $\sigma_{R/RN}$  is not dependent on resistance value

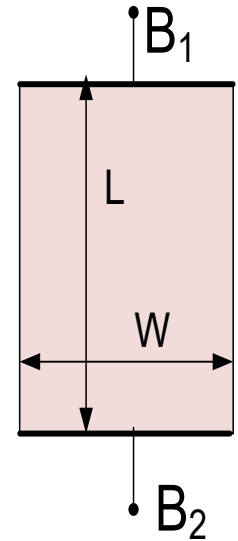Will term  $A_R$  the “Pelgrom parameter” (though Pelgrom only presented results for MOS devices)


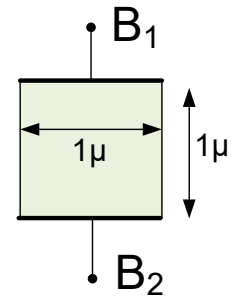
# How can $A_R$ be obtained?

Recall:  $\sigma_{\frac{R}{R_N}} = \frac{A_R}{\sqrt{A}}$  where  $A_R = \frac{\sigma_{REF}}{R_{\square N}}$



1. Obtain  $A_R$  from a PDK
2. Build a test structure to obtain  $A_R$

## Recall:

Let  $x$  be a random variable with mean  $\mu$  and standard deviation  $\sigma$  and let  $\vec{X} = \{x_i\}_{i=1}^n$  be  $n$  samples of the random variable  $x$ . Define  $\mu_s$  to be the mean of the sample and  $\sigma_s$  to be the standard deviation of the sample. Then the statistic  $\mu_s$  is an unbiased estimator of  $\mu$  and the statistic  $\sqrt{\frac{n}{n-1}}\sigma_s$  is an unbiased estimator of  $\sigma$

The mean and variance of a large sample of a random variable are unbiased estimators of the mean and variance of the random variable itself

# Strategy 1

$$A_R = \frac{\sigma_{REF}}{R_{\square N}}$$



1. Create a test circuit with a large number,  $n$ , of  $1\mu \times 1\mu$  resistors
2. Measure  $R_1, \dots, R_n$
3. Calculate the sample standard deviation and sample mean as estimators

$$\begin{array}{l} \hat{\sigma}_{REF} = \sigma_{SAMPLE} \\ \hat{R}_{\square N} = \mu_{SAMPLE} \end{array} \quad \longrightarrow \quad \hat{A}_R \cong \frac{\sigma_{SAMPLE}}{\mu_{SAMPLE}}$$

Is this a good strategy for obtaining  $A_R$ ?

No !

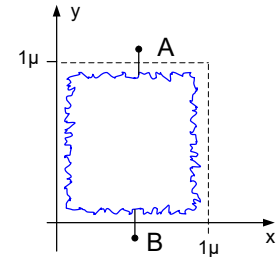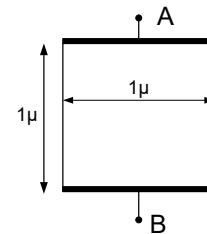- Fringe effects will increase variance
- Gradient effects will skew the results
- Die-level and wafer-level variations will skew the results
- Contact resistances will skew results



## Strategy 2

$$A_R = \frac{\sigma_{REF}}{R_{\square N}}$$

Create n large area test structures

$$\hat{R}_{\square N} \cong \frac{W}{L} \mu_{SAMPLE}$$

$$\sigma_R^2 = \sigma_{REF}^2 \bullet \frac{L}{W^3}$$


$$\hat{\sigma}_{REF} = \sigma_{R\_sample} \sqrt{\frac{W^3}{L}}$$

$\mu_{SAMPLE}$  is the mean resistance of the sample and  $\sigma_{R\_sample}$  is the standard deviation of the sample


$$\hat{A}_R = \frac{\hat{\sigma}_{REF}}{\hat{R}_{\square N}} = \frac{\sigma_{R\_SAMPLE} \sqrt{LW}}{\mu_{SAMPLE}}$$

Is this a good strategy for obtaining  $A_R$ ?

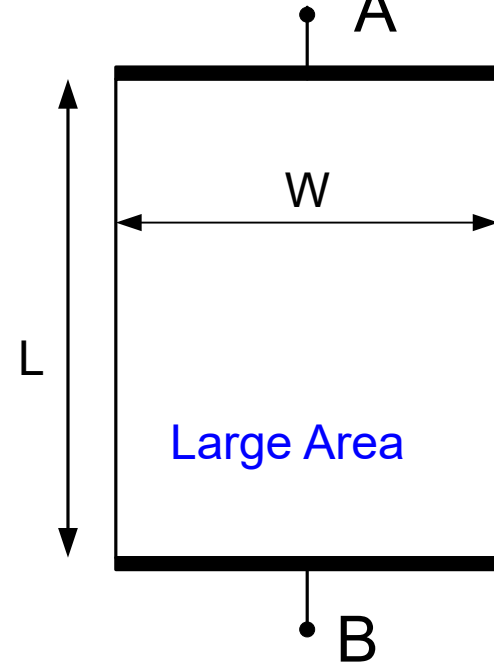- Significantly reduces the boundary and contact resistance associated with the  $1\mu \times 1\mu$  structure
- If devices are not really close, other random variations will skew results that are supposed to characterize local random variations



# Gradient Effects

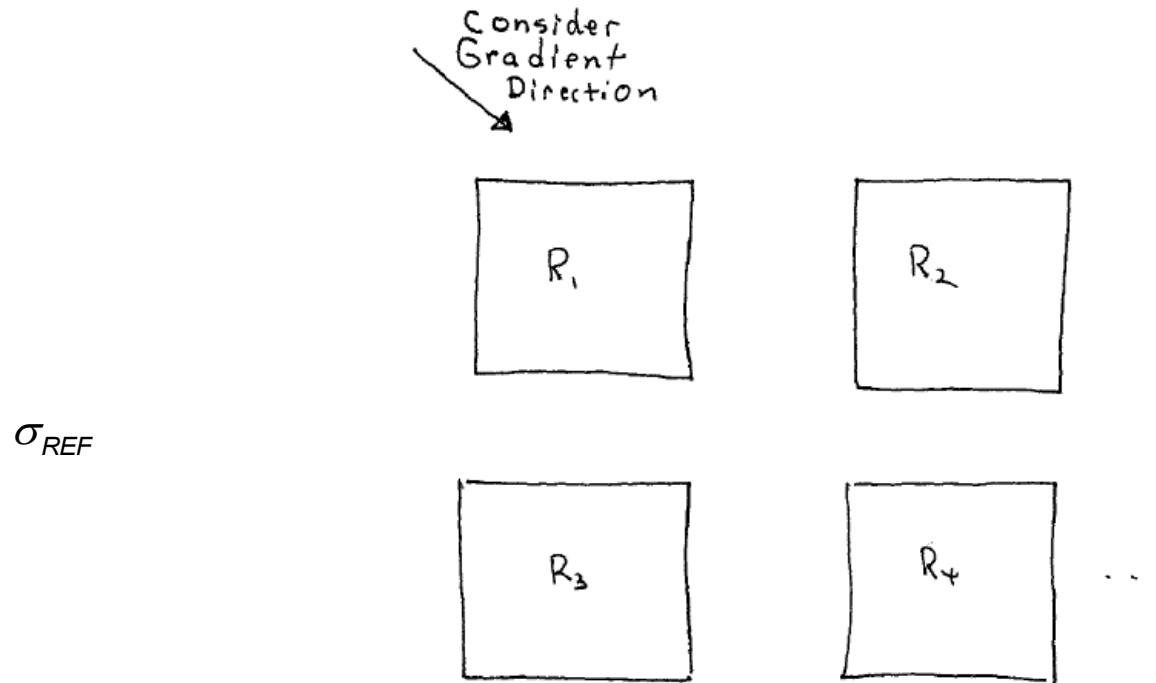

gradient effects will dramatically skew  $A_p$  extraction !

- need large test structures that are insensitive to gradient effects !
- consider a two-resistor test cell

How does the ratio matching of two resistors relate to the standard deviation of a single resistor?

$$\begin{array}{c} \text{---} \\ | \\ \text{---} \end{array} R \rightarrow \sigma_R \text{ or } \sigma_{\frac{R}{R_N}}$$

$$\begin{array}{c} \begin{array}{cc} \begin{array}{c} \text{---} \\ | \\ \text{---} \end{array} R_1 & \begin{array}{c} \text{---} \\ | \\ \text{---} \end{array} R_2 \\ R_{1N} = R_{2N} = R_N \end{array} & \begin{aligned} \Theta &= \frac{R_1 - R_2}{R_N} \\ &= \frac{R_N + R_{1R} - R_N - R_{2R}}{R_N} \end{aligned} \end{array}$$

$$\Theta = \frac{R_{1R} - R_{2R}}{R_N}$$

$$\therefore \sigma_{\Theta}^2 = \frac{1}{R_N^2} (\sigma_{R_{1R}}^2 + \sigma_{R_{2R}}^2)$$

$$\sigma_{\Theta}^2 = \frac{2\sigma_{R_R}^2}{R_N^2}$$




$$\sigma_{\frac{\Delta R}{R_N}}^2 = 2\sigma_{\frac{R}{R_N}}^2$$

## Strategy 3
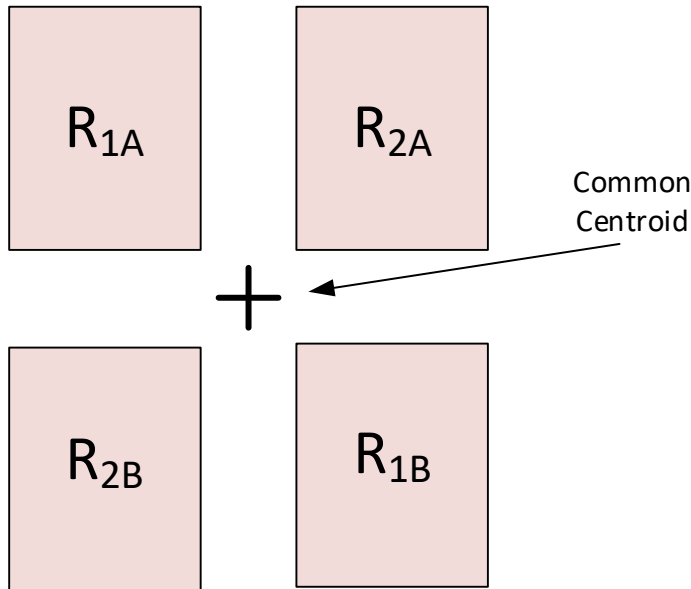
## Measurement of $A_R$

$$\sigma_{\frac{\Delta R}{R_N}} = \sqrt{2} \sigma_{\frac{R}{R_N}}$$

$$A_R = \sqrt{A} \bullet \sigma_{\frac{R}{R_N}}$$



- Create 2 resistors,  $R_1$  and  $R_2$ , using common centroid layouts

$$R_1 = R_{1A} // R_{1B} \quad R_2 = R_{2A} // R_{2B}$$

$A$  = area of one resistor

Define rv  $\frac{\Delta R_{1:2}}{R_N}$

- Create a large number of these test structures and distribute across a die or wafer. Sample standard deviation is

$$\sigma_{\frac{\Delta R}{R_N}} \text{ SAMPLE}$$

- calculate variance of these samples










$$\hat{A}_R = \sqrt{A} \bullet \sigma_{\frac{R}{R_N}} \text{ SAMPLE} = \sqrt{A} \bullet \frac{1}{\sqrt{2}} \sigma_{\frac{\Delta R}{R_N}} \text{ SAMPLE}$$

## Strategy 3
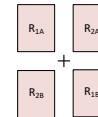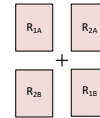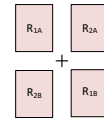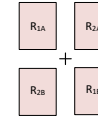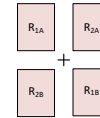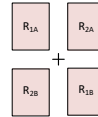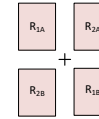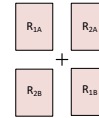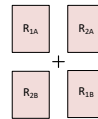
# Measurement of $A_R$

Large number of test structures across die, wafer, wafers, or process runs

$$\hat{A}_R = \sqrt{A} \cdot \frac{1}{\sqrt{2}} \sigma_{\frac{\Delta R}{R_N}} \text{ SAMPLE}$$



Will gradients skew the normalization by  $R_N$ ?

No, effects will be minor

Assumption is made that  $A_R$  is not dependent upon gradients or even run-to-run variations









Designs must be robust to mismatch effects anyway so even small errors in  $A_R$  should not compromise design

## Strategy 3
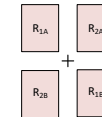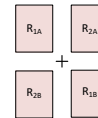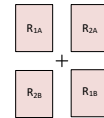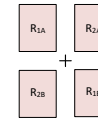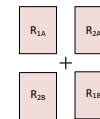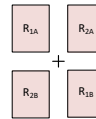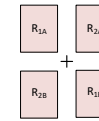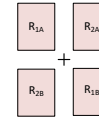
# Measurement of $A_R$

Large number of test structures across die, wafer, wafers, or process runs

$$\hat{A}_R = \sqrt{A} \cdot \frac{1}{\sqrt{2}} \sigma_{\frac{\Delta R}{R_N}} \text{SAMPLE}$$




Is this a good strategy for obtaining  $A_R$ ?

## Strategy 4
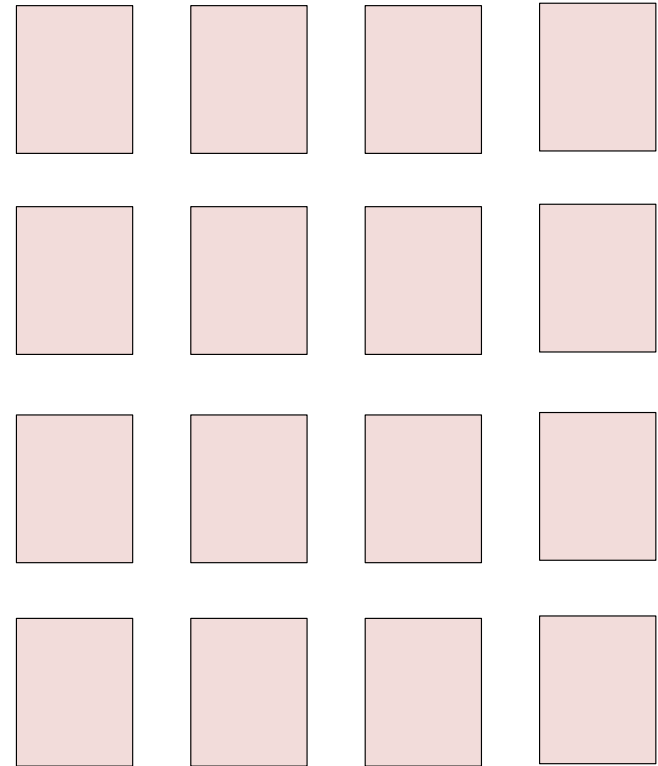
## Measurement of $A_R$

What about just taking a large number of resistors at multiple sites on a die, at multiple die locations on a wafer, and on many wafers and wafer lots:



$$\left. \begin{aligned} \hat{\sigma}_{\frac{R}{R_N}} &= \sigma_{\frac{R}{R_N} \text{ SAMPLE}} \\ \sigma_{\frac{R}{R_N}} &= \frac{A_R}{\sqrt{A}} \end{aligned} \right\} \hat{A}_R = \sqrt{A} \sigma_{\frac{R}{R_N} \text{ SAMPLE}}$$



Is this a good strategy for obtaining  $A_R$ ?

No! Highly dependent upon process variations, wafer variations, and gradients

## Strategy 6
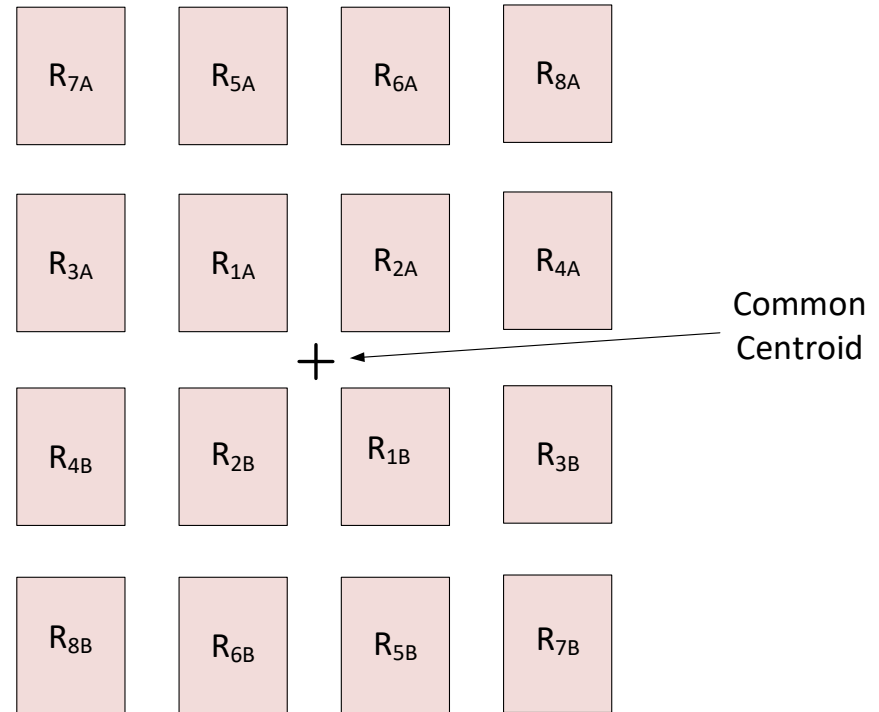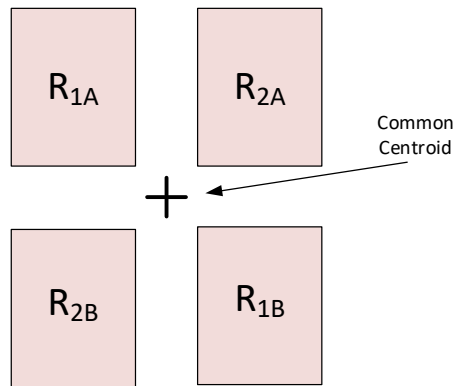
## Measurement of $A_R$


What about having arrays of common centroid test structures and taking pair-wise differences?



Is this a good strategy for obtaining  $A_R$ ?

Yes! Get more useful information per unit area than with single pair structures

# Measurement of $A_R$

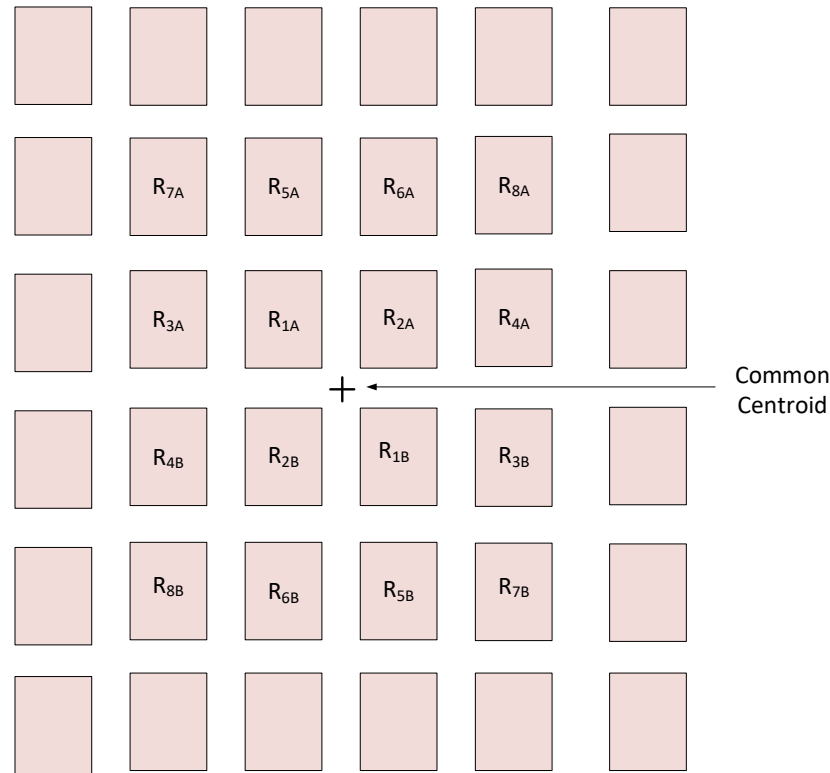

Regardless of which approach is followed, may need to have dummy devices that are nominally the same as the test devices surround test array

Sometimes two (or more) rings of dummy devices are used



# Ratio Matching Effects in Data Converters

- Ratio matching is often critical in ADCs and DACs
- Accuracy and matching of gains is also critical in some data converters

Example: If a ratio of 10:1 is desired, determine the ratio matching accuracy relative to the standard deviation of a single resistor


---

Consider

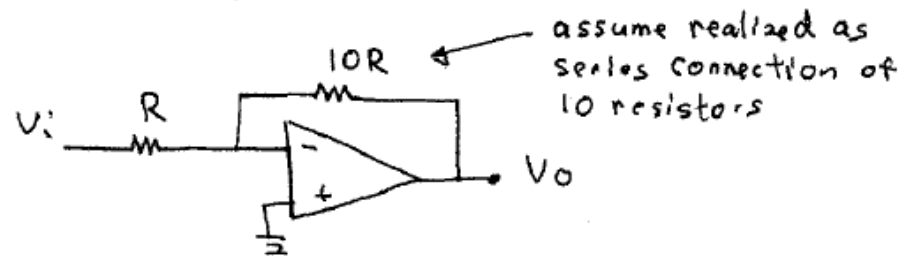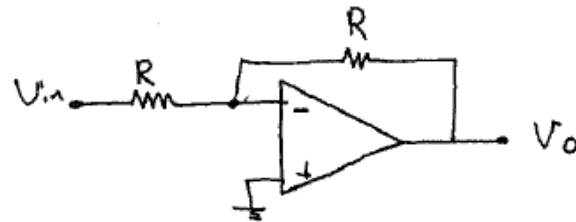

Question: what is the "yield" of these two amplifiers and how do they compare if a given gain accuracy requirement is specified?



# Amplifier Gain Accuracy

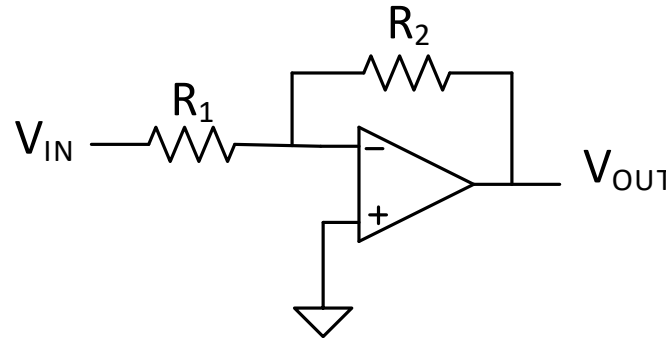

$$A_{CL} = -\frac{R_2}{R_1}$$

Does the ratio matching accuracy (A) depend upon the magnitude of the gain:

Consider:

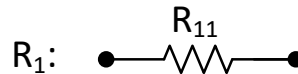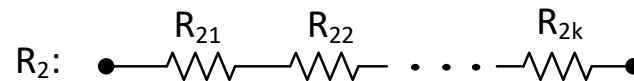

Assume ideally  $R_{21}=R_{22}=\dots=R_{2k}=R_{11}$  and the areas of the resistors are also ideally the same. Define  $A_{CL0}$  to be the nominal gain.

$$A_{CL0} = -\frac{R_{2NOM}}{R_{1NOM}} = k$$

Define  $\theta$  to be the gain error

# Amplifier Yield

Assume the closed-loop gain  $A_{CL}$  is a Gaussian RV with mean  $A_{CL0}$  and standard deviation  $\sigma_{ACL}$  where  $A_{CL0}$  is the nominal gain.

Assume yield is defined by amplifiers with a gain that satisfies the expression

$$A_{CL0}(1 - \theta_X) < A_{CL} < A_{CL0}(1 + \theta_X)$$

$$Y = P\{A_{CL0}(1 - \theta_X) < A_{CL} < A_{CL0}(1 + \theta_X)\}$$

$$Y = \int_{x=A_{CL0}(1-\theta_X)}^{x=A_{CL0}(1+\theta_X)} f_{ACL}(x) dx$$

$$Y = \int_{z=\frac{A_{CL0}(1-\theta_X)-A_{CL0}}{\sigma_{ACL}}}^{z=\frac{A_{CL0}(1+\theta_X)-A_{CL0}}{\sigma_{ACL}}} f_{N(0,1)}(z) dz$$

$$Y = \int_{z=\frac{-\theta_X A_{CL0}}{\sigma_{ACL}}}^{z=\frac{\theta_X A_{CL0}}{\sigma_{ACL}}} f_{N(0,1)}(z) dz$$

# Amplifier Yield

Assume the closed-loop gain  $A_{CL}$  is a Gaussian RV with mean  $A_{CL0}$  and standard deviation  $\sigma_{ACL}$  where  $A_{CL0}$  is the nominal gain

Assume yield is defined by amplifiers with a gain that satisfies the expression

$$A_{CL0} (1 - \theta_X) < A_{CL} < A_{CL0} (1 + \theta_X)$$

$$Y = \int_{z = \frac{-\theta_X A_{CL0}}{\sigma_{ACL}}}^{z = \frac{\theta_X A_{CL0}}{\sigma_{ACL}}} f_{N(0,1)}(z) dz$$

$$Y = 2F_{N(0,1)}\left(\frac{\theta_X A_{CL0}}{\sigma_{ACL}}\right) - 1$$

$$Y = 2F_{N(0,1)}\left(\frac{\theta_X}{\frac{\sigma_{ACL}}{A_{CL0}}}\right) - 1$$


Thus to obtain yield need to obtain  $\sigma_{ACL}$  or  $\frac{\sigma_{ACL}}{A_{CL0}}$

# Amplifier Gain Accuracy

Gain error  $\theta = A_{CL0} - A_{CL}$

It follows that  $\sigma_{\theta} = \sigma_{ACL}$

Thus need to obtain  $\sigma_{\theta}$

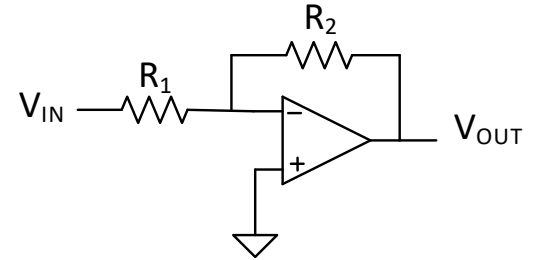

$$\theta = \frac{R_2}{R_1} \bigg|_{NOM} - \frac{R_2}{R_1} \bigg|_{ACT}$$

$$\theta = k - \frac{\sum_{i=1}^k R_{2i}}{R_{11}}$$

$$R_{2i} = R_0 + R_{R2i}$$

$$R_{11} = R_0 + R_{R1}$$

$$\theta = k - \frac{kR_0 + \sum_{i=1}^k R_{R2i}}{R_0 \left( 1 + \frac{R_{R11}}{R_0} \right)}$$

$$\theta = k - \frac{k + \sum_{i=1}^k \frac{R_{R2i}}{R_0}}{\left( 1 + \frac{R_{R11}}{R_0} \right)}$$

$$\theta = k - \left[ k + \sum_{i=1}^k \frac{R_{R2i}}{R_0} \right] \left( 1 - \frac{R_{R11}}{R_0} \right)$$

$$\theta = k \frac{R_{R11}}{R_0} - \sum_{i=1}^k \frac{R_{R2i}}{R_0}$$

# Amplifier Gain Accuracy


$$\theta = k \frac{R_{R11}}{R_0} - \sum_{i=1}^k \frac{R_{R2i}}{R_0}$$

$$\sigma_{\theta}^2 = k^2 \sigma_{\frac{R_{R11}}{R_0}}^2 + \sum_{i=1}^k \sigma_{\frac{R_{R2i}}{R_0}}^2$$

$$\sigma_{\theta}^2 = k^2 \sigma_{\frac{R_{R11}}{R_0}}^2 + k \sigma_{\frac{R_{R2i}}{R_0}}^2$$

$$\sigma_{\theta}^2 = (k^2 + k) \sigma_{\frac{R_{Ri}}{R_0}}^2$$
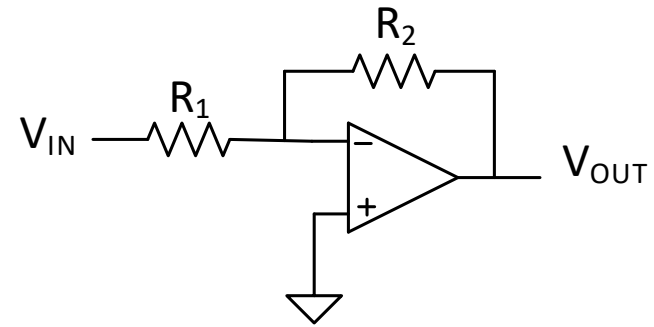
$$\sigma_{\theta} = \sigma_{\frac{R_{Ri}}{R_0}} \sqrt{k^2 + k}$$





If  $k=1$        $\sigma_{\theta} = \sigma_{\frac{R_{Ri}}{R_0}} \sqrt{2}$

If  $k=10$        $\sigma_{\theta} = \sigma_{\frac{R_{Ri}}{R_0}} \sqrt{101} \cong 10.5 \sigma_{\frac{R_{Ri}}{R_0}}$

Recall:  $\sigma_{\frac{R}{R_N}}^2 = \frac{A_R^2}{WL} = \frac{A_R^2}{A} \quad \Rightarrow \quad Y = 2F_{N(0.1)} \left( \frac{\theta_X A_{CL0}}{\sigma_{ACL}} \right) - 1$

# Amplifier Gain Accuracy


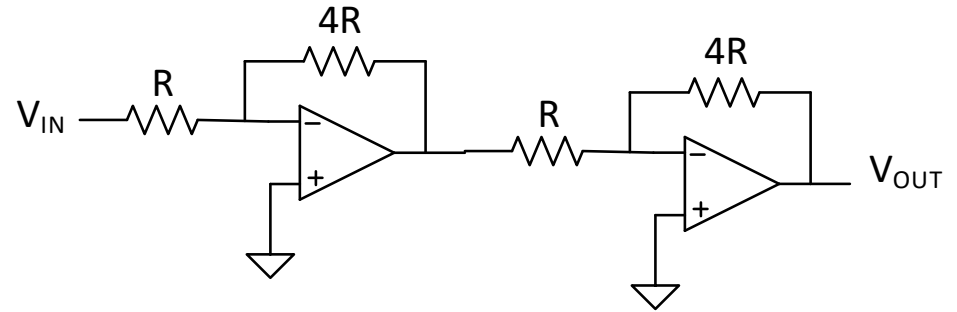
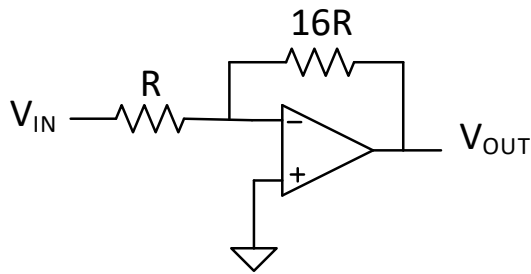


Which will have the lowest  $\sigma$ ?

Note:  $R_{TOT} = \begin{cases} 17R \text{ for Option 1} \\ 10R \text{ for Option 2} \end{cases}$
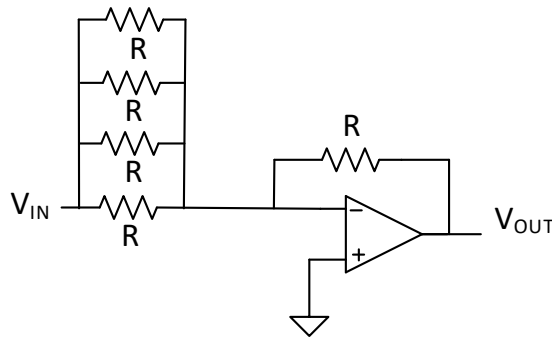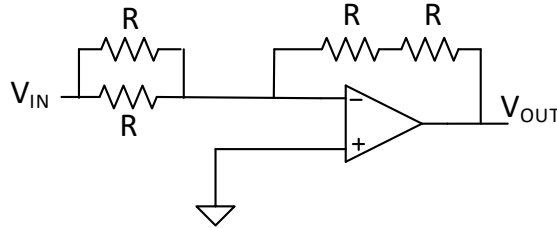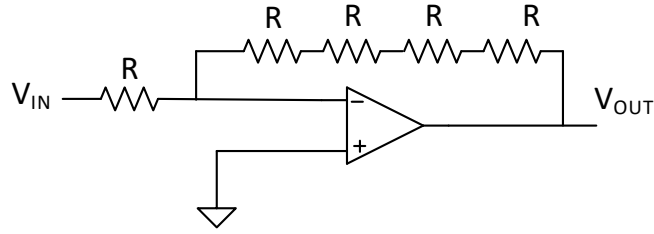
# Amplifier Gain Accuracy

Many different ways to achieve a given gain with a given resistor area



Which will have the best yield?



Stay Safe and Stay Healthy !

End of Lecture 9