

EE 505

Lecture 12

DAC Design

- DAC Architectures
- String DACs

Review from last lecture

Random Offset Voltages

Typical offset voltages:

MOS - 5mV to 50mV

BJT - 0.5mV to 5mV

These can be scaled with extreme device dimensions

Often more practical to include offset-compensation circuitry

Summary of Offset Voltage Issues

- Random offset voltage is generally dominant and due to mismatch in device and model parameters
- MOS Devices have large V_{OS} if area is small
- σ decreases approximately with $1/\sqrt{A}$
- Multiple fingers for MOS devices offer benefits for common centroid layouts but too many fingers will ultimately degrade offset because perimeter/area ration will increase (A_W and A_L will become of concern)
- Offset voltage of dynamic comparators is often large and analysis not straightforward
- Offset compensation often used when low offsets important

MOS:

$$\sigma_{V_{OS}}^2 \cong 2 \left[\frac{A_{VTO_n}^2}{W_n L_n} + \frac{\mu_p}{\mu_n} \frac{L_n}{W_n L_p^2} A_{VTO_p}^2 \right]$$

Bipolar:

$$\sigma_{V_{OS}}^2 \cong 2V_t^2 \left[\frac{A_{Jn}^2}{A_{En}} + \frac{A_{Jp}^2}{A_{Ep}} \right]$$

DAC Architectures

Types (Nyquist Rate)

- Voltage Scaling
 - Resistor String DACs (string DACs)
 - Interpolating
- Current Steering
 - Binary Weighted Resistors
 - R-2R Ladders
 - Current Source Steering
 - Thermometer Coded
 - Binary Weighted
 - Segmented
- Charge Redistribution
 - Switched Capacitor
- Serial
 - Algorithmic
 - Cyclic or Re-circulating
 - Pipelined
- Integrating
- Resistor Switching
- MDACs (multiplying DACs)

Observations

- Yield Loss is the major penalty for not appropriately managing parasitics and matching and this loss can be ruthless
- The ultimate performance limit of essentially all DACs is the yield loss associated with parasitics and matching
- Many designers do not have or use good statistical models that accurately predict data converter performance
- If you work of a company that does not have good statistical device models
 - Convince model groups of the importance of developing these models
 - (or) develop appropriate test structures to characterize your process
- Existing nonlinear device models may not sufficiently accurately predict device nonlinearities for high-end data converter applications

DAC Architectures

Structures

- Hybrid or Segmented
- Mode of Operation
 - Current Mode
 - Voltage Mode
 - Charge Mode
- Self-Calibrating
 - Analog Calibration
 - Foreground
 - Background
 - Digital Calibration
 - Foreground
 - Background
 - Dynamic Element Matching
- Laser or Link Trimmed
- Thermometer Coded or Binary
- Radix 2 or non-radix 2
- Inherently Monotone

DAC Architectures

- Type of Classification may not be unique nor mutually exclusive
- Structure is not mutually exclusive
- All approaches listed are used (and probably some others as well)
- Some are much more popular than others
 - Popular Architectures
 - Resistor String (interpolating)
 - Current Source Steering (with segmentation)
 - Charge Redistribution
- Many new architectures are possible and some may be much better than the best currently available
- All have perfect performance if parasitic and matching performance are ignored !
- Major challenge is in determining appropriate architecture and managing the parasitics

Nonideal Effects of Concern

- Matching
- Parasitic Capacitances
(including Charge injection)
- Loading
- Nonlinearities
- Interconnect resistors
- Noise
- Speed
- Jitter
- Temperature Effects
- Aging
- Package stress


Observations

- Experienced Designers/Companies often produce superior data converter products
- Essentially all companies have access to the same literature, regularly reverse engineer successful competitors products and key benefits in successful competitors products are generally not locked up in patents
- High-end designs(speed and resolution) may get attention in the peer community but practical moderate performance converters usually make the cash flow
- Area (from a silicon cost viewpoint) is usually not the driving factor in high-end designs where attractive price/mfg cost ratios are common
- Considerable ongoing demand for data converter designers – particularly in ASICs where DAC optimized for specific application

DAC Architectures




R-String

 

X_{IN} is decoded to close one switch

DAC Architectures

R-String

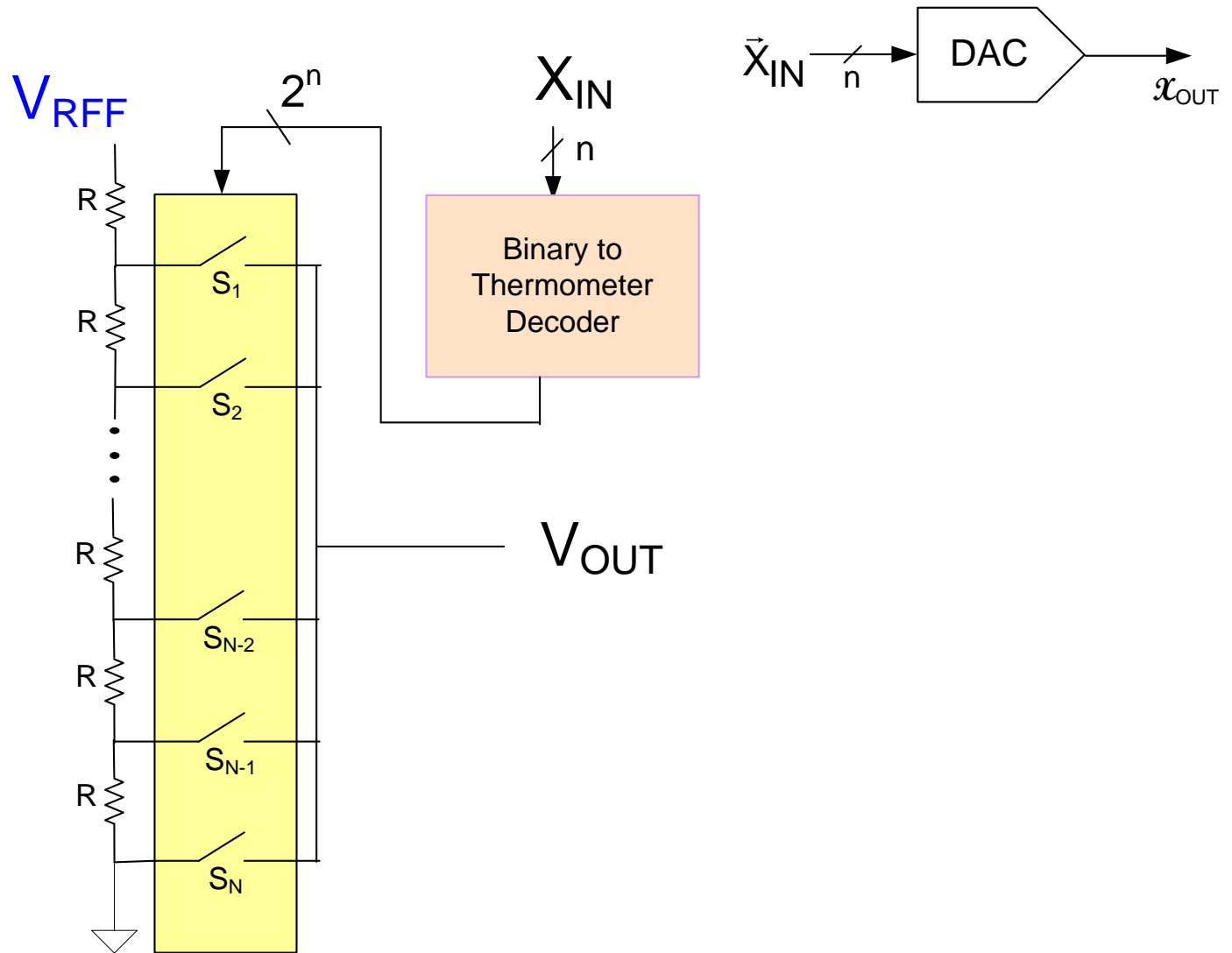


Basic R-String DAC including Logic to Control Switches

DAC Architectures




Current Steering

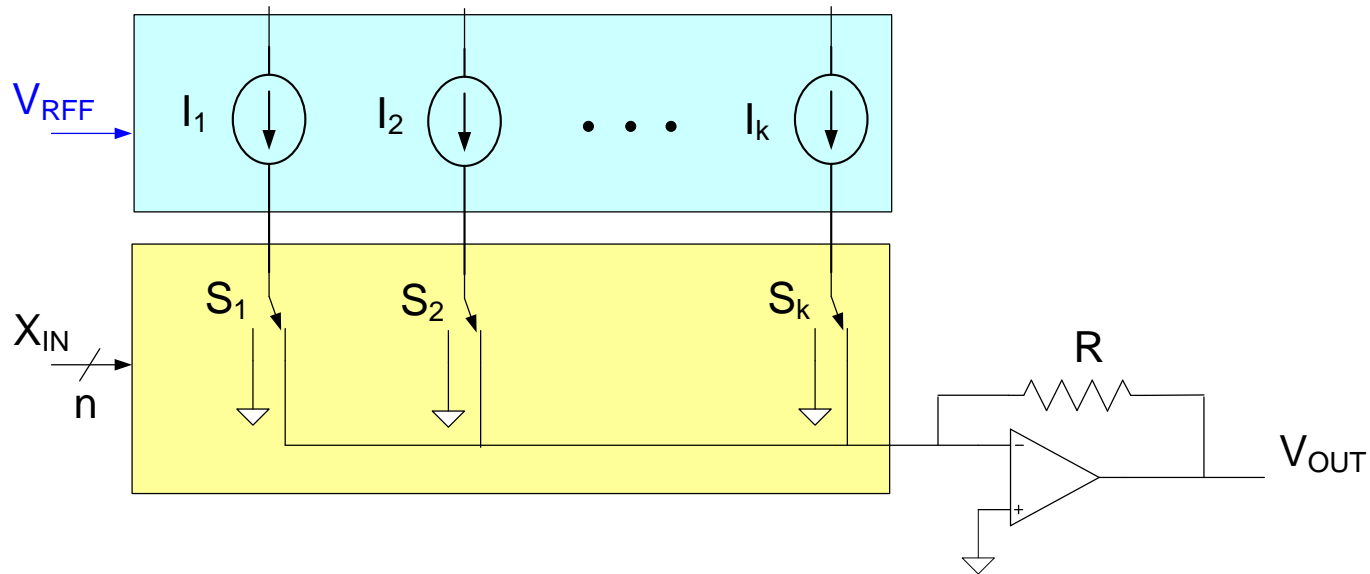


DAC Architectures

Current Steering

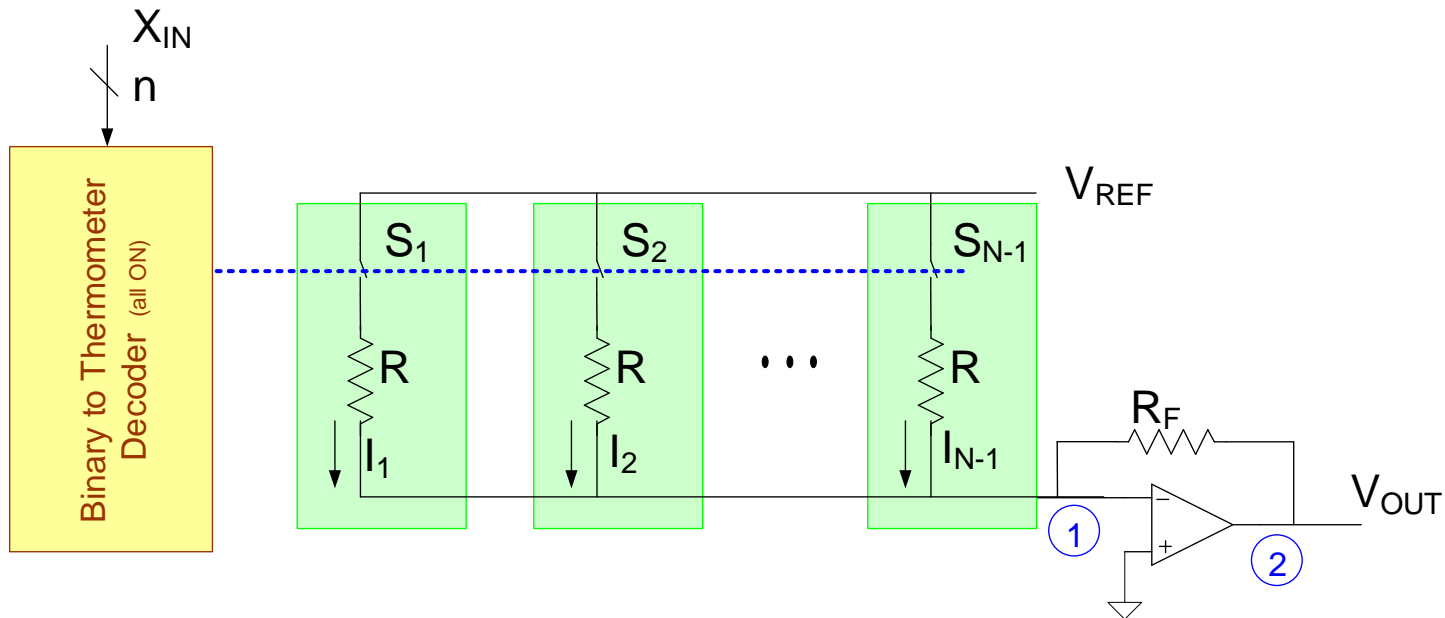

Inherently Insensitive to Nonlinearities in Switches and Resistors

 
- Termed “top plate switching”
- Thermometer coded
- Based upon unary cell
- Speed limited by Op Amp and clock transients



Unary bit cell


DAC Architectures

Current Steering

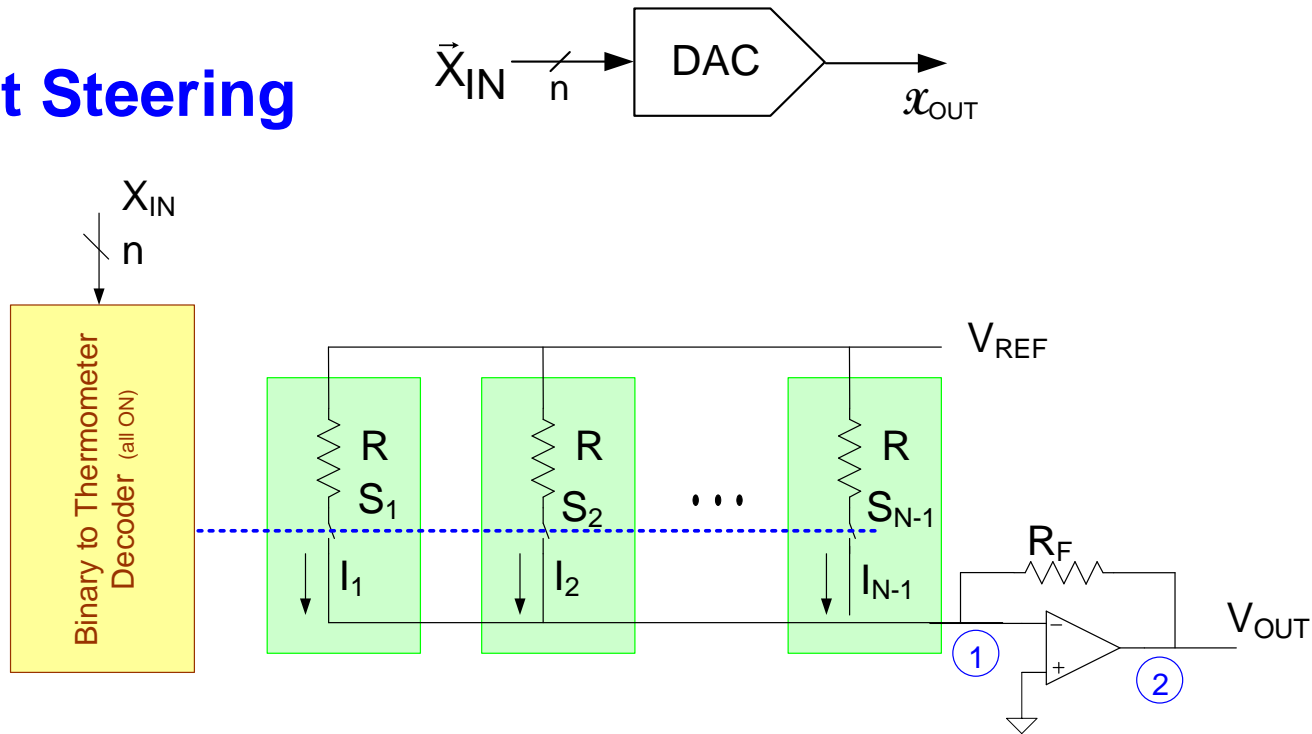


Inherently Insensitive to Nonlinearities in Switches and Resistors
Smaller ON resistance and less phase-shift from clock edges

 - Termed “bottom plate switching”
- Thermometer coded
- Based upon unary cell
- Speed limited by Op Amp



DAC Architectures

Current Steering

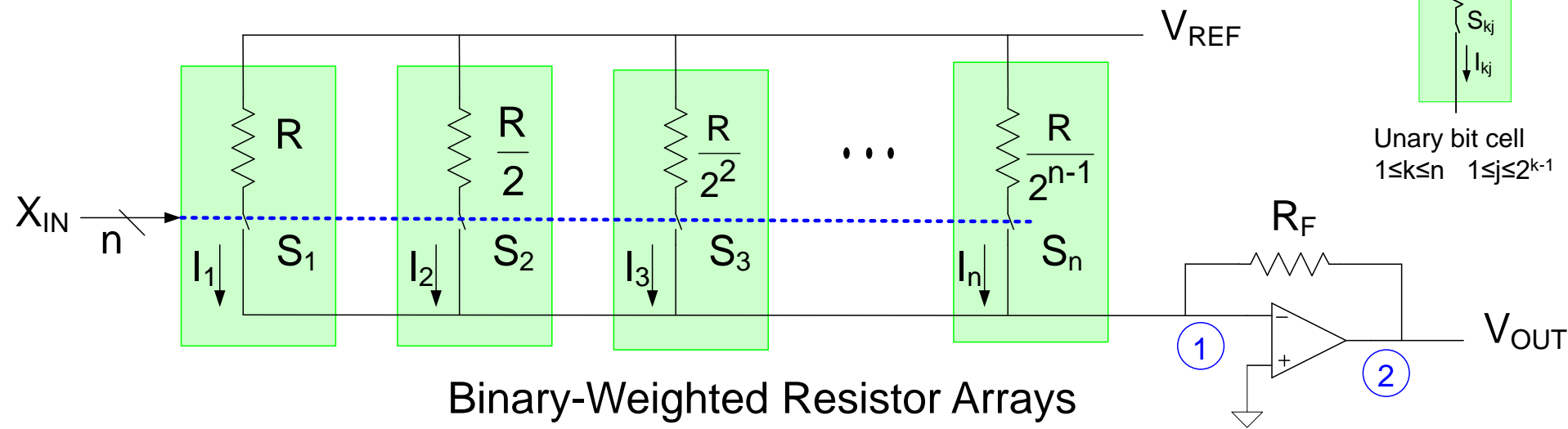

Binary-Weighted Resistor Arrays


- Unary bit cells usually bundled to make resistors
- Same number of unary cells needed as for thermometer coded structure
- Need for decoder eliminated !
- DNL may be a major problem
- INL performance about same as thermometer coded if same unit resistors used
- Sizing and layout of switches is critical

Observe thermometer coding and binary weighted both offer some major advantages and some major limitations

DAC Architectures



R-2R (one variant) (4-bits shown)

 

By superposition:


$$V_{OUT} = V_{REF} d_3 \cdot \frac{1}{2} + V_{REF} d_2 \cdot \frac{1}{4} + V_{REF} d_1 \cdot \frac{1}{8} + V_{REF} d_0 \cdot \frac{1}{16} = V_{REF} \sum_{k=0}^3 \frac{d_k}{2^{4-k}} = V_{REF} \sum_{k=1}^4 \frac{d_{4-k}}{2^k}$$

DAC Architectures

Current Steering



R-2R (another variant)


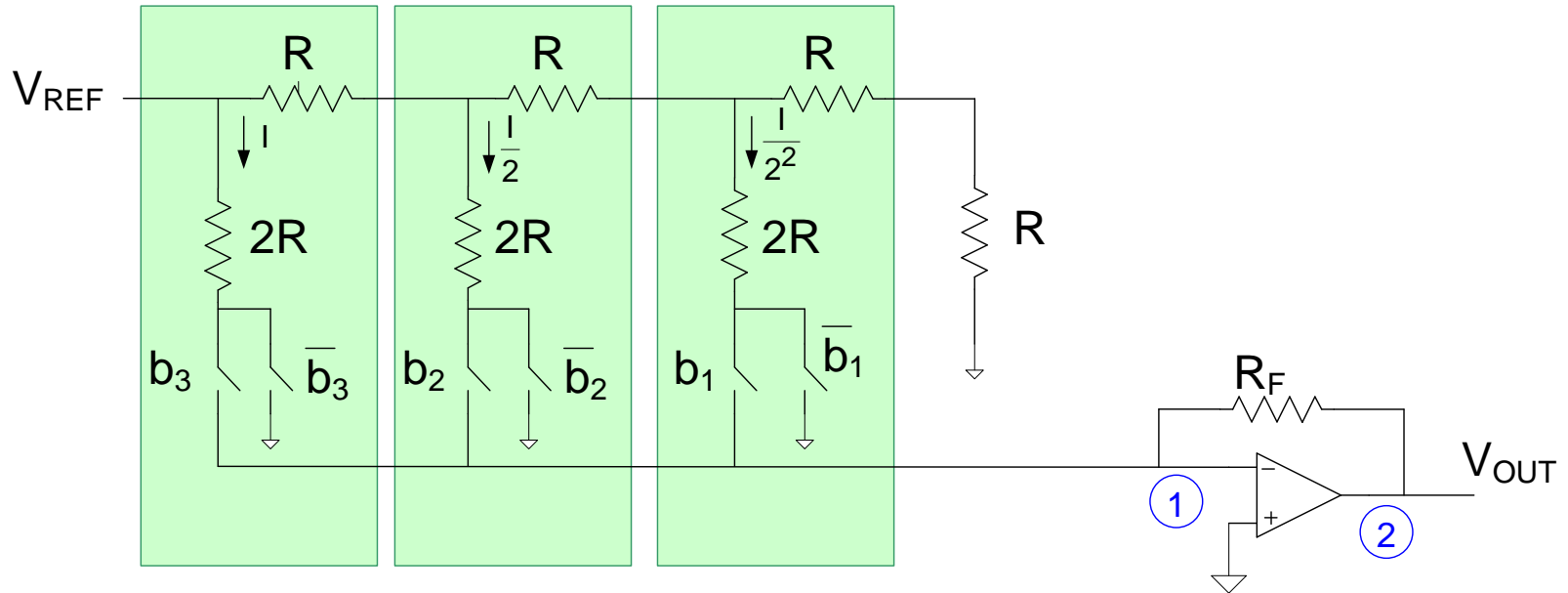


R-2R Resistor Arrays

DAC Architectures



Charge Redistribution

 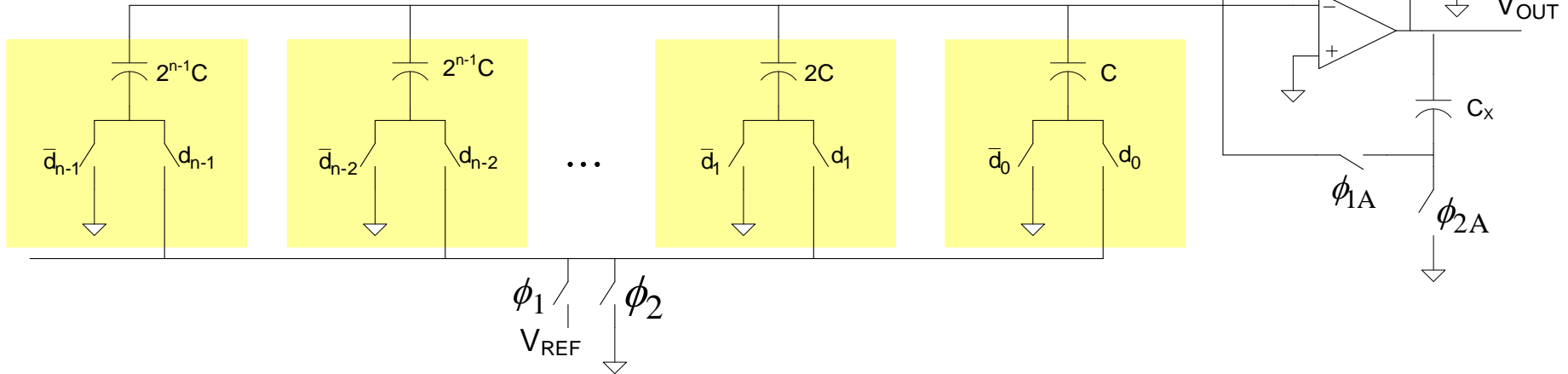


Unary cell used for capacitor array

C_x does some good things
(mitigates V_{OS} , $1/f$ noise and finite gain errors)

Will not consider C_x affects at this time

DAC Architectures

Charge Redistribution

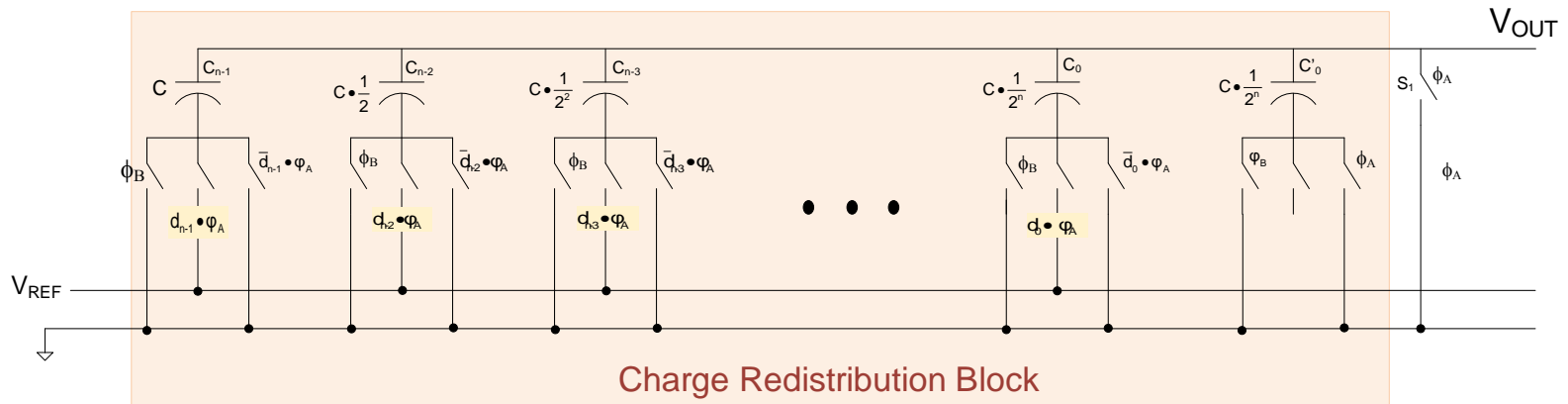


$$Q_{SET} = V_{REF} \sum_{i=0}^{n-1} d_i \frac{C}{2^{n-i}}$$

$$Q_{DIS} = V_{OUT} \left(\sum_{i=0}^{n-1} C_i + [C'_0] \right) = V_{OUT} \left(\sum_{i=0}^{n-1} \frac{C}{2^{n-i}} + \left[\frac{C}{2^n} \right] \right) = V_{OUT} C$$

$$Q_{SET} = Q_{DIS}$$


$$V_{REF} \sum_{i=0}^{n-1} d_i \frac{C}{2^{n-i}} = V_{OUT} C$$
 
$$V_{OUT} = V_{REF} \sum_{i=0}^{n-1} \frac{d_i}{2^{n-i}}$$




DAC Architectures

MDAC

 

V_{REF} fixed or limited range
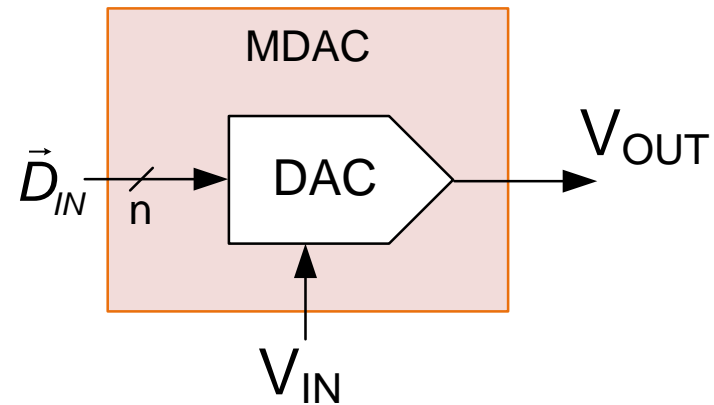
$$V_{OUT} = V_{REF} \cdot [\vec{D}_{IN}]_{DECIMAL}$$








V_{IN} Variable, often positive or negative

$$V_{OUT} = V_{IN} \cdot [\vec{D}_{IN}]_{DECIMAL}$$

- Some define MDACs to be DAC structures that have current outputs
- Many DAC structures can perform well as a MDAC (possibly one quadrant)
- Performance of some DAC structures limited if V_{REF} is varied

DAC Architectures


Suitable as MDAC?

  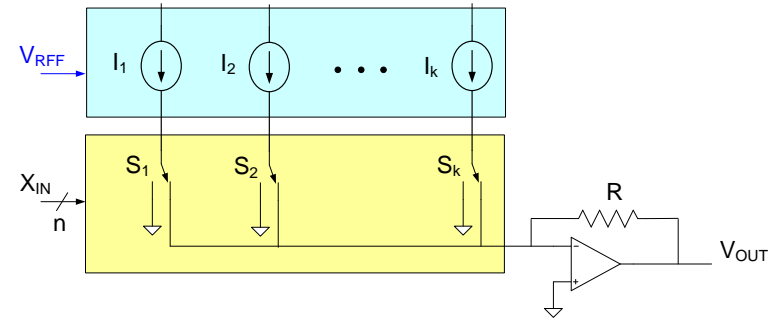 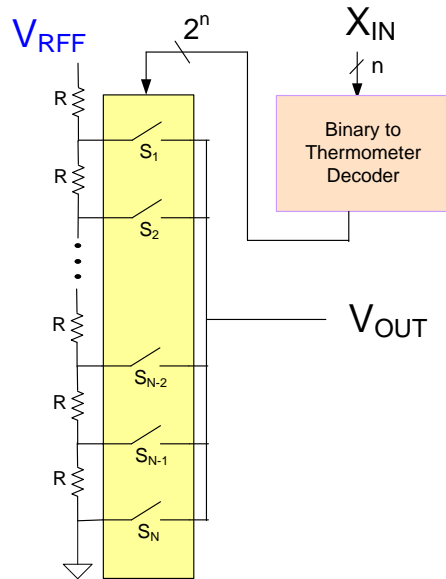

DAC Architectures



Single Slope

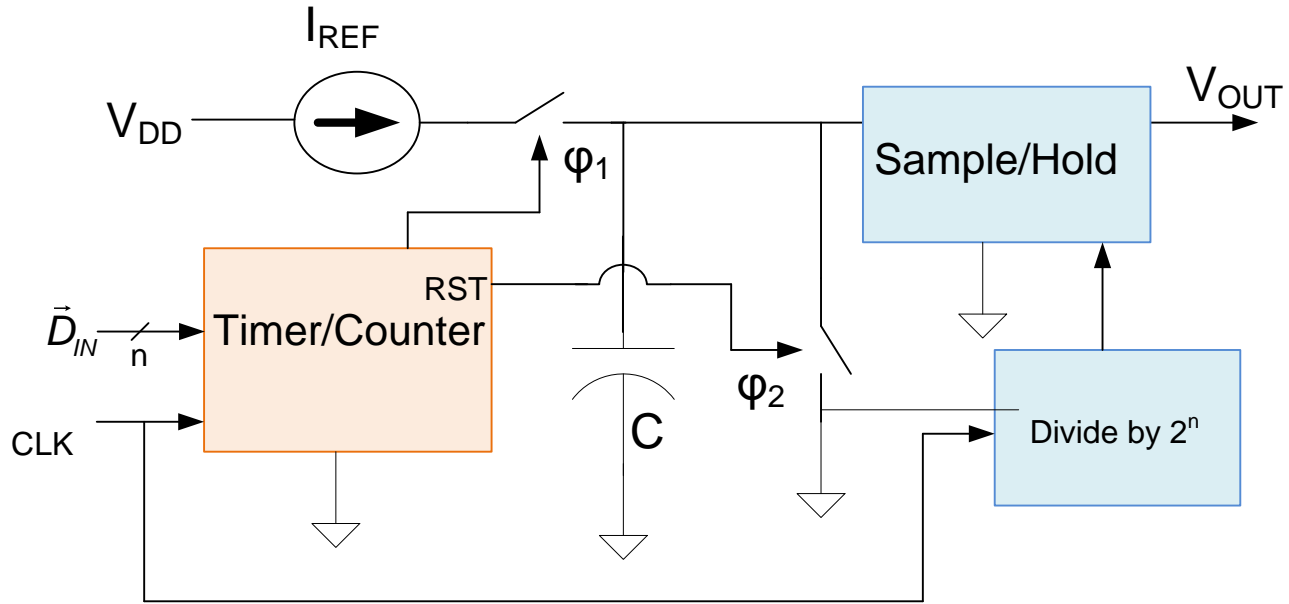


Single-Slope DAC


DAC Architectures



Dual Slope

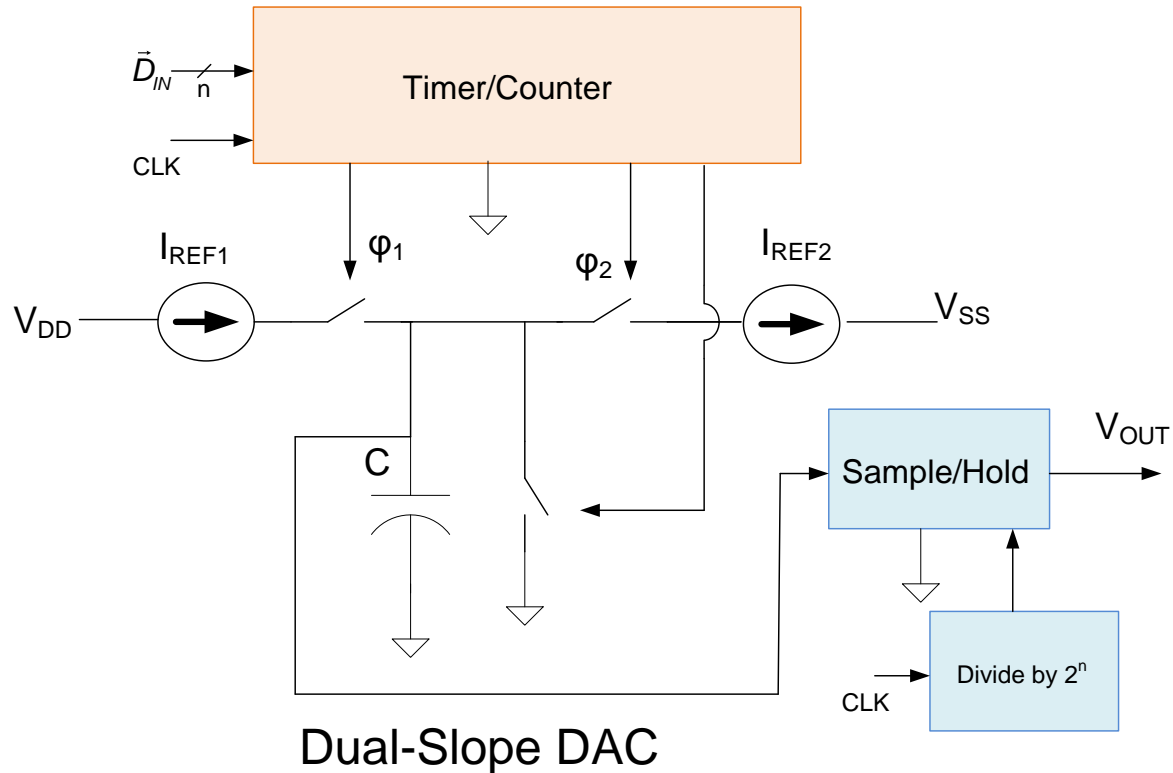

R-String DAC

 



- ❑ Simple structure
- ❑ Inherently monotone
- ❑ Very low DNL
- ❑ Potential for being very fast
- ❑ Low Power Dissipation
- ❑ Widely Used Approach (with appropriate considerations)

Challenges:

- Managing INL
- Large number of devices for n large (2^n or 2^{n+1} lines)
- Decoder
- Routing thermometer/bubble clocks
- Transients during Boolean transitions
- Switch implementation
- Thevenin impedance facing V_{OUT} highly code dependent

Conceptual

R-String DAC

  

Practical level shift

Switch Implementation


Basic Switch




- Large number required for large resolution
- Simple structure often used



 - Good when switch terminals near gnd
- Will not turn on when terminals near V_{DD}



 
- Good when switch terminals near V_{DD}
- Will not turn on when terminals near gnd



- Use devices where cross-over occurs
- Good for both high and low term voltages
- Extra clock signal required
- Try to avoid this complexity





Other switch structures (such as bootstrapped switch) used but not for basic string DACs

Switch Assignment




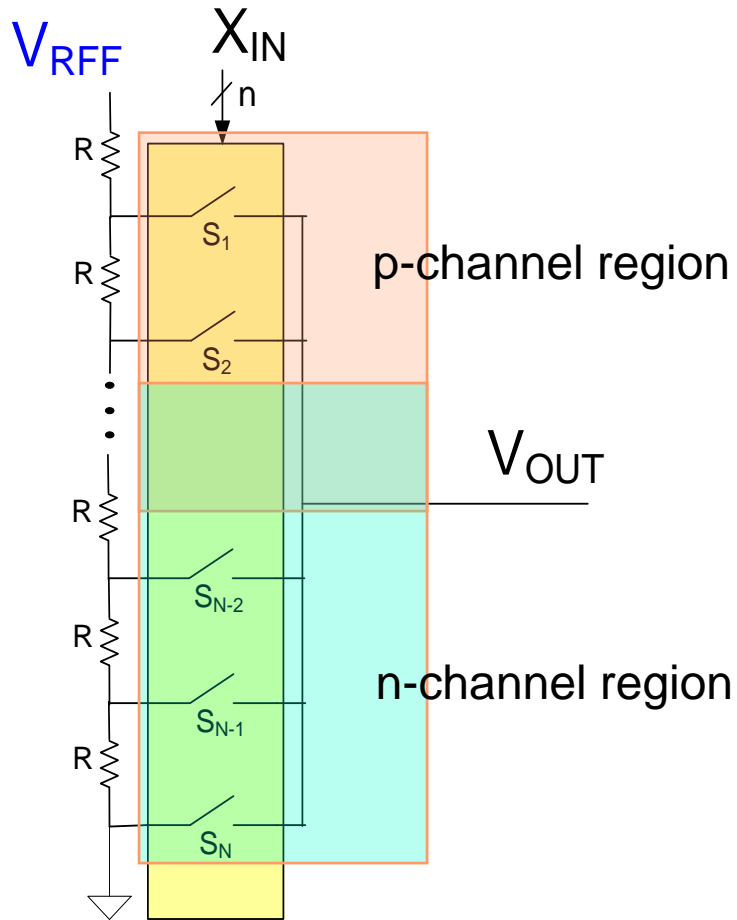


Challenges:

Switch Impedances

 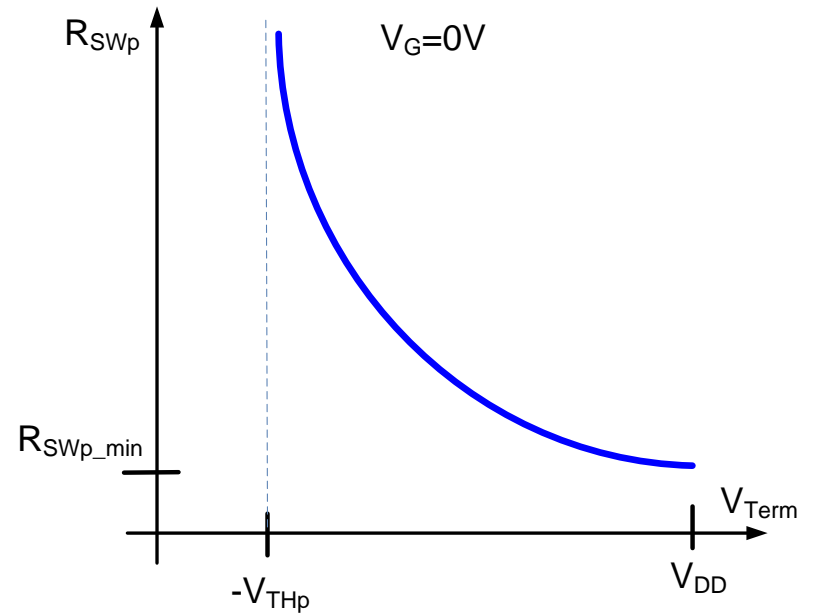  


Switch Impedances

 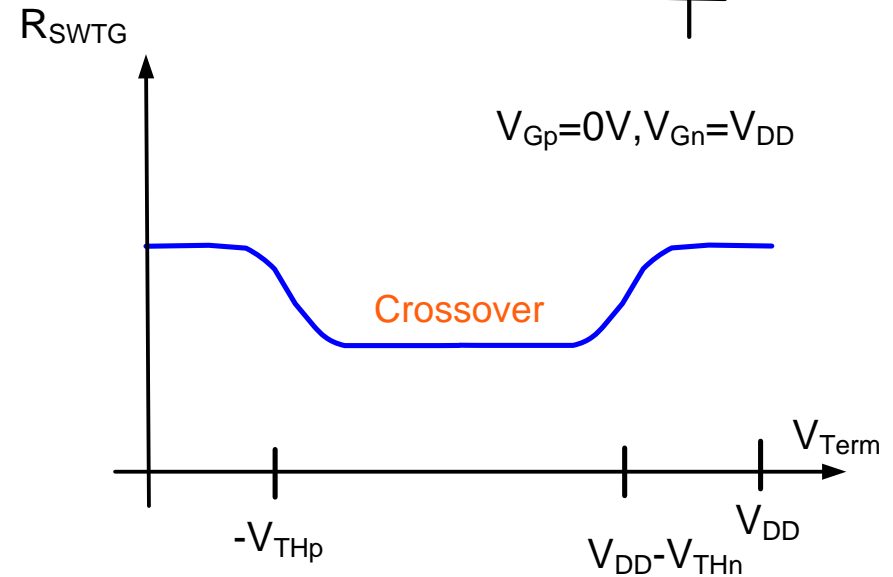  


Switch impedance significantly both position and device size dependent

Switch Parasitics

 

- C_{BD} and C_{BS} can be significant and cause rise-fall times to be position dependent
- C_{GDOL} can cause “kickback” or feed-forward
- C_{GS} can slow turn-on and turn-off time of switch


R-String DAC

 

Additional Challenges:

- Capacitance on V_{OUT} can be large
 - larger for p-channel devices
 - even larger for TG switches
- Switch impedances position dependent
- Kickback from switches to R-string
- Capacitance on each node (though small) of R-string from switch
- Thevenin impedance facing V_{OUT} highly code dependent


R-String DAC

 

Additional Challenges


- Delay in Decoder may be significant
- Delay in Decoder may be previous code and current code dependent
- Intermediate undesired Boolean outputs may occur
 - These may cause undesired opening and closing of switches
 - Could momentarily short out taps on R-string
 - Could introduce transients on all nodes of R-string that are code and previous code dependent

R-String DAC

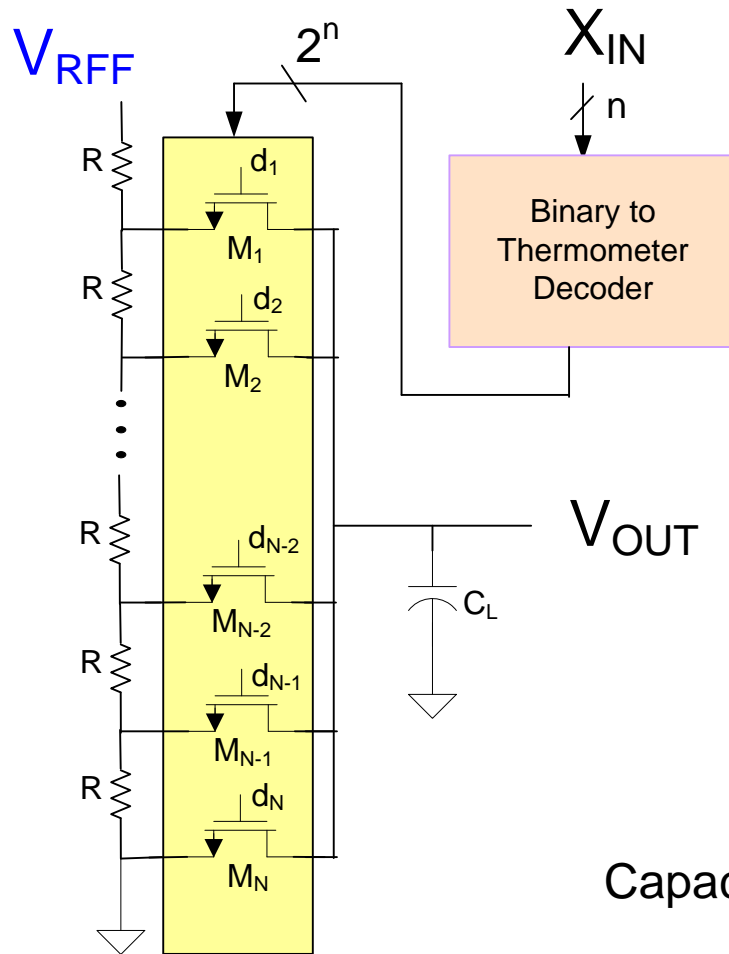

Capacitive loading due to switches

R-String DAC

 


- Uses matrix decoder as analog MUX
- Implements binary to decimal conversion with pass transistor analog logic
- Very structured layout
- Interconnection points are switches (combination of n-channel and p-channel)

Challenges


- Still many signals to route
- Large capacitance on V_{OUT} (over 2^{n+1} diff caps)
- Multiple previous code dependencies cause output transition time to be quite unpredictable
- Considerable transients introduced on R-string

R-String DAC

 

Parasitic Capacitances in Tree Decoder

R-String DAC

 


Previous-Code Dependent Settling

Assume all C's initially with 0V

Red denotes V_3 , black denotes 0V, Purple some other voltage

R-String DAC

 Transition from $\langle 010 \rangle$ to $\langle 101 \rangle$



Previous-Code Dependent Settling


Assume all C's initially with $0V$

Red denotes V_3 , green denotes V_6 , black denotes $0V$, Purple some other v

R-String DAC

Transition from $\langle 010 \rangle$ to $\langle 101 \rangle$

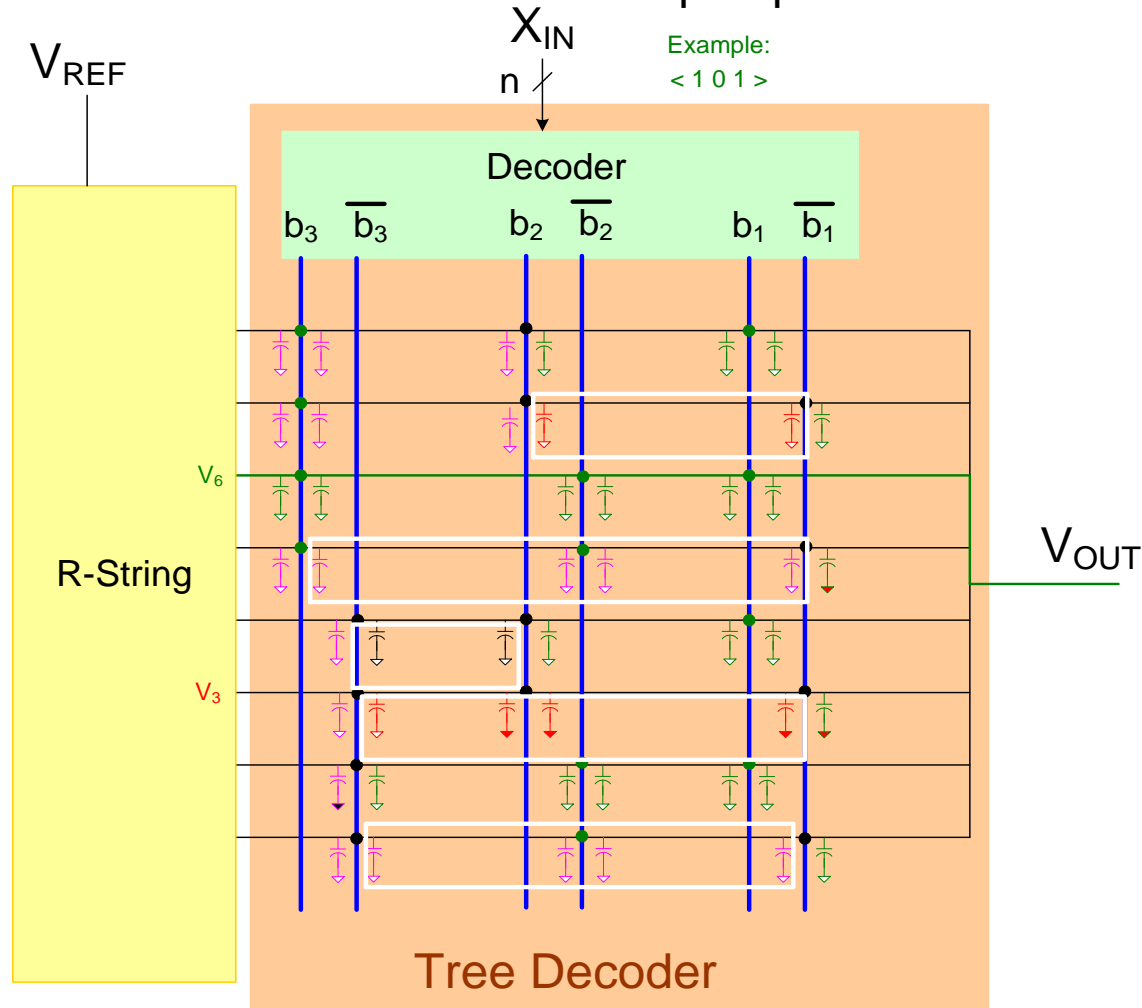White boxes show capacitors dependent upon previous code $\langle 010 \rangle$



Previous-Code Dependent Settling

Assume all C's initially with 0V

Red denotes V_3 , green denotes V_6 , black denotes 0V, Purple some other voltage

End of Lecture 12